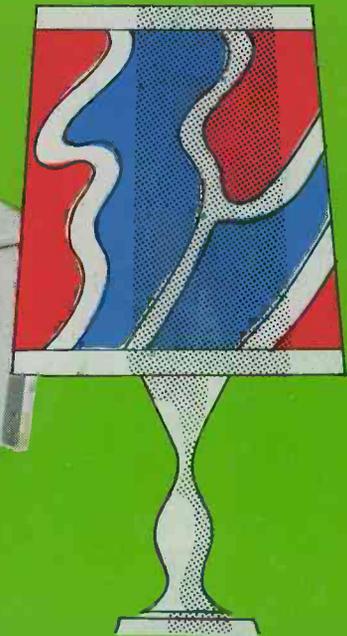


RADIO & ELECTRONICS CONSTRUCTOR


JUNE 1981

60p

FUMBLE-FREE ILLUMINATION




PROXIMITY ACTIVATED LIGHT SWITCH

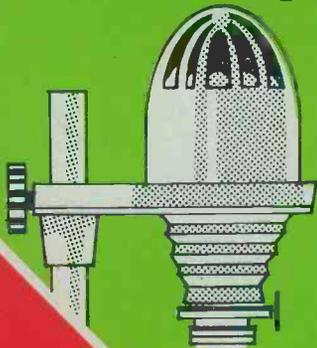

**ENLARGER
PROCESS
TIMER**

**BAMBOOZLE
BUZBY**

WITH A TELEPHONE
CHARGE REMINDER

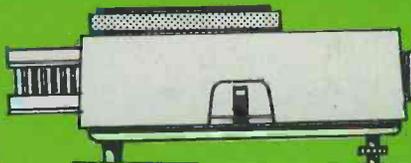

SLIDE PROJECTOR PULSER

PLUS

*** ELECTRONICS DATA
MILLER EFFECT**

**CB - THE UK SYSTEMS
SPECIFICATIONS
- AT LAST?**

READER SURVEY:
WHAT DO YOU WANT FROM
ELECTRONICS MAGAZINES
READER'S OFFERS:
REC ENTERS THE MARKET
WITH SOME
IRRESISTIBLE
GOODIES

RADIO & ELECTRONICS CONSTRUCTOR

JUNE 1981
Volume 34 No. 10

Published Monthly

First published in 1947

Incorporating The Radio
Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone
01-286 6141

Telegrams
Databux, London

©Data Publications Ltd., 1981. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £9.50, Eire and Overseas £10.50 (U.S.A. and Canada \$30.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production – Web Offset.

NEWS AND COMMENT	588
SLEEPY TIME RADIO SWITCH – Suggested Circuit by G. A. French	590
IN NEXT MONTH'S ISSUE	593
SCHMITT OSCILLATOR by R. J. Caborn	594
ENLARGER/PROCESS TIMER – Easy to use, gives accurate repeatable timings by Peter Roberts	596
NEW PRODUCTS – For the computer enthusiast	601
PROXIMITY LAMP SWITCH – No fumbling in the dark for manual switches, proximity of hand turns lamp on by R. A. Penfold	602
CB CB CB CB	607
MILLER EFFECT Electronics Data No. 70	611
TELEPHONE CHARGE REMINDER by I. M. Attrill	612
PROBLEMS WITH T.V. GAIN CONTROL Too much contrast? – In Your Workshop	617
SLIDE PROJECTOR PULSER Controls an automatic slide projector to give programmable intervals between slides by C. J. Bowes	624
SHORT WAVE NEWS – For DX Listeners by Frank A. Baldwin	628
AMATEUR SATELLITE NEWS REPORT by Arthur C. Gee	630
TRADE NEWS	632

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by LSG Printers, Portland Street, Lincoln.

OUR NEXT ISSUE
WILL BE PUBLISHED
15th JUNE

C.B.P.A.

MICROPHONES,

Hand held with thumb switch & Curly Lead, Type 1 600Ω dynamic at £4.25.

Type 2 600Ω, noise cancelling type at £7.25

Type 3 Power type, with volume control 1KΩ Imp, £7.95

SÉMICONDUCTORS

LM340 80p. BY103 10p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. MC4741CP 50p. 741 22p. 741S 35p. 723 35p. NE555 24p. 2N3773 £1.70. NE556 50p. ZN414 75p. BD238 28p. BD438 28p. CB4069 15p. 4" Red Led Displays, c.c. or c.a. 95p. TIL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p. BY223 20p.

PROJECT BOXES

Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

MOTOROLA PIEZO CERAMIC TWEETERS

No crossover required



2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65

TOOL SALE

Small side cutters 5" insulated handles £1. Radiopliers, snipe nosed insulated handles £1. Heavy duty pliers insulated handles £1.10. Draper side cutters spring loaded £1.

HANDY BENCH VICE

1" Jaw opening, £2.95.



Hand drill, double pinion with machine cut gears, 9/16", only £2.75p plus 50p p&p.

MORSE KEYS

Beginners practice key £1.05. All metal full adjustable type. £2.60

F.M. MICROPHONE, Electret condenser type, tuneable 85-95Mhz. Arrival distance 50 mtrs. (Approx outdoors) Size 163 x 35 mm £10.25. (Not licensable in U.K.).

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

TRANSFORMERS

All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA. Volts 100mA, 12-0-12V 50mA all 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 24 volt 2 Amp £2.45 (54p).

T.V. AERIAL AMPLIFIERS

Wide Band, 240 VAC operated, with two outlets, £7.75

MICROPHONES

Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95, ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. F.M. WIRELESS MICROPHONE, 88-108 MHz, Electret type £10.25. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromed copper body, £12.95. CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. GRUNDIG electric inserts with FET pre amp, 3-6VDC operation £1.00.

LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50

C.B. 40 CHANNEL RECEIVER

For car use, operates on 12v DC., £7.95

SPECIAL OFFER TAPE HEAD DEMAGNETIZER



240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p

MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50




20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £975.

40kHz Transducers. Rec/Sender £3.50 pair.

TELEPHONE PICK UP COIL

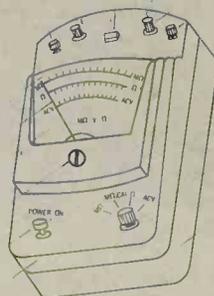Sucker type with lead and 3.5mm plug 62p.



500v electronic megger, push button operation. Ranges:- LO ohm Range 0 - 100Ω (MW scale 5Ω) - 100MΩ Mid scale 5MHΩ) £46.75p

Stabilized power supplies, 240V A.C. input output 13.8 volts at 3/5 amps D.C. £14.75p

TERMS:

Cash with order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.

S.A.E. for illustrated lists

MULTI-TESTER



KRT5001 50k/v range doubler multimeter, 0-1kv (125mv LO range) 0-1kv AC. 0-10amp DC. 0-20MΩ res. (LO ohm 0-2k range) 170 x 124 x 50mm £15.50.

YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts, 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

CRIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

SWITCHED TYPE PLUGS into 13 amp socket, 3-6-9 volts DC out at 300mA, £2.95. STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.

BUZZERS

MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, voltage operating 4-15VDC, 75p each. LOUD 12VDC BUZZER, with metal case. 50mm diam. x 30mm high 63p. Carters 12 volt Minimize Alarm sirens £7.65p. 12VDC siren, all metal rotary type, high pitched wall, £6.25.

TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

All Antex irons still at pre increase prices, order now as new stock will be going up next month.

Antex Model C 15 watt soldering irons, 240VAC £4.45

Antex Model CX 17 watt soldering irons, 240VAC £4.45

Antex Model X25 25 watt soldering irons, 240VAC £4.45

ANTEX ST3 iron stands, suits all above models £1.65

Antex heat shunts 12p each.

Servisol Solder Mop 50p

Neon Tester Screwdrivers 8" long 59p each.

Miyarna IC test clips 16 pin £1.95

SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p.

DPDT (8 x 7 x 7mm) 55p.

DPDT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

TEI Mobile SWR metre, with field strength, PL259 connection, £8.35.

RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz. R.F., output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95 BSR MN1330 1 track 50p. BSR SRP90 1 track £1.95. TD10 tape head assembly - 2 heads both 1 track R/P with built in erase, mounted on bracket £1.20

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.

ALL ORDERS DESPATCHED BY RETURN POST

THE MODERN BOOK CO

WORLD RADIO T.V. HANDBOOK 1981 EDITION £10.50p

REPAIRING POCKET TRANSISTOR RADIOS

by I. R. Sinclair Price £2.55

TEST GEAR PROJECTS by T. Dixon Price £4.50

ELECTRONICS - BUILD & LEARN by R. A. Penfold Price £3.20

AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR by I. R. Sinclair Price £3.00

BEGINNER'S GUIDE TO INTEGRATED CIRCUITS by I. R. Sinclair Price £3.50

BEGINNER'S GUIDE TO RADIO by G. J. King Price £3.50

ELECTRONIC PROJECTS IN THE WORKSHOP by R. A. Penfold Price £2.75

110 ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston Price £4.35

UNDERSTANDING MICROPROCESSORS by Texas Ins Price £4.00

AMATEUR RADIO OPERATING MANUAL by R. J. Eckersley Price £4.70

THE OSCILLOSCOPE IN USE

by I. R. Sinclair Price £3.50

PROJECTS FOR THE CAR & GARAGE by G. Bishop Price £4.00

SIMPLE CIRCUIT BUILDING by P. C. Graham Price £2.75

UNDERSTANDING HI FI SPECIFICATIONS by John Earl Price £3.40

BEGINNER'S GUIDE TO DIGITAL ELECTRONICS by I. R. Sinclair Price £3.50

ELECTRONICS POCKET BOOK by P. J. McGoldrick Price £5.00

PROJECTS IN RADIO & ELECTRONICS by I. R. Sinclair Price £2.50

UNDERSTANDING CALCULATOR MATH by Texas Ins Price £4.00

UNDERSTANDING SOLID STATE ELECTRONICS by Texas Ins Price £4.00

AMATEUR RADIO TECHNIQUES by P. Hawker Price £3.70

COST EFFECTIVE PROJECTS AROUND THE HOME by J. Watson Price 4.50

AUDIO CIRCUITS & PROJECTS

by G. Bishop Price £5.35

PRINTED CIRCUIT ASSEMBLY by M. J. Hughes Price: £2.75

MICROPHONES IN ACTION by V. Capel Price £5.00

BEGINNER'S GUIDE TO COLOUR TELEVISION by G. J. King Price £3.50

HOW TO BUILD ELECTRONIC KITS by V. Capel Price £2.50

ELECTRONIC GAME PROJECTS by F. G. Rayer Price £2.75

UNDERSTANDING DIGITAL ELECTRONICS by Texas Ins. Price £4.00

HOW TO BUILD SPEAKER ENCLOSURES by A. Badmaieff Price £3.50

BEGINNER'S GUIDE TO HAM RADIO by L. Buckwalter Price £3.50

We have the Finest Selection of English and American Radio Books in the Country
ALL PRICES INCLUDE POSTAGE

19-21 PRAED STREET (Dept RC) LONDON W2 1NP


Telephone: 01-402 9176

LINEAR ICs		LINEAR ICs		LINEAR ICs		4000 series		4000 series		TTL 'N'		'LPSN'		TTL 'N'		'LPSN'		TTL 'N'		'LPSN'		MICROMARKET		LEDS		LEDS	
TBA120S	1.00	SL1610P	1.60	HA11223	2.15	4000	0.18	4068	0.25	TTL 'N'	'LPSN'	8224	3.50	STD DOMED TYPE													
L200	1.90	SL1611P	1.60	HA11225	1.45	4001	0.18	4068	0.25	7400	0.13	0.20	7454	0.20	0.30	74128	0.74	7419	1.05	7419	1.05	8221	6.25	5mm RED	12p		
U237B	1.28	SL1612P	1.60	HA12002	1.45	4002	0.24	4070	0.30	7401	0.13	0.20	7455	0.30	0.30	74129	0.73	7419	1.05	7419	1.05	8255	5.40	3mm RED	15p		
U247B	1.28	SL1613P	1.89	HA12017	0.80	4007	0.30	4071	0.24	7402	0.14	0.20	7460	0.20	0.20	74130	0.74	7419	1.10	7419	1.10	8800P	7.50	3mm RED	15p		
U257B	1.28	SL1620P	2.17	HA12402	1.95	4008	0.80	4072	0.24	7403	0.14	0.20	7463		1.24	74131	0.72	7419	1.60	7419	1.60	6820	7.45	5mm GRN	15p		
U267B	1.28	SL1621P	2.17	HA12411	1.20	4008AE	0.80	4073	0.24	7404	0.14	0.24	7470	0.40		74141	0.75	7419	1.60	7419	1.60	6850	4.90	3mm GRN	15p		
LM301H	0.67	SL1623P	2.44	HA12412	1.55	4009	0.58	4075	0.25	7405	0.18	0.26	7472	0.30		74142	2.85	74247	0.93	74247	0.93	6852	4.85	3mm GRN	15p		
LM301N	0.30	SL1624C	3.28	LF13741	0.33	4010	0.58	4076	0.90	7406	0.36		7473	0.35	0.45	74143	3.12	74257	1.08	74257	1.08	6850	4.90	5mm GRN	15p		
LM308TC	0.65	SL1625P	2.17	SN76660N	0.80	4011AE	0.24	4077	0.35	7407	0.38		7474	0.35	0.35	74144	3.12	74260	0.89	74260	0.89	MC2708	6.00	3mm YL	15p		
LM324	0.64	SL1626P	2.44			4011B	0.24	4078	0.30	7408	0.19	0.24	7475	0.56		74145	2.85	74279	0.88	74279	0.88	6850	4.85	3mm GRN	15p		
LM338N	0.66	SL1627P	1.82	FREQ. DISPLAY AND SYNTH. DEVICES		4012	0.55	4082	0.28	7409	0.21	0.24	7476	0.41	0.45	74146	1.75	74283	1.20	74283	1.20	2114	6.50	5mm YL	15p		
LM348N	1.80	SL1640P	1.89			4013	0.55	4093	0.86	7410	0.18	0.24	7478	0.41	0.50	74148	1.09	74293	1.32	74293	1.32	4027	5.78	3mm YL	15p		
LF351N	0.49	SL1641P	1.89			4015	0.95	4175	1.15	7411	0.26	0.32	7480	0.52		74150	0.99	74365	0.66	74365	0.66	2112	3.40	2.5x5 YL	20p		
LF353N	0.76	TD2002	1.25	AAA1056	3.75	4016	0.52	4503	1.15	7412	0.27		7481	1.20		74151	0.55	74366	0.60	74366	0.60	HM4716	7.54	5mm ORA	20p		
LM374N	3.78	ULN2242A	3.05	AAA1058	3.35	4017	0.80	4506	0.88	7413	0.32		7482	0.75		74153	0.70	74367	0.64	74367	0.64	81LS97	1.25	2.5x5 ORA	24p		
LM380N-14	1.00	ULN2283B	1.00	AAA1059	3.35	4019	0.60	4510	0.99	7414	0.51		7485	1.04	0.99	74154	1.30	74368	0.92	74368	0.92						
LM380N-18	1.00	CA3080E	0.70	IC9000C	4.00	4020	0.98	4511	1.49	7415		0.40	7486		0.99	74155	0.75	74374	1.80	74374	1.80						
LM381N	1.81	CA3089E	1.84	LN1232	19.00	4021	0.82	4512	0.98	7416	0.30		7489	2.05		74156	0.80	74377	1.99	74377	1.99						
ZNA19CE	1.98	CA3090E	3.35	LN1242	19.00	4022	0.96	4514	2.55	7417	0.30		7490	2.02	0.90	74157	0.78	74379	2.15	74379	2.15						
NE544N	1.60	CA3123E	1.40	MSL2318	3.84	4023	0.25	4518	1.03	7420	0.19	0.24	7491	0.85	1.25	74158		74380	1.40	74380	1.40						
NE555N	0.30	CA3130E	0.80	MSM5523	11.30	4024	0.76	4520	1.09	7421	0.38	0.24	7492	0.57	0.99	74159	2.10	74381	1.40	74381	1.40						
NE556	0.50	CA3130T	0.90	MSM5524	11.30	4025	0.25	4521	2.36	7423	0.27		7493	0.57	0.99	74160	0.99	74382	1.40	74382	1.40						
NE560N	3.50	CA3140E	0.46	MSM5525	7.85	4026	1.80	4522	1.49	7425	0.27		7494	0.85		74161	0.99	74383	1.40	74383	1.40						
NE562N	4.05	CA3189E	2.20	MSM5526	7.85	4028	0.79	4529	1.61	7427	0.19	0.35	7495	0.70	1.15	74162	1.30	74384	1.40	74384	1.40						
NE564N	4.20	CA3240	1.27	MSM5527	9.75	4029	1.04	4539	1.28	7428	0.35	0.35	7496	0.58	1.20	74163	0.99	74385	1.40	74385	1.40						
NE565N	1.00	MC3357P	2.85	MSM55271	9.75	4030	0.59	4549	3.50	7430	0.17	0.26	7497	1.85		74164	1.20	74386	1.40	74386	1.40						
NE566N	1.60	LM3900N	0.60	MSL2312	3.94	4035	1.20	4554	1.73	7432	0.32	0.28	74107			74165	1.20	74387	1.40	74387	1.40						
NE570N	3.85	M3909N	0.68	SP9629	3.85	4040	0.98	4560	2.18	7437	0.40		74109	0.63		74167	2.50	74388	1.40	74388	1.40						
SL624	3.28	LM3914N	2.80	SP8647	6.00	4042	0.85	4566	1.59	7438	0.33	0.35	74110	0.68		74168		74389	1.40	74389	1.40						
TBA651	1.81	LM3915N	2.80	95H90PC	7.80	4043	0.85	4568	2.18	7440	0.20	0.28	74111	0.68		74170	2.30	74390	1.40	74390	1.40						
uA709HC	0.64	KB4400	0.80	HD10551	2.45	4043AE	0.93	4569	3.03	7441	0.74		74112	0.41		74174	1.05	74391	1.40	74391	1.40						
uA709PC	0.46	KB4406	0.80	HD44015	4.55	4044	0.94	4572	0.30	7442	0.70	0.99	74113	0.41		74175	0.87	74392	1.40	74392	1.40						
uA710HC	0.65	KB4412	1.95	HD12009	6.00	4046	0.85	4585	1.00	7443	1.15		74114	0.40		74176	0.80	74393	1.40	74393	1.40						
uA710PC	0.59	KB4413	1.95	HD44752	8.00	4047	0.99			7444	1.12		74115	0.85		74177	0.84	74394	1.40	74394	1.40						
uA711HC	0.66	KB4417	1.80	MC145151	12.45	4048	0.52			7445	1.05		74120	1.15		74181	2.80	74395	1.40	74395	1.40						
uA711PC	0.66	KB4417	1.80	MC145156	8.75	4050	0.55			7446	1.32		74121	0.48		74182	3.00	74396	1.40	74396	1.40						
uA714CN	0.27	KB4420B	1.09			4051	0.55			7447	0.56	0.99	74122	0.46		74184	1.35	74397	1.40	74397	1.40						
uA747CN	0.70	TD4420	2.65			4052	0.78			7448	0.52	0.99	74123	0.73		74185	1.34	74398	1.40	74398	1.40						
uA748CN	0.36	KB4423	1.30	MISC		4053	0.78			7449		0.99	74124	1.80		74186	1.40	74399	1.40	74399	1.40						

RX 80 MkII - A DIY SOLID-STATE-OF-THE-ART MODULAR DUAL CONVERSION RECEIVER SYSTEM FOR THE ENTHUSIAST

• AS DESCRIBED IN JAN/FEB/MAR 81 RADCOM BY TONY BAILEY-G3WPO : REPRINTS £1 inc

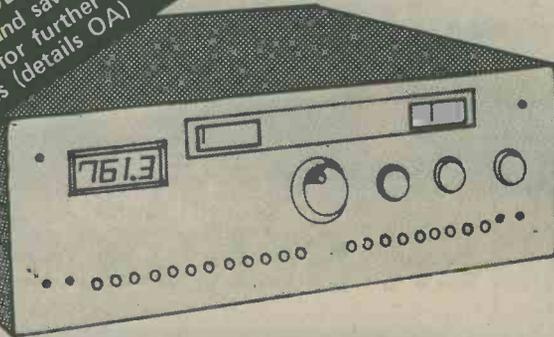CLUBS & COLLEGES:
Buy 5 kits and save 10%
Buy more for further reductions (details OA)



- ★ LOW DRIFT VARICAP TUNING (READILY ADAPTABLE FOR SYNTHESISED/ HUFF&PUFF STABILIZATION)
- ★ DUAL CONVERSION BASED ON A 3.4 MHz SSB IF, WITH MECHANICAL IF FILTER, AUDIO DERIVED AGC, BALANCED MIXER, WITH ON-BOARD AF AMP AND VOLTAGE REGULATOR
- ★ CAPACITY FOR UP TO 12HF/VHF/UHF 1 MHz WIDE CRYSTAL CONTROLLED CONVERTERS WITH TRACKED RF TUNING
- ★ EACH CONVERTER SELF CONTAINED - SO MORE CAN BE USED EXTERNALLY IF REQUIRED. RF PATHS ARE DC SWITCHED AT LOW IMPEDANCE

PRICES

RX 80 Mk II tuneable 3.4MHz SSB receiver/IF with MFL series	..£42.66
2.4kHz mechanical SSB IF filter	..£32.42
A/A but with low cost 4kHz CFM2 series filter	..£9.10 ea
HF Converters, including crystal for the following bands:	..£25.00
1-2MHz, 7-8MHz, 10-11MHz, 14-15MHz, 18-19MHz, 21-22MHz	..£132.50
24-25MHz, 28-29MHz, 29-30MHz	
Hardware: Case, meters, pots, knobs (exc. DFM)	
Complete RX 80, 6 converters, switches, case, PSU	

CURRENT OPTIONS INCLUDE

- ★ LCD DFM with built in IF offset, interface PCB ..£23.75
- ★ HUFF/PUFF vfo stabilizer ..£9.60
- ★ NBFM adapter inc 8kHz multielement ceramic IF filter ..£9.95
- ★ Constant Z PIN diode attenuator ..£4.95
- ★ 12v low RF noise mains PSU ..£7.95

PLANNED ADDITIONS TO THE SYSTEM

- 3.4MHz IF frequency synthesiser
- 'UP Conversion' front end system
- AM IF adapter
- Noise blanker
- VHF/UHF converters with helical filters



PRICES EXCLUDE VAT (15%). Postage 50p on orders under £12. Free postage on orders over £12, except please note any order including HARDWARE should be accompanied with a £2 carriage charge. General price lists are available FOC with an SAE - full AMBIT catalogues including a multitude of radio parts/components £1.80 a set - or 70p per section.

AMBIT international 200 North Service Road, Brentwood, Essex
TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

T & J ELECTRONIC COMPONENTS

METAL BOXES

Two piece design consisting of a "U" shaped base and cover. Finished in black stelvite.

WB1 6 x 4 x 1 1/2"	165p
WB2 8 x 5 x 2"	215p
WB3 9 x 5 x 2 1/2"	230p
WB6 4 1/2 x 2 1/2 x 2 1/2"	130p

PLAIN ALUMINIUM (With lid)

AB7 5 1/2 x 2 1/2 x 1 1/2"	90p
AB8 4 x 4 x 1 1/2"	90p
AB9 4 x 2 1/2 x 1 1/2"	90p
AB10 5 1/2 x 4 x 1 1/2"	105p
AB12 3 x 2 x 1"	72p

PLASTIC BOXES

PB1 4 1/2 x 3 x 1 1/2 white	70p
O25L 2 1/2 x 1 1/2 x 1" (Vero) white	50p

Many other boxes in catalogue.

MISCELLANEOUS

P.C.B. Transfers (13 sheets)	300p
Insulated crocodile clip	9p
Telephone pick up coil	75p
2.5" x 1", 0.1" Verobaard	16p
Small cable ties	2p
PP3 battery connectors	14p
F.M. ribbon dipole aerial	45p
Spirawrap 1" diameter (per metre)	16p
Spirawrap 1/8" diameter (per metre)	13p
Grommets 3/8" bore	1p
Grommets 1/2" bore	1.5p
3.5mm jack plug	10p
2.5mm jack plugs	10p
2.5 and 3.5mm sockets	10p
2 pin DIN plugs	8p
2 pin DIN sockets	8p
eropins 0.1" and 0.15" per 25	15p
s.p.s.t. toggle switches	38p

L.E.D.S.

0.125" red	12p
0.125" green or yellow	21p
0.2" red	13p
0.2" green or yellow	22p
0.2" clear, illuminates red	22p
Clips for all above types:	2p

RESISTORS

1/2W and 1/4W tolerance ± 5% 4.7Ω to 10M. E12 series. Price each 2p.
Miniature presets. Tolerance ± 20%
Power rating 0.1W. E6 series 100Ω to 1M. Price each, vertical or horizontal. 9p

I.C. SOCKETS

Low profile types by Texas.
8 pin 11p. 14 pin 13p. 16 pin 13p.

SEMICONDUCTORS

BC107/8/9 11p, BC182/3/4 11p, AC127/8 24p, 2N3702/3/4/6 11p, BC338 16p, BC169 12p, 2N3819 25p, 1N4001/2 5p, BY127 18p, 1N5401 15p, 1N914 5p, IS44 7p, BZY88C series 2.7V to 33V 10p.

COMPONENT KITS

All previously advertised kits still available.
Latest kit prices:
NICAD Battery Charger
March 1981 £6.75
Active Tone Control Module
April 1981 £5.20

Please note that some kits exclude certain items. Full details in list, available on receipt of an s.a.e.

98 Burrow Road, Chigwell Essex. IG7 4HB.
Mail order only. Prices include VAT, overseas deduct 15%
NO minimum order charge. Postage: Components 40p
(Overseas add £1.50, airmail at cost), kits 65p. Orders are despatched same day as received.
Full catalogue available 45p cheque or postal order.
Enquiries please enclose an s.a.e.



Wilmslow Audio


THE firm for speakers!

SEND 50p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN'S ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO DEPT REC
35/39 CHURCH STREET, WILMSLOW
CHESHIRE SK9 1AS.

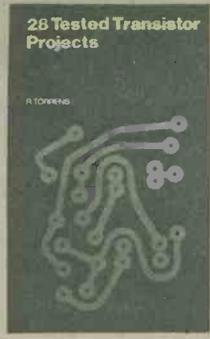Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits, etc.,
Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete speakers



DIRECT READER SERVICE RADIO & ELECTRONICS BOOKS

18. 50 Projects Using IC CA3130	£1.25	47. Practical Electronic Calculations and Formulae	£2.25
19. 50 CMOS IC Projects	£1.25	48. Radio Stations Guide	£1.45
20. A Practical Introduction to Digital IC's	95p	49. Electronic Security Devices	£1.45
22. Beginners Guide to Building Electronic Projects	£1.25	50. How to Build Your Own Solid State Oscilloscope	£1.50
23. Essential Theory for the Electronics Hobbyist	£1.25	51. 50 Circuits Using 7400 Series IC's	£1.45
26. 52 Projects Using IC741	95p	52. Second Book of CMOS IC Projects	£1.50
28. Two Transistor Electronic Projects	85p	53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators	£1.45
29. How to Build Your Own Metal and Treasure Locators	£1.00	54. Beginners Guide to Digital Techniques	95p
30. Electronic Calculator Users Handbook	95p	55. 28 Tested Transistor Projects	£1.25
31. Practical Repair and Renovation of Colour TVs	£1.25	56. Digital IC Equivalents and Pin Connections	£2.50
32. Handbook of IC Audio Preamplifier and Power Amplifier Construction	£1.25	57. Linear IC Equivalents and Pin Connections	£2.75
33. 50 Circuits Using Germanium, Silicon and Zener Diodes	75p	58. Electronic Household Projects	£1.75
34. 50 Projects Using Relays, SCR's and TRIACS	£1.25	59. Microprocessor Primer	£1.75
35. Fun and Games with your Electronic Calculator	75p	60. Remote control projects	£1.95
36. 50 (FET) Field Effect Transistor Projects	£1.25	61. Electronic Music Projects	£1.75
37. 50 Simple L.E.D. Circuits	75p	62. Electronic Test Equipment Construction	£1.75
38. How to Make Walkie-Talkies	£1.25	63. Power Supply Projects	£1.75
39. IC 555 Projects	£1.75	64. Elements of Electronics Book 4	£2.95
40. Projects in Opto-Electronics	£1.25	65. Practical Computer Experiments	£1.75
41. Radio Circuits Using IC's	£1.35	66. Radio Control for Beginners	£1.75
42. Mobile Discotheque Handbook	£1.35	67. Popular Electronic Circuits Book 1	£1.95
43. Electronic Projects for Beginners	£1.35	68. Electronics synthesiser Projects	£1.75
44. Popular Electronic Projects	£1.45	69. VMOS Projects	£1.95
45. IC LM3900 Projects	£1.35	70. Digital I.C. Projects	£1.95
46. Electronic Music and Creative Tape Recording	£1.25	71. International Transistor Equivalents Guide	£2.95

POSTAGE 30p PER BOOK, and 15p THEREAFTER FOR EACH BOOK ORDERED

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies

Book Nos:

I enclose Postal Order/Cheque for £

Name

Address

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

LATEST BOUND VOLUME No. 33.

of "Radio & Electronics Constructor"



Comprising
752 pages
inc. index

SEPTEMBER 1979
to AUGUST 1980

PRICE £6.20 P&P £1.50

BOUND VOLUME No. 27 (August 1973 to July 1974)
PRICE £3.00 p&p £1.50

BOUND VOLUME No. 28 (August 1974 to July 1975)
PRICE £3.20 p&p £1.50

BOUND VOLUME No. 29 (August 1975 to July 1976)
PRICE £3.50 p&p £1.50

BOUND VOLUME No. 30 (August 1976 to July 1977)
PRICE £3.70 p&p £1.50

BOUND VOLUME No. 31 (August 1977 to August 1978)
PRICE £5.20 p&p £1.50

BOUND VOLUME No. 32 (September 1978 to August 1979)
PRICE £5.50 p&p £1.50

We regret all other volumes are now completely sold out.

Available only from:

**DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON W9 1SN**

SUITABLE FOR


"CITIZEN'S BAND RADIO"

STEEL ENCLOSURES

Direct From Manufacturers

"QUINN TYPE"

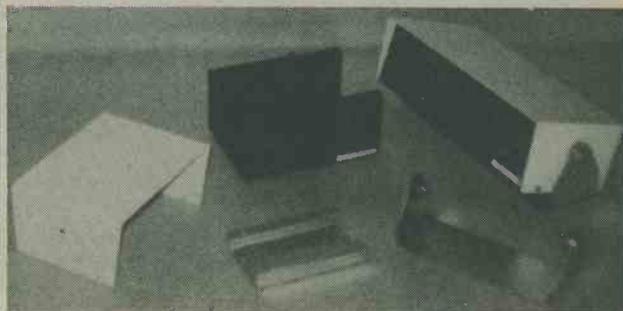Ridged Construction - Stove Enamelled
Front, Base & Rear one piece (Satin Black)
Wrap over cover one piece (White Gloss)



ACCESSORIES

Aluminium drop in Chassis (Blank)
Pivot Bracket "Bright Plated"

TRADE ENQUIRIES WELCOME
Larger Enclosures, Console, Brackets,
Chassis, Prototype or Production Runs.

"QUINN" TYPE SIZE IN MM

TYPE	LENGTH	HEIGHT	DEPTH	PRICE	CHASSIS	PIVOT BRACKET
A	120	60	90	£4.85	95p	£1.40
B	200	60	90	£5.70	£1.30	£1.90
C	180	100	150	£8.50	£2.95	£2.30
D	250	100	150	£12.60	£3.65	£2.85

POST AND PACKAGE £1.00.

JAMES ENGINEERING

(Phillips-James Engineering (North East) Ltd.)

Precision sheet metal and press work
Phone: Chester-le-Street 883230

Registered Office and Works:
Unit 4, Stella Gill Industrial Estate, Pelton Fell,
Chester-le-Street Co. Durham DH2 2RG.

PLEASE SUPPLY "QUINN TYPE" ENCL.

TYPE	ENCLOSURE	QTY	CHASSIS	QTY	PIVOT BRACKET	QTY
A						
B						
C						
D						

TICK REQUIREMENTS-

I ENCLOSE CHEQUE/PO

NAME

ADDRESS

.

.

.

BLOCK LETTERS PLEASE.

TRANSISTORS

AC122 30v.2w 12p	BCY31 64v.5w 59p	BFY75 30v.35w 15p	OC201 25v.25w 66p	2N2994 12v.36w 11p	2N6178 100v.25w 30p
AC126 30v.2w 16p	BCY56 45v.3w 11p	BFY90 30v.2w 59p	OC202 15v.25w 66p	2N2904 60v.6w 9p	2N6180 100v.25w 30p
AC128 36v.1wt 5p	BCY71 45v.35w 9p	BLY10 100v.115w 23p	OC603 22v.1w 50p	2N2905 60v.8w 15p	2N6181 75v.25w 30p
AC153 32v.1wt 11p	BCY72 25v.3w 9p	BR101 Prog. 20p	OC701 80v.35w 23p	2N2906 60v.4w 9p	2N6288 30v.40w 36p
AC176 32v.7w 11p	BCY79B 45v.3w 15p	BR339 Uni- 29p	ON222 23p	2N2907 A/6 60v.4w 9p	2N6290 60v.40w 36p
AC179 20v.1.1w 40p	BD115 25v.25w 32p	BRV36 Junct 29p	P77 Plastic 10wt 15p	2N2926 Y 25v.2w 4p	2N6292 80v.40w 30p
AC188 25v.1w 10p	BD133 60v.15w 57p	BSV60 45v.8w 30p	P346A 30v.6w 24p	2N2926 Orange 25v.2w 4p	2N6385 80v.100wt 55p
AC20 40v.3w 20p	BD116 80v.10w 35p	BSV64 100v.1w 36p	P7029 30p	2N3020 140v.8w 25p	Darlington 36p
ACV21 40v.3w 20p	BD131 45v.15w 15p	BSV79 40v.4w 50p	PXB103 30v.15w 20p	2N3054 90v.30w 35p	2N6486 40v.75w 36p
ACV28 40v.2w 22p	BD132 45v.15w 15p	BSV80 40v.4w 50p	RCP701A/B/D 15w 25p	2N3055RCA 100v.115wt 68p	2N6488 90v.75w 36p
AD161 20v.6wt 40p	BD133 90v.15w 28p	BSV81 Dep. Mos Fet 54p	R1039 (2008B) 30p	2N3133 50v.6w 24p	2S701 30v.5w 42p
AD162 20v.6wt 40p	BD135 45v.13w 22p	BSX19 40v.4w 75p	R2008B 66v.85w 54p	2N3135 50v.6w 24p	2SA12 16v.1w 42p
AD164 25v.6w 40p	BD136 45v.13w 14p	BSX20 40v.4w 7p	R2010B £1.18	2N3283 25v.1w 25p	2SA50 18v.1w 36p
AD165 25v.6w 40p	BD137 60v.8w 28p	BSX21 120v.3w 8p	R2306 100v.40w 26p	2N3418 85v.1wt 15p	2SA80 20v.1w 36p
AF119 30v.2w 35p	BD138 60v.8w 28p	BSX74 40v.3w 30p	R2540 £1.70	2N3442 160v.117w 75p	2SA83 25v.1w 36p
AF124 32v.1w 27p	BD137/8 mch pr 60p	BSY95A 20v.3w 30p	SB240 26p	2N3583 250v.38w 18p	2SA141 15v.1w 36p
AF127 32v.1w 23p	BD139 80v.12w 30p	BU105 1k5w 10w 64p	SFT357 20v.12w 26p	2N3645 60v.3w 3p	2SA124 15v.1w 36p
AF139 22v.1w 23p	BD140 80v.8w 26p	BU204 1k3v 10w 78p	SL102 40p	2N3663 30v.2w 6p	2SA236 18v.1w 50p
AF178 25v.1w 35p	BD142 60v.117w 35p	BU105/04 78p	TE886 £1	2N3702 40v.3w 22p	2SA354 25v.1w 38p
AF180 25v.16w 35p	BD156 70v.25w 50p	BU208 1k5v 12w 50p	T1929 40v.30w 22p	2N3703 50v.3w 3p	2SA350 20v.1w 34p
AF181 30v.16w 35p	BD182 70v.117w 44p	C1544 PNP £1.05	TIP30 40v.30w 22p	2N3704 50v.4w 4p	2SA367 20v.1w 56p
AF239 20v.1w 33p	BD201 45v.60w 86p	C1601 NPN 4p	TIP30C 100v.30w 26p	2N3705 30v.3w 4p	2SA18 18v.1w 38p
ALZ10 50v.5w 37p	BD202 45v.60w 86p	D40C4 40v.8wt 22p	TIP31C 100v.40w 26p	2N3707 30v.3w 4p	2SA634 50v.10w 80p
ASV60 35p	BD203 60v.60w 86p	Darlington 22p	TIP32C 100v.40w 26p	2N3711 30v.3w 8p	2SB75 25v.15w 25p
ASV63 26v.1w 4p	BD204 60v.60w 86p	D40D1 45v.7wt 22p	TIP32A 60v.40w 22p	2N3714 80v.150w 54p	2SB135 30v.1w 25p
ASV73 30v.15w 35p	BD232 50v.15w 34p	D40D2 45v.7wt 15p	TIP32C 100v.40w 26p	2N3794 75v.5w 14p	2SB156 16v.15w 60p
ASZ21 20v.12w 4p	BD233 45v.25w 20p	D40D4 60v.7wt 22p	TIP41 40v.65w 15p	2N3799 90v.36w 18p	2SB175 30v.15w 20p
AU110 160v.30w £1.43	BD238 80v.25w 25p	D41D2 45v.7wt 22p	TIP42C 100v.65w 33p	2N3823 FET 30v 25p	2SB176 32v.15w 20p
AU113 250v.30w £1.03	BD239C 115v.30w 29p	D43C7 70v.13wt 30p	TIP48 300v.40w 33p	2N3905 40v.3w 71p	2SB457 20v.15w 25p
BC107A/B 7p	BD240 55v.30w 30p	D45C8 50v.13wt 30p	TIP48 100v.60w Darl. 30p	2N4000 100v.15w 15p	2SC1061 50v.25w 50p
BC108A/B/C 7p	BD241 45v.40w 22p	D45C2 40v.30w 22p	TIP48 300v.40w 33p	2N4026 60v.5w 15p	2SD234 60v.25w 50p
BC109B 30v.3w 7p	BD242B 90v.40w 30p	DS70 Darl. 10wt 22p	TIP48 100v.60w Darl. 30p	2N4031 80v.1w 15p	2SD315D 200v 80p
BC109C 30v.3w 7p	BD246 55v.80w 32p	DS70 Darl. 10wt 22p	TIP112 100v.50w 45p	2N4289 MOSFET 45p	353-3 40v.5wt 22p
BC125 50v.3w 4p	BD253 35v.50w 44p	GET102 30v.2w 46p	TIP115 60v.50wt 30p	2N4403 40v.3w 71p	362-4 300v.6wt A/F 30p
BC126B 60v.3w 4p	BD275 50v.25w 35p	GET111 60v.2w 45p	TIP195 100v.90w 45p	2N4891 FET 30p	Video Amp (BF459) 30p
BC129A/B 50v.2w 7p	BD337 45v.36w 36p	GET120 30v.44w 30p	TIP3055 100v.90w 34p	2N4918 40v.30w 15p	2N5058 300v.5w 11p
BC130A/C 25v.2w 7p	BD338 45v.36w 36p	M103G MOSFET 30p	TIP3055 100v.90w 34p	2N5147 100v.7w 15p	2N5293 80v.36w 30p
BC131C 25v.2w 7p	BD347 60v.55w 28p	MA393 32v.5w 25p	TIS44 25v.25w 9p	2N5294 80v.36w 30p	2N5295 60v.36w 30p
BC139 40v.7w 11p	BD677 60v.40w 50p	ME21000 30v.7w dual £2.25	TIS60G 40v.3w 3p	2N5296 60v.36w 30p	2N5297 80v.36w 36p
BC140 40v.7w 15p	BD678 Pwr. Darl. 60v.40w 50p	ME2 15v.1w 14p	TIS61 40v.3w 3p	2N5449 30v.3w 3p	2N5484 30v FET 37p
BC141 60v.7w 11p	BDX33B 80v.70w Darl. 44p	ME0412 60v.2w 7p	TIS90 40v.65w 4p	2N5492 75v.50w 36p	2N5915 (16068) 450mHz 6WJ T.F. 12v 22.50
BC147 A/B/C 5p	BDX42 60v.3w 36p	ME0461 60v.3w 14p	TIS91 40v.65w 6p	2N6028 PUJT 6p	4039A 60v 1w 30p
BC148 A/B/C 5p	BDX77 80v.60w 50p	ME6101 70v.36w 7p	TIS92GY 40v.65w 6p	2N6106 80v.40w 44p	40633 NPN 40w 36p
BC149 A/B/C/S 5p	BDY20 60v.117w 86p	ME6102 60v.4w 7p	TIS94 30v.25w 14p	2N6109 60v.40w 44p	40911 (2N6261 + Ht. sink) 40p
BC154 40v.2w 7p	BF115 50v.2w 18p	ME8003 80v.4w 20p	TK24 30v.2w 20p	2N6111 40v.40w 36p	2N6124 45v.40w 24p
BC157 A/B 5p	BF167 30v.15w 18p	MJ481 60v.90w 25p	V435 30v.6w 20p	2N708 40v.4w 9p	2N718 80v.4w 10p
BC158 A/B 5p	BF173 25v.2w 23p	MJE371 40v.40w 40p	U14710 20p	2N718 80v.4w 9p	2N720A 120v.5w 12p
BC159 B/C 5p	BF178 185v.8w 28p	MJE2371 60v.40w 80p	ZT403P 30v.30p	2N720 120v.5w 12p	2N736 80v.5w 7p
BC160/10 40v.3.2w 12p	BF179 250v.6w 23p	MJE2901T (Higalv) 2955) 60v.90w 50p	ZT4186 110v.2.5w £1.10	2N740 15v.2w 12p	2N740 15v.2w 12p
BC168B 20v.3w 7p	BF180 30v.2w 12p	Mn 15 Russian 25p	ZTX341 100v.3w 9p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC171B 45v.3w 4p	BF182 25v.12w 18p	Mn41 Russian 25p	2G103 15v.3w 33p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC172 25v.3w 7p	BF183 25v.12w 18p	Mn41 Russian 25p	2G302 20v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC173 25v.3w 4p	BF184 20v.15w 18p	Mn41 Russian 25p	2G309 20v.3w 30p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC177A 45v.4w 10p	BF185 20v.15w 18p	Mn41 Russian 25p	2G339A 30v.15w 20p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC178A/B/C 10p	BF194 40v.25w 5p	Mn41 Russian 25p	2G371 20v.2w 18p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC179B 20v.3w 14p	BF197 40v.25w 5p	Mn41 Russian 25p	2N388 25v.15w 7p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC182/AL 50v.3w 5p	BF198 30v.3w 5p	Mn41 Russian 25p	2N456A 40v.90w 71p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC182L 50v.3w 3p	BF224 45v.36w 4p	Mn41 Russian 25p	2N525 45v.3w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC183A/AL/LC 3p	BF244C FET 30v 7p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC184 45v.3w 5p	BF245 FET 6p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC186 40v.3w 2p	BF254 30v.3w 12p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC187 30v.3w 8p	BF256FET 40p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC196A 30v 50mw 100 for £3.65p	BF256LBC/LC/FET 40p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC197A 50v 50mw 100 for £3.65p	BF257 160v.5w 20p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC198B 30v 50mw 100 for £3.65p	BF259 see 2N5058	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC199B 30v 50mw 100 for £3.65p	BF262 30v.12w 29p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC204 50v.3w 11p	BF263 30v.12w 29p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC212 50v.3w 5p	BF274 25v.12w 8p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC213L 45v.3w 5p	BF324 30v.3w 31p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC213LA 46v.3w 4p	BF336 185v.3w 16p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC213LB 45v.3w 4p	BF355 300v.3w 15p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC214B 45v.3w 5p	BF394B 40v.3w 3p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC214L 45v.3w 3p	BF451 40v.3w 3p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC237A 45v.3w 7p	BF494 20v.3w 10p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC237B 50v.3w 7p	BF495 20v.3w 5p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC238 20v.3w 7p	BF595C 30v.25w 91p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC238B/C 7p	BF615 27p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC239C 20v.3w 5p	BF617 27p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC251 45v.3w 3p	BFQ35 15p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC267B 45v.3w 7p	BFQ37 15p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC258B/C 7p	BFQ37 15p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC259C 20v.3w 7p	BFR34A 12v.2w £1	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC302 80v.9w 15p	BFR38 40v.2w 68p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC304 80v.9w 15p	BFR98 120v.8w 19p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC307 45v.3w 7p	BFS21 FET pair 53p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC308B/C 25v.3w 7p	BFS28 Dual M/Fet 23p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC309B 20v.3w 7p	BFT30 70v.36w 15p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC327 45v.7w 5p	BFT31 60v.36w 15p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC328 25v.7w 6p	BFT39 90v.8w 15p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC337 45v.7w 6p	BFT41 60v.8w 15p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC338 25v.7w 5p	BFT60 80v.8w 8p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC382L 50v.3w 7p	BFT61 60v.8w 15p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v.2w 12p
BC384B 45v.3w 7p	BFT70 70v.36w 15p	Mn41 Russian 25p	2N527 45v.2w 12p	2N742 15v.2w 12p	2N742 15v

PRICES SO LOW, THE POLICE INVESTIGATED ME TWICE
 ALL ENQUIRIES, ETC. MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

VAT & POST PAID
 (UK 2nd Class or Parcel) Just include stamped addressed envelope
 MINIMUM ORDER FIVE POUNDS, OTHERWISE ADD 50% FOR SMALL ORDER HANDLING COSTS

UK - Postal Orders for prompt service. Cheques require 9 days from a Monday banking to ensure clearance. Export - banker's draft (sterling) prompt service. Foreign currency not accepted. VAT content becomes documentation charge. Add additional postage for overseas mail.

OPTO ELECTRONICS
 Photo Diodes: 30F2, 31F2, 32F2, 33F2, BPX40, BPY10, BPY68, BPY69, BPY77, CQY17, CQY77.
 All types 38p
 Wire end neons 5p.
 Photo transistor: BPX43, BP103, 2N5777, Darlingtion 36p; LED's (Mulling Siemens) Red 5mm 8p, 3mm 13p; Green 5mm 13p, 3mm 13p; Yellow 5mm 13p, 3mm 13p, micro LD481 8p
 PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp 36p.
 CA3062 Photo Detector and power amp. £1.05p

7 SEGMENT L.E.D. DISPLAYS
 .3" Red com. anode 81p
 .6" Green C.A. £1.77
 5082-7650 Red com. anode.
 5082-7653 Red com. cath
 5082-7600 Yellow com. anode.
 H.P. Highbrilliance .43" 72p

HEWLETT PACKARD MULTIPLEXED .11" 7 SEGMENT LED DISPLAYS
 3 Digit HP5082 7413 45p
 4 Digit HP 5082 7414 45p
 5 Digit HP 5082 7415 45p
 Infra red transmit diodes CQY118 or LD271 High power 1.6-2v or 3-3.5v Pulse 32p
 LD242 36p
 H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p
 CNY17/1 opto coupler 70p
 Cold cathode tubes I.T.T. G517A or 5870L 60p

SPECIAL OFFER
 IN4004 or IN4006 Sealed manufacturers carton of 300. £6.85

SLIDE POTENTIOMETERS ALL TYPES 30p
 60mm 40mm
 LOG LOG
 250Ω 10K
 1K 22K
 5K 50K
 47K 100K
 50K Neg LIN
 100K 470Ω
 250K 1K
 470K 1K
 1M 100K
 2M 470K
 LIN
 500Ω
 1K 30mm
 2K2 LOG
 10K 5K
 22K 22K
 47K 50K
 50K 100K
 100K LIN
 250K 1K
 500K 5K

BOXES - Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 85p
 Clear perspex with sliding lid. 46 x 39 x 24mm 18p

ABS, ribbed inside 5mm centres for P.C.B. brass corner inserts screw down lid. 50 x 100 x 25mm orange 85p; 80 x 150 x 50mm black £1.39, 110 x 190 x 60mm black £1.98.

DIODES
 AA118 90v 50ma 4p
 AA119 30v 35ma 7p
 AA133 100v 50ma 9p
 AA144 100v 5ma 4p
 AA215 100v 250ma 15p
 AAZ17 50v 40ma 6p
 B1 11p
 BA101B varicap 10p
 BA116 20v 100ma 30p
 BA127 60v 100ma 3p
 BA128 50v 100ma 21p
 BA145 350v 500ma 21p
 BA148 350v 500ma 12p
 BA182 Varicap 8p
 BAX 13 50v 150ma 3p
 BAX14 40v 350ma 21p
 BAX20 25v 115ma 3p
 BAX21 50v 120ma 3p
 BAX22 100v 120ma 3p
 BAX54 8p
 BAY36P 30v 3ma 21p
 BAY44 50v 250ma 4p
 BAY68 25v 115ma 3p
 BAY72 100v 400ma 4p
 BB103 Varicap 24p
 BB104 Varicap 16p
 BB109 Varicap 24p
 BB110B Varicap 24p
 BB113 3x Varicap 43p
 BB139 varicap £1
 BR100 Diac. 15p
 BY206 350v 600ma 71p
 BY207 600v 600ma 23p
 BY402 100v 1A 21p
 BY403 200v 1A 21p
 Centercell 3p
 CG651 9p
 CR HG/3 10p
 CSD117YLZ 40p
 CV7095 21p
 CV7098 21p
 D3202Y Diac. 11p
 DC2845 Microwave 20p
 DODG53 11p

*Germanium: rest silicon
 FSY28A 40p
 HG1005 100v 45ma 3p
 HG1012 50v 50ma 10p
 MPN3401 VHF switch 30p
 OA5 100v 115ma 25p
 OA7 25v 50ma 25p
 OA10 25v 110ma 25p
 OA40 40v 50ma 4p
 OA47 30v 150ma 7p
 OA51 50v 50ma 4p
 OA70 22v 50ma 10p
 OA75 40v 50ma 11p
 OA79 45v 35ma 11p
 OA81 115v 150ma 31p
 OA90 30v 45ma 4p
 OA91 115v 150ma 6p
 OA95 115v 150ma 6p
 OA200 50v 250ma 21p

IN63 100v 40ma 4p
 IN337 200v 200ma 4p
 IN447 40v 25ma 3p
 IN604 400v 300ma 4p
 IN662 80v 40ma 21p
 IN916 100v 300ma 21p
 IN3062 75v 20ma 3p
 IN3063 (BAV10) 6p
 IN3064 75v 10ma 21p
 IN4009 25v 75ma 71p
 IN4148 100v 200ma 11p
 IN4149 100v 200ma 3p
 IN4150 50v 200ma 21p
 IN4151 50v 200ma 21p
 IN4152 40v 200ma 3p
 IN4446 100v 200ma 21p
 IN4449 100v 200ma 21p
 IN5154 25v 30ma 3p
 IN5456 Varicap 15p
 IS922 150v 200ma 4p
 IS940 30v 50ma 3p
 5082 2900 RF Schotky Barrier 50p

RECTIFIERS

Type	Volt	Amp	Price
BY126	650	1	5p
BY127	1250	1	5p
BY212	150v	500ma	6p
BY235	600	1 1/2	7 1/2p
BY236	900	1 1/2	7 1/2p
BY264	300	3	9p
BY265	600	3	11 1/2p
BY266	900	3	15p
BY275	600	5	19 1/2p
BY277	1200	5	27p
BY1202	2kV	10mA	6p
BYW55	800	2 (Oxide bead)	15p
BYW56	1000	2 (Oxide bead)	18p
BYX20-200	200	25	72p
BYX22-200	300	1 1/2	25p
BYX38 300R	300	6	48p
BYX38 600	600	6	52p
BYX38 900	900	6	60p
BYX38 1200	1200	6	65p
BYX42 300	300	12	36p
BYX42 600	600	12	46p
BYX42 900	900	12	46p
BYX42 1200	1200	12	£1.07
BYX46 300R	300	15	£1.19
BYX46 400R	400	15	Avalanche £1.75
BYX46 500R	500	15	£2.00
BYX46 600	600	15	£2.30
BYX48 300R	300	6	47p
BYX48 600	600	6	60p
BYX48 900	900	6	70p
BYX48 1200R	1200	6	82p
BYX49 300R	300	6	35p
BYX49 600	600	6	42p
BYX49 900R	900	6	47p
BYX49 1200	1200	6	60p
BYX52 300	300	48	£2.05
BYX52 1200	1200	48	£2.90
BYX70	100	4	4p
BYX72 150R	150	10	42p
BYX72 300R	300	10	52p
BYX72 500R	500	10	65p
BYX94	1250	1	6p
E250C50	250	1	14p
KS11394	800	3	23p
LT102	30	2	15p
M1	58	1	5p
MR56	600	3	24p
MSR5	800	3	12p
OA210	400	5	33p
RAS3 IOAF	1250	1 1/2	Avalanche 48p
RAS508AF	1250	1 1/2	Avalanche 50p
REC53A	1250	1 1/2	Pack of 4 66p
SKE4G	200	6	22p
SR100	100	1	9p
SR400	400	1	10p
SR1825	100	50	75p
IN3254	400	1	4p
IN4002	400	1	4p
IN4004	400	1	4p
IN4005	600	1	6p
IN4006	800	1	6p
IN4007	1250	1	6p
IN5059	200	3 1/2	10p
IN5401	100	3	12 1/2p
IN5402	200	3	11p
IN5406	600	3	15p
IN5408	1000	3	19p
IS027	800	1 1/2	11p
IS138	800	1	21p
25G100	100	60	£4.35
3052	200	3	11p
16094P	900	2	15p
16492	700	1 1/2	9p

BRIDGE RECTIFIERS

AMP	VOLT	Type	Price
0.6	60VOLT	BC30 C350	23p
1	1,600	BYX10	34p
1	110	EC433	20p
1	100V	B40C800	12p
1	140	05HNT-200	26p
1	400V	MDA104	29p
1 1/2	50V	WO05	27p
1 1/2	75V	IBIBY234	11 1/2p
1 1/2	150V	IBIBY235	15p
1 1/2	200V	WO2 Ex Equip	15p
1 1/2	400V	WO4	28p
1 1/2	400V	UE4R1	12p
1 1/2	800V	WO8	27p
1 1/2	1000	W10	36p
2 1/2	100	I.R.	40p
2 1/2	350V	9F2	53p
2 1/2	500V	9E4	85p
3	50	KBS005	30p
3	100	KBS01	30p
3	200	KBS02	30p
3	400	KBS04	30p
3	600	KBS06	30p
3 1/2	100	B40C 3200	39p
5	400	Texas	85p
			34p

THYRISTORS

Amp	Volt	Type	Price
0.8	200	2N5064	18p
1	240	BTX18-200	35p
1	240	BTX30-200	35p
1	400	BTX18-300	41p
1	700	BT 106	70p
2	400	S2710D with heatsink	40p
3	600	T3N06C00	53p
3	100	T3N1C00	36p
4	50	S107F Sensitive Gate	36p
4	50	S2060F Sensitive Gate	36p
4	400	S2061D Sensitive Gate	38p
4	500	40506 with heatsink	58p
4	500	17083	36p
4	600	C106M Sensitive Gate	37p
4	600	2N3228	36p
4	600	GAK	36p
5	400	S5800D/R	36p
5	500	17047A	40p
5	600	17058	44p
5	600	S5800M	44p
6.5	500	BT109/SCR957	71p
7	400	S2620D	45p
7	600	S2620M	45p
8	100	S2800A	36p
8	600	S122M	54p
12	1000	CR121-03-RB	£1
15	800	BTX95-800 Pulse Modulated	£1
20	600	BTW92-600RM	£3.40
75	800	71CG80	£6
110	20	72RC2A	£3
110	1000	151RA100	£10
120	1200	151RA120	£11
			70p
			£1

ZENER DIODES

4/500MW. BZY88, BZX97, etc. 5p
 2v. 2v7. 3v. 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v8. 7v5. 8v2. 9v1. 10v. 11v. 12v. 13v. 13v5. 15v. 18v. 20v. 22v. 24v. 27v. 30v. 33v. 43v.
 BZY61 Laboratory Standard 400MW 7v5. Voltage Regulator Diode 12p
 1.3/1.5WT BZX61, BZY97, etc. 11p
 2v7. 3v. 3v6. 3v9. 4v3. 4v7. 5v6. 6v2. 6v8. 8v2. 10v. 11v. 12v. 15v. 18v. 20v. 27v. 33v.
 2.5WT BZX70, etc. 13p
 3v6. 3v9. 5v6. 6v2. 7v. 7v5. 8v. 9v. 10v. 11v. 14v. 15v. (8p) 20v. 22v. 26v.
 5WT BZV40, etc. 15p
 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 8v7. 9v1. 10v. 11v. 12v. 15v. 20v. 33v. 68v. 120v.
 10WT Z5D, ZX, IS50, etc. 23p
 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 10v. 11v. 12v. 13v. 16v. 18v. 21v. 22v. 33v. 36v. 39v. 43v. 51v. 56v. 62v. 68v. 75v. 150v.
 15WT BZV15C 12R 12volt 37p
 20WT BZY93, etc. 44p
 8v2. 39v.

TEMPERATURE COMPENSATED REFERENCE 8p
 IN935B, IN936B, IN937B 9volt
 IN941B, IN942B, IN943B 11.7volt

ROTARY WAFER SWITCHES


Pole	Way	Price
1	3	26p
1	5	40p
1	8	40p
1	11	26p
1	12	26p
2	3	plus Mains D.P. 30p
2	4	26p
2	5	48p
2	6	40p
3	7	26p
4	2	26p
4	3	48p
4	5	49p
6	3	26p
7	4	plus Mains D.P. 26p
12	3	plus Off 26p

BULBS

MES
 2v5 .3A 12p. 3v5 .15A 11p.
 3v5 .3A 6p. 6v .3A 12p. 12v 2.2W 18p. 24v 2.8W 13p.
 14v .8W 13p. 24v 3W 13p.

WIRE END
 12v 13p. 19v 60ma 13p.
 Miniature Flange
 6v 12v 24v 28v 21p
 Submin. Flange
 8v. 28v. 26p

L.E.S.
 6v 11p. 12v 11p. 28v 19p.

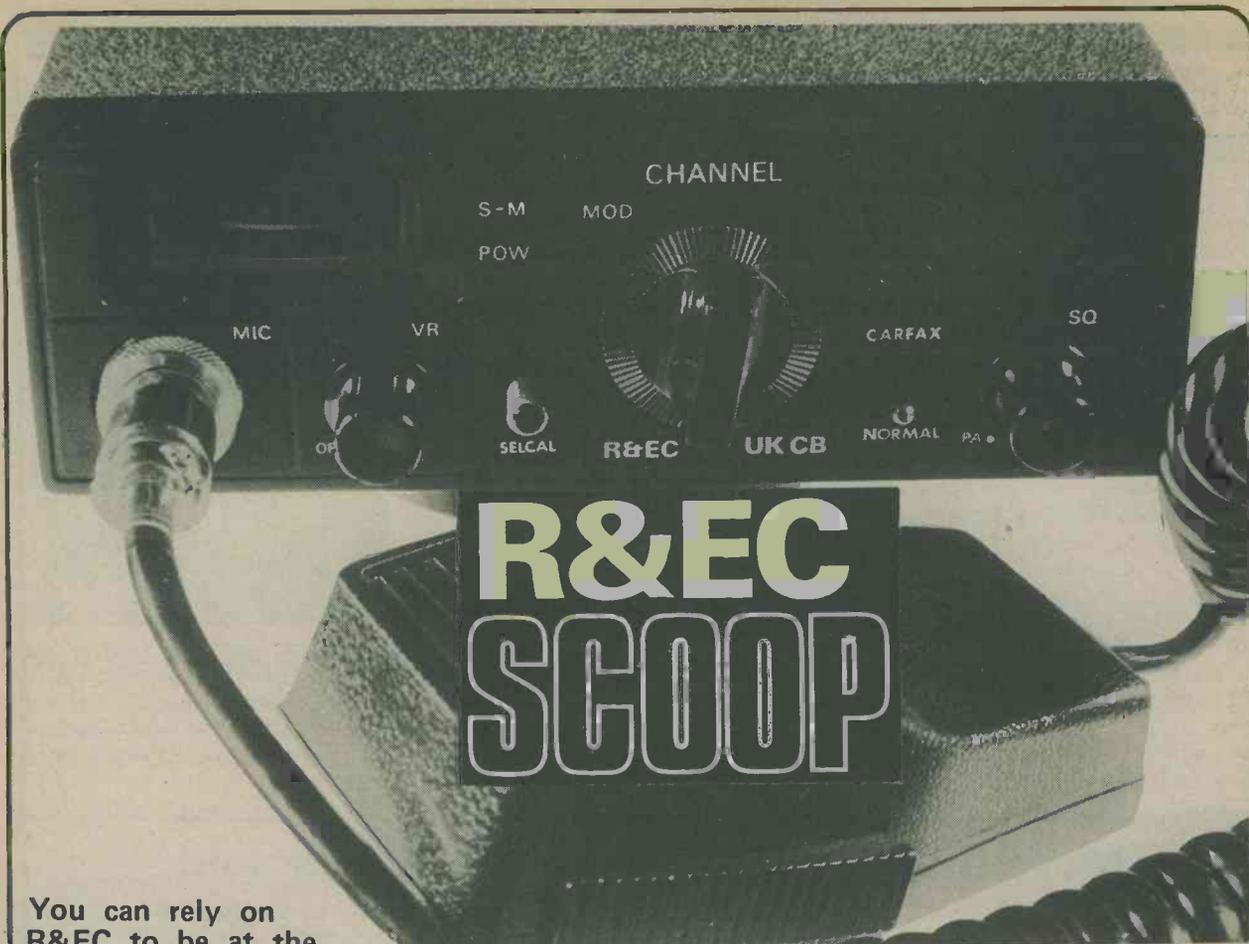

R&EC SCOOP

You can rely on
R&EC to be at the
forefront of development

- so here you are! **THE FIRST U.K. SPEC. C.B. RIG PROTOTYPE!**

Watch R&EC for details of availability of this SUPERB UNIT.....

£55.00 Built INC VAT*



**Kit price and
availability will
depend upon terms of U.K.
C.B. licence re approval etc.*

NEWS . . . AND

SOLDERING STATION FIRST

Adcola Products of Adcola House, Gauden Road, London, SW4 6LH believe that their new Unit 2001 is the first genuine complete soldering station. The Unit consists of an electronically controlled soldering tool, fume extractor, fluorescent lighting, and solder dispenser, which is suspended over the work piece by a pole system clamped to the rear or side of the bench. This system is fully adjustable in height and depth with the facility that the Unit can be swung away from the work when not required.

The electronically controlled soldering instrument is based on their already well accepted Unit 101, which is a 50 watt electronically controlled 3/16in./4.75mm

dia. bit soldering instrument with a temperature range of 120 deg. C to 420 deg. C. This soldering tool is potential free and has a positive earthing system which, should the user wish, may be connected to a known earth source. Also, being electronically controlled, there is no mains spiking or magnetic effect, thereby reducing any possibility of damage to voltage/temperature sensitive components.

The lighting system gives an excellent spread of light on the work piece from three diffused 6 watt fluorescent lamps.

The two 11 watt fans are dual speed which pass the flux fumes through a special filter to aid in obtaining a clean air situation. By



extracting and controlling the fumes from a soldering operation reduces operator fatigue and the hazards associated with soldering fumes in the hand soldering situations.

More than 1,000 Warden 4 receivers sold

The thousandth Warden 4 watchkeeping receiver ordered from The Marconi International Marine Company Limited, a GEC-Marconi Electronics company, is to be fitted aboard the 'Sea Conquest', an offshore drilling rig belonging to BP Petroleum Developments Limited. 'Sea Conquest' is currently operating in the North Sea and fitting will be carried out by Marconi Marine's office at Riverside, Aberdeen.

Warden 4, a watchkeeping receiver operating on the international radiotelephone distress frequency 2182kHz, was introduced in January 1980, by Marconi Marine in anticipation of the new requirements

resulting from the recommendations of the International Safety of Life at Sea Convention 1974. One of these requirements, now embodied in the Merchant Shipping (Radio Installation) Regulations 1980, is for all sea-going vessels of over three hundred tons to carry such a watchkeeping receiver, and to have it switched on in a place that is permanently manned, at all times whilst the ship is at sea.

So far the orders received by Marconi Marine are averaging one hundred per month. They are being received from owners and shipyards throughout the world.

Ultra low power DPM with digital hold

A new LCD meter from Lascar Electronics Ltd., Unit 1, Thomasin Rd., Basildon, Essex, is claimed to be the first of a new generation of DPMs, giving at least ten times the battery life of any existing type. A PP3 battery will power the meter for typically two years, if operated for eight hours a day, seven days a week.



LCD Watch manufacturing techniques are used to reduce the depth to a minimum, the meter being fitted into a DIN bezel of 72mm x 36mm. The 0.6in. (15mm) digits can be read at distances up to ten metres, and the display contains many other useful annunciators. The totally flush face makes it easy to screen print any other logo or engineering unit onto the display.

Other standard features include a Digital Hold facility, Auto-zero, Auto-polarity, External bandgap reference for maximum stability, single-rail supply of 5 - 15V d.c. drawing 200µA, programmable decimal points and a 200mV full scale deflection. The DPM can be used in single ended, differential or ratiometric modes, and may also be used in applications such as temperature measurement or weighting systems, where a variable offset or tare is required. Display backlighting is a customer option. The meter is supplied with brackets for front or rear panel mounting.

... COMMENT

Here we go

The changes at R & E C are gathering pace, and we now offer you a chance to influence the change of format and content, simply by completing the inserted reader survey form.

Our intention is to be a **magazine** of ideas, new techniques and viable projects – rather than a series of abstracts from standard textbooks, and projects that bear precious little resemblance in both technology and presentation to their commercial counterparts. We do concede that some aspects of theory need to be examined from time-to-time, since certain interpretations of basic concepts tend to get overlooked, unless given an occasional airing. To cater for the need for theory and tutorial reference works, we will soon be offering a vastly expanded range of titles from our book pages.

Special Offers

You can't be in the business of publishing electronics mags these days without some sort of 'Reader Offer' page, but we hope to keep ours reasonably different and diverse, even at the possible expense of some of the universality of their appeal. The radio headphones we offer with this issue are certainly slightly different, since as well as offering an entertaining alternative to simple ear defenders in noisy environments, the brave are invited to get inside and use them for derivative projects – such as infra red headphones for HiFi, magnetic loop communications etc. Even if you could get them, a set of 'phones with a battery compartment, volume control and switch would probably cost more.

Loudspeaker flat-back cabinet kits

To make life really easy for the loudspeaker constructor, Wilmslow Audio now offer flat-pack cabinet kits for many popular designs including the new Wharfedale E50, E70 and E90 kits.

All panels are accurately cut to size and baffle boards have the necessary speaker apertures cut and rebated where required. The cabinets when assembled may be painted or stained, or finished with iron-on veneer.

Wilmslow Audio Ltd, are now in new premises at 35/39 Church St., Wilmslow, Cheshire, where touch-control customer operated demonstration facilities enable prospective kit buyers to listen before purchase.


The company claims to have the largest selection of speaker drive units and kits available anywhere.

Quotation

"In those days ITN wasn't in smart premises in Wells Street in the heart of the West End. It had some rooms in an office block in Kingsway, which were so dingy they say vandals once broke in and decorated the place."

Peter Sissons presenting the tenth and final Richard Spriggs Memorial Lecture.

Excellent housing for portable equipment

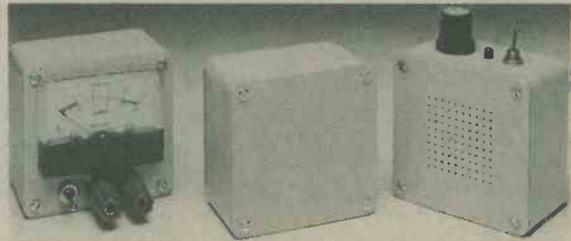

Electronic Products (Coventry) Ltd., of 20 Duke Street, Chapel fields, Coventry, are selling a moulded high impact styrene box no. 7544, which provides an excellent housing for electrical equipment such as, portable test instruments, alarms, etc. They are extremely robust and may be used in a variety of applications where a small enclosure or potting box is required.

The dimensions of the box are 75mm x 75mm x 44mm depth, and are in two colours, grey or black. (Other colours in large quantities are available on request).

They can be machined, engraved or silk screened and the maximum working temperature is 65 deg C. These extremely useful general purpose boxes come complete with lid and four self-tap fixing screws.

For original equipment manufacturers using quantities of 1,000 upwards a customised tooling service for the lids, grills, holes and logos, which can be foil blocked, can be provided.

The box singly is £0.49p. + V.A.T. postage and packing. For larger quantities a price list is available on request.


SUSSEX MOBILE RALLY

The second Sussex Mobile Rally to be held at Brighton Race Course will be on Sunday 19th July 1981, from 10.30 am to 6 pm. Last year nearly three thousand people attended the rally, with more than one hundred stands under cover. The rally is organised by six amateur radio clubs in the Sussex area.

This year's rally will be even larger (20,100 sq. ft of display area) with more trade stands dealing in all forms of electronics, including amateur radio, microprocessors, components and C.B. This is the rally which caters for the whole family, with free trips to the sea front by mini bus, super restaurant and bar facilities, side shows for the children, demonstrations by marching bands, majorettes etc.

Entrance charge will be 50p (with free lucky draw ticket). For disabled persons and children under 14 years there will be no charge. There are free parking facilities for more than four thousand cars. An area for caravan parking is available.

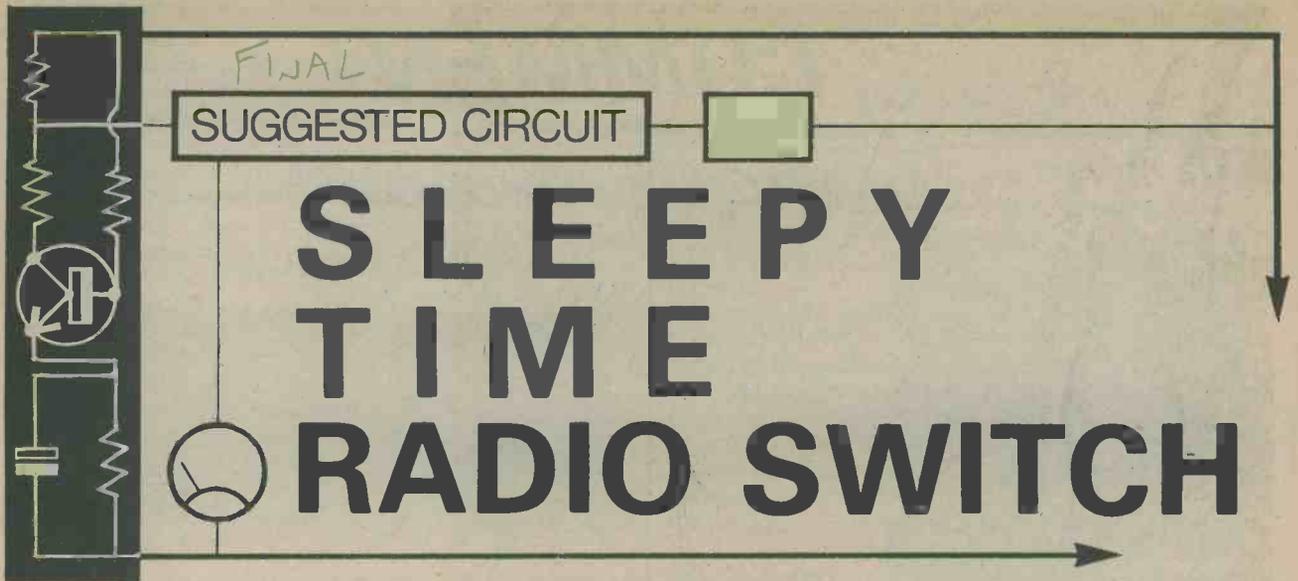Further details can be obtained from: – A. K. Baker. (G4GNX). 38, Elphick Road, Newhaven, Sussex. Tel: (07912) 5327 Evenings.



Many people like to have a bedside radio playing softly when, in bed, they settle down to sleep. Ideally, the radio should be switched off just before falling into final sleep but the necessity of reaching out and switching it off can, of itself, be a deterrent to sleep. Alternatively, it can happen that the radio does not get turned off at all, with the result that, on waking, the sleeper realises that the set has been switched on all night, shortening the life of its battery.

The circuit to be described this month is for a timing circuit which can switch off a radio about quarter of an hour after it has been activated. All that has to be done is press a button, snuggle down into the sheets and descend into the land of Nod, secure in the knowledge that the radio will switch itself off after the timing period has elapsed.

The switch-off circuit is primarily intended to be built as a separate unit with its own 9-volt battery. An important feature of the circuit is that an infinitesimal average current is drawn from this battery, so that its active life is virtually equal to its shelf life. In most instances, no measurable extra current is drawn also from the radio battery. The circuit is suitable for standard transistor superhets powered by 9 volt or 6 volt batteries, and the exceptionally low current requirements are due to the use of a VMOS power f.e.t. type VK1011.

PERFORMANCE CHECK

The VK1022 is a small device in a T092-style package, and has a maximum drain current rating of 0.5 amp. It is intended for operation with the source negative of the drain, and it is cut off when the gate is at the same potential as the source. Taking the gate positive causes the device to become conductive. An extremely high resistance is given between the gate and the remaining two electrodes. An input protection zener diode is provided inside the device and no special handling precautions are necessary.

It is often a good idea to check out new devices in simple characteristic testing circuits. The writer has not previously encountered the VK1011 and so he checked out several in the circuit of Fig.1. The gate voltage is adjustable by means of the 10k Ω potentiometer, the gate source voltage being

monitored by a voltmeter. The drain couples to a 9 volt positive supply by a load, R_L , and the drain-source voltage is measured by a second voltmeter.

Readings were taken with R_L at 10k Ω , at 1k Ω and at 100 Ω , and the results are shown in the curves given in Fig.2. When the gate voltage, V_{gs} , is at zero the f.e.t. is cut off, and its drain-source voltage, V_{ds} , is equal to the full 9 volts of the supply. With the 10k Ω load the f.e.t. commences to pass drain current when the V_{gs} is about 1.4 volts, and the f.e.t. is fully turned on with the V_{gs} at about 1.6 volts. The drain current through the 10k Ω resistor is then 0.9mA. With a 1k Ω load the device starts to draw current with a V_{gs} of around 1.6 volts and is fully turned on with a V_{gs} of slightly more than 2 volts. In this state there is about 0.2 volt across the drain and source, which reduces to zero at a V_{gs} of approximately 4 volts. The on-current here is 9mA. With a 100 Ω load, a significant drain current starts to flow at a gate voltage of around 1.8 volts, and there is 1 volt across the drain and source at 3 volts V_{gs} . V_{ds} settles down to around 0.4 volt at a V_{gs} of 4 volts and higher. The current here is slightly less than 90mA.

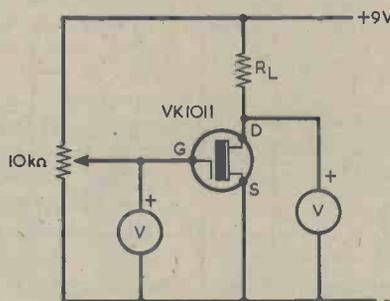


Fig.1. Simple test circuit to find the characteristics of the VK1011 VMOS power f.e.t.

The curves of Fig.2 are not taken from manufacturers' data, but are the result of measurements taken by the writer. In the application to be

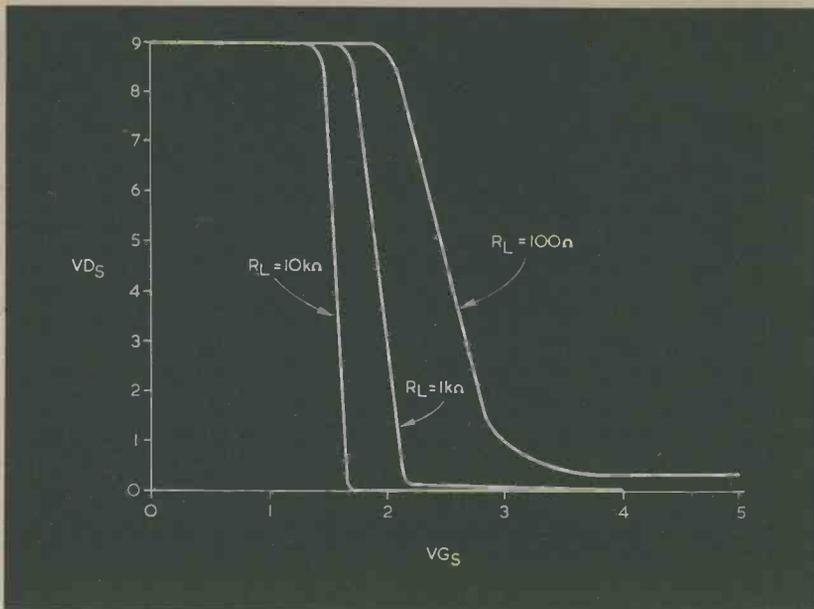


Fig.2. Curves obtained from the set-up of Fig.1. for load resistors of 10kΩ, 1kΩ, and 100Ω.

described, where precision in the timing is not necessary, they should be sufficiently close to central, typical, performance to enable a practicable circuit design to be realised. The average small transistor radio draws a quiescent current of about 10mA and, when it is used as a bedside radio late at night, will be turned low and draw few output current peaks. We can assume, therefore, that we will obtain about the same results if we use a VK1011 to turn a radio off as we get with the 1kΩ load resistor of Fig.2. (It should be noted, incidentally, that the timing circuit will still work with a radio having its volume turned high and drawing consequent current peaks at high a.f. output levels). Working from the 1kΩ load curve in Fig. 2, we can anticipate that, at gate voltages above around 2 volts, a VK1011 in series with a radio will be fully turned on, and that it will fully turn off when the Vgs is about 1.6 volts. The change from fully on to fully off with relation to Vgs is relatively fairly slow and so it is necessary to provide the timing circuit with a trigger action which will speed the turn-off operation.

COMPLETE CIRCUIT

The complete circuit of the bedside radio switch-off timer is given in Fig.3. TR2, a VK1011 is interposed in series with the

negative terminal of the radio battery and the radio negative supply rail. TR2 is the switching f.e.t., and R3 is merely a current limiting resistor which ensures that the surge current in TR2 cannot exceed 0.5 amp if it is turned on when the supply bypass electrolytic capacitors are discharged. R3 should have no effect on the performance of a standard radio having the usual supply bypass capacitors, and the voltage dropped across it at 10mA is less than 0.2 volt. S2 short-circuits TR2 and allows the radio to be played in normal manner.

Capacitor C1 is normally discharged, causing the voltage on TR2 gate to be equal to that on its source. If, with the radio turned on at its own switch, S2 is opened TR2 will pass no cur-

rent and the radio will then turn off. The full radio battery voltage appears across TR2, and the voltage on TR2 drain is passed to the gate of TR1, which is another VK1011. Push-button S1 is now pressed. A momentary pulse of 9mA is passed through R2 because, at the instant of closure of S1, TR1 has a high positive voltage on its gate. At the same time, 9 volts positive is applied to the gate of TR2, turning this f.e.t. on, and causing the radio to be turned on also. TR2 drain-source voltage, now very nearly zero volts, is applied to the gate of TR1, which turns off. C1 becomes charged to 9 volts.

When S1 is released, C1 commences to discharge into the 1MΩ resistor, R1. The discharge rate is slow, and is dependent upon the value of the capacitor. When the voltage on the positive terminal of C1 is greater than about 2 volts, TR2 is turned fully on and the radio continues to play. Near the end of the timing period the voltage on the gate of TR2 is at about 2 volts and TR2 starts to turn off. Its drain voltage begins to rise, taking the gate of TR1 positive. When TR1 gate voltage reaches the level at which this f.e.t. starts to conduct, it draws a discharge current from C1 and the voltage across the capacitor decreases more rapidly. So also does the gate voltage of TR2, whereupon its drain voltage rises further and TR1 is turned more fully on. There is a rapid cumulative changeover which results in TR1 being turned fully on, C1 fully discharged and TR2 (and the radio) fully

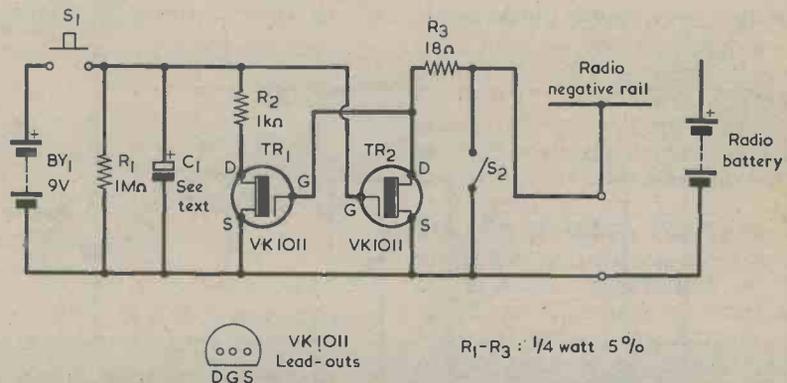


Fig.3. The circuit of the bedside radio switch-off timer. This can be built as a separate small unit coupled by two wires to the radio circuitry.

turned off. By this time the sleeper should be fully turned off too, and safely in the arms of Morpheus.

The quick changeover is due to the phase reversal between gate and drain in each f.e.t. When coupled together as here, the two f.e.t.'s give a high level of positive feedback during the brief period when they are both giving linear amplification. Working from the curves of Fig.2 it would be expected that TR1 starts to turn on when the voltage across TR2 reaches about 1.2 volts. In practice, the changeover occurs at a voltage lower than 1 volt across TR2. Doubtless, TR1 starts to draw a small drain current at gate voltages of this level, and such a current does not give significant indications in the analogue voltmeters which were used in the simple test set-up of Fig.1, and from which the curves of Fig.2 were drawn.

When the circuit has turned off the radio, the only current which flows from the radio battery is leakage current between the drain and source of TR2, and leakage current between the gate and source of TR1. This current was checked by inserting a meter in series with the radio negative rail. There was no perceptible current indication at all when the meter was switched to read 0-50 μ A.

TIMING VALUES

Working from the assumptions we have made, the circuit triggers to the off state when the voltage across C1 falls to about 2 volts. This is 22% of the initial voltage across C1 and the corresponding time of discharge is approximately 1.5CR. However, we can use this figure as a very rough guide only

because it does not take into account spread in gate voltage in TR2. There is also the fact that we shall have to use an electrolytic capacitor for C1 and such a component has a notoriously wide tolerance on value. Another factor is that some very high electrolytic capacitors tend to give unpredictable discharge times when discharging into a 1M Ω resistor. Because of all these factors, the value finally fitted in the C1 position has to be found after some experiment.

When the circuit has been assembled and wired up to the radio, a 10 μ F capacitor is employed for C1. This allows the circuit to be given a quick check-over. The radio is switched on, S2 is opened and S1 is pressed. The radio will then turn on and the timing period proceed until the radio turns off again. The length of the period should be measured by means of a watch with a sweep second hand or a digital read-out. From our assumptions, the period should be about 15 seconds, but in practice it will probably be somewhere between, say, 10 and 25 seconds. Let us say that it is 20 seconds. We then say that, if 10 μ F gives 20 seconds, 100 μ F should give 200 seconds, 300 μ F should give 600 seconds (10 minutes) and 500 μ F should give 1,000 seconds (17 minutes). A 10 minute delay before the radio turns off seems fairly reasonable for starting off and we could next try a 330 μ F capacitor for C1. It is quite possible that this will give a period significantly longer than 10 minutes, and this may then be considered satisfactory. Finding the final value for C1 is an experimental procedure

which follows the reasoning process just described. It will be preferable to avoid using values greater than 500 μ F.

The length of the timing period is affected by the current drawn by the radio through TR2. If this current decreases due to aging of the radio battery, TR2 gate has to be taken to a lower voltage by the discharging C1 before the f.e.t. starts to turn off. The length of the timing period thus increases. Although the reduction in required gate voltage is small it occurs when the CR discharge curve is flattening out and the increase in timing period will be disproportionately long. This raises no problems in the present application, where accuracy of timing is relatively unimportant. Nevertheless, it may be to advantage to find the final value in C1 with the radio at a low volume setting and with a partly exhausted battery fitted (around 8 volts for a 9 volt radio and a little more than 5 volts for a 6 volt radio).

The only current drawn from BY1 is a momentary 9mA pulse when S1 is pressed and BY1 can, in consequence, be a small battery. A PP3 will be adequate.

The components in the circuit are quite small and some constructors may decide to assemble the timer as an integral part of the radio. In this instance, BY1 is not required and capacitor C1 can be charged from the radio battery as shown in Fig.4. The negative side of the radio battery is already connected to the negative terminal of C1, and it is merely necessary to connect the contact of S1 which is remote from C1 to the positive side of the radio battery. Using the radio battery in this way has the slight advantage that, as it ages, the voltage to which C1 is charged is reduced, and this will partly counteract the lengthening of the timing period caused by the reduced current in TR2. The charging voltage will, of course, be smaller if the radio uses a 6 volt battery, but it should still be possible to find a value for C1 which gives a satisfactory long period between the pressing of S1 and the turning off of the radio. ■

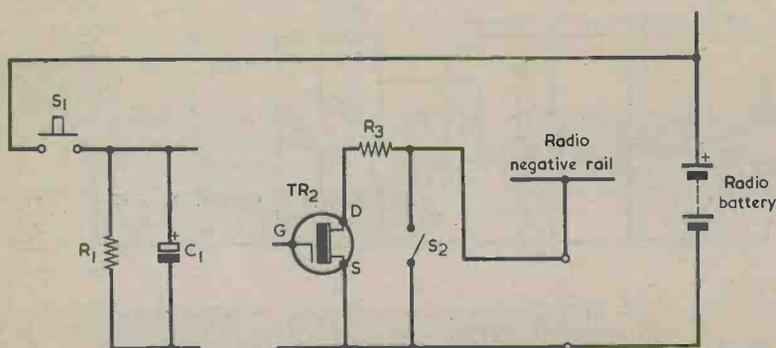



Fig.4. If desired, the timing circuit can be built into the radio. BY1 can then be dispensed with, and C1 can be charged from the radio battery itself.

in next month's

RADIO & ELECTRONICS CONSTRUCTOR

JULY 1981

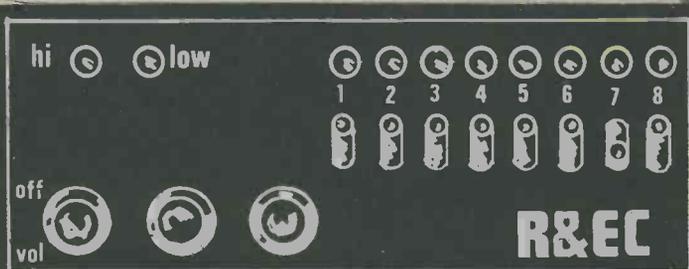UNIVERSAL 12 VOLT AUDIO AMP
designed for replacement purposes
in foreign car radios etc., and as a
useful workshop aid.



Build a **SCANNING VHF RECEIVER** covering
8 high channels &
8 low channels in the
30 — 200 MHz range.

LCD CLOCK/STOPWATCH
with **ALARM** and **DUAL**
TIME ZONE!

Runs for a year on a 1.5 cell



DESIGN IDEAS ■ ■ ■ ■

Practical Application Circuits
for use in your own
projects.



No 1 A real Buzz! Piezo — Acoustic Sounders.


◆ ◆ ◆ MICRO-LINK ◆ ◆ ◆

*THIS SERIES WILL ENABLE YOU TO
DEVELOP PRACTICAL CONTROL* ◆ ◆

*APPLICATIONS FOR MICROS INCLUDING
A SYNTHESISED RADIO AND PROBABLY*

◆ ◆ ◆ ◆ ◆ *THE WORLD'S MOST SOPHISTICATED*

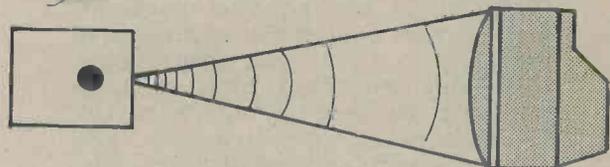◆ ◆ ◆ ◆ ◆ ◆ ◆ ◆ *WINDSCREEN-WIPER CONTROLLER* ◆ ◆ ◆ ◆



INFRA-RED REMOTE CONTROL
Cheap and Simple On-Off Switch

PLUS::: SPECIAL BOOK SELECTION
BOOK REVIEWS CB NEWS

and **MUCH MUCH MORE.....**

SCHMITT OSCILLATOR

By R. J. Caborn

Oscillation with negative feedback.

To make up an oscillator you normally need an amplifier with positive feedback from its output to its input. Some form of frequency-conscious filter is inserted in the feedback path and this controls the frequency at which oscillation takes place. A typical example is shown in Fig. 1(a), in which a parallel tuned circuit is connected between earth and the non-inverting input of the amplifier. A low value feedback capacitor, C_F , couples the output of the amplifier to the non-inverting input and, if the amplifier voltage gain and the feedback capacitance have reasonably practical values, the whole arrangement will oscillate sweetly at the resonant frequency of the tuned circuit.

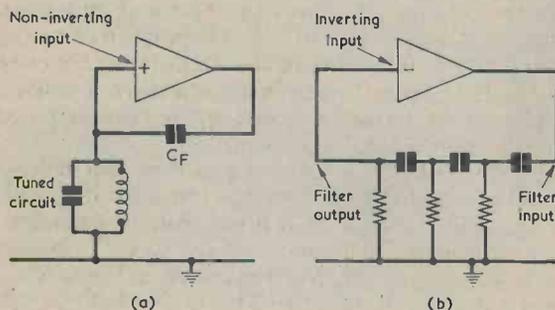


Fig. 1(a). A conventional oscillator incorporates an amplifier with positive feedback from its output to its input. A frequency-conscious filter is connected in the feedback loop. Here, the feedback is to a non-inverting input and the frequency is controlled by a parallel tuned circuit.

(b). In this phase shift oscillator circuit the feedback is to an inverting input. The feedback is still positive, nevertheless, because the three capacitors and resistors in the filter produce a phase shift of 180 degrees at the oscillator frequency.

POSITIVE FEEDBACK

Oscillation occurs because of the positive feedback given by C_F . When the non-inverting input of the amplifier goes positive so also, by a greater amount, does the amplifier output. So, any losses in the tuned circuit are overcome by the voltage gain of the amplifier and the circuit goes into oscillation.

There is positive feedback in the phase shift oscillator of Fig. 1(b), even though the amplifier output is this time coupled back to an inverting input. When that inverting input goes positive the amplifier output goes negative, by a larger amount. How does the circuit oscillate? It does so because there is a frequency at which, due to phase shifts in the feedback filter, the output of the filter is 180 degrees out of phase with the filter input. In other words, the filter output is exactly out of phase with its input. Thus, at the oscillation frequency there is a phase reversal in the amplifier and another compensatory phase reversal in the filter.

What about an oscillator using the circuit of Fig. 2?

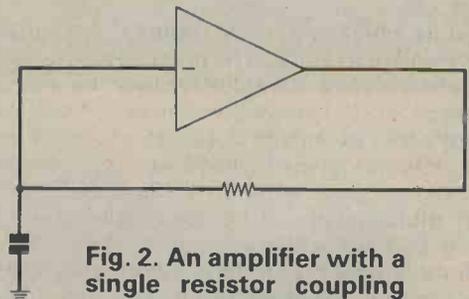


Fig. 2. An amplifier with a single resistor coupling back to an inverting input. A linear amplifier will not oscillate in this circuit, but an amplifier with a Schmitt characteristic will.

Here we have an amplifier output connecting back to an inverting input via a single resistor, with a single capacitor coupling that input to earth. Such an oscillator could not possibly work if the amplifier were an ordinary type because the feedback cannot help but be negative. On the other hand, the oscillator will work very well if the amplifier has a Schmitt input characteristic.

Fig. 3 shows a t.t.l. device type 74132, which has four Schmitt NAND gates. If we take one of the Schmitt

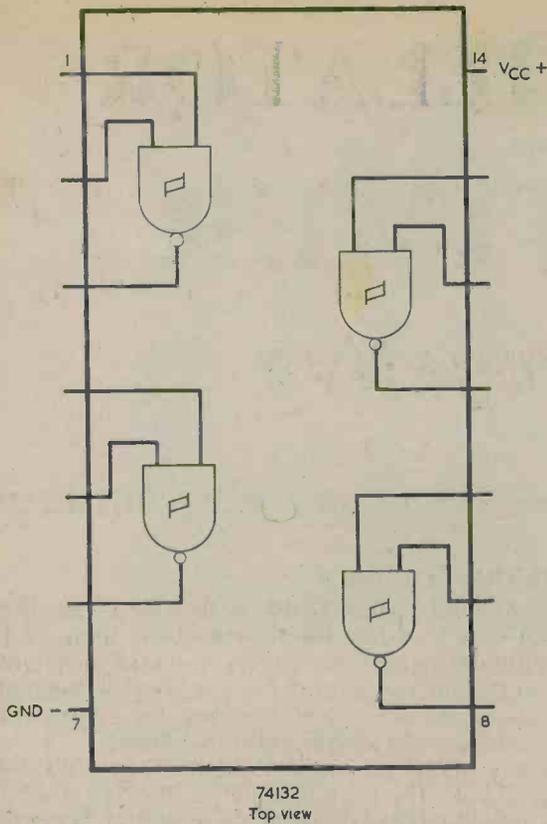


Fig. 3. The four Schmitt NAND gates in a 74132 t.t.l. chip.

NAND gates, strap its two inputs together to make it an inverter and connect these two inputs to the slider of a potentiometer connected across the supply rails we can examine its characteristic. The circuit is shown in Fig. 4 and, to be theoretically correct, the standing current in the potentiometer track must be significantly greater than the input current requirements of the gate.

We start with the potentiometer slider fully at the negative end of its track. The inverter output will then be high, i.e. positive. If we slowly move the slider up the potentiometer track we will arrive at an input voltage, with respect to the negative rail, at which the inverter output suddenly goes negative, or low. This voltage will be typically 1.7 volts. If we now slowly take the potentiometer slider back down the track to its negative end we will find that we have to take it considerably lower than the 1.7 volt level before the inverter output goes high again. This second voltage will be typically 0.9 volt.

PRACTICAL SCHMITT OSCILLATOR

A practical Schmitt oscillator using the 74132 NAND gate associated with pins 1, 2 and 3 is shown in Fig. 5. At switch-on C is discharged, whereupon the inverter input is low and the inverter output is high. The capacitor commences to charge via R until the voltage at the inverter input is sufficiently positive for the inverter output to go low. C next commences to discharge via R and the voltage across it falls. Because of the Schmitt action the voltage across C has to be considerably lower than the previous positive-going trigger voltage for the inverter output to go high again. And so the oscillation continues, with C alternately charging to the positive-going trigger voltage and discharging to the negative-going trigger voltage. The

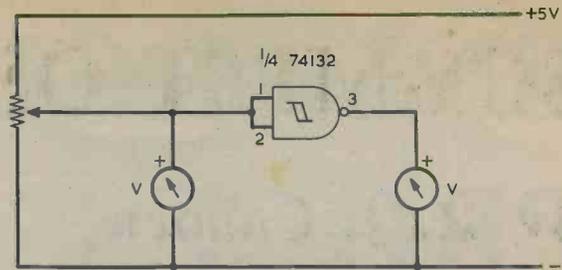


Fig. 4. Checking the input-output characteristic of a 74132 gate connected as an inverter. The two voltmeters monitor input and output voltage.

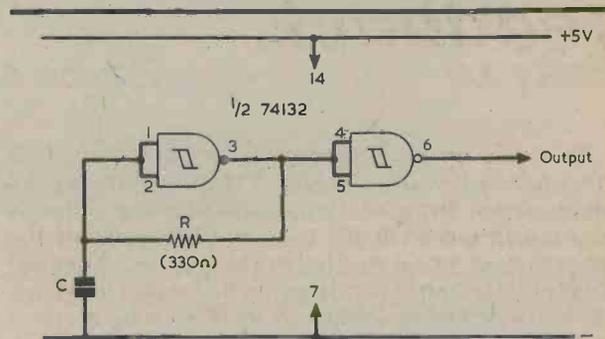


Fig. 5. A practical Schmitt oscillator. The second gate functions as a buffer amplifier. The units in the equation are Hertz and microfarads.

output of the inverter goes to a second Schmitt NAND gate which acts as a buffer amplifier. The output of the second gate can be loaded with all manner of t.t.l. circuitry without any effect on the oscillating gate.

The oscillator circuit of Fig. 5 is perfectly practical and has the full blessing of the manufacturers of the 74132. They specify that R should have a value of 330Ω, as is shown in Fig. 5, and say that the frequency range is from 0.1Hz to 10MHz.

The value of C? That's a bit experimental because, due to the wide tolerances on input characteristics with any t.t.l. NAND gate, it is impossible to calculate a precise value of capacitance for any given frequency. You'll find in practice that frequency, in Hertz is very approximately equal to 2,000 divided by the capacitance in microfarads. So if C is an electrolytic with a value of 2,000 μF (and there's no reason whatsoever why an electrolytic cannot be used in the circuit) you can expect the frequency of oscillation to be in the region of 1Hz. A 200μF capacitor will correspond to 10Hz, a 20μF capacitor to 100Hz, a 2μF capacitor to 1kHz and a 0.2μF capacitor (non-electrolytic now) to 10kHz. To get the oscillator to work at a specific frequency you start off with a capacitance approximately equal to the calculated figure. This will bring oscillator frequency close to the desired value. If the frequency is too high the value of C is experimentally increased, and if it is too low the capacitance is experimentally decreased.

An unusual feature of the oscillator is that if the capacitor is connected into circuit after switch-on of power the oscillator may not start. Similarly if, when the oscillator is running, the capacitor is temporarily disconnected and then reconnected the oscillator may stop and refuse to start until the power has been switched off and switched on again. ■

ENLARGER/ PROCESS TIMER

By Peter Roberts

Easy to use.

Gives accurate repeatable timings.

Long bright summer days – an ideal season for photography. Now you can ease the coming winter problems of the darkroom with the enlarger and process timer described here. The unit was designed for a photographer by the writer (who also has some interest in photography) and the following requirements have been incorporated.

1. To switch 'off' apparatus after required time lapse.
2. To switch 'on' apparatus after required time lapse.
3. Push-button start for easy darkroom operation and easy repeats without resetting dials.
4. Minutes/seconds selector with hours as optional extra.
5. Audible alarm to indicate end of process, with a 'disable' if not required.
6. Visible and Audible/'second' pulses allows full concentration on the enlarger whilst working.
7. Dial-up selection of process time or time-lapse easily visible in subdued light.
8. Manual override for focusing etc.
9. Can be positioned remote from enlarger to prevent vibration.
10. Can be used for other applications – 150 watts max. load.

Digital timers are not common, probably because of the extra cost involved, however such timers do have advantages. Pulses can be counted precisely, although the accuracy depends on the oscillator. Reading the setting on a thumbwheel switch is easier than finding a pointer on a dial, especially in the dark.

It was decided to use a relay to switch the load since this gives the option of switching the controlled apparatus 'on' or 'off' at the end of the selected interval. This option would not be so easy with thyristors or triacs. The relay contacts and mains switches are then the only limiting factors on the load which can be controlled.

Being a digital device, the circuit design is particularly easy and to simplify the drawings and the recognition of elements in the block diagram, the circuit has been drawn in sections. It should not be difficult to see how they fit together.

A printed circuit board has been designed for which copies of the track pattern and ready etched and drilled boards are available. The total parts cost is about £35.00, including the case and p.c.b. A cheaper version could be made by omitting those parts which provide facilities which are not required.

Fig. 1 shows the straight forward operation of the instrument. A 1 Hz oscillator applies pulses to two identical cascaded divide-by-sixty circuits thus producing 'seconds', 'minutes' and 'hours' pulses. These pulses are taken via a selector to the counter/detector circuit which operates the relay through the relay driver when the selected time has elapsed. The relay latches itself, resets the dividers and counter, stops the oscillator and controls the enlarger. When the 'start' button is pressed the relay releases, the oscillator starts and the sequence is repeated.


The 1 Hz oscillator (Fig. 2) uses a 555 timer ic. Both VR2 and VR3 are included so that a high degree of accuracy can be achieved for the long timing intervals. The writer has achieved an accuracy of 99.93% over 8 hours (for those interested the alarm sounded after 7 hrs. 59 mins. 40 seconds).

Both divide-by-sixty circuits are identical to that shown in Fig. 3. Each divider uses two 7490 counters, the first as a decade counter, the second resetting on the sixth pulse, to give a divide-by-sixty function overall.

The relay driver is a BC 107 or similar device (see Fig. 4). The diode across the relay coil absorbs any back-emf. The 10 μ F capacitor reduces the possibility of false relay operation due to 'sneak' pulses, noise or circuit transients. A positive – going voltage at the circuit input (on R4) causes the relay to operate and to latch over its own 'make' contact.

The 100 μ F capacitor causes the relay to operate immediately on first switch-on regardless of the setting of the selectors. The enlarger can be set up and the required time interval set on the selectors, then when the start button is pressed the relay releases and the selected time-lapse commences.

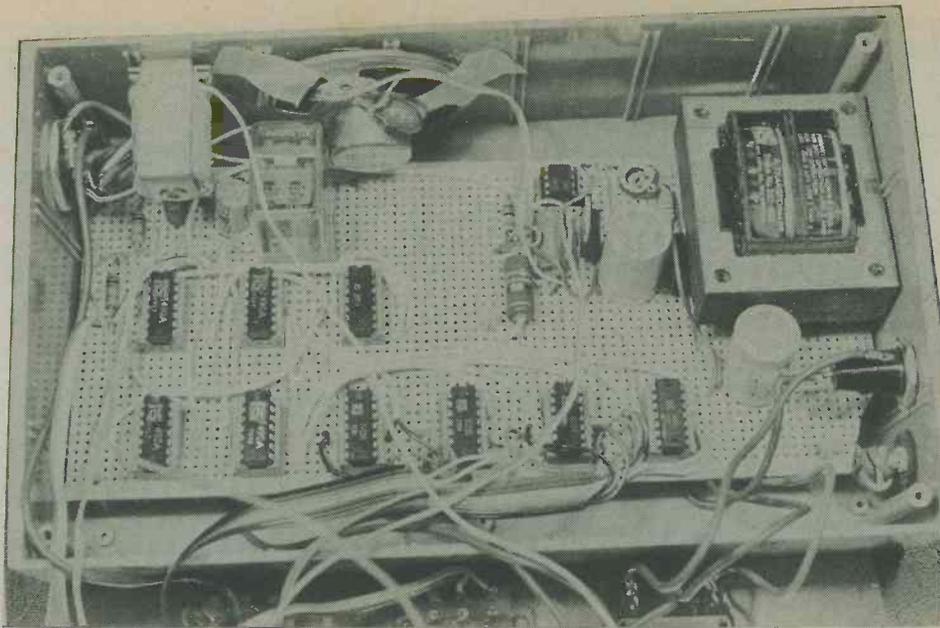The reset circuit is also derived from the relay contacts, but two gates from a 7400 are included in a bistable configuration to eliminate contact bounce which can give rise to inconsistent timings. The 1 μ F capacitor ensures that the bistable is correctly set on switch-on.



Internal view of the prototype unit.

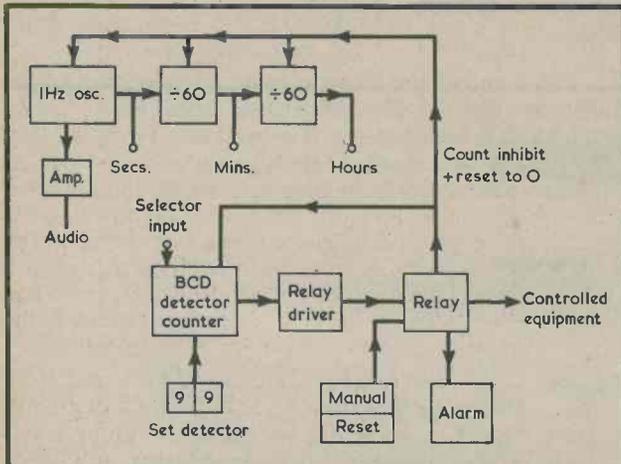


Fig. 1. Block diagram of enlarger/process timer.

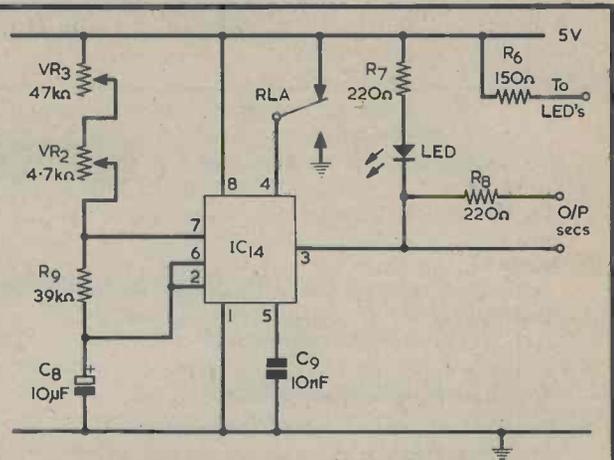


Fig. 2. 1 Hz oscillator. The Change-over contact is part of the output relay. VR3 and VR2 provide coarse and fine frequency adjustment.

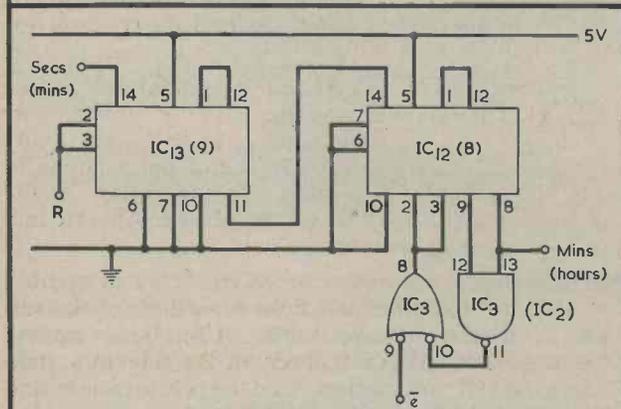


Fig. 3. Divide-by-60 circuit. This counter circuit is used twice. Once to derive a minutes count from a seconds input and also to derive an hours count from a minutes input.


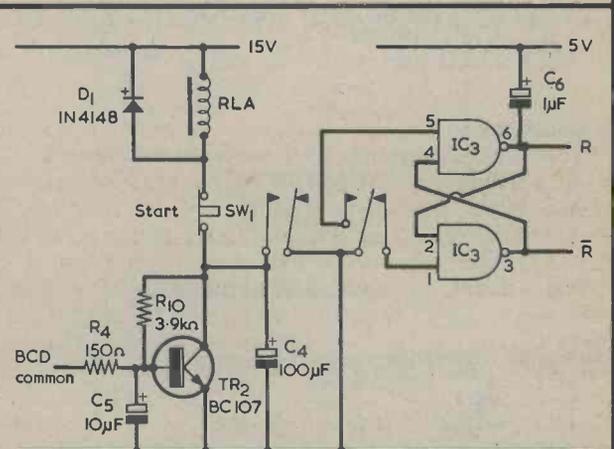


Fig. 4. Circuit of relay driver, latch and reset bistable. The two NAND gates in the bistable circuit are half of a 7400.

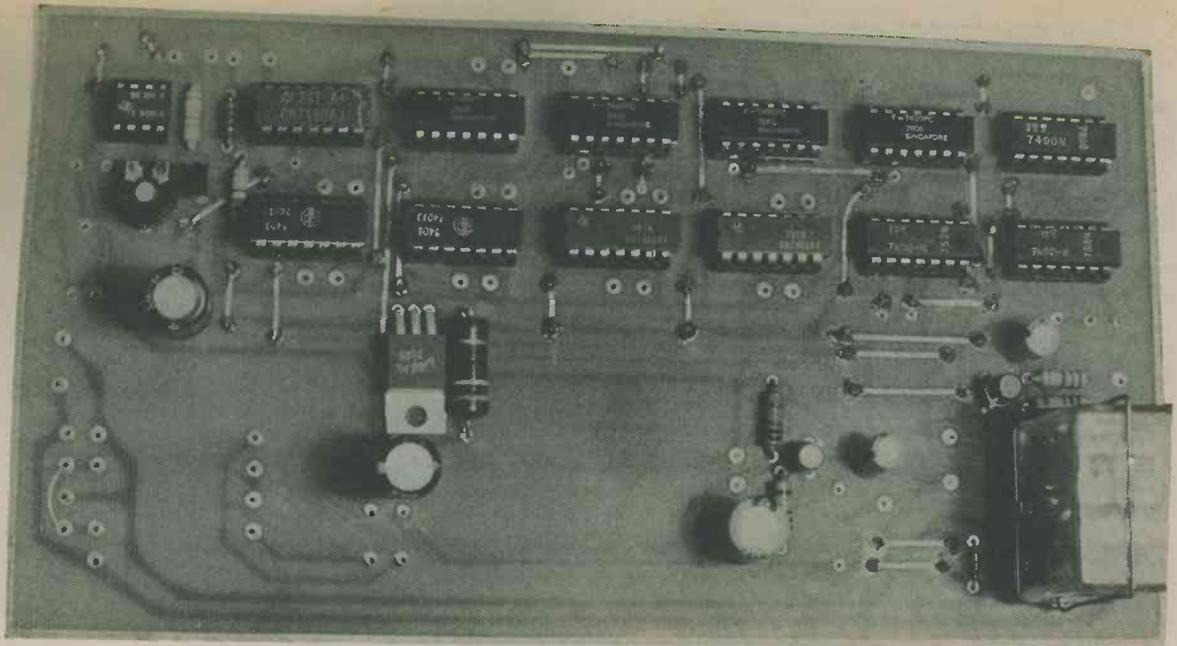

Photograph showing component layout using a pre-etched and drilled board.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 10% except where shown otherwise).

- R1 1.5K Ω or 1K Ω (not critical)
- R2 1K Ω
- R3 1K Ω or 500 Ω (not critical)
- R4 150 Ω
- R5 27 Ω 2 watt
- R6 150 Ω
- R7 220 Ω
- R8 220 Ω
- R9 39K Ω
- R10 3.9K Ω
- VR1 1K Ω preset
- VR2 4.7K Ω preset
- VR3 47K Ω preset

Capacitors

(All electrolytics are 15V working minimum)

- C1 100 μ F
- C2 10 μ F
- C3 470 μ F
- C4 100 μ F
- C5 10 μ F
- C6 1 μ F
- C7 470 μ F
- C8 10 μ F
- C9 0.01 μ F (10nF)

Integrated circuits

- IC1 +5V Regulator
- IC2 7400
- IC3 7400
- IC4 7403
- IC5 7403
- IC6 7403
- IC7 7403
- IC8 7490
- IC9 7490
- IC10 7490
- IC11 7490
- IC12 7490
- IC13 7490
- IC14 NE 555 or similar

Transistors

- TR1 BC107 or similar
- TR2 BC107 or similar

Diodes

- D1 IN914 or IN4148
- BD1 50V 1 Amp bridge rectifier.
- I.e.d. 3 high brightness 0.2" or suitable

Switches

- SW1 Push to break
- SW2 Single pole change-over slide
- SW3 Single pole miniature toggle
- SW4 Single pole miniature slide
- SW5 Mains neon rocker switch, single pole
- BCD Thumbwheel switches (2 off) R.S. Components type 338-399 or similar.

Selector switches: Single pole change-over slide switch. Double pole change-over slide switch or, one only, 2-pole 3-position rotary switch.

Miscellaneous

Relay, 'Continental' style 4 pole changeover, 12V nominal. Transformer, R.S. Components type 207-740 6VA 0-6, 0-6V. PCB ready prepared from WGR Enterprises Ltd., 64 Purford Green, Harlow, Essex, CM18 6HN.

Loudspeaker 8 Ω miniature.
Fuse holder to suit 20 mm mains fuse.
Buzzer 240V a.c. type
Case to suit location and application.
Nuts, bolts, wire etc.

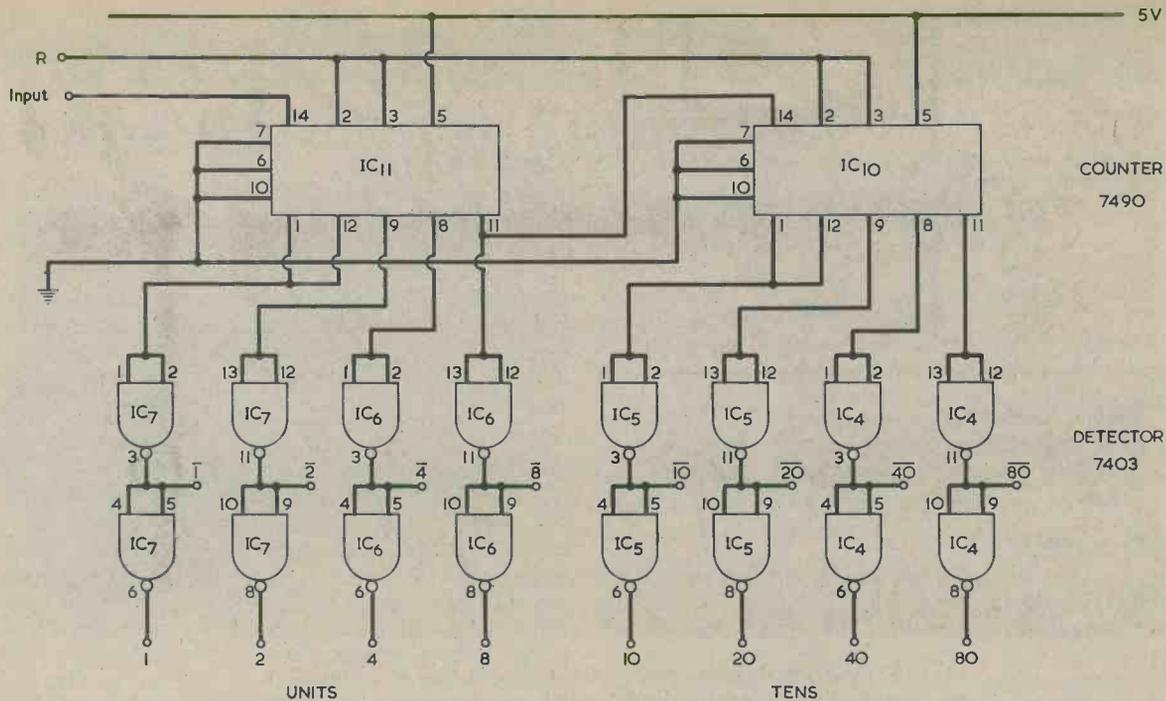


Fig. 5. Tens and Units counter and NAND gate detector circuits. This section is driven from the 'seconds' output, 'minutes' output or 'hours' output of Fig. 1 via a seconds, minutes or hours selector switch. The outputs of the NAND gates connect directly to the appropriate inputs on the BCD switch.

The hard work is done by the detector counter shown in Fig. 5. The counter consists of two 7490 decade counters with binary outputs of weightings 1, 2, 4 and 8. The inverse functions 1, 2, 4 and 8 are also generated by the detector section. The eight outputs from each of these two detector circuits are then taken to the appropriate eight inputs on the two thumbwheel switches. Thus we have two thumbwheel switches, one for units count and one for tens count.

By suitable switching we can choose to drive the counter input (see Fig. 5) from the seconds, minutes or hours pulse sources shown in Fig. 1, allowing timings of 0 to 99 seconds, 0 to 99 minutes or 0 to 99 hours using just these two thumbwheel switches and a selector switch.

The outputs from the thumbwheel switches are called 'common' and both these outputs are connected to the 'BCD common' input at R4 in the relay driver circuit (see Fig. 4.). When the correct number of tens and units of pulses from the selected seconds, minutes or hours source have been counted then the relay is energised to mark the end of the elapsed time.

The more technically minded reader may care to note that 7403 type open-collector NAND gates are used in the detector circuits rather than the more usual 7400 type totem-pole output NAND gates since the action of the BCD switch is such that these outputs can be commoned together in a wired-OR fashion. In this application the totem-pole outputs could self-destruct!

POWER SUPPLY

The power supply (Fig. 6) is a standard full wave bridge rectifier/smoothed circuit supplying +15V for the relay and audio amplifier and +5V for the logic circuits. The 27Ω 2 watt resistor takes most of the power which would otherwise be dissipated in the 5V regulator.

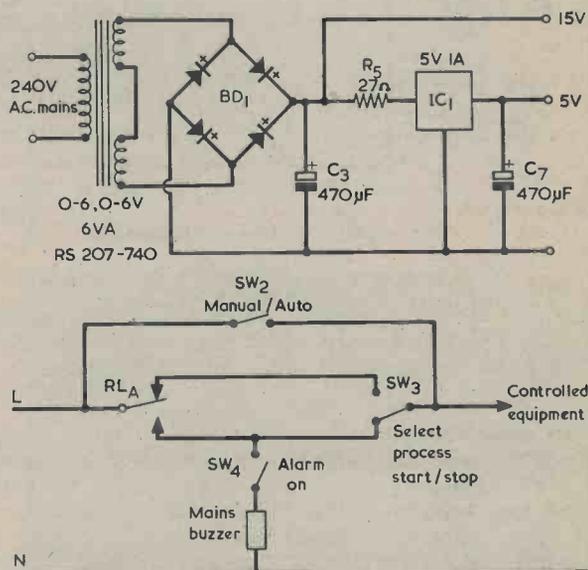



Fig. 6. Circuit of power supply and load switching arrangement.

New Products

For the Computer Enthusiast



High quality cassette deck for minis

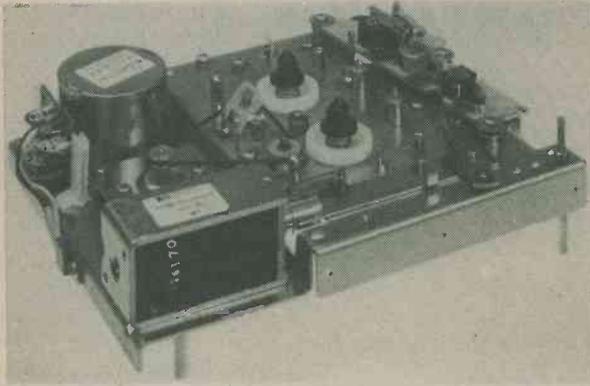

The C1000 from Monolith Electronics, a new low cost, high quality cassette tape deck for minis.

A new, low cost, high quality cassette tape deck, the C1000, has been introduced by Monolith Electronics, 5/7 Church Street, Crewkerne, Somerset. Aimed at the home mini-computer enthusiast, the C1000 is a development of Monolith's proven C2000 series tape transports which are widely used in industrial process control, data logging and computer

applications. It can be operated either remotely or locally via the control circuitry.

The C1000 is designed around the international compact cassette and consists of two motors (capstan and spooling), head plate and solenoid. It operates from a nominal 12V d.c. supply.

The basic control circuitry allows remote or local selection of fast forward, fast rewind, record and play. A Hall effect sensor and an opto end of tape sensor are optional extras to the control circuit and are supplied separately.

The Hall effect sensor can serve two functions viz. detection of tape motion and breakage of tape and also as a tape spool rotation counter. The device senses motion of the supply tape spool and delivers four pulses for each revolution of the spool.

The opto device is designed primarily for use with high speed tapes fitted with coded windows (available from Monolith).

The main motor, which is electronically speed controlled, drives the capstan. As supplied, the deck operates at the standard tape speed of 1 7/8 in/sec (4.76 cm/sec) but with a slight modification to the circuit this can be made variable over the range 2.4 cm/sec to 9.5 cm/sec – approximately 15/16 in/sec to 3 3/4 in/sec. Wow and flutter are typically 1.15% r.m.s. (DIN 45507). The C1000 is 180mm long x 145mm wide x 60mm tall, and weighs 1.4kg (3.1 lbs). Prices (inc. VAT) are: C1000 main unit £42.49, Opto sensor £13.80, Hall effect unit £5.75.

Valuable accessory for personal computers

Model 4881 GPIB Analyser announced by WASEC is an invaluable accessory for all personal computers which use the IEEE 488 bus for peripheral interconnection. With Talker, Listener and Controller capabilities the model 4881 facilitates development, investigation and troubleshooting of systems incorporating GPIB compatible processors such as the ABC80, Apple, Commodore PET, Hewlett Packard HP85 and Research Machines 380Z.


16 LED's monitor the GPIB signals with individual switch control over each line. Using the Single Step Listener facility the model 4881 can display system activity allowing the user to check through each Bus transaction one at a time. Alternatively, as a Talker, the Analyser can output switch selected data bytes to a Listener either in a continuous or a Single Step mode.

As a Controller model 4881 can send Bus Commands and control the Bus management signals ATN, EOI, SRQ, REN and IFC. This permits complete tests to be made on Bus Systems at a simple level prior to attempting to run complex Bus programmes.

Model 4881 is fully portable, self contained and is powered from any 240v. 50Hz. supply. A top-of-

panel GPIB connector facilitates easy CRO monitoring of Bus signals and a simple adaptor affords connection to the IEC 625.1 Instrumentation Bus.

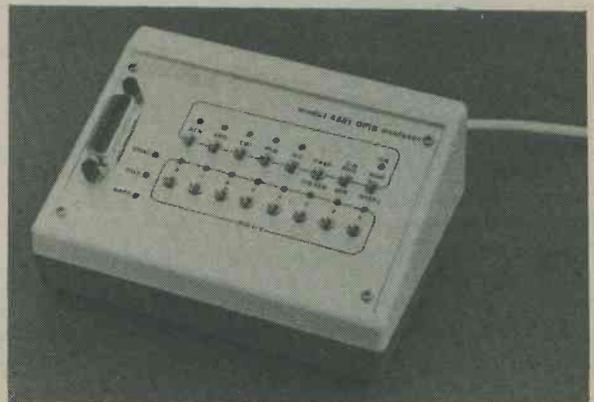For further information write to:- Sales Department, WASEC, 45 Hurstcourt Road, Sutton, Surrey SM1 3JF.



Proximity Lamp Switch

By R.A. Penfold

No fumbling in the dark for manual switches.

Proximity of hand turns lamp on.


This project is a proximity switch which can be used to turn on a bedside lamp by placing a hand on the insulated case of the unit. Switches of this type are often incorporated in clock-radios intended for bedside use, and it was the convenience of using one of these which led to the present design.

OPERATING PRINCIPLE

The block diagram of Fig. 1 shows the various stages of the circuit and the way they interconnect. A metal sensor plate is positioned near a strong source of mains hum (a mains transformer) and the 50Hz hum signal picked up in the plate is fed via a buffer stage to a high gain amplifier. The output from this is rectified and passed to a latching relay driver stage.

If the input signal level to the latching stage is high enough it triggers and energises the relay, which in turn switches on the lamp. The circuit is adjusted so that under normal conditions the input signal to the latching stage is just too small to produce triggering.

If a person's hand is held near without actually touching the sensor plate, hum picked up in the person's body is capacitively coupled to the plate. Although the coupling capacitance will be extremely low and the frequency involved, at 50Hz, is also low, the high input impedance of the buffer amplifier ensures that a significant amount of additional hum signal is coupled to the plate. This increases the input signal to the latching stage, causing the latter to be triggered and the lamp to be turned on. The unit can be returned to the off state by briefly pressing the reset button.

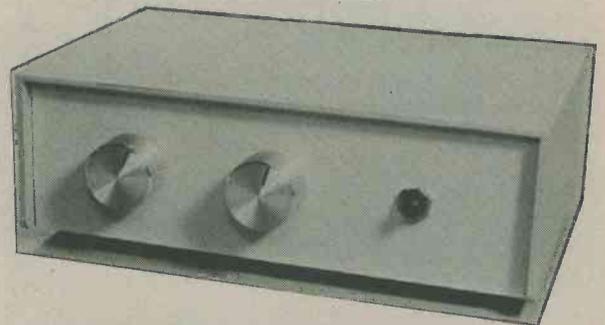

The proximity lamp switch circuitry is housed in an all-plastic case. Placing a hand on the insulated lid of the case switches on the lamp.

THE CIRCUIT

The complete circuit of the proximity switch appears in Fig. 2.

Power for the electronics is given by mains transformer T1 and the full wave rectifier circuit incorporating D1, D2 and C1. It is essential that the buffer and voltage amplifier stages have a supply with a low ripple content, as the input signal could otherwise be swamped by hum on the supply rails. Additional smoothing for these two stages is given by R6 and C7. S2(a)(b) is the main on-off switch. Fuse FS1 in the rectifier circuit gives protection against damage due to circuit faults. Its rating is somewhat higher than the secondary current rating of T1 but it is a quick-blow type which will blow rapidly in the event of excessive current.

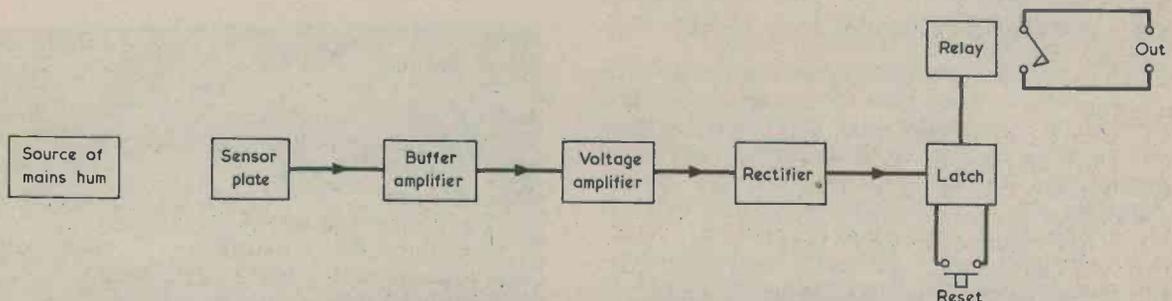


Fig. 1. Stage line-up of the proximity switch. The mains hum picked up by the sensor plate is amplified, rectified and fed to the latch. Placing a hand near the sensor plate increases the hum level, triggers the latch to its alternate state and causes the relay to energise.

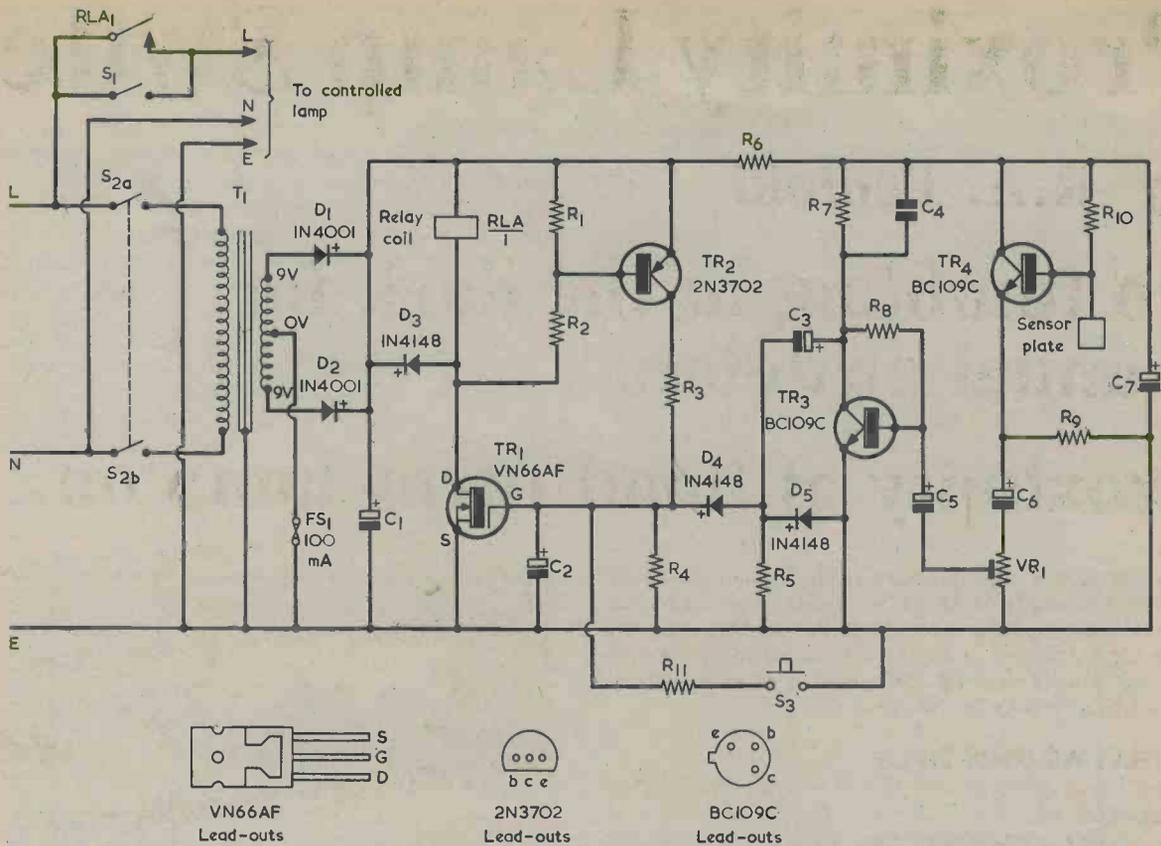


Fig. 2. The circuit of the switch. TR4 is the input buffer amplifier and TR3 the voltage amplifier. TR1 and TR2 are in the latching circuit and TR1 controls the relay.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated).

- R1 4.7k Ω
- R2 22k Ω
- R3 22k Ω
- R4 39k Ω
- R5 56k Ω
- R6 560 Ω
- R7 4.7k Ω
- R8 2.7M Ω 10%
- R9 4.7k Ω
- R10 1.8M Ω 10%
- R11 12 Ω
- VR1 10k Ω pre-set potentiometer, 0.1 watt, horizontal

Capacitors

- C1 100 μ F electrolytic, 16V. Wkg.
- C2 15 μ F electrolytic, 16V. Wkg.
- C3 1 μ F electrolytic, 16V. Wkg.
- C4 0.22 μ F polyester, type C280
- C5 2.2 μ F electrolytic, 16V. Wkg.
- C6 1 μ F electrolytic, 16V. Wkg.
- C7 100 μ F electrolytic, 16V. Wkg.

Transformer

- T1 sub-miniature mains transformer, secondary 9-0-9V at 67mA.

Semiconductors

- TR1 VN66AF
- TR2 2N3702
- TR3 BC109C
- TR4 BC109C
- D1 1N4001
- D2 1N4001
- D3 1N4148
- D4 1N4148
- D5 1N4148

Switches

- S1 s.p.s.t. rotary mains toggle
- S2(a)(b) d.p.s.t. rotary mains toggle
- S3 press-button, push to make

Relay

- RLA see text

Fuse

- FS1 100mA quick-blow cartridge fuse 20mm.

Miscellaneous

- Plastic case (see text)
- Veroboard, 0.1in. matrix
- Chassis-mounting fuseholder, 20mm.
- 2 control knobs
- Aluminium sheet (for sensor)
- 3-core mains wire
- Nuts, bolts, wire, etc.

TR4 is in the buffer stage, and is connected as a simple emitter follower. There is a high input impedance at its base, to which the sensor plate connects directly. TR1 output is coupled by C6 to VR1, a variable attenuator, the slider of which connects to the base of voltage amplifier TR3 through C5. This is a conventional common emitter amplifier, and its output couples via C3 to the rectifier comprising D4 and D5. The amplified and rectified hum signal takes the gate of TR1 positive, and the hum pulses are smoothed by C2.

C2 is not essential for triggering of the latching circuit and is included to improve reliability. It was omitted from the circuit during initial design work, and it was found that the lamp tended to frequently switch itself on! The problem was found to be due to large noise spikes on the mains supply (of which there are a great many in most areas these days). C2 helps to prevent these transients giving false triggering,

since the brief spikes have little charging effect and are absorbed by the capacitor. The much longer 50Hz hum pulses charge C2 up to virtually their peak amplitude.

Due to their short duration, the mains noise spikes consist largely of high frequencies. C4 gives further protection against false triggering by reducing amplifier gain at frequencies higher than 50Hz. When C2 and C4 had been added to the circuit there were no further problems with spurious triggering, and all attempts to purposely cause such triggering failed.

TR1 and TR2 form the latching circuit. In the standby condition there is insufficient gate bias to cause TR1 to pass a sufficient drain current. With the resultant low voltage across the relay coil, TR2 is cut off. When the rectified hum voltage at TR1 gate increases, due to a hand being placed near the sensor, TR1 drain current increases and TR2 starts to turn on. Its collector current, through current limiting



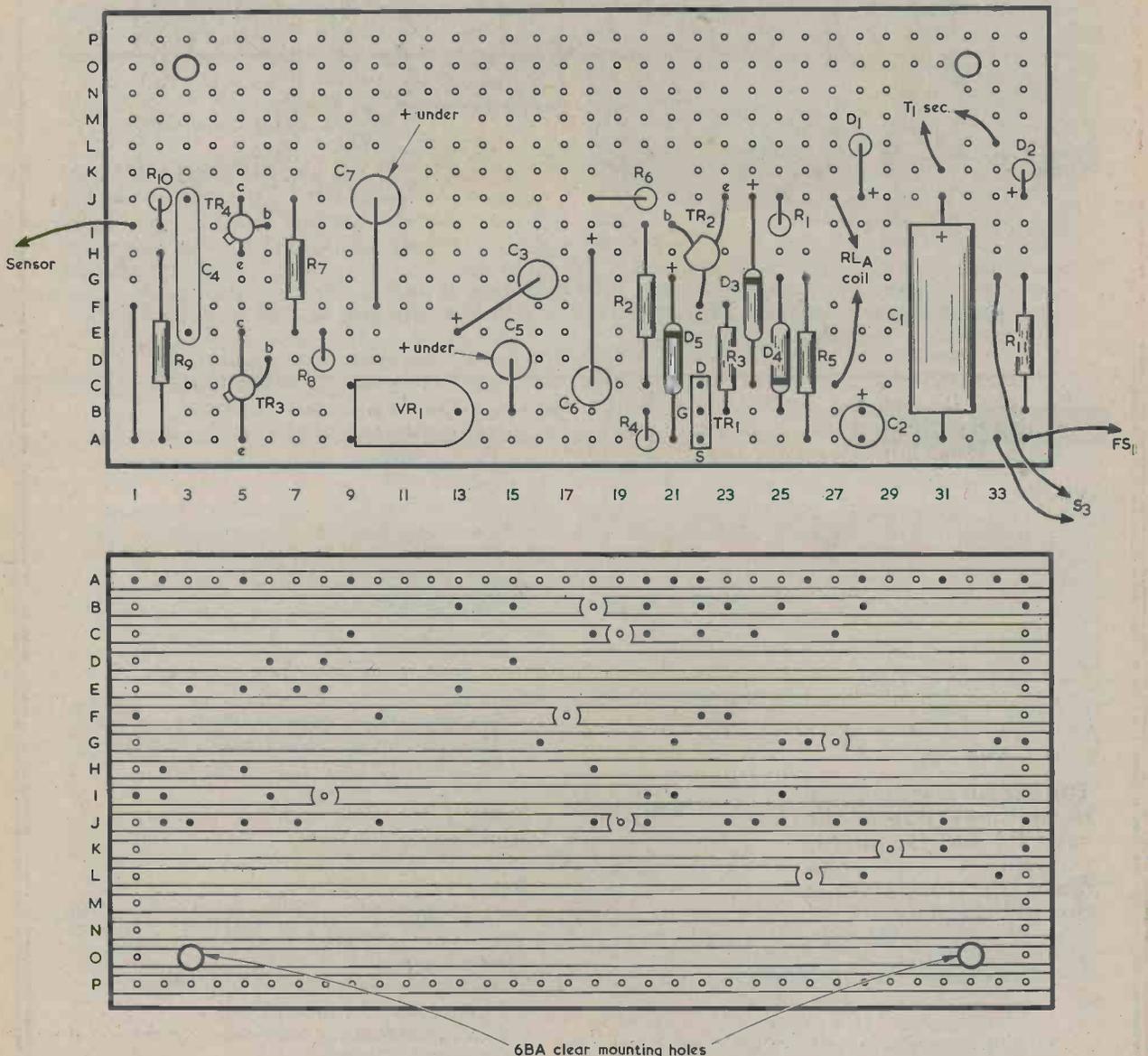


Fig. 3. The Veroboard assembly. After the board has been cut out the two mounting holes are drilled. Next, the breaks in the strips are made and then the components are soldered in position.

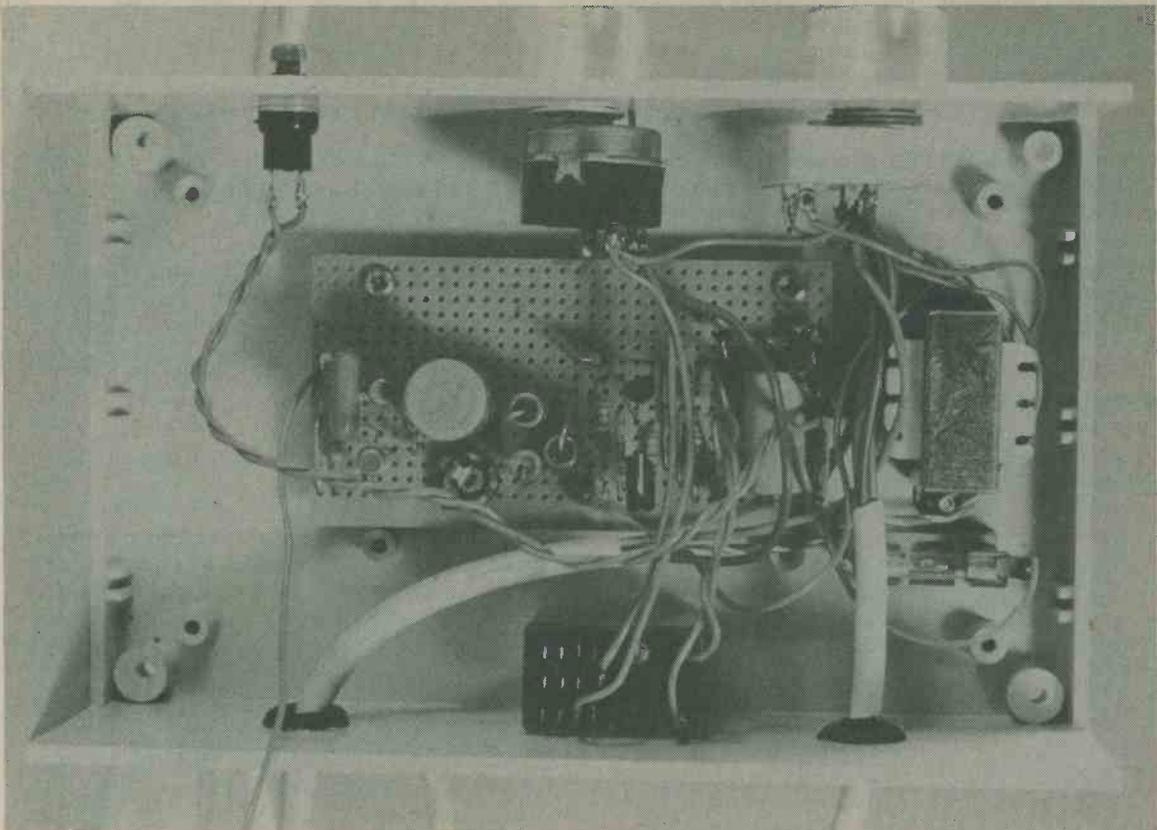

Internal layout inside the case. The mains transformer and fuseholder are positioned at one end of the case. The Veroboard assembly is positioned so that D 1 and D 2, mounted on the board, are close to the transformer. (NB constructors should use 'strain relief' grommets for mains wiring – or at least knot the cable inside the box).

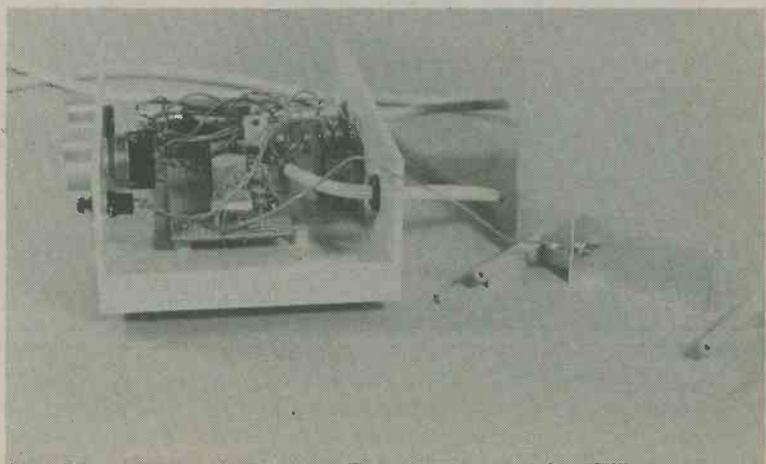The sensor plate is glued to the underside of the case lid and is roughly positioned over the mains transformer when the lid is in place.



resistor R3, causes the gate of TR1 to go more positive and the relay energises. Virtually the full supply potential appears across the relay coil and both TR1 and TR2 are turned hard on. The circuit now remains latched in this state. It can be returned to its previous state by pressing the reset switch S3. This reduces TR1 gate voltage to almost zero, whereupon both transistors turn off and the relay de-energises. D3 is the usual protective diode which prevents the formation of high back-e.m.f. voltages across the relay coil when it releases.

Two make contacts of the relay switch on the bedside lamp when the relay energises. S1 can be used to bypass these contacts so that the lamp can be switched on and off in the normal manner, if desired.

COMPONENTS

The relay should have a coil resistance of 185Ω or more with at least one make contact set of adequate rating for mains voltages. It should energise reliably at around 9 volts. The prototype employed a miniature plastic cased type having four changeover contact sets. As with many relays this had no provision for chassis mounting and it was glued to the rear panel of the case with an epoxy adhesive. Other means of mounting the particular relay to be employed can also be devised.

The low value electrolytic capacitors, C3, C5 and C6, are specified in the Components List as having working voltages of 16 volts. In practice it will be found difficult to obtain those components with this low working voltage and it will be quite in order to use capacitors having a much higher working voltage, such as 63 volts. The transistor specified for TR1 and the mains transformer are both available from Maplin Electronic Supplies. Any all-plastic case that will comfortably accommodate all the components can be used, the smallest suitable size being about 150 by 100 by 50mm.

CONSTRUCTION

Two holes are required in the rear panel of the case. Through one of these passes a 3-core mains input lead and through the other passes a 3-core output lead connecting to the bedside lamp. Each lead should be secured inside the case with a plastic or a plastic-faced clamp. The three switches are mounted on the front panel, S2 being to the left, S1 central, and S3 to the right. The mains transformer and the fuseholder are positioned to the left of the case, making sure that sufficient space is left for the component panel and the relay.

Details of the component panel are given in Fig.3. This is a piece of Veroboard of 0.1in. matrix having 16 copper strips by 34 holes. TR1 has a built-in zener protection diode and does not need any special handling precautions. The wiring external to the board is illustrated in Fig. 4.

The sensor plate merely consists of a piece of aluminium sheet of around 16 to 22 s.w.g., measuring about 60 by 25mm. A small flange about 8 to 10mm deep is bent at right angles at one end. A solder tag is bolted to this flange and this provides the connection for the input lead from the component panel. The plate is glued to the underside of the case lid so that it will be positioned roughly above T1 when the lid is fitted in place. The exact positioning of the plate is not critical, but it should not be too far away from T1 as there might then be insufficient pick-up of the mains hum signal.

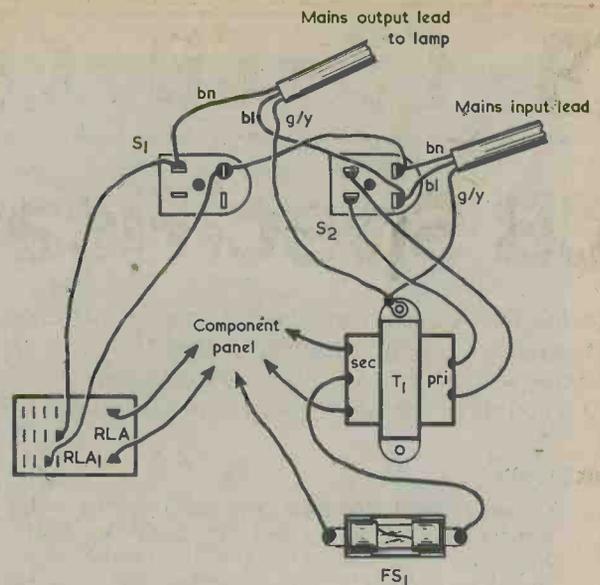


Fig.4. Wiring to the component panel. Two wires from S1 connect to a make contact set on the relay. Confirm the tags of S1 and S2 with a continuity tester before wiring to these switches. Not shown is S3, which simply connects to the two appropriate wires from the component panel.

ADJUSTMENT

One method of giving VR1 the correct setting is to stand with it fully backed-off (slider fully clockwise) and then advance it slowly until the relay energises. The potentiometer is then backed-off slightly to a setting which gives reliable operation. With this method the sensor plate has to be in its normal position, since the correct setting for VR1 varies according to the position of the plate. Access to VR1 can be obtained by drilling a small hole in the case lid directly above VR1.

Alternatively, since the adjustment of VR1 is a once-and-for-all operation, it can simply be adjusted by trial and error with the case lid being removed for the adjustment and then replaced. Whatever method is chosen, do not be tempted to adjust VR1 for the highest possible sensitivity. Instead, adjust the potentiometer down to the lowest setting which gives good results. There should then be no problems whatsoever with noise spikes on the mains causing spurious triggering. When adjusting VR1 by the second method, always remember that the mains supply is present at the rotary switches and the relay contacts, and take all precautions against accidental shock. The unit should not then be subsequently used without the case lid firmly secured in place.

Although the design is presented here as a light switch, it can of course be used to control other items of equipment provided that the relay contact ratings are not exceeded. It can also be used to switch a circuit off instead of on, and this is achieved by using a relay break contact set instead of a make contact set.



CB Specification at last...

Herewith an edited abstract from the official word LMSC/CB1 24th April. R&EC brings you this information on the understanding that this is the full and final specification, and that the frequencies, power and mode is not subject to any further discussion. But we cannot accept any responsibility for any errors and omissions that may have slipped through.

Foreward

1. Citizen's Band Radio, a personal two-way radio system, is available for use throughout the United Kingdom. It operates in the 27 MHz waveband and the 930 waveband.
 2. The Wireless Telegraphy Act 1949 provides that no radio equipment may be installed or used except under the authority of the Secretary of State. All citizens band radio equipment whether hand held, mobile or base station, must be covered by a licence; it is a condition of this that the apparatus fulfils, and is maintained to, certain minimum technical standards. This specification sets out these standards for 27MHz FM equipment; 934MHz FM equipment is subject to a separate specification.
 3. The manufacturer, assembler or importer of citizens band equipment is responsible for ensuring that the apparatus conforms with the specification; and any additional requirements imposed by regulations under the Wireless Telegraphy Act 1949. Conformity with the required standards may be established by tests carried out by the manufacturer, assembler or importer, or by a reputable test establishment acting on his behalf, but in either case conformity with the specification will remain the responsibility of the manufacturer, assembler or importer.
- 27MHz band equipment.

1. GENERAL

1.1 Scope of Specification

This specification covers the minimum performance requirements for frequency modulated radio equipments, comprising base station, mobile and hand held transmitters and receivers or receivers only and additionally any accessories e.g. attenuators, power amplifiers, vehicle adaptors for optional use with the above for use in the Citizens Band Radio service.

For all equipments covered by this specification, the nominal separation between adjacent channel carrier frequencies is 10kHz.

1.2. Permitted Effective Radiated Power

The output radio frequency power of the equipment is limited to 4W. With antenna permitted for use with the equipment this gives an effective radiated power of 2W.

If an antenna is mounted at a height exceeding 7m the licence will require a reduction in transmitter power of 10dB.

To enable the use to accomplish this easily the equipment manufacturer should provide as a standard accessory an attenuator or low power switch having a nominal attenuation of 10dB, which may be purchased by the licensee.

1.3. Operating Frequencies

The equipment shall provide for transmission and reception only of the frequency modulated emissions on one or more of the following radio frequency channels.

Channel 1	27.60125 MHz	Channel 21	27.80125 MHz
Channel 2	27.61125 MHz	Channel 22	27.81125 MHz
Channel 3	27.62125 MHz	Channel 23	27.82125 MHz
Channel 4	27.63125 MHz	Channel 24	27.83125 MHz
Channel 5	27.64125 MHz	Channel 25	27.84125 MHz
Channel 6	27.65125 MHz	Channel 26	27.85125 MHz
Channel 7	27.66125 MHz	Channel 27	27.86125 MHz
Channel 8	27.67125 MHz	Channel 28	27.87125 MHz
Channel 9	27.68125 MHz	Channel 29	27.88125 MHz
Channel 10	27.69125 MHz	Channel 30	27.89125 MHz
Channel 11	27.70125 MHz	Channel 31	27.90125 MHz
Channel 12	27.71125 MHz	Channel 32	27.91125 MHz
Channel 13	27.72125 MHz	Channel 33	27.92125 MHz
Channel 14	27.73125 MHz	Channel 34	27.93125 MHz
Channel 15	27.74125 MHz	Channel 35	27.94125 MHz
Channel 16	27.75125 MHz	Channel 36	27.95125 MHz
Channel 17	27.76125 MHz	Channel 37	27.96125 MHz
Channel 18	27.77125 MHz	Channel 38	27.97125 MHz
Channel 19	27.78125 MHz	Channel 39	27.98125 MHz
Channel 20	27.79125 MHz	Channel 40	27.99125 MHz



Citizens Band Radio equipment shall not contain facilities for transmission of radio frequencies other than those listed above, and those contained in the specification for 934MHz band equipment. Single channel equipment may be tested on any one of the approved channels. Multi-channel equipment shall be equipped to operate at the centre, and the upper and lower limits of the frequency range over which channel switching is possible.

1.4. Permitted Modulation

Only equipment which employs frequency or phase modulation and has no facilities for any other form of modulation will meet the requirements of this specification.

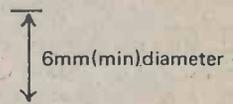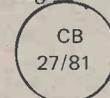1.6. Certificate of Compliance

Compliance with this specification shall be indicated by an authorised mark stamped or engraved on the front panel of the equipment. The mark used to indicate compliance shall be as shown in Fig.1.



Letter & Figure Height NOT less than 1mm

Figure 1

3. ELECTRICAL TEST CONDITIONS

3.1. Transmitter Artificial Load

Tests on the transmitter shall be carried out using a 50 ohm non-reactive, non-radiating load connected to the antenna terminals. If necessary an impedance matching device may be used for testing.

3.3. Test Site

The test site shall be located on a surface or ground which is reasonably level. At one point of the site, a ground plane of at least 5 metres diameter shall be provided. In the middle of this ground plane, a non-conducting support, capable of rotation through 360 degrees in the horizontal plane shall be used to support the test sample 1.5 metres above the ground plane.

The test site shall be large enough to allow the erection of a measuring or transmitting antenna at a distance from the test sample of not less than half the wavelength corresponding to the lowest frequency to be considered.

The distance actually used shall be recorded with the results of the tests carried out on the site. Sufficient precautions shall be taken to ensure that reflections from extraneous objects to adjacent to the site and ground reflections do not degrade the measurements.

3.3.3 Substitution Antenna

The substitution antenna shall be a half wave dipole resonant at the frequency under consideration, or a shortened dipole, calibrated against the half wave dipole. The centre of this antenna shall coincide with the reference point of the test sample it has replaced. This reference point shall be the point at which the external antenna is connected.

The distance between the lower extremity of the dipole and the ground shall be at least 0.3m.

The substitution antenna shall be connected to a calibrated signal generator when the site is used for radiation measurements.

The signal generator and the receiver shall be operating at the frequencies under investigation and shall be connected through suitable matching and balancing networks.

3.4. Normal Test Modulation

Where stated, the transmitter shall have normal test modulation as follows:

The modulation frequency shall be 1 kHz and the resulting frequency deviation shall be 60% of the maximum permissible frequency deviation (Clause 4.3.1.).

4. TRANSMITTER

4.1. Frequency Error

4.1.3. Limits

The frequency error, under both normal and extreme test conditions, or at any intermediate condition, shall not exceed ± 1.5 kHz. If — for determining the transmitter frequency — use is made of a synthesizer and/or a phase-locked loop system, the transmitter shall be inhibited when synchronisation is absent.

4.2. Carrier Power

The equipment manufacturer should provide as a standard accessory an attenuator having a nominal attenuation of 10dB, which may be purchased by the licensee. This attenuator is for insertion, where necessary, between the transmitter output and the antenna terminals of the equipment, a removable link may be necessary.

4.2.1. Definition

For the purpose of this specification: the carrier power shall be the value of the power of an unmodulated carrier at the output terminals of a transmitter. For equipment with an integral antenna, it is the maximum value of effective radiated power of an unmodulated carrier. The rated output power is the maximum value of the transmitter output declared by the manufacturer, at which all the requirements of this specification are met.

4.2.2. Method of Measurement (Terminal Power)

- a) The transmitter shall be connected to a test load equal to the impedance for which it was designed.
- b) With the transmitter operating without modulation in accordance with the manufacturers' instructions, the power delivered to the test load shall be measured.
- c) The measurement shall be made under normal test conditions (Clause 2.3.) and repeated under extreme test conditions Clauses 2.4.1. and 2.4.2. applied simultaneously.

4.2.3. Radiated Power

4.2.3.1. Method of Measurement under Normal Test Conditions

- a) On a test site fulfilling the requirements of Clause 3.3., the equipment shall be placed on the support in the following position
 - (i) equipment with internal antennae shall be arranged with that axis vertical which is closest to vertical in normal use;
 - (ii) for equipment with rigid external antennae, the antenna shall be vertical;
 - (iii) for equipment with non-rigid external antennae, with the antenna extended vertically upwards by a non-conducting support.
- b) The transmitter shall be switched on, without modulation, and the test receiver shall be tuned to the frequency of the signal being measured.
- c) The test antenna shall be orientated for vertical polarization and shall be raised or lowered through specified height range until a maximum signal level is detected on the test receiver*.
- d) The transmitter shall then be rotated through 360 degrees until the maximum signal is received.
- e) The transmitter shall be replaced by the substitution antenna, as defined in Clause 3.3. and the test antenna raised or lowered as necessary to ensure that the maximum signal is still received.
- f) The input signal to the substitution antenna shall be adjusted in level until an equal or a known related level to that detected from the transmitter is obtained in the test receiver.
- g) The carrier power is equal to the power supplied to the substitution antenna, increased by the known relationship if necessary.
- h) Steps a) to g) shall be repeated for any alternative integral antenna supplied by the manufacturer.
- j) A check shall be made at other planes of polarization to ensure that the value obtained above is the maximum. If larger values are obtained, this fact shall be recorded in the test report.

*Note: The maximum may be a lower value than that obtainable heights outside the specified range.

4.2.4. Limits

The carrier power measured under normal test conditions in accordance with Clause 4.2.2. shall not exceed 4 watts. The effective radiated power measured under normal test conditions in accordance with Clause 4.2.3. shall not exceed 2 watts.

The carrier power under extreme conditions shall not exceed by more than 2dB, that measured under normal conditions in accordance with Clause 4.2.2. in case of the fixed station equipment and Clause 4.2.3. in the case of portable equipment.

4.3. Frequency Deviation

The frequency deviation is the difference between the instantaneous frequency of the modulated radio-frequency signal and the carrier frequency in the absence of modulation. For test purposes, only the maximum value of the frequency deviation available in the transmitter will be measured.

Electronics Magazines: Are you getting what you want ?

Radio & Electronics Constructor is presently undergoing a metamorphosis to adapt its format and style to suit the interests and needs of the electronics *user* and enthusiast of the 1980's.

We are endeavouring to aim the content of *R&EC* very much at the 'sharp end' of the hobby and industry, where people are actively engaged in the design and use of electronics in situations that range from a simple hobby - through to the design and manufacture of commercial electronic systems. Particular prominence will be given to the endeavours of smaller scale enterprises in the field of electronics and communications - since so much of the hard work and basic innovation takes place outside the rigid structures of the giant multi-national electronics organizations.

During the past 20 years, electronics has evolved into three main streams:

1. Communications: now encompassing everything from broadcast radio, to satellite data transmissions into the consumers' back yards.
2. Computing: a subject that was virtually unknown 20 years ago - and now as commonplace as a TV
3. Electronics: the basic bread and butter aspects of design with modern components - everything from simple power supplies to 'state of the art' instrumentation and the building blocks of computing.

We would very much like our magazine to try and bring together as many of these disciplines as possible, and try to illustrate some of the many ways in which different aspects of electronics can be mutually beneficial. Design ideas will feature prominently, alongside practical projects that are designed to both provide an end 'article' and illustrate the thinking and techniques that have been employed from inception through to practical results.

This Survey will help us to identify both the nature of our readers - and the nature of their interests, so we ask for your assistance during this process of change. We anticipate that the 'new look' will be complete with our September issue (published August) - and we are using the intervening months to phase in some of the new ideas and style suggested by this survey, and our own reactions as active participants in both the design and use of modern electronics.

R&EC '81: Aims and objects

The Editorial will be guided by the most knowledgeable and best informed team of 'active' electronics users in the business of publishing. Our resources include the best equipped lab in either hobby or professional publishing - and some of the best informed exponents of the practical art of radio and electronics. We are always pleased to welcome new contributors - and can offer excellent support for those of you who would like to have a go, but feel slightly uncertain of their resources.

Radio and communications

With the advent of CB, it is anticipated that interest in this aspect of the hobby is set for a rapid increase. *R&EC* will be providing an informed and objective viewpoint of the situation as it unfolds in the UK, with coverage of all aspects from TVI to building your own gear - and also reviewing ready made units. CB will lead many followers onto the world of amateur radio - and it seems that the past few years has seen the demise of the practical side of the hobby, with the temptations of the ready made transceiver getting just too irresistible for most radio amateurs. This dearth of construction had led to a breed of radio amateur that is perilously unfamiliar with the more practical considerations of communications. We hope to strike a balance between equipment reviews, mods to commercial gear and constructional features. We certainly have a few eye-openers on the stocks.

Electronics

The nuts and bolts of the subject. *R&EC* will be publishing tutorials and updates - although we feel the basics of the subject are perhaps best learnt from one of the many books on the subject. (We will be expanding the *R&EC* book service, and providing regular reviews). New ideas and techniques will be explored with new features on design ideas and innovation, but we may have stop short of trying to include everything from basic resistor colour codes to communications satellites - most people have interests that lie somewhere in between.

Computing

The hobby of computing has suffered from the uncoordinated nature of the nascent market for the micro computer. Consequently, there are few 'standard' approaches - although one or two packages have emerged through weight of numbers to dominate the market. Our approach will be on three levels:

- 1) Practical applications of the MPU - eg controlling electronic systems, rather than playing Space Invaders.
- 2) Software and the complete microcomputer - here we intend to adopt one of the standard small scale systems as the basis for the features,
- 3) Peripheral, interface and support considerations - connecting (2) to the outside world.

A specific section on the back of this form covers some very detailed aspects of computing interest, since we are very keen to establish the levels of interest and experience we should aim for.

To summarize - we want R&EC to be intelligible to the beginner, but not insulting to the experienced - and we would like to cover as many topics as possible inside two covers - not necessarily splitting the format whenever a new publishing opportunity arises. With your help and support, we look forward to our first 400 page issue !!

R&EC

As a reward for your efforts in completing this comprehensive reader survey - subscriptions for R&EC received with this form will be charged at £8.50 - a saving of £1 from the *current* rate. So take this opportunity to subscribe now, and follow the metamorphosis of R&EC into the leading Radio and Electronics monthly.....

Reader Survey: 1981

Q1 : How do you rate the electronics press ??

Please check through the following lists of the electronics press, and indicate how you react to each under the headings provided. The scale of appreciation goes from 0 (worst) to 10 (best). Please make any specific comments you have about any of the magazines in the space left at the end.

If you have never heard of a magazine listed here, please put an 'X' in the first column -if you have heard of it, but do not frequently find it on offer on the bookstall, then please place a 'Y' in the first column.

Section one: 'Enthusiast Press'

- Column 1 = Project content and quality
 2 = News and features
 3 = Layout and presentation
 4 = Advertisement content
 5 = How often do you buy it

TITLE	1	2	3	4	5
a Practical Electronics					
b Practical Wireless					
c Everyday Electronics					
d Wireless World					
e Electronics Today Int					
f Hobby Electronics					
g R&EC					
h Elektor					
i RadCom					
j Short Wave Magazine					
k QST (USA)					
l 73 (USA)					
m Ham Radio (USA)					
n Radio-Electronics (USA)					
o Popular Electronics (USA)					
p Computing Today					
q Practical Computing					
r Personal Computer World					
s Byte (USA)					
t Liverpool software Gazette					
u Others					

- If you have any favourite features, please state the magazine, and the title of the feature:

Section two : 'Professional Press'

Much the same as above, but this time we would like you to consider carefully just how much effort you put into reading the magazine

- Column 1 = Newsworthiness
 2 = Feature articles
 3 = Product reviews
 4 = Advertisement value
 5 = How thoroughly do you read it

TITLE	1	2	3	4	5
a New Electronics					
b Electronic Engineering					
c Electronic Times					
d Electronics Weekly					
e Electronics & Power (IEEE)					
f Electronic Product Design					
g Electronic Equipment News					
h Electronic Product News					
i What's New in Electronics					
j Electronics Industry					
k Communications International					
l Communications Engineering					
m Electronics (USA)					
n Electronic Design (USA)					
o Microwave System News					
p RF Design (USA)					
q Microwaves (USA)					
r Others					

Q2 How much time do you spend each month on reading magazines? (Please tick the appropriate box):

- 0-2 hours 2-4 hours
 4-6 hours 6-10 hours
 over 10 hours (please indicate)

■ How closely do you read the adverts?

- a) when looking for something specific
 b) general scan to see what's new
 c) avidly
 d) try and avoid

Q3 How long do you keep your copies for?

- a) 0-2 months b) 2-6 months
 c) 6-12 months c) longer

If this time varies widely for different magazines, please insert the appropriate letter from the above after column 5 back in Q1.

Q4 How do you usually discover a magazine ?

- a) Advertisement b) Impulse buy
 c) Friends copy d) Seen at work
 e) Seen at college e) Mystery

Q5 Please list the 5 most recent constructional projects you have undertaken, indicating both the source of inspiration, and your overall estimate of the success achieved: (using a scale of 0-10)

1 Source _____
Success _____

2 Source _____
Success _____

3 Source _____
Success _____

4 Source _____
Success _____

5 Source _____
Success _____

■ Does the availability of a complete kit to support a project influence your decision? YES / NO
Would an easily accessible technical support service offered by a magazine influence your decision to build? YES / NO...and your choice of magazine? YES / NO
(Please delete as appropriate)

■ What 5 projects would you most like to see in a magazine?

1 _____

2 _____

3 _____

4 _____

5 _____

Q6 Do you buy from mail order advertizing:

- a) Exclusively b) Frequently
 c) Occasionally d) Last resort
 e) Never f) No longer

■ How do you prefer to pay?
 a) Access b) Barclaycard c) Cheque
 d) PO e) Other

Broadly speaking, is the service:
 a) Good b) Bad c) Indifferent

■ Where do you buy the majority of your electronic parts from?

■ Are you satisfied with the service?

■ What improvements could be made to the service you get from Mail Order suppliers?

Q7 Please rate your own interests on the 0-10 scale, using the following headings:

- a) Radio Communications
 b) CB
 c) HiFi
 d) Broadcast radio
 e) TV
 f) General electronics
 g) Computing hardware
 h) Software
 i) Computing *applications*
 j) Others

Q8 Test equipment: please tick the appropriate box

Column 1 : Currently owned
 Column 2 : Have ready access to (work/college)
 Column 3 : Hope to get soon
 Column 4 : Made/make yourself

Item	1	2	3	4
a) Multimeter	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
b) DVM	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
c) Frequency counter	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
d) GDO	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
e) RF sig gen	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input checked="" type="checkbox"/>
f) AF sig gen	<input type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>	<input checked="" type="checkbox"/>
g) AF powermeter	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
h) RF powermeter /SWR meter	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
i) Spectrum analyzer AF	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
j) Spectrum analyzer RF	<input checked="" type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
k) Logic analyser	<input checked="" type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
l) Others:	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
	<input checked="" type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>
	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Q9 About you, please. We promise names and addresses will not be supplied to any external mailing list agencies, and that you will not be pestered to subscribe to the Reader's Digest or Which.....

Your Name _____
 Your age and gender _____
 Your address _____

■ Your level of education, please:
 a) CSE b) O-Level c) A-Level
 d) ONC e) HNC f) Degree
 g) PhD h) other

■ If you are currently a student, please state the name of the establishment and the course:

Q10 Computing Survey:

A Survey within a Survey - we are trying to establish the present 'standards' - and exactly what approach our readers need:


- 1 ■ Do you own a 'personal' computer ?
YES / NO
- 2 ■ If 'YES', what make or configuration of hardware:

- 3 ■ Do you have access to a computer:
 - a) At school
 - b) At college
 - c) At university
 - d) At work
 - e) Other (please specify):

- What type of computer ?

Thankyou very much for your time and patience - anything you have said will be taken down and used as evidence that *R&EC* is responding to the needs and wishes of its readers. If you are school/college or you have friends who want more copies of this form to submit their own ideas - then please write and ask with an SAE that's big enough for the number you want.

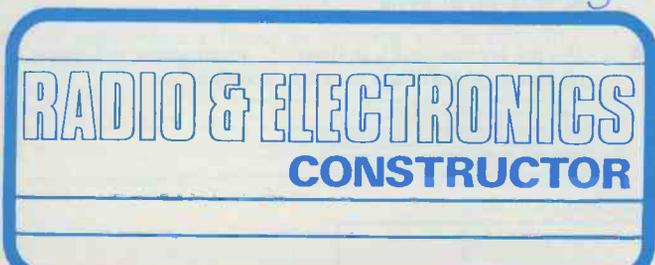*For the future student of Sociology:
This is a typical example of the onset of Thatcherism & all its works which brought*



about the downfall, in this ?small way of RC. RC's successor failed miserably. Sic transit gloria mundi. Jim Jobe 8 Feb. 2007.

- 4 ■ What programming languages do you know ?
Please rate your competence level from 1-10.....

a) Machine code(s) (please specify):

b) High Level languages (please specify and indicate any machine variant or dialect):

- 5 ■ How did you learn programming ?

- a) School
- b) College
- c) University
- d) Commercial course
- e) Self taught
- f) Other (please specify)

- 6 ■ Will you be following the BBC's course on computing

- a) Occasionally
- b) Whenever possible
- c) Thoroughly
- d) Not at all

- 7 ■ How would you like to see *R&EC* approach the subject of computing and microprocessors ?

Please send completed forms to:

RADIO & ELECTRONICS CONSTRUCTOR
1981 READER SURVEY
57 MAIDA VALE
LONDON W9 1SN

Subscriptions may be paid by PO, cheque, Access or Barclaycard. Please make the cheques out to "Radio and Electronics Constructor"

4.3.1.3. Limit

At any modulating frequency, the frequency deviation shall not exceed ± 2.5 kHz.

4.4. Adjacent Channel Power

4.4.1. Definition

The adjacent channel power is that part of the total power output of a transmitter under defined conditions of modulation, which falls within the bandwidth of a receiver of the type normally used in the system and operating on a channel either 10 kHz above or below the nominal frequency of the transmitter.

4.4.3. Limits

The adjacent channel power shall not exceed a value of 60dB below the carrier power of the transmitter, without the need to be below 2uW.

4.5. Spurious Emissions

4.5.1. Definition

Spurious emissions are emissions at frequencies other than those of the carrier and sidebands associated with normal modulation. The level of spurious emissions shall be measured as:

- Their power level in a specified load, where the equipment is fitted with output terminals and
- Their effective radiated power when radiated by an integral antenna or from the cabinet and chassis of the equipment.

4.5.2. Method of Measurement — Power Level

- The transmitter output shall be connected to either a spectrum analyser via an attenuator, or an artificial load, with means of monitoring the emission with a spectrum analyser or selective voltmeter.
- The transmitter shall be unmodulated and at each spurious emission in the frequency range 100 kHz to 1000 MHz, or four times the working frequency whichever is the greater, the level of the emission shall be measured relative to the carrier emission.
- The power level of each emission shall be determined by applying the ratio measured to the carrier power level determined in Clause 4.2.3.

4.5.3. Method of Measurement — Effective Radiated Power

- On a test site fulfilling the requirements of Clause 3.2, the transmitter shall be placed at the specified height on the support.
- The transmitter shall be unmodulated and its output connected to an artificial load, where the equipment is fitted with output terminals (Clause 3.1.)
- Radiation of any spurious emissions shall be detected by the test antenna and receiver, over the frequency range 30 to 1000 MHz or four times the working frequency whichever is the greater.
- At each frequency at which an emission is detected, the transmitter shall be rotated to obtain maximum response.
- The transmitter shall be replaced by a signal generator and dipole antenna and the effective radiated power of the emission determined by a substitution measurement.
- The measurements shall be repeated with the test antenna in the orthogonal polarisation plane.
- The measurements shall be repeated with the transmitter modulated with normal test modulation (Clause 3.4.)
- The measurements shall be repeated for any alternative integral antenna which can be supplied with the equipment.

4.5.4. Limits

Any spurious emission from the transmitter with and

without any ancillary equipment, expressed as a power into a test load or as a radiated power, in either plane of polarisation, shall not exceed 50nW within the following frequency bands:

80 MHz — 85 MHz	135 MHz — 136 MHz
87.5 MHz — 104 MHz	174 MHz — 230 MHz
108 MHz — 118 MHz	470 MHz — 862 MHz

The power of spurious emissions at any other frequency outside the above bands shall not exceed 0.25uW.

5. RECEIVER

5.1. Receiver Spurious Emissions

5.1.1. Definition

Spurious emissions from receivers are any emissions present at the input terminals or radiated from an integral antenna or the chassis and case of the receiver.

5.1.2. Method of Measurement for Equipment Fitted with Antenna Terminals

- The methods shall be as described in Clauses 4.5.2. and 4.5.3. except that the test sample shall be the receiver.

5.1.3. Method of Measurement for Equipment Incorporating Integral Antenna

- The method of measurement shall be as described in Clause 4.5.3. except that the test sample shall be the receiver.

5.1.4. Limits

Any spurious emission from a receiver expressed either as a power into a test load or as a radiated power, shall not exceed 20nW on any frequency.

Comment

The obviously noteworthy part of the specification is the choice of 40 channels (as opposed to the Euro standard of 23 channels), and the starting point of the band — which bears no relation to any other CB service anywhere in the world. Whilst this may have the CB fraternity beating its breast and wailing, it is basically good news for newcomers, since the band is a great deal less cluttered (at present it seems it is used for weather balloons and other non-civil purposes).

The use of straight 10kHz increments makes the use of existing CB synthesiser systems difficult — since the US 40 channel plan jumps from 10kHz to 30 kHz between 22 and 23, and channels 25/26 jump 20 kHz. The same sort of trouble occurs at channels 3/4, 11/12, 19/20.

The start point at 27.60125MHz also means that the simple 'decade' approach to synthesis would require a division of 2.760125 to arrive at the reference of 10kHz spacing.

The US plan starting at 26,965MHz is divided by 2,6965 to get 10kHz in a direct synthesis system. Obviously, a mixing synthesiser (Figure 2) where the synthesiser is responsible for controlling an scillator that does not directly correspond to the output frequency can simply produce any 40 channels in 10kHz increments — given that the channel spacing and numbering remains consistent. The start point is simply determined by the frequency of a crystal oscillator used to mix with the VCO — first get your synthesiser VCO to tune.—

10.000 to 10.400 MHz (simple stuff for the cognoscenti)
...then mix with 6.90125MHz from a crystal oscillator for 'receive' with a 10.7MHz IF offset (oscillator low), and 17.60125 for the direct transmit frequency.

This approach would call for a few extra coils to trap the mixing products, but it can readily be handled by a competent designer.

Power Politics

The power has been carefully considered to provide a realistic and workable range — and when you take into account the simple fact that the UK band is relatively uncluttered by continental users (in fact, it is unique as a

CB frequency), then you won't need extra urge to blast through the interference. In fact, the conditions may approach the relative calm of a VHF allocation.

The use of an 'Effective Radiated Power' of 2W means that the range will be about 3-5 miles in indifferent conditions mobile, peaking at 10-15 miles with a bit of luck and a good installation.

The base station power can still be 2W ERP — but if the base of the antenna is more than 7m above ground level, then a 10dB attenuation of the transmitter signal is required. The original draft suggested a fixed attenuator to actually plug into the set — but since this would lead to confusion and the unacceptable attenuation of the receiver sensitivity, this has been relaxed to include a simple high/low power switch on the front of the set.

Whether or not anyone will be good enough to observe this rule remains to be seen. Most realists agree that since no one has managed to stamp out CB in its currently totally illegal form, then it is doubtful if this rule will be closely observed.

The HO's main reason being that unless some steps are seen to be taken to prevent excessive range being achieved by base stations, then the band will get unduly clogged (witness the present naughty-forty channels), and the prime intention of the CB service will become submerged in a morass of pseudo radio amateur stations trying to work the DX by the sheer brute force and ignorance that this would require.

Another reason is that most domestic electronic and TV equipment is fairly impervious to 400mW (4W RF attenuated by 10dB) of 27MHz closeby, and thus the authorities have covered any potential uproar when the TV viewing public finds the breakers breaking up Coronation Street by showing that if their rules are followed, then this is not a problem.

That it will be a problem is tacitly acknowledged, since quite apart from failing to observe the power switch for a base station, there is little doubt that RF amplifiers will be hung on the output socket, and so 10dB of boost will be applied by those CBers who don't know any better. It might have been better to suggest that the manufacturer provides a set of five 27MHz traps with Belling-Lee coax terminations (universal for UK TVs) rather than this nebulous low power attenuator. It seems that we may all find out the hard way.

A la Mode....

FM with 2.5kHz peak deviation roughly equates to the range achieved by AM. Last months' supplements speculated on this point, so we won't repeat it here. The UK's deviation 'allowance' is more generous than most, and hopefully this will provide further persuasion for the AM brigade to give it a try.

We'll say this again though — an FM only set will be cheaper and far more reliable than an AM or AM/FM set — see the announcement elsewhere in this issue.

Come back....

There will doubtless be a tirade from some existing CB user groups. There always is, and isn't it getting boring? What we have here is the most workable solution yet offered in Europe, that avoids total destruction of the existing users service in 27MHz (like the paging services opt cited). The HO has pulled a hitherto unimagined 40 channels out of the bag, and could scarcely now be expected to retrace. They have possibly let themselves in for the first official 80 channel CB service anywhere, since unless human nature can be changed — or hanging reintroduced for sets using the illegal 27MHz allocations, then sooner or later some concession to the US standard may have to be made.

It would be nice to think that we British have a shade more sense than those others who have all but destroyed the CB service in other countries. If you want to talk across the Atalantic and have enormous DX potential, then for heaven's sake get an amateur radio operator's licence. Children of 13 manage to do it with surprising ease — and so can you, if you have shown enough enthusiasm to buy this magazine.

Putting away the toys....

Under any circumstances, CB is a toy compared to the capability of 'amateur radio'. The 144-146MHz band offers a plethora of ready made gear, a range that is 2 to 3 times that available from 27 MHz on a car-to-car basis, and over 60 miles if your use the repeaters available. The antenna is unobtrusive and efficient, and the people you meet mostly speak English, and are not engaged in overly illegal behaviour.

You will learn facts and information in the course of getting the radio amateur qualification that will provide you with a great deal of assistance in operating — and you will quickly appreciate that CB has too many limitations. CB will be fine for 'around the town' and other family members who simply want to keep in touch — but do not expect more than that.


The HF band allocations available to the radio amateur permit global coverage 24 hours a day if you have the time and patience to set up the right sort of station. By all means cut your teeth on CB to see if it seems like a hobby you would like to pursue, but please view it as a stepping stone to better things, and don't go out and try to blast your way through by using illegal power and spoiling CB for others.

CB is simply not suitable for 'DXing'.


Next time....

This month's big news has once again reshuffled the schedule. We will give a run down on 934MHz (as it now is) next month, and give more details on the equipment for legal CB.

Figure 2

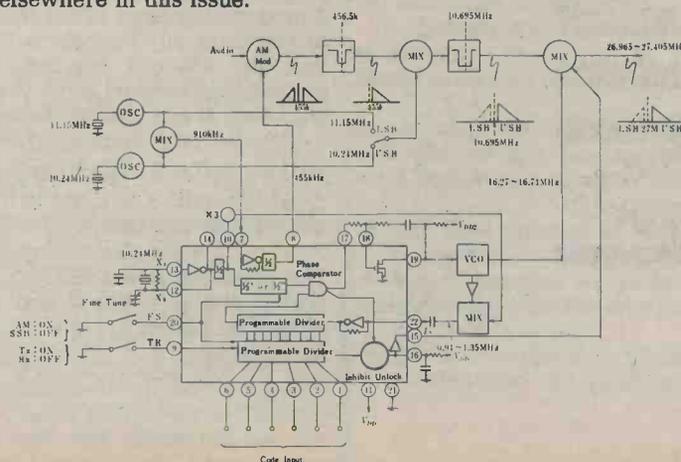

MILLER EFFECT

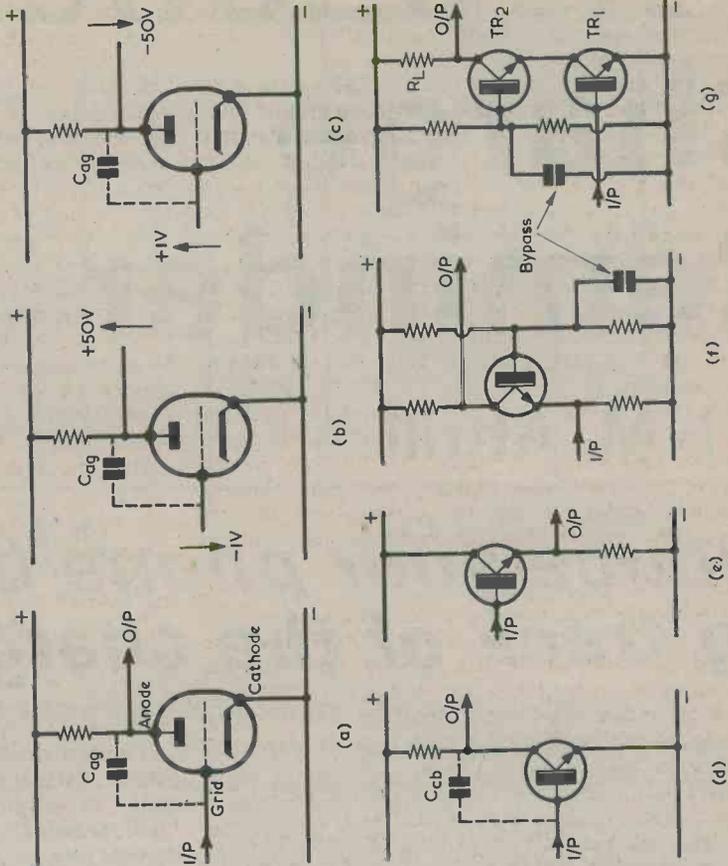

Miller Effect can be most readily explained with the old-fashioned triode valve. This is shown in (a) and there is a stray capacitance, C_{ag} , between anode and grid. Let us say the valve has a voltage gain of 50 times.

In (b) we take the grid negative by 1 volt, whereupon the anode goes positive by 50 volts. The voltage across C_{ag} increases by 51 volts and so the charging current flowing into it is 51 times that which would have been given if the anode voltage had been fixed. In (c) the grid goes positive by 1 volt and the anode goes negative by 50 volts, causing the voltage across C_{ag} to fall by 51 volts. There is a 51-fold increase in discharge current.

Charge and discharge currents are proportional to capacitance and so the effective grid input capacitance of the triode is 51 times C_{ag} . Generally, the effective input capacitance is equal to $(G + 1)C_{ag}$, where G is the voltage gain of the triode. This increase in input capacitance is known as Miller Effect.

Miller Effect is given in the common emitter transistor of (d) and is equal to $(G + 1)C_{cb}$, where G is the voltage gain from base to collector. Quite high effective input capacitance results and this can limit high frequency amplification. Miller Effect is absent in the emitter follower of (e) and the common base amplifier of (f). It is also absent in the cascode amplifier of (g). Here, TR_2 acts as a common base amplifier, holds the collector of TR_1 at a fixed voltage and allows the collector current of TR_1 to flow through R_L . Since there is no voltage change at TR_1 collector, Miller Effect is overcome.


Telephone Charge Reminder

By I. M. Attrill

Reduce your phone bill by keeping track of the charges.

When making telephone calls it is very easy to lose track of the passage of time, with consequent high phone bills arriving on the doormat in due course! One way of overcoming this problem is to have a device which gives an indication of the number of time units which are being accumulated while the call is in progress. This can either be in the form of a unit which gives an actual read-out of the number of units, or it can simply be an instrument which gives an indication of the passage of each unit. In most instances the second is probably the most practical approach since it is relatively cheap and simple, but is still, nevertheless, effective at preventing the telephone user from losing track of time (and money spent).

The unit to be described provides a brief audible tone each time a unit elapses. The units are for inland calls, as detailed in the British Telecom leaflet "Telephone Charges", and the amount of time corresponding to one unit depends on the distance involved and the time when the call is made, as shown in the Table. There are actually nine different time units in use at the present time. However, the accuracy of the unit does not really merit the inclusion of both the 45 second and 48 second times, as these are so close together, and they are therefore covered by an intermediate time of 46.5 seconds. Also, it was not considered to be worthwhile including a 9 minute interval since, at this rate, even long calls cost very little. The timing intervals which the unit provides can be seen in the range switching circuit of Fig. 2.

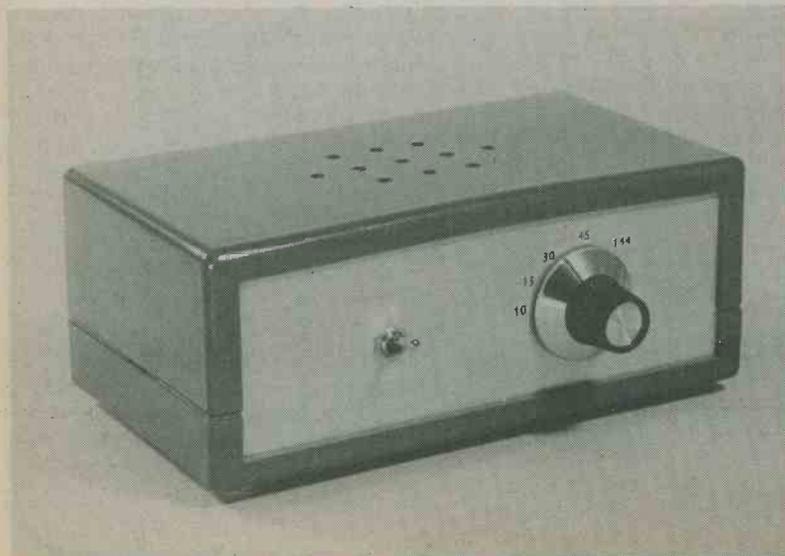

The finished unit is robust, compact, and simple to operate and free from trailing wires.

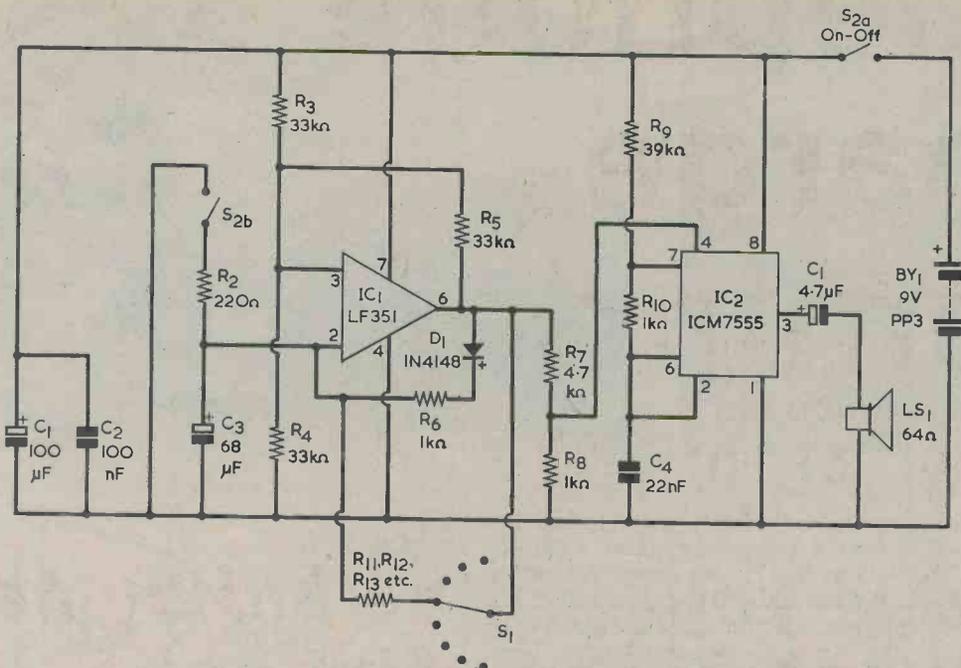


Fig. 1. The circuit diagram of the Telephone Charge Reminder.

THE CIRCUIT

There are two main sections in the unit, these being a timer which gives brief pulses at the ends of the appropriate intervals and a tone generator which produces an audible tone when these pulses are present. In the circuit given in Fig. 1, IC1 is in the timer section and IC2 is in the tone generator section.

IC2 is an ICM7555 employed in a standard astable circuit which oscillates at around 1.6kHz. It drives the loudspeaker via d.c. blocking capacitor C5. The ICM7555 has its pin 4 returned to the timer section, and it will only oscillate when this pin is taken more than about 0.5 volt positive of the negative coil. An ICM7555 is used instead of the standard 555 because it draws a much lower quiescent current. The ordinary 555 draws a current of about 6mA at 9 volts, and would cause the total current consumption of the circuit to be approximately 8mA. The quiescent current requirement of the ICM7555 is only about 60μA, and causes the total average current drawn to be of the order of 2mA. This is low enough to permit economic operation with a small PP3 battery, and such would not be the case if a standard 555 was used.

The timing circuit around IC1 is rather similar to a 555 circuit in that the timing capacitor, C3, charges to around two-thirds of supply voltage and discharges to one-third of supply voltage. At switch-on C3 is discharged, whereupon the output of IC1 is high and the non-inverting input of the i.c. at pin 3 is at two-thirds of supply potential since R5 is effectively in parallel with R3. The capacitor charges rapidly through D1 and R6 until the voltage at the inverting input very closely approaches that at the non-inverting input, whereupon the output swings low and effectively connects R5 in parallel with R4. The capacitor now discharges slowly, through whatever resistance is selected by S1, until the voltage across it falls to one-third of supply potential. The i.c. output then goes high again and the next half-cycle commences. The ICM7555 is enabled when the i.c. output is high and produces a tone burst for a fraction of a second. The potential divider given by R7 and R8 is needed because the output of IC1 does not, in practice, go to a sufficiently low voltage when it is low.


Thus, the overall circuit produces short tone bursts at intervals which are governed by C3 and the timing resistance selected by S1. As with all circuits of this nature the initial cycle is longer than the subsequent ones because the timing capacitor has to charge from zero volts instead of from one-third of the supply voltage. This causes no problems in the present application because the initial charge period is the very high brief time given as C3 charges through D1 and R6. The subsequent discharge period in the first cycle is the same as the discharge period in the following cycles. The unit produces a short tone burst at switch-on, and this is correct since the subscriber is charged one unit as soon as the phone call is answered, which is when the circuit is switched on.

TABLE

Telephone Time Units

	Local	Up to 56km	Over 56km
Peak	2 minutes	30 seconds	10 seconds
Standard	3 minutes	45 seconds	15 seconds
Cheap	9 minutes	144 seconds	48 seconds

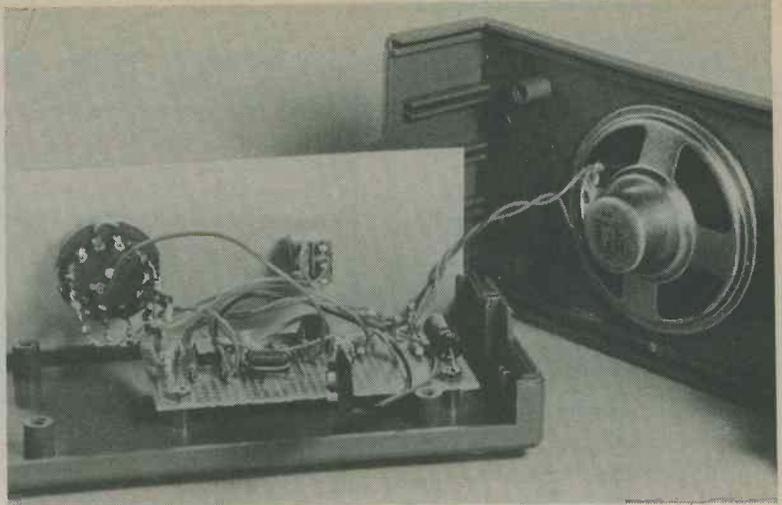The internal view shows the straight forward method of construction with the loudspeaker mounted underneath the lid.



The full timing resistance circuit is given in Fig. 2. The discharge time for C3 is approximately $0.685CR$ seconds and, with C3 at $68\mu F$, this means a timing resistance of approximately $21.5k\Omega$ per second. If, in the future, the telephone time units are changed, the timing resistors can be altered accordingly. The required value is equal to $21.5k\Omega$ multiplied by the required interval in seconds. Either the nearest preferred value can be used, or two resistors in series can be employed if the calculated value is too far from a preferred value. It is for this reason that two resistors are used at the 144 second position of S1. The switch is a 12-way type with adjustable end stop set for 7-way operation. If future changes in time units are introduced by British Telecom it is an easy matter to increase or decrease the number of ways provided, should this be necessary.

It is not necessary for the unit to have an extremely high degree of accuracy, but to keep errors reasonably small the timing resistors in Fig. 2 should have a tolerance of 5%. This may necessitate the use of $\frac{1}{2}$ watt instead of $\frac{1}{4}$ watt resistors for values above $1M\Omega$. Also, C3 should be a tantalum bead capacitor, which will have a much closer tolerance on value than an ordinary electrolytic capacitor. Tantalum bead capacitors with the value specified for C3 are available from several retail outlets, including Watford Electronics, 33/35 Cardiff Road, Watford, Herts.

S2(a)(b) is the on-off switch, with S2(a) being in the positive supply rail circuit. S2(b) discharges C3


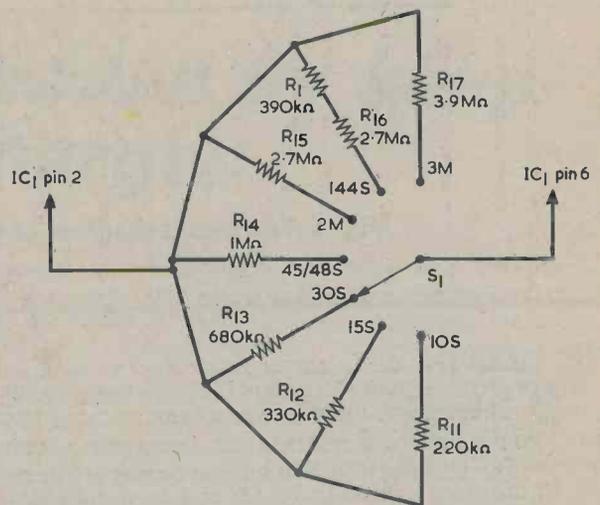


Fig. 2. Details of the range switching.

through current limiting resistor R2 when the unit is switched off. This is necessary because the capacitor can otherwise retain a charge if the unit is switched off for a brief time and is then switched on again, resulting in an incorrect initial timing period.

Close up view of the Veroboard showing the component mounting details.

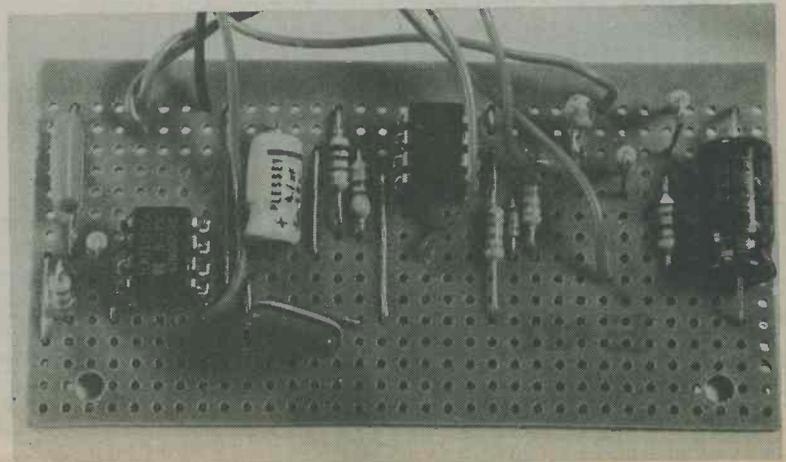

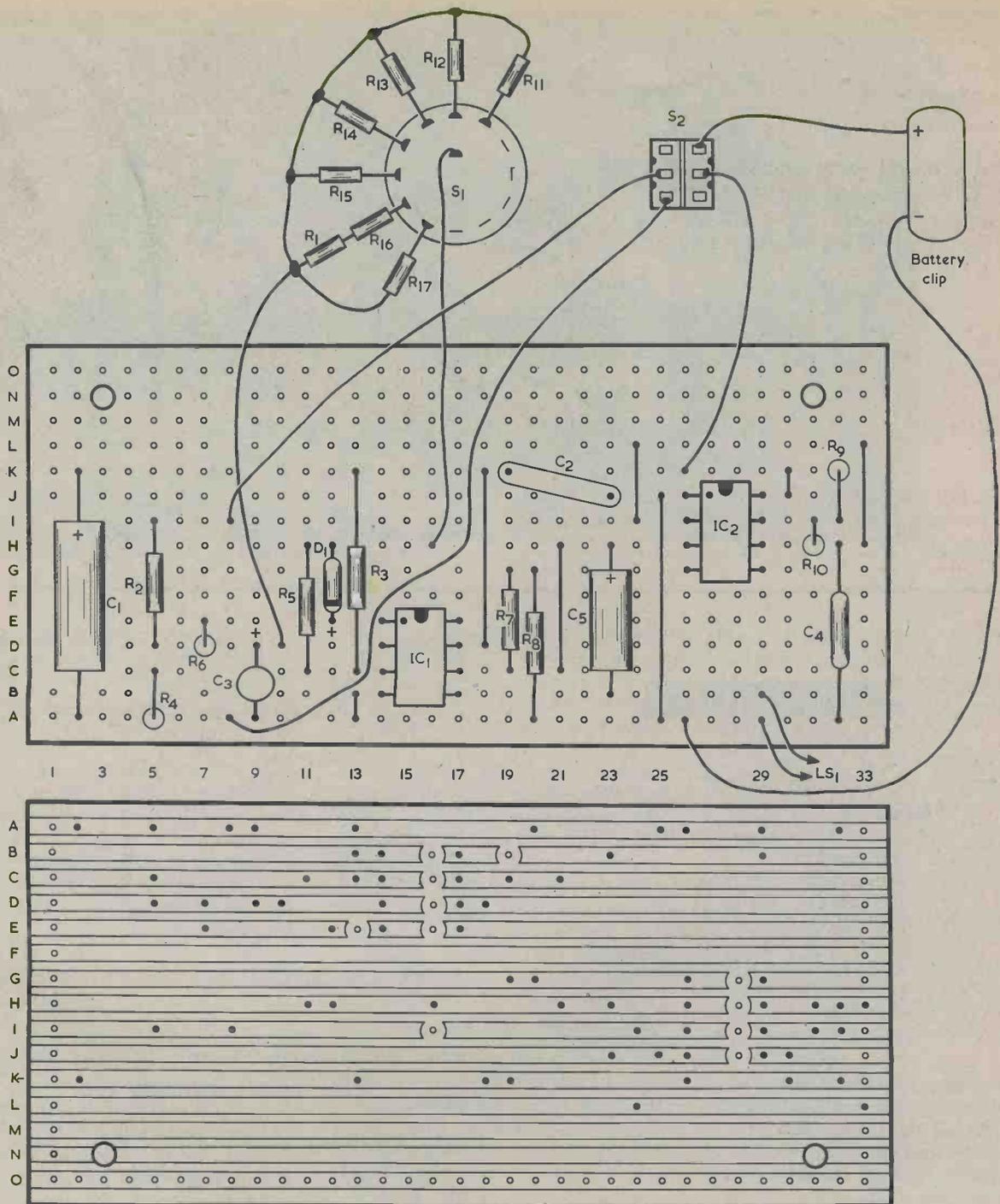



Fig. 3 Details of the component panel and the wiring of the unit.

CONSTRUCTION

A Verocase type 202 21041C (old part number 75-1238-D) measuring 153 by 84 by 59 mm. provides a suitable housing for the project. As is shown in the photographs, the two switches are mounted on the front panel. The speaker is mounted on the underside of the top panel of the case, and it is necessary to make a speaker grille here by drilling a matrix of small holes. The speaker is glued in place by means of a

modest amount of good quality adhesive taking care to ensure that none of the adhesive gets on to its diaphragm, where it could upset its operation.

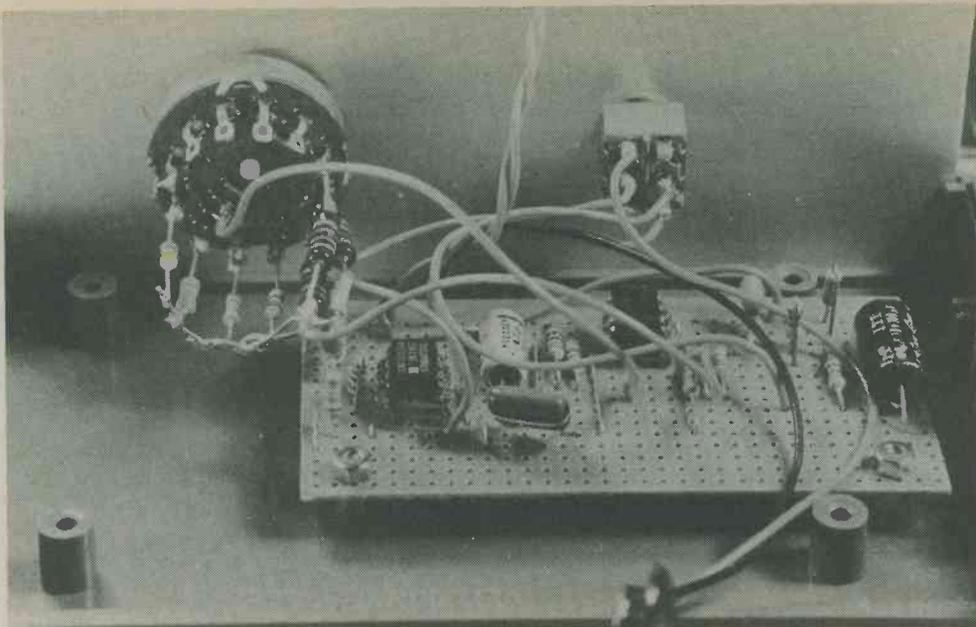Most of the other components are assembled on a piece of 0.1 in. Veroboard having 15 copper strips by 33 holes. The timing resistors are soldered direct to the tags of S1. Details of the Veroboard and all the wiring of the unit are given in Fig. 3. The board is secured to the bottom panel of the case by two M3 bolts and nuts, with spacing washers on the bolts to



COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5% - see text)

- R1 390k Ω
- R2 220 Ω
- R3 33k Ω
- R4 33k Ω
- R5 33k Ω
- R6 1k Ω
- R7 4.7k Ω
- R8 1k Ω
- R9 39k Ω
- R10 1k Ω
- R11 220k Ω
- R12 330k Ω
- R13 680k Ω
- R14 1M Ω
- R15 2.7M Ω
- R16 2.7M Ω
- R17 3.9M Ω

Capacitors

- C1 100 μ F electrolytic, 10V. Wkg.
- C2 0.1 μ F polyester, type C280
- C3 68 μ F tantalum bead, 6V. Wkg.
- C4 0.022 μ F polyester, type C280
- C5 4.7 μ F electrolytic, 10V. Wkg.

Semiconductors

- IC1 LF351
- IC2 ICM7555
- D1 1N4148

Switches

- S1 1-pole 12-way rotary with adjustable end stop
- S2 d.p.d.t. miniature toggle

Speaker

- LS1 miniature speaker, 64 Ω

Battery

- BY1 9 volt battery type PP3

Miscellaneous


- Plastic case (see text)
- Veroboard, 0.1 in. matrix
- Battery connector
- Control knob
- Nuts, bolts, wire, etc.

keep the board underside clear of the inside surface of the case. The board is mounted towards the left hand side of the case, as seen from the front, with the mounting holes to the rear. This will leave ample space for the PP3 battery on the right hand side of the case.

Although IC2 is a CMOS device it requires no special handling precautions because of its internal protection circuitry.

USING THE UNIT

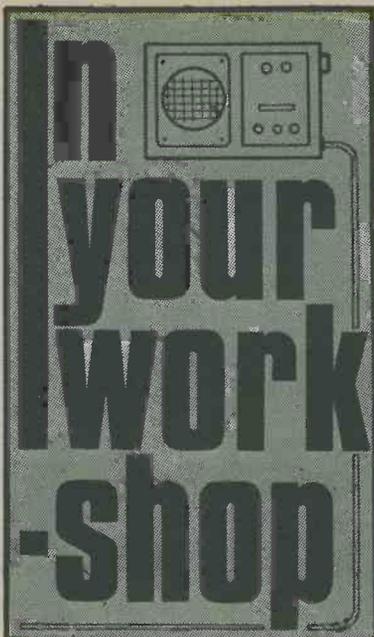In use, S1 is set to the appropriate timing interval with S2(a) (b) switched off. The call is dialled and S2(a) is turned on when the call is answered. The unit will give a brief tone burst at switch-on to indicate that the first time unit has been charged and will then produce further tone bursts at the timed intervals.



Problems with T.V. gain control:

Too much contrast?

Dick picked up the neat little Japanese monochrome television receiver and carried it over to his bench. A circular loop aerial was connected to two terminals at the upper rear of the cabinet and Dick decided initially to check the performance of the set with this aerial. He plugged the receiver into one of the mains sockets at the rear of his bench and then looked for the on-off switch for the set. On the front panel was the channel selector tuning control and, below the tube, two slide controls and a knob. The slide controls were patently for contrast and brightness, whereupon the knob had to be the volume control. Dick experimentally turned it clockwise. It moved freely without any switch operation, so he pulled it out.

The Workshop was at once filled with a babble of barking puppies. The tube soon came to life, to reveal an advertisement extolling the virtues of Woof-Woof, the Wonder Dog Food.

SOOT AND WHITEWASH

"For goodness's sake," roared Smithy from his side of the Workshop, "turn that down!"

"Sorry, Smithy," said Dick, as he hastily turned back the volume control. "I accidentally turned it up high before I switched the set on."

He looked back at the screen. The commercial had frozen in its final frame. It then faded, to be replaced by the title "Police Chopper Emergency Down Under". The picture reproduced on the tube screen was a little noisy and grainy but otherwise seemed satisfactory. Sound was obviously adequate. Dick tuned next to BBC1, to find a similar picture with a slight background of snow. He had to reduce the contrast slightly to obtain a good picture but no other adjustment was necessary.

He turned the volume control fully back, sat down and glared at the receiver.

Smithy, curious at the unwonted silence from Dick's bench, glanced round at his assistant.

"Dear, oh dear," he complained. "One minute you're raising Bedlam in here, and the next minute you're sitting there all useless just gazing into space."

"It's this set," stated Dick morosely.

"What's wrong with it?"

"Nothing for the moment!"

"Nothing?"

"Nothing at all," repeated Dick. "It's just my luck to have picked a set which has got an intermittent on it."

Smithy put down his soldering iron and walked over to Dick's bench. He looked criti-

cally at the picture on the television screen.

"Take off that loop aerial," he ordered, "and try it with the outside aerial."

Obediently, Dick unscrewed the two terminals, removed the loop and then plugged in the lead from the outside aerial. As soon as the aerial plug made contact the receiver produced a grossly over-contrasted picture having almost all its detail in black and white, and with hardly a trace of grey between the two extremes. Dick put the contrast control to minimum, but the excessive contrast was still present.

"That's what we used to call a 'soot and whitewash' picture in the old days," pronounced Smithy in a tone of satisfaction. "You haven't got an intermittent fault here, Dick, you've got a straight-forward automatic gain control snag. The a.g.c. circuitry should have reduced the gain of the set when you applied the much stronger signal which is available from the outside aerial. It didn't, and so that's your fault."

"An a.g.c. fault?" queried Dick as he switched off the set. "I think I'd rather have an intermittent!"

"Nonsense," snorted Smithy, "curing an a.g.c. fault in these monochrome receivers is a piece of cake. See if you can find the service sheet for

this set, and I'll show you where the a.g.c. bit is."

Dick walked over to the filing cabinet and, after some searching, located a service sheet for the receiver. He returned and handed it to Smithy, who opened out the circuit diagram on Dick's bench.

"Here we are," said Smithy. "The a.g.c. section in this receiver is very simple, and it uses a single gated a.g.c. amplifier transistor."

Smithy pointed to the a.g.c. section of the receiver circuit. (Fig. 1.)

"You call that simple?" gasped Dick. "To my eyes it looks horrible. For a start, that gated a.g.c. amplifier transistor has got connections going to the first video amplifier, to the line output transformer and to the first vision i.f. stage!"

"Take it easy," said Smithy soothingly. "Let's look at this a.g.c. business working from basic. The 625 line u.h.f.

transmitted signal has negative modulation, which means that sync pulse tips correspond to maximum signal strength and peak brightness corresponds to minimum signal strength." (Fig. 2(a).)

"Well, that's fair enough."

"Right," said Smithy. "Now, to get an a.g.c. voltage we have to get a measure of signal strength after the vision detector, and what could be better than sampling the amplitude of the sync pulse tips? To ensure that the a.g.c. voltage we get isn't influenced by interference, we sample the amplitude of the sync pulses only when they are present." (Fig. 2(b).)

"That's fair enough, too," conceded Dick.

"Good," said Smithy. "First of all we have to get the sync pulse tips from somewhere, and in this set they're obtained from the emitter of the first video amplifier, which hap-

pens to be an emitter follower. The vision detector is connected so that the sync pulses in the detected signal are negative-going. So also are the sync pulses at the emitter of the first video amplifier, and these are applied to the base of the gated a.g.c. transistor through a 330Ω resistor. We want to sample the sync pulse amplitude only when the pulses are present, and so we supply the a.g.c. transistor from a floating winding on the line output transformer. The waveforms accompanying the circuit diagram in this service sheet tell us that the line flyback section of the line output waveform, as applied to the transistor collector via a 1N60 diode, are negative-going." (Fig. 3.)

"I'm beginning to make sense of this now," said Dick keenly, as he gazed at the circuit. "The a.g.c. transistor is a p.n.p. type, and so it will only


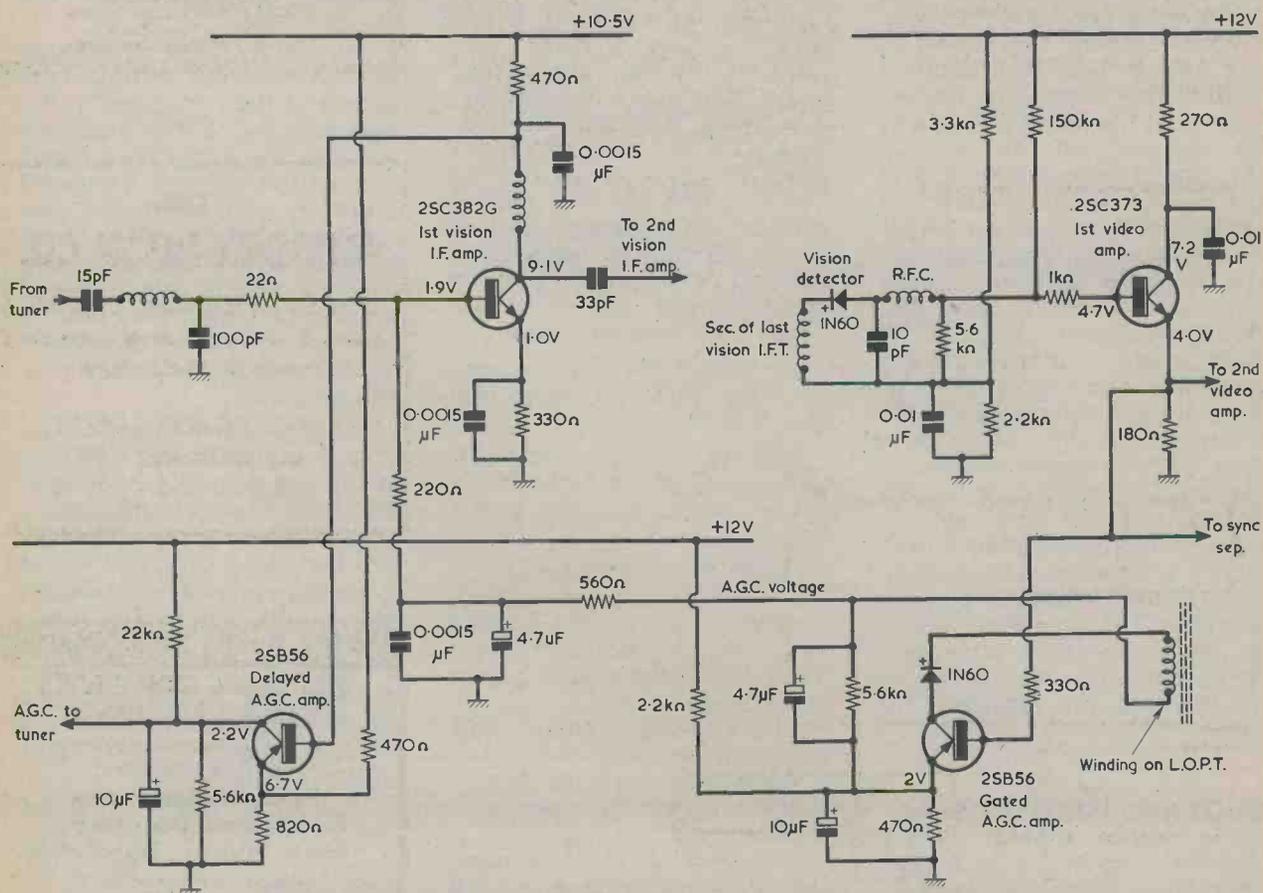


Fig. 1. The gated a.g.c. amplifier and associated circuits in the monochrome television receiver selected by Dick. This circuit is employed in the Teleton receiver model TW-12BS Mk II. The voltages shown are with respect to chassis under no-signal conditions.

MORSE MADE EASY

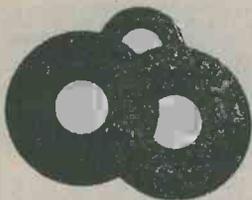

BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.

Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750grm). Details only s.a.e.

THE G3HSC MORSE CENTRE

S. Bennett, (Box 8), 45 Green Lane, Purley, Surrey.

Name

Address

RADIO & ELECTRONICS CONSTRUCTOR

ANNUAL SUBSCRIPTIONS

to this magazine may be obtained through your newsagent or direct from the publishers



INLAND £9.50
OVERSEAS . . . £10.50
per year, post free



Please send remittance with name and address and commencing issue required to:

DATA PUBLICATIONS LTD
57 Maida Vale, London W9 1SN

"And now," said Dick, suddenly crestfallen, "I'm stuck! How does the increased collector current get translated into an a.g.c. voltage?"

"Do you see that 5.6kΩ resistor with the 4.7μF electrolytic across it?"

"Yes."

"Well, when the a.g.c. transistor passes a higher collector current, the upper end of that 5.6kΩ resistor goes positive!"

A look of utter bewilderment spread over Dick's face.

"Goes *positive*?" he repeated incredulously. "How the flaming heck can the upper end of that resistor go positive?"

"To explain that," said Smithy in reply, "we can start off by assuming that the emitter of the gated a.g.c. transistor is held at a fixed voltage by the 2.2kΩ and 470Ω resistors which connect across the 12 volt supply rails. If we then freeze the action of the gated a.g.c. transistor circuit to an instant during the line flyback, we can pretend that it is fed by a floating battery instead of by a winding on the line output transformer." (Fig. 4.)

"Yes," said Dick slowly, "I think I can visualise that."

"Good," said Smithy. "Now the collector current of the transistor flows only in the circuit loop consisting of the battery and the 5.6kΩ resistor which takes the positive side of the battery back to the emitter. When increasing signal sync pulse amplitude takes the transistor base negative the collector current, as you so rightly said, has to increase. That increased collector current flows through the 5.6kΩ resistor and so the voltage across the resistor must also increase. Since the emitter end of the 5.6kΩ resistor is held at a fixed voltage relative to chassis the other end has to go positive. Got it?"

Dick looked at the circuit in the service manual in a bemused manner.

"Of course the voltage must go positive," he stated slowly. "But it's a bit of a shaker to find that increased collector current in a p.n.p. transistor causes an increased *positive* voltage. It seems all upside-down to me!"

"It does need a little imagination to see the effect," agreed Smithy. "Don't forget that our imaginary battery is floating and isn't connected to any part of the remaining television circuitry. When the transistor draws increased collector current it actually causes the whole battery to go positive with reference to the fixed emitter voltage on the transistor emitter."

"Yes," said Dick, "I can understand it now. So, the voltage goes positive with increased signal strength. What happens next?"

"The voltage, which is of course smoothed to a steady level by the 4.7μF capacitor across the 5.6kΩ resistor, is the a.g.c. voltage and it's fed to the base of the first vision i.f. transistor through a 560Ω resistor and a 220Ω resistor. There are two filter capacitors, a 0.0015μF one and another 4.7μF electrolytic, at the junction of these two resistors." (Fig. 5.)

"Hang on a minute. There's something queer here!"

"What's that?"

"Well, the i.f. transistor is an n.p.n. one," stated Dick. "Won't increasing the positive bias voltage increase its gain

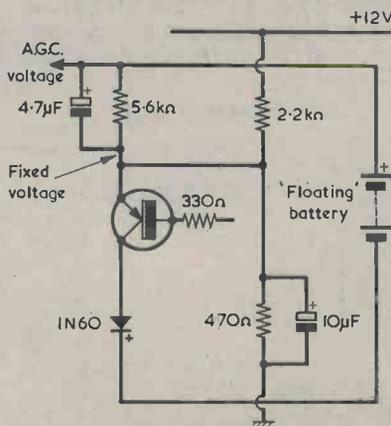


Fig. 4. Redrawing the circuit around the gated a.g.c. amplifier transistor with the action "frozen" to represent conditions during line flyback. The voltage from the line output transformer winding is presented as being given by a "floating" battery with the same polarity. If the transistor base is taken negative of the emitter, the increased collector current flows in the battery and the 5.6kΩ resistor, causing the voltage across the resistor to increase.

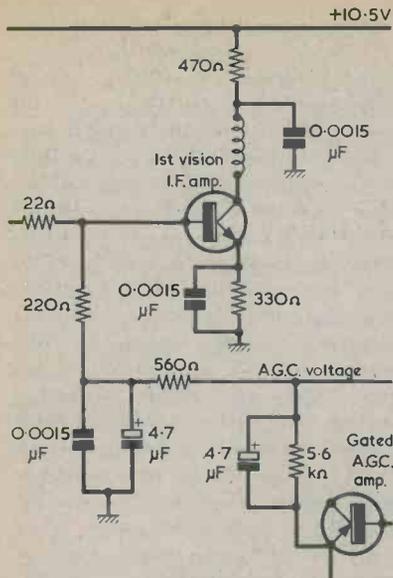


Fig. 5. The a.g.c. voltage at the upper end of the 5.6kΩ resistor is applied via a filter to the base of the first vision i.f. amplifier transistor. The circuit gives forward a.g.c..

rather than decrease it?"

"You're thinking of the a.g.c. systems you find in transistor radios," said Smithy. "With these, the base bias current of an i.f. transistor is reduced when a strong signal is received. But the circuit we've got here uses what is called forward a.g.c. When the a.g.c. voltage from the 5.6kΩ resistor goes positive the increased base bias current in the i.f. transistor causes the internal base-emitter impedance to reduce. This means that there is less signal voltage between the base and emitter and the signal amplitude at the collector goes down. The advantage of forward bias in a television receiver is that the transistor is always giving reasonably linear amplification and there's little risk of cross-modulation effects."

TUNER A.G.C.

"Well, that seems to have wrapped up the a.g.c. business," said Dick with satisfaction. "Just a minute, though, there's another transistor in the a.g.c. circuit. It's called a delayed a.g.c. transistor." (Fig. 6.)

"Ah yes," said Smithy. "That transistor provides delayed a.g.c. for the tuner. As you can

see, it's another p.n.p. transistor, and it's wired up so that under no-signal conditions, the emitter is about 6.7 volts positive of chassis and the collector is about 2.2 volts positive of chassis. Which means that the emitter is positive of the collector, which is just what is required for a p.n.p. transistor."

"The base of that transistor," put in Dick, scowling down at the circuit diagram, "goes to a 470Ω resistor in the collector circuit of the first vision i.f. transistor."

"It does," agreed Smithy. "Now, we already know that the base current of that transistor increases with increased signal strength because of the gated a.g.c. action. For low level signals, the voltage dropped across the 470Ω collector resistor will be such that the base of the delay transistor will be positive of its emitter, and the delay transistor won't pass collector current. If a high level signal comes along, the first vision i.f. transistor will pass increased collector current because of the forward a.g.c., whereupon the voltage across the 470Ω resistor will go up.

This means that the base of the delay transistor will be taken negative. If it goes sufficiently negative to overcome the base-emitter voltage drop, the delay transistor will start to pass collector current, whereupon its collector goes positive. That collector voltage is fed, as an a.g.c. voltage, to the tuner."

"Why," asked Dick, "do you only pass an a.g.c. voltage to the tuner when there are high level signals?"

"The tuner will have a signal frequency r.f. amplifier before the oscillator and mixer stage," replied Smithy, "and the a.g.c. voltage is applied to the r.f. amplifier. Now, it's very desirable to have the r.f. amplifier running at full gain for all but quite strong signals in order that its output over-rides the relatively high degree of noise which is generated in the following mixer circuit. When the input signal strength reaches a level at which a high degree of automatic gain control is being exerted in the i.f. amplifier the voltage delay is overcome, and a.g.c. is then also fed to the tuner. Signal strengths as high

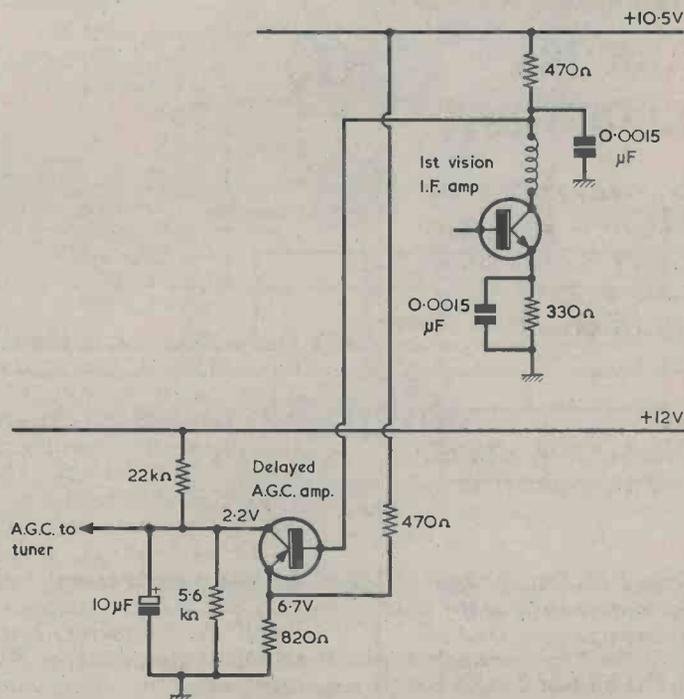


Fig. 6. Details of the delayed a.g.c. amplifier section. This provides a.g.c. for the tuner unit with signal strengths above a pre-determined level.

as this will be capable of overriding the noise which is given in the tuner mixer-oscillator stage. And that's all there is to the delayed a.g.c. section of the circuit."

Smithy glanced at his watch. "I see that I've done it again," he continued.

"Done what?"

"Spent my time nattering to you instead of getting on with my own work!"

Dick grinned.

"You know you enjoy doing it. Besides, it's necessary, isn't it?"

"In what way?"

"To keep this show of ours on the road!"

FAULT FINDING

Smithy chuckled.

"Perhaps you're right," he said. "Anyway, I might as well see this thing through to the bitter end now that I've started getting myself involved in it. The fact that the picture was so strongly over-contrasted when you plugged the outside aerial in makes it fairly probable, but by no means certain, that the fault is in the gated a.g.c. stage rather than in the delayed a.g.c. stage which controls the tuner.

So we'll start an investigation in the gated a.g.c. stage first."

"What sort of checks will you carry out?"

"Ohmmeter checks, I think. Seeing that there seems to be a complete lack of a.g.c. there may be just a simple open-circuit or short-circuit somewhere. Could you get the back off, Dick?"

Obligingly, Dick removed the mains plug from its socket, disconnected the input lead from the outside aerial and took off the back of the receiver. He was soon able to make the printed board available for testmeter checks. Smithy switched Dick's battered testmeter to a low resistance range, short-circuited the test prods and adjusted the set zero control. He next consulted the service sheet and then studied the printed circuit board.

"I'll begin," he announced, "by checking the winding on the line output transformer. Here goes!"

Smithy applied the test prods to the line output transformer winding. (Fig. 7(a).)

"There's very nearly zero resistance there," said Dick, as he observed the meter needle

"Just the odd ohm or so."

"Thank goodness for that," said Smithy in a relieved tone. "I'd had a horrible feeling that the winding might have been open-circuit. If it had been we'd have had to change the whole line output transformer. Well now, there was enough base bias current getting through to the first vision i.f. amplifier transistor for it to work, so I'll assume for the moment that there are no open-circuits in the 2.2kΩ and 470Ω resistors which supply the emitter of the gated a.g.c. transistor, or in the resistors between that emitter and the base of the i.f. transistor. Sync pulses must be getting to the sync separator so let's check that 330Ω resistor in series with the transistor base."

Smithy applied the test prods once more to the printed board. (Fig. 7(b).)

"Did you," asked Dick, "say that the resistance was 330Ω?"

"I did."

"The meter's reading a bit under 280Ω."

"Not to worry," replied Smithy cheerfully. "The lower reading will be due to other resistances in the circuit which


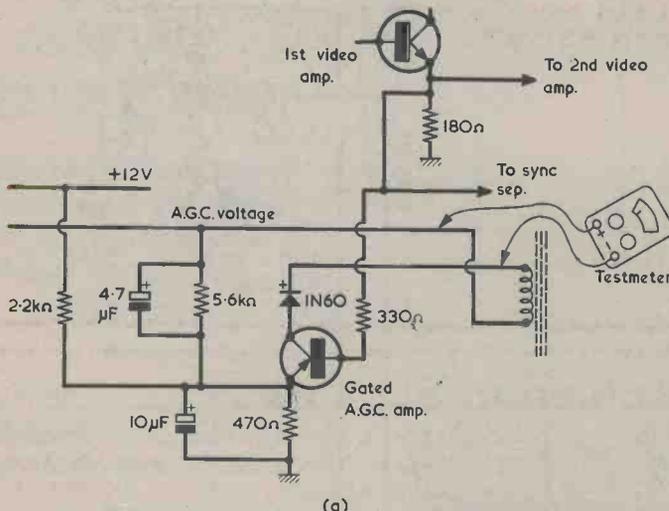


Fig. 7(a). Smithy first checked the line output transformer winding for continuity.

(b). Next to be checked was the 330Ω resistor in the base circuit of the gated a.g.c. amplifier.

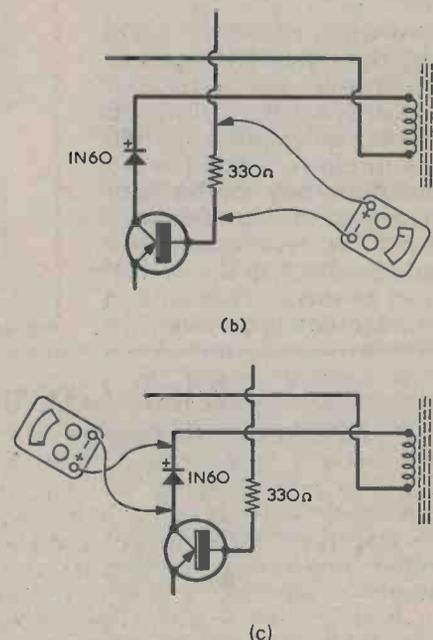(c). Checking the 1N60 diode. A standard analogue testmeter, switched to an ohms range, will pass forward current through a diode when connected with the polarity shown here.



happen to be connected across the one I'm checking. The next things to check are the 1N60 diode and the gated a.g.c. transistor itself. The diode will be the easier, so I'll do that first."

"Is it silicon or germanium?"

"If my memory serves me properly," said Smithy, "the 1N60 is a germanium diode." He glanced at the receiver circuit diagram, "Ah yes, it must be. There's another 1N60 which is used as the vision detector. Now, if I put the negative meter lead to the diode anode and the positive lead to its cathode, the diode should pass forward current and the meter should give a low resistance reading.

Smithy looked carefully at the printed board, then placed the test prods across the diode. (Fig 7(c)).

There was silence for a moment.

"Well," said Smithy, "what does the meter say?"

"It doesn't say anything," replied Dick. "Have you got the test prods in position?"

"Of course I have."

"Well, the needle hasn't even moved."

"Why that's great!" exclaimed Smithy triumphantly. "We've found the fault!"

"You mean the diode's gone open?"

"I mean just that," said Smithy gleefully. "I'll leave it to you to fit in a new diode."

"I don't think," objected Dick, "that we've got any 1N60 diodes in stock. I don't recall our handling any diodes with that type number before."

"Don't worry about it," advised Smithy happily. "Fit an 0A90 in its place. That should be an adequate substitute."

BACK IN SERVICE


Dick soon located an 0A90 in the spares cupboard and soldered it to the printed board in place of the unserviceable 1N60. He then re-connected the television receiver to the mains and once more plugged in the outside aerial.

The pair waited expectantly for the screen to come alive. The tube cathode soon commenced emission and a picture from BBC1 with weak contrast appeared. Smithy adjusted the contrast control and was pleased to find that correct contrast was given when the control was almost at the centre of its travel. He tuned to the local I.T.A. channel to find that the closing scenes of "Police Chopper Emergency Down Under" were being screened, and were being rep-

duced by the set with exactly correct contrast. He next removed the outside aerial and connected the loop aerial, to find that both channels produced a slightly noisy picture which still, nevertheless, had correct contrast.

"Another job done," he announced with satisfaction, tuning back to the I.T.A. signal and advancing the volume control.

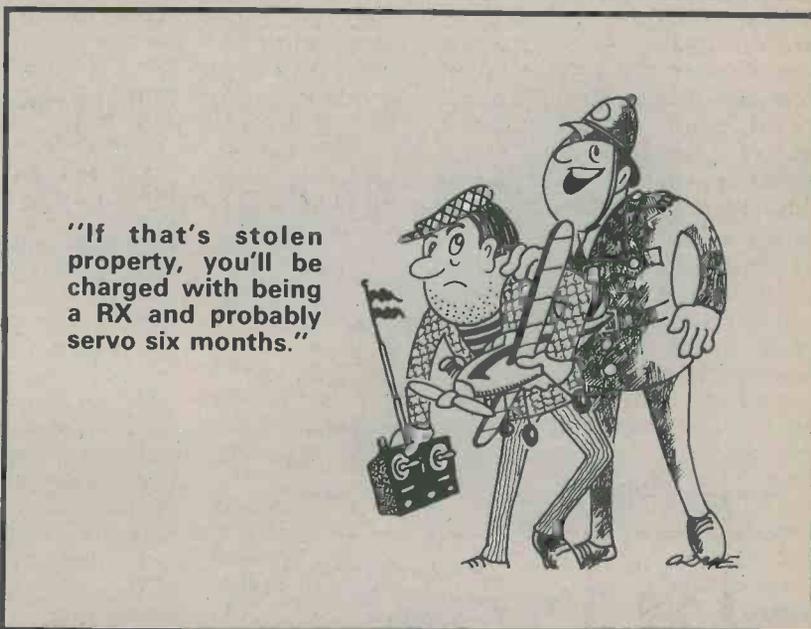The Workshop was suddenly filled with the sound of twittering birds. "And here," said a resonant voice from the speaker, "is the news that all British pet-lovers have been waiting for. The makers of Woof-Woof, the Wonder Dog Food, now proudly introduce their new product: Splat-Splat, the Wonder Bird Seed."



Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who have become the subject of liquidation or bankruptcy proceedings and who fail to supply goods or refund money. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.

For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

SLIDE PROJECTOR PULSER

By C. J. Bowes

Controls an automatic slide projector to give programmable intervals between slides

There are many occasions, such as at Exhibitions and lectures, when it is desirable to show a series of slides in sequence. The unit described in this article is designed to assist in such presentations by automatically changing the slides with an interval set by means of the speed control. This avoids the necessity of stationing someone alongside the projector to operate the slide change control.

It is suitable for use on any remote control slide projector but operates more easily on those models designed to take circular magazines since these can be started and then left unattended. The pulser can be used on projectors with different magazine mechanisms but it may be necessary to replace the magazine after it has run through the machine.

The device is designed to run off the power supply contained in the projector (usually used for operating the remote slide change and focusing mechanism) but if desired a separate power source, such as that shown in Fig. 4 can be used instead.


CIRCUIT DESCRIPTION

The pulser circuit diagram is shown in Fig. 1. and it can be considered in two parts. The part of the circuit to the left of and including R1, forms a power supply providing 12 V d.c., which is used to operate the timing and operating circuit.

The power supply consists of a smoothing capacitor C5, which removes any a.c. ripple from the voltage supplied by the projector and C1, C2 IC 1 & R1 which form a voltage stabilizer network which reduces the voltage supplied by the projector (of the order of 20 V) to a steady 12V suitable for operating the timer. Strictly speaking it is not necessary to fully stabilize the supply but this circuit provides a relatively cheap method of reducing the voltage from the projector and makes the circuit suitable for all voltages of operating mechanism.


The only important points concerning this section of the circuit are to make certain that the projector uses a d.c. voltage in excess of 15 V at the control

Fig.1. Circuit diagram of projector pulser. To the left of R1 the circuit is a conventional +12 V power supply

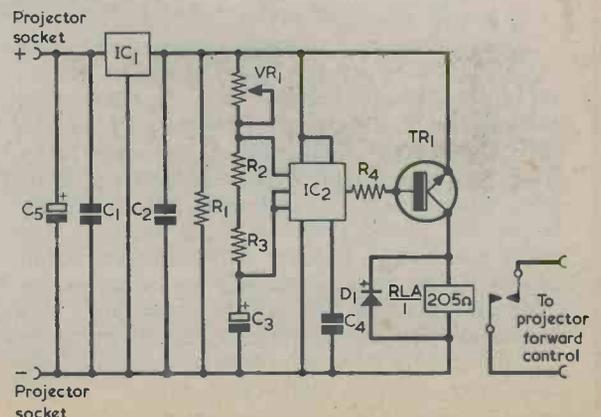



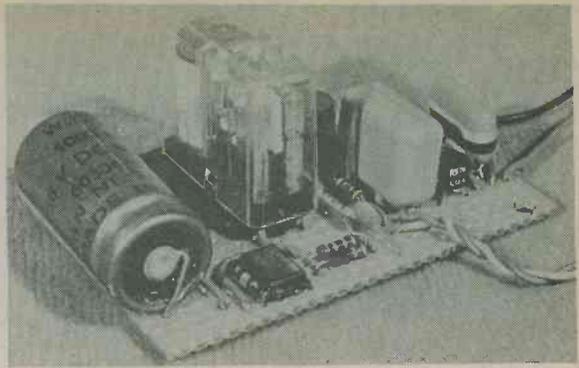Completed Veroboard with components ready for installation



socket (a look at the circuit diagram or interior of the projector will soon show this) and to ensure that both C1 & C5 are rated for working at the voltage supplied by the projector power supply.

PROJECTOR PULSER

The timing circuit is operated by a 555 timer, IC2. This useful device is programmed to produce an output from pin 3 which switches from +12 V to 0 V in a cycle controlled by VR1, R2, R3 & C3. The period for which this voltage remains positive is the interval between slide changes. In the circuit shown this period is adjusted by altering the setting of VR1 and with these component values the interval can be adjusted between 5 seconds and 2 minutes.

The time for which the output is at 0 V, which operates the slide change mechanism, is set by C3 and R3. The values given for Fig. 1. set this time to approximately 0.5s, which is generally long enough to operate the slide change mechanism of most projectors without giving a double change effect. If this time is too short it can be lengthened by increasing the value of R3, similarly the time can be shortened by decreasing the value of R3. The timer drives a relay through a simple transistor current amplifier circuit comprising Tr 1 and R4. D1 is a protection diode which limits the collector voltage when the relay is turned off.

The relay contacts operate the slide change mechanism and the unit is therefore universal in its application since it is capable of switching any polarity of current or voltage used on projector slide change mechanisms.

The alternative power supply, shown in Fig.4. is conventional and replaces part of the power supply section of Fig.1. This type of supply should be used if the projector remote controls are operated by an a.c. supply.

CONSTRUCTION

A straightforward method of construction is to mount all the components except for C5 (which is likely to be fairly bulky) on a piece of Veroboard. The board should be cut to size and the tracks cut to the pattern shown in Fig.2. The three mounting holes should be drilled using a 3mm bit.



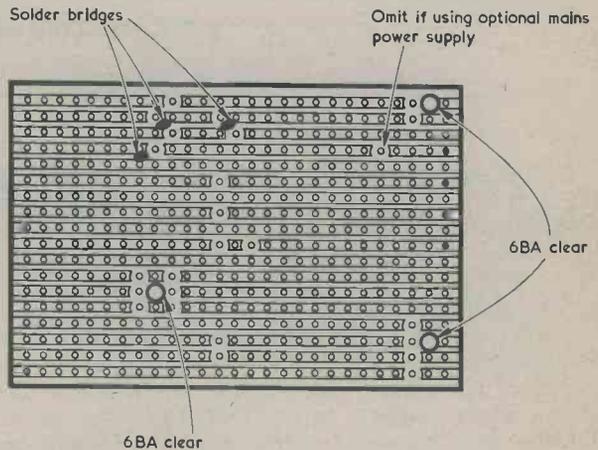


Fig.2. Veroboard cutting details. The tracks can be cut using a 4mm twist drill. All components except C5 and the alternative power supply are mounted directly on the Veroboard. Veropins may be used to make the external connections

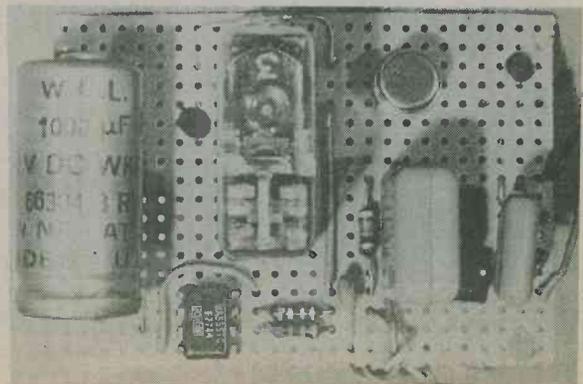

Veroboard layout

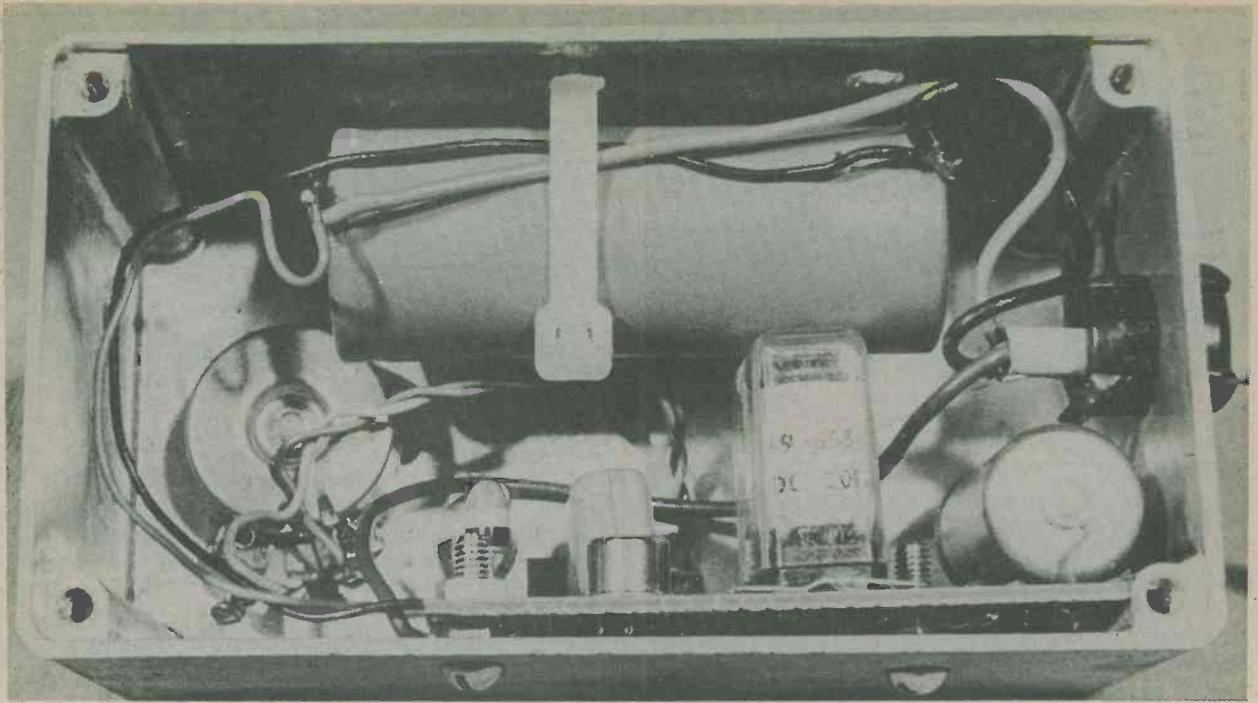



Completed unit, interior view

The components should be mounted as shown in Fig.2. It will be found easier to do this if the smallest components are mounted first. Once the components have been mounted the board should be carefully inspected for errors, broken tracks and solder bridges before testing.

If a d.c. power supply of between 15 and 50 volts is available the circuit can be tested using this, but it is important to ensure that C5 is incorporated in the circuit when testing is carried out. The relay should click in and release at a rate dependent upon the setting of VR1.


If this is satisfactory the device can be mounted inside a suitable box once the correct connections to the projector have been worked out. C5 should be connected to the positive and negative power supply leads from the projector and secured in the box. The

appropriate connections from the Veroboard to the projector remote control plug and to C5 should then be made and the Veroboard and VR1 mounted inside the box.

CONNECTING TO THE PROJECTOR

The correct plug connections to the projector should be worked out, preferably from the projector manufacturers circuit diagram and the connections made by a suitable cable. The positive and negative power supplies are usually connected to the focusing switch and the forward slide change contacts to the forward button of the remote control unit.

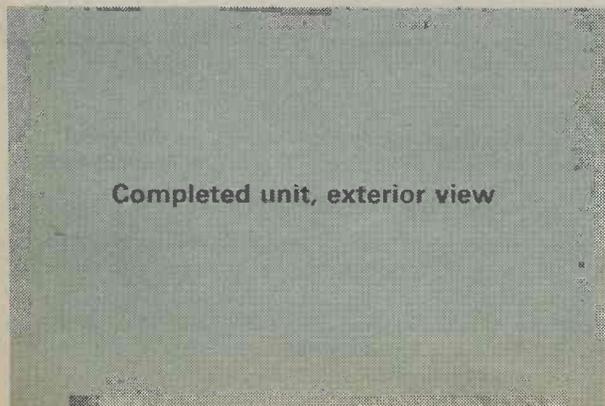On some projectors the forward control operates by making a connection between one of the power supply contacts and the forward control pin on the



Completed unit, exterior view



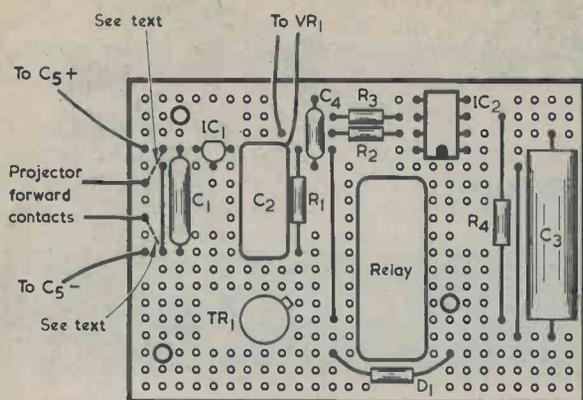


Fig. 3. Component layout on Veroboard

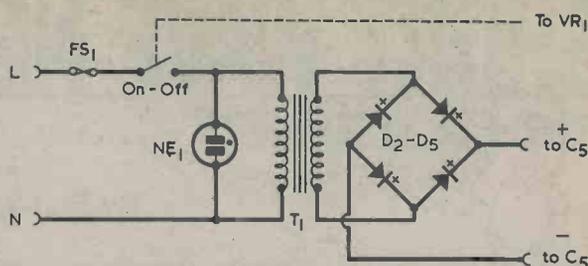


Fig. 4. Mains power supply for use when the projector supply is not suitable.

When using this supply IC1, R1, C1 and C2 (see Fig 1) can be omitted

The mains indicator Ne 1 must include a suitable limiting resistor

CAUTION: This circuit is mains powered and must be properly built into a protective box.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

R1 4.7K Ω

R2 2.2K Ω

R3 560 Ω

R4 6.8K Ω

VR1 100K Ω potentiometer, linear (with mains switch if a separate mains power supply is to be used).

Capacitors

C1 0.22 μ F

C2 0.47 μ F

C3 100 μ F 16V electrolytic

C4 0.1 μ F

C5 2200 μ F 40V electrolytic

Semiconductors

IC1 78L12 (12V 100mA regulator)

IC2 555 timer

TR1 BC461 or equivalent.

D1 IN914, IN4148, IN4001

Miscellaneous

Relay 12V 205 Ω printed circuit relay (RS type 349-658)

Veroboard 0.1 in. pitch 18 lines x 26 holes.

Plug to suit projector remote control outlet.

Knob for VR1.

Case to hold complete unit

Connecting cable.

Mains cable if required.

Nuts, bolts, plastic straps etc.

remote control socket. In this case a suitable wire link can be made on the Veroboard between the appropriate power supply line and the relay. This is shown by the two dotted lines marked on Fig. 3. Of course **only one** connection should be made and **not both of the connections shown**. The remaining relay contact should be connected to the "forward" pin on the remote control plug.

If the alternative power supply is used then the only connections to the projector are from the two relay contacts to the forward contacts on the remote con-


trol plug, the power supply leads to the Veroboard layout being connected to C5 on the power supply.

USING THE UNIT

The projector should be set up and focussed in the normal way. The pulser unit is then plugged into the projector and VR1 is set to give the required time between slide changes. The projection programme is most effective if a full magazine is used as the projection sequence is then uninterrupted.

SHORT WAVE NEWS

FOR DX LISTENERS

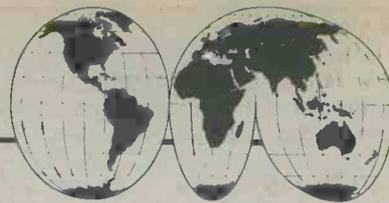

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

In these columns last month we dealt with the rather meagre results achieved in the quest for reception of transmissions from Laos and expressed the hope that greater success would be apparent after the next season. This month we very briefly review some of the log entries made with respect to other far-eastern based transmitters.

Information from China about some of the local stations is not all that plentiful, much of it provided by fellow enthusiasts listening sessions and the publication of such details in the SWL press. For those who would like to swell the ranks of the 'China-watchers' why not add the following to your list of targets?

● CHINA

PBS Hangzhou, Zhejiang, on **4785** at 2304, female announcer with a talk in Chinese. This rarely heard station was very soon blotted out by commercial QRM, in fact it is the first time I have logged this one owing to the unremitting interference usually on this channel but absent just long enough to make a log entry. Sheer good luck in fact! This is Zhejiang 1 which has a schedule from 2100 to 0500 and from 0850 to 1415 with local programmes and relays of Beijing (Peking) 1.

Xining, Qinghai, on **4940** at 1513, OM and YL alternate in Chinese. This one was audible under QRM from the more powerful Kiev transmitter in the Ukrainian SSR. Xining features both local and Home Service 1 programmes and operates from 2150 to 0100 and from 0930 to 1525.

Guizhou, Guiyang, on **7275** at 1435, OM with a talk in Chinese. The schedule is from 2130 to 0020, 0150 to 0620 and from 0850 to 1600.

Neimenggu, Hohhot, on **7300** at 1120, OM with the usual talk in Chinese. The schedule on this particular channel is unknown.

This review will be continued in the next issue.

AROUND THE DIAL

In which we feature some items of possible interest to readers of these columns. All details are correct at the time of writing although some may be subject to change during the intervening period. Most however will remain constant.

● SPAIN

Madrid on **9765** at 1910 when radiating a programme about Latin American folk music and its

origins followed by station identification and "Press Review" – all about local affairs – in the English programme for Europe, scheduled from 1900 to 2100 hours. It is however a one hour programme repeated.

● U.S.S.R.

Radio Moscow on **9585** at 0140, OM with a programme in Standard Chinese to China, scheduled from 0000 to 0300 on this channel.

● AUSTRALIA

Melbourne on **9570** at 0750, YL with pop song, OM announcer in the English programme for Europe scheduled from 0700 to 0900 on this frequency. Local temperatures announced at 0753.

Melbourne on **17725** at 0758, 'Waltzing Matilda', OM with station identification, frequency details and programme review, time-check for 0800 then a review of world news in the English programme for Europe (schedule as above). Also logged in parallel on **17725** and **21680**.

Melbourne on **21570** at 1018, pops on records, OM announcements in the English Service to the Pacific, Papua and New Guinea, scheduled from 0800 to 1100 on this channel.

● AFGHANISTAN

Kabul on **4740** at 0152, OM with songs and local-style music in the Home Service 1, schedule from 0125 to 1930.

● YEMEN ARAB REPUBLIC

Sana'a on **9780** at 1850, YL with Arabic songs, local-style music in the Home Service, scheduled here from 0300 to 0700 and from 1000 to 2100 (Fridays from 0300 through to 2100). Also logged in parallel on **4853**.

● CANADA

RCI (Radio Canada International) Montreal on **9555** at 1550, OM with station identification followed by a light musical interlude in the English programme for the U.S.S.R., scheduled from 1545 to 1600. This is a BBC Daventry relay of RCI.

● NETHERLANDS ANTILLES

Radio Nederlands, Bonaire, on **9715** at 0630, OM with station identification after the National Anthem. The Dutch programme for New Zealand followed, being timed from 0630 to 0725. Also logged in parallel on **9630**.

● **ISRAEL**

Jerusalem on **15585** at 1054, YL with a ballad in the Hebrew languaged Domestic Service Network B programme scheduled on this channel from 0610 to 1400 and from 1800 to 2000.

● **CAMEROON**

Radio Bertoua on **4750** at 2018, OM with announcements in French, local-style songs and chants. The schedule is from 0430 to 0800 and from 1600 to 2208, the power is 20kW.

● **NIGERIA**

Lagos on **4990** at 0506, OM with details of forthcoming programmes and station announcements in English. This is the National Programme which is in English and vernaculars and operates from 0430 to 1000 and from 1700 to 2310. The power is 20kW.

● **HONDURAS**

Radio Lux, Olanchito, on **4890** at 0227, local pops on records, OM announcer, commercials, two chimes and gabbled identification at 0232. Sign-off at 0300 after station identification over some soft and sweet music (not the National Anthem).

● **BRAZIL**

Radio Difusora Taubate, on **4925** at 0233, OM song in Portuguese, local-style dance music. This one operates from 0830 to 0300 and the power is 1kW.

Radio Cultural do Para, Belem, on **5045** at 0149, OM with pops in typical local manner. Station identification at 0200. The schedule is from 0900 to 0300 although it has been reported closing as late as 0700. The power is 10kW.

● **VENEZUELA**

Radio Sucre, Cumana, on **4960** at 0315, OM station identification in Spanish, local songs and folk music. The schedule is from 1000 to 0400 and the power is 1kW.

Radio Reloj Continente, Caracas, on **5030** at 0323, OM with local and world news in Spanish, frequent chimes between news items and several station identifications. This one is times from 0900 to 0500 and the power is 10kW.

● **COSTA RICA**

Faro del Caribe, San Jose, on **5055** at 0342, OM with a recorded religious programme in English followed by announcements of times of transmission, frequencies and address. National Anthem and off at 0353. The schedule is from 1030 to 0400 but has been reported closing at 0430 on occasions. The English programme is timed from 0300 to 0400 and consists mainly of American religious organisations taped programmes. The power is 5kW.

● **GREECE**

VOA (Voice of America), Kavalla, on **9770** at 0435, OM with a newscast of world events followed by the "Breakfast Show".

● **CLANDESTINE**

Bizim Radyo (Our Radio) on **9585** at 1507, OM with a news commentary in Turkish. This transmitter, located in East Germany, also identifies as "Voice of the Communist Party of Turkey" prior to some transmissions. ("Turkiye Komunist Partisinin Sesi").

● **CHINA**

Radio Peking on **9860** at 1512, YL with a news

review in the English programme directed to South Asia and scheduled from 1500 to 1600.

Radio Peking on **9880** at 1446, YL with the programme in Sinhalese for Sri Lanka, scheduled from 1400 to 1500.

PBS (People's Broadcasting Station) Nei Menggol on **7300** at 1453, YL with songs in Chinese, local-style music.

● **TAIWAN**

VOFC (Voice of Free China) Taipei on **9630** at 1240, YL with songs in Chinese, YL announcements and identification in Chinese at 1245.

VOFC Taipei on **9610** at 2115, OM and YL with an English/Chinese language lesson. Signal wiped out by Cologne signing on with interval signal and announcements at 2126.

● **VIETNAM**

Ho Chi Minh City on a measured **9623** at 1302, military music, YL in Vietnamese in the Domestic Service. The schedule of this one is from 2157 to 0030 (to 1540 on Saturdays), from 0200 to 0600 (not Sundays) and from 0930 to 1540 (not Sundays). All programmes are in Vietnamese.

Hanoi on **10040** at 1342, YL with station identification during the French programme intended for South East Asia and scheduled from 1300 to 1400 on this frequency.

● **SOUTH KOREA**

KBS (Korea Broadcasting System) Seoul on **15575** at 1049, YL with announcements and station identification, OM with a newscast mainly composed of local affairs. All in the English programme intended for Latin America, South East Asia, Africa, the Middle East and North Africa, scheduled from 1000 to 1100.

Seoul on **9870** at 1430, OM and YL announcers at the commencement of the Standard Chinese programme beamed to China, Korea and South Asia and scheduled from 1430 to 1520 on this channel.

● **PHILIPPINES**

FEBC (Far East Broadcasting Company) Manila on **9715** at 1440, OM and YL with an English/Chinese language lesson. This Standard Chinese programme is radiated to the Far East and South East Asia and is scheduled on this particular frequency from 1400 to 1615.

VOA (Voice of America) Tinang on **9555** at 1404, OM with announcements in an Asian dialect after 'Yankee Doodle' interval signal. The morning/afternoon schedule is from 0800 to 1700.

● **INDIA**

AIR (All India Radio) Delhi on **7280** at 1500, YL with station identification and programme review then OM with news of purely local affairs, all in the Domestic Service English programme.

● **PAKISTAN**

Karachi on **17665** at 1008, OM with a newscast of world affairs in the English section of the World Service transmission to the U.K., scheduled from 0715 to 1100 on this channel. The English newscast is timed from 1005 to 1010, most of the remainder of the transmission being in Urdu.

AMATEUR SATELLITE NEWS REPORT

By Arthur C. Gee

First Bulgarian Satellite: On the occasion of the 1300 years jubilee of the creation of the Bulgarian State, later this year, the first Bulgarian satellite is to be launched. Designated B-1300, it will have a near circular orbit at 900 Km in an inclination of 85 degrees. The satellite will be equipped with laser reflectors, for laser tracking, thereby giving an improvement in detailing the satellite's position. Amongst the experiments to be carried out will be an investigation into the influence of the atmosphere on orbital parameters. The coordinator and manager of the "B-1300" tracking program is the Central Laboratory for Geodesy of the Bulgarian Academy of Sciences, Sofia 7, Noemvri - Str. No. 1, Bulgaria.

University of Surrey's UOSAT Scientific Satellite Progress: Britain's first amateur satellite-UOSAT-which is under construction at the University of Surrey, is now entering its final stages before launch into a polar earth orbit on the 15th September next. It is scheduled for launch on a NASA Delta 2310 rocket, along with a Solar Mesosphere Explorer Spacecraft, from the Western Test Range at Vandenberg, California, U.S.A. The programmed orbital elements are: - Altitude 530 Km; inclination 97.5 degrees; period 98 minutes. Assuming all goes to plan, launch time is to be 11.19 GMT and the separation from the launch vehicle should be at 12:30 GMT over the Sudan.

International Solar Polar Mission in Jeopardy: Severe budgetary cuts imposed on NASA by the Office of Management and Budget in preparation of the Reagan Administration's federal budget, resulted in NASA's decision to cancel the American spacecraft forming part of the two-spacecraft International Solar Polar Mission.

The European Space Agency, the other partner in the project, has however, rejected this decision. At a high level meeting between the two agencies in February last, ESA officials pointed out that this decision had been arrived at without consultation with the ESA, which was a breach of the Memorandum of Understanding between the two agencies.

As a result of this decision, European scientists from 17 scientific institutes who were supplying experiments for the NASA spacecraft, would no longer be able to fly them. These experiments were in many cases, in an advanced state of development. More than 50% of the total costs had been committed and would consequently be lost without corresponding scientific return. Furthermore, ESA pointed out, that when the ISPM project was decided upon, by the ESA Science Programme Committee in 1979, it was chosen in preference to a number of other, purely European missions, because of the value ESA attached to transatlantic cooperation. ESA stressed

that unilateral actions of this kind would be detrimental to future space cooperation between Europe and the U.S.A. The ESA Management Board resolved that immediate and strong action should be taken to obtain the full restoration of the ISPM programme.

European Scientific Spacecraft to Explore Halley's Comet: A major space "first" is going to be undertaken as part of the ESA's scientific activities. The Agency's Science Programme Committee have approved a European project under which a spacecraft will be sent to Halley's Comet. This exploratory mission involves flying a spacecraft through the comet in 1986 at a speed of 70 Km/sec. The scientific objective of the mission is to make measurements of the constituents of the comet's tail, or "coma"; ionised particles, dust, atmospheric constituents, etc, which boil off from the nucleus under the effect of the solar heating. Such measurements, as well as the taking of pictures of the nucleus by means of an onboard camera, are of fundamental importance in understanding the birth of comets, which are believed to consist of matter stemming from the formation of the planets in the solar system.

The spacecraft, derived from the GEOS satellite, will have a payload consisting principally of a camera and mass spectrometers for measuring the atomic composition of the comet. Of a total mass of approximately 750 Kg, it will be launched in July 1985 by an Ariane rocket.

The project has been given the name GIOTTO, which it takes from the "Adoration of the Magi" scene in the famous fresco cycle executed by the Florentine painter, Giotto di Bondone, that decorates the interior of the Arena Chapel, in Padua. Halley's comet, which can be seen in the sky background of the Adoration scene, enters the inner part of the solar system about every 76 years, and one of its appearances was made in 1301. Giotto was consequently able to use it as a model for the star of Bethlehem when he painted the Adoration scene, which he completed in 1304. In a way, Giotto's painting of this star can be considered as the first scientific description of Halley's comet.

The Arsene Project: In the January/February 1981, (No. 5) issue of "ORBIT", - the "Journal of the Radio Amateur Space Program", published by AMSAT; a very interesting account appears of the Radio Amateur Satellite organisation in France, under the heading "The Arsene Project". (ORBIT Vol. 2 No. 1 p.13.)

A group of amateurs in CNES (National Centre for the Study of Space in France) realising that France, the third power in space, is creating its own capability to orbit satellites thanks to the Ariane rocket, felt that France should at the same time, support amateur

radio scope activity, particularly as it is such an advanced technical non-profit cause.

This idea was submitted to the Directors of CNES, towards the end of 1978. They were extremely favourable to supporting a program provided no financial commitment would be required. CNES's active support would consist of providing left-over parts and equipment from prior programs, which were not required for future projects, permitting its employees to take part in the project and helping to make appropriate tests preceding flights. They would also provide space on vehicles for missions not requiring the entire capacity of the Ariane.



The Directors of CNES suggested this idea should be submitted to the French Technical Schools which are training the future leaders in the French Space Program. These schools showed immediate and enthusiastic support for the scheme, many students offering specific participation in their third year thesis, by devoting them to concrete, highly technical projects relating to the program.

Next, most of the French companies, who are involved in the Space program were approached and they agreed to participate. As a first step (for two or three years) these companies will participate by employing and paying trainees from these technical schools and permitting them to work on matters arising in connection with the development project under the supervision of each company's own technical employees. Several have offered to help complete various parts of the satellite as part of the practical training in their own educational program.

In order to formalise the scheme, the Amateur Radio participants who have been most involved, have grouped together under an association called "RACE" - Radio Amateur Club de l'Espace. Since all Amateur Radio operators are more or less involved, the French national amateur radio association, the "Reseau des Emmitteurs Francais" (REF) with its 12000 members has also joined RACE.

The entire effort will be coordinated by a joint committee of the Directors of the Technical Schools involved; the Director of the Space Centre in Toulouse and the President of RACE.

The first project is to build a satellite to be designated ARSENE. It will be about 100 Kgms weight, have two transponders using amateur radio space allocated frequencies, a very high frequency beacon which will be used for a small scientific experiment which is yet to be defined. Stabilization of the satellite will be maintained by coupling with the earth's magnetic field. Energy to be provided by solar panels and rechargeable batteries. Ground communication and control station functions could be maintained by three ground stations, one being located on the French mainland; with the other two located in French Guiana and Reunion Island. All amateur radio stations throughout the world would be able to use the transponders. Technical schools could equip themselves with simple earth stations to make demonstrations and engage in practical experiments. The life expectancy for a satellite as the one envisaged should be several years.

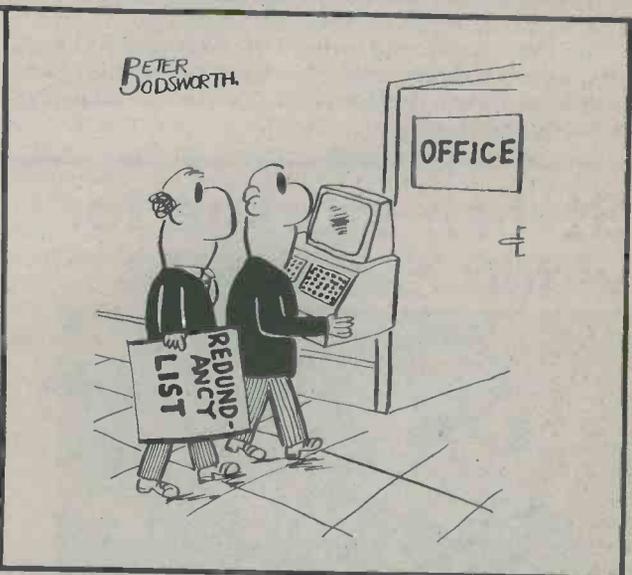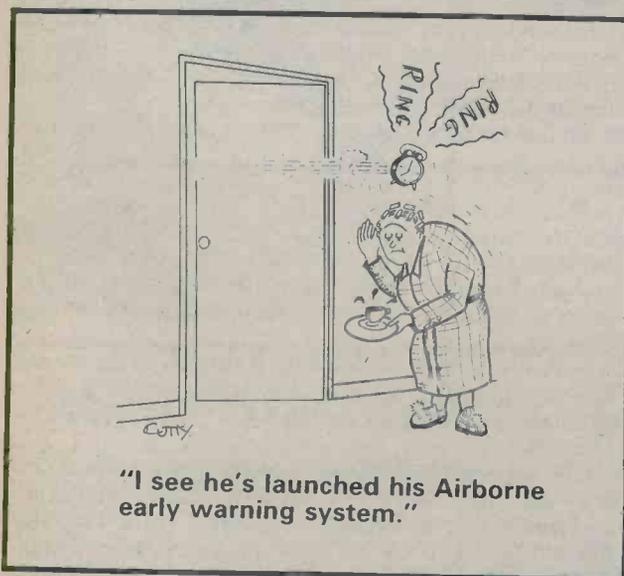

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 80p, inclusive of postage and packing.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

TRADE NEWS

INTEGRATED HI-FI SYSTEMS

The latest design in audio equipment, the integrated hi-fi system, has until recently remained a costly purchase. The introduction of the IS 100 and the IS 200 to the range of audio equipment from Fidelity Radio Limited of Victoria Road, London NW10, sees two products more attractively priced for the middle market.

With the living area in flats and houses becoming more limited many householders are finding free space for their audio equipment an increasing problem. The integrated system has grown in popularity over the last few years as its compactness deals ideally with this situation.

However, the price of these systems has been comparatively high when compared with the selection of music centres that are available. Fidelity Radio is one of the few companies to produce a product which is competitively priced, the IS 100 and the IS 200 are expected to retail at approximately £170 and £200.

The IS 100 is a compact shelf top unit finished in silver with matching open fronted speakers; whereas, the IS 200 has a glass fronted storage cabinet, dark fabric fronted speakers and is finished in a wood effect. The technical specifications for both units are the same.

The record player, with its hinged removable lid, has a semi-automatic two speed belt drive turntable; with stereo ceramic cartridge and cue.

The three waveband radio, LW, MW and FM has LED signal strength and FM stereo indicators; FM mono and mute selection; AFC on FM and frequency shift on long wave.



The new IS 100 integrated hi-fi system from Fidelity Radio seen in its compact shelf top version.

The cassette section has ferrous and chrome dioxide tape selection and noise reduction system. There are also two LED record/power bargraphs and indicators to show which mode is in operation. A tape counter and reset button are also incorporated.

The total output music power is 35 watts into 4 ohms.

Other facilities include: two way speaker system; stereo headphone socket; public address facility; push button controls; rotary volume, bass, balance and treble controls and the unit is fitted with a 13 amp moulded fused safety plug.

Stylish storage for video cassettes



With the proliferation of home video equipment on the market, it is good to know that the important question of video cassette storage has not been overlooked. Elegance combined with utility are two features of the new Lawco Video 90 cassette storage Cabinet.

Suitable for both VHS and Betamax systems, the Lawco Cabinet can house 36 video cassettes, yet is compact in size measuring 673 mm x 394mm x 165mm.

The Cabinet has a highly polished wood finish and is an attractive piece of furniture in its own right. In addition it can easily accommodate a video recorder placed directly on top if space is at a premium. The flat top design also allows for the storage system to grow vertically or horizontally to keep pace with increased demand.

The Cabinet's three drawers are made from tough polypropylene which can be easily wiped clean if dust or dirt accumulates inside. Each drawer contains dividers to ensure the cassettes remain in an upright position. The front opening action allows for easy access and instant visual recognition of the cassettes inside.

The Lawco Video 90 Cabinet has a recommended retail selling price of £36.00 exclusive of VAT.

Further details are available from Lawtons Limited, Stationery & Filing Division, 60 Vauxhall Road, Liverpool L69 3AU.


Octobox cases

Recently introduced by ZAERIX Electronics Ltd, their new OCTOBOX Series of easily assembled, professional quality, Instrument Cases are available in 72 sizes with heights ranging from 80 to 130mm, widths from 150 to 400mm, and depths from 150 to 300mm.

A very rigid and aesthetically pleasing design is achieved by utilising 3mm thick extruded aluminium front and rear panels, firmly attached by countersunk headed screws to 4mm thick side panels, these being manufactured with either plain or 'protruding handle' front edges. Having natural anodised finish, all four sides of these cases are substantial enough to also double as power semiconductor heatsinks.



DIY SILICON CHIP KITS

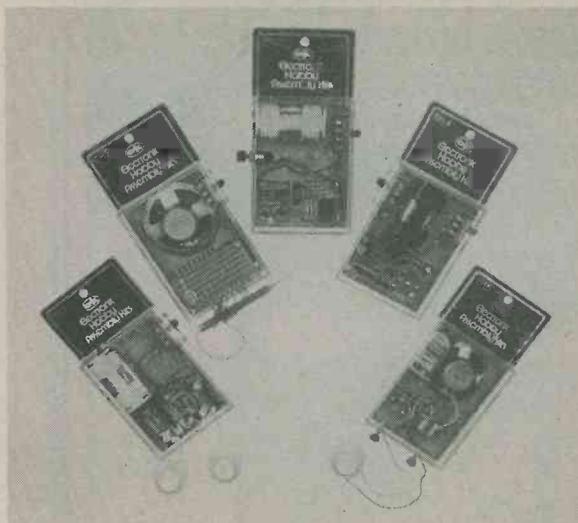

You don't have to be an electronics expert to assemble OK's new range of micro electronic hobby kits. Silicon chip based, these kits have very comprehensive step-by-step instructions which also describe the various terms and components used in electronics. Priced substantially less expensive than many electronic toys from only £3.99 to £8.60, they contain carefully selected components and when made fit into their original plastic packaging containers. OK say that these are suitable for 12 year olds upwards.


Five kits are available, Quick Reaction (£5.80), Electronic Dice (£7.98), Digital Roulette (£8.60), Morse Code (£3.99) and Electronic Organ (£6.70). All prices include VAT and p & p and items are available by mail order or by telephoning OK on 0703 610946 (24 Hour) or 0703 610944 9-5pm and placing a credit card order. OK Hobby Products are at Dutton Lane, Eastleigh, Hants SO5 4AA. Batteries, soldering irons and other tools are not provided but are available from OK. Soldering iron and solder £4.99, pliers, £2.50, cutters £2.99.

Servo amplifier IC for industrial use

To meet the strong market demand for a low cost servo-amplifier suitable for use in general industrial applications, Ferranti Electronics Ltd., Fields New Road, Chadderton, Oldham, has developed and is now offering the ZN409CE, a servo-amplifier device in a 19.3mm (standard length) dual in-line package.

This use of standard packaging has enabled the Company to market the new product at a pricing level which is some twenty five per cent below that of the popular and well established ZN419CE servo amplifier, which in its shorter length package (17.78mm) was specifically designed for use in areas where available space was limited.

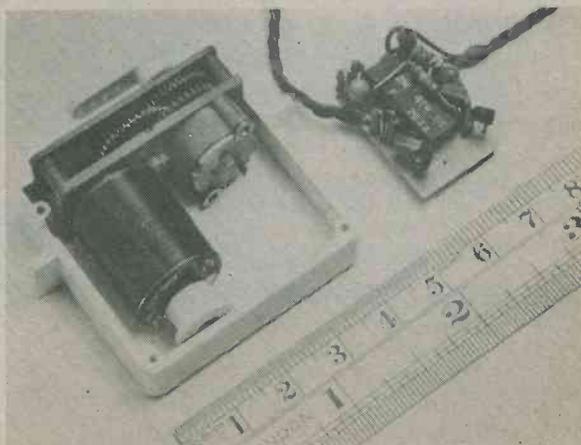
Both the ZN409CE and ZN419CE have the same specifications, either being ideal for inclusion in a variety of pulse-width position control applications ranging from model control to industrial equipment control. The two devices are also well suited for use in motor speed control circuits.




A precision servo-amplifier integrated circuit manufactured by Ferranti Electronics Limited.

DIRECT SUPPLY SERVICE TO READERS

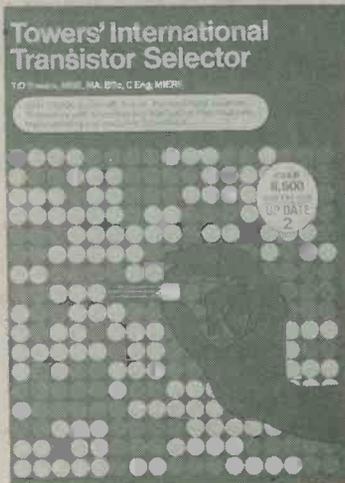TOWERS INTERNATIONAL TRANSISTOR SELECTOR (NEW REVISED EDITION)



This is dead! 
Would this replace it?

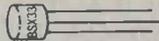

If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. It's one of the most useful working books you will be offered this year. And probably the cheapest! In it, you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries. Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price £10-70 inc P&P

(Please allow 21 days for delivery)

TOWERS INTERNATIONAL FET SELECTOR



If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price £4-60 inc P&P

Tower's International Transistor Selector by T. D. Towers MBE, MA, BSc, C Eng, MIERE £10-70 inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies to the address shown below.

NAME

ADDRESS

.

. (Block capitals)

Tower's International FET Selector by T. D. TOWERS MBE, MA, BSc, C Eng, MIERE £4-60 inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies to the address shown below.

NAME

ADDRESS

.

. (Block capitals)

SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge
£2.00
Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers.

Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. Replies to Box Numbers should be addressed to: Box No. —, **Radio and Electronics Constructor**, 57 Maida Vale, London, W9 1SN.

ANY SINGLE SERVICE SHEET £1 plus S.A.E. Thousands of different service/repair manuals/sheets in stock. Repair data your named TV £6 (with circuits £8). S.A.E. newsletter, price lists, quotations. (0698-883334). Ausrec, 76 Churches, Larkhall, Lanarkshire.

BOOKS. BOOKS. BOOKS. Large range of radio and electronic books in stock. Send s.a.e. for lists. Servio Radio, Dept. REC6, 156-158 Mer-ton Road, Wimbledon, London SW19 1EG.

BOOKS FOR SALE: *Experiments with Operational Amplifiers*, by George B. Clayton. £3.75. *Experimenting with Electronic Music* by Brown & Olsen. £1.20. *Electric Model Car Racing* by Laidlaw-Dickson. 60p. *Electronics Unravelled* by Kyle. £1. *Auto Electronics Simplified*, by Tab Books. £1.20. Box No. G394.

WIRELESS, VALVES, PRE-WAR ONWARD S.A.E. Modern bargains list 15p. Sole Electronics, (REC), 37 Stanley Street, Ormskirk, Lancs., L39 2DH.

B. J.'s DICTIONARY OF CB SLANG. Quality printed. 95p + stamp. Refund if not highly delighted. Trade welcome. Bailey & Co., Tondy, Bridgend, Mid-Glam.

FOR SALE: A number of "D & S" three pin, fused, mains plugs and fuses. S.A.E. for details. Box No. G396.

RADIO VALVES 1930 ONWARDS. Ex-equipment, guaranteed. Magazines, P.W., W.W., etc. S.A.E. list. Malnors Radio, 12 Kirkham Close, Chilton, Ferryhill, Co. Durham, DL17 ORL.

BREAKER, BREAK. Build your own C.B. rig. (27MHz transceiver). Circuit diagram, parts list, etc. All components available in U.K. Send £2.95 & large s.a.e. to: P. Sherwood, 8a Ayles-tone Walk, Manchester, M10 9NU. I'm down and on the side.

(Continued on page 636)

RECHARGEABLE BATTERIES


PRIVATE & TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE SEND SAE
FOR LISTS. £1.45 for Booklet "Nickel
Cadmium Power" plus Catalogue.
Write or call:

*NEW SEALED
LEAD RANGE AVAILABLE*

SANDWELL PLANT LTD

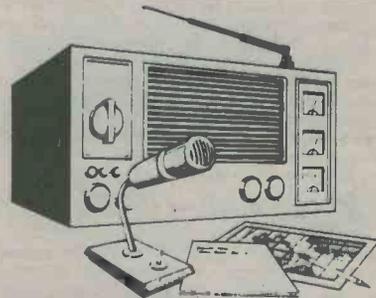2 Union Drive, Boldmere,
Sutton Coldfield, West Midlands,
021-354 9764.



BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact
with the whole world. We give skilled preparation
for the G.P.O. licence.

No previous knowledge required.

Brochure without obligation to :-

**British National Radio
& Electronic School**

4 Cleveland Road, Jersey, Channel Islands.

Name

Address

REC/6/815


BLOCK CAPS PLEASE

Self-Binder

for "Radio & Electronics
Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

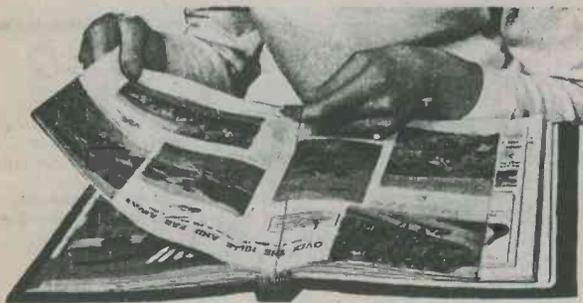

PRICE £2.25 P. & P. 60p
including V.A.T.

For your other magazines

Plain-backed in Maroon or Green
(Please state colour choice)

PRICE £2.25 P. & P. 60p
including VAT

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 635)

FOR SALE: FM Transmitter microphone – hear your own voice on radio, price £15.00. Holograms £12.50. Mini cassette recorder and 10 C60's, £20.00. LED watches £3.50. 50 2W zeners £1.00. 50 BZY88 type zeners £1.00. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

FOR SALE: Newnes Radio TV Service Manuals Volumes 1 – 5 plus 1955-1967. 17 volumes. £1 each, £15 the lot. Telephone Royston (Herts.) 60641.

BOOK CLEARANCE. Bound volumes *Radio & Electronics Constructor* Nos. 27, 28 and 29, £3.00 each. *Cost Effective Projects Around the Home* by John Watson, £1.50. *Talk-Back TV: Two-Way Cable Television*, by Richard Veith, £1.00. *Solid State Short Wave Receivers for Beginners*, by R. A. Penfold, 60p. *50 Simple LED Circuits*, by R. N. Soar, 50p. All prices include postage. Box No. G399.

JOIN THE INTERNATIONAL S.W. LEAGUE.

Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. – both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine etc., £9-00 per annum U.K. Overseas rates on request, Secretary Grove Road, Lydney, Glos., GL15 5JE.

ELECTRONIC COMPONENTS. 6 x CD4011 £1.00. Veroboard 0.1, 4" x 4" 80p. 13 x TIL 209 £1.00. 30 x C280 capacitors 95p. 130 mixed resistors £1.00. 30 assorted electrolytics capacitors 70p. 12 x BC212 £1.00. 40 mixed capacitors 80p. 12 x 2N3702 £1.00. 10 x BC108 £1.00. 7 x TIL 211 £1.00. Add 25p P. & P. Lists 35p. John E. Harris, 9 Ivybridge, Broxbourne, Herts.

FOR SALE: Oscilloscopes, Tektronix 545 with CA plug-in, double switched beam 15MHz. £110. Solartron CD1017 (CT436) compact double beam, 6MHz. £80. Signal generators: RF/AM 100kHz–25MHz £20. Audio, Advance 20Hz – 50kHz £10. Avo electronic multimeter (CT38) £20. Avo 7 £20. 500V megger £15. Large auto transformer 240/115V £10. All working order with handbooks. S.A.E. enquiries please. Carriage extra. Box No. (Middlx.) G400.

FOR SALE: 120 Blank E180 video tapes due to system change. All J.V.C. brand. £5.00 each. Please send s.a.e. for telephone number. Box No. G.401.

(Continued on page 637)

SMALL ADVERTISEMENTS

(Continued from page 636)

100 1N4148 £1. 150 Resistors £1. 100 Capacitors £1. P. & P. 25p. S.A.E. Lists. Dept. R, D. B. Products, P.O. Box 8, York, YO1 1FT.

THE RADIO AMATEUR INVALID & BLIND CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey, KT6 4TE.

FOR SALE: LED non-working repairable watches £2.50 each. C60 cassettes 15p each plus postage 10p. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

FOR SALE: Bound Volume No. 26 Radio & Electronics Constructor 1972/1973. As new. £2.50 plus £1.50 Post & packing. Box No. G402.

MICRO TRANSMITTERS. Range 1 mile. Tunable 60-150MHz. Receive on VHF/FM radio. Supplied assembled and working. With sensitive microphone and data £4.75 plus 25p. P & P. P.D. Electronics, 11 Bluebell Close, Orpington, Kent, BR6 8HS.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

OSCILLOSCOPE TUBE 3" with mu-metal screen, unused, £15 (cost £40). Books: **Radio Constructor 1962-1971** £15 the lot. **Television: 1963-1969** £10 the lot. **Practical Wireless: 1960-1971** £20 the lot. **Wireless World: 1957-1966**, bound volumes, £30 lot. Many others bound. All o.n.o. Telephone: 0622-30504.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

TELEPHONE ANSWERING MACHINE. Build your own for under £10 plus any cassette recorder. Send £3 for circuit and plans. S. D. Cross, 24 Thorney Road, Streetly, Sutton Coldfield, West Midlands.

WANTED - Handbook for the 8 valve Trio 9R-59DE. Please contact P. Bradbury, 2A Colwood Road, Harpenden, Herts., Telephone: 63942.

(Continued on page 639)

REVOR OPTICAL & TECHNICAL

6-SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536



PRICED FROM £148.75 Stereomaster

This microscope's working distance and field of view is relatively large; this feature ensures convenience to the operator who works with both hands while assembling precision mechanisms.

IDEAL FOR PRINTED CIRCUITS AND OTHER DELICATE WORK. COMES COMPLETE WITH

built-in x 10 Mag.
Objectives x 20
Objectives x 35
At extra cost

We stock one of the largest selections of second hand microscopes and optical magnifiers, on and off stands. Please phone for details.

A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs - they can do the same for *you*.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
Radio TV Electronics Technicians'
Electrical Installations Technicians'
Electrical Installation Work
Radio Amateurs'

MPT Radio Communications Cert

EXAMINATION STUDENTS - GUARANTEED COACHING UNTIL SUCCESSFUL

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:
Electronic Engineering & Maintenance
Computer Engineering/Programming
Radio, TV & Audio Engineering
& Servicing
Electronic Engineering Installations & Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name Age

Address

Occupation

ICS

Accredited by CACC
Member of ABCC

To International Correspondence Schools
Dept 278H, Intertext House, LONDON
SW8 4UJ or phone 01-622 8911 (anytime)

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the issue of RADIO & ELECTRONICS CONSTRUCTOR

➔			

15 words at 14p
equals £2.10

**ALL WORDING
IN
BLOCK LETTERS
PLEASE**

Enclose remittance being payment at 14p a word. **MINIMUM £2.50**
Box Number, if required, 50p extra.

NAME
ADDRESS

*Copy to be received four weeks prior to publication.
Published on the 3rd of every month, forward dated.*

INTERNATIONAL SHORT WAVE LEAGUE



Membership £9.00 per annum (Overseas rates on request) including 12 monthly issues of *Monitor* – the League journal. Including free use of all Services, QSL Bureau etc.

THE LARGEST S.W.L. ORGANISATION IN THE WORLD

For full details write to:
**The Secretary,
I.S.W.L.,
1, GROVE ROAD, LYDNEY,
GLOS. GL15 5JE.**

BUILD YOUR OWN

P.A., GROUP & DISCO SPEAKERS by R. F. C. Stephens
Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman
(full constructional details for versions using 15", 12" and 10" (drive units). £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens
This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING
5 Swan Street, Wilmslow, Cheshire

PRINTED CIRCUIT BOARDS FOR "RADIO & ELECTRONICS CONSTRUCTOR" PROJECTS.

OCT 20dB amp. Part 1 68p plus 30p P&P
NOV. 20dB amp. Part 2 62p plus 30p P&P
NOV. Basic Med. Wave radio 69p plus 30p P&P
DEC. Volume Expander £2.25 plus 30p P&P
FEB. '81 Cricket Game £1.67 plus 30p P&P
APR. Med. & Short Wave radio £1.20 plus 30p P&P
APR. Active tone control mod. £1.25 plus 30p P&P
All boards ready for use, roller tinned and drilled,
glassfibre.

Trade enquiries welcome. Highly competitive prices.

Write now for quote to:
BRB PRINTED CIRCUITS (REC)
109, Potter Street, Worksop, Notts. S80 2HL.

SMALL ADVERTISEMENTS

(Continued from page 637)

FOR SALE: Photographic enlarging equipment: Vivitar enlarger. Model E.36 with 50mm f. 3.5 and 75mm f.3.5 lenses. Kodak safety light. Kodak contrast filter set. 11 in. x 14 in. printing frame with copying facilities. Measuring flask. Three trays, three tweezers. Three plastic bottles. Clips. Printing paper. Antistatic brush for cleaning negatives. Kodak Photoguide Booklet. Man's protective apron. £75 o.n.o. Pair of Goodman's speakers 8 ohms, 15 watts, £50 o.n.o. R. L. Gee, 9 Glanmead, Shenfield, Essex.

INTERESTED IN RTTY? You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk, NR32 3PJ.

OSCILLOSCOPE, Calscope, (Scopex) Super 6, single beam 6MHz. Little used, now surplus. £100. Telephone: Tonbridge (0732) 832923 after 6 p.m.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Ick-nield," Hilly Plantation, Thorpe St. Andrew, Norwich, NR0 85S.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

TWO'S COMPANY for friendship/marriage. Introductions with the personal touch for people of discernment. Brochure on request. TWO'S COMPANY, Dept. 1E/R, 111 High Holborn, London WC1V 6JS. Telephone: 01-242-2345.

SPONSORS required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary; 195 White Woman Lane, Old Catton, Norwich, Norfolk.



The larger Catalogue that means FREE POSTAGE IN U.K.

ADDITIONAL DISCOUNTS

GUARANTEED SATISFACTION

GOOD STOCKS GOOD DELIVERY

We pay postage.

Semi-Conductors • I.C.s • Opto-devices • Rs and Cs in great variety • Pots • Switches • Knobs • Accessories • Tools • Materials • Connectors

ELECTROVALUE

FREE FOR THE ASKING

ELECTROVALUE LTD., (RC6), St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB. Phone: 33603 (London 87) STD 0784. Telex 264475.

NORTHERN BRANCH (Personal shoppers Only): 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

THE SPECTACULAR 1981 GREENWELD

Component Catalogue Bigger and better than ever!!!

- 60p discount vouchers
 - First Class reply paid envelope
 - Free Bargain List
 - Priority Order Form
 - VAT inclusive prices
 - Quantity prices for bulk buyers
- SEND 75p FOR YOUR COPY NOW!!!

CALC CHIPS 60p!!!

New full spec. supplied with data. Type MK50321 - full function inc. memory. Only 60p.

DISPLAYS

8 and 9 digit 7-segment bubble type for above chips - most have minor faults dud segment etc. Mixture of 2 or 3 different types with data. 5 for £1.00

NICADS

Ex-equip size C approx. £1 each; 10 for £8.00

1N4006 DIODES

Special purchase of 1A rects, Russian made. Packed in boxes of 300, £8.50 per box; 4 boxes £30.00; 10 boxes £75.00

DISC CERAMICS

0.22uF 12V 9mm dia. Ideal for decoupling. 100 for £2.75; 1000 £20.00 0.05uF 12V 15mm dia. 100 £1.50; 1000 £12.00

Pack of disc ceramics, assorted values and voltages - 200 for £1.00

TRANSFORMERS

Mains primary, 50V 20A sec. £20.00 Mains pri. 110V 15A sec £30.00; 20A £40.00

FSRA60 relay, 2 x 10A contact, 1M, 1B. Coil is 250R, and rated 60V ac, but works on 12-24V DC. Solid Encapsulation with screw terminals makes it ideal for car use. £1.20

ALL PRICES INCLUDE VAT; JUST ADD 40p POST

SLIDER POT SCOOP!!!

Made by Pifer, type PL40CP Silly prices for superb goods!!!

PL40CP - 69 x 16 x 9mm, 40mm slide length. 220R, 2k2 or 10k lin only. Prices (any mix): 1-24 20p; 25-99 17p; 100+ 14p.

TTL, LINEAR, OPTO

All new full spec - Fairchild/SGS: TTL: 5400 5401 5402 5403 5404 5405 5410 5421 5430 5450 5451 5453 5460 - All 12p ea. 5470 5472 5474 5475 5476 5480 5486 5490 54107 54121 54122 - All 20p ea. 5482 54126 - 40p ea. Others (74S, H) on B/L 12 (SAE please)

LINEAR: 9665 or 9666, 7 x 50V Darlington in 16 DIL 60p; 75452 or 4 dual periph driver 70p; XK1444 7 CMOS P-channel buffers, 15V 16DIL 24p.

OPTO: Isolators, FCD831 60p; TIL115/118 60p; FPE100/106 Infra red LED £2.50; FND847 7 seg 0.8" CA £2.00; FND850 CC £2.00 (Data on request for linear & opto devices)

TRANSISTOR PACK K516

Take advantage of this unbelievable offer!!! Small signal NPN/PNP transistors in plastic package at an incredibly low, low price!!! Almost all are marked with type number - almost all are full spec devices, some have bent leads. Over 30 different types have been found by us, including BC184/212/238/307/328; BF196/7; ZTX107/78/9/342/450/550 etc. Only available as a mixed pack at £3/100; £7/250; £25/1000.

REGULATED PSU PANEL

Exclusive Greenweld design, fully variable 0-28V & 20mA-2A. Board contains all components except pots and transformer. Only £7.75. Suitable transformer and pots £6.00. Send SAE for fuller details.

GREENWELD

443G Millbrook Road Southampton SO1 0HX

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 60p each, p&p 20p

Issue(s) required

Annual Subscription

Price £9.50 inland, £10.50 overseas (including Eire)

post free, commence with issue

Bound Volumes:

Vol. 27.	August 1973 to July 1974	Price £3.00, post & pkg £1.50
Vol. 28.	August 1974 to July 1975	Price £3.20, post & pkg £1.50
Vol. 29.	August 1975 to July 1976	Price £3.50, post & pkg £1.50
Vol. 30.	August 1976 to July 1977	Price £3.70, post & pkg £1.50
Vol. 31.	August 1977 to August 1978	Price £5.20, post & pkg £1.50
Vol. 32.	September 1978 to August 1979	Price £5.50, post & pkg £1.50
Vol. 33	September 1979 to August 1980	Price £6.20 post & pkg. £1.50

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price £2.25, post & pkg 60p

With no title on spine, maroon

Price £2.25, post & pkg 60p

With no title on spine, green

Price £2.25, post & pkg 60p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages Price £1.20, P.&P. 30p

DB6 Radio Amateur Operator's Handbook,
New edition in course of preparation

DB17 Understanding Television, 504 pages Price £3.95, P. & P. £1.20

DB19 Simple Short Wave Receivers
140 pages Price 80p, P. & P. 30p

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording – White – 6 sheets Price £1.50, P. & P. 13p

Set 4: Wording – Black – 6 sheets Price £1.50, P. & P. 13p

Set 5: Dials – 6 sheets Price £1.50, P. & P. 13p

Prices include V.A.T.

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

THE LOWEST PRICES FOR PRIME CMOS/TTL/74C IN THE UK

TRANSISTORS

LINEAR ICs	1.00	1.60	2.15	4000 series	4566	7448	0.56	74125	0.40	74190	0.55	7405	0.14	7496	1.20	74190	0.60	74C CMOS	18p
TBA120S	1.00	1.60	HAI1223	4000	4566	7448	0.56	74125	0.40	74190	0.55	7405	0.14	7496	1.20	74190	0.60	74C CMOS	BF194
L200	1.95	1.60	HAI1225	4001	4568	7450	0.14	74126	0.40	74191	0.55	7408	0.14	74107	0.25	74191	0.60	74C CMOS	BF195
U247B	1.28	1.60	HAI1202	4002	4568	7451	0.14	74128	0.65	74192	0.55	7409	0.14	74109	0.25	74192	0.60	74C CMOS	BF224
U257B	1.28	1.60	HAI2017	4003	4572	7453	0.14	74132	0.50	74193	0.55	7410	0.13	74112	0.25	74193	0.68	74C CMOS	BF224
U267B	1.28	1.60	HAI2402	4008	4582	7460	0.14	74136	0.65	74194	0.55	7411	0.15	74113	0.25	74194	0.42	74C CMOS	BF440
LM301H	0.67	1.20	HAI2411	4008	4584	7460	0.28	74142	1.85	74196	0.55	7413	0.28	74122	0.40	74196	0.65	74C CMOS	BF440
LM301H	0.67	1.20	HAI2411	4009	4584	7460	0.28	74142	1.85	74196	0.55	7413	0.28	74122	0.40	74196	0.65	74C CMOS	BF440
LM308TC	0.65	1.20	LF13741	4011	4592	7472	0.27	74143	2.50	74199	0.85	7415	0.49	74123	0.55	74199	0.65	74C CMOS	BF362
LM324	0.64	1.20	SN76660N	4011	4602	7472	0.28	74144	2.50	74199	0.85	7415	0.49	74123	0.55	74199	0.65	74C CMOS	BF395
LM339N	0.66	1.20	FREQ. DISPLAY	4012	4703	7474	0.28	74145	1.50	74221	1.00	7421	0.15	74126	0.29	74202	0.60	74C CMOS	BF479
LM348N	1.86	1.80	AND SYNTH.	4012	4704	7474	0.35	74147	1.50	74221	1.00	7421	0.15	74126	0.29	74202	0.60	74C CMOS	BF679S
LF351N	0.49	1.80	DEVICES	4013	4705	7476	0.26	74148	1.09	74246	1.50	7422	0.15	74132	0.29	74202	0.60	74C CMOS	BF679S
LM374N	3.75	3.05	SAA1056	4015	4706	7480	0.26	74149	0.75	74248	1.51	7426	0.18	74133	0.30	74241	0.99	74C CMOS	BF91
LM380N-14	1.00	3.05	SAA1058	4016	4720	7481	0.26	74150	0.75	74248	1.51	7426	0.18	74133	0.30	74241	0.99	74C CMOS	BF91
LM380N-8	1.00	3.05	SAA1059	4017	4723	7481	0.26	74151	0.75	74248	1.51	7426	0.18	74133	0.30	74241	0.99	74C CMOS	BF91
LM381N	1.81	1.80	11C90DC	4018	4724	7482	0.60	74153	0.55	74249	1.85	7428	0.35	74139	0.40	74242	1.65	74C CMOS	BF91
NE544N	1.80	1.80	LN1232	4020	4725	7485	0.60	74154	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
NE555N	1.80	1.80	MSL2318	4021	4725	7485	0.60	74155	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
NE560N	0.50	1.80	MSM5523	4022	4725	7485	0.60	74156	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
NE562N	3.50	1.80	MSM5524	4023	4725	7485	0.60	74157	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
NE564N	4.29	1.80	MSM5526	4024	4725	7485	0.60	74158	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
NE565N	1.00	1.80	MSL2312	4025	4725	7485	0.60	74159	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
NE566N	1.60	1.80	SP8629	4026	4725	7485	0.60	74160	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
NE570N	3.88	1.80	HD10551	4027	4725	7485	0.60	74161	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
SL624	0.81	1.80	HD10552	4028	4725	7485	0.60	74162	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
UA705H	1.64	1.80	HD10553	4029	4725	7485	0.60	74163	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
UA709PC	0.46	1.80	HD10554	4030	4725	7485	0.60	74164	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
UA710PC	0.65	1.80	HD10555	4031	4725	7485	0.60	74165	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
UA710PC	0.59	1.80	HD10556	4032	4725	7485	0.60	74166	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
UA7141C	0.66	1.80	MC145151	4033	4725	7485	0.60	74167	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
UA747CN	0.70	1.80	MC145152	4034	4725	7485	0.60	74168	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
UA747CN	0.27	1.80	MC145153	4035	4725	7485	0.60	74169	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
UA753	2.44	1.80	MISC	4036	4725	7485	0.60	74170	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
UA758	2.25	1.80	ICM7106CP	4037	4725	7485	0.60	74171	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
TBA820M	1.80	1.80	ICM7107CP	4038	4725	7485	0.60	74172	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
TCA940E	1.80	1.80	ICM7168P	4039	4725	7485	0.60	74173	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
TDA1029	2.11	1.80	ICM7555	4040	4725	7485	0.60	74174	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
TDA1054	1.45	1.80	32.768KHz	4041	4725	7485	0.60	74175	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
TDA1062	1.95	1.80	100KHz	4042	4725	7485	0.60	74176	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
TDA1074A	5.04	1.80	455KHz	4043	4725	7485	0.60	74177	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
TDA1083	1.95	1.80	1.000MHz	4044	4725	7485	0.60	74178	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
TDA1090	3.05	1.80	3.2768	4045	4725	7485	0.60	74179	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
HAI1137	1.20	1.80	4.000	4046	4725	7485	0.60	74180	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
HAI1196	2.00	1.80	2.00	4047	4725	7485	0.60	74181	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
HAI1220	1.00	1.80	4.1934	4048	4725	7485	0.60	74182	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
TDA1197	1.40	1.80	2.00	4049	4725	7485	0.60	74183	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
LM1307	0.99	1.80	4.032	4050	4725	7485	0.60	74184	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
LM1303	1.55	1.80	2.03	4051	4725	7485	0.60	74185	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
MC1310P	1.90	1.80	4.800	4052	4725	7485	0.60	74186	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
MC1350	1.20	1.80	2.00	4053	4725	7485	0.60	74187	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
HAI370	1.90	1.80	4.433619	4054	4725	7485	0.60	74188	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
TDA1490	2.75	1.80	2.00	4055	4725	7485	0.60	74189	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
MC1456P	1.26	1.80	6.5536	4056	4725	7485	0.60	74190	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
			2.00	4057	4725	7485	0.60	74191	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
			2.00	4058	4725	7485	0.60	74192	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
			2.00	4059	4725	7485	0.60	74193	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65	74C CMOS	BF91
			2.00	4060	4725	7485	0.60	74194	0.55	74251	1.05	7430	0.30	74139	0.40	74242	1.65		

MAPLIN make it easy...



in SOUTHEND
284 London Road
Westcliff-on-Sea
Essex
Tel: (0702) 554000
(Closed Mondays)



in HAMMERSMITH
159-161 King Street
Hammersmith
London W6
Tel: 01-748 0926
(Closed Mondays)

For personal service visit one of our stores.
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our CATALOGUE

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!
Don't miss out on your copy.

On sale now in all branches
WH Smith price £1.

In case of difficulty check the coupon below.

by MAIL ORDER
A fast service
You can rely on

- * Same day service on in-stock lines
- * Very large percentage of our stock lines in stock
- * All prices include VAT
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components—no rejects—no re-marks
- * Competitive prices
- * Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **MAPLIN** your first choice for components every time!

make it easy... with MAPLIN

The Maplin Matinée
Amazing value for only £299.95 plus £99.50 for cabinet if required

Easy to build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in Electronics & Music Maker commencing March, 1981 issue. Back numbers available.



MAPLIN ELECTRONIC SUPPLIES LTD.

Post this coupon now.
Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name _____
Address _____

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911