


WARRACK

RADIO & ELECTRONICS CONSTRUCTOR

AUGUST/SEPTEMBER 1981

60p

LAST ISSUE

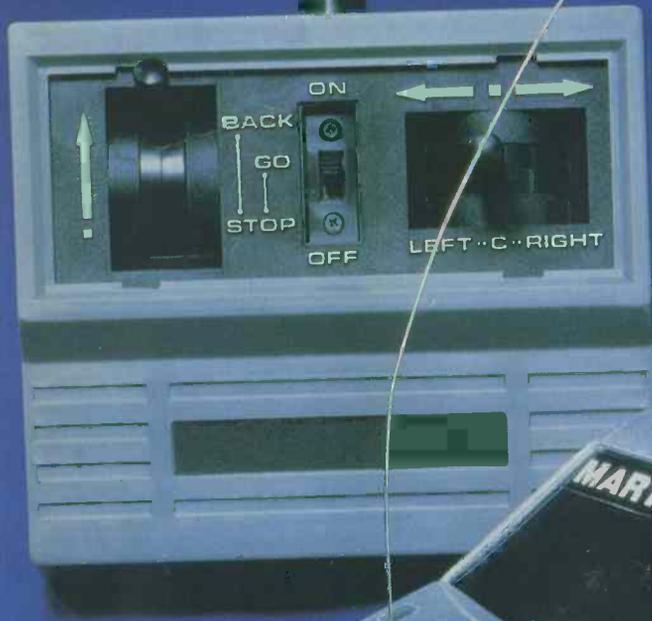

* FULLY PROPORTIONAL
5 CHANNEL R/C SYSTEM
— SIMPLE 2 IC CONSTRUCTION

* STYLISH HI-FI STEREO-AMP
30w + 30w
COMPLETE PARTS SUPPORT

AN EXTRA 16 PAGES OF
CONSTRUCTIONAL ARTICLES
AND FEATURES

The beginning of the
WORLD
is nigh.



RADIO & ELECTRONICS CONSTRUCTOR

AUGUST/SEPTEMBER 1981
Volume 34 No. 12

Published Monthly

First published in 1947

Incorporating The Radio
Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone
01-286 6141

Telegrams
Databux, London

©Data Publications Ltd., 1981. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £9.50, Eire and Overseas £10.50 (U.S.A. and Canada \$30.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production - Web Offset.

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The Radio & Electronics Constructor is printed by LSG Printers, Portland Street, Lincoln.

NEWS AND COMMENT *The Last Issue RIP +* 712

VMOS DEVICES AND CONSTANT CURRENT SUPPLIES
Design Ideas No. 2 by Jonathan Charles Burchell 714

BBC CLOCK TO BE MADE BY McMICHAEL 717

SIMPLE STEREO AMPLIFIER by T. J. Johnson 718

SHORT WAVE NEWS - For DX Listeners
by Frank A. Baldwin 724

THE INTERNATIONAL AMATEUR RADIO UNION
REGION 1 CONFERENCE
Report by Arthur C. Gee 726

IN NEXT MONTH'S ISSUE 727

MW AND LW SUPERHET RADIO by John Baker 728

THE ZN1034 PRECISION IC TIMER
by R. A. Penfold 734

INFRA-RED REMOTE CONTROL SYSTEM
Part 2 (Conclusion) by I. M. Attrill 739

THE AUDIO MASTER -
A 30W+ 'Bookshelf' HiFi Stereo Amplifier 743

KNOW YOUR RF CONNECTIONS
Part 2 - Electronics Data No. 72 751

'RADIO & ELECTRONICS WORLD' - Preview 752

A 5 CHANNEL DIGITAL-PROPORTIONAL
RC SYSTEM 756

PROGRAMMES, PROGRAMMING LAUNGUAGES AND
PROGRAMMING - Compulink Series No. 2 763

TRADE NEWS 765

A SCANNING MONITOR RECEIVER SYSTEM
Part 2 by L. Power 766

A NEW RECRUIT - In Your Workshop 771

ANNUAL INDEX
September 1980 - August/September 1981 783

Where is "Suggested Circuit"?
G.A. French obviously opted out!

OUR NEXT ISSUE
WILL BE PUBLISHED
3rd SEPTEMBER

C.B. P.A. MICROPHONES,
Hand held with thumb switch & Curly Lead, Type 1 600Ω dynamic at £4.25.

Type 2 600Ω, noise cancelling type at £7.25
Type 3 Power type, with volume control 1KΩ Imp, £7.95

SEMICONDUCTORS

LM340 80p. BY103 10p.
2N5062 100V 800mA SCR 18p
MC4741 (Quad 741) 14 pin 50p. CA3130 95p.
MC4741CP 50p. 741 22p.
741S 35p. 723 35p. NE555 24p.
2N3773 £1.70. NE556 50p.
ZN414 75p. BD238 28p.
BD438 28p. CB4069 15p.
4" Red Led Displays, c.c. or c.a. 95p.
TIL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p.
2N3055 39p.

PROJECT BOXES

Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p.
95 x 71 x 35mm 75p.
115 x 95 x 37mm 85p.

MOTOROLA PIEZO CERAMIC TWEETERS
No crossover required



2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65

TOOL SALE

Small side cutters 5" insulated handles £1. Radiopliers, snipe nosed insulated handles £1. Heavy duty pliers insulated handles £1.10. Draper side cutters spring loaded £1.

HANDY BENCH VICE
1" Jaw opening, £2.95.



Hand drill, double pinion with machine cut gears, 3/8", only £2.75p plus 87p p&p.

MORSE KEYS

Beginners practice key £1.05. All metal full adjustable type. £2.60

F.M. MICROPHONE, Electret condenser type, tuneable 85-95Mhz. Arrival distance 50 mtrs. (Approx outdoors) Size 163 x 35 mm £10.25. (Not licensable in U.K.).

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

TRANSFORMERS

All 240VAC Primary (postage per transformer is shown after price).
MINIATURE RANGE: 6-0-6V 100mA, Volts 100mA, 12-0-12V 50mA both 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 24 volt 2 Amp £2.45 (54p).

T.V. AERIAL AMPLIFIERS

Wide Band, 240 VAC operated, with two outlets, £7.75

MICROPHONES

Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. EM103 Microphones, Omni, Electret, 600Ω, 50-16000Hz, 170 long, £6.50p. EM506 dual impedance condenser microphone 600ohms or 50K, heavy chromed copper body, £12.95. CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. GRUNDIG electric inserts with FET pre amp, 3-6VDC operation £1.00.


LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50

C.B. 40 CHANNEL RECEIVER

For car use, operates on 12v DC., £7.95

SPECIAL OFFER TAPE HEAD DEMAGNETIZER

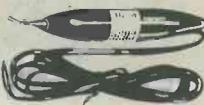

240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p

MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50




20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £975.

40kHz Transducers. Rec/Sender £3.50 pair.

TELEPHONE PICK UP COIL

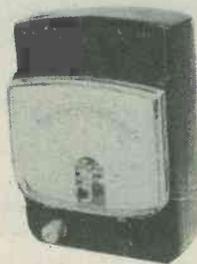Sucker type with lead and 3.5mm plug 62p.



500v electronic megger, push button operation. Ranges:- LO ohm Range 0 - 100Ω (MW scale 5Ω) 10 - 100MΩ Mid scale 5MΩ) £46.75p

Stabilized power supplies, 240V A.C. input output 13.8 volts at 3/5 amps D.C. £14.75p

TERMS:

Cash with order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.

MULTI-TESTER



KRT5001 50k/v range doubler multimeter, 0-1kv (125mv LO range) 0-1kv AC. 0-10amp DC. 0-20MΩ res. (LO ohm 0-2k range) 170 x 124 x 50mm £15.50.

YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts, 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

CRIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

POWER SUPPLIES

SWITCHED TYPE PLUGS into: 13 amp socket, 3-6-9 volts DC out at 300mA, £2.95. 12 volts DC out at 250mA, £1.00 each. Panel Vu meter, rectangular 55 x 50mm/m 150μA FSD. £1.00p.

AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.

BUZZERS

MINIATURE SOLID STATE BUZZERS, low consumption, available in either 6 or 12 volts D.C. 75p each. **LOUD 12VDC BUZZER,** Heavy duty metal body, 50mm diam. x 30mm high 63p. **Carters 12 volt Minimate Alarm sirens** £7.65p. 12VDC siren, all metal rotary type, high pitched wail, £6.25.

New catalogue at printers, apologies for delay, all S.A.E.'s received are being held until catalogue is ready.

TOOLS

Set of ten screwdrivers, in wallet, good mixture £1.00 per set.

Automatic wire stripper, cuts and strips 1.1, 1.4, 1.6, 1.8, 2.4 and 3.5 m/m, £5.75p.

Antex Model C 15 watt soldering irons, 240VAC £4.45

Antex Model CX 17 watt soldering irons, 240VAC £4.45

Antex Model X25 25 watt soldering irons, 240VAC £4.45

ANTEX ST3 iron stands, suits all above models £1.65

Antex heat shunts 12p each.

Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 59p each.

Miyarna IC test clips 16 pin £1.95

SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p. DPDT (8 x 7 x 7mm) 55p. DPDT centre off 12 x 11 x 9mm 77p. **PUSH SWITCHES,** 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

TEI Mobile SWR metre, with field strength, PL259 connection, £8.35.

RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz. (harmonics) internal modulator at 100Hz. R.F., output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95. BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly - 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.

ALL ORDERS DESPATCHED BY RETURN POST

FREPAR

plug-in cases
12 & 16 TERMINALS

Mounting base Connection screws M 3,5 with self-lifting clamping plates, maximum cable cross section $2 \times 1,5 \text{ mm}^2$ (also suitable for use with cable shoes).

Gold plated contact springs guarantee good contact even at low currents or voltages (contact resistance approximately $10 \text{ m}\Omega$). Separators between the terminals guarantee leakage path and voltage spacings in accordance with VDE VDE 0110/11,72, § 5, insulation group C at 250V AC/300V DC. Cable entries: 5 (in ZA 12) or 6 (in ZA 16) PVC cable entry sleeves




printed circuit board. The cases are normally supplied with covers made of polystyrol

ACCESSORIES:

Printed circuit boards: Made of laminated paper HP 2063, 2,0 mm thick, single clad with a $35 \mu\text{m}$ copper coating with gold plate contact strips.
Front labels: Made of light grey PVC without printing
Size for ZA 12 = $83,5 \times 44,5 \text{ mm}$
Size for ZA 16 = $119,5 \times 67,5 \text{ mm}$
Earthing terminal block: 4-pole
Coding Bars: For polarising of printed circuit boards.

2 prestamped cable entries in the base.

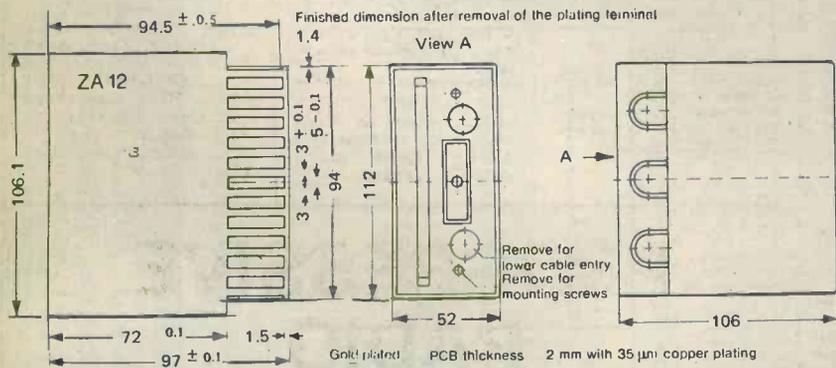Cover: Closed, without holes, with a recess 0,6 mm deep for an adhesive label, two mounting screws for attaching the plug-in upper part to the base. Intermediate plate for covering the equipment space and for retaining the



Dimensions in millimetres

ALSO

Hand-held, low-cost Digital Thermometer

£60 INCLUDING ADAPTOR and P.P.P. + V.A.T.

FREPAR

ELECTRONICS LTD

119 Newland Street Witham Essex CM8 1BE England Tel Witham (0376) 516617

TRANSISTORS

— Germanium other-
— wise silicon
* PNP, otherwise
NPN

AC122 30v.2w	12p
AC126 30v.2w	16p
AC128 36v.1wt	5p
AC153 32v.1wt	11p
AC176 32v.7w	11p
AC179 20v.1.1w	40p
AC188 25v.1w	10p
AC20 40v.3w	20p
AC21 40v.3w	20p
AC28 40v.2w	22p
AD161 20v.6wt	40p
AD162 20v.6wt	40p
AD164 25v.6wt	40p
AD165 25v.6wt	40p
AF119 30v.2w	35p
AF124 32v.1w	27p
AF126 32v.1w	27p
AF127 32v.1w	27p
AF139 22v.1w	23p
AF178 25v.1w	35p
AF180 25v.1w	35p
AF181 30v.16w	35p
AF239 20v.1w	35p
AL210 50v.5w	37p
ASV60	35p
ASV63 26v.1w	4p
ASV73 30v.15w	35p
AS221 20v.12w	4p
AU107 200v.30w	1.55
AU110 160v.30w	£1.43
BC107A/B	7p
BC108A/B/C	7p
BC109B/30v.3w	7p
BC109C 30v.3w	7p
BC125 50v.3w	4p
BC125B 60v.3w	4p
BC129A/B 50v.2w	7p
BC130A/C 25v.2w	7p
BC131C 25v.2w	7p
BC139 40v.7w	11p
BC140 40v.7w	15p
BC141 60v.7w	11p
BC143 60v.8w	11p
BC147A/B/C	51p
BC148A/B/C	51p
BC149A/B/C/S	51p
BC154 40v.2w	7p
BC157A 50v.4w	51p
BC158A/B	51p
BC159B/C	51p
BC160 40v.3.2w	12p
BC168B 20v.3w	7p
BC171B 45v.3w	4p
BC172 25v.3w	6p
BC172C 25v.3w	7p
BC173 25v.3w	7p
BC177A 45v.4w	10p
BC178A/B/C	10p
BC179B 20v.3w	10p
BC182/AL 50v.3w	5p
BC182L 50v.3w	3p
BC183A/AL/L/LC	3p
BC184 45v.3w	5p
BC186 40v.3w	21p
BC187 30v.3w	8p
BC190B 64v.3w	71p
BC196A 30v.50mw	4p
BC197A 50v.50mw	4p
BC198B 30v.50mw	£3.65
BC199B 30v.50mw	£3.65
BC204 50v.3w	11p
BC212B 50v.3w	5p
BC213L 45v.3w	5p
BC213LA 45v.3w	4p
BC213LB 45v.3w	4p
BC214B 45v.3w	5p
BC214L 45v.3w	3p
BC237A 45v.3w	71p
BC237B 60v.3w	71p
BC238 20v.3w	5p
BC238B/C	71p
BC239C 20v.3w	71p
BC251 45v.3w	3p
BC257B 45v.3w	71p
BC258B/C	71p
BC259C 20v.3w	71p
BC301 90v.9w	15p
BC302 80v.9w	15p
BC304 80v.9w	15p
BC307 45v.3w	7p
BC308B/C 25v.3w	71p
BC309B 20v.3w	71p
BC327 45v.7w	5p
BC328 25v.7w	6p
BC337 45v.7w	6p
BC338 25v.7w	5p
BC382L 50v.3w	71p
BC384B 45v.3w	71p
BC546 80v.6w	5p
BC547A/B 45v.5p	5p
BC548A/B/C	5p
BC549C 30v.5w	5p
BC556 80v.5w	5p
BC557B	5p
BC558A 30v.5w	5p
BC559 30v.5w	5p
BC612L 75v.3w	4p

BCX32 80v.8w	80p
BCX33 60v.75w	10p
BCX 34 40v.8w	10p
BCX36 60v.15w	10p
BCY11 60v.5w	28p
BCY31 64v.6w	59p
BCY56 5v.3w	10p
BCY59 8v.45v.1w	10p
BCY70 50v.35v.9p	10p
BCY71 45v.35v.9p	10p
BCY72 25v.3w	15p
BCY79B 45v.3w	15p
BCZ11 25v.25w	32p
BD113 60v.5w	27p
BD115 250v.6w	35p
BD116 80v.10w	35p
BD131 45v.15w	15p
BD132 45v.15w	15p
BD133 90v.15w	28p
BD135 45v.13w	22p
BD136 45v.13w	22p
BD137 60v.8w	28p
BD138 60v.8w	28p
BD137/8 mtch pr	60p
BD139 80v.12w	30p
BD140 80v.8w	26p
BD142 50v.117w	35p
BD156 70v.25w	50p
BD182 70v.117w	44p
BD201 45v.60w	86p
BD202 45v.60w	64p
BD203 60v.60w	86p
BD204 60v.60w	86p
BD232 500v.15w	34p
BD233 45v.25w	20p
BD235 60v.25w	35p
BD238 80v.25w	25p
BD239C 115v.30w	29p
BD240 55v.30w	36p
BD240B 90v.30w	36p
BD240C 115v.30w	39p
BD241 45v.40w	22p
BD242 90v.40w	30p
BD243 55v.65w	32p
BD244 90v.65w	43p
BD244C 115v.65w	45p
BD246 55v.80w	32p
BD253 350v.50w	44p
BD277 45v.70w	37p
BD375 50v.25w	35p
BD437 45v.36w	28p
BD438 45v.36w	28p
BD597 60v.55w	36p
BD677 60v.40w	50p
BD678 Pwr. Darl.	50p
BDX33A 88v.20w	44p
BDX42 60v.3w	36p
BDX77 80v.60w	71p
BDY20 60v.117w	86p
BF115 50v.2w	18p
BF137 160v.7w	11p
BF167 30v.15w	18p
BF173 25v.2w	18p
BF178 188v.6w	23p
BF179 250v.6w	23p
BF180 30v.2w	12p
BF181 30v.2w	8p
BF182 25v.12w	18p
BF183 25v.12w	18p
BF184 20v.15w	18p
BF185 20v.15w	18p
BF194A/B	51p
BF195C/D	51p
BF196 40v.25w	51p
BF197 40v.25w	51p
BF198 30v.3w	13p
BF200 30v.2w	13p
BF224 45v.36w	4p
BF244C FET 30v	7p
BF245 FET	6p
BF254 30v.3w	12p
BF256FET	8p
BF256BL/LC/FET	6p
BF257 160v.5w	20p
BF259 see 2N5058	50p
BF262 30v.12w	29p
BF263 30v.12w	29p
BF274 25v.12w	8p
BF324 30v.3w	31p
BF336 185v.3w	16p
BF335 300v.3w	16p
BF394B	3p
BF451 40v.3w	6p
BF494 20v.3w	10p
BF494B 20v.3w	10p
BF495 20v.3w	5p
BF595C 30v.25w	91p
BF615	27p
BF617	27p
BF635	16p
BF637	16p
BFR34A 12v.2w	£1
BFR38 40v.2w	68p
BFR86 120v.8w	19p
BFS21 FET pair	£3
BFS28 Dual M/Fet	50p
BFT30 70v.36w	15p
BFT31 60v.36w	15p
BFT39 90v.8w	15p
BFT41 60v.8w	15p
BFT60 80v.8w	6p
BFT61 60v.8w	15p
BFT70 70v.36w	15p
BFT71 40v.36w	15p
BFW10 FET 30v	46p
BFW11 FET 30v	46p
BFW30 20v.25w	15p

*BFW31 50v.5w	15p
*BFW57 80v.5w	18p
*BFW58 80v.5w	18p
*BFX12 20v.3w	23p
*BFX29 60v.6w	11p
*BFX30 60v.6w	16p
*BFX37 60v.4w	16p
*BFX84 100v.8w	20p
*BFX85 100v.8w	14p
*BFX88 40v.6w	20p
*BFX89 30v.2w	20p
*BFY39 45v.3w	20p
*BFY50 35v.1wt	15p
*BFY51 60v.1w	15p
*BFY52 40v.1w	15p
*BFY75 30v.35w	15p
*BFY90 30v.2w	59p
BR101 Prog.	20p
BRV39 Univ.	29p
BRY56	29p
BSV60 45v.8w	30p
BSV64 100v.1w	36p
BSV79 40v.4w	50p
BSV80 40v.FET	50p
BSV81 Dep. Mos Fet	75p
BSX19 40v.4w	15p
BSX20 40v.4w	7p
BSX21 120v.3w	10p
BSX78 40v.3w	8p
BSY24 40v.6w	21p
BSY40 25v.3w	30p
BSY95A 20v.3w	10p
BU105 1k5v.10w	64p
BU105/04	78p
BU204 1k3v.10w	75p
C1544	4p
C1601	4p
D40C4 40v.8wt	22p
D40D1 45v.7wt	22p
D40D2 45v.7wt	15p
D40D4 60v.7wt	22p
D41D2 45v.7wt	22p
D43C7 70v.13wt	30p
D43C8 50v.13wt	30p
D45C2 40v.30w	26p
D22HF50 50MHz	50p
DS70 Darl. 10wt	22p
GET102 30v.2w	46p
GET111 60v.2w	45p
GET120 30v.44w	30p
M103 MOSFET	30p
MA393 32v.5w	25p
MD7000 30v.7w dual	£2.25
ME2 15v.1w	13p
ME041 60v.2w	14p
ME0461 60v.3w	71p
ME6101 70v.36w	71p
ME6102 60v.4w	71p
ME8003 90v.4w	20p
MJ481 60v.3w	25p
MJE370 30v.25w	32p
MJE371 40v.40w	40p
MJE371 60v.40w	80p
MJE2901T (Higan)	25p
295E 60v.90w	50p
Mn 15 Russian	25p
Mn41 Russian	25p
MP8113 60v.3w	25p
MPF131 Dual MOSFET	21p
MPS 8513 60v.3w	31p
MPSA131 30v.31w	21p
Darl.	21p
MPU131 Prog. Uni J.	15p
MRF502 Improved	90p
BFY90	90p
MST 1027 80v.100w	40p
MST 1072 300v.100w	50p
MST2007	4p
MST2013	4p
MST2015	TO18
MST2018	TO18
n 16A Russian	25p
n 12A Russian	25p
NKT49	23p
NKTA52 10v.1w	20p
NKTB54 10v.1w	30p
NKTI52 6v.1w	38p
NKTI53 32v.1.6w	24p
NKTI54 6v.1w	24p
NKT251 30v.2w	18p
NKTM2E 15v.1w	13p
NSD102 45v.10wt	23p
NSD104 80v.10w	26p
NSD129 250v.10wt	23p
NSD131 250v.10wt	30p
NSD132 250v.10wt	30p
NSD134 300v.10wt	30p
NSD151 30v.10wt	22p
Darlington	22p

NSD457 160v.10wt	23p
NSD U45 40v.10wt	30p
Darlington	30p
*NSD U51 30v.10wt	22p
*NSD U55 60v.10w	25p
OC23 55v.16w	53p
OC28 80v.30w	78p
OC41 16v.1w	4p
OC42 16v.1w	21p
OC43 15v.1w	55p
OC44 15v.1w	4p
OC45 15v.1w	13p
OC71 30v.2w	4p
OC72 32v.2w	4p
OC73 22v.13w	15p
OC77 60v.13w	46p
OC81 32v.6w	5p
OC84 32v.6w	30p
OC200 30v.25w	41p
OC201 25v.25w	66p
OC201 15v.25w	66p
OC603 22v.1w	50p
OC701 80v.35w	50p
ON222	23p
P77 Plastic 10wt	15p
P346A 30v.6w	24p
P7029	30p
PXB103 30v.15w	25p
R1039 (200B)	54p
R2008B 66v.85w	54p
R2010B	£1.18
R2306 100v.40w	26p
R2540	£1.70
RC467 Pwr. Darl.	22p
RC701A/B/D 10wt	115wt
RC703 80v.30w	30p
RCPT03 80v.40w	30p
S3017	25p
SB240	26p
SFT357 20v.12w	26p
SL102	40p
TE886	£1
TIP29 40v.2w	22p
TIP30 40v.3w	22p
TIP30C 100v.30w	26p
TIP31C 100v.40w	26p
TIP32A 60v.40w	22p
TIP32C 100v.40w	26p
TIP41 40v.65w	15p
TIP42C 100v.65w	33p
TIP48 300v.40w	33p
TIP 110 60v.50w	40p
TIP112 100v.50w	45p
TIP115 60v.50wt	30p
Darlington	30p
TIP2955 100v.90w	45p
TIP3055 100v.90w	34p
TIS44 25v.25w	91p
TIS60GY 40v.3w	3p
TIS61 40v.3w	7p
TIS73L FET	4p
TIS90 40v.65w	4p
TIS91 40v.65w	6p
TIS92GY 40v.65w	14p
TIS98 30v.25w	3p
TK24 30v.2w	20p
U14710	20p
V435 30v.6w	20p
XA101 20v.12w	5p
ZT403P 30v.3w	30p
ZT1485 110v.25w	£1.10
ZTX341 100v.3w	9p
ZG103 15v.3w	33p
ZG302 20v.2w	12p
ZG309 20v.3w	30p
ZG339A 30v.15w	20p
ZG371 20v.2w	18p
ZN388 25v.15w	71p
ZN486A 40v.90w	71p
ZN525 45v.2w	12p
ZN527 45v.2w	12p
ZN597 45v.25w	16p
ZN598 35v.25w	16p
ZN601 35v.75w	£1.50
ZN644 30v.15w	22p
ZN698 120v.8w	12p
ZN699 120v.6w	12p
ZN706A 25v.3w	10p
ZN708 40v.4w	3p
ZN718 60v.4w	10p
ZN720A 120v.5w	12p
ZN720 120v.5w	12p
ZN736 80v.5w	71p
ZN914 40v.4w	15p
ZN918 15v.2w	12p
ZN929 45v.3w	16p
ZN954 15v.3w	7p
ZN967 40v.1w	45p
ZN1091 25v.2w	16p
ZN1132 50v.6w	14p
ZN1302 25v.2w	16p
ZN1303 30v.2w	

PRICES SO LOW, THE POLICE INVESTIGATED ME TWICE
 ALL ENQUIRIES, ETC. MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

VAT & POST PAID
 (UK 2nd Class or Parcel) Just include stamped addressed envelope (14p) or label
 MINIMUM ORDER FIVE POUNDS. OTHERWISE ADD 50% FOR SMALL ORDER HANDLING COSTS

UK - Postal Orders for prompt service. Cheques require clearance. Export from a Monday banking to ensure clearance. Export banker's draft (sterling) prompt service. Foreign currency not accepted. VAT content becomes documentation charge. Aq additional postage for overseas mail.

OPTO ELECTRONICS
 Photo Diodes: 30F2, 31F2, 32F2, 33F2, BPX40, BPY10, BPY68, BPY69, BPY77, CQY17, CQY77, All types 38p
 Wire end neons 5p.
 Photo transistor: BPX43, BP103, 2N5777, Darlington 36p; LED's (Mullard Siemens) Red 5mm 8p, 3mm 13p; Green 5mm 13p, 3mm 13p; Yellow 5mm 13p, 3mm 13p, micro LD481 8p
 AMBER 5mm 13p, 5mm Bar 13p.
 PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp 36p.
 CA3062 Photo Detector and power amp. £1.05p

7 SEGMENT L.E.D. DISPLAYS
 .3" Red com. anode 81p
 .6" Green C.A. £1.77
 5082-7650 Red com. anode.
 5082-7653 Red com. cath.
 5082-7600 Yellow com. anode.
 H.P. Highbrilliance .43" 72p

HEWLETT PACKARD MULTIPLEXED .11" 7 SEGMENT LED DISPLAYS
 3 Digit HP5082 7413 45p
 4 Digit HP 5082 7414 45p
 5 Digit HP 5082 7415 45p
 Infra red transmit diodes CQY11B or LD271 High power 1.6-2v or 3-3.5v Pulse 32p
 LD242 36p
 H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p
 CNY17/1 opto coupler 70p
 Cold cathode tubes I.T.T. G517A or 5870L 60p

SPECIAL OFFER
 IN4004 or IN4006 Sealed manufacturers carton of 300. £6.85

Transmit - Receive Transducers 40kHz murata £3.55p pair.

MONOLITHIC CERAMICS
 Professional quality to military standards, very stable, high volumetric efficiency giving high capacitance in sub-miniature size.

15PFD	6N8
23PFD	01
33PFD	015
47PFD	022 7 1/2p
68PFD	033
100PFD	047
150PFD	6p
330PFD	068 15p
680PFD	1
IN	
IN5	
2N2	15
2N7	22
3N3	33 24p
4N7	68
	1MFD

MERCURY TILT SWITCH
 Ex unused equipment 22.5mm x 9.5mm diam. epoxy resin encapsulated contacts 240vac/28vdc 0.5A 40p with free adjustable mounting bracket.
 Like Gold Dust! 470mfd, 6.3 volt Tantelium Bead yet only 64p.

DIODES

*AA118 90v 50ma	4p
*AA119 30v 35ma	7p
*AA133 100v 50ma	9p
*AA144 100v 5ma	4p
*AAZ15 100v 250ma 15p	
*AAZ17 50v 40ma	6p
B1	11p
BA101B varicap	10p
BA116 20v 100ma	30p
BA127 60v 100ma	3p
BA128 50v 100ma	2 1/2p
BA145 350v 500ma	2 1/2p
BA148 350v 500ma	12p
BA182 Varicap	6p
BAX 13 50v 150ma	3p
BAX14 40v 350ma	2 1/2p
BAX20 25v 115ma	3p
BAX21 50v 120ma	3p
BAX22 100v 120ma	3p
BAX54	8p
BY36P 30v 3ma	2 1/2p
BAY44 50v 250ma	4p
BAY68 25v 115ma	3p
BAY72 100v 400ma	4p
BB103 Varicap	24p
BB104 Varicap	16p
BB109 Varicap	24p
BB110B Varicap	24p
BB113 3x Varicap	43p
BB139 varicap	£1
BR100 Diac.	15p
BY206 350v 600ma	7 1/2p
BY207 600v 600ma	23p
BY402 100v 1A	2 1/2p
BY403 200v 1A	2 1/2p
Centercell	3p
CG651	9p
CR HG/3	10p
CSD117YLZ	40p
CV7095	2 1/2p
CV7098	2 1/2p
D3202Y Diac.	11p
DC2845 Microwave	20p
DOG53	11p

*Germanium: rest silicon
 FSY28A 40p
 HG1005 100v 45ma 3p
 HG1012 50v 50ma 10p
 MPN3401 VHF switch 30p
 OA5 100v 115ma 25p
 OA7 25v 50ma 25p
 OA10 25v 110ma 25p
 OA40 40v 50ma 4p
 OA47 30v 150ma 7p
 OA51 50v 50ma 4p
 BA128 50v 100ma 2 1/2p
 OA70 22v 50ma 10p
 OA75 40v 50ma 11p
 OA79 45v 35ma 11p
 OA81 115v 150ma 3 1/2p
 OA90 30v 45ma 4p
 OA91 115v 150ma 6p
 OA95 115v 150ma 6p
 OA200 50v 250ma 2 1/2p
 IN63 100v 40ma 4p
 IN337 200v 200ma 4p
 IN447 40v 25ma 3p
 IN604 400v 300ma 4p
 IN662 80v 40ma 2 1/2p
 IN914 75v 225ma 1 1/2p
 IN916 100v 300ma 2 1/2p
 IN3062 75v 20ma 3p
 IN3063 (BAV10) 6p
 IN3064 75v 10ma 2 1/2p
 IN4009 25v 75ma 2 1/2p
 IN4148 100v 200ma 1 1/2p
 IN4149 100v 200ma 3p
 IN4150 50v 200ma 2 1/2p
 IN4151 50v 200ma 2 1/2p
 IN4152 40v 200ma 3p
 IN4446 100v 200ma 2 1/2p
 IN4449 100v 200ma 2 1/2p
 IN5154 25v 30ma 3p
 IN5456 Varicap 15p
 IS922 150v 200ma 4p
 IS940 30v 50ma 3p
 5082 2900 RF Schotky Barrier 50p

RECTIFIERS

Type	Volt	Amp	Price
BY126	650	1	5p
BY127	1250	1	5p
BY212	15kv	500ma	6p
BY235	600	1 1/2	7 1/2p
BY236	900	1 1/2	7 1/2p
BY264	300	3	9p
BY265	600	3	11 1/2p
BY266	900	3	15p
BY275	600	3	19 1/2p
BY277	1200	5	27p
BY1202	2KV	10mA	6p
BYW55	800	2 (Oxide bead)	15p
BYW56	1000	2 (Oxide bead)	18p
BYX20-200	200	25	72p
BYX22-200	300	1 1/2	25p
BYX38 300R	300	6	48p
BYX38 600	600	6	52p
BYX38 900	900	6	60p
BYX38 1200	1200	6	65p
BYX42 300	300	12	35p
BYX42 600	600	12	46p
BYX42 900	900	12	92p
BYX42 1200	1200	12	£1.07
BYX46 300R	300	15	£1.19
BYX46 400R	400	15	Avalanche £1.75
BYX46 500R	500	15	£2.00
BYX46 600	600	15	£2.30
BYX48 300R	300	6	47p
BYX48 600	600	6	60p
BYX48 900	900	6	70p
BYX48 1200R	1200	6	92p
BYX49 300R	300	6	35p
BYX49 600	600	6	42p
BYX49 900R	900	6	47p
BYX49 1200	1200	6	60p
BYX52 300	300	48	£2.05
BYX52 1200	1200	48	£2.90
BYX70	500	1	4p
BYX72 150R	150	10	42p
BYX72 300R	300	10	52p
BYX72 500R	500	10	65p
BYX94	1250	1	6p
DD3026	400	2 1/2	10p
E250C50	250	1	14p
KS11394	800	3	23p
LT102	30	2	15p
M1	68	1	5p
MR856	600	3	24p
MSR5	800	3	32p
OAE210	400	5	13p
RA53 10AF	1250	1 1/2	Avalanche 48p
RA5308AF	1250	1 1/2	(Avalanche) 50p
REC53A	1250	1 1/2	Pack of 4 66p
SK645	200	6	22p
SR100	100	1 1/2	9p
SR400	400	1 1/2	10p
SR1825	100	50	75p
IN3254	400	1	4p
IN4002	100	1	4p
IN4004	400	1	4p
IN4005	600	1	4p
IN4006	800	1	6p
IN4007	1250	1	6p
IN5059	200	1 1/2	10p
IN5401	100	3	12 1/2p
IN5402	200	3	11p
IN5406	600	3	15p
IN5408	1000	3	19p
IS027	800	1 1/2	11p
IS138	800	1	21p
25G100	100	60	£4.35
30S2	300	2	11p
16094P	900	2	15p
16492	700	1 1/2	9p

BRIDGE RECTIFIERS

Amp	60VOLT	B30C350	23p
1	1,600	BYX10	34p
0.6	110	EC433	20p
1	100V	B40C800	12p
1	140	USH01-200	25p
1	400V	MDA104	29p
1 1/2	50V	WO05	27p
1 1/2	75V	IBIBY234	11 1/2p
1 1/2	150V	IBIBY235	15p
1 1/2	200V	WO2 Ex Equip	15p
1 1/2	400V	WO4	28p
1 1/2	400V	UE4R1	12p
1 1/2	800V	WO8	27p
1 1/2	1000	W10	36p
2 1/2	100	I.R.	40p
2 1/2	350V	9F2	53p
2 1/2	500V	9E4	85p
3	50	KBS005	30p
3	100	KBS01	30p
3	200	KBS02	30p
3 1/2	100	B40C 3200	39p
5	400	Texas	85p
	Miniature	Meter	Type

THYRISTORS

Amp	Volt	THYRISTORS	Price
0.8	50	2N5061	15p
0.8	200	2N5064	19p
1	240	BTX18-200	35p
1	240	BTX30-200	35p
1	400	BTX18-300	41p
1	700	BT 106	70p
2	400	S2710D with heatsink	40p
3	600	T3N06C00	53p
3	100	T3N1C00	36p
4	50	S107F Sensitive Gate	36p
4	50	S2060F Sensitive Gate	36p
4	400	S2060D	36p
4	400	S2061D Sensitive Gate	38p
4	500	40506 with heatsink	58p
4	500	17083	36p
4	600	C106M Sensitive Gate	37p
4	600	2N3228	36p
4	600	GAK	36p
5	400	S5800D/R	36p
5	500	17047A	40p
5	600	17058	44p
5	600	S5800M	44p
5	600	BT121	70p
6	100	SCR 6/100	33p
6.5	500	BT107	£1
6.5	500	BT109/SCR957	71p
7	400	S2620D	45p
7	600	S2620M	45p
8	100	S2800A	36p
8	300	83904c(I.T.R.)	50p
8	600	S122M	54p
12	1000	CR121103-RB	£8
16	400	2N6403	£1
20	600	BTX95-800 Pulse Modulated	£1
75	800	BTW92-600RM	£3.40
110	20	71C680	£6
150	1000	151RA100	£3
150	1200	151RA120	£11

ZENER DIODES
 4/500MW. BZY88, BZX97, etc. 51p
 2v. 2v7. 3v. 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v8. 7v. 8v2. 9v1. 10v. 11v. 12v. 13v. 13v5. 15v. 18v. 20v. 24v. 27v. 30v. 33v. 43v.
 BZY61 Laboratory Standard 400MW 7v5. Voltage Regulator Diode 12p
 1.3/1.5WT BZX61, BZY97, etc. 11p
 3v. 3v6. 3v9. 4v3. 4v7. 5v6. 6v2. 6v8. 8v2. 10v. 11v. 12v. 15v. 18v. 20v. 27v. 33v.
 2.5WT BZX70, etc. 13p
 3v6. 3v9. 5v6. 6v2. 7v. 7v5. 8v. 9v. 10v. 11v. 14v. 15v. (8p) 20v. 22v. 26v.
 5WT BZV40, etc. 15p
 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 8v7. 9v1. 10v. 11v. 12v. 15v. 20v. 33v. 120v.
 10WT Z5D, ZX, IS50, etc. 23p
 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 10v. 11v. 12v. 13v. 16v. 21v. 22v. 33v. 36v. 39v. 43v. 51v. 56v. 62v. 68v. 75v. 150v.
 15WT BZV15C 12R 12volt 37p
 20WT BZY93, etc. 44p
 8v2. 39v.

TEMPERATURE COMPENSATED REFERENCE
 IN935B, IN936B, IN937B 9volt
 IN941B, IN942B, IN943B 11.7volt

MY CATALOGUE (75p + 25p post/pack) OFFERS AT VERY LOW PRICES, THE FOLLOWING:
 CAPACITORS . . . ELECTROLYTIC; CAN, WIRE END, TANTALUM, MULTIPLE, COMPUTER GRADE, NON POLAR PAPER BLOCK, CAN POLY, MICA, CERAMIC LOW AND HIGH VOLTAGE, RESISTORS 1/8 WATT TO 100 WATT; 0.1% TO 10% CARBON, METAL AND WIRE WOUND + NETWORKS, FANS, BATTERIES, SOLENOIDS, TAPE SPOOLS, VARIABLE CAPACITORS AND RESISTORS, TRIMMERS, PRESETS, POTS . . . SINGLE, DUAL, SWITCHED, CARBON, CERMET AND WIREWOUND, SINGLE OR MULTITURN, ROTARY AND SLIDE, DIODES, RECTIFIERS, BRIDGES, CHARGERS, STYLII, SOCKETS, PLUGS, RELAYS, TRANSISTORS, IC'S, CLIPS, CRYSTALS, ZENERS, TRIACS, THYRISTORS, BOXES, PANELS, DISPLAYS, LED'S, COUPLERS, ISOLATORS, NEONS, OPTO'S, LEADS, CONNECTORS, VALVES, BOOKS, MAGAZINES, TERMINALS, CHOKES, TRANSFORMERS, TIMERS, SWITCHES, COUNTERS, LAMPS, INDICATORS, BELLS, SIRENS, HOLDERS, POWER SUPPLIES, HARDWARE, MODULES, FUSES, CARRIERS, CIRCUIT BREAKERS, KNOBS, THERMISTORS, VDR'S, INSULATORS, CASSETTES, METERS, SOLDER, HANDLES, LOCKS, INDUCTION, WIRE, UNITS, MOTORS, COILS, CORES, CARTRIDGES, SPEAKERS, EARPHONES, SUPPRESSORS, MIKES, HEATSINKS, TAPE, BOARDS AND OTHERS.

BRIAN J. REED

SEE PRECEDING PAGES FOR ORDERING INSTRUCTIONS
Continued American and European distributors
bankruptcies keep my stocks high and my prices low

326 HINIL 2, 2, 3, 3, Input Nand	20p
332 Hex inverter, HINIL	11p
343 4 bit comparator	5p
370 HINIL Quad D Flip Flop	11p
371AJ (MC684) Decade count, HINIL	5p
542 Servo Amp	18p
555 Timer	24p
5/6-14 audio amp, 2 watt	60p
577 Mod A.F. Equaliser/Pre-amp	69p
702/72702 wide band OP. AMP	25p
709/72709 OP Amp High Gain	18p
723 2v - 37v 150ma Regulator	36p
724 Zero Crossing A.C. Trigger	20p
733 diff. wide band video amp	40p
741 OP Amp	17p
747 Dual OP Amp	44p
930DC Dual 4 in ext Nand	5p
933DC Dual 4 in ext	5p
936DC Hex Inverter	5p
937DC Hex Inverter	5p
946DC Quad 2 in Nand	5p
949DC Quad 2 in Nand, Fast	5p
961DC Dual 4in Ext Nand	5p
963DC	5p
1315P2 Multivib. 1 shot processor	36p
1535 MOS decoder	50p
1702A eprom 256 x 8	£3.10
2102 Memory 1024 static 450ns	73p
2107B see µPDA11AC	-
2125 1024x1 Static 95ns RAM	£1.25
2140 4 x 8 P.D.T. for D/A	£1.83
2472-MOS decoder	50p
25 LS 374 Octal D edge Trig F/F	£1.30
2708 Eprom 1024 x 8	£2.60
2716 Eprom 2048 x 8	£5.00
3351-2DC 40 x 9 Bit FIFO 2MHz	£1.07
3624-4 prom 512x8 90ns	£1
4060 Dynamic RAM 300ns 4k BIT	£1.45
5203 see 1535	-
5224 see 2472	-
7400 } Quad 2 Input	11p
7400H } Positive Nand	26p
74LS00 } Gates	13p
74S00 }	18p
7401 } Quad 2 Input positive	71p
74H01 } Nand + O/C out	26p
7402 quad 2 in pos nor	12p
7403 Quad 2 in Nand O/C	12p
7404 Hex. Inverter	11p
547406 Hex. Inv./Buff/Drive	15p
74LS08 Quad 2 in pos. and	10p
7410 } Triple 3 Input	25p
74L10 } Positive Nand	25p
74H10 } Gates	18p
7411 Triple 3 In. Pos. and	8p
7414 Hex. Schmitt trlg. Inverter	29p
7420 } Dual 4 Input	11p
74S20 } Positive Nand Gates	19p
74S22 Dual 4 In. Pos. Nand o/c	18p
7425 dual 4in nor strobe	18p
7428 4 x 2 in + Nor Buff/CL. Drive	16p
5430 } 8 In. Pos. Nand	12p
7430 } 11p	11p
74L30 } 11p	11p
547437 Quad 2 In. Pos. Nand. Buf.	13p
7438 Quad 2in nand buf O/P	14p
7440 Dual 4 in Nand Buffer	13p
74H40 Dual 4 In. Pos. Nand. Buffer	26p
7441 BCD to DEC. Decoder/Drive	42p
7442 BCD to Decimal Decoder	26p
7445 BCD to Decimal Decoder	40p
7445 BCD Decimal Decoder	42p
Expandable Dual 2	26p
74H50 } Wide 2 Input and/or Inv.	26p
7454 } 4 Wide 2 in. and/or Inv.	11p
74L54 } 11p	11p
547472 } And Gated JK Master	17p
74L72 } Slave F.F. Preset + Clear	25p
5473 } Dual JK Master	12p
7473 } Slave Flip Flops	17p
74H73 } with Clear	26p
7474 } Dual D. Pos. Trigger	13p
74L74 } FF 2/Preset + Clear	25p
7475 Quadlatch	24p
547476 Dual JK Mas./SL Flip Flop	19p
5480 gated full adder	22p
7482 2 Bit Binary Full Adder	35p
7483 } 4 Bit Binary full	45p
74LS83 } Add + Fast carry	47p
547486 Quad exclusive or	181p
7489 Static ram 16 x 4, 60ns	£1.52p
5490/7490 Decade Counter	25p
7493 Binary Counter 4 Bit	25p
7495 4 Bit Shift Reg. P.I.P.O.	35p
5474L95 4 Bit Ser./Par. In. Out	25p
74LS98 4 bit storage register	£1.25
74107 Dual JK Flip Flop Clear	20p
74S112 Dual JK N.E.T. Flip Flop	78p
74118 Hex Reset latch	35p
74121 Monostable Multivibrator	12p
5474123 Dual Retrigger. Multivibrator	38p
54S124 dual volt cont. osc.	£1.10
74125 Tristate Quad Buffer	38p
74132 Quad 2 in nand schmitt	44p
74141 BCD To Decimal Dec/Drive	42p
74LS145 BCD to decimal Dec/Drive	93p
74151 1 of 8 Data Sel/Multivibrator	32p
74153 Dual 4 to 1 multiplexer	36p
74154 16 Way Distribution	35p
74155 Dual 2 to 4 line decoder	12p
74157 Quad 2 line to 1 Data	12p
74165 8 bit shift reg. Piso	58p
74167 Synch. Dec. Rate Multivibrator	23p
74173 Quad 3 state latch	44p

74174 Hex D/F/F and clear	55p
74S174 Hex D Flip Flop + clear	72p
74176/8280 Pre-set 35MHz Decode	30p
74180 8 bit parity gen.	12p
74181 Arith. Logic unit/funt. Gen.	56p
74H183 Dual full adder	36p
74192 } Synch. Dec. Up/Down	33p
74LS192 } Count + Dual Clock	60p
74193 reversible binary count	38p
74196 Pre-set 50MHZ.	36p
74S196/82S90 Decade Count/Latch	65p
74LS221 Dual Monostable M/VIB	52p
74221 dual Mono Multit. Schm. Trig.	72p
74285 binary 4 x 4 mult.	47p
74LS290 Decade counter	47p
74293 4 bit binary counter	80p
74298 Quad 2 in multi plus store	£1
74S387 Prom 256 x 4, 60ns	£2.50
IM5603AC see 74S387	-
74490 dual decade ripple count	£1.30
78M12 Pos. Reg. 12v 1a	54p
7905 - 5v Reg. 1 Amp	54p
8080A C.P.U. 8 bit	£3.60
8284 Binary up down synch.	36p
82S126 256 x 4 prom	90p
82S129 Tri state prom 256 x 4	£5
9093DC Dual M.S.J.K. Flip Flop	4p
9112DC Hex TTL to DTL Inverter	4p
93S10 Synchronous Decade Count	£1
93L11 6 to 16 line Decoder/Demulti.	£1.20
93L16 Binary count synch. P/S/in	36p
9370 BCD to 7 Seg. Dec/Drive ALOC	25p
16963	72p
93453 Schottky prom 1024 x 4	£1.83
930399 256 Bit Shift Register	47p
930399 480 Bit Shift Register	5p
930399 500 Bit Shift Register	5p
AY5-3507 3d Digit DVM	£1.65
AY5-8300 Ch/Time Display	38p
BRCM300 Volt Regulator	£1.40
BTT822 Tight Match mon PNP Pr.	£1.25
C500 Calculator	39p
CA101T Wide Band Op Amp	40p
CA139AG Quad Volt Comparator	54p
CA239G Quad volt comparator	54p
(T)CA270AE } Signal	£1
(T)CA270CW/AW } Processing	35p
(T)CA270CE } 36p	36p
CA920 TV Horiz. system	72p
CA3001 RF Amp	86p
CA3028A balanced OP. AMP.	75p
CA3044 TV Aft System	£1.20
CA3045 Transistor Array (5)	£1.43
CA3046 Transistor Array (5) NPN	40p
CA3060 Variable OP AMP	72p
CA3065 TV Sound I.F.	42p
CA3080 Prog. Transconduct. Amp.	£1.65
CA3083 NPN Transistor array	65p
CA3086 NPN 5 transistor array	29p
CA3089 FM IF. amp plus detector	1.10p
CA3090 Q/AQ FM decoder	£1.72p
CA3094 Prog. Sw. Pwr. OP Amp.	36p
CA3097 Thyristor - Transistor array	75p
CA3123 AM Radio RF/IF Amp	73p
CA3132EM Audio Amp. 10watt	£2.22
CA3140T Bimos op amp	40p
CA3146E Hi-volt 5 transistor array	90p
CA3160s BIMOS OP AMP	75p
CA3183 NPN transistor array	80p
CA3189 FM receive I.F. system	£1.40
CA3290 Comparator	59p
CA3401 (LM3900) Quad OP Amp	36p
CD4000 Dual 3 input Nor + Invert	12p
CD4002 Dual 4 Input Nor	12p
CD4004	56p
CD4006 18 Stage Static Shift Reg.	12p
CD4007 Dual Comp. Pair + Invert	12p
CD4008 4 Bit Binary Full Adder	30p
CD4010 Hex Buffers	54p
CD4012 Dual 4 Input Nand	13p
CD4013 Dual D Flip Flop	36p
CD4014 8 Bit Shift Register	36p
CD4016 Quad Bi-Lateral Switch	36p
CD4017 Decade Count/Divide	54p
CD4018 Preset Divide N Count	43p
CD4019 Quad 2 Input Multiplex	25p
CD4020 14 Stage Binary Counter	54p
CD4021 Shift register, 8 bit	78p
CD4022 Divide by 8 Count/Divide	36p
CD4023 Triple 3 Input Nand	19p
CD4024 7-Stage Binary Counter	14p
CD4025 Triple 3 Input Nor	14p
CD4027 Dual JK Flip Flop + R/S	30p
CD4028/MC14028 BCD/Decimal	42p
CD4029 Synch. Preset Bin/Decode	54p
CD4030 Quad Exclusive or	40p
CD4031 64 stage static. shift reg.	£1.20
CD4032 Trip. Ser. Add. Neg.	72p
CD4033 Dec. Count. 7 Seg. Output	72p
CD4034 Static shift register	£1.48p
CD4035 4 Bit Par. in out Shift	54p
CD4036 Word Buff. Store/decode	£2.00
CD4037 triple and/or BI Phase pairs	72p
CD4038 Triple serial/parallel	54p
CD4040 12 stage binary counter	80p
CD4041 Quad True/Comp. Buffer	54p
CD4042 Quad clocked D type catch	56p
CD4043 Quad Nor R/S Latch	54p
CD4044 Quad Nand R/S Latch	54p
CD4045 4 Bit Par. in out shift	72p
CD4046 Micro Power PH. Lock Loop	36p
CD4047 monostable	72p
CD4048 Exp 8 input gate	36p

CD4049 Hex Inverter Buffers	36p
CD4050 Hex Buffer converter	38p
CD4051 Analogue Multi/Demulti	36p
CD4052 Analogue Multi/Demulti	56p
CD4053 Analogue Multi/Demulti	52p
CD4054 4 Line LCD driver/count	72p
CD4055 BCD 7SEG. Decoder/Drive.	72p
CD4056 Decoder	£1
CD4060 count 14 stage + osc.	90p
CD4061 256 x 1 Bit Static RAM	£5.30
CD4063 4 bit magnitude comp.	72p
CD4066 Quad Bilateral Switch	27p
CD4067 1.16 MULTIPLEXER	£2.12
CD4068 8 bit I/P Nand	20p
CD4069 Hex inverter	16p
CD4071 quad 2 input or buffer	16p
CD4072 dual 4 input or	15p
CD4076 Quad D Flip-Flop	54p
CD4077 Quad Exclusive Nor	30p
CD4078 8 Input Nor	19p
CD4081 Quad 2 Input and Buffer	15p
CD4082 Dual 4 Input and	15p
CD4086 4 Wide 2 Input and/or Inv.	54p
CD4093 quad 2 input Nand S.T.	54p
CD4094 8 bit ser. par. hold bus reg.	72p
CD4095 JK. Gated flip flop non Inv.	72p
CD4096 gated JK flip flop	72p
CD4097 mux/demux 8ch.	£2.90
CD4502 Strobed Hex Inverter	44p
CD4508BF dual 4 bit latch	£1.78
CD4511 BCD 7 seg. latch dec/divider	72p
CD4514 decoder	£1.46
CD4515 decoder	£2.12
CD4517 2x64 bit Shift Register	£3.60
CD4519/MC14519 4 bit and/or Sel.	54p
CD4520 Dual Synch. 4 Bit BINARY	72p
CD4527 BCD rate multiplier	£1.20
CD4532 8In Priority encoder	£1.08
CD4556 decoder	72p
CD4556 Decoder	£1.46
CD22100 cross point switch	£1.78
CD40103 32 bit L/R Shift Reg.	£1.78
CD40101 9 bit Par. Gen. Check	£1.08
CD40108 4 x 4 Multiplex Reg.	£3.10
CD40160 Dec. Count. Async. clear	72p
CD40162 4 bit synch. Dec. Count R/S	72p
CD40163 Bin. count synch. clear	72p
CD40181BE Quad 2 Input and	£2.12
CD40182 look ahead carry block	72p
CD40192 Sync 4 bit BCD U/D count	72p
CD40194 4 bit L/R SR	72p
CD40208BF 16 bit multi port RAM	£2.12
CD40257 Data Selector	£1.15p
CDP1833 Cosmac Rom 1824 x 8	£3.60
CDP1834 Cosmac Rom 1024 x 8	£3.60
CM4116AE CMOS Quad Bilat. Switch	36p
CT11012 C Frequency Synthesiser	75p
CT1112	75p
CT1115 Frequency Synthesiser	75p
CT1116 Non Volatile NMOS Ram 16 x 14.	£1.50
Data held 30 hrs. after supply removed	75p
CT1119 NMOS 16 x 14 RAM Freq. Synth.	75p
DM8093 See 74125	-
FCH111 8 input Nand/Nor	8p
FCH201	18p
FCJ101	50p
FPO/MPQ3725 4 Tr. Array	45p
FZH11	18p
FZH191	18p
FZH201	18p
IG17103 4j Digit DVM/DPM	£2.04
IG3412 see 1535	-
LM300 Volt Regulator	42p
LM377 Dual 2 wt audio amp	£1
LM378 Dual 2 wt audio amp	£1
LM380 audio amp, 2 watt	60p
LM34076v Regulator	36p
LM1011N Dolby system	£1.00
LM1303N Stereo Pre Amp low noise	65p
LM3900 (See CA3401)	-
MC830P Dual 4 In Ext and	5p
MC833P dual 4 input expander	5p
MC837P Hex invert fast rise	5p
MC846P Quad 4 in Extend	5p
MC849 quad 2 in Nand/Nor fast	11p
MC862P Triple 3 in Nand	5p
MC863P Triple 3 in Nand Fast	5p
MC1127 Hybrid	5p
MC1306P Audio Amp, 6 watt	40p
MC1307P FM Stereo Decoder	35p
MC/CA/BRC 1310P St. Decoder	35p
MC1312P Stereo Decoder	40p
MC1314P 4 Channel sound	35p
MC1315P 4 Channel sound	35p
MC1350P Video I.F. Amp - A.G.C.	35p
MC1463P sound I.F. + Demod.	38p
MC1469G Pos 2 - 32v 200ma Reg.	38p
MC1723C Pos 2 - 37v 150ma Reg.	38p
MC3302L Quad amp (volt comparator)	75p
MC4044P Phase/Frequency detector	£1
MC4344P Phase/Frequency Detect.	£3.50
MIC2 monolithic sample hold	26p
MIC7C	25p
MK2686	36p
MK4012 Memory Static Shift Reg	38p
ML236B (6024) 6ch. touchtone	£1

ML237B (6108) 6 channel tuner	£1
MM5262 PMOS 2048 x 1 Dyn. RAM	80p
MM8008 C.P.U.	36p
MP3202 3j Digit DVM	£1.45
MT300 Volt Regulator	8p
MT305 Volt Regulator	8p
MW4050D Static Ram 200ns	£1.60
MWS5101 256x4 SOS CMOS RAM	£2.60
SAA661 FM 1F Amp/Detector	36p
SAA1025 TV Remote control	£4
SAA 5012 Teletext Binary Tuner	£2.75p
SGS308 4 diode array	5p
SGS9202	5p
SL4034 3 Wt. Amp.	38p
SL35203 see 1535	-
SN7528 Dual Core Memory S.A.	11p
SN15836 Hex. Inverter	25p
SN15845 Clocked Flip Flop	50p
SN15846 Quad 2 input Nand	37p
SN15851 Monostable Multivib.	50p
SN15858N Quad 3 input Nand	55p
SN15862 Triple 3 input Nand	6p
SN15707 Dual line Receiver	£1.15
SN15708 Diff line Receiver	36p
SN15710 Dual line driver	46p
SN157125 7 Line Rec. Interface	72p
SN157235N Dual Core mem. 5 Amp	11p
SN157451 Dual Periph. driver	36p
SN157463 dual periph. or driver	36p
SN16001 Audio Amp 5 watt	36p
SN16003 5Wt. Amp	36p
SN16013 5Wt. Amp	92p
SN16023 5Wt. Amp	36p
SN16110P FM Stereo Decoder	35p
SN16115N Stereo Decoder	35p
SN16131 Dual Pre Amp	51p
SN7627	36p
SN7628N	£1.60
SN76396 (TBA396)	£1.60
SN76650N 1 stage video I.F. + A.G.C.	50p
SN76660N	35p
SN76660N TV Sound Circuit	35p
SN76666N Sound I.F. + Demod. + Driver	35p
SN158093 Dual M.S.J.K. Flip Flop	50p
SN158097 Dual M.S.J.K. Flip Flop	5p
SN158099 Dual M.S.J.K. Flip Flop	50p
SP4021 ±64 VHF/UHF 50mv TTL O/P.	75p
SP4022 VHF/UHF + 64 hi-speed	75p
SP4030	75p
TAA263 Amp (low level)	75p
TAA320 Integrated most AMP.	35p
TAA550 Volt Reg.	10p
TAA700	£2.30
TAD100 AM Radio	£1.22
TBA120CQ/SB/B TV Amp	36p
TBA240	£3.90
TBA395Q TV Chroma Circuit	£1.50
TBA396 Luminescence and chrom.	35p
TBA550Q Synch. Sep. + A.G.C.	£1.25
TBA560C Lum/Chrom. control	52p
TBA800 Amp 5 Watt Audio	52p
TBA920 TV Line System	70p
TCA270Q/SA/ AE/QS Vlt. Det.	£1
TCA270/5B synch. demodulator	55p
TCA440 A.M. Receiver	£1.25
TCA830S Ex. Equip. A.F. Amp.	18p
TCA4401	£1.25
TDA0470 Organ, 2 tone Generator	37p
TDA1003 Pre-amp and eq	£1
TDA2020 audio amp 20 watt	£2.60
TDA2610 6 watt audio amp	71p
TDA2880 T.V. Signal processor	£1.83
TID25A 16 diode array	5p
TL41 Log-antilog amp	36p
TL 4720 AM Radio RF/IF Amp	73p
TMS 7B J. Fet SPDT switch + driver	53p
TMS 3409 memory 80 bit shift reg.	£1.10p
TMS4034 Memory	£1.08
µPD4111C 200ns Dynamic 4096 x 1 ram	£1.30
XR215 Hi-freq. phase lock loop	£2

THE MODERN BOOK CO

THE ART OF ELECTRONICS by P. Horowitz **Price £13.50**
 Suitable for those with no previous exposure to electronics and takes the reader through to a reasonable level of design proficiency.

World Radio T.V. Handbook 1981 Edition Price £10.50p	UNDERSTANDING MICROPROCESSORS by Texas Ins Price £4.00	ARRL Amateur Radio Handbook 1981 Price £8.00
REPAIRING POCKET TRANSISTOR RADIOS by I. R. Sinclair Price £2.55	THE OSCILLOSCOPE IN USE by I. R. Sinclair Price £3.50	COST EFFECTIVE PROJECTS AROUND THE HOME by J. Watson Price 4.50
TEST GEAR PROJECTS by T. Dixon Price £4.50	PROJECTS FOR THE CAR & GARAGE by G. Bishop Price £4.00	AUDIO CIRCUITS & PROJECTS by G. Bishop Price £5.35
ELECTRONICS - BUILD & LEARN by R. A. Penfold Price £3.20	SIMPLE CIRCUIT BUILDING by P.C. Graham Price £2.75	PRINTED CIRCUIT ASSEMBLY by M. J. Hughes Price: £2.75
AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR by I. R. Sinclair Price £3.00	UNDERSTANDING HI FI SPECIFICATIONS by John Earl Price £3.40	MICROPHONES IN ACTION by V. Capel Price £5.00
BEGINNER'S GUIDE TO INTEGRATED CIRCUITS by I. R. Sinclair Price £3.50	BEGINNER'S GUIDE TO DIGITAL ELECTRONICS by I. R. Sinclair Price £3.50	BEGINNER'S GUIDE TO COLOUR TELEVISION by G. J. King Price £3.50
BEGINNER'S GUIDE TO RADIO by G. J. King Price £3.50	ELECTRONICS POCKET BOOK by P. J. McGoldrick Price £5.00	HOW TO BUILD ELECTRONIC KITS by V. Capel Price £2.50
110 ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR by R. M. Marston Price £4.35	PROJECTS IN RADIO & ELECTRONICS by I. R. Sinclair Price £2.50	ELECTRONIC GAME PROJECTS by F. G. Rayer Price £2.75
ELECTRONIC PROJECTS IN THE WORKSHOP by R. A. Penfold Price £2.75	UNDERSTANDING CALCULATOR MATH by Texas Ins. Price £4.00	UNDERSTANDING DIGITAL ELECTRONICS by Texas Ins. Price £4.00
	UNDERSTANDING SOLID STATE ELECTRONICS by Texas Ins Price £4.00	HOW TO BUILD SPEAKER ENCLOSURES by A. Badmaieff Price £3.50
	AMATEUR RADIO TECHNIQUES by P. Hawker Price: £3.70	

We have the Finest Selection of English and American Radio Books in the Country
ALL PRICES INCLUDE POSTAGE


19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone: 01-402 9176

RX 80 MkII - A DIY SOLID-STATE-OF-THE-ART MODULAR DUAL CONVERSION RECEIVER SYSTEM FOR THE ENTHUSIAST

AS DESCRIBED IN JAN/FEB/MAR 81 RADCOM BY TONY BAILEY-G3WPO : REPRINTS £1 inc

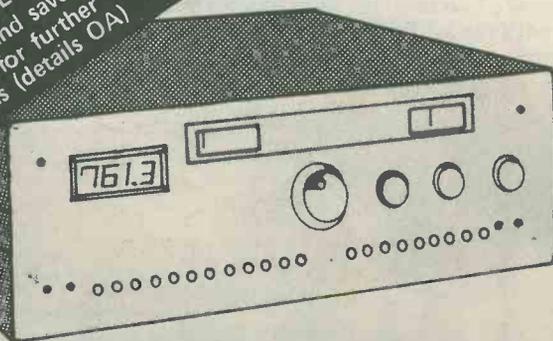CLUBS & COLLEGES:
 Buy 5 kits and save 10%
 Buy more for further
 reductions (details OA)



- * LOW DRIFT VARICAP TUNING (READILY ADAPTABLE FOR SYNTHESISED/ HUFF&PUFF STABILIZATION)
- * DUAL CONVERSION BASED ON A 3-4 MHz SSB IF, WITH MECHANICAL IF FILTER, AUDIO DERIVED AGC, BALANCED MIXER, WITH ON-BOARD AF AMP AND VOLTAGE REGULATOR
- * CAPACITY FOR UP TO 12HF/VHF/UHF 1 MHz WIDE CRYSTAL CONTROLLED CONVERTERS WITH TRACKED RF TUNING
- * EACH CONVERTER SELF CONTAINED - SO MORE CAN BE USED EXTERNALLY IF REQUIRED. RF PATHS ARE DC SWITCHED AT LOW IMPEDANCE

PRICES

RX 80 Mk II tuneable 3-4MHz SSB receiver/IF with MFL series 2.4kHz mechanical SSB IF filter	..£42.66
A/A but with low cost 4kHz CFM2 series filter	..£32.42
HF Converters, including crystal for the following bands: 1-2MHz, 7-8MHz, 10-11MHz, 14-15MHz, 18-19MHz, 21-22MHz 24-25MHz, 28-29MHz, 29-30MHz	..£9.10 ea
Hardware: Case, meters, pots, knobs (exc. DFM)	..£25.00
Complete RX 80, 6 converters, switches, case, PSU	..£132.50

CURRENT OPTIONS INCLUDE

* LCD DFM with built in IF offset, interface PCB	..£23.75
* HUFF/PUFF vfo stabilizer	..£9.60
* NBFM adapter inc 8kHz multielement ceramic IF filter	..£9.95
* Constant Z PIN diode attenuator	..£4.95
* 12v low RF noise mains PSU	..£7.95

PLANNED ADDITIONS TO THE SYSTEM

- 3-4MHz IF frequency synthesiser
- 'UP Conversion' front end system
- AM IF adapter
- Noise blanker
- VHF/UHF converters with helical filters




PRICES EXCLUDE VAT (15%). Postage 50p on orders under £12. Free postage on orders over £12, except please note any order including HARDWARE should be accompanied with a £2 carriage charge. General price lists are available FOC with an SAE - full AMBIT catalogues including a multitude of radio parts/components £1.80 a set - or 70p per section.

AMBIT international TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG
200 North Service Road, Brentwood, Essex

NEWS . . . AND

USEFUL TOOL FOR THE WORKSHOP

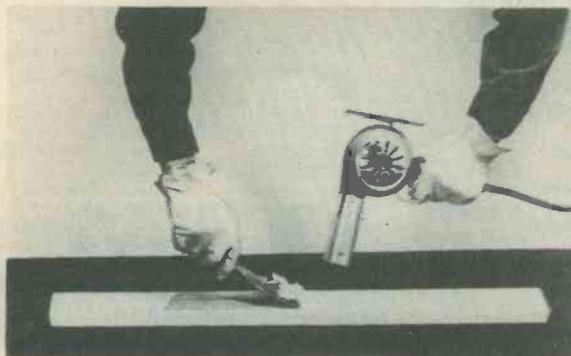

Eraser International have announced the availability of a new Heat Gun, the Model 4499E.

The Heat Gun provides controllable blowing hot air at a temperature of up to 750 deg.F which when

applied to the work piece will soften paint right through to the bottom layer. The softened paint may then be lifted off with a spatula or scraper, the paint scrapings are dry, not gooey, avoiding the mess traditionally associated with paint stripping.

Unlike chemicals and open torches, the Heat Gun method releases no vaporised lead fumes nor at any time will it scorch the wood surface as a torch will.

The Heat Gun is also a useful tool for such applications as shrinking tubing, soldering, P.C.B. drying, glue curing, and any other application where a controllable flameless heat source is required.

The Heat Gun is light in weight, 1.5lbs and operates from 220/240 volt 50Hz single phase electricity supply.

Further information is available from Eraser International Limited, Unit M, Portway Industrial Estate, Andover, Hants.

HOME VIDEO

Many people buy video recorders for the benefit of recording programmes while they are away or watching another channel and to show the odd pre-recorded tape bought for a special occasion. But the convenience the video tape recorder brings to the home is not the only benefit it provides. When the recorder becomes the heart of a home video system it can provide hours of fun, entertainment and a source of inspiration for the creative members of the family who can select from a wide range of accessories and additional equipment to record everything from family parties to home movies. A most comprehensive range for the beginner or amateur enthusiast is available from Sony.

CAMERAS

The recent introduction of high quality colour video cameras enables owners to produce their own tapes easily, instantly and economically. Sony has a range of colour and black and white cameras to meet all requirements.

Cine cameras have provided much amusement in the past but are more expensive than video to run - just compare 3¼ hours of video fun for under £10 with six minutes of cine film at £12 (including processing and printing).

C7 RECORDERS

Over the last year Sony's SLC7UB has become much sought after due to exceptional picture quality as well as features which offer flexibility and convenience. It is also well styled to fit unobtrusively into the home.

PORTABLE RECORDERS

Having recorded activities in the home and become more enterprising with the addition of a portable recorder, the camera can be taken out of doors for holi-

days, picnics and sporting occasions. The Sony SL3000 runs off a rechargeable battery pack and is easily carried with the aid of a shoulder strap.


The camera and recording equipment is so easy to use, because most of the critical adjustments can be taken care of automatically, that it does not take long to become an expert: To add the finishing touch to video tapes a Sony Special Effects Generator can be used to superimpose images. With this simple equipment tapes can be given titles and credits, subtitles can be added to pictures and family tapes can be transformed into professional productions.



Shown in this picture are the HVC 200P colour video camera, the SLC7UB video recorder and the KV1612UB Trinitron television.

... COMMENT

The beginning of the
WORLD
is nigh...

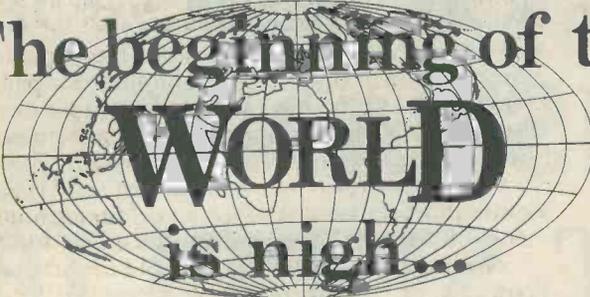

... part 1.

Regular readers of this magazine will have no doubt been wondering where the recent comments, surveys and promises of 'things to come' were leading. The answer is supplied herein, in the shape of a sample from the new-style **Radio & Electronics World**.

We have been taking careful note of the comments we have received (even the rude ones!), and these have all been taken into consideration with the new style and presentation of the magazine. Whilst this new style will seem a complete departure from the current format of *R&EC*, the aims and objects of the magazine remain essentially similar to those set out by Arthur Gee in the first issue of *Radio Constructor* in August 1947.

That issue was launched into the post-war era, when civil electronics was able to reap many of the benefits brought about by the enormous advancement of the science that had been telescoped down into the war years. We entered WW II using bi-planes, yet came out with the first turbo jet aircraft. We enter this new era in supersonic civil transport, yet unless technologists can do something drastic and meaningful, we may emerge at the turn of the century back on our push-bikes.

The age of energy conservation is upon us, and just as the nascent communication age provided much scope for original thought and experiment, so we feel the exploitation of alternative energy sources provides scope for the enthusiastic technologist. And after all is said and done, technology is about serving people and creating a more desirable environment in which to live.

Just at the present time, this may seem a rather presumptuous statement. But the tools to achieve this end have been at our disposal for some time now. The resolve of the more narrow minded, short sighted - and to be perfectly honest - technologically ignorant and naive politicians seems to have been the main stumbling block.

The key to the course of progress towards a society that is better aware of the technology, and that can thereby lead to an enhancement of the quality of life, is largely in the hands of those who attempt to disseminate the basic knowledge and ideas. Let us hope that the millenium sees us emerging in supersonic transport, powered by ecologically pure hydrogen, created by solar energy. Not on those push bikes - which presently seem to loom all too large.

You and **Radio and Electronics World** could have a very real part to play in the charting of this progress.

NEW AMERICAN POWER SUPPLY SERIES

Telecommunications, military environment, undersea mining, aerospace and high reliability commercial applications are among many uses projected for the new Y-95 Series of modular, encapsulated, switching regulated, DC to DC converters now being offered by Technipower, A Penril Company, of Danbury, Connecticut.

The new power supply series is designed to meet 30,000 hours MTBF at stress levels of 95 deg. C base temperature and has a switching frequency of 25 KHz to assure maximum (80%) efficiency consistent with latest state-of-the-art circuitry. A company spokesman pointed out that there are 100 models in the series, with output voltage ranges from 2.8 VDC to 250 VDC and that design efforts are close to completion for units up to 400 Watts. It was further stated that the modular, sealed and encapsulated package was designed for harsh environment reliability.



VMOS DEVICES AND CONSTANT CURRENT SUPPLIES

Jonathan Charles Burchell

The electronics enthusiast is often faced with the task of building reliable regulated supplies and the introduction of three terminal voltage regulators has made the building of constant voltage supplies a simple matter, and superseded the need for boards full of op-amps and steaming power transistors.

The constant current source, an equally valuable item, is an area which seems to have been sadly neglected, yet the introduction of so much new equipment with rechargeable batteries increases the need for a three terminal approach to such supplies even further.

The Vmos fet offers just such a solution, and perhaps it will come to be regarded as a three terminal current regulator with the same popularity as the 78xx series of voltage regulators.

WHAT IS VMOS TECHNOLOGY?

For many years ago Fet's were only available at power levels below 1 watt this limited their application in power supplies. Little interest was shown in them as power devices.

The breakthrough came with a new fet technology which allows the production of high current, high voltage fets. This is the so called Vmos technology, which exploits a vertical current flow to achieve its

high power capabilities. It is now possible to obtain fets with voltage and current levels similar to the largest bipolar devices.

Fig.1. shows a cross section of both a conventional fet and the new Vmos type, illustrating clearly where the name comes from.

In the conventional fet the current flow is horizontal, unlike Vmos and bipolar devices where the current flow is vertical. For a given current the chip area had to be much larger than its bipolar counterpart, this meant higher cost and lower yield of working devices. Medium power conventional fet's were therefore very costly and higher power devices almost unthinkable.

The epi layer of the Vmos device increases the drain-source breakdown voltage, by absorbing the depletion region from the drain-body junction which is normally reverse biased.

In use, both the gate and drain are positive with respect to the source. The gate produces an electric field which induces an N-type channel in the body facing the gate, allowing electrons to flow from the source, through the n-type channel and epi layer into the drain. The depth of the channel is controlled by the voltage on the gate and the current flow through the device is similarly affected.

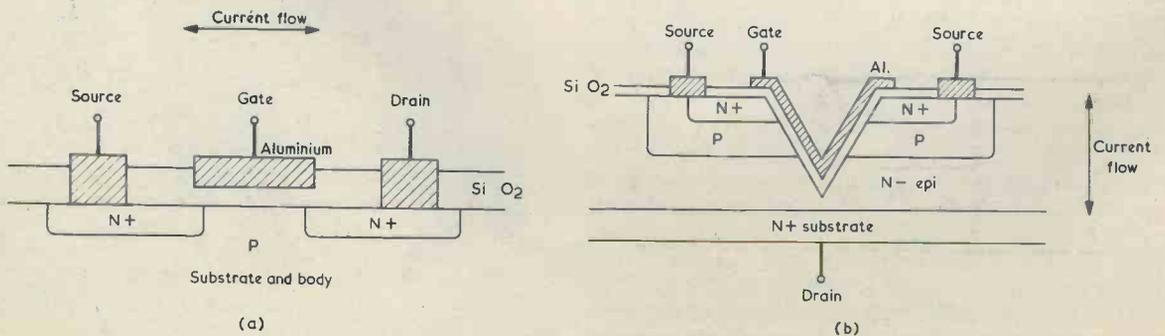


Fig. 1. (a) Cross section of Conventional Mosfet (b) Cross section of Vmos device

VMOS CHARACTERISTICS

Fig. 2. shows the output characteristics of a typical Vmos device. The very low output conductance of the device leads to the curves being very flat. (Note that the drain current will remain at 0.4A for a gate voltage of 4V over the range 8V-50V). Unlike bipolar devices the temperature coefficient of the Vmos drain-source voltage is positive, the device therefore draws less current as it heats up, making thermal runaway an impossibility. If the current density were to increase at one point in the channel the local heating would cause a drop of current in that area and a redistribution throughout the rest of the channel. This mechanism prevents the formation of 'hot-spots' - a major cause of breakdown in bipolar devices.

It also means that Vmos devices may be paralleled, and automatic current sharing will take place without the need for ballasting resistors.

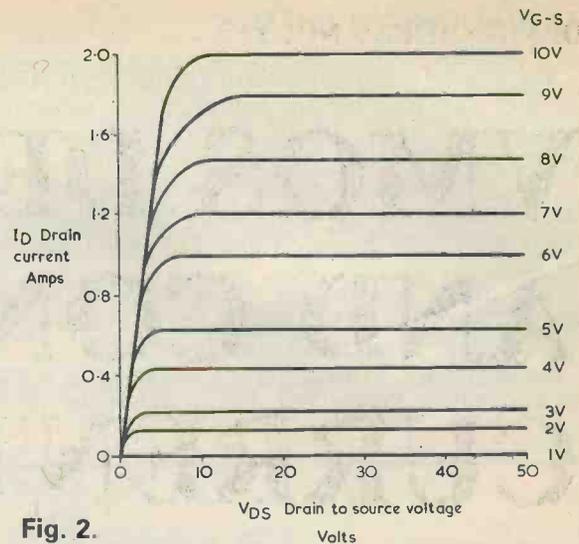


Fig. 2.

CONSTANT CURRENT SUPPLIES

Fig. 3. shows three types of constant current supplies 3 (a) is a conventional bipolar circuit. The base of T1 is held at a constant voltage by Zener Z1. R1 serves to monitor the current flowing and the developed voltage is applied to the emitter of T1. The result is that T1 will attempt to pass a current which maintains the voltage across R as close as possible to that of Z1. The performance of this type of circuit is not good, firstly the current measured by R1 is not exactly the load current as it also contains the base current of T1 which can be an appreciable amount of the total current, this also means that Z1 and R2 must be generously rated in order to provide a stable base voltage under all conditions of load.


Secondly, R1 must pass the load current plus the base current and the resulting dissipation leads to the use of large resistors and consequent difficulties. Lastly, the transistor T1 must be generously rated to prevent the possibility of thermal runaway and secondary breakdown.

The circuit of 3 (b) shows the ubiquitous 78xx device as a current regulator, the output current is controlled by R3 which must again pass the full load current and is therefore not easily made variable. The circuit is also limited to supplies of less than 1A and there is a


loss of some 7.5V across the typical 5 volt regulator. 3(c) shows the approach using a Vmos device, the gate is held at a constant potential by the potential divider network R4 and R5 and the drain current will thus remain constant, despite the variation in drain source voltage caused by the load.

As the gate current is microscopic (about 10 na) the potential can easily be made variable using a standard potentiometer resulting in a variable constant current source.

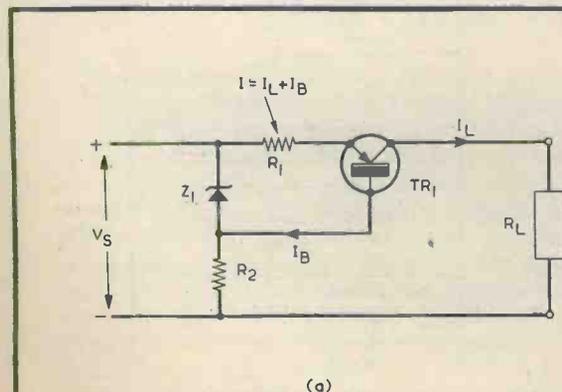
In fact the beta or current gain of a Vmos device is well over 10E9 so that it may be considered as truly voltage controlled.



(a)

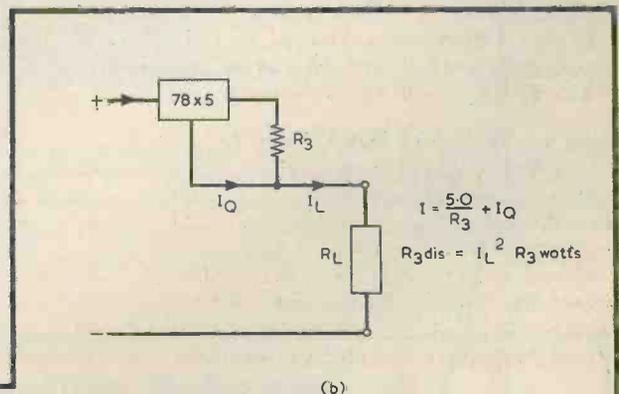

(b)

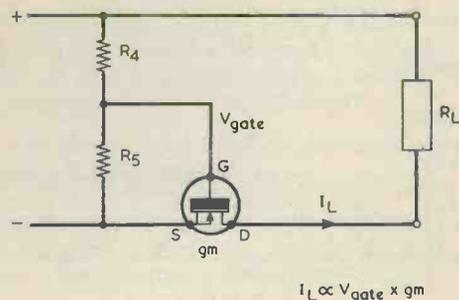

(c)

Fig. 3

ACTUAL CIRCUIT DETAILS

Fig.4. is the circuit diagram of a prototype 0-300mA variable constant current source. Fig.5. shows the performance of the circuit, and as can be seen it is pretty good.

The gate voltage is not stabilised in any way and relies on the input voltage current being constant, if this is not so then the Zener stabilisation of Fig.6. may be used.

The device selected for use is the VN66Af, this allows currents of up to 1 amp to be controlled and an input voltage of up to 40 volts to be used.

As the device is operating in a linear mode it must be adequately heatsinked. Fig.7. shows the power

dissipation curves for the VN66Af). The prototype used a 20W 6 degree C/watt heatsink and temperature effects were hardly noticeable.

Preset P1 is included as a means to set an upper current limit mainly to protect the included ammeter and transformer etc. rather than the Vmos device. For drain currents greater than .4A the gm of the Vmos device is constant, below this it tends to follow a square law and a resistor may be added at 'X' to improve the linearity of the output/input voltage for low current variable supplies.

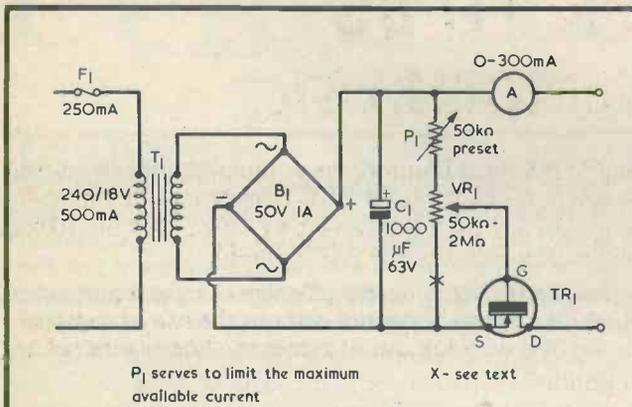


Fig. 4

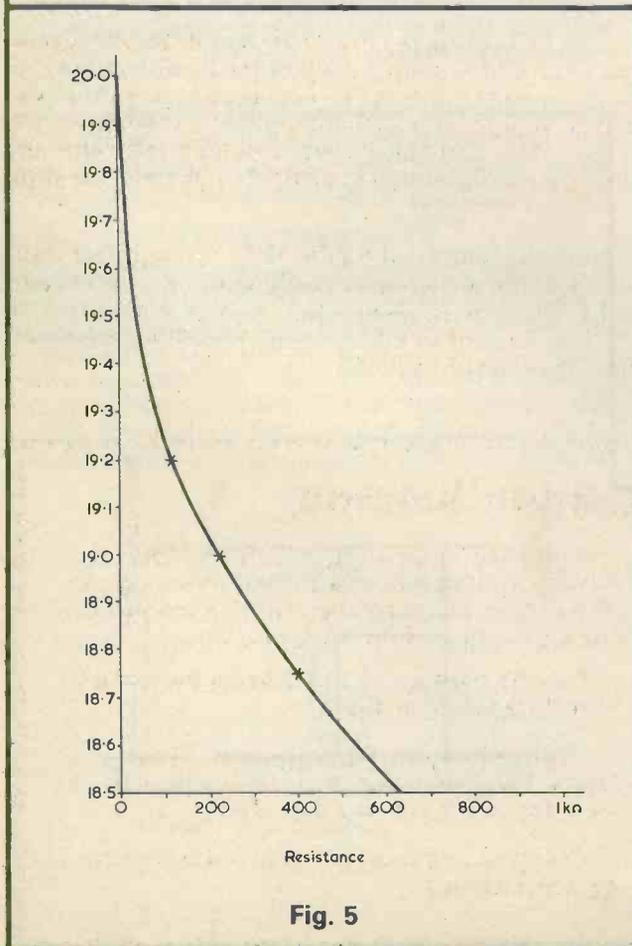


Fig. 5


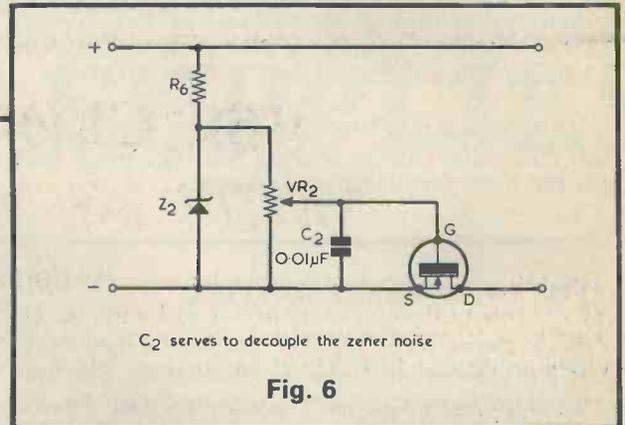


Fig. 6

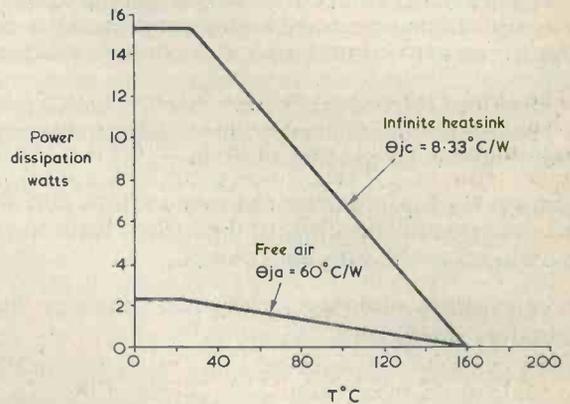VN66AF POWER DISSIPATION V_D CASE TEMPERATURE OR AMBIENT TEMPERATURE



VN66AF D.C. SAFE OPERATING REGION (log scale)

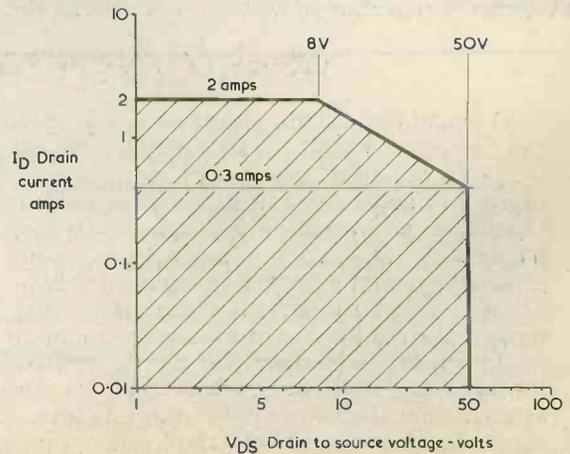


Fig. 7

INCREASED CURRENT SUPPLIES

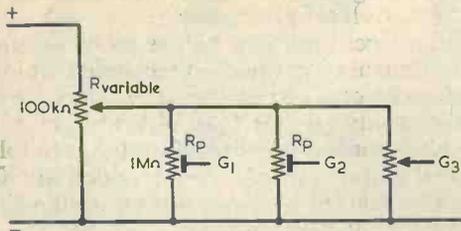


Fig. 8

Because of the inherent current sharing property of these devices any number of them may simply be connected in parallel to increase the load capacity. However sampling of a large batch of VN66AF's showed that there was considerable variation in gm between devices, and so the circuit of Fig.8. is recommended as this allows the devices to 'track together'. Another good idea is to install 0.1 μ f capacitors from gate to earth, as with such a high impedance input, a good deal of noise pickup can occur. ■

BBC CLOCK TO BE MADE BY McMICHAEL

Following an agreement reached between the BBC and McMichael Limited, the equipment that electronically produces the clock and logos, which appears at programme junctions on BBC television, is to be made available to other broadcasters. It will be manufactured by McMichael Limited under licence from the BBC, and will allow other broadcasting organisations to benefit from this advanced technology.

The equipment was developed by Richard Russell of the BBC's Engineering Designs Department, who said, "We needed to find a cheap way of producing a clock and network symbol without the use of cameras. Adopting a solid state approach avoids the problems associated with the use of cameras, slide scanners and mechanical clocks, especially when in continuous operation".

The microprocessor generated symbols have been in use on BBC 2 since last September. Besides producing the clock and its associated logo the equipment can also be programmed to produce static logos such as the Open University symbol, or simple animated logos.

The clock symbol is generated from two components. The first covers the fixed elements of the clock face such as numerals, centre spot and gating circles, which are produced by storing the positional information in a Programmable Read Only Memory (PROM). The other component involves the moving elements, the clock hands themselves. These are generated in a similar fashion, although the data is stored in a random access memory (RAM). A microprocessor keeps track of the time of day, and once every second it calculates the correct angles and positions of the hands. The network logo data is also stored in a PROM and it is possible to generate up to 32 different colours.

The facilities offered by the generating equipment were demonstrated at the IBC 80 exhibition last September. Many visitors to the show expressed an interest in the equipment, resulting in the new licence agreement. BBC designs are often available for licence by British manufacturers and industry; and this is the second such licence taken by McMichael this year. The first, the advanced four fields standards conversion equipment ACE, will be at the Montreux International Television Symposium.

Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who have become the subject of liquidation or bankruptcy proceedings and who fail to supply goods or refund money. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.

For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

Simple Stereo * * Amplifier * * *

T. J. Johnson



View of front panel of amplifier

The simple stereo amplifier to be described here was originally constructed to be a useful addition to the workshop as a test instrument. However the design and general appearance is such, that it would not look out of place in any home as the basis of an audio system.

DESIGN

As the amplifier was required to fulfil a specific purpose, a quick and easy way of connecting a signal was needed. For this reason terminals have been used for the input connections. Although a standard DIN socket, wired to suit most equipment has also been included.

The circuit is based on a familiar IC, the TBA810S. Although this type of IC may be considered obsolete when compared with more recent types, it does have the advantage of offering good performance at low cost with a low quiescent current and at the same time being thoroughly tried and tested.

The IC is capable of delivery 7W maximum (RMS) into a 4ohm load when used with a 16 volt supply. At very high outputs the distortion is noticeable, but when used at normal listening levels is insignificant. The full amplifier contains tone controls based on the familiar Baxandall tone network*, and gives a remarkable range of control over the bass and treble frequencies. The table of Fig. 1. gives the specification for the complete stereo amplifier.

CIRCUIT DESCRIPTION

The full circuit for the Simple Stereo Amplifier is shown in Fig. 2. Only one channel is shown, the second being identical. The power supply is common to both of course.

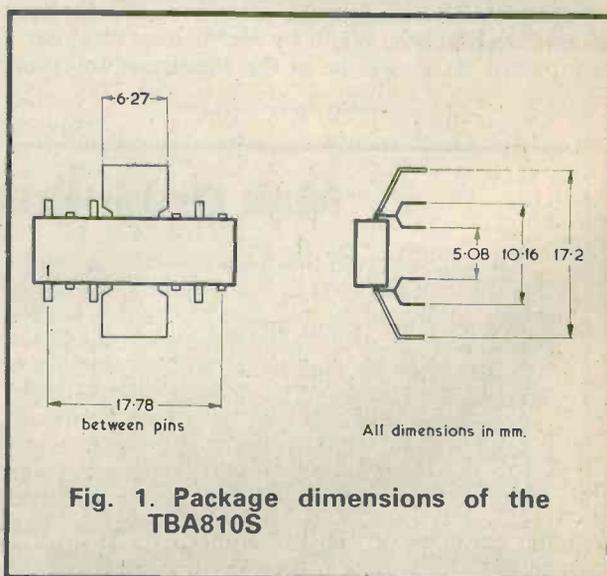


Fig. 1. Package dimensions of the TBA810S

*Baxandall considerations, see National Semiconductor Audio Handbook.

The input signal is applied via the chosen sockets to the volume control VR1. The signal is then tapped off by the wiper and applied to the tone control network consisting of VR2/VR3 and their associated components. Operation of the tone control network is quite complicated* and would be too lengthy to show here. Suffice to say that VR2 has control over the bass frequencies, and VR3 controls the treble frequencies. From the tone control network (wiper of VR3) the signal passes to the input of the IC at pin 8. The majority of components associated with the IC provide for hum rejection and stability.

The overall gain of the IC is dependent on the ratio of the internal feedback resistor, nominally 4kR and the value of R5. With the values shown, the gain is about 80. Capacitor C6 reduces any hum present on IC bias voltages to a very low level. Capacitors C7 and C10 control the overall frequency response of the IC. To some extent the values are affected by the value of R5. With the values here the upper cut-off frequency is about 15kHz, after which the response falls very rapidly. R6 and C8 form a "Zobel" network. These components in parallel with the speaker, present a load to the output of the IC which is close to a pure resistance at RF. This arrangement greatly reduces instability at high frequencies.

The output coupling capacitor C11, to some extent determines the bass content of the output signal. Basically a high value will give a large amount of bass, while a smaller value will give less bass in the output. The value has been chosen with particular speakers in mind, so some experimenting could be tried here.

POWER SUPPLY

The power supply is conventional and consists of a mains transformer and a few other components. Mains voltage is stepped down by T1 to give about 15V RMS across the bridge rectifier arrangement consisting of D1 to D4. After rectification, approximately 17V appears across the smoothing capacitor C14. No further regulation is required, so the DC voltage is applied directly to the remainder of the circuit. A neon indicator, NE1 is provided across the mains input to indicate that the amplifier is switched on.

COMPONENTS

There are no critical components. All types used here are readily available. It is important to obtain the correct IC. There are two available, one which has its heatsink tabs straight and punched with holes for mounting, and one which has preformed tabs for mounting directly onto a PCB. It is the latter, suffixed "S" which should be purchased.

A metal case measuring 9" x 5" x 2.5" was used for construction. Any other type of case could be used, although it must not be any smaller. A choice must be made at this stage to the type of input sockets to be used. As the main intention for the amplifier was for it to be used as a test instrument a quick and universal method was adopted for connecting a signal to the input. For this reason 4mm terminals were used and have since proved to be very useful. In parallel with the terminals is a standard 5 pin DIN socket wired to suit the majority of "Hi-Fi" equipment. If used as part of a "Hi-Fi" system then the terminals may be omitted, and perhaps phono sockets might also be used. Standard 2 pin DIN sockets are used for the speakers.


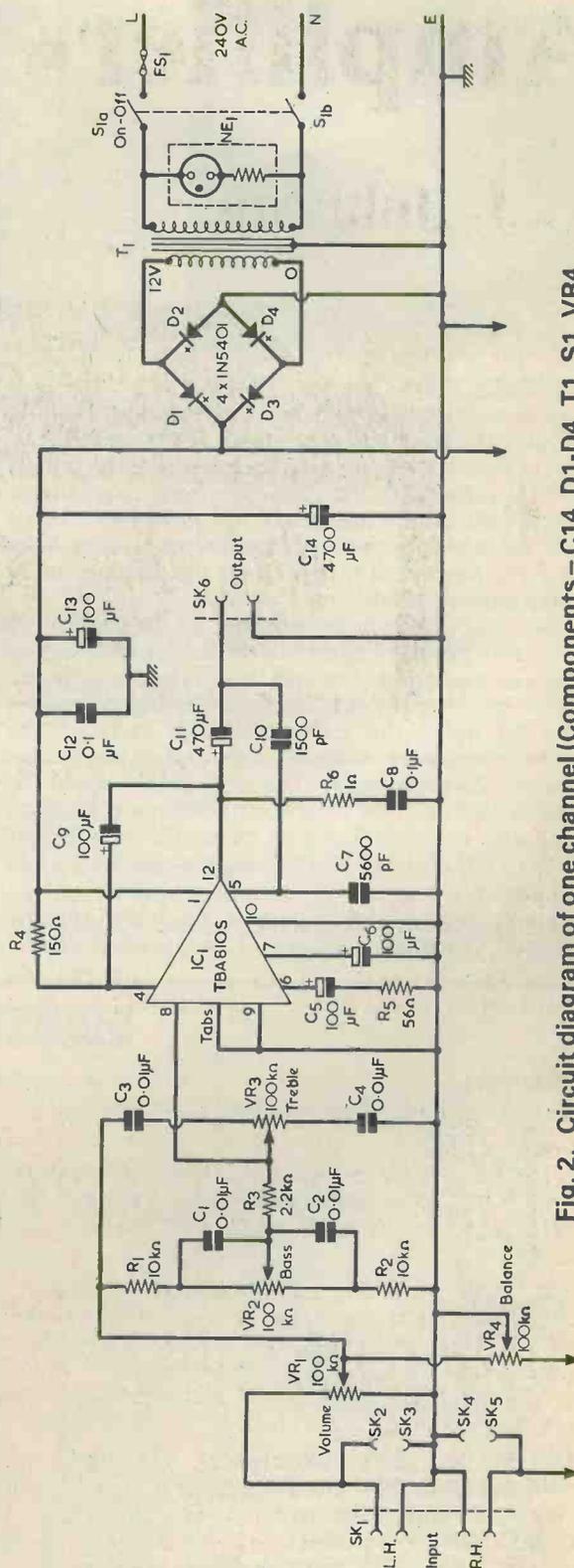


Fig. 2. Circuit diagram of one channel (Components - C14, D1-D4, T1, S1, VR4 and FS1 are common to both channels).

Internal layout of amplifier.

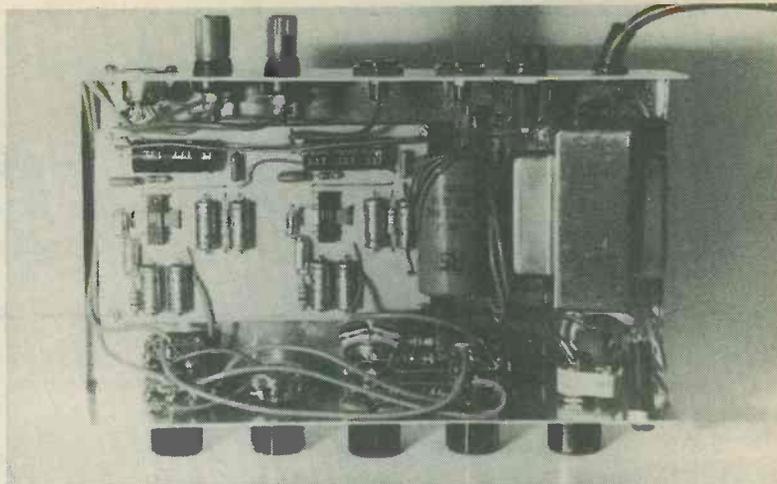

CONSTRUCTION

Construction can commence with the case. Drilling details for the front and rear panels is shown in Fig.3. The rear panel details assume the use of both terminals and DIN sockets. In the prototype both panels were covered with white Fablon and lettered using "Panel Signs" transfers. No drilling details for the base have been given as these will depend on the dimensions of the components used.

If the components to be mounted on the base are to hand, then offer each in turn to the base and mark the holes. The transformer should be mounted near to the right hand edge of the chassis, remembering to mount a solder tag under one fixing nut. The PCB will be mounted eventually at the opposite end of the chassis on four .25in. spacers. The tag strip should be positioned between the PCB and transformer. Position the tag strip so that it is slightly nearer the transformer than the PCB and with its feet facing towards the right hand edge.

Next the front and rear panel components may be mounted. Orientate the tags of the potentiometers

upwards vertically. This will then give the correct angle of rotation for the knobs. The body of the mains switch is turned through a slight angle to give a symmetrical appearance of the knob.

PRINTED CIRCUIT

Most of the components are mounted on a printed circuit board measuring 5" x 3". It is not essential to use a PCB, other forms of wiring board such as plain matrix board can be used. Providing the input connections are kept well away from the output no problems should arise. Note however that the PCB has been designed to act as a heatsink for the two ICs, hence the large amount of unetched copper. If a PCB is not used then some other form of heatsinking must be provided. A good alternative consists of a piece of copper board about 2.5" x 1.25" soldered to the tab of the IC. Four such pieces are required for the two ICs.

The copper pattern for the board is shown in Fig.4. This also shows the top side component side. The printed circuit board may be produced easily by an etch resist pen, the tracks are quite large to afford any

COMPONENTS

Resistors.

All .5w 10% 2 of each

- R1 10k Ω
- R2 10k Ω
- R3 2.2k Ω
- R4 150 Ω
- R5 56 Ω
- R6 1 Ω

Capacitors

2 of each

- C1 0.01 μ F polyester
- C2 0.01 μ F polyester
- C3 0.01 μ F polyester
- C4 0.01F polyester
- C5 100 μ F 25V electrolytic
- C6 100 μ F 25V electrolytic
- C7 5600pF polystyrene
- C8 0.01 μ F polyester
- C9 100 μ F 25V electrolytic
- C10 1500pF polystyrene
- C11 470 μ F 25V electrolytic
- C12 0.01 μ F polyester
- C13 100 μ F 25V electrolytic
- C14 4700 μ F 5V electrolytic (1 off)

Semiconductors

- IC1 TBA810S (2 off)
- D1-D4 1N5401 rectifier (4 off)

Potentiometers

- VR1 100k + 100k dual gang log
- VR2 100k + 100k dual gang lin
- VR3 100k + 100k dual gang lin
- VR4 100k balance single lin

Miscellaneous

- T1 mains transformer 12V AC secondary at 1A
- NE1 mains neon 240V
- FS1 1A 20mm fuse
- S1 d.p.s.t. switch
- SK1 5 pin DIN socket
- SK2-SK5 4mm terminals 2 off red, 2 off black
- Metal case (see text) e.g. ARBOUR EX2
- Panel mounting 20mm fuseholder
- SK6 2 pin DIN socket (2 off)
- Knobs, spacers, 6BA hardware, printed circuit board etc.

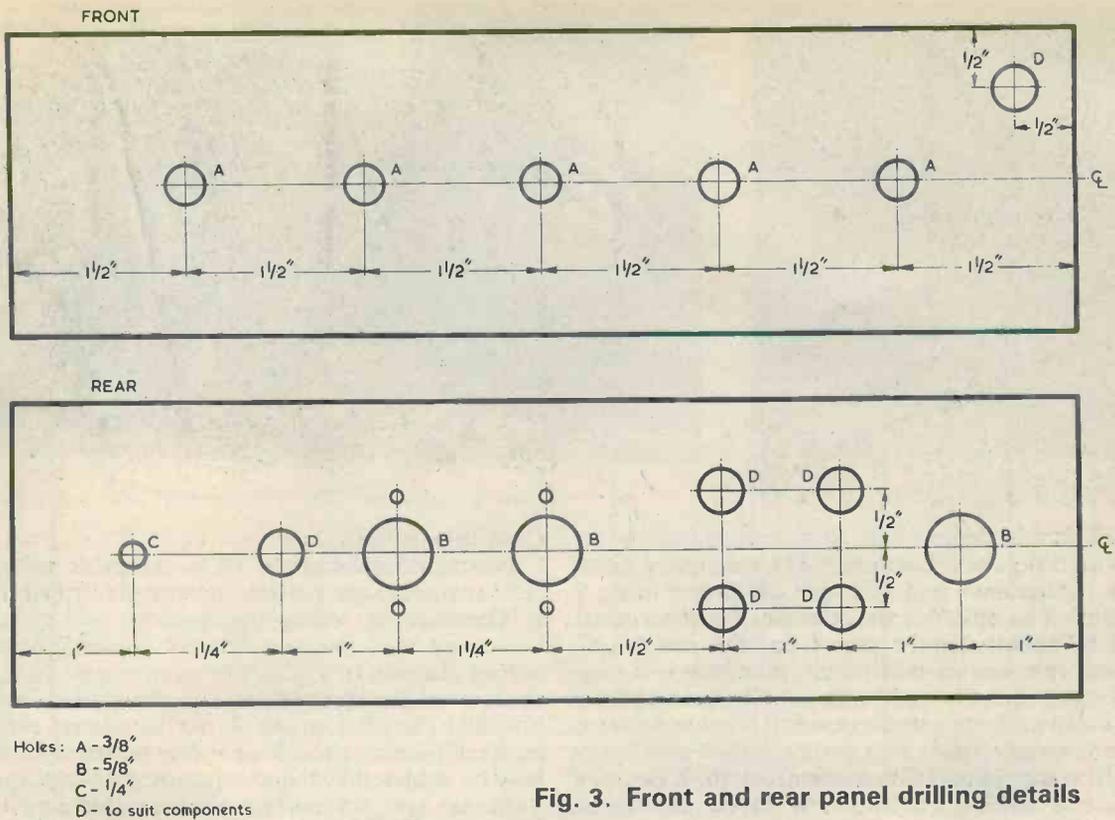


Fig. 3. Front and rear panel drilling details

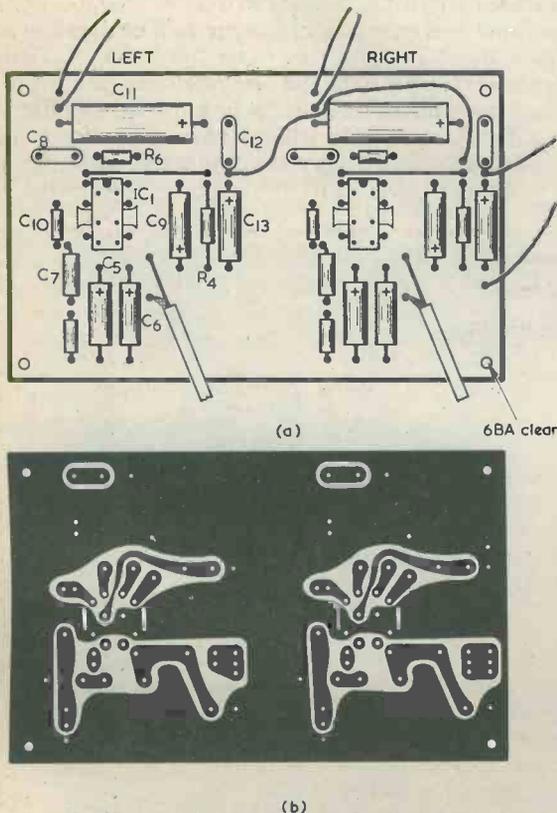


Fig. 4. (a). Component layout on top-side of board
 (b) P.C.B. underside (Note the four slots needed for the tabs of the i.c.'s)


Amplifier Specification

Output;
 6w into 4ohm load
 Frequency response;
 80Hz-19kHz+/- 2dB (Tone controls at mid-range)
 Distortion;
 At 1W - 0.17%
 At 3W - 0.21%
 At 6W - 3.2% } Measured at 1kHz.
 Input Sensitivity;
 (Volume control at max, frequency 1kHz)


Typical Voltages (IC1 and IC2 pin connections)

Pin	Voltage
1	- 17V
2	- NC
3	- NC
4	- 16.8V
5	- 0.76V
6	- 0.2V
7	- 8.7V
8	- Input
9	- Earth (OV)
10	- Earth (OV)
11	- NC
12	- 8.6V (Output)

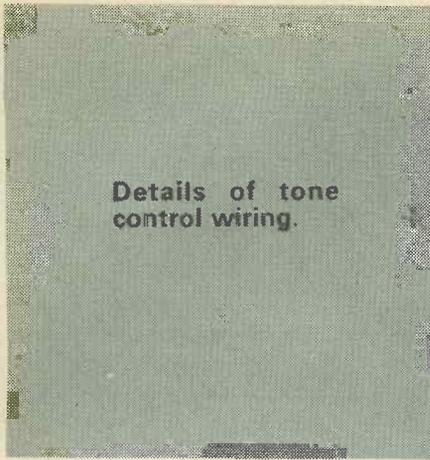(Measurements taken under no signal conditions with volume control at minimum. Supply voltage of 17.12V. Voltages taken using a DVM).



Details of tone control wiring.

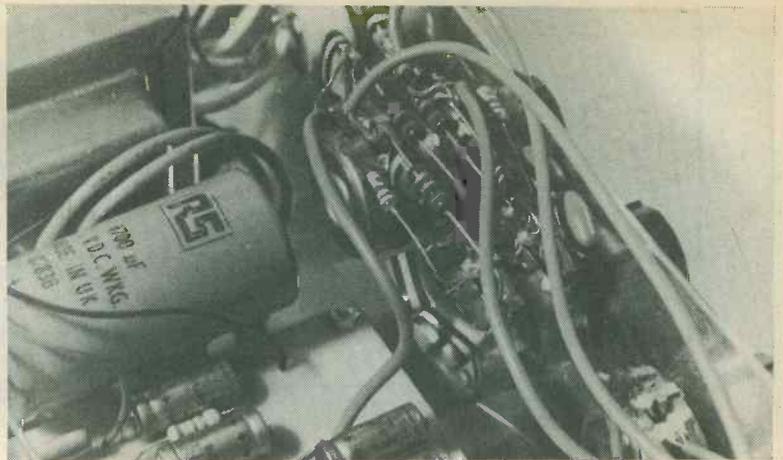

mistakes should the pen slip. Etch resist transfers can also be used to good effect here. After etching, the holes for the components and ICs may be drilled using a 1mm drill. The holes for the screen of the input leads should be drilled slightly larger. The slots for the IC mounting tabs are more difficult, and here it is suggested that a series of 1mm holes are drilled and then with a sharp knife the excess cut out. It is not imperative that the slots are neat, as long as the tabs can pass freely without the pins of the IC becoming distorted. The tabs can then be soldered to sufficient copper and there should be no problems.


The resistors and capacitors are mounted first, ensuring that the electrolytic capacitors are the correct way round. The two ICs can then next be mounted, observing the precautions mentioned in the previous paragraph. The screened leads can then be soldered, allowing about three or four inches for each. Similarly the speaker leads and supply leads each with a length of about four to five inches. Do not forget the two plain link wires and the insulated wire on the PCB.

CHASSIS WIRING

Having completed the PCB, mount it using four .25" spacers in the position previously drilled out for it. Continue by wiring the resistors and capacitors associated with the tone control network using the wiring diagram of Fig.5. The components have been opened out for clarity here, and should not be wired like this! The photograph shows the relative positions each component should take. The screened leads can now be soldered to their respective resistor/capacitor junctions and soldered at the opposite end to the volume controls. When wiring the balance control, if it is difficult to solder to the metal case of the potentiometer then a short lead can be taken to an earthed tag of one volume control.

The input and output sockets can then be wired in a similar manner.

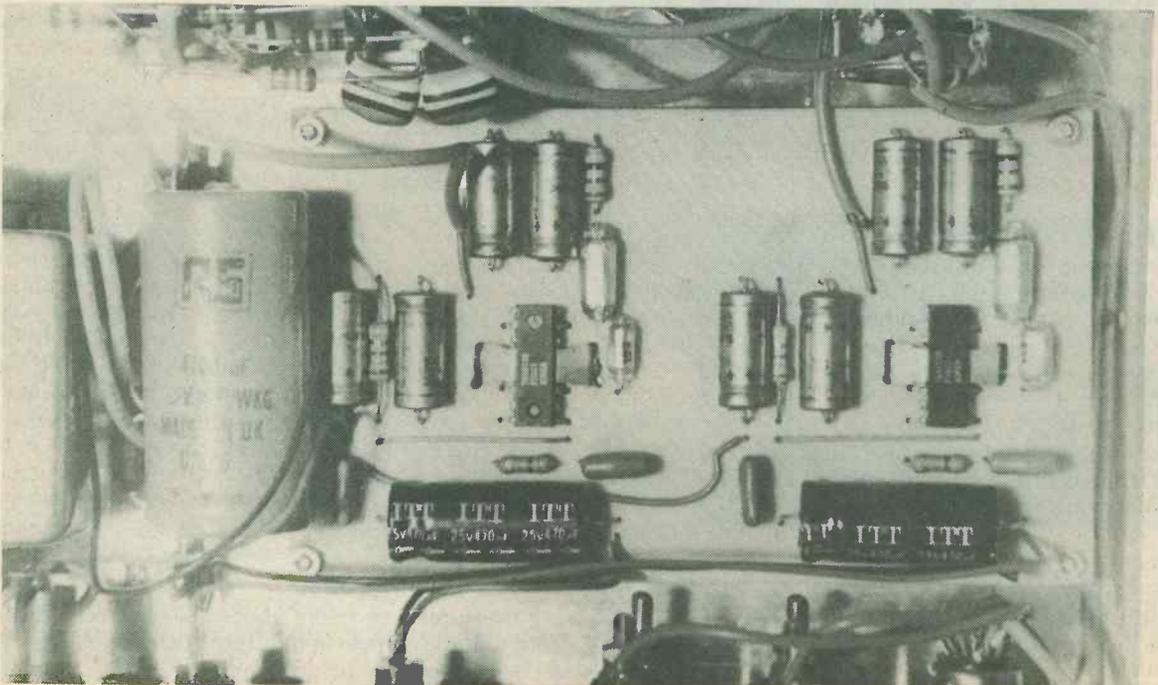The power supply is the last section to be wired. Here it is suggested that the leads of the large capacitor be left long and insulated. This will enable the capacitor to rest gently on the PCB thus providing some support for



Close-up of the amplifier p.c.b.

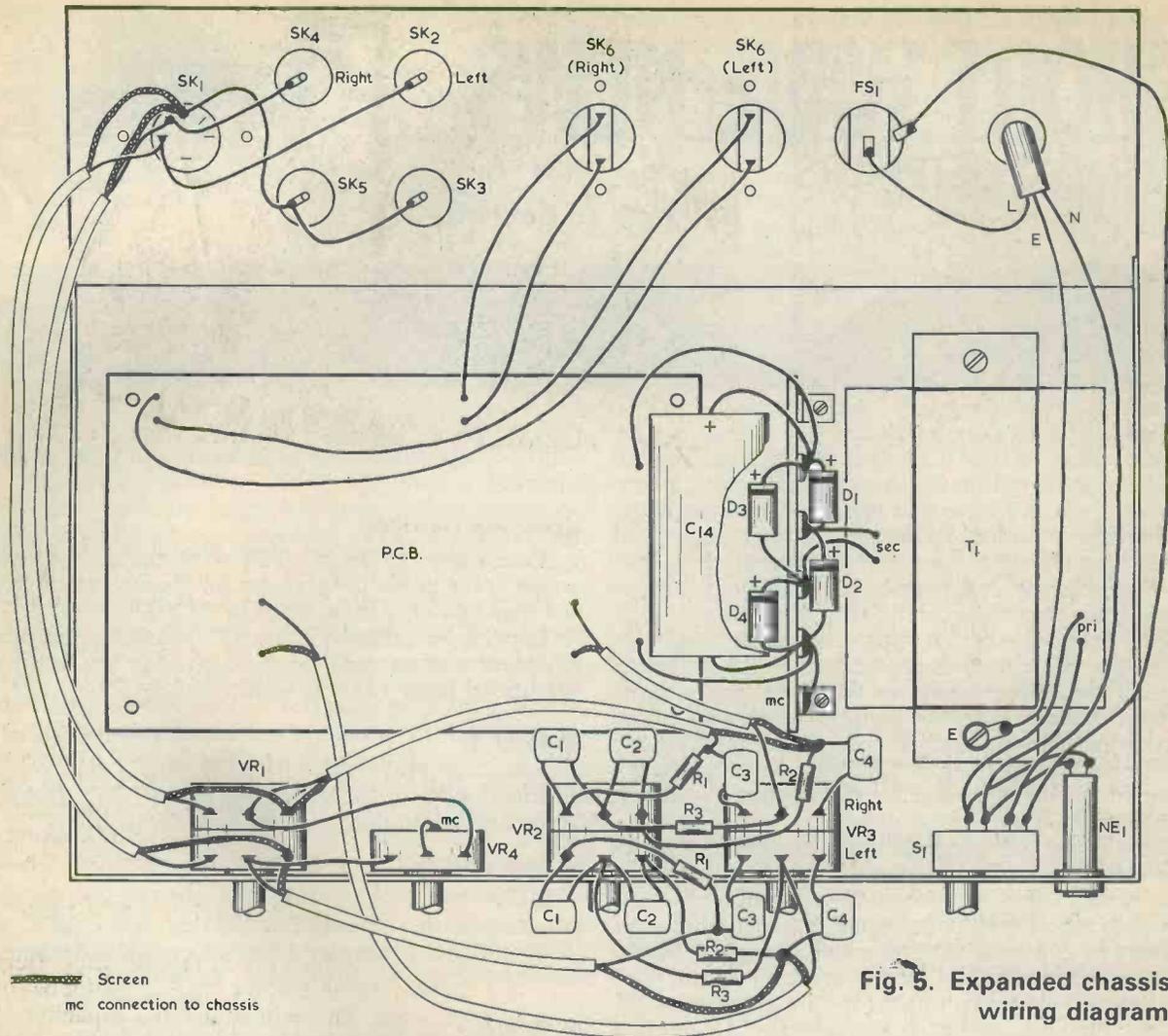


Fig. 5. Expanded chassis wiring diagram

this component. Note that only one tag of the tag strip is earthed and has wiring going to it. For safety reasons the exposed tags of the fuseholder, neon and mains switch should be insulated with tape. Also ensure that the centre tag of the fuseholder cannot touch the case of the transformer.

Finally the knobs may be pushed on and checked to see that their rotation is symmetrical, they should align correctly if the potentiometers have been positioned as mentioned earlier.

TESTING

Before switching on, remove the positive lead connected to the tag strip. Fit a one amp fuse and switch on. If possible measure the voltage across the smoothing capacitor C14. This should be 17 volts, and certainly no more than 20 volts which is the absolute maximum for the ICs. If all is well, switch off and reconnect the positive lead.

Set the volume control fully anticlockwise, and all other controls to mid position. Switch on and apply a signal to one input. A suitable signal if no signal generator is available, would be the loudspeaker output from a cassette or radio. Slowly rotate the volume control until the amplified signal is heard in the appropriate speaker. If no sound is heard check for faults before continuing.

If all is well, transfer the signal to the other input, and check this also.

Once both channels are working the two inputs can

be connected together and the tone control operation checked.

Turn the balance control to attenuate one channel, set the volume control to a comfortable listening level. Rotate the Bass control clockwise, the bass frequencies should be accentuated. Conversely, rotating the control in the opposite direction will attenuate the bass frequency response. Rotate the balance control to attenuate the other channel and repeat the tests.

A similar set of tests should be carried out using the Treble control.


If all checks out, then the amplifier may be connected to its intended input source. When the full rated output is being delivered, the ICs will get very warm over a long period of time, but providing there is sufficient heatsinking – and the heat is being dissipated effectively – there should be no real cause for concern. Note also that for normal listening levels, say up to three watts, the harmonic distortion is very low, typically less than 0.2%. Much above this power the distortion increases rapidly, and this should be kept in mind if comparative listening tests are being made.

CONCLUSIONS

Finally some constructors may prefer to have separate volume controls rather than the ganged controls as in the prototype. Here it is a simple matter to change the existing volume control to a single type and to use the balance control as a second volume control. ■

SHORT WAVE NEWS

FOR DX LISTENERS

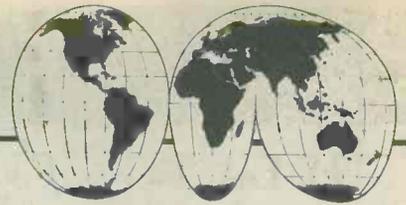

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

From time to time I receive letters from readers and from those within the short wave listening fraternity with whom I have had previous contacts. Much useful information is exchanged in this manner, one of my long standing correspondents being Bob Iball of Worksop – a well-known and respected Dixer of many years experience.

The exchange of Dx information by mail and telephone is a common occurrence in the Dx world and the writer is no exception when it comes to maintaining contacts by these methods. Bob and I have been in regular contact for more years than I care to remember, the arrival of his news and Dx notes – dumped on the doormat by the postman – always being received with great pleasure.

Then there are the general queries I receive, such as which receiver is best; which should I purchase; what is the best type of aerial for reception of so and so; what time should I listen for this or that station, country or continent and on which channels? Which club is the best; should I modify my receiver and how; can you tell me if this or that station sends out QSL cards? What equipment do you operate? Or perhaps the two classics “I cannot receive Sri Lanka, what is wrong with my receiver” and “I note the times in your article, when do you sleep”?

However, one reader has just sent in some items from his log and although I do receive these results from time to time it is the youthfulness and enthusiasm that impress me. M. Lavocah of Elm Park, Hornchurch, tells me he has received Helsinki on 11835 at 1950 with the English programme, Trans World Radio, Monte Carlo on 9500 at 0749 in English and Radio Norway on 9590 at 0811 also in English. Being 14½ years of age, he has been short wave listening for a year and half and the dedication to the hobby shines out from the pages of his letter. All success to him and the many other readers like him.

AROUND THE DIAL

In which are listed some of the transmissions heard recently and which, I hope, will be of some interest to some readers some of the time.

● NETHERLANDS

Hilversum on 11930 at 0816, when radiating the Dutch programme for Europe and the Middle East, which is scheduled from 0730 to 0820.

● FRANCE

Paris on 11770 at 0820, OM with a talk in the French programme intended for Central and Eastern

Europe, scheduled from 0800 through to 1700 on this channel.

● VATICAN CITY

Vatican on 11715 at 0822 with choral religious songs in the music programme for Europe scheduled for Sundays only from 0820 to 0830.

Vatican on 11740 at 1415, OM station identification followed by the Polish programme for Europe, scheduled from 1415 to 1430.

● ITALY

Rome on 11810 at 0850, OM with a talk about tourism in the Spanish programme directed to Australia and scheduled from 0830 to 0930.

● PORTUGAL

Lisbon on 11800 at 0848, OM with the Portuguese programme for Europe, scheduled from 0800 to 1800 on this particular channel on Saturdays and Sundays only.

● SPAIN

Madrid on 11730 at 0840, OM's with a discussion about Spanish democracy in the Spanish programme for Australia, scheduled from 0730 to 0900 (not Sundays).

Madrid on 11920 at 1404, YL announcer with a newscast in the Spanish programme for Africa, the Americas, Australia and the Philippines, scheduled from 1400 to 2045. Also for Europe and the Middle East up to 1800.

● YUGOSLAVIA

Belgrade on 11735 at 0845, OM with a talk in Albanian. This is one of a series of programmes which are relays of various local stations for the benefit of Yugoslavs abroad. The broadcasts are made on Saturdays and Sundays only and are timed from 0700 to 1100. That logged here emanated from Radio Pristina and is scheduled from 0800 to 0900 on Sundays. On Saturdays at the same time a programme in Serbo-Croat is radiated.

● ALBANIA

Tirana on 11985 at 0930, YL with station identification then OM with a newscast in the English programme for Asia and Australia, scheduled from 0930 to 1000. Also logged on the same channel at 1410 when the station identification was made, this being followed by a news review in the English programme to South East Asia and Australia, scheduled from 1400 to 1430.

● WEST GERMANY

Cologne on **11785** at 1747, OM with announcements concerning times of transmissions and frequencies, all at the end of the English programme for Asia and Australia, scheduled from 1720 to 1750.

Cologne on **11850** at 0955, YL announcer in a rendering of choral folk music in the English programme to Asia and Australia, scheduled from 0930 to 1030.

● EAST GERMANY

Berlin ("Radio Berlin International") on **11700** at 1334, YL with station identification then OM with a talk about Polish internal affairs in the English programme for South East Asia, scheduled from 1300 to 1345.

● CZECHOSLOVAKIA

Prague on **11855** at 0904, OM with a talk about local affairs in the English programme for Africa, the Far East, South Asia and the Pacific, scheduled from 0830 to 0900 (to 0930 on Saturdays and Sundays).

● ROMANIA

Bucharest on **11775** at 1510, OM and YL with news commentary in the English programme directed to Asia and scheduled from 1500 to 1530.

● GREECE

Athens on **11730** at 1515, OM with announcements, local music in typical style all in the Greek programme for North America, scheduled from 1500 to 1550.

● HUNGARY

Budapest on **11910** at 1521, when radiating a programme of folk songs and music in the Italian programme for Europe, scheduled from 1500 to 1530 (not on Sundays).

● FINLAND

Helsinki on **11755** at 1527, interval signal, station identification in several European languages and Arabic in the Finnish programme intended for Europe, North America and the Middle East and scheduled from 1500 to 1630.

● BULGARIA

Sofia on **11720** at 1900, YL with station identification followed by a programme in Italian for European consumption, scheduled from 1900 to 1930.

● CANADA

Montreal on **11935** at 1545, YL with station identification followed by "Reports from our Correspondents". All in the English programme for the USSR, scheduled from 1545 to 1600.

● BANGLADESH

Dacca on **11765** at 1906, OM with a newscast in English at dictation speed for Europe, scheduled from 1900 to 1915. The English programme is timed from 1815 to 1900.

● AUSTRALIA

Melbourne on **11740** at 0758, 'Waltzing Matilda', YL with station identification, time-check, OM with a newscast in English to Europe, the programme scheduled from 0700 to 0900 on this channel.

Melbourne on a measured **11819** at 0738, OM with

a newscast in the English programme for Papua New Guinea and the Pacific Islands, scheduled from 0700 to 0845 on this frequency.

● ZIMBABWE

Gwelo on **3396** at 1815, OM with a talk in English about local personalities in the General Service, scheduled from 0350 (Sundays from 0500) to 0545; from 1500 to 2200 (Sundays until 2105) on 100kW and from 0545 to 0615 on 10kW.

● BENIN

Cotonou on **4870** at 2043, OM & YL's with local music and songs in vernacular. This is the Home Service in French and vernaculars, scheduled from 0415 (Sundays from 0550) to 0800; from 1300 (Saturdays 1100) to 2400, closing time variable. Sundays from 0415 through to 2400. The power is 30kW.

● NIGERIA

Lagos on **4990** at 0534, YL with a religious talk in English. This is the National Programme in English and vernaculars being scheduled from 0430 to 1000 and from 1700 to 2310. The power is 20kW - I often listen to this one in the early mornings, it is an old habit as far as I am concerned.

Kaduna on **4770** at 0411, OM and YL with announcements in English then into a programme of local pops on records. This is the Home Service reportedly closing at 2320. The power is 50kW.

● NAMIBIA

Windhoek on **3270** at 2303, YL with a ballad in Afrikaans then local pops on records. This is the South West Africa Broadcasting Corporation operating from 1615 through to 0515 (also in parallel on **4965**). The power is 100kW.

● COLOMBIA

Radio Super, Medellin, on **4875** at 0359, OM with station identification "Radio Super", YL with announcements in Spanish, Latin American dance music in typical style. Radio Super operates around the clock with a power of 2kW.

Radio Melodia, Bogota, on **6045** at 0421, OM with announcements in Spanish ending with station identification and a few local news 'flashes'. Schedule unknown, power 5kW.

Radio Colosal, Neiva, on **4945** at 0346, OM with a newscast in Spanish of world events. The schedule is ground the clock and the power is 2.5kW.

La Voz del Cinaruco, Arauca, on **4865** at 0141, local pops on records, OM with announcements and commercials. The schedule is from 0900 to 0330 (closing time is variable) and the power is 1kW.

La Voz del Norte, Cucuta, on **4875** at 0041, local style dance music, OM announcer in Spanish, YL with a love song. The schedule is from 0930 to 0500 (both opening and closing times are subject to variation) and the power is 5kW.

● NICARAGUA

La Voz de Nicaragua, Managua, on a measured **5949.5** at 0428, OM with station identification followed by a talk about local affairs, all in Spanish. The power is 50kW, and this is the Domestic Service operating around the clock.

Continued overleaf

THE INTERNATIONAL AMATEUR RADIO UNION REGION 1 CONFERENCE

Report by Arthur C. Gee

The I.A.R.U. Region 1 triennial Conference was held at Brighton, between the 27th April and the 2nd May last.

The Conference was opened by the Rt. Hon. Timothy Raison, MP, Minister of State at the Home Office. Lord Wallace of Coslany and other distinguished visitors were also speakers at the opening session.

Some 140 or so delegates from more than 40 countries were present, and included delegates from the USSR, Africa, Middle East, USA and Canada, as well as of course, from European countries. Representatives from Japan and South America were also present.

A very large number of papers were presented covering all aspects of amateur radio activity. There can have been no previous conference of this nature which covered such a diverse range of topics. From I.A.R.U. Region 1 Finance and Administration through technical papers from 1.8 MHz to VHF and UHF and Microwaves, Contests and Direction Finding Rallies, RTTY and Amateur TV, Traffic procedures, Emergency Communications and DX expeditions, CB and its relationship with amateur radio, satellites and propagation studies, so one could go on. An infinite variety of matters affecting the future of amateur radio were very thoroughly discussed.

Amongst some of the interesting recommendations agreed were:- an offer by the RSGB to provide data processing facilities for the IARU Monitoring System; the Observation Service should include the supervision of technical quality of transmissions from amateur transmitters; the production of a pamphlet for distribution to new radio amateurs explaining what is necessary for good amateur operation in an endeavour to stop the deterioration of conduct on the amateur bands; speeds of 50, 75 and 100 bauds for RTTY operation to be encouraged; emergency networks to be fostered in those countries where they do not yet exist; the dividing line between VHF/UHF and microwaves to be 1 GHz; a Region 1 Satellite Co-ordinating Group to be formed; proposals put forward to transfer ATV from 70 cms to 23 cms, to stop the wideband interference on 70 cms from this mode of transmission; a new Locator System was put forward for consideration but was rejected; a proposal to limit the number of contests taking place on the HF bands; and very many more.

The above is of necessity a very brief resumé of some of the activities which took place during a very hectic week, which kept the hard working delegates well occupied. Whilst the recommendations of Conferences such as this one are not often immediately implemented, it is to be hoped that many of the recommendations soon will be.

SHORT WAVE NEWS (Continued)

● PERU

Radio Atlantida, Iquitos, on 4790 at 0425, dance music Euro-style, OM announcements in Spanish, station identification and off with the National Anthem at 0500. The schedule is from 0900 to 0500 (Sundays 0400) but sometimes around the clock. The power is 1kW. Be careful however, Sistema de Emisora Atalaya, Guayaquil, Ecuador also sometimes comes through on this channel but closes at 0400.


Radio Chinchaycocha, Junin, on 4860 at 0435, OM with announcements and a clear station identification then local pops on records. The schedule of this one is around the clock but sometimes operates on a Tuesday from 0800 to 0600. The power is 0.5kW.

Radio Loreto on a measured 5049.2 at 0440, OM with announcements in Spanish, local pops in usual style. The schedule is from 1100 to 0500 and the power is 2kW.

● COSTA RICA

Radio Reloj, San Jose, on a measured 6006 at 0418, YL with a talk in Spanish about Nicaragua (mentioned several times), OM with announcements at 0420 then into a programme of songs. The schedule is around the clock and the power is 1kW.

(Concluded)

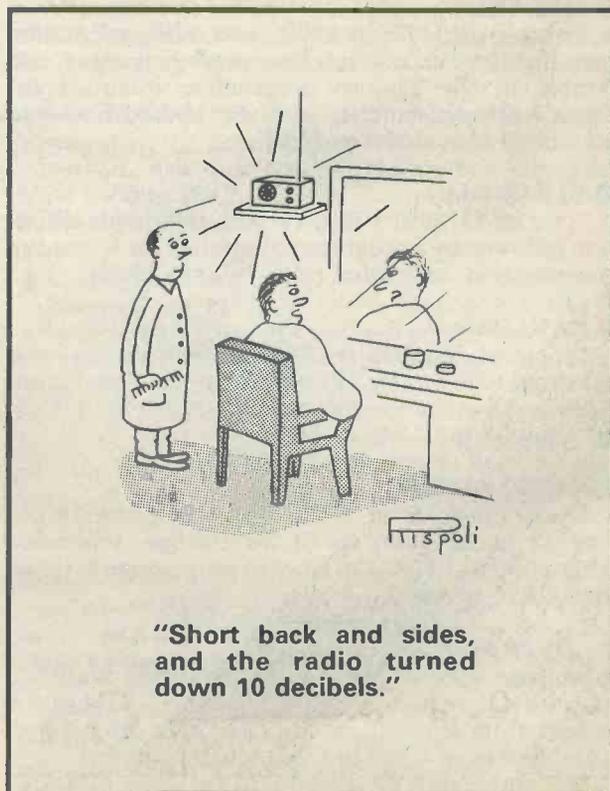


NEXT MONTH

The beginning of the
WORLD
 is nigh...

RADIO & ELECTRONICS
 CONSTRUCTOR
 metamorphoses to reappear as

ERADIO &
 ELECTRONICS
 WORLD

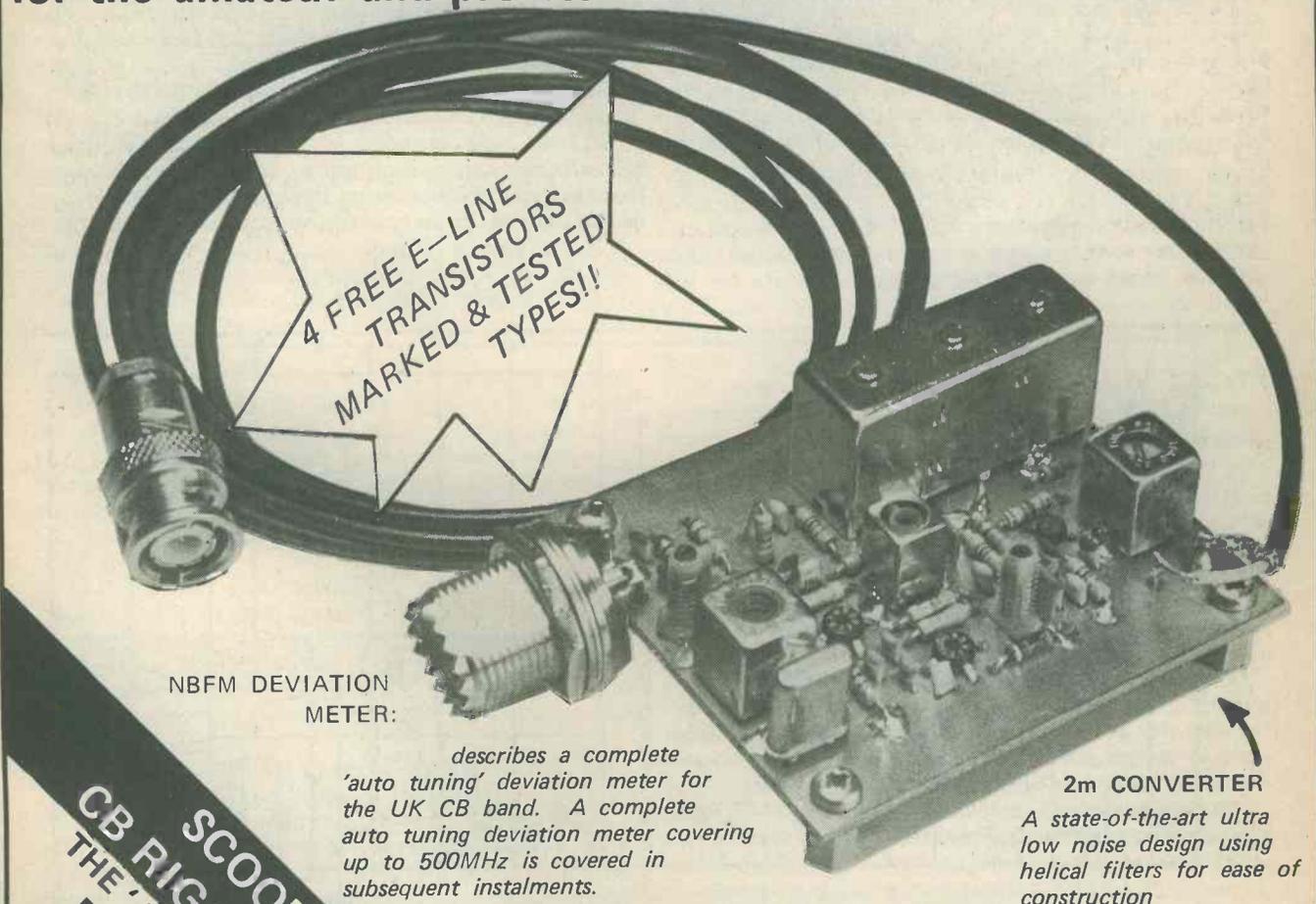The most feature-packed, up-to-date electronics magazine for the amateur and professional enthusiast. Issue 1 includes...



4 FREE E-LINE
 TRANSISTORS
 MARKED & TESTED
 TYPES!!

NBFM DEVIATION
 METER:

describes a complete 'auto tuning' deviation meter for the UK CB band. A complete auto tuning deviation meter covering up to 500MHz is covered in subsequent instalments.

2m CONVERTER

A state-of-the-art ultra low noise design using helical filters for ease of construction

AM/FM portable, 60kHz MSF receiver, loudspeaker protector, IC2E reviewed, 50 circuits for the free Ferranti E-Lines, news, comment - and plenty more. Order your copy now to avoid disappointment we are only printing 60,000 !!

SCOOPI!
CB RIGALISER
THE 'NAUGHTY CB'
DETECTOR IS
THE
DESIGNED BY
DESIGNER

On Sale 3rd September

MW AND LW SUPERHET RADIO

John Baker

This article describes a relatively simple MW and LW superhet receiver which is completely self-contained, having an internal ferrite aerial, battery supply, and loudspeaker. A maximum output power of about 300mW is available, and the use of an integrated circuit in the audio stages provides a high quality output despite the simplicity of the circuitry. The only other active devices used in the unit are three inexpensive and readily available transistors.

As the unit is a superhet design, once completed it does need to be accurately aligned in order to produce good results. However, this particular set is quite easy to align and no test equipment is required when adjusting the finished receiver. This ease of alignment is aided by the use of mechanical filters in the IF stages. These filters are pre-aligned and require no adjustment; in fact there is no way of adjusting their operating frequency.

THE CIRCUIT

Fig. 1 shows the complete circuit diagram of the receiver. There are two sets of coils on the ferrite rod; L1 and L2 are the LW tuned and coupling windings respectively, while L3 and L4 perform the same functions on the MW band. S1(a) selects the appropriate tuned winding for the selected wave band and couples it to the tuning capacitor, VC1 is an alignment trimmer. The LW winding requires a small amount of additional tuning capacitance, and this is provided by C3. There is no need to switch the two coupling windings, and these are simply wired in series so that the outputs from both coils are coupled into the input of the mixer by DC blocking capacitor C4.

TR1 is used in what is virtually the standard mixer/oscillator configuration, the only departure from normal practice being the use of a resistor (R3) as the load at the output of the mixer. Normally the


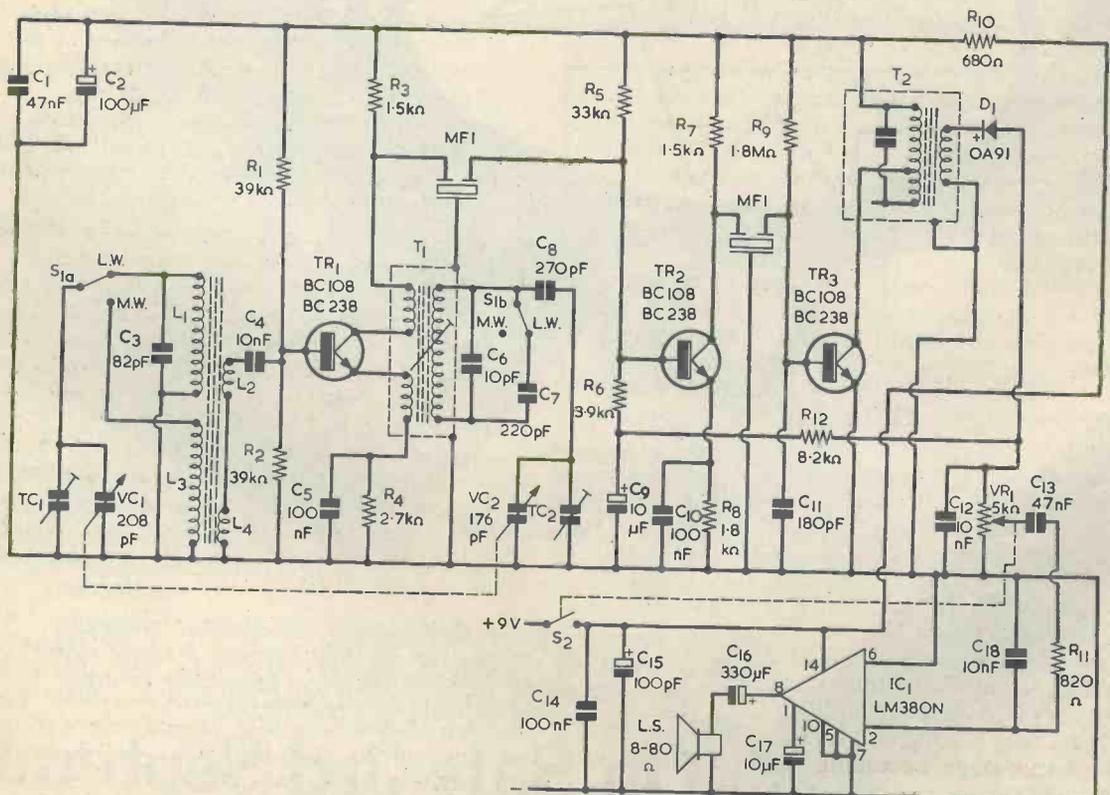


Fig. 1. The complete circuit diagram of MW/LW superhet radio.

External view of LW and MW superhet.

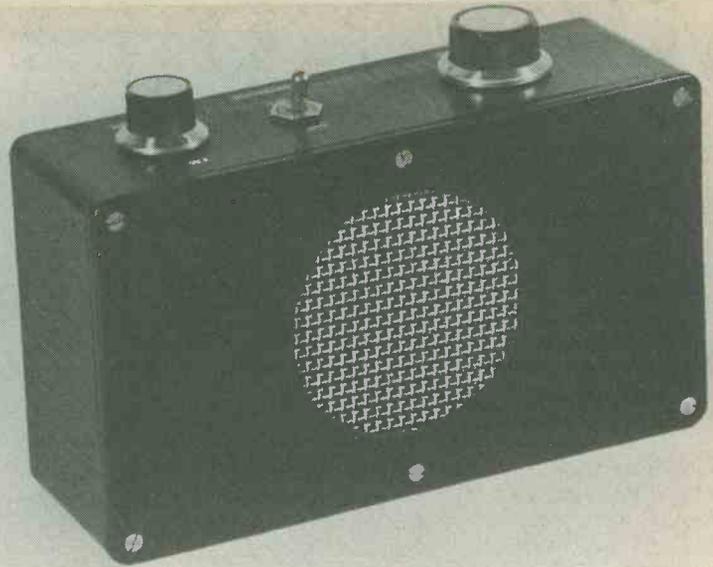

primary of the first IF transformer would be used here, but this is not possible in this case as mechanical filters are used to provide the interstage coupling, and so a resistive load has to be used.

R1 and R2 are the bias resistors for TR1, and R4 plus C5 are the emitter bias resistor and bypass capacitor. T1 is the oscillator transformer, and this produces oscillation by supplying positive feedback between the collector and emitter of TR1 (which is used in the common base mode as far as the oscillator circuit is concerned). The frequency of oscillation is determined by the resonant frequency of the tuned winding of T1. This must always be 455kHz higher than the input frequency in order to produce the required 455kHz IF output signal.

The non-earthly end of the tuned winding is coupled to the oscillator tuning capacitor, VC2, via padder capacitor C8. A small amount of fixed capacitance is required across the tuned winding of T1, and this is provided by C6. Together these two capacitors ensure correct tracking between the RF and oscillator circuits on the MW band provided the unit is aligned properly.

A lower and more restricted range of oscillator frequencies is needed for LW operation, and this is accomplished by C7 shunting the oscillator tuning capacitance when S1(b) is in the LW position.

The two tuning capacitors are ganged, and note that alignment trimmers TC1 and TC2 are also part of this component.

The output from the mixer is coupled by mechanical filter MF1 to the input of the first IF amplifier stage. This is a high gain common emitter stage which is biased by the potential divider chain which is comprised of R5, R6, R12, and VR1. R8 and C10 are the emitter bias resistor and emitter bypass capacitor. R7 is the collector load for TR2.

MF2 couples the output from TR2 collector to the input of the second IF amplifier stage. This is another high gain common emitter amplifier and it uses TR3. R9 provides base biasing and C11 is needed in order to prevent this stage becoming unstable. T2 is an ordinary IF transformer and its primary winding forms the collector load for TR3. Mechanical and ceramic filters tend to have out of band responses

which can result in a lot of strong spurious signals reaching the detector unless precautions against this are taken. The normal precaution is to use an ordinary IF transformer (which is free from such responses) at some point in the IF circuitry, and this is the reason T2 is used at the IF output, rather than a third mechanical filter or an untuned coupling.

Detector diode D1 is fed with the IF output signal from T2 secondary. VR1 forms the load for D1, and C12 filters out the RF half cycles to leave the required audio signal. When a strong signal is received there will be a large negative DC bias produced across VR1, and this will result in a reduction in the bias voltage fed to TR2. This reduces the operating current of TR2 with a consequent reduction in its gain. This gives the circuit a simple form of A.G.C. (Automatic Gain Control) with the gain of the unit being reduced on strong signals. This gives a more consistent audio output level, combats fading to a certain degree, and makes the receiver less susceptible to overloading on very strong signals.

An LM380N IC is used as the basis for the audio amplifier. The output from the volume control, VR1, is fed to the non-inverting input of IC1 by way of a simple RF filter which consists of R11 and C18. It is essential that no significant RF signal should be allowed to enter the audio stages as this would almost certainly result in instability. C13 provides DC blocking at the input and C16 provides the same function at the output of the device. The voltage gain of the LM380N is preset at 34dB (50 times) by an internal negative feedback loop. It is possible to raise or lower the gain of the device using a discreet feedback circuit, but this is not necessary in this case as the preset voltage gain is just about right anyway.

The circuit does not seem to need extensive supply decoupling despite the fact that there is a high overall level of gain, and the decoupling provided by C14, C15, C17, R10, C1 and C2 is more than adequate. S2 is the on/off switch and is ganged with VR1. The quiescent current consumption of the circuit is approximately 8mA, but the LM380N has a class B output stage and the supply current rises to several times this level at high output volumes.

COMPONENTS

Resistors

(All miniature 1/3, 1/4, or 1/8 watt 5% tolerance)

R1	39k
R2	39k
R3	1.5k
R4	2.7k
R5	33k
R6	3.9k
R7	1.5k
R8	1.8k
R9	1.8Meg.
R10	680ohms
R11	820ohms
R12	8.2k
VR1	5k log carbon with switch (S2) e.g. ALPS UMBR

Capacitors

C1	47nF type C280/Mylar
C2	100mfd 10vw
C3	82pF ceramic
C4	10nF ceramic, etc.
C5	100nF type C280
C6	10pF polystyrene
C7	220pF ceramic
C8	270pF ceramic
C9	10mfd 10vw
C10	100nF type C280
C11	180pF ceramic
C12	10nF type C280/Mylar
C13	47nF type C280/Mylar
C14	100nF type C280/Mylar
C15	100mfd 10vw
C16	330mfd 10vw
C17	10mfd 10vw
C18	10nF type C280/Mylar
VC1/2	208pF plus 176pF air spaced with trimmers (Jackson type 0)

Semiconductors

TR1	BC108/BC238
TR2	BC108/BC238
TR3	BC108/BC238
IC1	LM380N
D1	OA91

Inductors

L1/L2	MW antenna coil type MWC2
L3/4	LW antenna coil type LWC1
T1	MW oscillator coil type YMRS16726/302
T2	455kHz IFT type YHCS11100AC2
MF1	Mechanical filter type CFM2 B.
MF2	Mechanical filter type CFM2 B.

(All above are available from Ambit International)

Switches

S1	D.P.D.T. toggle type.
S2	Part of VR1

Loudspeaker

LS1	About 3in. diameter, 8 to 80 ohm impedance (see text)
-----	---

Miscellaneous

Plastic case measuring approx. 185 x 109 x 60mm (or similar non-metallic housing).
Plain 0.15in. matrix board and 0.1in. matrix stripboard.
Two control knobs.
140mm x 9.5mm F14 grade ferrite rod (Ambit type FRA).
Two mounting clips for ferrite aerial (Ambit type FRPC).
PP3 battery and connector to suit.
Speaker fret, connecting wire, etc.

CONSTRUCTION

A plastic box having approximate outside dimensions of 185 x 109 x 60mm is used to house the prototype receiver. Any non-metallic case of about the same size should also be suitable, but a metal case cannot be used as it would screen the ferrite aerial and prevent signals from being picked up.


The case has a removable lid which in this application becomes the front panel. A cutout for the speaker is cut in the centre of this panel using a fretsaw or a miniature round file, and then a piece of speaker fret or speaker material is glued in position over the rear of the cutout. The loudspeaker is then carefully glued in place onto the speaker material. Only a small amount of adhesive should be applied to the front rim of the speaker, and care must be taken not to get any of the adhesive onto the diaphragm of the speaker. A good quality adhesive such as an epoxy type must be used.

The speaker can be of any type having a diameter of up to about 89mm (3.5in.) and an impedance in the range 8 to 80 ohms. Ideally the speaker should have an impedance of about 15 to 25 ohms, but such

units are not very widely available. In practice an 8ohm speaker seems to give good results, although at the expense of slightly reduced battery life. Higher impedance types give a lower current consumption and longer battery life due to the reduced maximum output power (only about 75mW into an 80ohm speaker). Speakers having an impedance of less than 8ohms should not be used.

The three controls are mounted on the top panel of the case (one of the 185 x 60mm sides). VR1 and S1 are mounted on the lefthand side of the case and VC1/2 is mounted on the right hand side. Assuming VR1 and S1 are standard components they will require 10mm (3.8in.) and 12.5mm (0.5in.) diameter mounting holes respectively.

The tuning capacitor has a rather unusual mounting arrangement which requires a central hole of about 10mm in diameter for the spindle of the component, and three 4BA clearance mounting holes for the short 4BA countersunk mounting screws. These fit into three threaded holes in the front of the tuning capacitor. One way of locating the positions of the three smaller mounting holes is to make up a paper template with the aid of the component itself, but

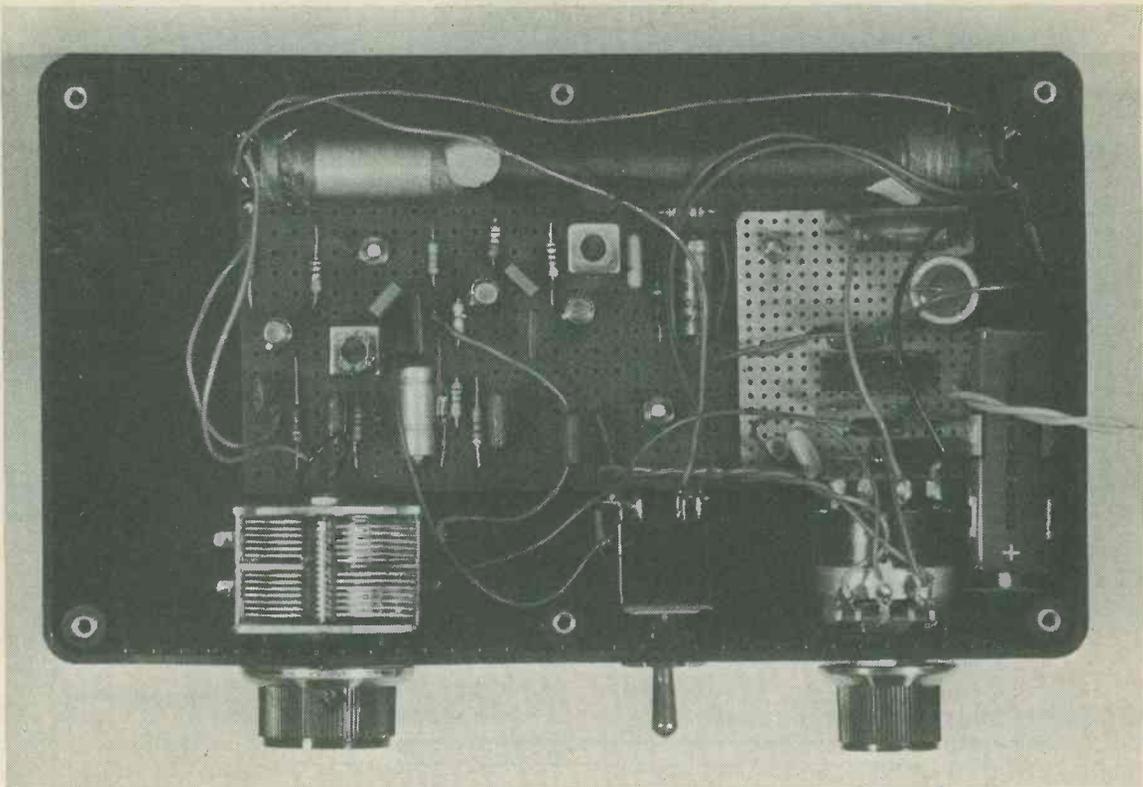

Internal layout of radio.

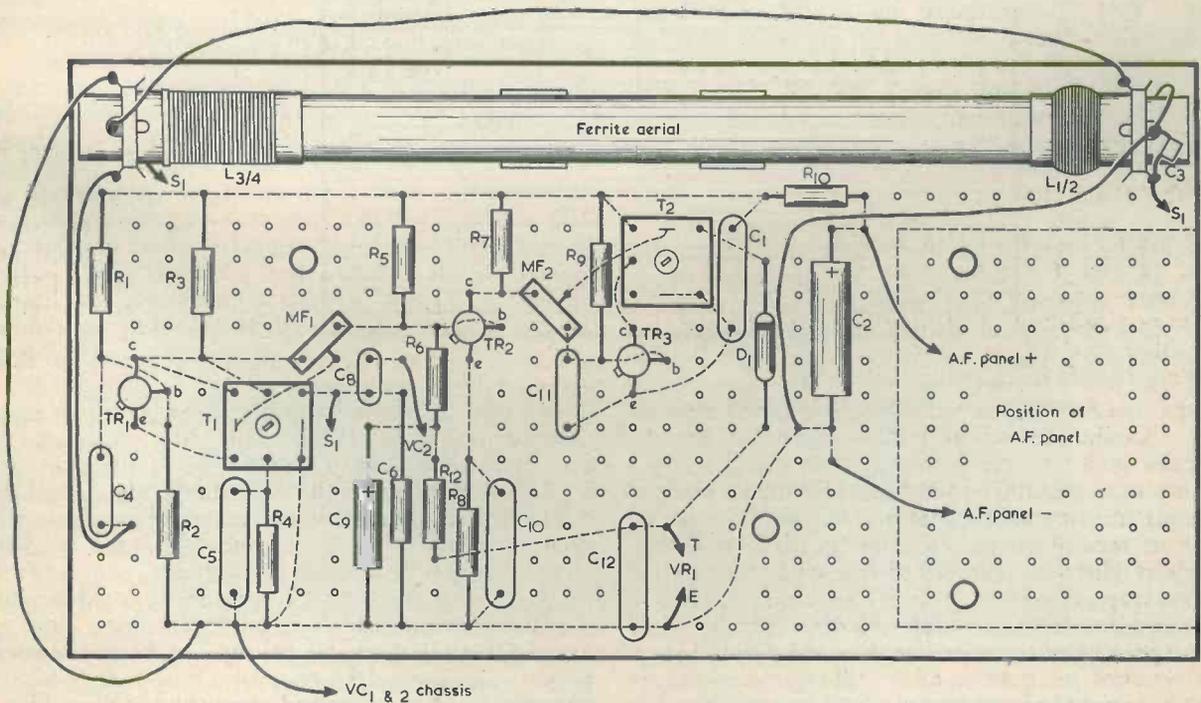


Fig. 2. Details of the plain 0.15in. matrix component panel.

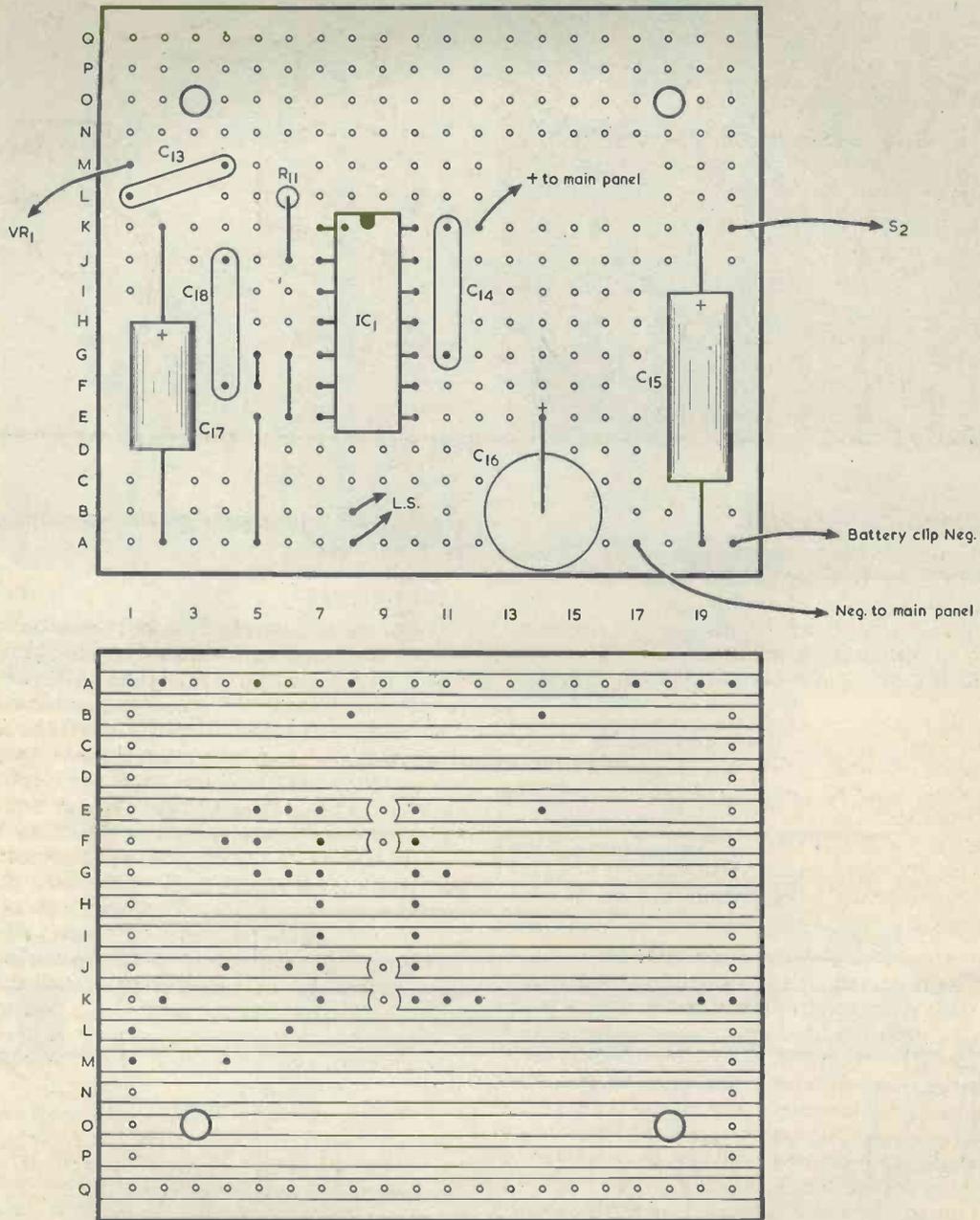



Fig. 3. Details of 0.1in. stripboard panel on which the AF amplifier is assembled.

other methods have been described in previous articles in this magazine. The three 4BA clearance holes are drilled using a No. 24 or similar twist drill.

It is important that suitably short mounting screws are used, or that washers are placed over them, bet-

ween the front of the tuning capacitor and the case, so that their penetration is limited to an acceptable level. If these screws fit right through the front plate of the tuning capacitor it is likely that the component will be jammed, and it could be irreparably damaged.

Fig. 4. The wiring to VR1, S1 and S2.

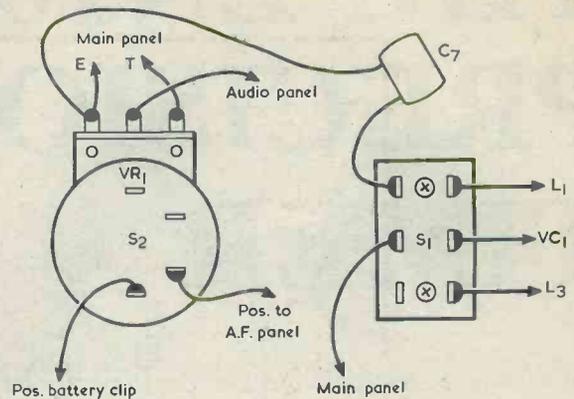

MAIN COMPONENT PANEL

Most of the circuitry is assembled on a plain 0.15in. matrix board which has 33 x 17 holes, and this is cut down from a standard 127 x 95mm (5 x 3.75in. and 33 x 24 holes) board using a hacksaw. The audio amplifier is constructed on 0.1in. strip-board, and this sub-assembly is bolted to the main panel.

Details of the main panel are given in Fig. 2. The ferrite aerial is mounted on two plastic clips which are in turn mounted on the panel using short 6BA bolts and nuts. In order to mount T1 and T2 on the board it is necessary to slightly enlarge four of the holes with a drill bit of about 1.5 to 2mm in diameter in order that they will accommodate the mounting lugs of these two components.

Construction of this type of component panel is quite straightforward with the component being mounted in the positions indicated in the diagram, the leadout wire then bent flat against the underside of the panel, and then these leads are directly connected to one another. In instances where the leadout wires are inadequate to complete the wiring, link wires made from 22 s.w.g. (approx.) tinned copper wire are used. Next the connections between the component panel and the ferrite aerial are completed, and V3, which is mounted directly onto L1, is soldered into position.

The AF board has 17 copper strips by 20 holes and uses the layout shown in Fig. 3. First a board of the required size is cut out, then the two 6BA clearance mounting holes are drilled using a No. 31 or equivalent twist drill, and next the four breaks in the copper strips are made. The components and link wires can then be soldered into place.

The mounting holes for the AF panel are then drilled in the main panel, and the two mounting holes for the main panel itself can also be drilled at this stage. Also, the two mounting holes for this whole assembly can be drilled in the case. However, before the two panels are finally bolted together and fitted in the case, the remaining wiring must be completed including the wiring to the controls. Fig. 4 illustrates the wiring to S1, S2 and VR1. There is plenty of space for the PP3 battery, and on the prototype this is held

in position by some strategically placed pieces of Bostik Blue Tack.

ALIGNMENT

With the set switched on and the waveband switch in the 'MW' position, it should be possible to receive a few stations, and by sliding the MW coil along the ferrite rod it should be possible to peak each station. The coverage of the set will probably be found to be rather high in frequency with the low frequency end of the band not covered, and the high frequency coverage extending into the SW spectrum. This can be corrected by screwing the core of T1 inwards.

When the MW coverage is approximately correct, with the set switched to the LW band it should be possible to receive one or two stations and to peak them by adjusting the position of the LW coil on the ferrite rod. It should be possible to find a setting for the core of T1 that causes the BBC 200kHz LW transmission to be received with the tuning capacitor at roughly a central setting, and which gives full MW coverage with S1 set back to the MW position. This is the correct setting.

LW alignment is very simple, and it is merely necessary to tune to the BBC 200kHz transmission and then adjust the position of the LW coil on the ferrite rod for maximum signal strength. The coil is then glued in this position. A multimeter set to a low volts range and connected across R8 (negative test lead connected to the negative rail) will provide a visual indication of signal strength. Maximum signal strength corresponds to minimum voltage.

To align the set on the MW band first tune to a station at the low frequency end of the band (VC1/2 vanes almost fully meshed) and position the MW aerial coil on the ferrite rod for maximum signal strength. Then tune to a station at the high frequency end of the band and adjust TC1 for maximum signal strength. Next retune to the station at the low frequency end of the band and once again adjust the position of the MW coil on the rod for maximum signal strength. Repeat this procedure a few times until the set has good sensitivity over the entire MW band. The setting of TC2 is not important, provided it is not screwed down tightly, otherwise it may then be impossible to accurately align the receiver.

THE ZN1034 PRECISION IC TIMER

R. A. Penfold

Most simple electronic timer devices operate on the simple principle of a capacitor being charged via a resistor. Usually the timing period starts when the capacitor first begins to charge up, and ends when the voltage across the capacitor reaches a certain percentage of the supply rail potential. The popular NE555V timer IC is a good example of a timer of this general type, but virtually all timers featured in the amateur electronics magazines use the same basic arrangement.

While circuits of this sort have the advantage of being relatively simple and inexpensive, the main drawback is that even to obtain quite short times it is necessary to use fairly large timing component values. For example, when used in the monostable mode the NE555V IC has an output pulse length which is approximately equal to $1.1 CR$ (with C in farads and R in ohms, or more conveniently with C in mfd and R in Meg. ohms). Thus C and R values of say 10mfd and 1 Meg. ohm would produce an output pulse of approximately 11 seconds.

Therefore, even to obtain fairly short timing periods it is necessary to use an electrolytic capacitor in the timing network. The main drawback of this is that electrolytics tend to have comparatively high leakage currents (or low insulation resistances if viewed in this way) and even if a good quality capacitor is used it is not practical to obtain times of more than about 1 or 2 hours. Also, the repetitive timing accuracy may not be particularly good, especially in the long term. Similarly, the insulation resistance of an electrolytic capacitor usually varies signifi-

cantly with ambient temperature, and so temperature stability may be rather poor as well.

Using a low grade electrolytic in a timing application will almost certainly provide very poor results, if the circuit functions at all that is!

PRECISION TIMER


Where short pulses of very high precision are required, such as in digital frequency meters, the usual method of deriving them is by employing a high stability crystal oscillator and a digital frequency divider chain. It is quite feasible to use the same method to obtain long output pulses, but for virtually all practical purposes the accuracy yielded by a crystal oscillator is not required, and a good quality C R oscillator can be used instead.

This system has the advantage of being able to produce quite long timing periods using a non-electrolytic timing capacitor, or extremely long timings by using an electrolytic component.



Obviously a timer of this type could be constructed using a separate oscillator and logic circuitry, but this is not necessary since a special precision timer IC is available. This is the Ferranti ZN1034, this is capable of producing an output pulse of less than one second to more than one month! It will provide much better accuracy than simple timer circuits, although the ZN1034 admittedly cost considerably more than the NE555V and similar devices.

Fig.1 shows in block diagram form the internal arrangement of the ZN1034 and it also shows the pin

Fig. 1. Block diagram showing the internal arrangement of the ZN1034E IC

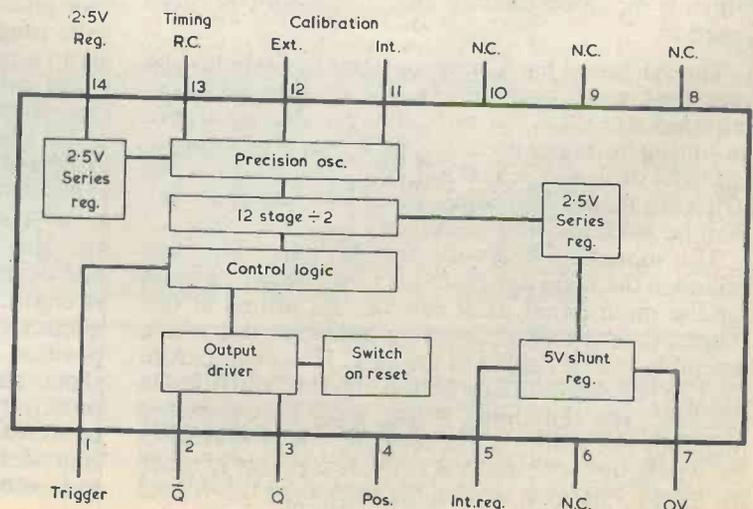

The front of the unit.

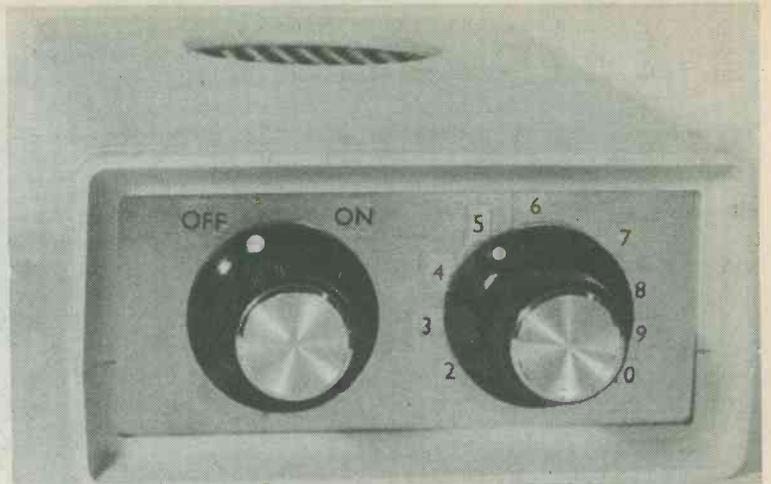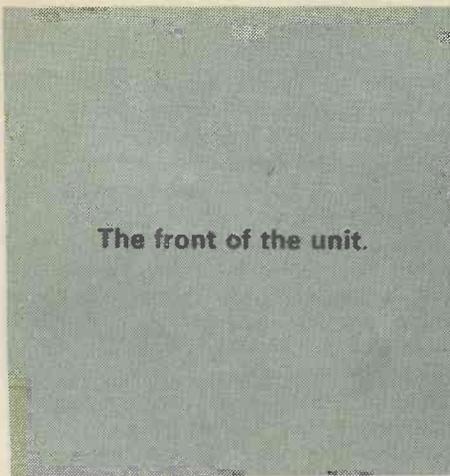

function of the ZN1034E, which is the 14 pin DIL plastic package version of the device, and is the version normally supplied by retail sources. As will be seen from Fig.1, the device contains a highly stable oscillator, 12 stage binary divider, control circuitry, and output driver circuitry. The unit can be powered from a stabilised 5 volt supply, or from a nominal supply potential of 6 volts or more using a series resistor and the internal 5 volt shunt regulator.

A practical circuit using the ZN1034 can be very simple, the basic method of using the device is shown in Fig.2.

CT and RT are the frequency determining components of the oscillator, but the frequency of oscillation is also affected by the resistance between pins 11 and 12 of the IC. In many applications these two pins can simply be connected together, and the oscillator then has only a 100k internal Cal. resistor connected into circuit. This gives optimum temperature stability, and the length of the output pulse is approximately equal to $2736 CT RT$.

If RT is to be a series of close tolerance resistors which are calculated to give a series of preset times, or RT is to be a potentiometer so that the length of the output pulse can be varied between certain limits, the ability to trim the output pulse using a separate preset resistor is almost essential. It then becomes necessary to connect a preset between pins 11 and 12. With an external Cal. resistance of 200k (300k total Cal. resistance) the output pulse is approximately equal to $7500 RT CT$. The total Cal. resistance should not be much more than about 300k.

RT should not be less than 5k or more than about 10 Meg. CT should not be less than 3.3nF, and there is no definite upper limit to the value of this component. This is determined by the required accuracy and the leakage current of the capacitor which is used.

RL is the load resistor for the internal 5 volt shunt regulator, and this must limit the supply current to 50mA or less. On the other hand, it must provide a current of 7mA for the ZN1034 plus the maximum output current that will be required (the device can provide an output current of up to 25mA). CD is merely a supply decoupling capacitor.

If the circuit is supplied from a stabilised 5 volt supply, this is applied to pin 4 and pin 5 is left unconnected.

The output pulse is started by taking 1 to the negative supply rail potential, or a voltage of no more than 1 volt. The circuit is actually a non-retriggerable monostable multivibrator, and so either taking pin 1

low briefly or continuously will produce an output pulse of the correct length, unlike some timer circuits where the trigger terminal must be returned to the high state before the end of the output pulse, or the pulse is extended until the trigger terminal is returned to the high state.

The circuit has both Q and not-Q outputs. The Q output is normally low and produces a positive output pulse and the not-Q output is normally high and produces a negative output pulse.

In an application where it is necessary for the circuit to operate an alarm of some kind for a short time at regular intervals, this can be achieved by connecting the Q output to the trigger terminal via an R - C network. (Fig.3). The length of time between the output pulses is approximately $0.6 C R$.

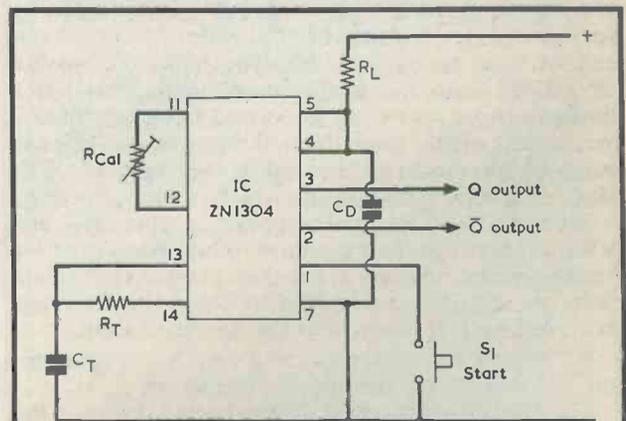


Fig. 2. Basic ZN1034E Timer circuit.


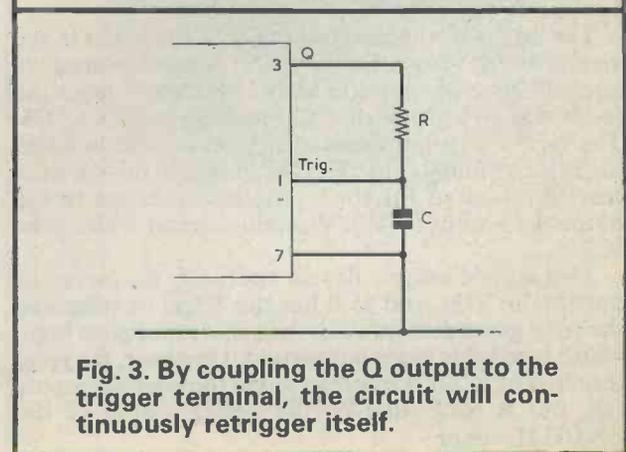


Fig. 3. By coupling the Q output to the trigger terminal, the circuit will continuously retrigger itself.

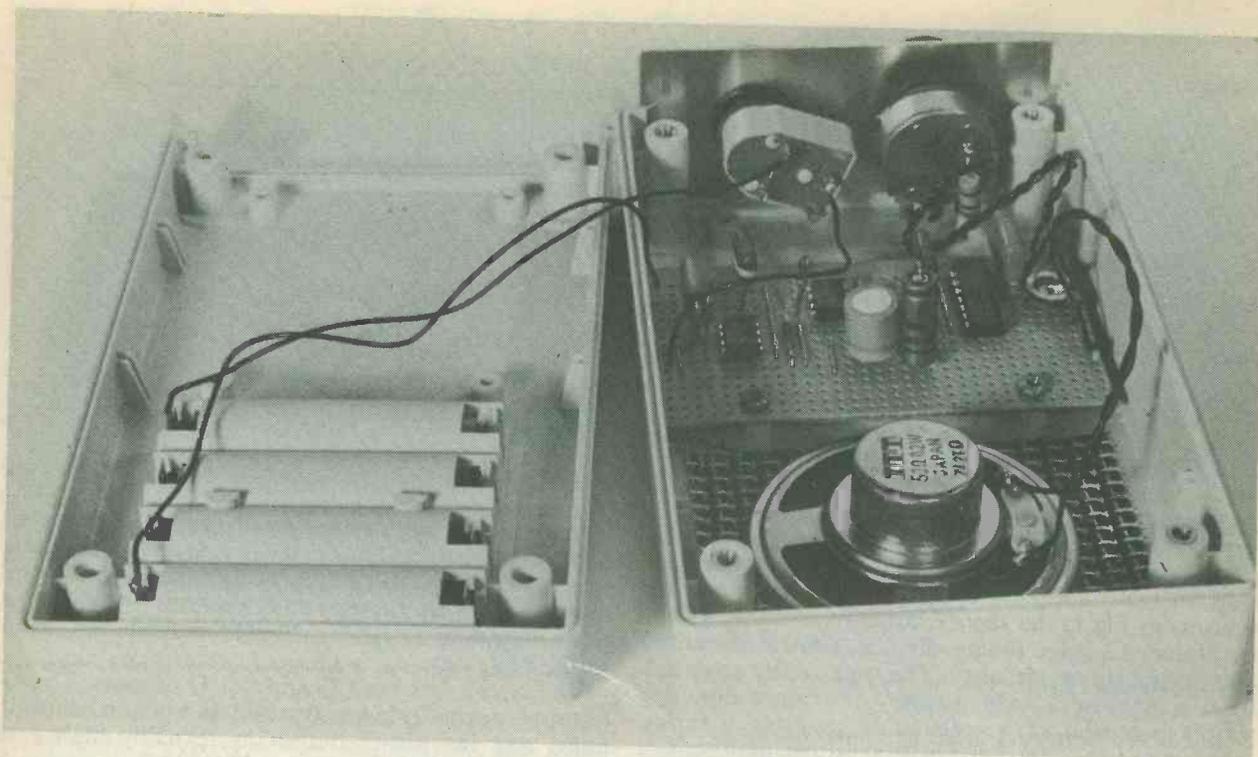

Layout showing built-in battery box.

SIMPLE TIMER UNIT

Simple timer circuits which provide an audio alarm after some preset length of time has elapsed can be very useful in a number of applications, and the circuit of a simple unit of this type which employs a ZN1034E timer IC is shown in Fig.4. This has a timing period which can be varied from less than 2 minutes to a little more than 10 minutes, but this can easily be altered to suit individual requirements. The alarm is a pulsed audio tone which is very effective.

VR1, R2, and C1 are the timing components, and VR1 enables the timing period to be varied over the limits specified above. R1 is the external calibration resistor, and this is adjusted to bring the coverage provided by VR1 to within the specified limits.

R3 is the load resistor for the 5 volt shunt regulator, and C2 is a supply decoupling capacitor.

The trigger input (pin 1) is connected direct to the negative supply rail so that the circuit is triggered the moment on/off switch S1 is closed, and power is applied to the unit.

The audio alarm used two NE55V timer ICs in the astable mode. One of these (IC3) is used to produce an audio tone of approximately 1kHz which feeds the loudspeaker by way of DC blocking capacitor C5. The NE555V astable circuit will only oscillate when the reset terminal (pin 4) is taken high. In this case the reset terminal of the tone generator is taken to the output of another NE55V astable circuit which uses IC2.

This second astable has an operating frequency of only about 2Hz, and so it has the effect of switching the tone generator on each time its output goes high, which is roughly twice per second. However, the reset terminal of IC2 is not connected to the positive supply rail, but is controlled by the not-Q output of the ZN1034E timer.

The not-Q output will go low as soon as the supply is connected to the circuit, and it will remain in this state until the end of the timing period. Thus IC2 will not oscillate until the end of the timing period and its output will go low until it does start to oscillate. This results in the tone generator also being disabled until IC2 is switched on.

Once the alarm does start to sound, it will continue until the unit is switched off using S1. The circuit is then ready to commence operation from the beginning once again when S1 is returned to the 'on' position.

The circuit is powered from a 6 volt battery supply which comprises four HP7 cells connected in series. The quiescent current consumption is about 25mA, and this increases slightly when the alarm operates.

CONSTRUCTION

The prototype timer is housed in a Verocase type 65-2067G which has approximate outside dimensions of 155 x 92 x 33mm, and has an integral battery compartment for the four HP7 cells. Any similar case of about the same size should also be suitable, but a plastic battery holder for the HP7 cells and a matching battery clip (PP3 type) will then be required.

S1 and VR1 are mounted side by side on the front panel with S1 on the left, and both these components require a 10mm diameter mounting hole. A cutout of about 50mm in diameter is made in the top section of the case above the battery compartment, and a piece of speaker fret or cloth is glued in place behind the cutout. The speaker is then glued in place on the speaker material, and only a small amount of high quality adhesive must be used here, as otherwise adhesive could be smeared over the diaphragm of the speaker. If this should be allowed to happen it could easily impede the operation of the speaker.

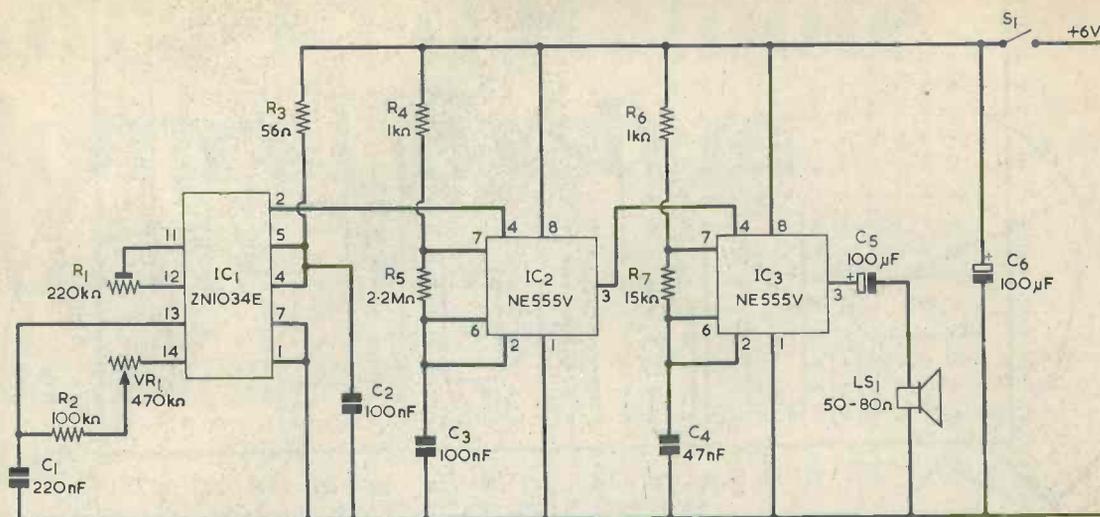


Fig. 4. The circuit diagram of a simple timer using the ZN1034E Timer IC.

COMPONENTS

Resistors

All 1/8 or 1/3 watt 5 or 10% except R1.
 R1 220k sub miniature (0.1 watt) horizontal preset.
 R2 100k
 R3 56 ohms
 R4 1k
 R5 2.2 Meg.
 R6 1k
 R7 15k
 VR1 470k 1in. carbon

Capacitors

C1 220nF type C280
 C2 100nF type C280
 C3 100nF type C280
 C4 47nF type C280
 C5 100mfd. 10vw.
 C6 100mfd. 10vw.

Semiconductors

IC1 ZN1034E
 IC2 NE555V or equivalent
 IC3 NE555V or equivalent

Switch


S1 Rotary on/off switch

Loudspeaker

LS1 50 to 80 ohm impedance, about 50-66mm in diameter.

Miscellaneous

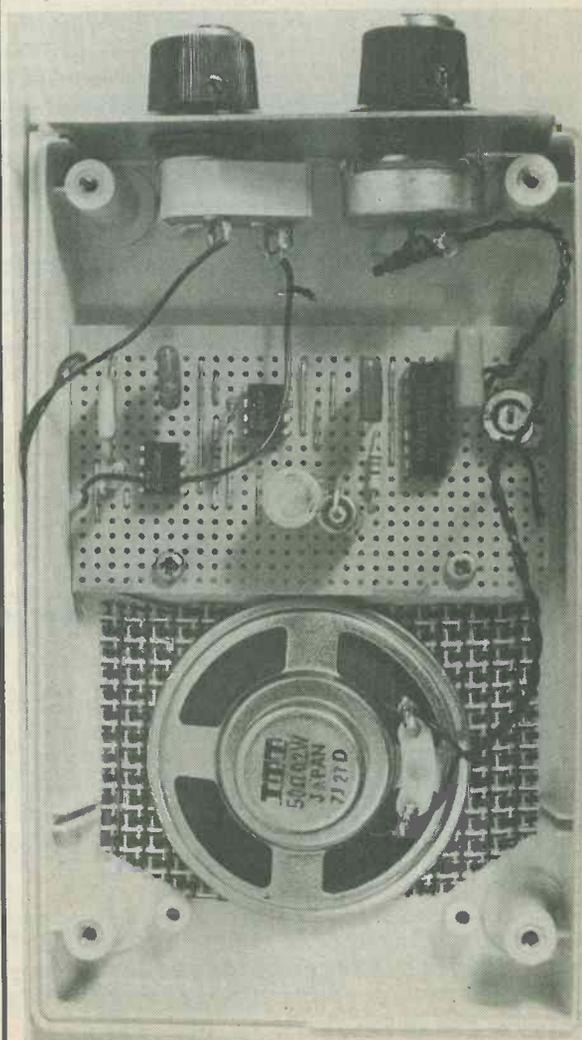Verocase type 65-2067G or similar and plastic battery holder for four HP7 size cells.
 Two control knobs
 Four HP7 cells
 0.1in. matrix Veroboard panel.
 Speaker fret or cloth, wire, solder, etc.



Internal layout of the unit.

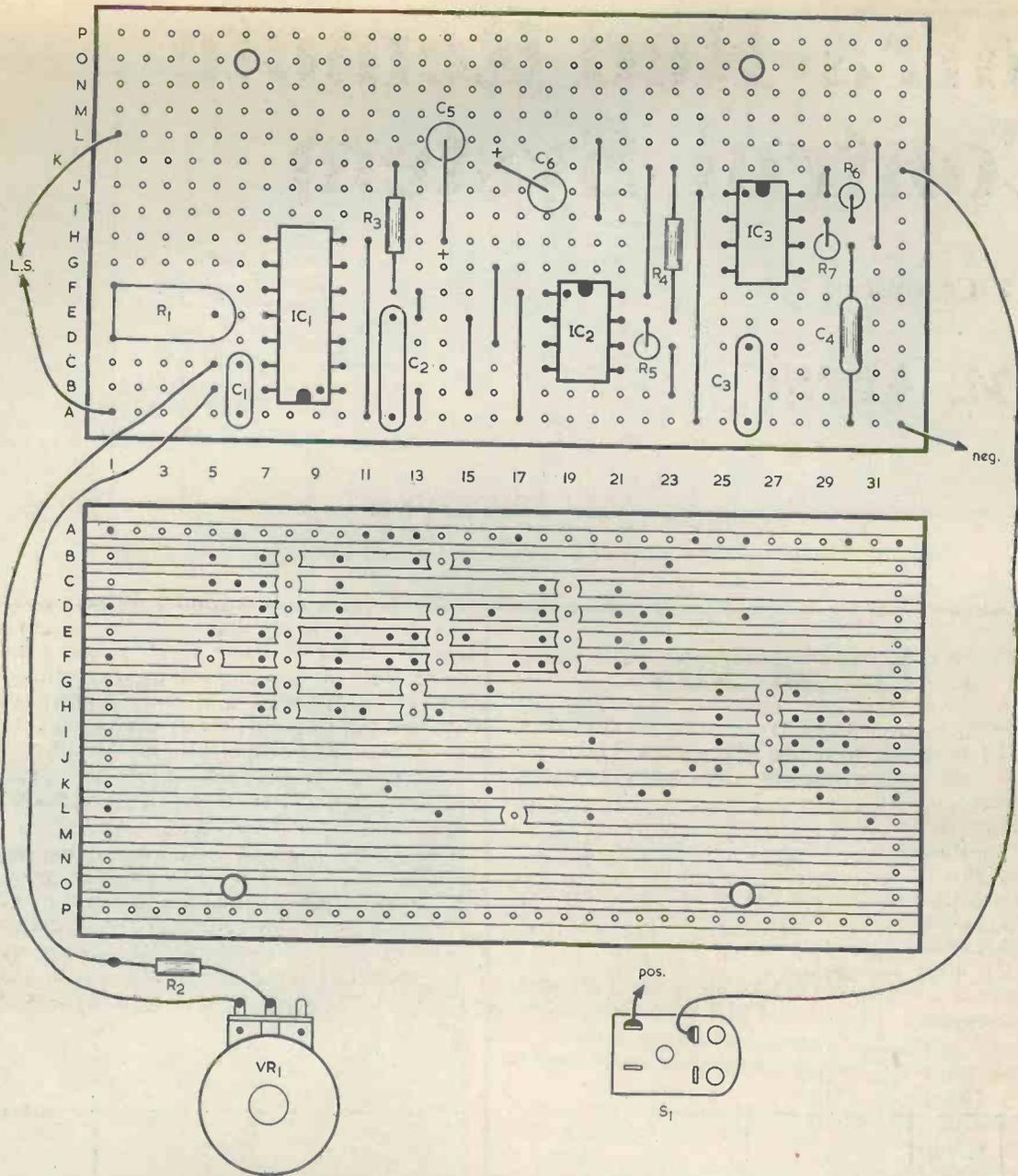


Fig. 5. The wiring of the Timer and details of the component panel.

With the exception of R2, which is mounted on VR1, the other components are assembled on a 0.1in matrix veroboard panel which has 32 holes by 16 copper strips. Details of the component panel and wiring are given in Fig.5. After the completed panel has been wired up to the rest of the unit it is mounted on the two mounting pillars just in front of the speaker using two short 6BA self tapping screws. The case has p.c.b. mounting slots and some of these may well be found to obstruct the component panel. This can be remedied by filing down the offending mounting rails, and this is not difficult as they are made of a reasonably soft plastic.

ADJUSTMENT

With the slider of R1 set at about the centre of its track the range of the unit will probably extend from less than 2 minutes to a little over 10 minutes, but

some adjustment of R1 may be needed in order to achieve this coverage. Adjusting R1 in a clockwise direction has the effect of shortening the timings, and adjusting it in an anti-clockwise direction has the opposite effect.

A time scale should be marked around the control knob of VR1, and this can either be calibrated at regular intervals, or just the times which will be required by the user. In either case, finding the calibration points is really a matter of trial and error, and there is no easy short cut here.

If suitable test gear to accurately measure the length of each oscillator cycle is available, the output pulse length can be calculated by multiplying this figure by 4095. However, this may not be entirely reliable as loading by the frequency measuring apparatus could easily affect the frequency of the oscillator to a slight but significant degree. ■

Infra-Red Remote Control System

Part 2 (Conclusion)

I. M. Attrill

THE RECEIVER

The circuit diagram of the receiver is shown in Fig.4.

D1 is the infra-red detector diode, which has a built-in filter so that it is only sensitive to infra-red light. R1 forms the load resistor for D1, and the supply polarity is such that D1 is reverse biased. The pulses of infra-red from the transmitter, cause an increase in the leakage current of D1 which produces a series of negative pulses at the junction of D1 and R1, which are coupled to the amplifier via C2.

The amplifier is a two stage common emitter configuration, with capacitive coupling between the stages provided by C4. C2 and C4 have both been given quite low values so that they are inefficient at low frequencies, and the circuit has poor sensitivity at 100Hz. This is necessary because mains lighting emits a certain amount of infra-red, and this is modulated at

100Hz. If the unit had good sensitivity at 100Hz it would be quite likely that this signal would operate the unit, causing the load to be spuriously switched on and off. With the unit as it stands, no problems of this kind are experienced, and more sophisticated low frequency filtering was found unnecessary. C3 rolls off the high frequency response of the amplifier, and this is necessary to prevent instability. The circuit achieves a high mid-band gain of about 80dB., giving good sensitivity and operating range.

The Schmitt trigger circuit is based on operational amplifier IC1. R8 is used to bias the inverting (-) input to the same potential as appears at the collector of Tr2. R7 couples the voltage at Tr2's collector to the non-inverting (+) input of IC1. Under quiescent conditions the output of IC1 remains in a constant state, but in the presence of an input signal it operates


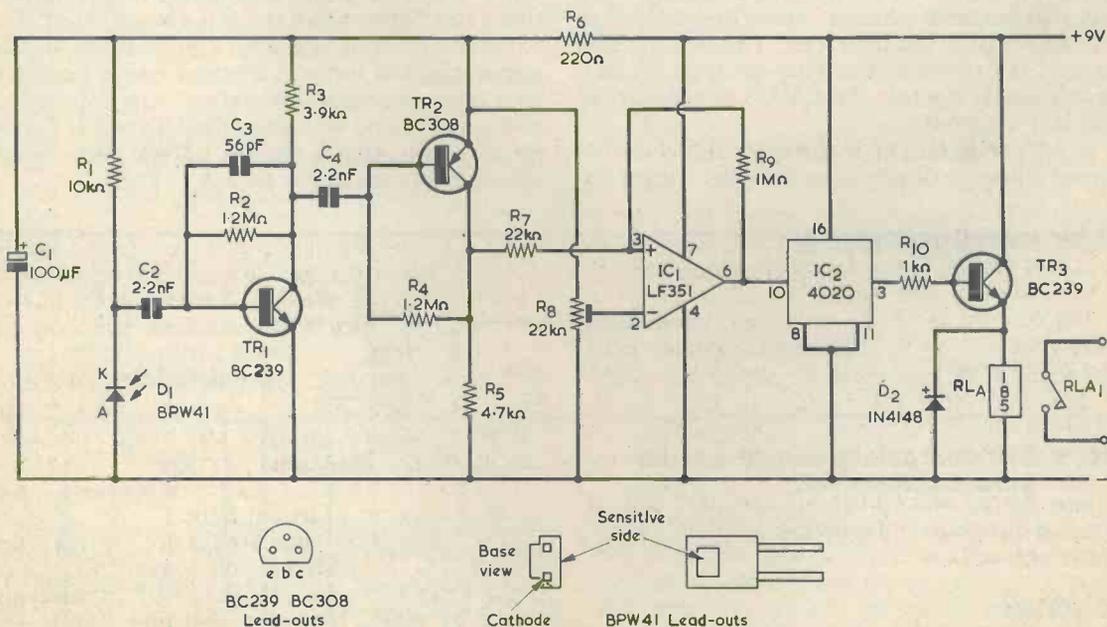


Fig. 4. The circuit diagram of the Infra-Red Receiver.

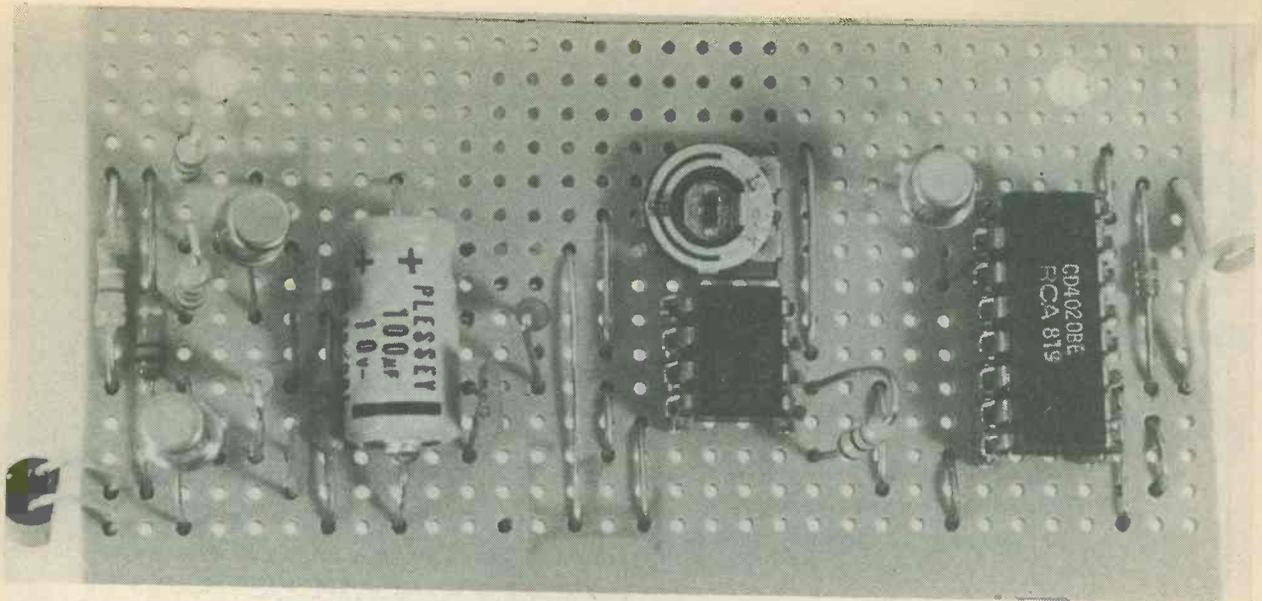

The receiver layout.

as a voltage comparator. When the voltage fed to the non-inverting input goes above that fed to the inverting input, the output of IC1 goes to the high state.

When the input signal causes Tr2's collector potential to go below the voltage fed to the inverting input, the output of IC1 goes low. Positive feedback is provided by R9, and this also introduces a small amount of hysteresis, which ensures that the output of IC1 triggers rapidly and reliably from one state to the other. For example, if the non-inverting input starts to go to a higher voltage than the inverting one, the output of IC1 starts to change from the high state to the low one.

Due to the coupling through R9, as the output swings more positive it takes the non-inverting input more positive as well.

This in turn sends the output more positive, and thus this regenerative process causes the output to almost instantly go to the high state. This ensures that the rise and fall times of the output signal are fast enough to reliably operate the CMOS divider circuit fed from IC1's output.


This is advantageous as it prevents noise on the input signal from spuriously operating the trigger circuit,


and ensures that under quiescent conditions the output of IC1 rests in a stable state.

The 14 stage divider IC is a CMOS 4020 device, with the output of the 14th stage used to drive the relay coil via the emitter follower stage, Tr3. The reset terminal of IC1 is connected to the negative supply rail, and serves no useful purpose in this application. D2 is the protective diode that is normally included across highly inductive loads in semiconductor circuits. This suppresses the high reverse voltage which is developed across the relay coil as it de-energises. The relay can be any type having a 6/12 volt coil with a resistance of about 185 ohms or more, provided it has contacts of adequate rating for the intended load.

The current consumption of the receiver is about 4mA. when the relay is switched off, and about ten times this figure when the relay is activated. The unit could be powered by a large 9 volt battery, but in most applications of the unit a mains power supply would be a more practical alternative. Any supply that can give a stable and well smoothed 9 volts at currents of up to about 40mA should be suitable. A suitable mains P.S.U. circuit is shown in Fig.5.

Fig. 5. Suitable power supply for the Infra-Red Receiver.

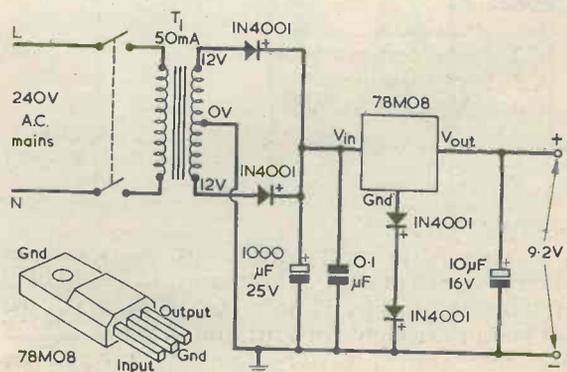

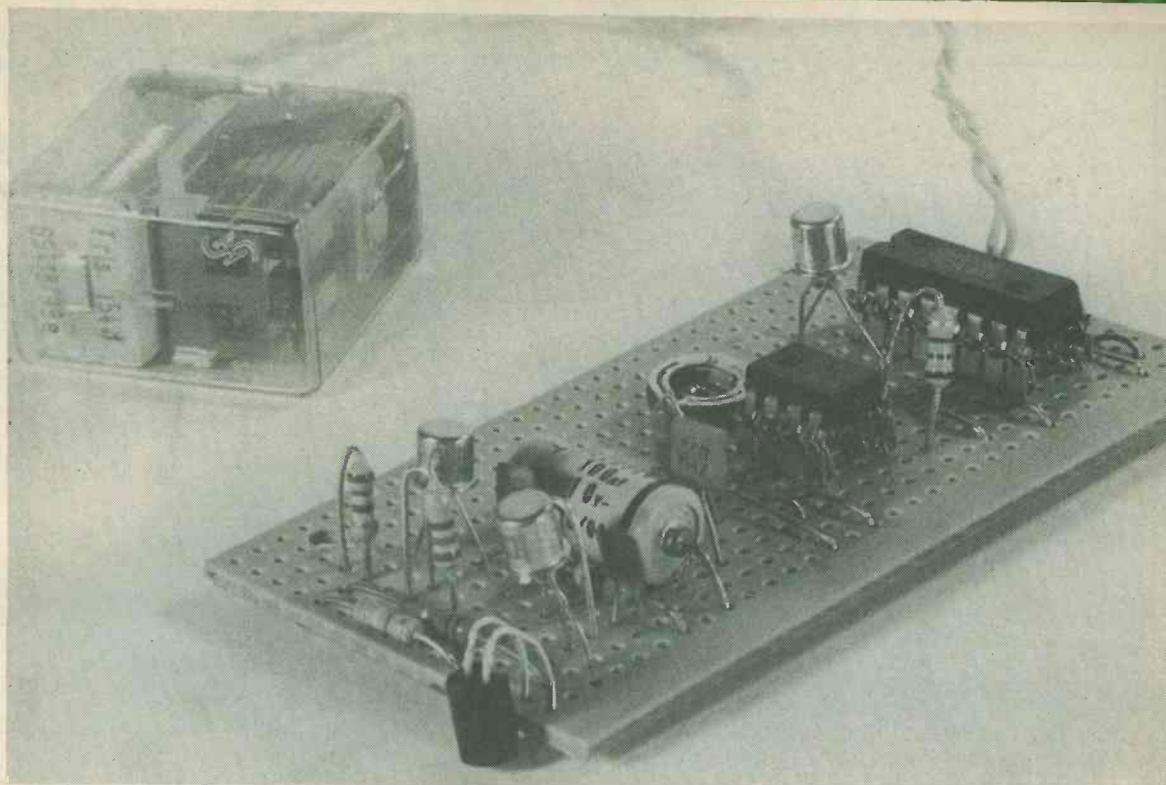

Inside of the receiver.

COMPONENTS

Receiver

Resistors

- 1/3 watt 5% (10% over 1M), except R8
- R1 10k
- R2 1.2M
- R3 3.9k
- R4 1.2M
- R5 4.7k
- R6 220 ohms
- R7 22k
- R8 22k 0.1 watt horizontal preset
- R9 1M

Capacitors

- C1 10 μ F 10V
- C2 2.2nF ceramic plate
- C3 56pf ceramic plate
- C4 2.2nf ceramic plate

Semi-conductors

- Tr1 BC239
- Tr2 BC309
- Tr3 BC239
- IC1 LF351
- IC2 4020
- D1 BPW41
- D2 1N4148

Relay

6/12 volt coil having a resistance of 185 ohms or more, at least one contact of appropriate type and adequate rating.

Miscellaneous

- 0.1in. matrix stripboard
- Wire, solder, etc.

CONSTRUCTION

A suitable 0.1 in. matrix stripboard layout for the receiver is shown in Fig.6. This requires a board having 15 copper strips by 32 holes. Construction of the board is quite straight forward, but IC2 is a CMOS device and normal CMOS handling precautions should be taken. The use of an IC socket is recommended.

The mechanical construction of the unit must be varied to suit individual requirements, and it can either be built as a self contained unit into which any item of equipment can be plugged, or it can be built into another project. In either case D1 must be mounted behind a hole in the front panel of the equipment so that the infra-red beam from the transmitter can reach it. The sensitive surface of D1 must

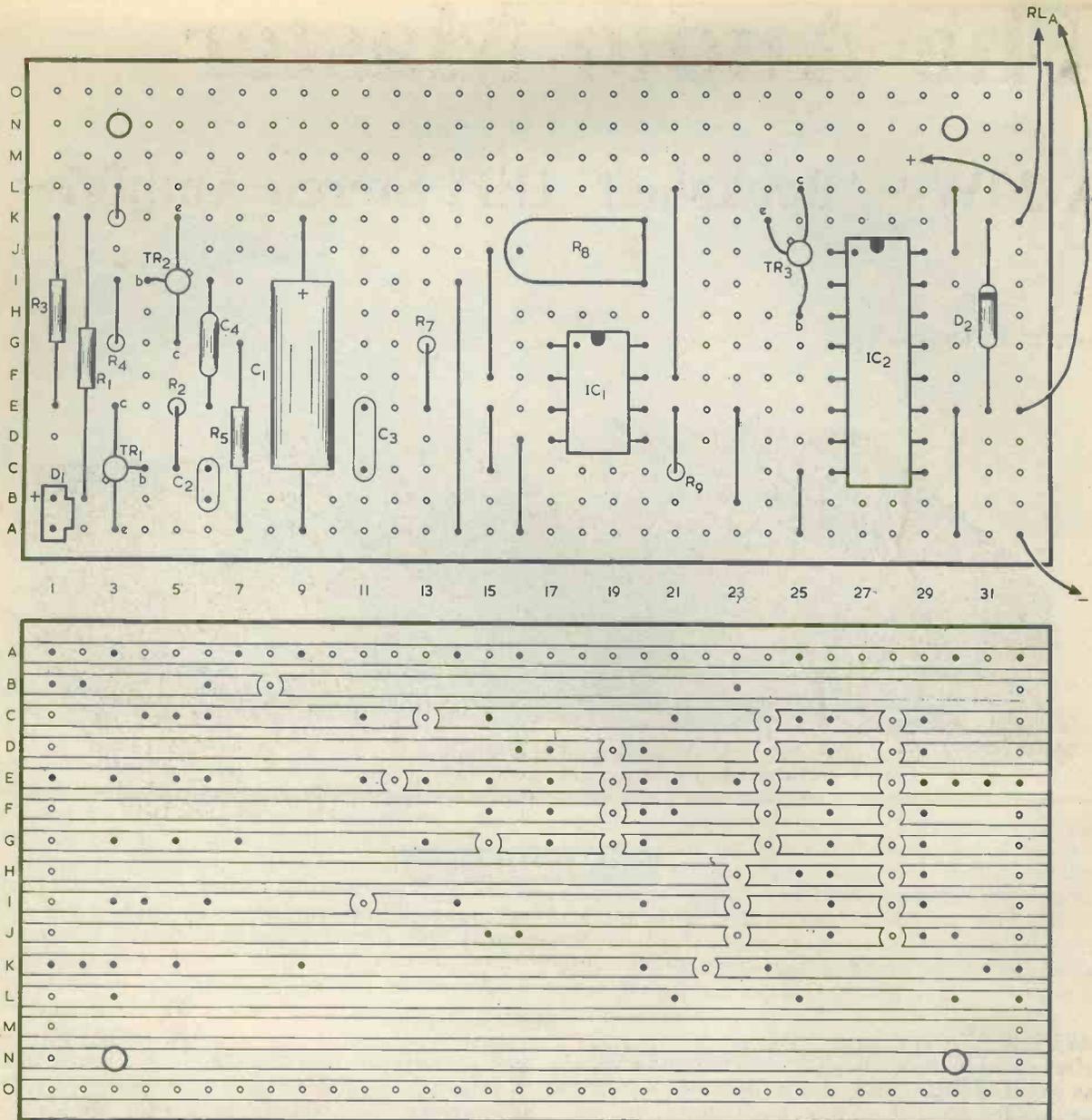


Fig. 6. The 0.1in. matrix stripboard layout for the Infra-Red Receiver.

be facing the hole, and this is opposite the face with writing on. If D1 is mounted direct on the component panel its leads must be bent through 180 degrees in order to face the sensitive surface away from the panel. The unit should not be positioned where it will pick up strong mains hum that could cause spurious operation.

ADJUSTMENT

In order to adjust R8 correctly, a multimeter should be used to monitor the voltage between pin 6 of IC1 and the negative supply rail. With R8 adjusted almost fully clockwise, a low voltage reading of only about 1 volt or so should be obtained. R8 is then

slowly adjusted in an anti-clockwise direction until the voltage reading jumps to almost the full supply voltage. The unit should then give optimum sensitivity.

The L.E.D. in the transmitter has an integral lens which gives a fairly narrow beam of infra-red light. For best results the transmitting L.E.D. should therefore be roughly aimed at the detector diode in the receiver.

Components

The VN66AF is available from Maplin Electronic Supplies and Ambit International. The CQY99 and BPW41 diodes are also available from Ambit International.

The Audio Master

A 30W+ 'Bookshelf' HiFi Stereo Amplifier

Larsholt Electronics



INTRODUCTION

Before embarking on the trail to that most nebulous of all destinations – the land of High Fidelity, consider for a moment these questions:

How much audio power does an average living room need for 'Hi Fi' sound reproduction?

What levels of distortion can be detected by the trained ear?

Opinions on the first point vary widely, but usually come down to the type of loudspeaker you are aiming to use, and (obviously enough) the dimensions and acoustic nature of the living/listening room. For most popular 'bookshelf' systems, and they are very popular indeed these days, and are frequently used in a secondary system elsewhere in the house, 20-30 watts RMS is considered to be about right by both listeners and loudspeaker manufacturers.

Those with long memories may think back to the days of valve amplifiers when (by the standards of those days, and when loudspeakers tended to be more efficient anyway) the famous Mullard circuits provided 'deafening' sound levels from 15 watts. True enough, a badly distorted 15 watt amplifier does indeed 'sound' intolerably loud, but in order to begin to appreciate the dynamic range of modern audio, 25 watts per channel is where you start, and 200 watts is where you should stop if you wish to retain all your aural faculties.

Anything much less can be acceptable for 'wall-paper' musical reproduction, but cannot really deserve the accolade of 'Hi Fi', when the term is used *correctly*. Anything much more than 30 watts per channel deserves a closer and more thorough approach than can be provided in the space available here. *'Radio and Electronics World'* will be publishing a very detailed description of the ultimate in DIY HiFi systems, and the philosophy behind 'real' HiFi based on the widely acclaimed Ambit Mark III series. So if you want a 100 watt+ per channel system, restrain yourself until the autumn.

THE BOOKSHELF AMPLIFIER

This article describes a thoroughly engineered combined stereo preamplifier/30 watt RMS power amplifier developed in Denmark by Larsholt Electronics. Part of the new policy of this magazine is to try to locate and identify worthy subjects for constructional features based purely on the merit of the feature.

Larsholt have been kind enough to permit us to use their descriptive constructional text and diagrams, which you may choose to follow wholly or in part. The one-board construction technique which combines the switching with the associated circuitry makes life a great deal easier for the constructor.

In order that the amplifier can be placed in perspective with its commercial counterparts, the NAD2020 was chosen on the basis of the similarity of specifications and overall concept. The NAD design has been widely acclaimed as the greatest thing to hit 'HiFi' since Johnson's Cotton Ear Buds, so it was interesting to see that none of the listeners managed to hear the difference. When we unravel some of the technicalities, there is a certain similarity, in that both amplifiers are designed to drive into low impedance loads without undue stress, thus masking their relatively low quoted power outputs.

The performance of the amplifier does justice to any loudspeaker capable of producing the necessary sound levels from a 30 watt drive source:

SPECIFICATIONS:

Output per channel	33W/ 4Ω (at 1% THD)
Signal to noise ratio	over 80dB (inputs loaded)
Crosstalk	better than 40dB at 1kHz
Total Harmonic Distortion	better than
	0.1% at 4 watts RMS
	0.5% at 28 watts RMS*
IMD	8kHz/6kHz -70dB 20W/10W
	8kHz/250Hz -62dB 20W/10W
Input sensitivity for 25W	100mV (tuner, aux)
	200mV (tape)
	5mV (magnetic PU)
Tone range BASS	+/- 12dB at 100Hz
TREBLE	+/- 15dB at 5kHz
Loudness	+4dB at 400Hz
	+6dB at 20kHz

Apart from simply sounding 'good', this amplifier is notable for its high signal/noise performance (which equates to dynamic range within the limitations of the output power), and the ease with which it handles transients.

CIRCUIT DESIGN

Fig. 1 shows the complete circuit diagram of the unit - the inputs are on the left, working across to the outputs on the right-hand side. Starting at the beginning with the phono/pickup stages


A quad Norton amplifier is used for all the pre-amplifier functions - with two sections being dedicated to boosting the 5mV (nominal - remember it varies with frequency) signal from a typical magnetic cartridge. Correction for the RIAA response curve is applied by the negative feedback from the output to the inverting input in exactly the same way as you would find with a 'regular' operational amplifier.

The 47KΩ cartridge load is presented in series, since this is a classic 'virtual earth' input system, and the 100mV 'equalized signal' is then fed to the switchbank where it is routed, according to selection, to the tone and volume controls.


The high input impedance emitter follower stage serves a number of purposes, firstly to present an impedance that can be AC coupled via relatively small capacitors (electrolytics this early in the signal path are invariably bad news, due to charge/discharge times and the occasional leaky one), and secondly to present the tone control stage with a well isolated and low impedance drive source. The 1n0 capacitor (108) provides RF decoupling to prevent your neighbourhood CB operator from getting in where he shouldn't.

The tone control stage utilizes two further sections of the LM3900 in a classic 'Baxandall' arrangement in the negative feedback path. If you subscribe to the 'no tone control' philosophy (you live in an anechoic chamber ??!!), then simply wire the output of the emitter follower to the top of the volume control

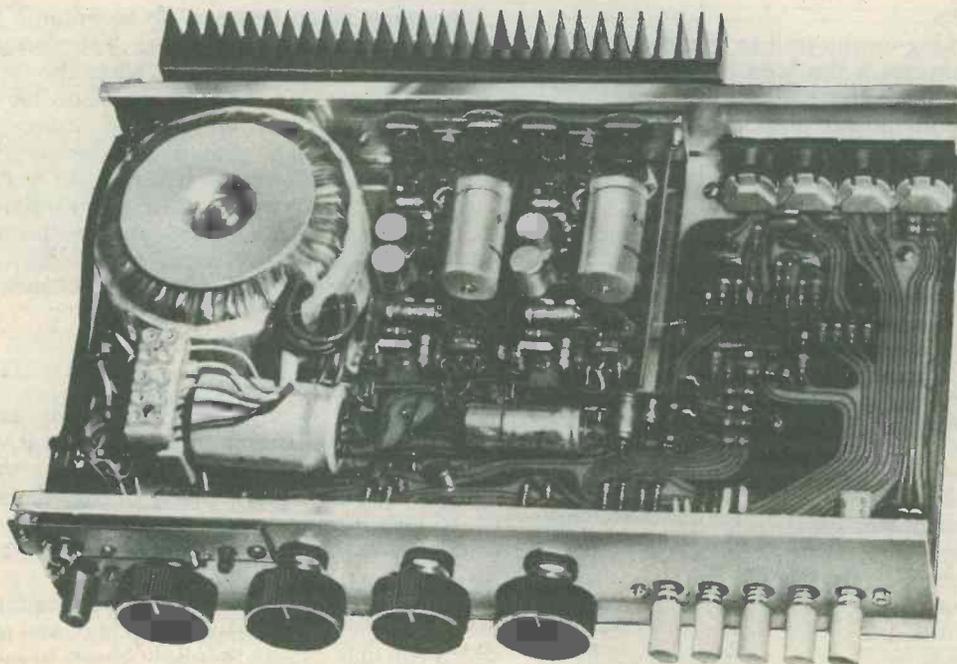The volume control is tapped to provide a facility for volume related loudness, whereby the physiological response of the ear is compensated for at low listening levels by boosting the low and high frequencies. This boost is progressively decreased until the



The unit assembled in the chassis.

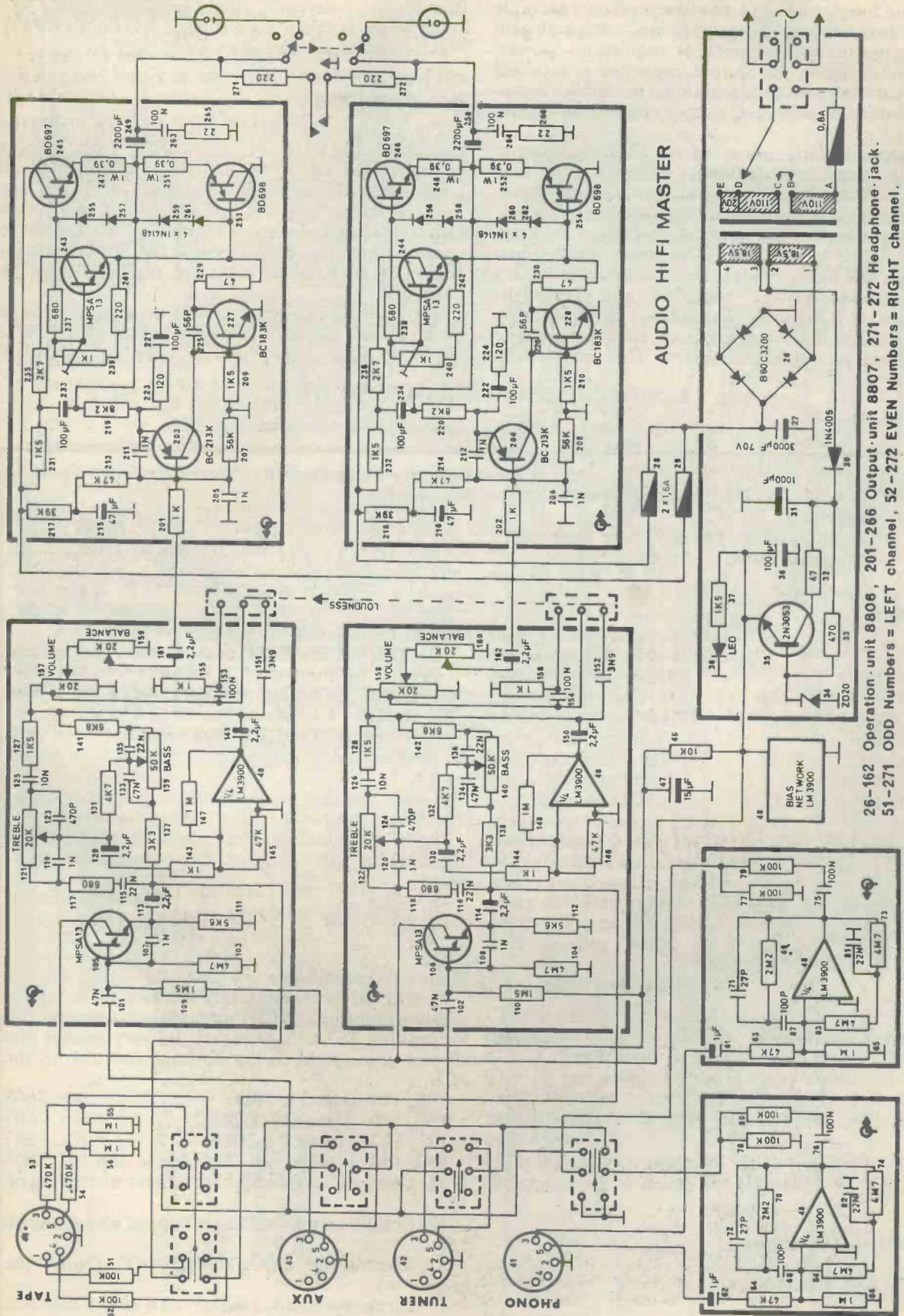

26-162 Operation-unit 8806, 201-266 Output-unit 8807, 271-272 Headphone-jack.
 51-271 ODD Numbers = LEFT channel, 52-272 EVEN Numbers = RIGHT channel.

Fig. 1. The complete circuit diagram of the unit.

control is sufficiently advanced for the ear to be operating in its 'linear' frequency response regions.

The power amplifier modules are separately powered and fused, wherein you will see a classic example of the class AB output configuration, using high gain Darlington output devices that require no 'power' driver transistors. An output capacitor is retained rather than introduce the additional protection complexities demanded by DC output connection techniques.

Headphones are connected via 220Ω resistors to prevent premature deafness, although you may choose to alter these values to 'balance' the loudspeaker volume to the particular headphones you use.

Finally, consider the power supply, since the amplifier can only be as good as the power supply 'driving' it. A low field toroidal mains transformer feeds a conventional bridge rectifier and reservoir capacitor. It is arguable that 3000μF is not enough, and if you can find room for more, then this is a wise investment in transient reserves. The preamplifier

stages are provided with their own regulated rail via a series pass transistor, which despite being only half-wave rectified does not cause any problems with hum. Bias for the potentially ripple sensitive emitter follower stages is taken via a further RC filter (46/47) which completely eliminates hum.

CONSTRUCTION

Fig. 2 gives the parts layout, and we would be interested to learn of constructors' preferences regarding the use of sequential numbering for all components, without the usual prefixes of 'R-, C-' etc. Perhaps this technique is less ambiguous, but from a publishers point of view, it requires great care not to overlook any part when devising the initial numeration – or all numbers after the omission must be changed.

The PCB patterns are available on request (plus an SAE please), although you will see that we are making the PCBs available via our 'etched but undrilled'

1. SWITCHING AND PREAMP UNIT (Fig. 2)

Components

No. on PCB		Polyester Capacitors (Read 3 colour codes from top downwards)	
10-18	9 solder tags (turn the edges parallel to the edge of PCB)	125, 126	10n brown-black-orange
30	Rectifier diode (1N4005) note position	115, 116	22n (red-red)-orange
34	20v zener diode of marker rings	101, 102, 133, 134	47n yellow-violet-orange
		75, 76, 153, 154	100n brown-black-yellow
Resistors			
32	47Ω yellow-violet-black	Further Components	
33	470Ω yellow-violet-brown	105, 106	MPSA-13 Transistors (Note the position of the flats)
117, 118	680Ω blue-grey-brown	35	2N3053 Transistors (Direction of the lap as shown)
143, 144, 155, 156	1kΩ brown-black-red	48	IC socket. The LM3900 should be placed with the position mark on the topside in the direction of tag 18.
37, 127, 128	1,5kΩ brown-green-red	9	4 pol. terminal block. Mount with the wire openings turned against the edge of the printboard.
137, 138	3,3kΩ orange-orange-red	28, 29	Fuseholders. Note the little stoplap, the free opening side is against the edge of the printboard.
131, 132	4,7kΩ yellow-violet-red	45	Push-button unit.
111, 112	5,6kΩ green-blue-red	41, 42, 43, 44	Input sockets (DIN stereo)
141, 142	6,8kΩ blue-grey-red	Double Potentiometers	
46	10kΩ brown-black-orange	One of the potentiometers has two extra tags in addition to the basic PCB mounting pins – reserve this for position 157-158 (volume). Be very careful that all pins come right to the bottom, and rest on the PCB.	
63, 64, 145, 146	47kΩ yellow-violet-orange	139, 140	Bass 2 x 50kΩ No. 7668
51, 52, 77, 78, 79, 80	100kΩ brown-black-yellow	159, 160	Balance 2 x 20kΩ No. 7667
53, 54	470kΩ yellow-violet-yellow	121, 122	Treble 2 x 20kΩ No. 7667
55, 56, 65, 66, 147, 148	1MΩ brown-black-green	157, 158	Volume 2 x 20kΩ log w. tap No. 7669
109, 110	1,5MΩ brown-green-green	11	Connect tag 11 with bare copper wire to tag on 157
69, 70	2,2MΩ red-red-green	12	Connect tag 12 with bare copper wire to tag on 158
73, 74, 83, 84, 103, 104	4,7MΩ yellow-violet-green	31	Electrolytic cap. 1000uF-40V (Note the groove +)
Ceramic Capacitors		27	Electrolytic cap. 3000uF-70V (Note that one of the wires has a black dot. Mount as shown)
71, 72	27pF (Fig. 2) grey w. black top	26	Rectifier B80C3200
67, 68	100pF (Fig. 3) grey w. black top		
123, 124	470pF (Fig. 1) cream w. yellow top		
107, 108, 119, 120	1nF (Fig. 2) cream w. yellow top		
151, 152	3,9nF (Fig. 3) cream w. yellow top		
81, 82	22nF (Fig. 3) cream w. green top		
Electrolytic Capacitors			
113, 114, 129, 130,			
149, 150, 161, 162	2,2uF-40V		
47	15uF-40V		
36	100uF-25V		
61, 62	Tantalum, 1uF		


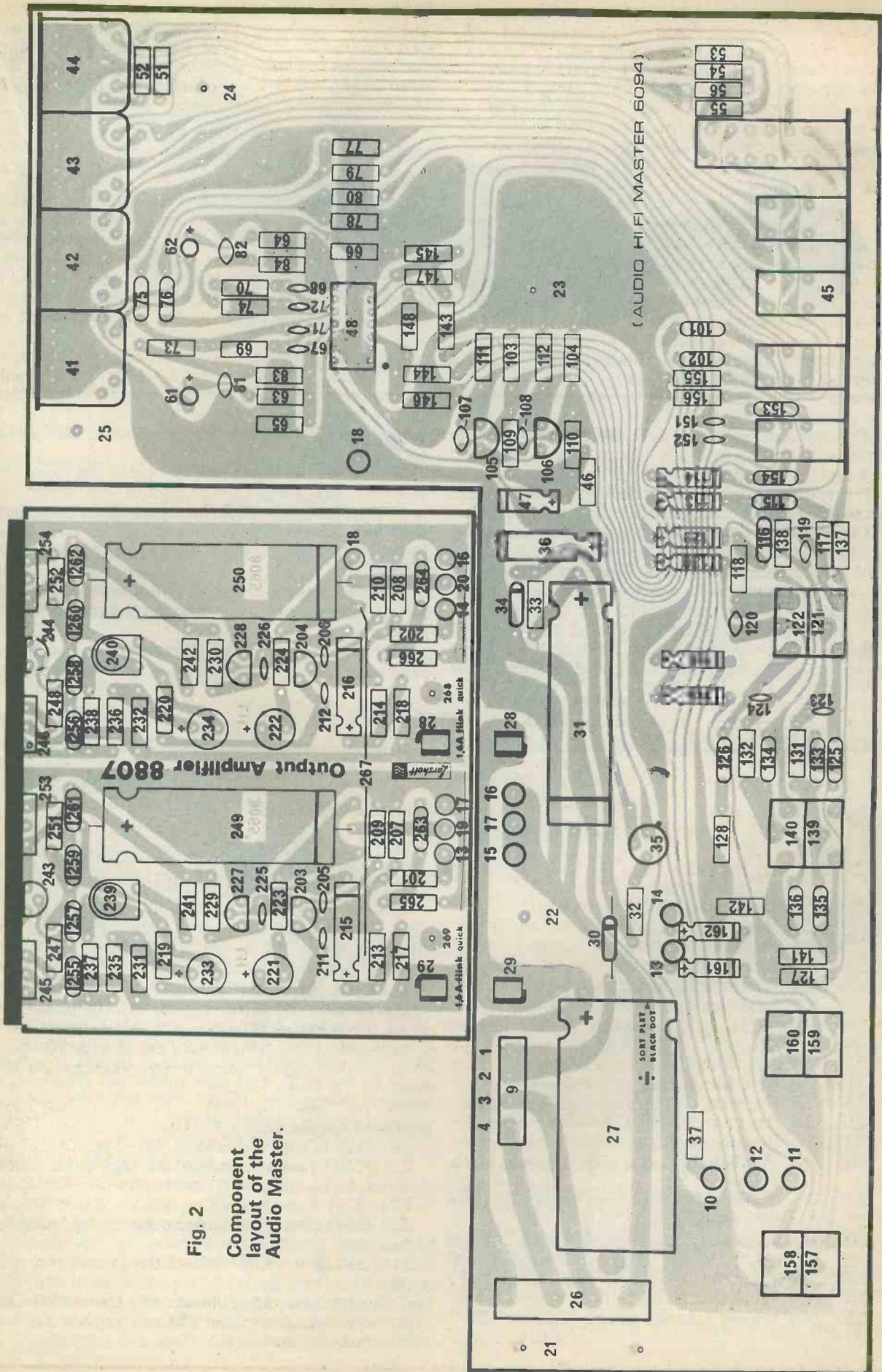


Fig. 2
Component layout of the Audio Master.

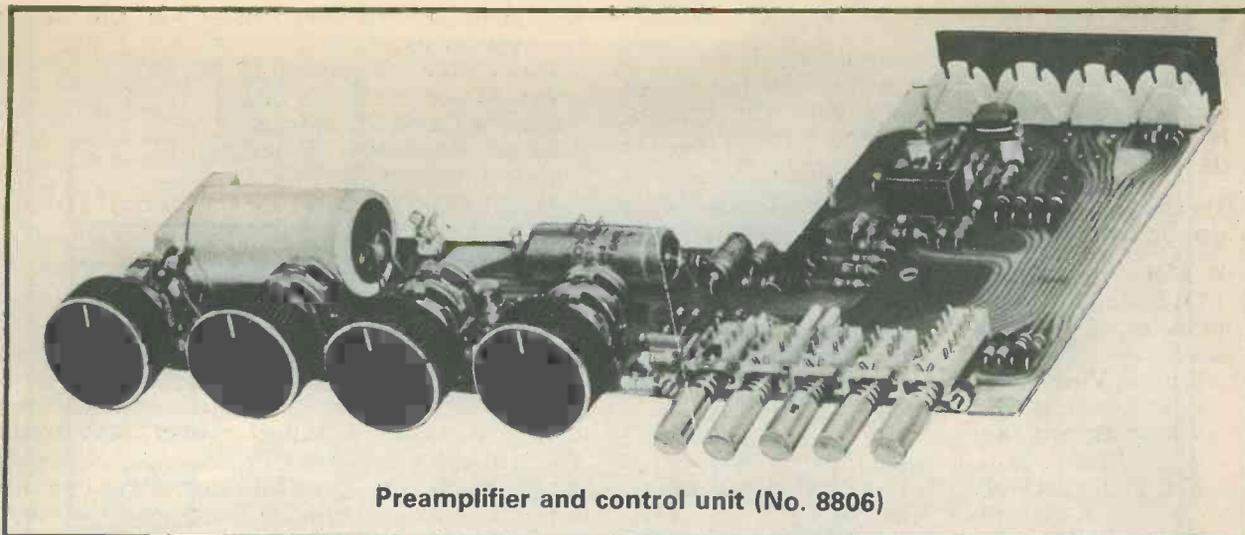

Preamplifier and control unit (No. 8806)

PCB service, whereby we feel the low cost is quite persuasive compared to the 'etch-it-yourself' approach.

The following instructions describe a convenient mounting order for the parts on the assemblies. You will find that all the described position numbers are also printed on the PCBs, which should make errors impossible. Your attention is drawn to the notes in the text, concerning the placing of diodes, transistors, electrolytic capacitors and ICs – all of which have a specific orientation which must be observed.

Resistors, non-polarised capacitors and polyester capacitors can all be mounted in either direction – but

where possible, place the components so the identification is visible.

Solder the components in place as they are mounted, and clip away the surplus wire ends.

Be careful when soldering on the PCBs to check that there are no short circuits caused by inadvertent bridging of the solder between the tracks of the board.

Now the operation unit 8806 is finished. With the aid of the position plan, you can determine all the locations.

Once again: Inspect the soldering work and be sure that no short circuits are left.

2. OUTPUT AMPLIFIER UNIT NO. 8807

Components

No. on Printboard

13, 14, 16-20 7 solder tags (the flats parallel with the edge of PCB)

255-262 inc. 8 diodes 1N4148 (note position of marker ring)

265, 266 Resistors 22Ω red-red-black

229, 230 Resistors 47Ω yellow-violet-black

223, 224 Resistors 120Ω brown-red-brown

241, 242 Resistors 220Ω red-red-brown

237, 238 Resistors 680Ω blue-grey-brown

201, 202 Resistors 1kΩ brown-black-red

209, 210, 231, 232 Resistors 1,5kΩ brown-green-red

235, 236 Resistors 2,7kΩ red-violet-red

219, 220 Resistors 8,2kΩ grey-red-red

217, 218 Resistors 39kΩ orange-white-orange

213, 214 Resistors 47kΩ yellow-violet-orange

207, 208 Resistors 56kΩ green-blue-orange

263, 264 Polyflat capacitor 100nF brown-black-yellow

225, 226 Ceramic capacitor 56pF (grey with black top) marked 56p

205, 206, 211, 212 Ceramic capacitor 1nF (cream with yellow top) marked 1n0

227, 228 Transistor BC183K) note position of

203, 204 Transistor BC213K) flat side

239, 240 Pre-set potentiometers 1kΩ

Mounting the heatsink complex

(which is supplied ready assembled by Larsholt)

243, 244 2 MPSA-13 Darlington transistors

245, 246 2 BD 697A Darlington transistors

253, 254 2 BD 698A Darlington transistors

The mounting will be easier if the two brass cooling clips, encasing the transistors, are temporarily dismantled, while the 12 wire ends from the power transistors are led through the holes provided in the PCB. When the aluminium block rests close on the board – and at 90 degrees to the PCB, then solder all 12 of the wires. After that, remount the two brass cooling clips (with the transistors) and tighten carefully. See that the block continues to stay at a right angle to the PCB, and then solder the remaining 6 legs.

Further Components

247, 248 4 wire resistors 0,39Ω, 1W

251, 252) (avoid bending the legs close to the body)

221, 222) 4 electrolytic capacitors 100uF-40V

233, 234) (the + leg nearest the cooling block)

249, 250 2 2200uF-40V) Note the position

215, 216 2 47uF-40V) of the groove (+)

28, 29 2 Fuseholders (Note the little retention clip, fix with the opening against the edge of the PCB)

Now the output amplifier 8807 is complete. Inspect the module for correct locations and soldering.

3. MOUNTING OF CHASSIS NO. 8805

- 1) To ensure safe transportation, the mains transformer is screwed down by Larsholt – but remove the transformer while you assemble the chassis. However, note the position of the wire-out tag, and the order of the steel and rubber washers.
- 2) The unit with 5 position terminal block should also be temporarily removed.
- 3) **Mounting the headphone jack**
Dismount the jack from the PCB and solder in the following wires and resistors as shown in the wiring plan:
Wire R Violet 235mm to terminal 6
Wire S Yellow 270mm to terminal 2
Wire T Brown 180mm to terminal 3
Wire U Black 150mm to terminal 7
271, 272 2 resistors 220 Ω , red-red-brown respectively to 1 & 8 and to 4 & 5.
Y Sleeve 90mm to pull over violet and yellow wire
X Sleeve 120mm to pull over brown and black wire
Put the jack aside for fixing later.
- 4) Wire A Grey 60mm between mains switch and fuse unit
Wire B Grey 60mm solder on the fuse unit
Wire C Grey 60mm solder on the mains switch
- 5) **Mounting the output amplifier module 8807**
 - a) Put the three protruding screws from the cooling block through the holes in the rear of the chassis. (And through the holes in the extruded ribbed element).
 - b) Mount 2 screws (6mm) respectively by the fuseholder 28 & 29 at positions 268 and 269 – but do not tighten them yet.
 - c) Three brass blind nuts with notches should now be fixed onto the ends of screws (point (a) above), which are located between the ribs of the external heatsink. Tighten these evenly and carefully to ensure optimum heat transfer to the radiating element.
 - d) Now tighten the two screws mentioned in point b.
- 6) **Mounting the Operation-Unit 8806**
 - a) Unscrew the nuts and locking washers from the potentiometers, and the two nuts from the push button switch unit.
 - b) Place the unit in position and refit the lock washers and nuts – but don't tighten them yet.
 - c) Refit the console with the terminal block in position 21 and mount the remaining 4 screws on positions, 22, 23, 24 and 25 but don't tighten yet.
 - d) Now tighten the nuts on the front of the chassis (Potentiometers and switch) and then the 5 screws on the PCB (as point (c) above).
- 7) **Mounting the wires on the loudspeaker sockets**
Wire V Bare copper wire between the two sockets.
Wire L Blue 235mm from the lower socket to operation unit point 15.
- 8) The jack with wires (mounted as at point 3) should now be fitted.
Push both the sleeves close up to the jack.
Carry the yellow and violet wire (covered by sleeve) back at the same level as the jack, and as far as possible from the open mains voltage points on the main switch and fuse unit – and connect to:
Yellow wire (S) to the output amplifier No. 20
Violet wire (R) to the output amplifier No. 19
(The brown and black wire will be connected later)

9) Connections between operation unit and the output amplifier unit

- Wire G Red 70mm from 13 to 13
 - Wire H Green 110mm from 14 to 14
 - Wire M Black 70mm from 16 to 16
 - Wire N Bare copper from 17 to 17
 - Wire P Bare copper from 18 to 18
- The white wire from the LED PCB on the front of the chassis should be connected to point 15.
(The grey and orange wires from the same PCB will be mentioned later)

10) Remounting the Mains Transformer

Under the bottom of the chassis: Screwhead and 70mm steel-washer

Over the bottom of the chassis: 70mm rubber-washer, transformer, rubber washer, steel washer with centre depression, fixing nut.

Before you tighten, the transformer must be close to the chassis rear and about 1mm from the output PCB.

Turn the transformer so that the tag connector strip is positioned at 4.30 (o'clock) when seen from the front.

Make certain that no wires get caught between the washers.

T (brown wire from jack): connect to the lower loudspeaker socket

U (black wire from jack): connect to the upper loudspeaker socket

11) The Mains Transformer connections

The thick wires to the 4 pole terminal block on the operation block on the operation unit

Blue to No. 4

Green to No. 3

Yellow to No. 2

Red to No. 1

The thin wires to the 5 pole terminal block on the console

Violet to point A

White to point B

Grey to point C

Black to point D

Brown to point E

12) Connection to mains supply

The mains lead and plug are not supplied with the kit, as different rules and regulations exist regarding these in most countries. The mains lead should be passed through the plastic grommet in the bottom of the chassis under the clamps and connected to the on/off switch.

13) Wire B from the fuse unit: connect to pole A

Wire C from on/off switch: connect to pole D and connect pole B to C.

Other Mains Voltages 110, 130 or 240V (see the label under the chassis)

14) Now check all connections with the wiring plan and examine all soldered joints.

15) Adjustment of the output amplifier


You will find two resistors enclosed:

47 Ω (Yellow-violet-black)

100 Ω (brown-black-brown)

a) The orange and grey wire from the LED PCB on the chassis front should be soldered to these resistors as shown here:

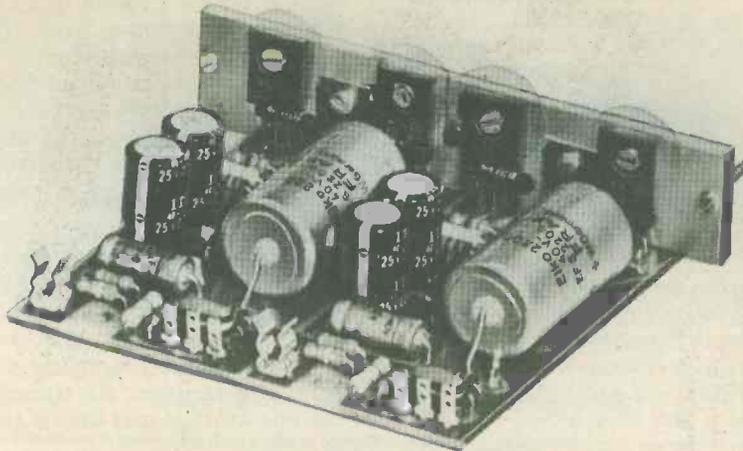b) The end of the 47 Ω resistor with the orange wire:
solder lightly to the exterior of the fuseholder 29 on



Stereo output amplifier.

the output amplifier.

The end of the 100 ohm:

Solder to fuseholder 29 on the operation unit.

c) Turn the two preset potentiometers 239 and 240 to the left (anti-clockwise) completely to the end stop.

d) Volume control in a closed position. Balance, Bass and Treble set midway.

e) Connect the mains and switch on – but not before you are sure that the two preset potentiometers are turned completely anti-clockwise.

Incorrect setting will damage the output stages

f) With the correct tool, turn preset 239 SLOWLY clockwise until the LED glows faintly, and turn back until the diode just extinguishes. Stop at this point and the left hand channel is now adjusted.

g) Repeat the procedure for the right hand channel by moving the resistor network to the fuseholder 28. (as in point b).

h) The set is now adjusted completely. Switch off,

and remove the resistor network. The disconnected wire must now be connected to the preamp unit:

Orange to tag No. 17 and

Grey to tag No. 10 after shortening.

i) Finally, the 1.6 amp fuses are placed in fuseholders 28 and 29.

16) After final inspection, and an extra check of the tightening of the transformer cooling block and heat-sink, you can now mount the wood veneered cabinet, with the four burnished screws provided, and fit the front panel with the two cross head screws. Now fit the knobs, we suggest that the white line on the knobs be laced at 12 o'clock when the volume control is closed off, and the balance, bass and treble are midway.

Complete kits of parts, and individual components are available from the R&EW reader services department. Total cost for the complete kit as illustrated herein for this project is £65.00 inc VAT. Postage is £4 extra, or you can collect from our offices at 200 North Service Road, Brentwood, Essex.

"He takes these video games very seriously."



NC-559 T-ADAPTOR
 Three female
 Delrin insulation
 Net weight: 42gr.



NC-560 (M-358) T-CONNECTOR
 Double female - single male
 Delrin insulation
 Net weight: 44gr.



NC-553 (PL-258)
 Delrin insulation
 Net weight: 22gr.



NC-580 FOUR CONNECTION ADAPTOR
 Three female - single male
 Delrin insulation
 Net weight: 60gr.



NC-563
 Delrin insulation
 Net weight: 22gr.



DOUBLE FEMALE ADAPTOR

NC-567 LIGHTNING ARRESTOR
 Double female
 Delrin insulation
 Net weight: 45gr.



NC-566 LIGHTNING ARRESTOR
 Male to female
 Delrin insulation
 Net weight: 50gr.



NC-558 (M-359)
 Delrin insulation
 Net weight: 33gr.




RIGHT ANGLE CONNECTOR

DOUBLE MALE ADAPTOR

Know your RF connectors (2)

Continuing where we left off last time, the PL-259 series extends into a wide range of special function adapters - some of which are shown here. Care should be taken in the use of 'splitters' and 'T' pieces, since the antenna impedance will be completely altered if placed in parallel with some other 'termination'. Such adapters are frequently most useful in test fixtures (oscilloscope inputs etc.) The lightning arrestors provide a spark gap to earth, and consequently must be earthed via the tag provided using the stoutest wire or braid available - or if you rely on the basic equipment mains earth, most of the energy will still pass through the equipment. The enormous energy available from a static discharge through the 'chassis' is still likely to damage sensitive RF environments.

EDITORIAL

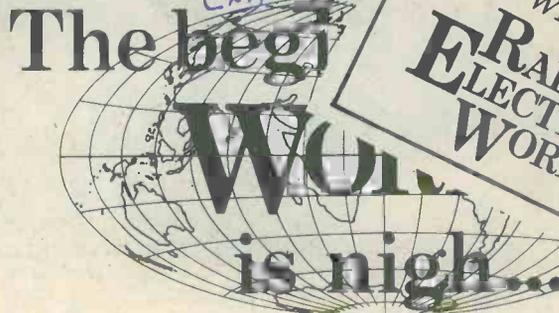

A SNEAK PREVIEW OF
PART OF WHAT
YOU WILL FIND IN
**RADIO &
ELECTRONICS
WORLD**

Welcome

The beginning of the world is nigh...

The occasion of a launch of a new publication such as **R&EW** is usually accompanied by much smugness and back slapping, with assertions that the universe will be a finer place as a direct result of the publication of 'XYZ'. We don't necessarily subscribe to this attitude, since **R&EW** is very much a publication for the 'sharp end' of the business of electronics, communications and computing - and not simply for the business of publishing.

Accordingly, you will find that **R&EW** is not constrained by the corporate policies of some of the larger publishing houses, and our route to provide the readers with what they *really* want will accordingly be rather more direct and succinct.

This sneak preview section contains an introduction to some of the features and style that **R&EW** will provide on a monthly basis, but rather than provide a page from a number of incomplete items, we thought you would rather see an example of a complete feature in the **R&EW** style. **R&EW** is a very 'vertically integrated' concept, with all the necessary lab and technical facilities to provide the sort of documentation from within our own organization. This policy of integration extends to the supply of parts to support these features.

If we are responsible for researching/sponsoring state of the art features and articles, then we feel we should carry this through into the supply and support of the necessary parts for those of you wishing to copy an idea or feature *per se*; and those wishing to develop it further. After all, **R&EW**'s prime aim is to try and spur readers onto greater things, and to try and halt the slide of our electronics industry before too much lands in the lap of foreign equipment makers.

The UK's record on innovation and competitive industrial production over the past few years has not been good. In fact, bearing in mind the skills and brainpower at our disposal, the comment that most frequently springs to mind is 'dismal'. Our electronics industry has mainly shone as a result of tactical considerations (i.e. the government doesn't want to rely too heavily on overseas supply for items of national defence). The consumer and 'volume' business has all but disappeared, with a couple of notable exceptions.

So without getting into too much of the 'cant' mentioned at the outset of this piece, **R&EW** would like to help resuscitate some of the self esteem and confidence of British electronics *user*, be he or she a professional engineer, student or hobbyist. A lot of our success will depend on your contributions - so watch for the first 'real' issue of **R&EW** for details of how we are going to make life easier for those of you with a few ideas of your own to put them into practise using *free* components and design support. And get paid around £50 a page into the bargain.

An invitation

If you have anything to say on the subjects you find covered in **R&EW**, then please write and let us hear about it. If you have any ideas that you would like to offer for publication, then send them in.

If you have ideas, but do not know how to go about presenting them, then watch **R&EW** for details of how to set out feature articles for submission.

If you have viable design ideas for practical features, and would like to avail yourself of the **R&EW** feature sponsorship scheme that is available to those groups or individuals with the resolve to see such a project through to a conclusion - then write (enclosing an A5 size SAE) to the 'Readers' Services' department for the details. This scheme may be particularly useful to schools and colleges with good ideas, but hindered by a shortage of funds to implement them using the best and most modern technology.

Radio and Electronics World is keen to support any practical endeavour, and we are pleased to offer advice and information through the medium of our **Readers Q-A** page. There is likely to be a flood of enquiries for this department, and we must point out that we cannot guarantee an answer to all enquirers. (other than '43'). And one rule is absolutely rigid — no SAE, no answer.

Interesting and original enquiries will tend to take precedence, and although we cannot promise to be the fount of all knowledge in electronics, communications and computing — the **R&EW** book service is a most comprehensive and carefully considered 'complement' to provide the readers with 'background support'.

Goodbye RC. RIP.

William Bell

a state-of-the-art vhf converter

timothy edwards

Despite the plethora of ready made equipment for the 2 metre (144-146MHz) amateur communication band, most radio enthusiasts like to try and salve their consciences as participants in the once exclusively 'practical' art of amateur radio, by making at least one or two items of equipment that can justifiably be described as 'home grown'.

Most of the commercial transceivers for the VHF bands are primarily FM systems for simply 'nattering', and some of the hobby's traditionalists might suggest that the use of 2m NBFM bears more than a passing resemblance to the principles behind CB radio - but that's an entirely more contentious subject.....

The exclusive use of NBFM tends to overlook the more interesting aspects of CW and SSB communications (morse code and single sideband to the uninitiated). But since most enthusiasts have an HF communications receiver (or two) at their disposal, it is an easy enough task to make a thoroughly professional converter for 144-146MHz, with an IF output to be tuned on the 28-30MHz section of the HF receiver. The radio enthusiast may thus fulfil the repressed constructional instinct, as well as being able to have a serious look at the CW and SSB aspects of the 2 metre band before launching into a few hundred pounds worth of oriental temptation.

The converter is basically a linear device within the expected range of input signal levels, and so any mode (AM, FM and SSB) can be converted to the required HF output. Some HF receivers are available with NBFM demodulators, but to do the job properly, the correct bandwidth IF filter needs to be used with a purpose made NBFM IF system. In the absence of this facility, slope detection of NBFM is better than nothing. (Slope detection relies on the IF filter passband edge to translate the frequency modulation information into an amplitude variation for detection as simple AM).


However, failing all this, you can build the R&EW NBFM tuneable IF, or the R&EW add-on NBFM adapter - both of which are scheduled to appear in an early issue.

Judging by the numbers of 'nearly new' SSB transceivers advertised for sale, it is no doubt better to investigate your long term interest in this aspect of communication without first contributing to the wrong side of the balance of payments. This converter provides reception of repeaters, NBFM simplex, and demanding

Probably the most advanced UK electronics magazine, giving commercial techniques and design philosophy made by a relatively inexperienced enthusiast

A SNEAK PREVIEW OF PART OF WHAT YOU WILL FIND IN
RADIO & ELECTRONICS WORLD

a silly

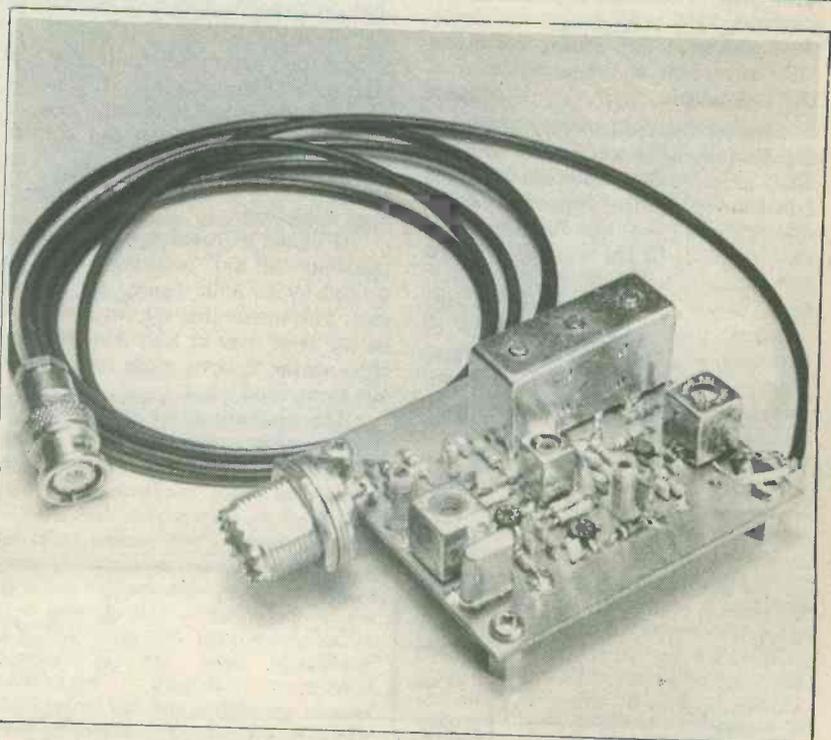

long range communications using CW or SSB.

The R&EW 2 metre converter

This converter was originally designed to compliment the RX80 receiver described in "Radio Communication", although it will obviously operate with such receivers as the FRG7, R1000, DX160 etc. It has been designed with the latest state-of-the-art components, notably the NEC 3SK88 MOSFET (note one), which has been chosen for its repeatably low noise figure and low cost. The TOKO CBT series helical filter provides an outstanding bandpass and stopband response, but most significantly of all from the point of view of those of you wishing to duplicate this converter, it is supplied prealigned, and requires virtually no trimming to optimize alignment.

Although a VHF converter usually requires considerable expertise, and recourse to a selection of signal generators and other analytical equipment, the R&EW converter can be built by anyone with 'kit building experience' and a multimeter.

Circuit Description

Fig.1 shows the complete circuit diagram. C1,C2 and L1 provide the optimum noise match between the 50 ohm antenna input and the RF amplifier - this is a carefully derived selection of values, and not simply a haphazard choice from the junkbox. Gate 2 of Q1 is biased at 5v (externally derived - ie from the main receiver or tuneable IF - negative going AGC may be applied at this point by those with adequate confidence and experience). The source of the RF amplifier Q1 is then taken directly to ground to ensure minimum impedance.

The drain of Q1 through R3 termi-

A SNEAK PREVIEW OF PART OF WHAT YOU WILL FIND IN RADIO & ELECTRONICS WORLD

... to VHF circuit 'variable' has substituted by a 'building block' that takes out most of the problems for the less experienced designer and user. More than 75% of the problems associated with VHF radio designs are simply those associated with getting lost in the MHz as a result of the uncertainties of DIY coil designs.

Helical filters will not salvage designs that fall into the all too familiar abyss of 'dry' joints, and a shortage of basic experience in handling components and a soldering iron - but these filters will help allay the fears of the more experienced audio constructor whose neat RF projects have always been relegated to the 'pending' tray, since the problems of alignment associated with the 'green' fingers of the RF engineer, sometimes seem insurmountable.

The circuit below illustrates some of the typical test voltages (nom 12v input)

Unlike the RF amplifier, the mixer does not use any DC bias on either of its gates. This is because the amplitude of the local oscillator injection voltage is designed to be sufficient to switch Q2 directly at 116MHz, thereby improving the intermodulation performance of the converter. This technique is used in some professional receivers, and is similar in concept to the esoteric Schottky diode double balanced mixer - except, of course, this system is single ended. It is possibly the first time that this approach has been used in an enthusiasts constructional feature. Unless you know better....

At the drain of Q2, the wanted mixer product (28-30MHz) is selected in the tuned circuit formed by L3 and C8, and matched at the secondary to 50 ohms to feed the main receiver. It is this output network that mainly constitutes the 3dB bandwidth of the converter. This means that the gain is approximately 25dB at 144MHz, 28dB at 145MHz and 25dB at 146MHz. This reduction of gain is of no consequence as the design has plenty in hand at all times.

It should be noted that the ultimate sensitivity of any receiving system is defined by its noise figure, and *not* its gain. This means that the sensitivity will be the same over at least 144-146MHz, although the 'S' meter might read slightly less at the band edges.

The oscillator chain uses a 58MHz crystal, rather than the more usual 116MHz type. Transistor Q3 serves the function of both oscillator, and the


Specifications	
Noise figure	less than 2dB
Gain	28dB nominal
3dB Bandwidth	144-146MHz
IF output	28-30MHz
1dB compression	+ 5dBm output
Saturated output	+ 7dBm
Supply voltage	8-16v
Supply current	15mA nominal
In out impedance	50 ohms
Size	70 x 60 x 20mm

frequency doubler. L4 tunes out the capacitive reactance presented to the third overtone crystal and allows fine adjustment of its operating frequency. L5, C15 and C16 select the second harmonic from the oscillator at 116MHz and matches it into Q4 where it is amplified to an adequate level to switch the mixer, Q2. The capacitive divider, C19 and C20, provide the necessary level and impedance adjustment to feed the oscillator injection of approximately 2mW to gate 2 of Q2.

On a general point about decoupling, note the way in which the earthy end of the tuned circuit are decoupled with capacitance and inductance. Taking the example of L3 (R8/C9), R8 is apparently superfluous.


Continued in October R&EW

Figure one

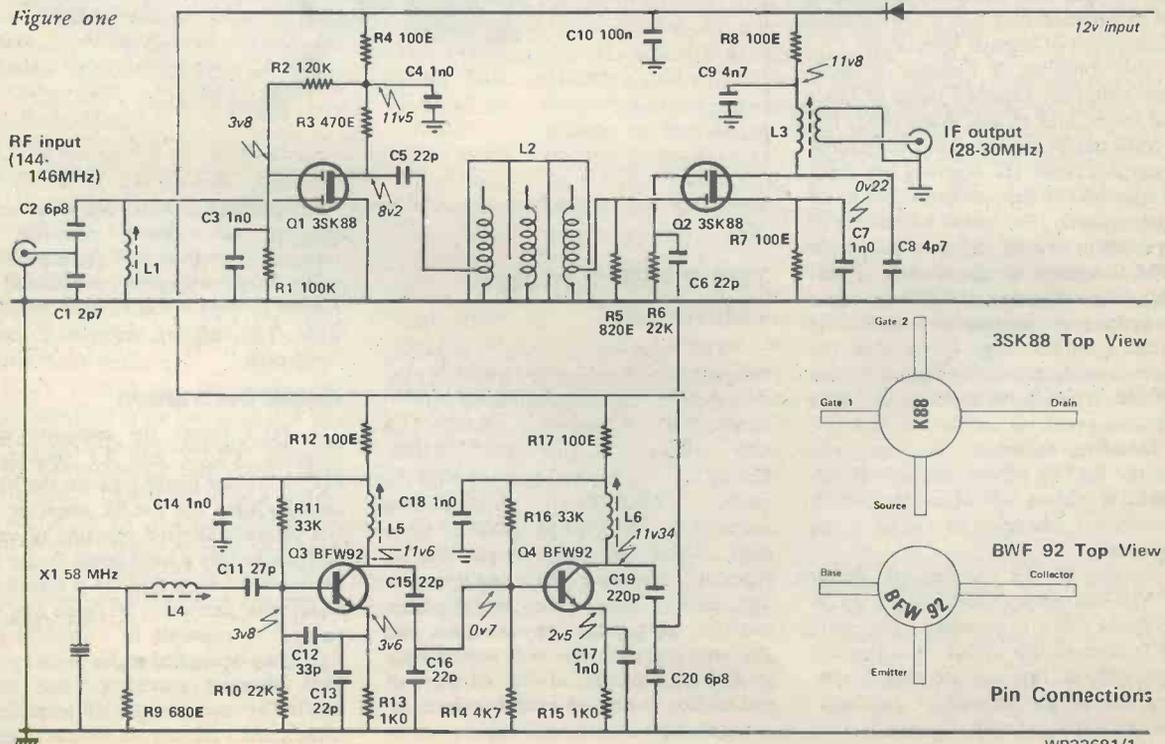

D1 1N4148

12v input

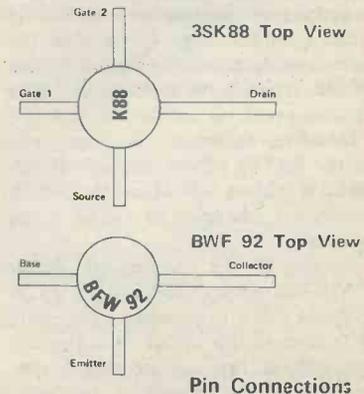

WP22681/1

READERS Q·A

Dear Sirs,

I have purchased a pulse induction metal locator - but now find that it appears to be susceptible to 'ground' interference - and I am very disappointed, since the immunity to ground effect problems was my main reason for choosing this type of machine.

Are you aware of any modifications that can be employed to eliminate these problems?

JS
Glamorgan

R&EW:

The short answer is that the pulse induction system cannot (by definition) suffer from 'ground effects' in the most frequently used sense of the term. 'Ground effect' is usually associated with tuned search head detectors that rely on the detuning effects of eddy currents induced in the 'target' metal.

But 'tuned' circuits are tuned by a combination of inductance and capacitance, and the 'ground' effect is the capacitive interference (damp ground is usually the cause) with the inductive aspects of the detection process.

In a pulse induction system (PI), the search head is untuned, being simply an inductor used to transmit a pulse of electromagnetic energy at no particular 'resonant' frequency.

The effect you are getting is most likely due to ferrous mineralization of the soil, which is a fairly widespread phenomenon in this country. The PI system is particularly susceptible to iron, due to the magnetization characteristics and the hysteresis of the metal 'storing' the pulse charge particularly effectively and then retransmitting it back to the detector head.

R&EW will be running a series of articles describing the theory and practise of metal detection in unique detail, and we suggest that you watch for further coverage.

Dear Sir,

I need a replacement for a 2N5915 or BLY53A. Please advise.

BR
Hants

R&EW:

The BLY53A is basically a 470MHz, 7w output 13.2v FM RF device. As it happens, Ambit International presently offer this at £5.02 at one off, although an alternative is the Motorola 2N5946. We can't offer you an off-the-cuff price for this part, however, since Motorola RF

devices are not easily available in one in the UK (would Motorola care to help out at R&EW with pricing and availability of their excellent range devices via the World of Radio and Electronics catalogue??)

The 2 watt version (2N5944) of the family is listed at over £9 each, so prepare for a shock...

Dear Sir,

I recently decided to upgrade my PA system (used by a local rock group), and was pleasantly surprised to find the simple and elegant AMBIT PA101 used in conjunction with D.C. Read's active loudspeaker article in April's *Wireless World*.

I am not sure if it is possible to beef the design up by paralleling more FET's. I am after 150w/8 ohms, or 250w/4 ohms. Can you comment on feasibility and potential problems?

MK
Czechoslovakia

R&EW:

A good question. One of the most endearing aspects of the power MOSFET is the ease with which it can be paralleled, and the indestructibility of high powered systems built with them. So the short answer is 'yes'.

The 140v devices used on the PA101 will drop around 10v - leaving, say, a swing of 110v pp across the load - around 180w into 8 ohms. A lot of care should be taken over the PSU design, since the use of a PSU with 5% load regulation as opposed to the more frequently encountered 10-20% regulation transformers will help keep power up, and avoid problems from modulation of the power rail.

The PA101 has recently been superseded by the PA105, which is specifically designed for parallel output devices, and is available with a heatsink bracket designed accordingly. The track layout of any high powered PA is a great deal more critical than most unsuspecting constructors take into account, and can easily make the difference between 0.005% and 1% distortion. Or worse still, complete instability.

R&EW will be charting a course through such design concepts and problems with our series on 'The Last Word in DIY Audio' - the first part of which describes the R&EW MOSFET PA, featuring an 80-160w MOSFET power amplifier, with bridging (for over 400w) and a very comprehensive overload and speaker protection circuit. Watch out around the November issue for the start of the series.

A SNEAK PREVIEW OF
PART OF WHAT
YOU WILL FIND IN
**RADIO &
ELECTRONICS
WORLD**

On
About
to shore) but
for 'navigational'

The second is a M CB
transceiver with a relatively low power
requirement, say 5 watts.

WJF
Hants

R&EW:

Hold on there, Mr F. Your secret is safe with us, but you had better take note of the Wireless Telegraphy Act which says many things about the devices you ask about. Most of them boil down to the £400 fine, confiscation and possible prison sentence for such illicit equipment as you have requested - doubtless in all innocence.

The first item is an ideal case for a 934MHz CB transceiver. Since the licensing is simple, and the actual device not as daunting as some would have you believe. And, you've guessed it, R&EW will be covering just this type of application of CB which will probably be getting overlooked by the avaricious Oriental hordes in their anxiety to plunder our balance of payments with a plethora of car mobiles and hand-helds.

The specification of the 27MHz CB radio is quite plain, and since 4w RF is the maximum, then 5w is relatively high in terms of output. You can pick up a set for around £50 when it all 'happens', although there will be many useful accessories and gadgets to be made to complement your gear.

Dear Sir,

Can you please advise me of a suitable alternative for the J305 FET as used in the Aztec UM1181 FM varicap tunerhead - since I am unable to locate a source.

J.J. Essex

R&EW:

The J305 is a low noise N-channel FET, made by Siliconix. If you cannot get this from any Siliconix source, then you can substitute this by a Hitachi 2SK55, which has a similar noise figure, but remember to watch the base connections.

Please address correspondence to:

Readers Letters
Radio and Electronics World
117a High Street
Brentwood
Essex. CM14 4SG

A 5 CHANNEL DIGITAL- PROPORTIONAL RC SYSTEM

Radio Control is a perennially popular feature in electronics magazines, although the ready availability of complete systems from the mystic orient has tended to suppress the construction instincts of radio modelling enthusiasts. However, there seems to be a sufficiently large number of hard core enthusiasts who are willing to wield a soldering iron in the interests of providing their own electronic control link, and their patience has been rewarded by the arrival of several families of purpose-made integrated circuits that make this task somewhat more straightforward and reliable.

The recently released 35MHz band for radio control within the UK is primarily aimed at model aircraft enthusiasts, and understandably enough, the association governing club flying has decided to try and enforce certain minimum standards on equipment used in competition flying, to prevent interaction and mutual interference. The system described here is primarily aimed at land and water based control, where the uncertainties of home construction will not prove too catastrophic. A subsequent feature in *Radio & Electronics World* will cover a more sophisticated system for the 35MHz band, and also for the UHF 459MHz band which is presently used very little except by the most avid enthusiast and professional modellers.

THE BASICS OF PROPORTIONAL CONTROL SYSTEMS

Once upon a time, the shortage of ready made equipment for model radio control ensured a very widespread appreciation of the principles involved, since the majority of equipment was at least, in part,

home constructed. However, the gradual slide into dependency on ready made equipment has somewhat obscured the basic operational principles of a radio control link, and so it is worthwhile to re-examine these concepts in some detail. Fig.1 shows the nature of the control wave form as derived from the control encoder, where you will see the output signals from the control sticks (or other preset control mechanism), is translated into five varying pulse widths that are transmitted as part of a complete "frame". The repetition rate of this frame is approximately 50Hz, hence listening to a model radio control signal on a radio frequently sounds somewhat like a 50 cycle mains hum.

Each of the five channels is represented by an individual pulse width in this frame, which is built up of the standard pulse of 200 micro seconds plus the variable pulse width attributable to the control stick position. The logic clocks along from the leading edge of the pulse in the frame. The long delay between the final pulse of one frame and the first pulse of the next frame allows the reset period to be detected at the receiver, thereby ensures that each servo is fed the correct pulse information each time the frame is updated.

As a matter of interest, it should be borne in mind that pure square waves cannot be modulated upon an RF carrier, since this requires an infinitely wide bandwidth for the transmission (whether AM or FM) and this is obviously a somewhat antisocial practice, which is remedied by passing the frame information through a low pulse filter before modulating the signal onto the RF carrier wave.

In this system, frequency modulation is employed since it offers better immunity from interference, and



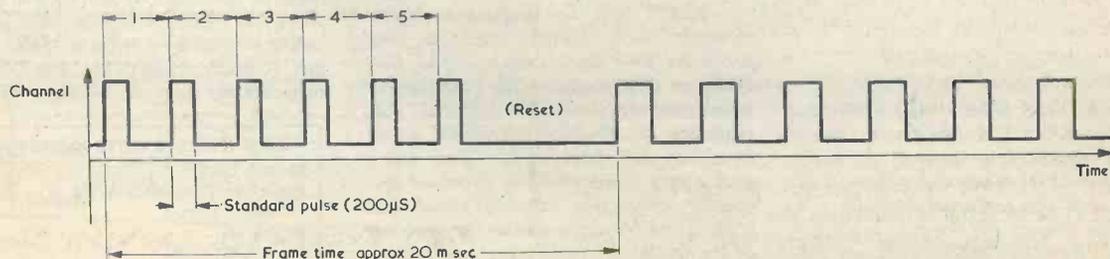


Fig. 1. The control waveform at the encoder output and decoder input.

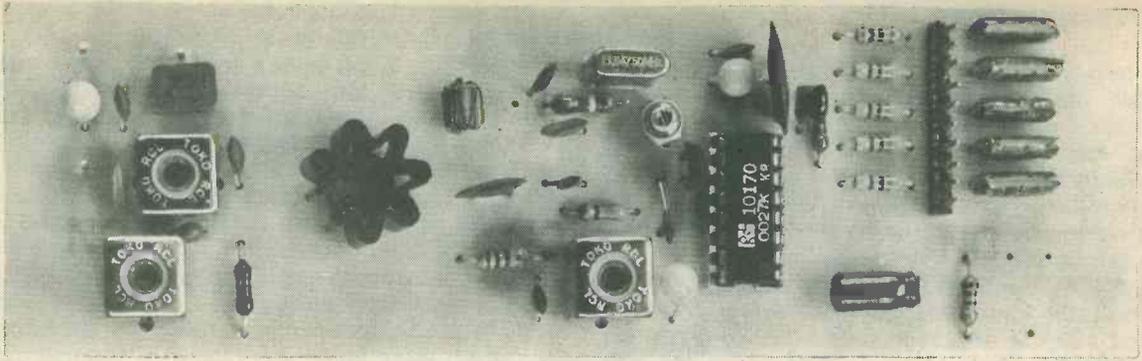

The completed transmitter board.
(Actual size)

Fig. 2. Derivation of the simple reset pulse on C13 of the receiver/decoder, i.e.

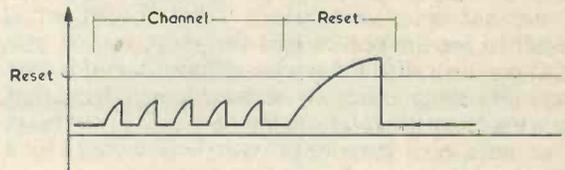

it is widely appreciated as being a more sociable medium in areas of dense activity since the nature of the transmission is not so drastically altered by the effects of different antenna loadings as can be the case with AM. Enthusiastically modulated AM systems have been known to occupy at least ten channels of the radio control band, and are thus perhaps not entirely suitable for amateur construction techniques. An incorrectly aligned FM system will simply produce bad results at the receiver, and it is thus self-evident without such severe effects on channel bandwidth. A grossly overmodulated AM system may still appear to be working perfectly from the point of view of the control of the model.

Fig.2 shows the signal as it arrives at the top of the reset capacitor on the receiver (C13) where you will see that the reset pulse is simply derived by waiting for the voltage on C13 to reach the reset threshold causing all the counters to be returned to the initial setting. If you have access to an oscilloscope, then you can view the demodulated frame at Pin 1 of the receiver IC, and this should look like the waveform in Fig.1. although the edges will be slightly rounded in accordance with the necessity to preserve bandwidth. The rounded edges are sharpened up before passing into the decoder. The composite information frame is decoded into the individual servo control pulses (Fig.3) where you will see that the individual servo pulses (between 1 and 2 milliseconds wide) are directed to the appropriate control mechanism. With a frame time of 20 milliseconds, the refresh period is such that the occasional "glitch" will be quickly covered by a subsequent information update causing no discernible effect on the controls.

ABOUT THE 'R&EC' SYSTEM

The 'R&EC' system is based on a pair of IC's from TOKO that contain virtually all the signal processing and encoder/decoder functions. Some external transmitter power amplification is required at the transmitter end, although for close range operation, the output from the integrated circuit on its own is adequate. The IC's have been designed to provide simple, repeatable and reliable operation in mass production, and thus they present an excellent opportunity for the erstwhile radio control constructor to re-acquaint himself with the state of the art.

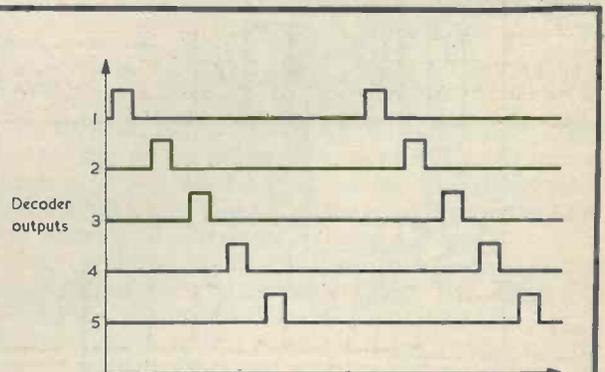


Fig. 3. Decoded output pulses to drive the servos.

THE TRANSMITTER CIRCUIT (Fig. 4).

The transmitter includes an encoder with five input facilities, fed from standard radio control stick assemblies – which can either be of the multi-axis or “preset” varieties. It is designed to be used with FM radio control crystals, which operate in the fundamental mode, on half the RF output frequency. The suggested load capacity is 20 pF, although other values can be used.

The ‘R&EC’ system uses 220kΩ control pots. The actual value to choose depends on several points:

- the amount of travel available in the control stick assembly.
- the ‘law’ (ie relationship between the travel of the wiper and the resistance value at the terminals) of the potentiometer, since some manufacturers use pots where the entire range of the resistance changes occurs over a much smaller arc than you would expect to find from ‘normal’ volume control type pots. In such cases, 220kΩ is too much, and a value of 22kΩ with 0.1μF capacitors is more suitable.
- the nature of the ‘trim’. This adjustment is essential to set the servos (via the pulse width) at a neutral position with the sticks ‘released’, and it may be accomplished either by a mechanical trim that adjusts the ‘neutral’ relationship of the stick-pot body and its shaft, or it may be provided electrically by a preset resistor in series with the stick pot.

The encoded signal modulates the FM carrier by simply switching TC2 across the crystal – which instead of the usual AM 3rd overtone type, is a fundamental cut at half the output frequency. This is because fundamental crystals can be ‘pulled’ much

further than the overtone types – with the frequency doubling, also doubling the deviation.

‘Deviation’ is perhaps a misnomer, since this is more accurately frequency shift keying (FSK) between two fixed frequencies approx. 2-3kHz apart. TC1 trims the basic centre frequency of the oscillator (used to set the higher of the two frequencies with the switching modulator turned ‘off’). TC2 then determines the degree of shift between the ‘on’ and ‘off’ periods of the modulator.

The signal from the oscillator is then fed into the IC’s doubler/amplifier at pin 14, with T1 providing the 27MHz selectivity and a suitable coupling link for the output stage amplifier transistor. Stopper resistors are used to prevent parametric instability, and render the output stage almost totally stable under any output loading conditions. (Unless you know different).

The collector load of TR1 has to perform one of the most trying tasks in radio transmitter design – namely matching the output to an ‘electrically short antenna’ (ESA). An ESA is basically anything much under a quarter wavelength, and matching is accomplished by considering the antenna as a series RC network to ground. The equivalent capacitance is given by:

$$C_a = \frac{1.42L}{((1n \times 2L/d) - 1) \times (1 - (fL/2808)^2)} \text{ pF}$$

where L is the antenna length in inches (sorry all you metric fans) d is the diameter of the antenna in inches

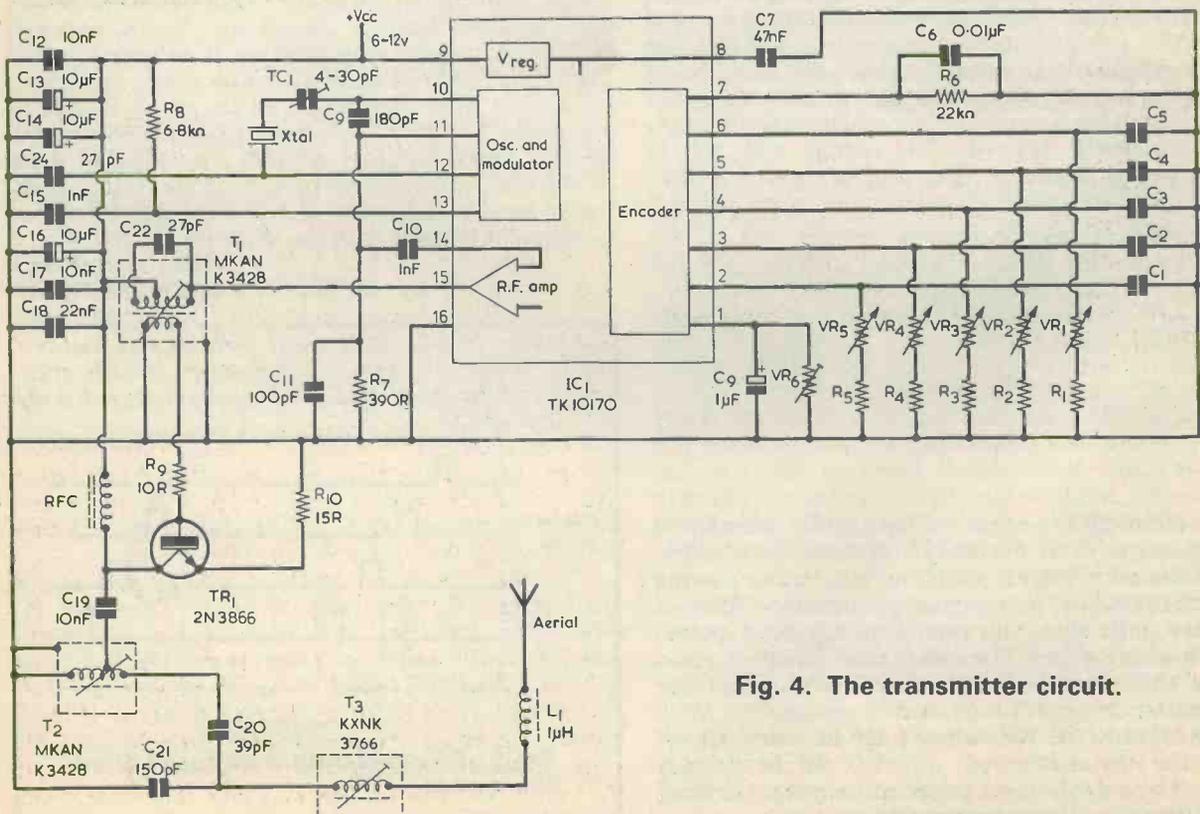


Fig. 4. The transmitter circuit.

COMPONENTS

THE TRANSMITTER

Resistors

(0.25w/0.33w carbon film 5%).

R1-R5 8K2
R6 22K
R7 390Ω
R8 6K8
R9 10Ω
R10 15Ω

VR1-5 220K Stick pots (SEE TEXT)
VR6 50K miniature preset

Semiconductors

IC1 TK10170 (TOKO)
TR1 2N3866/MRF472

Coils

T1 MKANK3428
T2 MKANK3428
T3 KXNK3766
L1 7BA1R0K 1μH
RFC 5 turns on FX1115 ferrite bead

Capacitors

C1-C5 22nF mylar/polyester
C6 10nF
C7 100n
C8 1u0 low leakage electrolytic or tantalum
C9 180pF ceramic
C10 1n0
C11 100pF
C12 10n
C13 10uF 16v electrolytic
C14 10uF
C15 1n0 ceramic
C16 10uF 16v electrolytic
C17 10nF ceramic
C18 22nF ceramic
C19 10nF ceramic
C20 39pF ceramic
C21 150pF ceramic
C22 27pF ceramic

Trimmer Capacitors

TC1/2 4-30pF foil or ceramic

Miscellaneous

Crystals: fundamental cut, 20pF parallel resonance at half output frequency
PCB, heatsink for output transistors, hardware, batteries etc.

f is the frequency in MHz
the equivalent resistance is given by:

$$R_a = 273 (Lf)^2 \times 10^{-8} \text{ ohms}$$

The radiated power from such a system is that power which would be dissipated in R_a if the antenna was replaced by the equivalent series RC circuit. By placing a loading inductor in series with the antenna, a series resonant circuit is provided that has essentially zero impedance at the transmitter frequency. And this is derived from:

$$L1 = \frac{1}{(2 \times \pi \times fc)^2 \times Ca} \text{ } \mu\text{H}$$

The circuit used here has a fixed 1mH coil in series with a 1-2uH variable at the capacitive tap point across the output 'tank circuit', which allows room to trim the loading inductance to suit a variety of antenna conditions. This capacitive tap also provides DC blocking to the antenna. The circuit should be aligned for best field strength as measured on a meter about 4-5 feet away.


The input to the RF output stage has been set for about 1W from a 9v supply, although the inefficiency of the relatively short antennas ensures that effective radiated power is rather less than half that.

THE RECEIVER CIRCUIT Fig.5.

The most important aspect of this version of the receiver is the fact that the unit employs a ceramic filter (CF1) at 27MHz that provides selectivity which equates to 2 or 3 RF coils. Whilst this is good news for 27MHz users, this means that although the whole system works at 35Mhz, the filter cannot be used, and thus the selectivity relies upon a single 35MHz RF coil. At 35MHz, there is virtually no image rejection - which may bother some users, although at that frequency, there is a great deal less scope for any interference on the image frequencies than is presently the case around the 27Mhz band.

At the start of this article, we did mention that this feature was aimed primarily at land and water based users, so if you want a receiver for 35MHz for airborne applications, wait until we cover that in the first few issues of *Radio and Electronics World*.

TR1 provides about 20dB of voltage gain and a good match for the ceramic filter. The main IC (KB4446) contains a balanced mixer at the input, which is really rather essential if the receiver is to have a sufficiently good overload performance to handle operation in an environment where several models are being operated simultaneously. The RF stages of an RC receiver cannot begin to separate the RF signal in such situations, and they all end up at the mixer input.

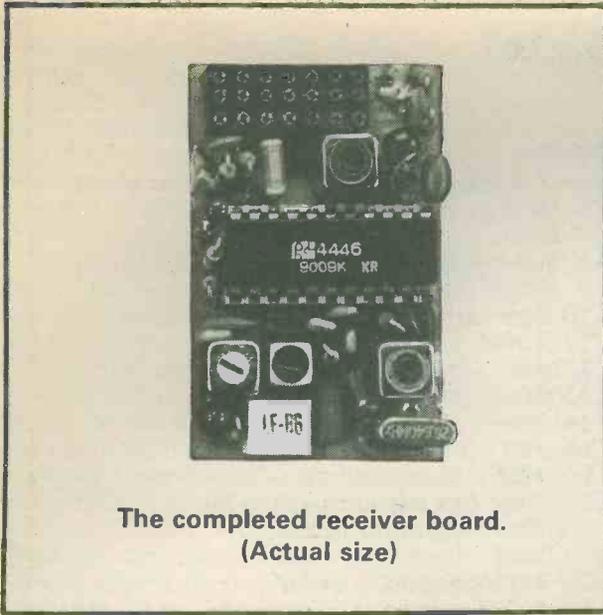

The completed receiver board.
(Actual size)

The channel selectivity (10kHz) is provided at the output of the mixer in the IF filter assembly at 455kHz (F1A and F1B). The combination of these two filters provides a low cost filter of excellent band-pass, with low weight and volume consumption. F1A possesses an excellent 'out of band characteristic', although the pass band (the 'close-in' response) isn't too hot. F1B is an exact complement, possessing a good pass band, but indifferent 'out of band' attenuation.

The mixer and IF stages of the IC closely resemble MC3357P (used in the VHF NBFM scanner feature in last month's 'R&EC'), but the oscillator of the KB4446 is designed specifically for parallel 20pf load, third overtone crystals. Pin 10 of the IC is the collector of the oscillator stage, and pin 11 is the base input to the same transistor.

The IF amplifier of the KB4446 has rather high input impedance to match the filter – and this means that it is prone to stray pickup if the layout isn't quite perfect. In fact, if you test the receiver using equipment connected to the mains with mains earth connections, there is a chance that you will be able to hear 909kHz medium wave broadcast stations getting through the works and being audible at pin 1, the demodulated output. This is a result of the imperfect nature of mains wiring at 'RF', since the detector operates at approximately half 909kHz (455kHz).

Most people who have fiddled with a crystal set in their time will probably have discovered that a cold water pipe makes a good antenna – although in terms of house wiring, this is essentially at the same potential as the mains earth. But don't for heaven's sake try connecting a crystal set to the mains earth unless your will is up to date, or you are very certain of what you are doing.

When battery powered and isolated from such things as cleverly disguised earth leads masquerading as MW antennas, the receiver is completely unaware of 909kHz.

The detector output is fed to a differential comparator (input on pin 21). This section provides a paradox in that its prime function is to remove unwanted fast edges, but at the same time to 'clean

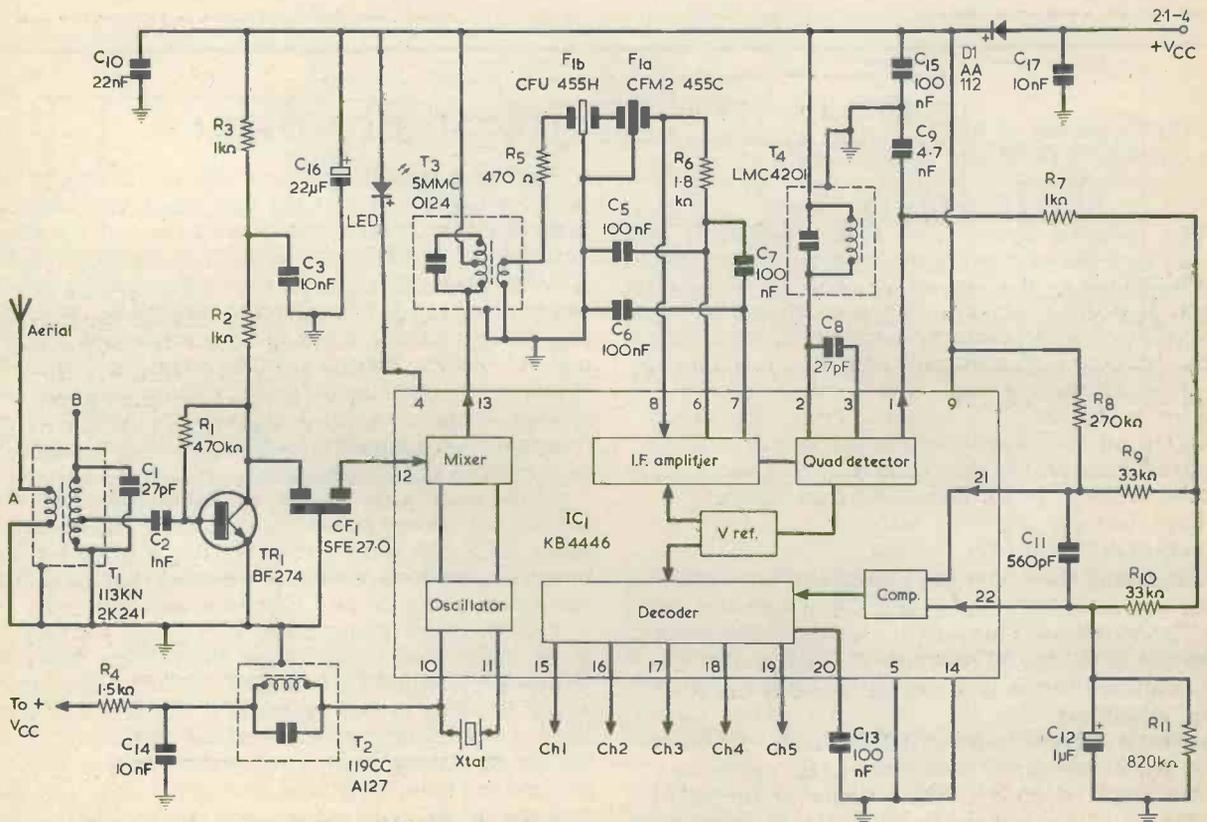


Fig. 5. The receiver circuit.

COMPONENTS

THE RECEIVER

Resistors

(0.25 or 0.125w carbon film)

R1 470K
R2 1K0
R3 1K0
R4 1K5
R5 470E
R6 1K8
R7 1K0
R8 270K
R9 33K
R10 33K
R11 820K

Semiconductors

IC1 KB4446 (TOKO)
TR1 BF274

Inductors

T1 113KN2K241
T2 119CCA127EK
T3 5MMC0124
T4 LMC4201

Capacitors

(all min ceramic disc/plate unless otherwise shown)

C1 27pF
C2 1n0
C3 10n
C4
C5 100n monolithic ceramic
C6 100n
C7 100n
C8 27pF
C9 4n7
C10
C11 560pF
C12 6v 1uF low leakage electrolytic
C13 100n mylar or polyester
C14 10n
C15 100n monolithic ceramic
C16 6v 22uF miniature electrolytic
C17 10n

Filters

F1a LFB6 (NTK)
F1b CFM455D (TOKO)

Miscellaneous

Case (SLM), servo connector block (SLM), PCB etc

NOTE all parts for this project are available either in complete 'kit form' or individually via the 'R&EC' reader services department, please send for details of the kit and prices.

up' and speed up the fast edges of the actual data stream. It provides a very effective noise filter by virtue of the R/C time constant on pin 22, but nevertheless this does not compromise the wanted edges of the data stream which enter the comparator unmolested by the RC roll-off. Spikes and other noises (in an environment where a number of high current DC motors are operating in servos, there are a good number of potential interference sources) are thus kept from passing to the decoder logic and causing false operation of the servos.

The decoder clocks along as the data arrives, directing the servo control pulses to the appropriate outputs. The frame reset occurs by checking the voltage on the top of C13, and resetting the decoder to the initial condition when this voltage exceeds the reset threshold voltage.

The servo outputs (pins 15-19) are collector loads of 20k, and if more drive is required (it isn't necessary with modern IC decoders), the outputs can be pulled up to the positive supply by the provision of an external load resistor of not less than 4k7 ohms on each output.

CONSTRUCTION

Fig. 6 (a) details the PCB design used for the transmitter. You can etch it yourself, or buy it ready made from the 'R&EC' (shortly to be 'R&EW', don't forget) PCB service. Fig. 6 (b) gives component position information. There isn't a lot to say about constructional technique, if you read electronics magazines at all, you will have had all the points to watch drummed in long ago.



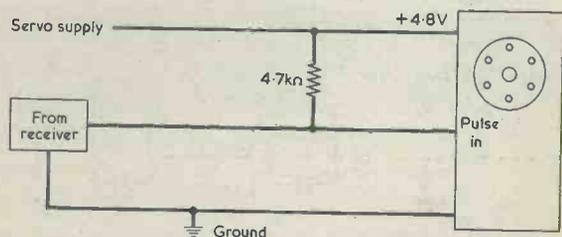


Fig. 6. Using a 'pull-up' resistor at the servo input in cases of marginal operation.

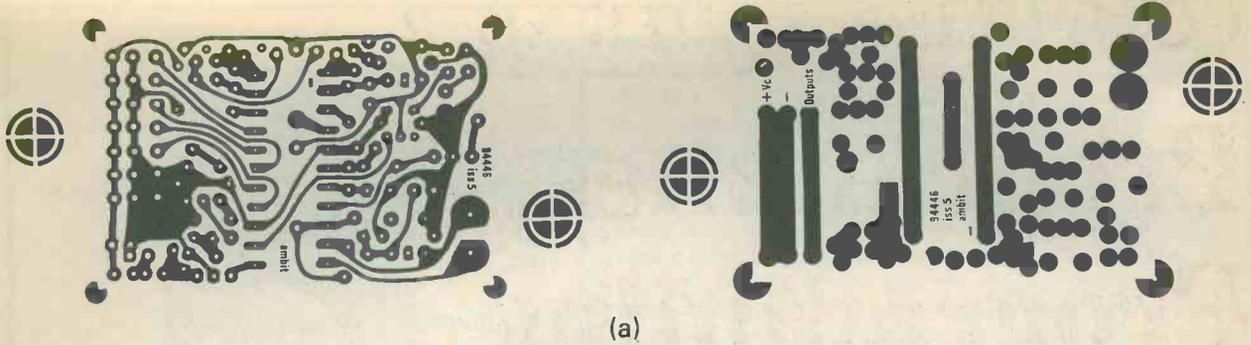

94446 RECEIVER OVERLAY

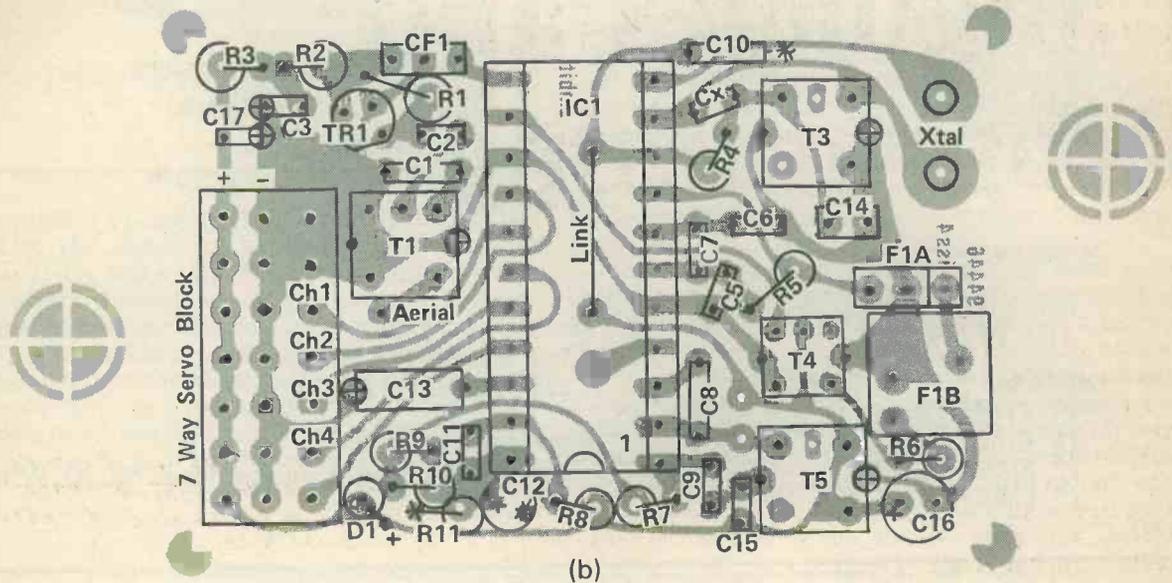

- ⊕ Solder to top and bottom of P.C.B.
- * Solder to top side only.

Fig. 7(a). Printed circuit board—actual size. (b) Receiver overlay.

Fig. 7 (a) shows the receiver PCB design (which is double-sided to save space), and Fig. 7 (b) shows the component overlay. Care must be taken to use the correct components, since there is absolutely no space to spare. An SLM servo connector block is used to provide the connection points for the servos and the power plug.

Further details of final assembly and alignment will

be given in the first edition of *Radio and Electronics World* on sale on or about September 3rd., but since we appreciate that some of you would prefer to get on with this during the summer months, an SAE to the publishers will bring you a copy of the remainder of the feature to enable you to complete the whole project in one instalment.

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 80p, inclusive of postage and packing.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

Programmes, Programming Languages and Programming

Any science as new as computing tends to generate a vast quantity of jargon, buzz-words, and 'in' phrases in an attempt to express new and radically different ideas. This jargon is extremely difficult for the newcomer to start to comprehend.

On the 'software' side of computing, you will be confronted with such words as BASIC, compiler, COBOL, assembler, macro, operating system (OS) monitor, machine code, interpreter, etc.

The task of understanding the implications and relations of these different words is daunting, and is not aided by unhelpful reversion into 'jargon' when many of these expressions and concepts are used, in fact they are quite simple to understand if approached in 'lay' terminology.

WHAT IS A PROGRAMME?

A programme is a set of ordered instructions stored in a readable form which may be read and acted upon by a controlling device.

This broad definition includes knitting patterns, washing machine controllers and computer programmes. It is fundamental to the concept of programming that a difficult and complex task can be subdivided into a number of sequential and simple steps - whether it be.

"knit 1, purl 1"

"turn the water on, turn the heaters on"
or "multiply A by B".

This ability to express complex ideas by limited numbers of fixed statements is something with which we are all familiar. The English language has only 26 such statements (the alphabet), and yet possesses a limitless ability to express concepts and ideas.

Microprocessors usually have between 100 and 400 simple built-in statements referred to as the "Microprocessors Instruction Set". All the programmes are then constructed from these basic instructions, in the same manner that words are constructed from the letters of the alphabet.

HOW PROGRAMMES ARE STORED AND READ

For a knitting pattern, the method of programme storage is one of decipherable marks upon paper. The programme is read by the moving finger of the human who is acting as the controller.

Having read one instruction and acted upon it, the finger moves on to the next instruction. In computing the finger which marks the current position of the controller (NB controlled device) in the programme is referred to as the "Instruction Pointer", or "Programme Pointer". In effect, the Instruction Pointer indicates where the controller must retrieve the next programme step from, having finished the current one. In the case of the washing machine controller, the programme is stored as a series of bumps and dents on the cam surfaces which operate microswitches connected to the motor, water solenoid and heater. In this example the microswitches are the instruction set, the cams are the programme, and the programme pointer is the angular displacement of the cam shaft.

In a computer or microprocessor the programme is stored within a semiconductor device known as a 'memory' chip. The memory chip contains a number of discrete locations which may be selected by the instruction or address counter of the microprocessors. Each of these memory locations can be set to a value which will cause the microprocessor reading it to execute one of the instructions from its instruction set. The value stored in the memory location thus tells the microprocessor which of the instructions to execute. The memory chip and its locations are filled with pointers to the instructions in the microprocessor's instruction set, and is analogous to the paper and marks of the knitting pattern, and the instruction pointer of the microprocessor is the moving finger.

PROGRAMMING LANGUAGES AND THEIR RELATIONSHIPS

Microprocessors are only capable of executing programmes written in terms of their built-in instructions sets, much as an English person cannot inherently read something written in Russian. All the programmes must therefore ultimately be translated into the processors native instruction set.

The steps of the instruction sets are very simple, and of the nature "add A to B", "read from a memory location", and "write to a memory location".

A programme presented entirely in the form of instructions from the processor's instruction set is known as a "machine code programme". Unfortunately, it is extremely tedious for humans to write in machine code, since it is rather like having to work out how to spell each word as you want to use it.

Nevertheless, many applications of simple computers rely on machine code programming, so a thorough understanding of it is fundamental to a complete understanding of computers – and computing in general.

To assist the machine code programmer, nearly all the computer systems contain a small machine code programme stored in a memory device known as the "Monitor Program". When the microprocessor is made to execute (read) the monitor program, instructions within it enable the human to locate and 'access' memory 'locations' within the computer's memory, and write a value into the memory representing the machine code step which the programmer wants the micro to execute.

This 'accessing' is carried out via some sort of computer 'terminal' – and the monitor contains programme steps which allows the micro to 'write' data to the terminal, and read data entered into the terminal by the programmer.

When the programmer has finished entering his programme into memory, he can instruct the microprocessor to go and 'read' (execute) his newly entered programme via the monitor programme. This method of programme construction and entering is really only feasible for very short programmes, such as those programmes of less than a thousand discrete steps.

In order that the programmer can be freed from the tedium of writing machine code programmes, there are programmes which help to write programmes.

These programmes are known as "programming languages".

A 'programming language' helps the operator to write 'programmes' by supplying a language which can be used to communicate with the computer using stock words, phrases and even sentences. Thus the effort changes from constructing one's own words, (and writing a dictionary as you go along), to that of stringing together the supplied words and phrases in the correct order.

The programming language creates a pseudo 'instruction set.' This pseudo instruction set is a lot more powerful than the simple inherent instruction set that is supplied with the microprocessor. Instead of instructions such as 'read from memory location', 'add A to B' – the programming language offers instructions such as:

"Print on the terminal A x B"

and

"Input from the terminal the value of A."

Examples of programming languages are BASIC, FORTRAN and COBOL. It should be remembered that these languages are themselves programmes, and are of course written in machine code.

Ultimately, these programmes convert the programmer's programme to machine code, much as a translator converts Russian into English, and then breaks the words down to the alphabet, or the basic 'instruction set'.

There is therefore a hierarchical relationship amongst programming languages, and the further from machine code a language is – the more power the pseudo instruction set has – allowing complete concepts to be expressed by a single 'pseudo instruction', or at least a small group of them.

As you can imagine, the more powerful the pseudo instruction set of a language, the greater the 'overhead' of converting a programme written in that language to machine code becomes. Thus a programme written in an advanced programming language runs more slowly than the same programme written directly in machine code, unless special techniques are employed, e.g. few bilingual English people read Russian as quickly as their own native tongue.

Next month we will begin to look at what machine code is, and how programmes can be 'structured' using it. ■

'BANGS AND BUMPS' AT BROADCASTING HOUSE

For the past few months workmen have been very busy carrying out repairs and modernisation at BBC Broadcasting House. The work, which will take two years to complete, will result in much needed improvements in the studios used by news and current affairs programmes. Contractors using special drills and saws have been engaged in cutting through a foot-thick re-inforced concrete chimney, and elaborate schedules were worked out to ensure that 'bangs and bumps' were not picked up by microphones in the studios.


The arrangements have worked extremely well with one notable exception – during a morning news

bulletin when the dulcet tones of Radio 4 newsreader Dilly Barlow were interrupted by the banging of a hammer two floors above the studio!

The latest mishap was of a less noisy though equally inconvenient nature. When a workman accidentally cut through a water pipe, part of the second floor became flooded so quickly that special equipment had to be rushed in by the House Services staff in order to prevent the whole floor becoming completely flooded! Fortunately, there was no need for the radio newsreaders to sit at their desks while the waters lapped around their ankles – they work on the third floor!

TRADE NEWS

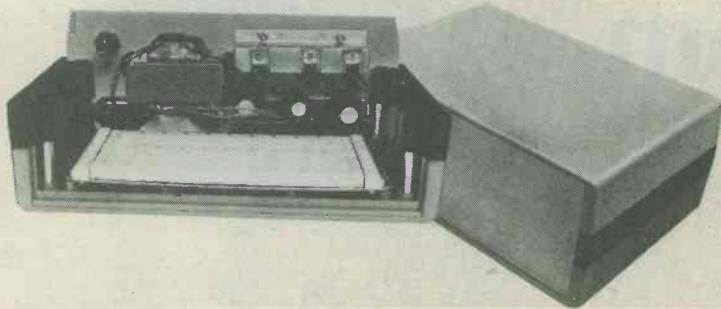IDEA BOX FROM GLOBAL SPECIALITIES CORPORATION



New prototyping aid combines circuit cards and power supplies in easy-to-use package

The Idea Box from GSC is a new concept in prototyping aids for electronic circuit design. Combining three fully regulated power supplies and three choices of circuit cards in a rugged plastic case, the Idea Box is designed specifically to offer the ease of solderless breadboarding systems to the user who wishes to construct a fully packaged 'one-of-a-kind' instrument.

The basic Idea Box system is an extension of GSC's Experimentor solderless breadboard concept, which allows designers to move from an initial breadboard layout to a fully finished circuit board in the minimum of stages. The Idea Box is available with a choice of a solderless breadboard (Model IDB - 100); a pre-etched, pre-drilled printed-circuit board which emulates the hole and connection pattern of the solderless breadboard. (Model IDB 102); or an unetched printed-circuit board that can be used for existing

printed-circuit board designs (Model IDB 103).

For added component capacity and circuit capability, any of three circuit cards can be stacked in any combination in the Idea Box. Additional cards of all three types are available, and other accessories include a blank aluminium front-panel replacement and printed paper pads which also duplicate the hole-and-connection patterns of the circuit cards.

The power supplies, which are mounted on the back plate of the Idea Box, provide three separate outputs: +5V d.c., 1A; +15V d.c., 0.5A; and -15V d.c., 0.5A. Line regulation is better than 0.15% at 1A output.

The Idea Box measures 178 x 254 x 102mm and weighs 625g.

Enquiries to Global Specialities Corporation, Shire Hill Industrial Estate, Saffron Walden, Essex.

BIB CHANGE COMPANY NAME

Bib Hi-Fi Accessories Limited, one of Britain's leading maker of products for audio and video care and maintenance, has announced that, with effect from 1st July 1981, it will be trading under the name of Bib Audio/Video Products Limited.

Bib, whose business growth coincided with the immense rise in popularity of hi-fi systems in Britain during the 60s and 70s, says the change in name better reflects the company's current trading interests and the development of the market over recent years, particularly the rapid growth in video despite the world economic recession.

Bib, part of Kelsey Industries, which includes Multicore Solders, was founded in 1954, and has established itself as the leading name in its market, not only in Britain but also in the United States where it began manufacturing and marketing its products in 1977.

The comprehensive range of Bib products for the care and maintenance of audio and video equipment is manufactured in the company's plant at Kelsey House, Wood Lane End, Hemel Hempstead, Herts HP2 4RQ.

Plessey Semiconductors wins Queen's Award

Plessey Semiconductors has won the Queen's Award for Export Achievement.

The award, given for outstanding export performance over three consecutive years, demonstrates the success with which the company has penetrated world-wide markets.


Ken Bradshaw, Marketing Director of Plessey Semiconductors said "I personally feel tremendous gratification at this recognition of our success in exporting to 45 countries. It demonstrates the realism with which the company has addressed the international marketplace over the past 7 years." He added: "Indeed, our growth is accelerating and, in the year just closed, exports have grown from 7½ to 10 million units. This continued growth, in a recession, should show the world, once and for all, that Plessey Semiconductors is not merely a high technology job shop!"

The company currently exports over 70 percent of production and its successes include selling integrated circuits for Japanese television receivers and military circuits to the USA.

A Scanning Monitor Receiver System

Part 2

L. Power

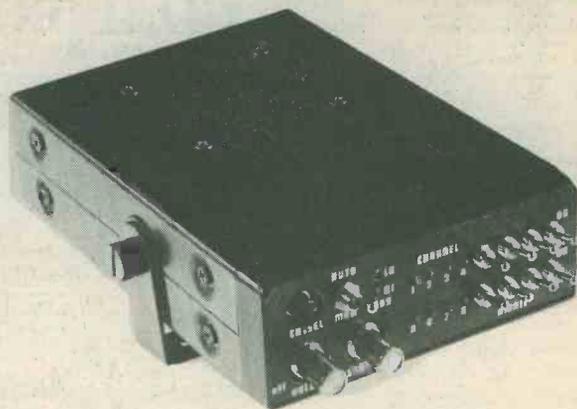

CONSTRUCTIONAL CONSIDERATIONS

The only practical solution to a circuit of this complex nature is to use a PCB derived from a 2:1 artwork, and photographic reduction. Fig.4 details the PCB foil pattern, which can be used for a direct photographic reproduction (beware the commercial copyright aspects). It seems unlikely that anyone should want to try to make a hand drawn copy – but if you have a steady hand and a good deal of patience, then the best way is to pin the layout on a piece of PCB, and use a centre punch to locate all the hole centres. Then take away the ‘template’ and join up the dots with a PCB etch resist pen.

Part of R&EC’s evolving range of reader services now includes a low cost photographic film positive master facility for selected projects (this is one of them), where you can obtain a film positive of the

PCB to enable those of you with access to a ‘Photolab’ or similar, to achieve perfect results on the more complex boards. Or failing this, you can go the whole hog and get a complete PCB from Ambit.


The component position overlay of Fig.5, identifies the positioning of the various components used. Between this and the circuit diagram published in part one, you should be able to locate the components with minimum difficulty. The only area for possible misinterpretation concerns the sections of the circuit that are connected via the flying lead terminations (display and lockout switch board, potentiometers etc.), and these items are shown as clearly as possible on the scale available.

Component identification should present few problems – except for items such as the coils, where a different coil type is used for the RF sections of the different frequency bands covered by this unit.


TABLE

RF range C3 = C5 = C5 = C8 = C10 T1 = T2 = T3
= T4 = T10 C4/C9


26-32MHz	Not required. . .	119CCA127EK . . .	2p2
32-40MHz	Not required . . .	199KCA314N. . .	2p2
40-60MHz	15 15 15 15	113CN2K159DZ . . .	2p2
60-80MHz	15 15 15 15	214SN10252N . . .	1p8
80-100MHz	10 10 10 10	214SN10252N . . .	1p8
100-130MHz	8p2 8p2 8p2 8p2	214SN10250X . . .	1p8
130-150MHz	5p6 5p6 5p6 5p6	214SN10250X . . .	1p5
150-170MHz	8p2 8p2 8p2 8p2	214SN10248X . . .	1p5

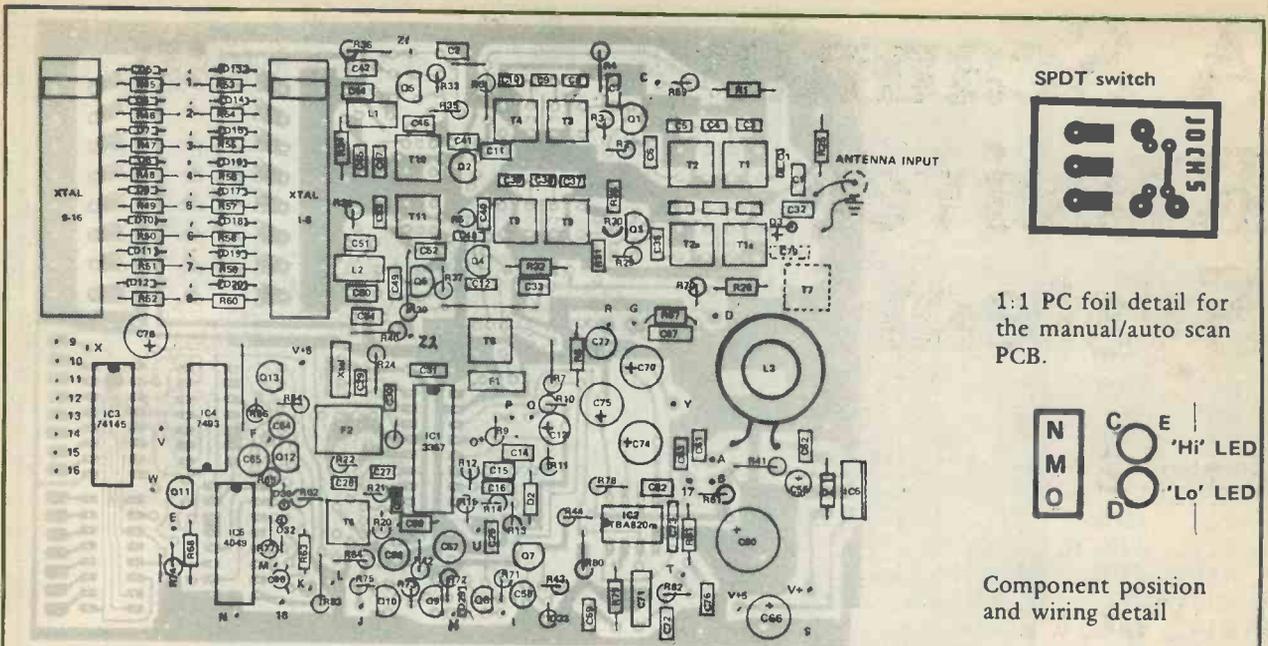

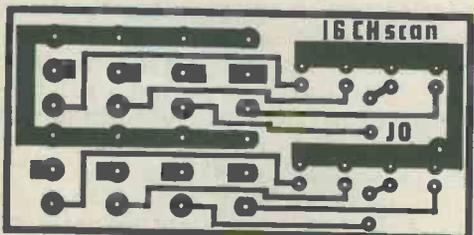
The numbered points on the PCB should be connected to the corresponding numbered point on the front panel PCBs.



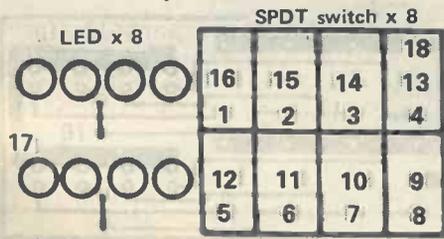
PC foil detail (1:1) for the lockout switch and LED front panel PCB



Component position and wiring detail

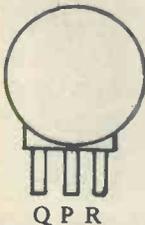

Mute control viewed from behind

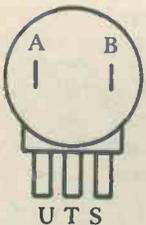

Volume control and ON/OFF switch

Interconnections:

- A ... Switch on volume control
- B ... Switch on volume control
- C ... 'C' on small manual/auto switch PCB
- D ... 'D'
- E ... 'E'
- F ... Channel advance push button
- G
- H ... Z2 (across board link)
- I ... Z1 (across board link)
- J ... V (across board link)
- K ... 'Delay' switch on back panel
- L
- M ... 'M' on man./auto switch board
- N ... N (across board link)
- O ... O (across board link)
- P ... Mute control.....
- Q
- R
- S ... Earth connection point
- T ... Audio from volume control
- U ... Audio to volume control
- V ... J (across board link)
- W ... X (across board link)
- Y ... Loudspeaker output
- V +5 ... V +5 (across board link)

Fig. 5. Component positions and layout. NB All overlays are viewed from component side with view of track through the PCB.

* The value of the coupling capacitor is given for approx 5-6MHz bandwidth. Increasing C4/C9 will increase bandwidth - but too much capacity here will cause the characteristic 'double hump' of an over-coupled circuit.

C46 and C52 (the oscillator tripler tank resonant-capacitors) should be approx 10% more than the C3 value for a given band.
For the second band, C37 = C39 = C3, in other words, duplicate the above values for the required second band coverage.

COMPONENTS

Resistors

* = Value changed in the course of optimisation

R1	3k3	R36	2k2
R2*	150k	R37	100k
R3	68E	R38	100E
R4	470E	R39*	210E
R5*	330k	R40	2k2
R6*	68	R41	10E
R7	120E	R42	
R8	33k	R43	
R9	47k	R44	
R10	100k	R45-60	2k2
R11	47k	R61	680E
R12	680k	R62	2k2
R13	2k2	R63	3k3
R14	18k	R64	33k
R15	8k2	R65	33k
R16		R66	2k2
R17		R67	330k
R18		R68	47E
R19		R69	680E
R20	33k	R70	680E
R21	47k	R71	33k
R22	1k8	R72	4
R24	100k	R73	4k7
R25	1k5	R74	4k7
R26	3k3	R75	
R27	1k0	R76	
R28	470E	R77	1M0
R29*	150k	R78	56E
R30*	68k	R79	120E
R31*	470E	R80	100k
R32	330k	R81	
R33	100k	R82	
R34	100E	VR1	100k + switch
R35*	210E	VR2	10k + switch

Capacitors

C1	10n	C39	see table
C2	10n	C40	1n0
C3	see table	C41*	2p2
C4	see table	C42	10n
C5	see table	C43	140p
C6	1n0	C44	68p
C7	10n	C45	10n
C8	see table	C46	see table
C9	see table	C47	10n
C10	see table	C48	2p2
C11	1n0	C49	150p
C12	10n	C50	82p
C13	1u0 - low leak	C51	10n
C14	10n	C52	see table
C15	470p	C53	10n
C16	470p	C54	10n
C17		C55	3u3
C18		C56	47uF
C19		C57	47uF
C20		C58	10uF
C21		C59	47n
C22		C60	1000pF
C23		C61	47n
C24		C62	47n
C25	22n	C63	10n
C26	10pF	C64	1u0
C27	47n/100u	C65	1u0
C28	47n/100u	C66	100uF
C29	120p	C67	47n
C30	47p	C68	2u2
C31	47n	C69	
C32	10n	C70*	1000uF AF/OP
C33	10n	C71	47n
C34		C72	22n
C35	1n0	C73	
C36	10n	C74	
C37	see table	C75	
C38	see table		

X Tals

X1 10.245/30pf 11
channel Xtals -
series resonant 3rd O/T FRF -10.7

3

Coils

L1
L2
L3 100t 36 SWG
T1 see table
T2 see table
T3 see table
T4 see table
T5* 119LC30099N
T6 LMC4200 or LMC4201
T7 not used (10.7mm trap)

T8 see table
T9 see table
T10 see table osc tripler
T11 see table osc tripler
T12

Diodes

D1 BA244
D2 0A91
D3 BA244
D4 1N4002
D5-D20 1N4148
D21-D28 1N4148
D29 1N4148
D30 1N4148
D31/2 LED
D33* 1N4148

Filters

F1 10M15A
F2 LFH 8/CFW445F

ICs

IC1 MC3357/MPS5701
IC2 TBA820M
IC3 74145
IC4 7493
IC5 78L05
IC6 4049
IC7

Transistors

Q1 BF594
Q2 BF594
Q3 BF594
Q4 BF594
Q5 BF594
Q6 BF594
Q7 BC238
Q8 BC308
Q9 BC308
Q10 BC238
Q11 BC238
Q12 BC238
Q13 BC238
Q14

Misc.

Micrometals T40/26
Xtal sockets
DC power jack

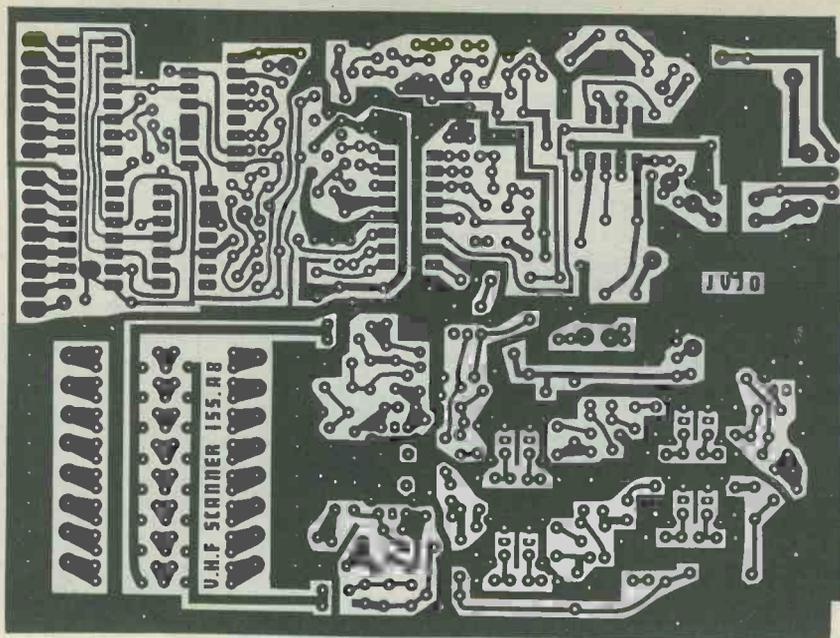


Fig. 6. Foil layout.

CHOOSING THE BANDS

The top coupled RF circuits are consistent in terms of the value of the L/C combinations regardless of the position in the circuit. It may be necessary to clip the centre pin from the base of the RF coils, since some of the above coils are supplied with primary taps that are not required – and could accidentally make contact with the ground plane of the PCB.

The coils for the LF bands are complete with internal capacitors.

CONSTRUCTION

First get your PCB. The author's basic philosophy is to fill as many of the holes as possible with larger components, so that the scope for incorrect insertions of the simpler items such as Rs and Cs is reduced. Things like the IC sockets (make certain pin one is the right end) should be fitted – Zetronix low profile types are probably best, since they are small (important in this layout), forgiving (unlike common TI low profile types which don't like being bent 90 degrees and then returned), and really tight contacts.

The ceramic filters, coils, and crystal holders should be fitted next. If you are concerned about 'progressive' checking, then work backwards from the loudspeaker. Fit all components associated with the audio stage, and then plug in a loudspeaker, apply 12v (remember L3 in supply noise filter) and place your finger on the audio input at pin 3 of IC2. There will be a buzz in the speaker if all is well so far, and quiescent current will be about 10-12mA with no signal.

Switch off, having acquired the first instalment of our sense of achievement, then complete the circuit around IC1 (the main IF system). The power supply voltage at the emitter of Q7 should be checked before inserting IC1 into its socket – assuming 8-10v, fit the

IC and switch on. There should be a hiss in the speaker, which changes dramatically as you place your finger near pin 16 of IC1. If you put a piece of wire about 12 inches long on to pin 16, it will act as an antenna and you will hear a load of miscellaneous HF mush from the output. If not, turn the squelch (mute) control Vr1 until the squelch drops out. If nothing happens when doing this, disconnect one end of R14 to prevent the mute amplifier from getting any input, and if there is still nothing, check the component positioning, soldering etc.

The RF, oscillator and first mixer stages are not so easily isolated for progressive testing. Insert the remaining components, check the whole assembly carefully, and prepare yourself for the most tricky part of the operation thus far.

TESTING THE COMPLETE UNIT

First things first, check the current consumption is reasonable (ie between 20 and 50mA). Rather than be defeatist plug in a crystal (or two) and with the mute open (ie noise coming out of the speaker), step the selector along to the crystal position in use. If you have a GDO or similar, you can check to see if anything is happening at the oscillator coil – if not, you will have to rely on a signal generator for your source, or a local strong signal on a known frequency.

If the logic is not selecting the correct crystal and RF section, then check the wiring and component positioning very carefully. There is no scope for any shades of grey here – either it works or it does not. If it does not, the easy mistakes are wrong transistor types (mixed up NPN/PNP – if you use AEG BC308s for the PNP types, you will notice these have a white painted stripe along the top to help easier identification). The band indication LED only lights up when

the scanning stops – or the mute is held open. During mute closed conditions, the channel LEDs will step along in sequence until halted.

With the characteristic hiss in the loudspeaker, turn the core of T6 (the detector) until the hiss suddenly changes from being broken and crackling, to a 'balanced' white noise. If you check the DC voltage at pin 9 of IC1 at this point, you should find it settles about midway between the supply voltage and ground when the noise sounds 'cleanest'. This is because the DC offset condition when the detector is not correctly aligned down the centre of the IF passband causes the noise to limit 'hard against' the supply rail, creating the characteristic clipped sound.

Those of you with the means of more precise alignment probably do not need any instruction in their employment for this task.

With your signal source to hand, set this to the expected RF frequency, and turn the output of the generator up until some sounds are heard in the speaker. If you do not have an FM source (ie you are relying on a crystal oscillator for alignment) then tune all the cores of the RF and oscillator stages for best quieting, whilst progressively decreasing the signal at the input.

Start with the oscillator coil T10/T11. If you can get absolutely nothing, then check to see that the crystal is selected by measuring the voltage at the appropriate output of IC3, and that the oscillator has been selected by the high/low select circuitry by checking to see that collector volts are present on the appropriate oscillator stage.

Still nothing? Then try and measure the frequency of the oscillator by capacitive coupling (5-20pF) into

a reasonable HF DFM, do the sums on the multiplication ($x3 + 10.7$) MHz, and see if this corresponds with your expectations from the value stamped on the crystal. It should not be more than a kHz or two out. If it is a couple of kHz HF of expectations, you can solder up to about 30pF across the crystal base (track side of the board) to trim it onto channel. Take care where you measure the crystal frequency (the collector of Q5/6 seems best), since the loading of the DFM probe would make a small difference on the base of the oscillator.

You probably won't be able to measure the tripled output directly, since the presence of the basic 3rd OT frequency will tend to 'capture' the DFM. All well and good if you can. A simple absorption wavemeter could be constructed for the injection ($x3$) frequency, and this can be coupled into the secondary of the oscillator tripler coil to provide a means of peaking the LO injection frequency in the absence of any other signals.

When you have established success at the oscillator, and you still don't have any sound at the output to assist in the trimming RF stages, then check for daft things, like reversed transistors, diodes, solder bridges, capacitors where the pF and nF markings have been swapped over.

If you still haven't got anything to go on, then the best thing is to try and get access to a suitable piece of test gear. R&EC's new constructor services department may be able to help in cases of dire need, but this is strictly for equipment that has been correctly assembled and is working from the 10.7MHz IF on IC1 to the loudspeaker, where no specialised equipment of any sort is required to achieve progress.

MANUFACTURER SWITCHES TO CIBA-GEIGY'S MELOPAS

Ciba-Geigy's Melopas moulding compound has recently been selected for the manufacture of miniature circuit breaker housings after a detailed examination of several materials.


MCB Lupus of Winsford, Cheshire, who produce the "Midget" circuit breakers for incorporation into electrical distribution equipment, chose the Ciba-Geigy compound during a general review of moulding materials used by the company.

BEST COMBINATION OF PROPERTIES


The company had previously used a wood-filled urea-formaldehyde resin for the moulding. They therefore required a material that would offer the same or better mechanical, electrical and thermal properties with advantages in costs and/or moulding characteristics.

After looking at many materials, including a detailed survey of three or four materials, MCB Lupus chose Melopas MPL. This offered the company the best balance of cost, production speed and usability and also provided more scope for future development in the company's products.

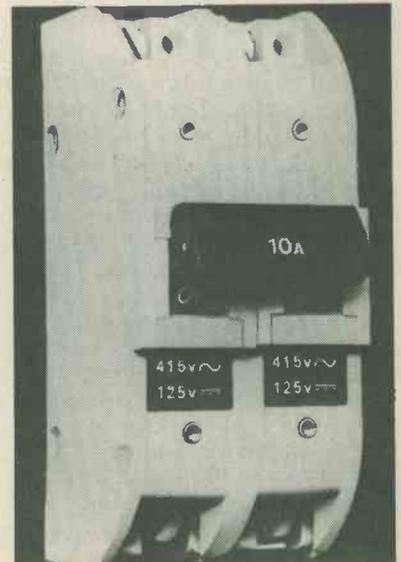Melopas moulding compounds are a range of phenol-modified melamine resins available for compression, transfer or injection moulding. All offer good mechanical and electrical properties, good resistance to surface cracking and low water absorption. Melopas MPL has a track resistance of class KA3b/KA3c (DIN 53480) and an arc resistance of 120-130s.



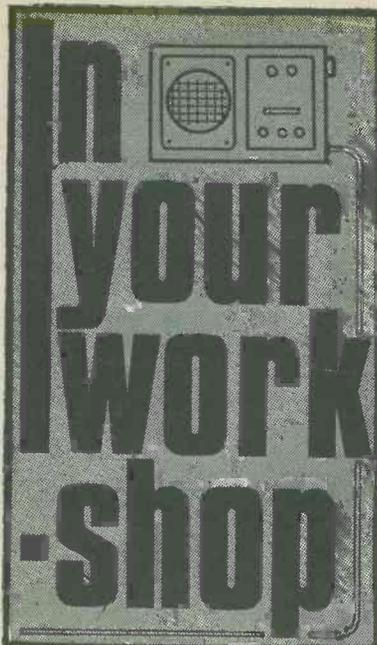"Midget" circuit breaker produced by MCB Lupus of Winsford, Cheshire using Ciba-Geigy's Melopas MPL.



A New Recruit

SMITHY GETS CRACKING ON TRACKING AND TRACKS DOWN THE CRACKLING

"Cripes!" yelled Dick as he leapt back from the window. "It's alive!"

"Well don't touch it then," muttered Smithy unsympathetically, and continued scrutinising the job on his bench.

"Well I'm blowed, it's you, you little perisher," Smithy heard Dick expostulate. Smithy maintained that if someone survived an electric shock well enough to shout about it and then go on to remark about the problems of life, then there couldn't be too much damage done.

However, after a moment or two he turned away, not unthankfully, from the problem-ridden colour TV on his bench. He'd spent several unsuccessful minutes looking for the cause of a persistent but intermittent crackling on the sound.

"What's alive?" he asked, and looking at the small portable radio spread open on Dick's bench added, "You *can't* get a shock from that!"

But Dick wasn't listening, he had now opened the window and was leaning far out, "Come here you!" he exclaimed.

Smithy was again surprised by Dick's abrupt manner but then grinned broadly when Dick re-appeared holding a small tabby kitten.

"Of course its alive," chuckled Smithy.

"Well I meant the aerial actually," said Dick sheepishly. "I opened the window to look at it and it suddenly moved and frightened the wits out of me, but it was only this little chap playing with it out on the roof."

Smithy glanced at Dick's so-called aerial, which was simply a piece of flexible wire run out through the window and strung up to a nearby gutter. A temporary lash-up years ago, it had survived both Smithy's scorn and the gales which had brought down trees in the local park.

"Why the interest in this – er – aerial?" queried Smithy.

"I thought it was shorting to earth or something," explained Dick hurriedly, "I was getting this intermittent crackling noise."

Smithy peered at the small radio on Dick's bench. It was a cheap 'tranny', almost certainly of Far Eastern origin, which wouldn't normally be worth the cost of any repair work.

Dick looked somewhat flustered. "It belongs to a mate at college," he explained and added, "It's rather deaf and I said I'd look at it for him if I had time today." Smithy was silent and Dick continued, rather embarrassed, "I hooked on my aerial to try to get something

out of it but all I'm getting now is this 'crackling' which I thought was the aerial." Dick's voice tailed off. "I think he's been fiddling with it," he added and fell into silence.

"Perhaps it would like a saucer of milk," said Smithy.

"Eh?" said Dick, then as the penny dropped he seized the chance to change the subject and added hurriedly, "oh yes – yes could be. Yes its been hanging around for a couple of days now, it does look half starved." Dick lifted the kitten carefully in one hand. "There's nothing of it," he concluded.

Smithy poured a little milk into the workshop's only saucer. "See if he'll drink that," he said. "He's very small. Only a few weeks old by the look of him. Probably unwanted and abandoned."

The kitten sniffed the air as Dick put him on the floor near the saucer and our two heros grinned broadly as the kitten lapped hungrily.

"Well he's enjoying that," said Dick and before the kitten had finished he topped up the saucer to the brim. The kitten continued without a pause, but after a while and with the saucer still nearly full, it looked up, licked its whiskers and moved away to explore the new surroundings.

"Its got the right idea," said Dick brightly. "Its been a busy

afternoon – lets have a break. I'll put the kettle on."

Dick busied himself with the tea things and Smithy wandered back to Dick's bench where the deaf 'tranny' lay. "You say you think he's fiddled with it," he remarked non-committally.

"Yes," said Dick cautiously. "The IF was say out. I've re-aligned that but its still fairly deaf."

"Probably disturbed the tracking too then," said Smithy and picking up Dick's aerial between thumb and forefinger and with an exaggerated gesture of distaste he put it to one side adding, "but you shouldn't need *that*."

Dick came over, stood alongside Smithy and explained, "I've tried moving the aerial coil on the ferrite rod, but I can't seem to get it right. It still seems deaf over most of the band."

"Well we've had a good day so far," said Smithy resignedly, "so lets have a go at 'tracking' this 'foreigner'."

Dick ignored Smithy's sly dig at his 'home service' job and said, "I'm not really sure how. It's a Medium Wave only set so I guess it ought to be dead easy."

Smithy took his note pad off the shelf and started to sketch a circuit (Fig.1). "It helps to understand a little about what 'tracking' is," he said as he finished his sketch. "All these sets are basically similar," he explained. "They have a self-oscillating mixer as the first stage."

"Sounds like two for the price of one," commented Dick.

"Sort of," said Smithy. "The signal from the ferrite rod aerial is the received frequency which in this case is within the Medium Wave band. The oscillator generates its own frequency about 465kHz higher than the received frequency and the difference between them is the 465kHz intermediate frequency."

Smithy paused as Dick frowned slightly. "The difference between them?," Dick said uneasily.

"Yes," explained Smithy. "You see this oscillator has two signals being mixed together

at its inputs, the Medium Wave frequency on its base and its own frequency on its emitter. And since its working hard as an oscillator it is operating non-linearly and so it also produces the sum and difference frequencies at its output by 'mixing'."

Dick looked at Smithy. "You didn't mention this 'mixing' when you explained about non-linear resistors," he said accusingly.

"That's because with the non-linear resistors we were dealing with dc," explained Smithy. "Even if we had used ac the non-linear effects are due to temperature changes and are far too slow to be considered like this."

"Okay," said Dick, "but perhaps you would explain the idea of 'mixing' some time. But what does this have to do with 'tracking'?"

Smithy was pleased to leave, the subject of mixing for the

present and said, "the intermediate frequency amplifier includes filters to *select* just this difference in frequency which is usually about 460 to 470 kHz, and to *reject* the other frequencies which come out of the mixer. So we need to ensure that we keep this difference between the tuned input frequency and the oscillator frequency constantly equal to the fixed intermediate frequency."

"But its automatic," objected Dick pointing to Smithy's circuit. "The two variable capacitors are both joined together – mechanically I mean!"

"Yes," agreed Smithy, "the tuning capacitor certainly has two sections on one shaft, but even then its almost impossible to tune two circuits over two separate frequency ranges and still keep the difference constant."

Smithy carefully drew a

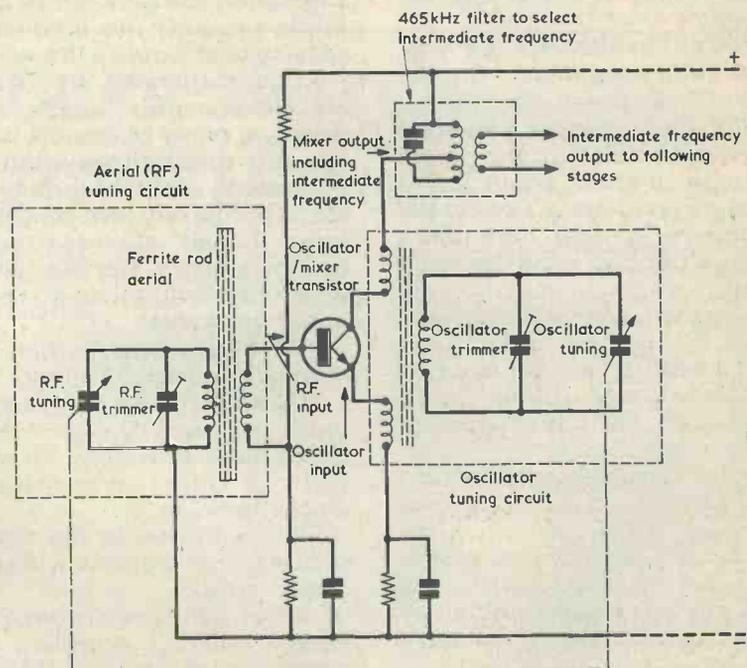


Fig.1. Smithy's sketch of a simple Oscillator/Mixer stage shows the first important sections of Dick's 'tranny' superhet radio. The variable capacitors are 'ganged' together and each has an additional trimmer capacitor to help with the 'tracking'.

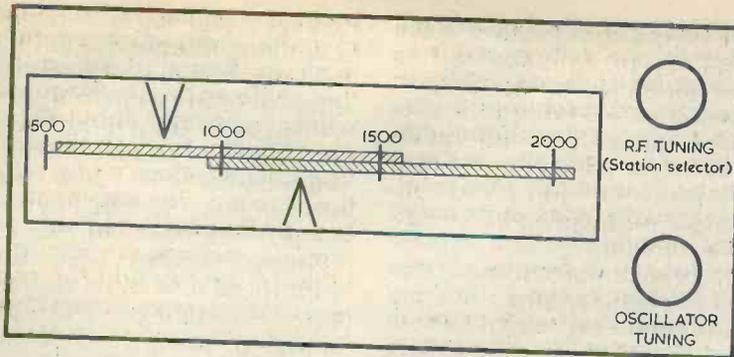


Fig.2. Smithy's idea of the tuning arrangements for a hard-to-tune superhet which nevertheless could achieve perfect tracking. The top pointer is set to select the station. The bottom pointer is then set to be 465kHz higher.

sketch to illustrate his point (Fig.2).

"If radios had two scales and two tuning controls, we could first tune the received signal to the station we want, and then we could adjust the oscillator frequency to be exactly 465kHz higher, so that the IF amplifier could get the signal and do its job."

"Thank goodness we don't have to do that!" snorted Dick. "My uncle Sid would never find the 'Archers', poor chap!" Smithy wondered if Dick's uncle's penchant for Radio 4's time honoured soap opera was the reason why Dick's family always laughingly referred to him as 'Silly Sid', but dismissed the ignoble thought and continued with his explanation.

"No," said Smithy, "we don't have to do that because we put the two tuning capacitors onto the one spindle. But," he continued, "we still can't keep the frequency difference constant unless we are very careful with the choice of inductance-capacitor ratios for each circuit."

Smithy switched on the workshop's very dusty old pocket calculator and pointed again to his second sketch (Fig.2). "You see the Medium Wave goes from about 1620kHz down to about 520kHz which is a frequency span of

1100kHz. Now, to give the correct Intermediate Frequency of say 465kHz, the oscillator *must* tune from 2085kHz down to 985kHz which is the same frequency *span*. But look, while the frequency *span* is the same, the *ratios* of the top and bottom frequencies are *different*. For the RF, that's the signal from the ferrite rod, the ratio is 1620kHz to 520kHz which is 3.12:1 while for the oscillator the ratio of the maximum to minimum frequencies is 2085kHz to 985kHz or only 2.12:1. So the tuning capacitors must have not only different maximum to minimum *values* but also different *ratios* and therefore the tuning 'laws' will be different."

"How do you mean 'the tuning laws' will be different?" Dick asked as he grappled with the concept of tuning capacitors slowly moving round, with pointers moving over scales and frequencies falling in unison.

"What happens is that you may start at one end with a frequency difference of 465kHz, and you may even finish at the other end with the same 465kHz difference, but in between the difference may well increase or decrease or first go one way and then the other..." Smithy's voice trailed off. "It's difficult to make them both keep in step you see," he finished.

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply:

Radio & Electronics
Constructor Data Books
Panel Signs Transfers

Also a postal service

PEATS

the world of electronics

25 Parnell Street, Dublin 1. Tel 749972

THE

MODERN BOOK CO.


Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET

LONDON W2 1NP

Tel: 01-402 9176

MORSE MADE EASY

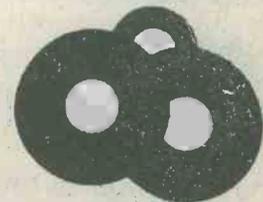

BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.

Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750gram). Details only s.a.e.

THE G3HSC MORSE CENTRE

S. Bennett, (Box 8), 45 Green Lane, Purley, Surrey.

Name

Address

GAREX

RESISTOR KITS new extended range at old prices: E12 series 10Ω to 1M, 61 values, 5% carbon film, general purpose ratings ½W or ¼W (please state).
Starter pack 5 each value (305) £3.10
Standard pack 10 each (610) £5.55
Mixed pack, 5 each ½W plus ¼W (610) £5.55
Giant pack 25 each (1525) £13.60
NICAD RECHARGEABLES physically as zinc carbon: AA(U7) £1.30, C(U11) £3.35; PP3 £5.55.
 Any 5+: less 10%; any 10+: less 20%.
VHF FM MONITOR RECEIVERS
HF 12 POCKET SIZE 12 channel xtal controlled, 4MHz bandwidth in range 130-174MHz. With nicad & charger. £57.95 Xtals extra, see below.
SOUNDAIR 008 PORTABLE SCANNER 8 channel xtal controlled. Nicad, charger. £59. Xtals extra.
SR-9 top selling monitor: 2m FM with 144-146MHz full coverage VFO, plus 11 xtal controlled channels, ideal for fixed or mobile listening. 12V DC operation. £47.50. Xtals extra.
MARINE BAND SR-9, 156-162MHz £47.50.
CRYSTALS FOR HF-12, NR-56, SR-9, SOUNDAIR 008, TM56B: all 2m channels in stock from 0(145.0) to 32(145.8) at £2.46 (plus 15p post). Over 40 popular marine channels at £2.85 (plus 15p post). See list.
AMPLIFIER MODULE new, fully assembled 6W IC unit, 12V DC. Low impedance (4-8:.) input & output for extn. speaker amplification, with circuit £2.75
CO-AXIAL CONNECTORS & ADAPTORS see list
 PL259 UHF plug plus reducer 75p;
 SO239 UHF socket panel mtd. 60p;
 2xSO239 Inline coupler £1
 2xPL259 Inline coupler £1
 Co-ax fitting - any 5+: less 10%
MAINS P.S.U. 12v 1A regulated. British made by GAREX £15.95.
 Main distributor of Revco aeriels and special products.

Access - Barclaycard

PRICES INCLUDE UK POST & VAT
 CALLERS BY APPOINTMENT
 GAREX ELECTRONICS
 7 NORVIC ROAD, MARSWORTH.
 TRING, HERTS HP23 4LS
 Cheddington (STD 0296) 668684

RADIO & ELECTRONICS CONSTRUCTOR

ANNUAL SUBSCRIPTIONS

to this magazine may
 be obtained through
 your newsagent or
 direct from the
 publishers



INLAND £9.50
 OVERSEAS . . £10.50
 per year, post free



Please send remittance with
 name and address and
 commencing issue required to:

**DATA PUBLICATIONS
 LTD**
 57 Maida Vale, London
 W9 1SN

Smithy sketched a simple tuned circuit and added two extra preset capacitors, (Fig.3). "If we add a 'trimmer' and a 'padder' to each tuned circuit we can arrange to alter the tuning laws so that they keep more 'in step'. We can even make them be perfectly 'in step' in two, three or more places over the tuning range." Smithy straightened-up and took a deep breath. "Do you follow that?" he asked. While Dick digested this information and pondered over Smithy's sketches, Smithy poured the now well-boiled water over the fresh tea leaves in the tea pot.

"Er - yes," said Dick after a long silence, "but I never realised it was so complicated, this 'tracking' business."

"Oh, this is only the start . . ." But Smithy stopped himself. "Some other time," he said, "I'll tell you about multipoint tracking in communications receivers. That's when you need to really understand trimmers and padders, and you'd give your right arm for a small computer." Then turning again to Dick's bench he added, "but this 'tranny' should be fairly straightforward. *Much* easier in fact."

"Firstly," Smithy instructed "tune in a station near the low frequency end of the band."

"That's easy," said Dick, "it seems quite lively down there."

"Probably because you've been adjusting the coil,"

remarked Smithy.

"Now move the aerial coil along the rod to get maximum signal and then tune to the high frequency end."

"That's where its deaf" explained Dick.

"You've probably adjusted the coil on the ferrite rod and not adjusted the aerial trimmer," said Smithy.

"Which one is that?" asked Dick.

"Well you'll have to trace it on the pcb," said Smithy.

"There's no band switching to complicate things so just look for the trimmer which is across the aerial tuning capacitor. It's probably on the main body of the tuning capacitor itself."

"Oh *those*," said Dick, "I try not to touch those if I can help it."

"Well when you've identified the aerial trimmer try adjusting it carefully," persisted Smithy.

"Suppose we're not tuned to a station?" said Dick.

"Don't worry you'll hear the background noise increase - even that blooming crackling will get louder - there!"

Sure enough as Dick slowly turned the trimmer the radio seemed to come to new life.

"Now you should repeat that operation once more," said Smithy. "Go back to the low frequency end, adjust the coil position slightly to improve the signal level and then come back to the 'top' end and retweak the trimmer. Twice at each end should be enough."

Dick was amazed. "That's all there is to it?" he asked, rather surprised.

"For a simple one band receiver, yes," said Smithy.

"Now if it had a Long Waveband as well, the band switching would switch in a different coil on the ferrite rod and some extra fixed capacitors and trimmers across the aerial and oscillator coils." Smithy paused and set two tea cups alongside the teapot.

"You set up the Long Waves in a similar way to the Medium Waves," continued Smithy. "First adjust the coil on the ferrite rod for maximum signal level at the low frequency end, at about 160kHz, then tune to the top end, about 270kHz and set the trimmer, again for maximum signal. Repeat once more and there you are!"

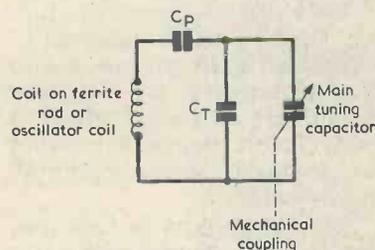


Fig.3. Smithy sketched a simple tuned circuit and added two extra preset capacitors . . . Cp is the 'padder' which can effectively reduce the maximum value of the main tuning capacitor. Ct is the 'trimmer' which can effectively increase the minimum value of the main tuning capacitor. By adjusting Cp and Ct the overall tuning range can be altered.

"You said the Long Wave circuit used *extra* capacitors," mused Dick. "Won't the Medium Wave adjustments muck up the Long Wave?"

"Not if you do the Medium Wave first," replied Smithy. "Get that right first and then do the Long Wave."

"Sounds straightforward," said Dick.

"It's not too tricky," agreed Smithy, and added, "but you could take two or three days to track up a multi-band communications receiver." And Smithy remembered briefly some frustrating days which he had spent, many years ago, as a new recruit at his RAF training camp, juggling the settings of waxy trimmers and padders. That was when he had first met John Davies who was to be a lifelong friend and the news of whose recent death had so saddened him.

Smithy's private thoughts about his old friend were suddenly interrupted by his present younger and more explosive company.

"Well that'll please him!" exclaimed Dick as he loudly snapped the back of the case into place on the now squawking 'tranny'.

"You've probably done yourself no favours," commented Smithy. "Once word gets around your crowd at college."

"Oh well," said Dick philosophically, "that's the name of the game."

"Speaking of names," Smithy nodded towards the kitten, "what are you going to call him?"

"He did *me* no favours by playing 'chase' with my aerial," mused Dick. "Properly led me down a false track." Then suddenly he added, "I know, I'll call him 'Tracker'."

"Or 'her'," added Smithy looking at the fluffy bundle which was sitting looking up at them. "Still it is a *trim* little thing *padding* around the workshop," chuckled Smithy.

"Yes, another one for the gang," added Dick.

"Good grief!" muttered

Smithy turning to the tea things, and then he cried, "Oh no, you've given it the last of the milk! All this tea and no milk!" wailed Smithy pointing to the nearly full saucer.

In the painful silence that followed the two service engineers bent to their tasks to finish off their days work. The silence was broken only by the occasional crackle from Dick's 'tranny' and Smithy's television and the contented purring of the cat as it curled up on Dick's anorak which it had found crumpled on the floor.

Suddenly, "Cripes!" yelled Smithy as he leapt back from his bench, "it's alive!"

"Well don't touch it then," said Dick quickly and as our gentle reader might agree - rather cruelly. "Well I'm blown - look," cried Smithy pointing into the dusty interior of the television. "That's where the crackling is coming from. Where the EHT lead touches the cabinet - its arcing over. Would you believe it - its *tracking*!"

The WORLD of RADIO & ELECTRONICS

AMBIT INTERNATIONAL



CONCISE PARTS CATALOGUE

OUT NOW!

AMBIT'S NEW CATALOGUE

In an attempt to collate and organize our burgeoning ranges of 'stock' components (now over 7000 line items), we have at last produced a 'concise' 80 page parts catalogue to supplement the popular 'Tecknowledgery' series of 'wordy' applications catalogues, which now lists a wide range of basic components - as well as our unique RF and Communications components. The *World of Radio and Electronics* contains everything the informed electronics user needs, at prices which we guarantee will match the lowest on the market for equivalent product.

Prices appear on the page alongside the part numbers, and the catalogue is now updated quarterly - available either direct from here (60p all inc) or at most newsagents and bookstalls where you can find electronics publications. So as well as all the 'run-of-mill' items like resistor, capacitors, hardware, solder etc - you now have the first genuinely complete parts source for the radio, communication, electronics, computer user.

Ambit International
200, North Service Road,
Brentwood,
Essex CM14 4SG

T & J ELECTRONIC COMPONENTS

METAL BOXES

Two piece design consisting of a "U" shaped base and cover. Finished in black stelvite.

WB1 6 x 4 x 1 1/2" 165p
WB2 8 x 5 x 2" 215p
WB3 9 x 5 x 2 1/2" 230p
WB6 4 1/2 x 2 1/2 x 2 1/2" 130p

PLAIN ALUMINIUM (With lid)

AB7 5 1/2 x 2 1/2 x 1 1/2" 90p
AB8 4 x 4 x 1 1/2" 90p
AB9 4 x 2 1/2 x 1 1/2" 90p
AB10 5 1/2 x 4 x 1 1/2" 105p
AB12 3 x 2 x 1" 72p

PLASTIC BOXES

PB1 4 1/2 x 3 x 1 1/2 white 70p
O25L 2 1/2 x 1 1/2 x 1" (Vero) white 50p
Many other boxes in catalogue.

MISCELLANEOUS

P.C.B. Transfers (13 sheets) 300p
Insulated crocodile clip 9p
Telephone pick up coil 75p
2.5" x 1", 0.1" Veroboard 16p
Small cable ties 2p
PP3 battery connectors 14p
F.M. ribbon dipole aerial 45p
Spirawrap 3/4" diameter (per metre) 16p
Spirawrap 1/2" diameter (per metre) 13p
Grommets 1/2" bore 1p
Grommets 3/4" bore 1.5p
3.5mm jack plug 10p
2.5mm jack plugs 10p
2.5 and 3.5mm sockets 10p
2 pin DIN plugs 8p
2 pin DIN sockets 8p
Veropins 0.1" and 0.15" per 25 s.p.s.t. toggle switches 15p
38p

L.E.D.S.

0.125" red 12p
0.125" green or yellow 21p
0.2" red 13p
0.2" green or yellow 22p
0.2" clear, illuminates red 22p
Clips for all above types: 2p

RESISTORS

1/2W and 1/4W tolerance $\pm 5\%$ 4.7 Ω to 10M. E12 series. Price each 2p.
Miniature, presets. Tolerance $\pm 20\%$
Power rating 0.1W, E6 series 100 Ω to 1M. Price each, vertical or horizontal. 9p

I.C. SOCKETS

Low profile types by Texas.
8 pin 11p. 14 pin 13p. 16 pin 13p.

SEMICONDUCTORS

BC107/8/9 11p, BC182/3/4 11p, AC127/8 24p, 2N3702/3/4/6 11p, BC338 16p, BC169 12p, 2N3819 25p, 1N4001/2 5p, BY127 18p, 1N5401 15p, 1N914 5p, IS44 7p, BZY88C series 2.7V to 33V 10p.

COMPONENT KITS

All previously advertised kits still available.
Latest kit prices:
Voltmeter Sensitivity Booster £3.15
May 1981
Crystal Calibrator May 1981 £14.85

Please note that some kits exclude certain items. Full details in list, available on receipt of an s.a.e.

98 Burrow Road, Chigwell Essex. IG7 4HB.

Mail order only. Prices include VAT, overseas deduct 15% NO minimum order charge. Postage: Components 40p (Overseas add £1.50, airmail at cost), kits 65p. Orders are despatched same day as received.
Full catalogue available. 45p cheque or postal order. Enquiries please enclose an s.a.e.

A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for you.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
Radio TV Electronics Technicians'
Electrical Installations Technicians'
Electrical Installation Work
Radio Amateurs'
MPT Radio Communications Cert

**EXAMINATION STUDENTS —
GUARANTEED COACHING
UNTIL SUCCESSFUL**

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:
Electronic Engineering & Maintenance
Computer Engineering/Programming
Radio, TV & Audio Engineering
& Servicing
Electrical Engineering Installations
& Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name Age

Address

Occupation

ICS Accredited by CACC Member of ABCC To International Correspondence Schools Dept 278K, Intertext House, LONDON SW8 4UJ or phone 01-622 9911 (anytime)

SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge £2.00
Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. Replies to Box Numbers should be addressed to: Box No. —, Radio and Electronics Constructor, 57 Maida Vale, London, W9 1SN.

WIRELESS, VALVES, PRE-WAR ONWARD S.A.E. Modern bargains list 15p. Sole Electronics, (REC), 37 Stanley Street, Ormskirk, Lancs., L39 2DH.

BREAKTHROUGH FOR BATTERY USERS. If you use a PP9 or PP3, you need a "Battery Miser". Get up to twice normal life. Just clips to your battery. £2.00 includes VAT and postage UK. Mail order only. Stephenson Evans, The Radio Station, Parbold Hill, Lancs., WN8 7TG.

BOOKS. BOOKS. BOOKS. Large range of radio and electronic books in stock. Send s.a.e. for lists. Servio Radio, Dept. REC8, 156-158 Merton Road, Wimbledon, London SW19 1EG.

PUSH BUTTON G.P.O. TELEPHONES. Saves you time and improves your image and efficiency. £35 + £2 P. & P. Returnable if not satisfied. P.D. Electronics, 11 Bluebell Close, Orpington, Kent, BR6 8HS.

ANY SINGLE SERVICE SHEET £1 plus S.A.E. Thousands of different service/repair manuals/sheets in stock. Repair data your named TV £6 (with circuits £8). S.A.E. newsletter, price lists, quotations. (0698-883334). Ausrec, 76 Churches, Larkhall, Lanarkshire.

BOOKS FOR SALE: Experiments with Operational Amplifiers, by George B. Clayton. £3.75. *Experimenting with Electronic Music* by Brown & Olsen. £1.20. *Electric Model Car Racing* by Laidlaw-Dickson. 60p. *Electronics Unravalled* by Kyle. £1. *Auto Electronics Simplified*, by Tab Books. £1.20. Box No. G394.

INTERESTED IN RTTY? You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk, NR32 3PJ.

FOR SALE: A number of "D & S" three pin, fused, mains plugs and fuses. S.A.E. for details. Box No. G396.

(Continued on page 777)

SMALL ADVERTISEMENTS

(Continued from page 776)

SPECIAL OFFER. Portable 40 CH C.B. monitors. Also receives 54-176MHz. Telescope aerial. Squelch control. Only £15.95. Convert standard car radio to 40 CH C.B. receiver. CB/Normal switch. Easily installed. £10.45. All post paid. Killinghall Electronics, 16 Killinghall Road, Bradford 3, Yorkshire.

SIMPLE BEGINNERS KITS: L.E.D. flasher £3.25. Crystal set £2.95. 1 transistor radio £3.25. Variable tone generator £3.25. All less case. Cheques made payable to: Elektron Kits, 51 Fairfield, Gamlingay, Sandy, Beds., SG19 3LG.

C.B. RADIO CONVERSIONS. Add extra channels to most modern C.B. radios using a resistor, a switch and our comprehensive data on P.L.L. chips. E.G. sharp 40CH + 1k/ res. = 64CH. Also crystal substitution information and much more. Send £1 for details. Mark your reply for the attention of J. McMahon, Selectronics Inc., P.O. Box 5, Ennis, Co. Clare, Ireland. Selectronics technical services to the home, hobby and industry.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

B. J.'s DICTIONARY OF CB SLANG. Quality printed. 95p + stamp. Refund if not highly delighted. Trade welcome. Bailey & Co., Tondu, Bridgend, Mid-Glam.

MICRO TRANSMITTERS. Highly sensitive. Range up to 1 mile. Tuneable 60-150MHz. Receive on VHF/FM radio. Supplied working with microphone and data. £4.75 + 25p P. & P. To: P.D. Electronics, 11 Bluebell Close, Orpington, Kent, BR6 8HS.

THE RADIO AMATEUR INVALID & BLIND CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey, KT6 4TE.

INTERESTED IN CB? Be the first in your street with the very latest receiver. It's legal and covers 2 CB bands, PB/WB and medium wave/AM FM/VHF aircraft and 2M ham. In fact everything you ever wanted in a radio. It's just arrived in England so it's not in the shops yet! Send cheque or P.O. for £24.50 inclusive. S. & M. Sales, 99 St. Leonards Road, Windsor, Berks.

(Continued on page 778)

RECHARGEABLE BATTERIES AND CHARGERS

PRIVATE OR TRADE ENQUIRIES WELCOME

FULL RANGE AVAILABLE SEND SAE FOR LISTS. £1.45 for Booklet "Nickel Cadmium Power" plus Catalogue. Write or call:

*NEW SEALED
LEAD RANGE AVAILABLE*

SANDWELL PLANT LTD

2 Union Drive, Boldmere,
Sutton Coldfield, West Midlands,
021-354 9764.



Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLDS BEST
CATALOGUE OF SPEAKERS, DRIVE UNITS KITS,
CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER ●
BOWERS &
WILKINS ● CASTLE ● CELESTION ●
CHARTWELL ● COLES ● DALESFORD ●
DECCA ● EAGLE ● ELAC ● EMI ● FANE ●
GAUSS ● GOODMAN ● HARBETH ●
ISOPHON ● I.M.F. ●
JORDAN ● JORDAN WATTS ● KEF ●
LOWTHER ● MCKENZIE ● MISSION ●
MONITOR AUDIO ● MOTOROLA ●
PEERLESS ● RADFORD ● RAM ●
ROGERS ● RICHARD ALLAN ● SEAS ●
SHACKMAN ● STAG ● TANNON ●
VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO

DEPT REC

35/39 CHURCH STREET, WILMSLOW
CHESHIRE SK9 1AS.

Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits,
etc.,


Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete
speakers

Self-Binder

for "Radio & Electronics
Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

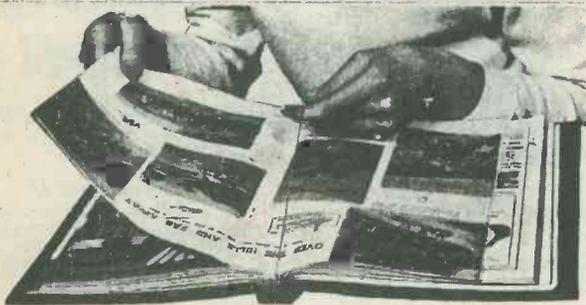

PRICE £2.25 P. & P. 60p
including V.A.T.

For your other magazines

Plain-backed in Maroon or Green
(Please state colour choice)

PRICE £2.25 P. & P. 60p
including VAT

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

Continued from page 777)

LOOK TRANSISTORS - BC182L 9p. BC184 10p. BC212L 10p. BC214L 10p. 2N3055 35p. OA81 3p. 1N4148 2p. 1N4004 6p. P. & P. 25p. C. Pearce, 14 Launde Park, Market Harborough, Leics.

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

WANTED: Army wireless sets and instruction books on same. Hallicrafter receivers, and speakers. Will collect during my holidays in September. Please write to: A. Huizer (PE1 - DMN), Wilhelminasingel 16, 3135 JP Vlaarding, Holland.

HIGH VOLTAGE FROM 9 VOLTS. This circuit will convert a low battery voltage into 450 volts or more. Applications include high voltage for neon displays, geiger counters, strobes, etc. Supplied working and assembled. Price £3.95 plus 35p P. & P. P.O.'s to: P. D. Crisp, 32 Churchill Crescent, Wickham Market, Suffolk, IP13 0RW.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

COMMUNICATIONS RECEIVER BC348R. Ex-U.S. army. £50.00 or offer. Wavemeter type D £5 or offer. Eddystone side operated key £10. Telephone: Maidenhead (Berks) 22902.

MINI FANS: Uses HP11 battery. Pocket Size. Ideal for hot weather. Only £1.50 or £2.75 for two, inc. P & P. To: - P.D. Electronics, 11 Bluebell Close, Orpington, Kent, BR6 8HS.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine etc., £9-00 per annum U.K. Overseas rates on request, Secretary Grove Road, Lydney, Glos., GL15 5JE.

BREAKER, BREAK. Build your own C.B. rig. (27MHz A.M. transceiver). Circuit diagram, parts list, etc. All components available in U.K. Send £3.95 and large s.a.e. to: P. Sherwood, 8 (T) Aylestone Walk, Manchester, M10 9NU. I'm down and on the side.

(Continued on page 779)

SMALL ADVERTISEMENTS

(Continued from page 778)

FOR SALE. Non-working video tape recorders from £25.00 for spares. Also non-working CCTV cameras from £15.00. Box No. G403.

FOR SALE: Photographic enlarging equipment: Vivitar enlarger. Model E.36 with 50mm f. 3.5 and 75mm f.3.5 lenses. Kodak safety light. Kodak contrast filter set. 11 in. x 14 in. printing frame with copying facilities. Measuring flask. Three trays, three tweezers. Three plastic bottles. Clips. Printing paper. Antistatic brush for cleaning negatives. Kodak Photoguide Booklet. Man's protective apron. £75 o.n.o. Pair of Goodman's speakers 8 ohms, 15 watts, £50 o.n.o. R. L. Gee, 9 Glanmead, Shenfield, Essex.

MAPLIN AUTO ORGAN. Rhythm unit fitted for use with pedals, can be fitted to any organ. Best offer secures. Telephone: Andover (Hants.) 65029.

FOR SALE: FM Transmitter microphone - hear your own voice on radio, price £15.00. Holograms £12.50. Mini cassette recorder and 10 C60's, £20.00. LED watches £3.50. 50 2W zeners £1.00. 50 BZY88 type zeners £1.00. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

WANTED. High voltage gas discharge tubes, i.e. Tesla tubes, "Maltese Cross" tube, small gas discharge tubes, neons, etc., to work from induction coil for demonstration purposes. Details to Box No. G404.

WANTED. Two Books - *Circuit Consultants Handbook* by T. K. Hemingway, 1970, and *Practical Design with Transistors* by M. Horowitz, 1969. Box No. G405.

ELECTRONIC COMPONENTS. 6 x CD4011 £1.00. Veroboard 0.1, 4" x 4" 80p. 13 x TIL 209 £1.00. 30 x C280 capacitors 95p. 130 mixed resistors £1.00. 30 assorted electrolytic capacitors 70p. 12 x BC212 £1.00. 40 mixed capacitors 80p. 12 x 2N3702 £1.00. 10 x BC108 £1.00. 7 x TIL 211 £1.00. Add 25p P. & P. Lists 35p. John E. Harris, 9 Ivybridge, Broxbourne, Herts.

(Continued on page 780)

PRINTED CIRCUIT BOARDS FOR "RADIO & ELECTRONICS CONSTRUCTOR" PROJECTS.

OCT 20dB amp. Part 1 68p plus 30p P&P
 NOV. 20dB amp. Part 2 62p plus 30p P&P
 NOV. Basic Med. Wave radio 69p plus 30p P&P
 DEC. Volume Expander £2.25 plus 30p P&P
 FEB. '81 Cricket Game £1.67 plus 30p P&P
 APR. Med. & Short Wave radio £1.20 plus 30p P&P
 APR. Active tone control mod. £1.25 plus 30p P&P
 MAY. Crystal Calibrator £1.75 plus 30p P&P
All boards ready for use, roller tinned and drilled, glassfibre.

Trade enquiries welcome. Highly competitive prices.

Write now for quote to:

BRB PRINTED CIRCUITS (REC)

109, Potter Street, Worksop, Notts. S80 2HL.

REVOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE
 LONDON W.C.1
 Tel. 01-836 4536



PRICED FROM £148.75
Stereomaster


This microscope's working distance and field of view is relatively large; this feature ensures convenience to the operator who works with both hands while assembling precision mechanisms.

IDEAL FOR PRINTED CIRCUITS AND OTHER DELICATE WORK.

COMES COMPLETE WITH

built-in x 10 Mag. Objectives x 20 Objectives x 35
 At extra cost

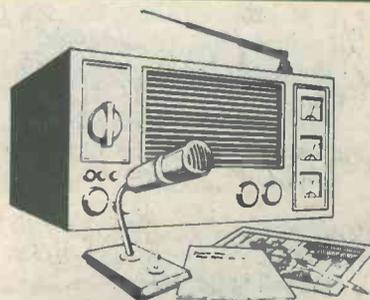We stock one of the largest selections of second hand microscopes and optical magnifiers, on and off stands. Please phone for details.



BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

Brochure without obligation to :-

British National Radio & Electronic School

4 Cleveland Road, Jersey, Channel Islands.

Name

Address

REC/8/815

BLOCK CAPS PLEASE

LATEST BOUND VOLUME No. 33

of
"Radio & Electronics
Constructor"



SEPTEMBER 1979 to AUGUST 1980

Comprising
752 pages
inc. index

PRICED £6.20 P&P £1.50

BOUND VOLUME No. 27
(August 1973 to July 1974)
Price £3.00 P&P £1.50

BOUND VOLUME No. 28
(August 1974 to July 1975)
Price £3.20 P&P £1.50

BOUND VOLUME No. 29
(August 1975 to July 1976)
Price £3.50 P&P £1.50

BOUND VOLUME No. 30
(August 1976 to July 1977)
Price £3.70 P&P £1.50

BOUND VOLUME No. 31
(August 1977 to August 1978)
Price £5.20 P&P £1.50

BOUND VOLUME No. 32
(September 1978 to August 1979)
Price £5.20 P&P £1.50

Limited number of these
volumes still available.

We regret all earlier volumes are now
completely sold out.

Available only from

DATA PUBLICATIONS LTD.,
57, MAIDA VALE, LONDON, W9 1SN

PERSONAL

TWO'S COMPANY for friendship/marriage. Introductions with the personal touch for people of discernment. Brochure on request. **TWO'S COMPANY**, Dept. 1E/R, 111 High Holborn, London WC1V 6JS. Telephone: 01-242-2345.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NR0 85S.

CLOSE ENCOUNTERS GROUP. Personal introductions/dances, parties, talks, social events. Meet interesting, attractive people. All areas. Telephone: 01-278 0203 and 051-931 2844.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

SPONSORS required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

INTERNATIONAL SHORT WAVE LEAGUE



Membership £9.00 per annum (Overseas rates on request) including 12 monthly issues of *Monitor* - the League journal. Including free use of all Services, QSL Bureau etc.

**THE LARGEST S.W.L. ORGANISATION
IN THE WORLD**

For full details write to:

The Secretary,
I.S.W.L.,
1, GROVE ROAD, LYDNEY,
GLOS. GL15 5JE.

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 60p each, p&p 20p

Issue(s) required

Annual Subscription

Price £9.50 inland, £10.50 overseas (including Eire)

post free, commence with issue

Bound Volumes:

Vol. 27.	August 1973 to July 1974	Price £3.00, post & pkg £1.50
Vol. 28.	August 1974 to July 1975	Price £3.20, post & pkg £1.50
Vol. 29.	August 1975 to July 1976	Price £3.50, post & pkg £1.50
Vol. 30.	August 1976 to July 1977	Price £3.70, post & pkg £1.50
Vol. 31.	August 1977 to August 1978	Price £5.20, post & pkg £1.50
Vol. 32.	September 1978 to August 1979	Price £5.50, post & pkg £1.50
Vol. 33.	September 1979 to August 1980	Price £6.20 post & pkg. £1.50

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price £2.25, post & pkg 60p

With no title on spine, maroon

Price £2.25, post & pkg 60p

With no title on spine, green

Price £2.25, post & pkg 60p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages Price £1.20, P.&P. 30p

DB6 Radio Amateur Operator's Handbook,
New edition in course of preparation

DB19 Simple Short Wave Receivers Price 80p, P. & P. 30p
140 pages

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording - White - 6 sheets Price £1.50, P. & P. 13p

Set 4: Wording - Black - 6 sheets Price £1.50, P. & P. 13p

Set 5: Dials - 6 sheets Price £1.50, P. & P. 13p

Prices include V.A.T.

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

INDEX TO VOLUME THIRTY-FOUR

September 1980 – August/September 1981

AMPLIFIERS

Audio Master743	Aug./	'81
Guitar Practice Amplifier, by R. A. Penfold480	Apl.	'81
Simple Stereo Amplifier, by T. J. Johnson718	Aug./	'81
Two 20dB Amplifiers – Part 1, by M. V. Hastings92	Sept.	'80
Two 20dB amplifiers – Part 2, by M. V. Hastings168	Oct.	'80
Universal 12v 5W Amplifier686	Nov.	'80
		July	'81

AMPLIFIER ANCILLARIES

Active Tone Control Module, by A. P. Roberts502	Apl.	'81
Add-on Clipping Monitor, by M. V. Hastings212	Dec.	'80
High Quality Compressor, by John Baker416	Mar.	'81

CB

607 June '81	666 July '81752	Aug./	'81
			Sept.	

CALCULATORS

Reciprocal Working, by G. B. Brown210	Dec.	'80
---	--------	------	-----

COMPUTERS

Compulink Series – No. 1684	July	'81
Compulink Series – No. 2763	Aug./	'81
		Sept.	

ELECTRONICS

Airing Cupboard Warmer, by Owen Bishop108	Oct.	'80
Battery Voltage Monitor, by M. V. Hastings412	Mar.	'81
Burglar Alarm With Entrance Delay, by G. A. French528	May	'81
Calculating Resonance, by P. Rogers25	Sept.	'80
Capacitance Combination Lock, by G. A. French80	Oct.	'80
Car Voltage Monitor, by I. Peterson273	Jan.	'81
CMOS Combination Switch, by M. P. Horsey148	Nov.	'80
Constant Current Nicad Charger, T. J. Johnson18	Sept.	'80
Electronic Door Buzzer, by A. P. Roberts341	Feb.	'81
Fail-Safe, by P. Jenner539	May	'81
Fuzz Box, by I. M. Attrill288	Jan.	'81
Infra-Red Remote Control System – Part 1, by I. M. Attrill662	July	'81
Infra-Red Remote Control System – Part 2, by I. M. Attrill739	Aug./	'81
		Sept.	
Low Current Pilot Lamp, by F. L. Stephenson340	Feb.	'81
Make-Before-Break, by R. F. Peters542	May	'81
Meddle Monitor, by F. Bowden282	Jan.	'81
Model Train Controller, by M. V. Hastings474	Apl.	'81
Monitoring T.T.L. Current, by G. A. French14	Sept.	'80
Morse Practice Buzzer, by P. Fletcher216	Dec.	'80
Nicad Battery Charger, by P. R. Arthur436	Mar.	'81
Owizzee!!, by David Arts360	Feb.	'81
Piezo Acoustic Transducers. Design Ideas No. 1, by Jonathan Charles Burchell658	July	'81
Proximity Lamp Switch, by R. A. Penfold602	June	'81
Pulse Power Supply, by Stephen P. Narey564	May	'81
Radio Switch-Off Timer, by John Baker680	July	'81
Regulator Circuits, by D. H. Trent302	Jan.	'81
Relay Switching, by P. F. Bowles556	May	'81
Room Thermostat Unit, by R. A. Penfold402	Mar.	'81
Schmitt Oscillator, by R. J. Caborn594	June	'81

Slide Projector Pulsar, by C. J. Bowes624	June	'81
Soldering Iron Reminder, by John Baker466	Apl.	'81
Telephone Charge Reminder, by I. M. Attrill612	June	'81
The Magic Hand, by G. A. French208	Dec.	'80
The ZN1034 Precision IC Timer, by R. A. Penfold734	Aug./	Sept.
				'81
Timer With Trigger Action, by F. Craig470	Apl.	'81
Tremolo Modulation Unit, by I. M. Attrill152	Nov.	'80
9 Volt 1 Amp Power Supply, by I. M. Attrill 26	Sept.	'80
VMOS Devices and Constant Current Supplies. Design Ideas No.2, by Jonathan Charles Burchell	714	Aug./	Sept. 81

GENERAL

A Century of GMT299	Jan.	'81
Amateur Radio Satellites, by Arthur C. Gee 48	Sept.	'80
Amateur Radio Satellites, by Arthur C. Gee284	Jan.	'81
Amateur Satellite News Report, by Arthur C. Gee630	June	'81
Circular Hole Jig, by D. M. Pitkin376	Feb.	'81
Enlarger/Process Timer, by Peter Roberts596	June	'81
Experimental Electronics, by R. J. Caborn276	Jan.	'81
Fax Progress, by Arthur C. Gee365	Feb.	'81
Hi-Fi P.C.M., by J. R. Davis 83	Oct.	'80
LCD Digital Stopwatch/Clock, by J. L. Mills690	July	'81
Matching Transformers, by R. J. Caborn 46	Sept.	'80
Measuring Electrolytics, by T. H. Reynolds297	Jan.	'81
Multi-Option Chip, by R. J. Caborn231	Dec.	'80
Neglected Oscillator, by R. S. Burns246	Dec.	'80
OHMS Per Volt, by D. Snaith301	Jan.	'81
Satisfactory Soldering, by D. Snaith184	Nov.	'80
TV Programmes By Fibre Optic Cable538	May	'81

IN YOUR WORKSHOP

In-Situ Ohmmeter 50	Sept.	'80
Crowbar Protection Circuit114	Oct.	'80
Radio Distortion Fault172	Nov.	'80
The "Haunted" Radio240	Dec.	'80
The Transformer With A Memory307	Jan.	'81
Fixing An F.M. Radio366	Feb.	'81
Ohm's Law Revisited430	Mar.	'81
A Session Of Puzzles - No. 1494	Apl.	'81
A Session Of Puzzles - No. 2566	May	'81
Problems With T.V. Gain Control617	June	'81
Further Thoughts On Ohm's Law692	July	'81
A New Recruit771	Aug./	Sept.
				'81

MICROPROCESSORS

Monitoring T.T.L. Current, by G. A. French 14	Sept.	'80
The INSTRUCTOR - Part 2, by Ian Sinclair 32	Sept.	'80
The INSTRUCTOR - Part 3, by Ian Sinclair100	Oct.	'80
The INSTRUCTOR - Part 4, by Ian Sinclair156	Nov.	'80
The INSTRUCTOR - Part 5, by Ian Sinclair218	Dec.	'80
The INSTRUCTOR - Part 6, by Ian Sinclair293	Jan.	'81
The INSTRUCTOR - Part 7, by Ian Sinclair345	Feb.	'81
The INSTRUCTOR - Part 8. (Conclusion) by Ian Sinclair408	Mar.	'81

RADIO CONTROL

A 5 Channel Digital Proportional RC System756	Aug./	Sept.
				'81

RECEIVERS

Basic Medium Wave Radio, by T. F. Weatherley180	Nov.	'80
Further Notes on Some Recent Receivers - Part 1, by Sir Douglas Hall, Bt., K.C.M.G.440	Mar.	'81
Further Notes on Some Recent Receivers - Part 2, (Conclusion) by Sir Douglas Hall, Bt., K.C.M.G.472	Apl.	'81
"Lisa" 2-Band Portable - Part 1, by Sir Douglas Hall, Bt., K.C.M.G. 40	Sept.	'80
"Lisa" 2-Band Portable - Part 2, (Conclusion) by Sir Douglas Hall, Bt., K.C.M.G.104	Oct.	'80
Medium and Short Wave Radio, by I. M. Attrill489	Apl.	'81
M.W. and L.W. Superhet Radio, by John Baker728	Aug./	Sept.
				'81
Personal Medium Wave Radio, by R. A. Penfold 88	Oct.	'80
3-Stage M.W. Superhet, by R. A. Penfold549	May	'81

RECEIVER ANCILLARIES

A Scanning Monitor Receiver System – Part 1, by L. Power	...670	July	'81
A Scanning Monitor Receiver System – Part 2, by L. Power	...766	Aug./	Sept. '81
Coil-Coupled S.W. Converter, by R. A. Penfold	...161	Nov.	'80
"K" Tone Generator, by Trevor Hopkins	...236	Dec.	'80
Reverberation Unit, by R. A. Penfold	...352	Feb.	'81
Opto-Coupled Volume Expander, by R. A. Penfold	...224	Dec.	'80
Sleepy Time Radio Switch, by G. A. French	...590	June	'81

TEST EQUIPMENT

Constant Current HFE Meter, by D. Snaith	...558	May	'81
Crystal Calibrator, by T. J. Johnson	...532	May	'81
Current Checkers, by P. G. Smith	...312	Jan.	'81
Double Output Test Oscillator, by R. A. Penfold	...278	Jan.	'81
Diode Evaluator, by G. A. French	...398	Mar.	'81
Go-No Go Transistor Tester, by A. P. Roberts	...96	Oct.	'80
Linear Scale Ohmmeter, by G. A. French	...142	Nov.	'80
Single I.C. Signal Tracer, by M. V. Hastings	...372	Feb.	'81
Transistor Gain Meter, by G. A. French	...270	Jan.	'81
Transistor Gain Tester, by R. A. Penfold	...424	Mar.	'81
Voltage Calibrator for Oscilloscopes, by G. A. French	...464	Apl.	'81
Voltmeter Sensitivity Booster, by A. F. Olivera	...544	May.	'81
Zener Diode Analyser, by G. A. French	...334	Feb.	'81

NEWS AND COMMENT

16 Sept. '80	78 Oct. '80	146 Nov. '80	206 Dec. '80
274 Jan. '81	338 Feb. '81	400 Mar. '81	462 Apl. '81
526 May '81	588 June '81	656 July '81	Aug./
			Sept. '81

NEW PRODUCTS

112 Dec. '80	239 Dec. '80	300 Jan. '81	441 Mar. '81
	601 June '81	697 July '81	712 Aug./
			Sept. '81

RADIO TOPICS

56 Sept. '80	120 Oct. '80	248 Dec. '80
304 Jan. '81	500 Apl. '81	561 May '81

RECENT PUBLICATIONS AND BOOK REVIEWS

31 Sept. '80	24 Sept. '80	145 Nov. '80	178 Nov. '80
337 Feb. '81	377 Feb. '81	531 May '81	560 May '81

SHORT WAVE NEWS

38 Sept. '80	106 Oct. '80	166 Nov. '80	234 Dec. '80
285 Jan. '81	358 Feb. '81	422 Mar. '81	487 Apl. '81
547 May '81	628 June '81	677 July '81	724 Aug./
			Sept. '81

TRADE NEWS

55 Sept. '80	87 Oct. '80	313 Jan. '81	429 Mar. '81
569 May '81	632 June '81	679 July '81	765 Aug./
			Sept. '81

ELECTRONICS DATA

No. 61 Bias	...iii	Sept.	'80
No. 62 Stray and Self-Capacitance	...iii	Oct.	'80
No. 63 Bandspreading	...iii	Nov.	'80
No. 64 Voltage Regulators	...iii	Dec.	'80
No. 65 Truth Tables	...iii	Jan.	'81
No. 66 Seven Segment Displays	...iii	Feb.	'81
No. 67 Low Inductance Coils	...iii	Mar.	'81
No. 68 Linear Amplification	...iii	Apl.	'81
No. 69 Digital Audio	...iii	May	'81
No. 70 Miller Effect	...611	June	'81
No. 71 Know Your RF Connectors – Part 1	...689	July	'81
No. 72 Know Your RF Connectors – Part 2	...751	Aug./	Sept. '81

Ambit's new concise component catalogue is out !!

Our new style concise parts/prices catalogue is available at most newsagents for 50p - or direct from here.

CMOS 4000

4000	0.13
4001	0.20
4002	0.14
4007	0.19
4008	0.70
4008AE	0.80
4009	0.30
4010	0.30
4011AE	0.24
4011	0.15
4013	0.35
4015	0.70
4016	0.30
4017	0.65
4019	0.68
4021	0.75
4022	0.68
4023	0.19
4024	0.45
4025	0.18
4026	1.05
4028	0.60
4029	0.75
4030	0.35
4035	0.75
4040	0.68
4042	0.65
4043	0.68
4043AE	0.93
4044	0.68
4046	0.69
4047	0.69
4049	0.30
4050	0.30
4051	0.65
4052	0.69
4053	0.69
4054	1.30
4055	1.30
4056	1.35
4059	5.75
4060	0.95
4063	1.15
4066	0.38
4067	4.30
4068	0.18
4069	0.18
4070	0.25
4071	0.22
4072	0.22
4073	0.22
4075	0.18
4076	0.60
4077	0.23
4078	0.25
4081	0.15
4082	0.25
4093	0.45
4099	0.99
4175	1.15
4502	0.90
4503	0.55
4506	0.75
4507	0.45
4508	1.99
4510	0.70
4511	0.85
4512	0.70
4514	2.20
4515	2.50
4516	0.75
4518	0.75
4520	0.80
4521	2.36
4522	1.49
4527	0.95
4528	0.95
4529	1.40
4539	1.10
4543	1.00
4549	3.50
4553	3.10
4554	1.73
4555	0.72
4556	0.58
4557	2.10
4558	1.00

4559	2.75
4560	2.18
4561	0.70
4562	2.75
4566	1.59
4568	2.18
4569	1.95
4572	0.30
4580	3.25
4581	1.50
4582	0.99
4583	0.80
4584	0.49
4585	1.00
4702	4.50
4703	4.48
4704	4.24
4705	4.24
4706	4.50
4720	4.00
4723	0.95
4724	0.95
4725	2.24
40014	0.54
40085	0.99
40098	0.54
40106	0.54
40160	0.69
40161	0.69
40162	0.69
40163	0.69
40174	-0.69
40175	0.69
40192	0.75
40193	0.75
40194	0.69
40195	0.69

TTL 'N'

7400N	0.10
7401N	0.10
7402N	0.10
7403N	0.11
7404N	0.12
7405N	0.12
7406N	0.22
7407N	0.22
7408N	0.15
7409N	0.15
7410N	0.12
7411N	0.18
7412N	0.19
7413N	0.27
7414N	0.51
7416N	0.27
7417N	0.27
7402N	0.13
7421N	0.28
7422N	0.20
7423N	0.22
7425N	0.22
7426N	0.22
7427N	0.22
7428N	0.35
7430N	0.13
7432N	0.23
7437N	0.22
7438N	0.22
7440N	0.14
7441N	0.54
7442N	0.42
7443N	0.62
7444N	0.62
7445N	0.62
7446N	0.62
7447N	0.62
7448N	0.56
7450	0.14
7451N	0.14
7453N	0.14
7454N	0.14
7460N	0.14
7470N	0.28
7472N	0.27
7473N	0.28
7474N	0.28
7475N	0.35

7476N	0.30
7480N	0.26
7481N	0.20
7482N	0.75
7485N	0.75
7486N	0.24
7489N	1.05
7490N	0.30
7491N	0.55
7492N	0.35
7493N	0.35
7494N	0.70
7495N	0.60
7496N	0.45
7497N	1.40
74100	1.10
74104	0.62
74105	0.62
74107	0.26
74109N	0.35
74110N	0.54
74111N	0.68
74112N	1.70
74116N	1.98
74118N	0.85
74119N	1.20
74120N	0.95
74121N	0.34
74122N	0.34
74123N	0.40
74125N	0.40
74126N	0.40
74128N	0.65
74132N	0.50
74136N	0.65
74141N	0.45
74142N	1.85
74143N	2.50
74144N	2.50
74145N	0.75
74147N	1.50
74148N	1.09
74150N	0.79
74151N	0.55
74153N	0.55
74154N	0.55
74155N	0.55
74156N	0.55
74157N	0.55
74159N	1.90
74160N	0.55
74161N	0.55
74162N	0.55
74163N	0.55
74164N	0.55
74165N	0.55
74166N	0.70
74167N	1.25
74170N	1.25
74173N	1.10
74174N	0.75
74175N	0.75
74176N	0.75
74177N	0.75
74178N	0.90
74179N	1.35
74180N	0.75
74181N	1.22
74182N	0.70
74184N	1.20
74185N	1.20
74188N	3.00
74190N	0.55
74191N	0.55
74192N	0.55
74193N	0.55
74194N	0.55
74195N	0.55
74196N	0.55
74197N	0.55
74198N	0.85
74199N	1.00
74221N	1.00
74246N	1.50
74247N	1.51
74248N	1.89
74249N	0.11
74251N	1.05

74LSN series

74LS00N	0.11
74LS01N	0.11
74LS02N	0.12
74LS03N	0.12
74LS04N	0.14
74LS05N	0.14
74LS08N	0.14
74LS09N	0.14
74LS10N	0.13
74LS11N	0.14
74LS12N	0.15
74LS13N	0.28
74LS14N	0.49
74LS15N	0.14
74LS20N	0.13
74LS21N	0.15
74LS22N	0.15
74LS26N	0.18
74LS27N	0.14
74LS28N	0.35
74LS30N	0.13
74LS32N	0.14
74LS33N	0.16
74LS37N	0.17
74LS38N	0.16
74LS40N	0.13
74LS42N	0.40
74LS47N	0.42
74LS48N	0.65
74LS49N	0.61
74LS51N	0.14
74LS54N	0.15
74LS55N	0.15
74LS63N	1.50
74LS73N	0.21
74LS74N	0.18
74LS75N	0.28
74LS76N	0.22
74LS78N	0.24
74LS83N	0.50
74LS85N	0.70
74LS86N	0.18
74LS90N	0.32
74LS91N	1.25
74LS92N	0.39
74LS93N	0.38
74LS95N	0.48
74LS96N	1.20
74LS107N	0.25
74LS109N	0.25
74LS112N	0.25
74LS113N	0.25
74LS114N	0.25
74LS122N	0.40
74LS123N	0.55
74LS124N	1.80
74LS125N	0.29
74LS126N	0.29
74LS132N	0.45
74LS133N	0.30
74LS136N	0.25
74LS138N	0.40
74LS139N	0.40
74LS145N	1.20
74LS147N	2.10
74LS148N	1.60
74LS151N	0.35

74265N	0.66
74273N	2.67
74278N	2.49
74279N	0.89
74283N	1.30
74284N	3.50
74285N	3.50
74290N	1.00
74293N	1.05
74297N	2.36
74298N	1.85
74365N	0.85
74366N	0.85
74367N	0.85
74368N	0.85
74390N	1.85
74393N	1.85
74490N	1.85

74LSN series

74LS153N	0.35
74LS154N	0.99
74LS155N	0.50
74LS156N	0.50
74LS157N	0.36
74LS158N	0.40
74LS160N	0.40
74LS161N	0.40
74LS162N	0.40
74LS163N	0.40
74LS164N	0.50
74LS165N	1.20
74LS166N	1.75
74LS168N	0.85
74LS169N	0.85
74LS170N	1.85
74LS173N	0.75
74LS174N	0.55
74LS175N	0.55
74LS181N	1.35
74LS183N	2.96
74LS189N	1.28
74LS190N	0.60
74LS191N	0.60
74LS192N	0.68
74LS193N	0.68
74LS194N	0.42
74LS195N	0.42
74LS196N	0.65
74LS197N	0.65
74LS200N	3.45
74LS202N	3.45
74LS221N	0.60
74LS240N	0.99
74LS241N	0.99
74LS242N	1.65
74LS243N	1.65
74LS244N	0.83
74LS245N	1.50
74LS247N	1.35
74LS248N	1.35
74LS249N	1.35
74LS251N	0.46
74LS253N	0.46
74LS257N	0.55
74LS258N	0.39
74LS259N	0.39
74LS260N	0.70
74LS266N	0.24
74LS273N	0.90
74LS275N	3.20
74LS279N	0.35
74LS280N	2.05
74LS283N	0.44
74LS290N	0.58
74LS293N	1.30
74LS295N	1.50
74LS298N	1.50
74LS365N	0.35
74LS366N	0.35
74LS367N	0.35
74LS368N	0.35
74LS373N	0.78
74LS374N	0.78
74LS375N	1.15
74LS377N	1.99
74LS378N	1.40
74LS379N	2.15
74LS384N	2.50
74LS385N	4.20
74LS386N	0.29
74LS390N	0.68
74LS393N	0.61
74LS395N	2.10
74LS396N	1.99
74LS398N	2.75
74LS399N	2.30
74LS445N	1.40
74LS447N	1.95
74LS490N	1.10
74LS668N	1.05
74LS669N	1.05
74LS670N	1.70

74CXX series

74C00	0.20
74C02	0.20

74C04	0.20
74C08	0.20
74C10	0.20
74C14	0.55
74C20	0.20
74C30	0.20
74C32	0.20
74C42	0.80
74C48	1.03
74C73	0.50
74C74	0.50
74C76	0.48
74C83	0.98
74C85	0.98
74C86	0.26
74C89	2.68
74C90	0.80
74C93	0.80
74C95	0.94
74C107	0.48
74C151	1.52
74C154	2.26
74C157	1.52
74C160	0.80
74C161	0.80
74C162	0.80
74C163	0.80
74C164	0.80
74C165	0.84
74C173	0.72
74C174	0.72
74C175	0.72
74C192	0.80
74C193	0.80
74C195	0.80
74C200	4.52
74C221	1.06
74C901	0.38
74C902	0.38
74C903	0.38
74C904	0.38
74C905	5.64
74C906	0.38
74C907	0.38
74C908	0.84
74C909	1.52

MAPLIN make it easy...



in SOUTHEND
284 London Road
Westcliff-on-Sea
Essex
Tel: (0702) 554000
(Closed Mondays)



in HAMMERSMITH
159-161 King Street
Hammersmith
London W6
Tel: 01-748 0926
(Closed Mondays)

For personal service visit one of our stores.
Our new store at Hammersmith is conveniently situated near the end of the M4 and the North and South Circular Roads. There is excellent street parking on meters a few steps away and Hammersmith Underground Station is nearby. Call in and see us soon.



in our CATALOGUE

320 big pages packed with data and pictures of over 5,500 items

Over 100,000 copies sold already!
Don't miss out on your copy.

On sale now in all branches
WH Smith price £1.

In case of difficulty check the coupon below.

make it easy... with MAPLIN

The Maplin Matinée

Amazing value for only £299.95 plus £99.50 for cabinet if required

Easy to build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in Electronics & Music Maker commencing March, 1981 issue. Back numbers available.



MAPLIN ELECTRONIC SUPPLIES LTD.

by MAIL ORDER
A fast service You can rely on

- * Same day service on in-stock lines
- * Very large percentage of our stock lines in stock
- * All prices include VAT
- * Large range of all the most useful components
- * First class reply paid envelope with every order
- * Quality components—no rejects—no re-marks
- * Competitive prices
- * Your money is safe with a reputable company

On price, service, stock, quality and security it makes sense now more than ever to make **MAPLIN** your first choice for components every time!

Post this coupon now.

Please send me a copy of your 320 page catalogue. I enclose £1.25 (incl. 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name _____

Address _____

REC 881

All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend (0702) 554155 Sales: (0702) 552911