

RADIO & ELECTRONICS


CONSTRUCTOR

FEBRUARY 1981
60p



REVERBER- ATION UNIT

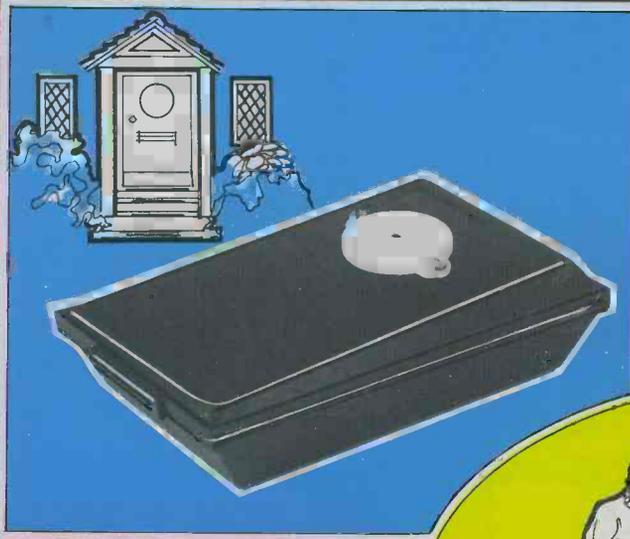SELF CONTAINED -
SELF POWERED BY A
PP6 SIZE BATTERY*





ELECTRONIC DOOR BUZZER

LOW CONSUMPTION UNIT - PRODUCES
A DISTINCTIVE TWO-NOTE TONE

WINTER
CRICKET



FIXING AN F.M. RADIO

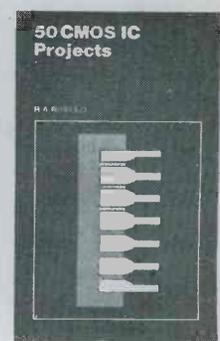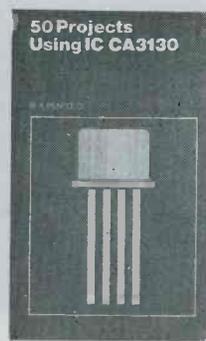

DIRECT READER SERVICE RADIO & ELECTRONICS BOOKS

18. 50 Projects Using IC CA3130	£1.25	40. Projects in Opto-Electronics	£1.25
19. 50 CMOS IC Projects	£1.25	41. Radio Circuits Using IC's	£1.35
20. A Practical Introduction to Digital IC's	95p	42. Mobile Discotheque Handbook	£1.35
22. Beginners Guide to Building Electronic Projects	£1.25	43. Electronic Projects for Beginners	£1.35
23. Essential Theory for the Electronics Hobbyist	£1.25	44. Popular Electronic Projects	£1.45
26. 52 Projects Using IC741	95p	45. IC LM3900 Projects	£1.35
28. Two Transistor Electronic Projects	85p	46. Electronic Music and Creative Tape Recording	£1.25
29. How to Build Your Own Metal and Treasure Locators	£1.00	47. Practical Electronic Calculations and Formulae	£2.25
30. Electronic Calculator Users Handbook	95p	48. Radio Stations Guide	£1.45
31. Practical Repair and Renovation of Colour TVs	£1.25	49. Electronic Security Devices	£1.45
32. Handbook of IC Audio Preamplifier and Power Amplifier Construction	£1.25	50. How to Build Your Own Solid State Oscilloscope	£1.50
33. 50 Circuits Using Germanium, Silicon and Zener Diodes	75p	51. 50 Circuits Using 7400 Series IC's	£1.45
34. 50 Projects Using Relays, SCR's and TRIACS	£1.25	52. Second Book of CMOS IC Projects	£1.50
35. Fun and Games with your Electronic Calculator	75p	53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators	£1.45
36. 50 (FET) Field Effect Transistor Projects	£1.25	54. Beginners Guide to Digital Techniques	95p
37. 50 Simple L.E.D. Circuits	75p	55. 28 Tested Transistor Projects	£1.25
38. How to Make Walkie-Talkies	£1.25	56. Digital IC Equivalents and Pin Connections	£2.50
39. IC 555 Projects	£1.75	57. Linear IC Equivalents and Pin Connections	£2.75

POSTAGE: 20p PER BOOK. IF MORE THAN 3 BOOKS ORDERED: 10p PER BOOK

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies

Book Nos:

.

I enclose Postal Order/Cheque for £

Name

Address

.

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

RADIO & ELECTRONICS CONSTRUCTOR

FEBRUARY 1981
Volume 34 No. 6

Published Monthly

First published in 1947

Incorporating The Radio
Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone
01-286 6141

Telegrams
Databux, London

©Data Publications Ltd., 1981. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £9.50, Eire and Overseas £10.50 (U.S.A. and Canada \$25.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production – Web Offset.

ZENER DIODE ANALYSER – Suggested Circuit by G. A. French	334
RECENT PUBLICATIONS	337
NEWS AND COMMENT	338
LOW CURRENT PILOT LAMP by F. L. Stephenson	340
ELECTRONIC DOOR BUZZER – Low consumption unit by A. P. Roberts	341
The INSTRUCTOR – A Practical Introduction to Microprocessors – Part 7 by Ian Sinclair	345
TRADE NOTE – Ultrasonic Transducers	350
IN NEXT MONTH'S ISSUE	351
REVERBERATION UNIT – Self-contained self-powered unit. Reverberation amplitude control by R. A. Penfold	352
SHORT WAVE NEWS – For DX Listeners by Frank A. Baldwin	358
OWIZZEE!! – How to play cricket in comfort by David Arts	360
FAX PROGRESS – Report by Arthur C. Gee	365
FIXING AN F.M. RADIO – In Your Workshop	366
SINGLE I.C. SIGNAL TRACER – Inexpensive design with low component count by M. V. Hastings	372
CIRCULAR HOLE JIG by D. M. Pitkin	376
BOOK REVIEW	377
SEVEN SEGMENT DISPLAYS Electronic Data No. 66	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by LSG Printers, Portland Street, Lincoln.

OUR NEXT ISSUE
WILL BE PUBLISHED
MID-FEBRUARY

MOTORS

1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3rpm Motors 32p. 6 volt standard cassette motors new £1.20. 8 track 12V Replacement Motors 55p. Ex. Equip. BSR record player motors, C129, C197 type, £1.20.

SEMICONDUCTORS

LM340 80p. BY103 10p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. CA3020 45p. 741 22p. 741S 35p. 723 35p. NE555 24p. 2N3773 £1.70. NE556 50p. ZN414 75p. BD238 28p. BD438 28p. CB4069 15p. 4" Red Led Displays, c.c. or c.a. 95p. TIL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p. BY223 20p.

PROJECT BOXES

Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

MOTOROLA PIEZO CERAMIC TWEETERS

No crossover required



2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65

TOOL SALE

Small side cutters 5" insulated handles £1. Radiopliers, snipe nosed insulated handles £1. Heavy duty pliers insulated handles £1.10. Draper side cutters spring loaded £1.

HANDY BENCH VICE

1" Jaw opening, £2.95.



Hand drill, double pinion with machine sut gears, 3/16", only £2.75p plus 50p p&p.

MORSE KEYS

Beginners practice key £1.05. All metal full adjustable type. £2.60

MINIATURE LEVEL METERS

1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

TRANSFORMERS

All 240VAC Primary (postage per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.85 (54p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 20V 2.5 amp £2.45 (54p).

TRIAC/XENON PULSE TRANSFORMERS

1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.

MICROPHONES

Min. tie pin. Omni. uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. DYNAMIC stick microphone dual imp., 600 ohms or 20K, 70-kHz., attractive black metal body £7.75. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromed copper body, £12.95 CASSETTE replacement microphone with 2.5/3.5 plugs £1.35 GRUNDIG electric inserts with FET pre amp, 3-6VDC operation £1.00

LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50

RIBBON CABLE

8 way single strand miniature 22p per metre.

SPECIAL OFFER TAPE HEAD DEMAGNETIZER



240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p

MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50




20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £975.

40kHz Transducers. Recr Sender £3.50 pair.

TELEPHONE PICK UP COIL

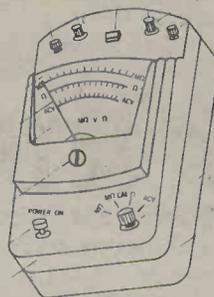Sucker type with lead and 3.5mm plug 62p.



500v electronic megger, push button operation. Ranges:- LO ohm Range 0 - 100Ω (MW scale 5Ω) 0 - 100MΩ Mid scale 5MΩ) £46.75p

Dalo 33PC Etch Resist printed circuit maker pen, with spare tip, 79p.

TERMS:

Cash with order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.

S.A.E. for illustrated lists

MULTI-TESTER



KRT5001 50k/v range doubler multimeter, 0-1kv (125mv LO range) 0-1kv AC. 0-10amp DC. 0-20MΩ res. (LO ohm 0-2k range) 170 x 124 x 50mm £15.50.

YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts, 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

CRIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

POWER SUPPLIES

SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 40 0mA, switchable £3.45. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.

BUZZERS

MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, voltage operating 4-15VDC, 75p each. LOUD 12VDC BUZZER, with, metal case. 50mm diam. x 30mm high 63p. Carters 12 volt Minimate Alarm sirens £7.65p. 12VDC siren, all metal rotary type, high pitched wail, £6.25.

TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

All Antex irons still at pre increase prices, order now as new stock will be going up next month.

Antex Model C 15 watt soldering irons, 240VAC £3.95

Antex Model CX 17 watt soldering irons, 240VAC £3.95

Antex Model X25 25 watt soldering irons, 240VAC £3.95

ANTEX ST3 iron stands, suits all above models £1.65

Antex heat shunts 12p each.

Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 59p each.

Miyarna IC test clips 16 pin £1.95

SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p. DPDT (8 x 7 x 7mm) 55p. DPDT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

PACE Mobile SWR metre, with field strength, PL259 connection, £5.95.

RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz R.F., output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95 BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly - 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.
ALL ORDERS DESPATCHED BY RETURN POST

THE MODERN BOOK CO

WORLD RADIO T.V. HANDBOOK 1981 EDITION £10.50p

REPAIRING POCKET TRANSISTOR RADIOS

by I. R. Sinclair Price £2.55

TEST GEAR PROJECTS

by T. Dixon Price £4.50

ELECTRONICS - BUILD & LEARN

by R. A. Penfold Price £3.20

AUDIO AMPLIFIERS FOR THE HOME

CONSTRUCTOR

by I. R. Sinclair Price £3.00

BEGINNER'S GUIDE TO INTEGRATED

CIRCUITS

by I. R. Sinclair Price £3.50

BEGINNER'S GUIDE TO RADIO

by G. J. King Price £3.50

ELECTRONIC PROJECTS IN THE

WORKSHOP

by R. A. Penfold Price £2.75

110 ELECTRONIC ALARM PROJECTS

FOR THE HOME CONSTRUCTOR

by R. M. Marston Price £4.35

UNDERSTANDING MICROPROCESSORS

by Texas Ins Price £4.00

AMATEUR RADIO OPERATING MANUAL

by R. J. Eckersley Price £4.70

THE OSCILLOSCOPE IN USE

by I. R. Sinclair Price £3.50

PROJECTS FOR THE CAR & GARAGE

by G. Bishop Price £4.00

SIMPLE CIRCUIT BUILDING

by P. C. Graham Price £2.75

UNDERSTANDING HI FI SPECIFICATIONS

by John Earl Price £3.40

BEGINNER'S GUIDE TO DIGITAL

ELECTRONICS

by I. R. Sinclair Price £3.50

ELECTRONICS POCKET BOOK

by P. J. McGoldrick Price £5.00

PROJECTS IN RADIO & ELECTRONICS

by I. R. Sinclair Price £2.50

UNDERSTANDING CALCULATOR MATH

by Texas Ins. Price £4.00

UNDERSTANDING SOLID STATE

ELECTRONICS

by Texas Ins Price £4.00

AMATEUR RADIO TECHNIQUES

by P. Hawker Price £3.70

COST EFFECTIVE PROJECTS AROUND

THE HOME

by J. Watson Price 4.50

AUDIO CIRCUITS & PROJECTS

by G. Bishop Price £5.35

PRINTED CIRCUIT ASSEMBLY

by M. J. Hughes Price £2.75

MICROPHONES IN ACTION

by V. Capel Price £5.00

BEGINNER'S GUIDE TO COLOUR

TELEVISION

by G. J. King Price £3.50

HOW TO BUILD ELECTRONIC KITS

by V. Capel Price £2.50

ELECTRONIC GAME PROJECTS

by F. G. Rayer Price £2.75

UNDERSTANDING DIGITAL

ELECTRONICS

by Texas Ins. Price £4.00

HOW TO BUILD SPEAKER ENCLOSURES

by A. Badmaieff Price £3.50

BEGINNER'S GUIDE TO HAM RADIO

by L. Buckwalter Price £3.50

We have the Finest Selection of English and American Radio Books in the Country
ALL PRICES INCLUDE POSTAGE

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone: 01-402 9176

Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

MASTER ELECTRONICS

LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope.
- Recognition of components.
- Understanding circuit diagrams.
- Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.


MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK - THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library.
- Special educational Mini-Computer supplied ready for use.
- Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

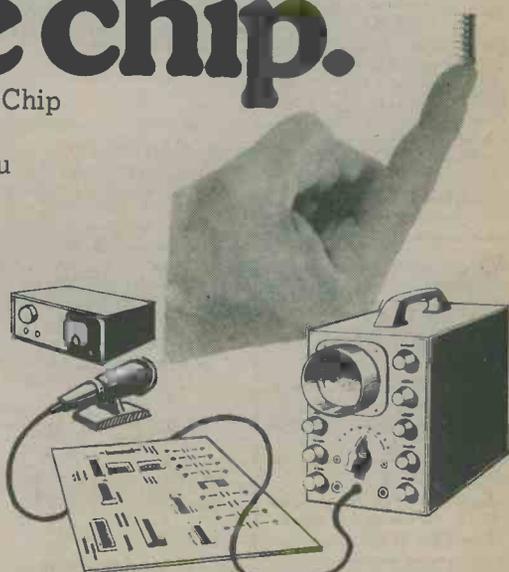- Radio Amateurs Licence.
- Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.



Please send your FREE brochure without obligation to **REC/2/813**

Name

Address

I am interested in -

PRACTICAL ELECTRONICS

COMPUTER TECHNOLOGY

OTHER SUBJECTS

(please state your interest)

BLOCK CAPS PLEASE

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.

MAGENTA ELECTRONICS LTD.

R.E.C. PROJECT KITS

Make us YOUR No. 1 SUPPLIER OF KITS and COMPONENTS for R.E.C. Projects. We supply carefully selected sets of parts to enable you to construct R.E.C. projects. Project kits include ALL THE ELECTRONICS AND HARDWARE NEEDED - we have even included appropriate screws, nuts and I.C. sockets. Each project kit comes complete with its own FREE COMPONENT IDENTIFICATION SHEET. We supply - you construct. PRICES INCLUDE CASES UNLESS OTHERWISE STATED. BATTERIES NOT INCLUDED. IF YOU DO NOT HAVE THE ISSUE OF R.E.C. WHICH CONTAINS THE PROJECT - YOU WILL NEED TO ORDER THE INSTRUCTIONS/REPRINT AS AN EXTRA - 45p. each.

LIGHT CHANGE ALARM Dec. 78. £11.84

In daylight detects someone moving around a room - after dark can be triggered by just torchlight. Units output rs from a relay (included).

DYNAMIC MIC PRE AMP Sept. 78 £5.82

Features the ZN424E - with very low distortion and noise.

ULTRA SENSITIVE ULTRASONIC REMOTE CONTROL Feb 79 £12.45 and DOPPLER SHIFT ADD ON UNIT Mar 79. extra £5.22

First part covers the construction of a sensitive remote control switch - an ultrasonic transmitter and receiver. The Doppler Shift add on unit detects movement within the vicinity of the transducers, and so has applications as a burglar alarm.

RING OF LEDS PRINT TIMER Jan 80 £11.22.

Unusual display indicates 8 segments of timing period. A ring of 8 leds light progressively. Switch selectable timing periods of 1, 2, 3, and 4 minutes. Very smartly housed in a Vero Case.

LOGIC TESTER Jan 80 £5.89.

Detects overload, logic state and pulse voltages in TTL circuits. A piece of veroboard is included - but the layout is left to the constructor. Portable. Battery operated. Supplied with test leads.

TELEPHONE BELL REPEATER Feb 80 £7.48.

Includes 2 cases and speakers. Twin fig 8 cable to link units 7p per metre extra. Remote unit warns when the telephone rings. Battery powered.

INFRA RED INTRUDER ALARM. Mar 80 £9.98 less cases.

Invisible infra red beam protects property - when the beam is broken the relay in the receiver is activated. Max. range 3 metres. Kit includes relay. Requires 9V supply.

STEREO MIXER Mar. 80 £12.73

Mixes high impedance dynamic mic and nurse inputs. Based on 4 LF351 ICs. Two dual pots form the controls for mic. and line. Sockets for inputs and outputs.

CONSTANT CURRENT NI-CAD CHARGER. Sept 80. £19.98

Charges up to 10 cells - suitable for all normal ni-cads. Continuously variable output current. Panel meter indicates the output current. Supplied with leads.

BASIC SHORT WAVE RADIO June 78 £18.95

3 band trf design covering 1.2 to 24 MHz. Features five front panel controls - wavechange, bandset, bandspread, reaction, and aerial attenuator. Built on a pcb. The frequency range covers all the HF broadcast and amateur bands.

3 BAND SHORT WAVE PRESELECTOR Feb 79 £15.98

Uses a dual gate MOSFET. Tunes from 1.6 to 30 MHz in 3 bands. Adjustable rf gain control. Provides additional selectivity and sensitivity when used with a receiver.

BEGINNERS MEDIUM WAVE RADIO Aug. 79. £6.98

Provides crystal earpiece reception of the M.W. band. Crystal earpiece is supplied.

TOP BAND FERRITE AERIAL UNIT Sept 79 £8.98

An active tuned and amplified 160 metre band ferrite rod aerial unit. Provides directional reception facilities when used with a 160 metre receiver. Reduces interference and increases sensitivity.

SINGLE CHIP M.W. RADIO Sept 79 £11.37

Simple sensitive M.W. receiver with loudspeaker. Uses an LM389 IC for rf gain, af gain and power output. Ideal for beginners.

SHORT WAVE AERIAL TUNING UNIT Dec 79 £11.98

Improves receiver performance over 1.6MHz to 30MHz. Provides an increase in signal strength and rejection of strong interfering signals, spurious responses etc.

SIMPLE SHORT WAVE SUPERHET. Feb and Mar 80 £27.39

Covers 180 to 20 metres. No alignment problems. Very low battery current. Plug in coils. Uses a dual gate MOSFET as a mixer. Regenerative RIF stage allows reception of a.m., c.w., and s.s.b.

80 METRE AMATEUR BAND RECEIVER July 80 £19.98

Expressly designed for ssb and cw amateur signals. This simple homodyne design provides world wide reception of amateur transmissions. Housed in a smart Vero case.

PORTABLE SHORT WAVE RADIO Aug 80. £18.94.

Suitable for beginners. Covers 25, 31, 41, and 49 metre bands. Fitted with telescopic aerial. Use of TB820M amplifier IC provides loudspeaker output. Regenerative t.r.f. receiver. Smart ABS case.

LATEST KITS: S.A.E. OR 'PHONE FOR PRICES

MAGENTA ELECTRONICS LTD.

RC3, 98 CALAIS ROAD, BURTON-ON-TRENT,
STAFFS., DE13 0UL. 0283-65435. 9-12, 2-5 MON.-FRI.
MAIL ORDER ONLY

ADD 35p. P.&P. TO ALL ORDERS. ALL PRICES INCLUDE 15% V.A.T. OFFICIAL ORDERS FROM SCHOOLS ETC. WELCOME. ENQUIRIES MUST INCLUDE S.A.E. OVERSEAS: SEND ORDER WITH 3 INTERNATIONAL POSTAL COUPONS WE WILL QUOTE EXACT PRICE BY AIR MAIL.

WIRE & BFPO ORDERS U.K. PRICES - LESS 10% (COVERS V.A.T. REFUND & EXPORT DOCUMENTS) PAYMENT: STERLING U.K. BANK DRAFT, U.K. POSTAL ORDERS or U.K. CHEQUE. ENQUIRIES: ENCLOSE 2 INTERNATIONAL POSTAL COUPONS.



80/81 ELECTRONICS CATALOGUE

**KITS
ICs
TRANSISTORS
CAPACITORS**

Hundreds of illustrations, product data, circuits and details of all our kits and educational courses. Up to date price list included. All products are stock lines for fast delivery by FIRST CLASS POST. Send 6 x 10p stamps for your copy.

**TOOLS
RESISTORS
HARDWARE
CASES**

ADVENTURES WITH ELECTRONICS

by Tom Duncan

An easy to follow book suitable for all ages, ideal for beginners. No Soldering. Uses an 'S Dec' breadboard. Gives clear instructions with lots of pictures. 16 projects - Including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec and the components for the projects. Adventures With Electronics. £1.75. Component Pack £16.72 less battery.

ADVENTURES WITH MICROELECTRONICS

Same style as above book; 11 projects based on integrated circuits - includes: dice, two-tone doorbell, electronic organ, MW/LW radio, reaction timer, etc. Component pack includes a Bimboard, 1 plug-in breadboard and the components for the projects. Adventures with Microelectronics £2.35. Component pack £27.95 less battery.

The INSTRUCTOR A FULLY CONSTRUCTIONAL PROJECT INCORPORATING AN INS8060 MICROPROCESSOR CHIP

• A Practical introduction to microprocessor functioning
Relatively small number of components required
Instructional

8 part series. Part 1 in Aug. 80 issue. Reprints of previously published part available. 45p each part.

The Instructor is a low cost assembly which provides a practical introduction to microprocessors and their functions. It is not a computer, but it is a working circuit which allows microprocessor working to be followed, one program step at a time. Build the Instructor and you will gain microprocessor experience. The series is based on the INS8060 microprocessor IC, also known as the SC/MP Mk.2. Circuits are built on a plug in Eurobreadboard. Kit is available with or without the breadboard. INSTRUCTOR COMPONENT PACK: Including Eurobreadboard £27.85; or less Eurobreadboard £21.65.

HEADPHONES AND EARPIECES.

The short wave radios require a crystal earpiece or high impedance mono headphones.

MONO HEADPHONES £2.98.

High impedance 2k. Sensitive, Lightweight. Adjustable padded earpieces. Fitted with 3.5mm jack plug.

CRYSTAL EARPIECE 56p.

Fitted with lead and 3.5mm jack plug. Top quality.

STETHOSCOPE. 69p.

Optional attachment for use with our earpiece.

TOWERS INTERNATIONAL TRANSISTOR SELECTOR £10.35

ANTEX X25 SOLDERING IRON. 25W.

£4.98.

SOLDERING IRON STAND. £2.03.

SPARE BITS. Small, standard, large.

65p each.

SOLDER. Handy size. 95p.

EUROBREADBOARD. £6.20.

LOW COST LONG NOSE PLIERS. £1.68

LOW COST CUTTERS. £1.69.

SIREN. 12V. £5.18

P.C.B. ASSEMBLY JIG. £11.98.

P.C.B. ETCHING KIT. £4.98.

MONO HEADPHONES. 2K Padded.

Superior, sensitive. £2.98.

STEREO HEADPHONES. 8 ohm.

Padded. £4.35.

MAGENTA gives you FAST DELIVERY BY FIRST-CLASS POST OF QUALITY COMPONENTS AND KITS. All products are stock lines and are new and full specification. We give personal service and quality products to all our customers - HAVE YOU TRIED US?

INTO ELECTRONICS CONSTRUCTION

R.E.C. LATEST KITS

Tremelo modulation unit Nov 80

£11.27.

CMOS combination switch Nov 80

£7.22.

Coil coupled 5W converter Nov 80

£20.90.

Go no go transistor tester Oct 80

£7.58.

Personal M.W. Radio, Oct 80.

£10.36.

PRICES INCLUDE V.A.T.

BI-AND SAVE SALE-81

<p>200 Mixed Diodes - mainly Germ OA81-91-1N34/60 GC61/62, etc. Case DO-7. Coded and uncoded - You to test - value all the way! O/N. SJ127. £1.00 per Pak.</p>	<p>BC108 FALLOUTS</p> <p>50 NPN BC107/108 SJ124 £1.00 Manufacturers out of spec. on volts or gain or neither - Metal TO18 case - You test.</p> <p>50 PNP BC177/178 SJ1244 £1.00</p>	<p>NPN</p> <p>BD131 TO-126-NPN untested. O/N. SJ84. 25 for £1.00</p> <p>SCR'S</p> <p>TO66 SCR'S 5 Amp - ALL GOOD - untested for volt - good yield 400 plus O/N. SJ130. 10 for £1.</p>	<p>IC SOCKET PAKS</p> <p>SJ36 14 8 pin SJ41 6 22 pin SJ37 12 14 pin SJ42 5 24 pin SJ38 11 16 pin SJ43 4 28 pin SJ39 8 18 pin SJ44 3 40 pin SJ40 7 20 pin</p> <p>ALL AT ONLY £1.00 each</p>
<p>SIL. DIODES</p> <p>200 Mixed Diodes - mainly SILICON case DO-7 OA200/202. General purpose 200mA marked and uncoded - you to sort and test - Outstanding Value! O/N. SJ128. £1.00 per Pak.</p>	<p>DIODES</p> <p>300 IN4148 Type - uncoded Silicon Diodes Case DO-35 - you to test. O/N. SJ 129. £1.00 per Pak.</p> <p>Silicon Fast Switch NPN - like 2N706/2N2369 - You test! O/N. SJ125. 50 for £1.00</p>	<p>AERIALS</p> <p>FM Indoor Tape/Ribbon Aerial O/N. 107. 40p each</p> <p>Hi-Fi CAR AERIAL 4-section fully retractable and locking SPECIAL PRICE O/N. 109. £1.40 each</p>	<p>The last of the Germanium PNP - OC71-71-75 etc. Mullard Black/Glass Type - You test (5 could cost you that!) O/N. SJ126. 50 pcs £1.00</p> <p>GERM. POWER TRANS.</p> <p>AD149-OC26-AD140 £0.50 each AD142-OC28-2N3614 £0.65 each</p>
<p>AUDIO AMPLIFIER</p> <p>5 watt Audio Amplifier Module. Special Clearance offer O/N. AL20. £2.50</p>	<p>GERM. TRANSISTORS</p> <p>Special Introductory Offer COMPUTER IC'S</p> <p>EPROM 2708 at £3.00 EPROM 2516/2716 at £6.00 D.RAMS 4116 at £2.25</p>	<p>BI-PAK'S OPTO BARGAIN!</p> <p>Valued at over £10 - Normal Retail</p> <p>We offer you a pack of 25 Opto devices to include LED's large and small in Red, Green, Yellow & Clear. 7 segment Displays both Common Cathode and Common Anode PLUS bubble type displays - like DL-33. Photo Transistors - similar to OCP71 and Photo Detectors - like MEL11-12. This whole pack of 25 devices will cost you just... £4.00!</p> <p><i>And we guarantee your money back if you are not completely satisfied.</i> Full data etc included O/N. SJ120.</p>	<p>MICRO E</p> <p>NPN silicon transistors plastic case - perfect and coded. C108 equals BC108 TO-18 plastic O/N. SJ29. 50 off £2.50 100 off £4.00. 1,000 off £35.00</p>
<p>HEADPHONES</p> <p>NEW Improved Lightweight Stereo Headphones including double headband and padded earcups - Impedance 8ohms - Frequency 30-18000HZ ALL Black O/N. 885. £4.00</p> <p>As above but with coiled lead and rotary volume controls O/N. 884. £7.00</p>	<p>SPECIAL OFFER LINEAR IC'S</p> <p>NE555 5 for £0.90 741P 5 for £0.80 NE556 5 for £2.50 LM380 5 for £3.50 72723 14 pin 5 for £1.75</p>	<p>And we guarantee your money back if you are not completely satisfied. Full data etc included O/N. SJ120.</p>	<p>AUDIO ACCESSORIES</p> <p>SJ75. FM coax cable - plain copper conduction cellular polythene insulated and plain copper braided PVC sheath - Impedance 75ohms £0.10 per metre SJ76. 1 Board containing 2 x 5 pin DIN sockets 180° 02-2 pin DIN loudspeaker sockets £0.30 SJ77. A 5-pin DIN 180° chassis/normal socket incl. DPDT switch £0.20</p>
<p>HEADPHONE ACCESSORIES</p> <p>7 metre Headphone Extension Lead O/N. 136. £1.50</p>	<p>Semiconductors from Around the World</p> <p>100 A collection of Transistors, Diodes, Rectifiers, Bridges, IC's, SCR'S Triacs both Logic & Linear plus Opto's all of which are current everyday usable devices. 100</p> <p>Guaranteed Value over £10 at Normal Retail Price yours for only £4.00 Data etc in every pak. Order No. SJ220.</p> 		<p>DISC CERAMIC CAP</p> <p>100 Disc Ceramic CAP. Mixed values covering complete range 3PF - 4,700PF. SUPER VALUE O/N. SJ121. £1.00</p>
<p>ANTEX</p> <p>Antex X25 Iron - 25watt soldering iron. OUR SUPER SALE PRICE Great reduction. O/N. 1931. £4.00</p> <p>ST3 Iron Stand - Suitable for above - OUR Sale Price O/N. 1939. £1.25 each.</p>	<p>SILICON TRANS.</p> <p>SJ25. 100 Silicon NPN transistors all perfect and coded - mixed types with data and equivalent sheet - no rejects £2.50</p> <p>SJ26. 100 Silicon PNP transistors all perfect and coded - mixed types and cases, data and equivalent sheet £2.50</p> <p>SJ27. 50 Assorted pieces of SCR'S, diodes and rectifiers incl. stud types, all perfect - no rejects, fully coded - £2.50 incl.</p>	<p>PRECISION VOM MULTIMETER 20,000ohms/volts DC. Complete with test leads and instructions. OUR SPECIAL OFFER PRICE</p> <p>O/N. 1323 £11.00 each. Use your Barclay or Access Card!</p> 	<p>SWITCHES</p> <p>Push-to-make. 6mm panel mounting. O/N. SJ131. 5 for £0.50</p> <p>Push-to-break as above O/N. SJ132. 4 for £0.50</p> <p>Silicon Heat Sink Compound 3mL in syringe £0.25</p>
<p>POPULAR (CMOS)</p> <p>CD4001 CD4007 CD4011 CD4017 CD4081</p> <p>1 of each normal price £1.80 for 5 - our price £1.30 for 5 O/N. SJ1245</p>	<p>TTL'S</p> <p>SJ28. 20 TTL74 series gates - assorted 7401-7460 £1.00</p> <p>SJ53. Mammoth IC Pak - Approx 200 pcs assorted fall-out integrated circuits including logic 74 series - Linear - audio and DTL many coded devices but some unmarked - you to identify £1.00</p>	<p>NPN TRANSISTORS</p> <p>SJ68. 30 ZTX300 type transistors NPN pre-formed for P/C Board colour coded Blue - all perfect £1.00</p> <p>SJ70. 25 BC107 NPN TO106 case perfect transistors code Green spot £1.00</p> <p>SJ71. 25 BC177 PNP TO106 case perfect transistors code C1395 £1.00</p> <p>SJ72. 4 2N3055 silicon power NPN transistors TO3 £1.00</p>	<p>LED</p> <p>2nd Quality Packs</p> <p>1507. 10 Assorted colours and sizes £0.65</p> <p>S122. 10.125 RED. £0.50</p> <p>S123. 10.2 RED. £0.50</p> <p>LED CLIPS</p> <p>1508/125. 125. 5 for £0.10 1508/2. 2. 5 for £0.12</p>
<p>PLUGS & SOCKETS</p> <p>Set of 4 1-metre Colour coiled leads with phono plug ends - ideal for audio and test use. Outstanding Value O/N. SJ122. £1.00 per Pak</p> <p>1mm Plugs and Sockets in Red and Black. O/N. SJ123. 5 pairs £1.00</p>	<p>RESISTORS</p> <p>SJ1. 200 Resistors mixed values £0.50</p> <p>SJ2. 200 Carbon resistors 1/4 watt pre-formed £0.50</p> <p>SJ3. 100 1/2 watt miniature resistors mixed values £0.50</p> <p>SJ4. 60 1/2 watt resistors mixed values £0.50</p> <p>SJ5. 50 1-2 watt resistors mixed pot values £0.50</p> <p>SJ7. 30 2 1/2 watt wirewound resistors mixed £0.50</p>	<p>POTENTIOMETERS</p> <p>16173. 15 Assorted Pots £0.50</p> <p>SJ54. 20 Assorted Slider Pots. £1.00</p> <p>SJ56. 10 100K Lin Slider Pots £0.50</p> <p>16186. 25 Pre-sets Assorted £0.50</p> <p>SJ49. 8 Dual gang carbon pots log and lin mixed values. £1.00</p> <p>SJ50. 20 Assorted slider knobs - chrome/black. £1.00</p>	<p>MISCELLANEOUS</p> <p>SJ20. 2 Large croc clips 25A rated - ideal for battery chargers, etc. £0.30</p> <p>SJ21. Large 7 1/2" Mains Neon Tester - screwdriver chrome finish £0.85</p> <p>SJ22. Small pocket size Mains Neon Tester screwdriver. £0.55</p> <p>SJ23. Siemens 220v AC relay DPDT contacts 10 amp rating - housed in plastic case £1.00</p> <p>SJ24. Black PVC Tape (1/2) 15mm x 25m - strong tape for electrical and household use. £0.35 per roll</p>
<p>CAPACITORS</p> <p>SJ11. 150 Capacitors mixed types and values £0.50</p> <p>SJ12. 60 Electrolytics all sorts mixed £0.50</p> <p>SJ13. 40 Polyester/polystyrene capacitors mixed £0.50</p> <p>SJ14. 50 C280 type capacitors mixed £1.00</p> <p>SJ15 Polystyrene caps 1 160v 50p £0.50</p> <p>SJ16. 40 Low volts electrolytics mixed values up to 10v. 10.50</p>	<p>CASSETTES</p> <p>SUPER VALUE and a GREAT SAVING!!! C120 Dinky Cassettes - Low noise - astounding value and sound. O/N. SJ32. 10 for £3.50</p> 	<p>TRIACS</p> <p>4A 400v TO-202 non-isolated TAG136D £0.40</p> <p>8A 400v TO-220 isolated TAG425 £0.60</p> <p>Diac D32/BR100 £0.15</p> <p>SCR C106D plastic case £0.30</p>	<p>ODDMENTS</p> <p>16170. 50 metres asst. colours single strand wire £0.50</p> <p>16187. 30 metres stranded wire mixed colours £0.50</p> <p>16178. 5 Malm slider switches assorted. £0.50</p> <p>SJ76. 1 Board containing 2 x 5-pin. DIN sockets 180 and 2 x 2-pin. DIN Loudspeaker sockets. £0.30</p>
<p>TRANSFORMERS</p> <p>MINIATURE MAINS Primary 240v.</p> <p>No. Secondary £0.75</p> <p>2021. 6v-0-6v 100mA £0.95</p> <p>2023. 12v-0-12v 100mA £0.95</p> <p>240v Primary 0-55v. £5.50</p> <p>2035. 2A Secondary</p>	<p>Send your orders to Dept RC2 BI-PAK PO BOX 6 WARE HERTS. SHOP AT: 3 BALDOCK ST. WARE HERTS. TERMS: CASH WITH ORDER. SAME DAY DESPATCH. ACCESS. BARCLAYCARD ALSO ACCEPTED. TEL: (0920) 3182. GIRO 388 7006 ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING</p>		<p>KNOB'S</p> <p>SJ62. 5 15mm chrome knobs standard push fit £0.50</p> <p>SJ63. Instrument knob - black winged (29 x 20mm) with pointer. 1" standard screw fit. £0.15</p> <p>SJ64. Instrument knob - black/silver aluminium top (17 x 15mm). 1" standard screw fit. £0.12</p>

NEW! JUST PUBLISHED TOWERS INTERNATIONAL MICROPROCESSOR SELECTOR



**ONLY
£16.25
POST PAID**

If you come into contact with microprocessors (whether as hobbyist, student, circuit engineer, programmer, buyer, teacher, serviceman, or just humble reader) you often find you would like data information on a specific microcircuit element. Specifications apart, you may be even more interested in where you can get the device in question. And perhaps even more important still (particularly with obsolete devices), you may be looking for guidance on a readily-available second source or possible substitute.

This microprocessor selector (working on the same basis as the TRANSISTOR, FET, and OPAMP LINEAR-IC selectors already compiled by the author) is designed to provide in one handy reference volume a comprehensive body of readily-accessible, user-slanted essential information across the field of microprocessors.

In the data tabulations will be found set out the essential basic specifications of over 7,000 commercially-available microprocessor 'chips', including not only the microprocessor elements themselves (e.g. MPUs and CPUs) but also the many other LSI 'support' circuits (e.g. ROMs, RAMs, PROMs, clocks, UARTs, I/Os) normally used in harness with the microprocessors proper to produce complete microcom-

puters or microcontrollers. For ease of reference, the descriptions and control specifications of the individual circuits are set out in the detailed data tables on separate single lines, arranged in alpha-numeric order by type number.

For the newcomer to the very new field of microprocessors, the selector includes a full introductory note on these devices before the data tables.

Besides this, the tables are supplemented by separate appendices giving additional information on: (a) Microprocessor chip applications (and codings); (b) Microprocessor 'families'; (c) Microprocessor LSI chip manufacturers (and codings); (d) Semiconductor LSI technologies (and codings); (e) Microprocessor chip packages (and codings); (f) Microprocessor trainer and development systems; (g) Microprocessor bibliography; (h) Manufacturers' house codes; (i) Glossary of microprocessor terms; (j) Explanatory notes to tabulations.

This selector is fully international in scope and covers not only microprocessors and related devices from the USA and Continental Europe, but also from the UK and the Far East (Japan).

TO:- DATA PUBLICATIONS LTD, 57 MAIDA VALE, LONDON W9 1SN

Please send me copy/copies of

**TOWERS INTERNATIONAL
MICROPROCESSOR SELECTOR**

Price: £16.25 inc P&P


NAME

ADDRESS

(BLOCK CAPITALS PLEASE)

IT'S AS EASY AS A,B,C...

...ASK OUR DEALERS.

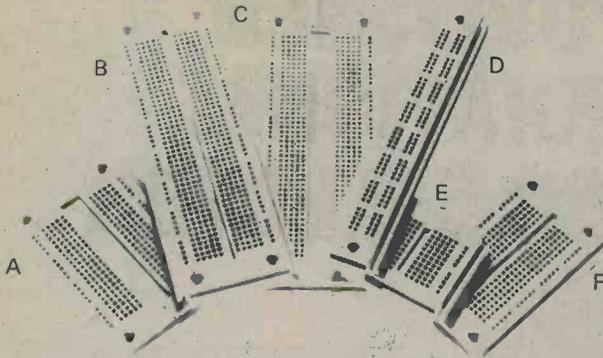

- A EXP 650 For microprocessor chips. **£3.60**
- B EXP 300 The most widely sold breadboard in the UK; for the serious hobbyist. **£5.75**
- C EXP 600.6" centre channel makes this the Microprocessor Breadboard. **£6.30**
- D EXP 4B An extra 4 bus-bars in one unit. **£2.30**
- E EXP 325 Built in bus-bars accepts 8, 14, 16 and up to 22 pin ICs. **£1.60**
- F EXP 350 270 contact points, ideal for working with up to 3 x 14 pin DIPS. **£3.15**
- G PB6 Professional breadboard in easily assembled kit form. **£9.20** (Not illustrated.)
- H PB 100 Kit form breadboard recommended for students and educational uses. **£11.80** (Not illustrated.)

& IT'S AS EASY AS 1,2,3 with THE EXPERIMENTOR SYSTEM

- SCRATCHBOARD
- BREADBOARD
- MATCHBOARD

1. EXP 300PC which includes one item. A matchboard pre-drilled PCB - **£1.32**
2. EXP 302 which includes three items. Three 50-sheet scratchboard workpads - **£1.65**
3. EXP 303 which includes three items. Two matchboards and an EXP 300 solderless breadboard - **£8.60**.
4. EXP 304 which includes four items. Two matchboards and EXP 300 breadboard and a scratchboard workpad - **£9.30**

The above prices do not include P&P and 15% VAT

TOMORROW'S TOOLS TODAY

CONTINENTAL SPECIALTIES CORPORATION C.S.C. (UK) Limited, Dept. 1600
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682.
Telex: 817477.

NAME _____

ADDRESS _____

I enclose cheque/PO for £ _____
or debit my Barclaycard, Access, American Express card
No. _____ Exp. date _____
or Tel: (0799) 21682 with your card number and your order will be in the
post immediately.

A EXP 650 £5.00	Qty. Reqd.	B EXP 300 £7.76	Qty. Reqd.
C EXP 600 £8.39	Qty. Reqd.	D EXP 4B £3.50	Qty. Reqd.
E EXP 325 £2.70	Qty. Reqd.	F EXP 350 £4.48	Qty. Reqd.
G PB6 £11.73	Qty. Reqd.	H PB 100 £14.72	Qty. Reqd.

Experimentor System

1 EXP 300 PC £2.38	Qty. Reqd.	2 EXP 302 £2.79	Qty. Reqd.
3 EXP 303 £11.04	Qty. Reqd.	4 EXP 304 £11.85	Qty. Reqd.

Boxed prices include P & P and 15% VAT
If no dealer in your area contact CSC direct. **FREE catalogue tick box**

Continental Specialties Corporation (UK) Limited, Dept. 1600
Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

AITKEN BROTHERS,
35 High Bridge, Newcastle Upon Tyne, NE1 1EW.
Tel: 0632 26729.

ARROW ELECTRONICS LTD.,
Leader House, Coptfold Road, Brentwood, Essex.
Tel: 0277 226470.

BASIC ELECTRONICS LTD.,
18 Epsom Road, Guildford, Surrey, GU1 3JN.
Tel: 0483 39984.

BI-PAK SEMICONDUCTORS,
P.O. Box 6, Ware, Herts.
Tel: 0920 3442.

F. BROWN & CO.,
45 George IV Bridge, Edinburgh, EH1 1EJ, Scotland.
Tel: 031 225 3461. Telex: 922131.

THE CHILDRENS SHOP & TACKLE BOX.,
73-75 High Street, Ryde, Isle of Wight.
Tel: 0983 63437.

CUBEGATE LTD.,
301 Edgware Road, London, W2 1BN.
Tel: 01 724 3565.

ETESON ELECTRONICS,
15b Lower Green, Poulton-Le-Fylde, Blackpool, FY6 7JL.
Tel: 0253 885107.

H. GEE ELECTRONIC SUPPLIES,
94a Mill Road, Cambridge, CB1 2BD.
Tel: 0223 358019.

LEEDS AMATEUR RADIO,
27 Cookridge Street, Leeds, LS2 3AG.
Tel: 0532 452657.

MARSHALLS,
108A Stokes Croft, Bristol.
Tel: 0272 426801.

85 West Regent Street, Glasgow, G2, Scotland.
Tel: 041 332 4133.

325 Edgware Road, London, W2.
Tel: 01 723 4242.

40 Cricklewood Broadway, London, NW2 3ET.
Tel: 01 452 0161.

RASTRA ELECTRONICS LTD.,
275-281 King Street, Hammersmith, London, W6.
Tel: 01 748 3143. Telex: 24443 RASTRA G.

SHUDEHILL SUPPLY COMPANY,
53 Shudehill, Manchester, M4 4AW.
Tel: 061 834 1449.

SPECTRON ELECTRONICS (M/C) LTD.,
7 Oldfield Road, Salford, M5 4NE.
Tel: 061 834 4583.

SWANLEY ELECTRONICS,
32 Goldsel Road, Swanley, Kent, BR8 8EZ.
Tel: 0322 64851.

TECHNOMATIC LTD.,
17 Burnley Road, London, NW10 1ED.
Tel: 01 452 1500. Telex: 922800.

TOMORROW'S TOOLS TODAY

Also ask your local stockist.
If no dealer in your area, contact CSC direct.



CONTINENTAL SPECIALTIES CORPORATION C.S.C. (UK) Limited, Dept. 1600
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682
Telex: 817477

TRANSISTORS

AC126	16p	BD239C	29p	D45C2 40v. 30w	9p	ZTX341	9p	2SA518	38p
AC127 12v .3wt	16p	BD240	30p	220HFE 50MHz	50p	2G103	33p	2SA634	80p
AC128 16v .3wt	16p	BD241 45v 40w	22p	DS70 Darl. 10wt	22p	2G302	12p	2SB75	25p
AC153	11p	BD242B 90v 40w	30p	GET102	46p	2G309	30p	2SB77	25p
AC176	11p	BD246	32p	GET111	45p	2G339A	20p	2SB135	25p
AC188	10p	BD253	44p	GET120	30p	2G371	18p	2SB136	25p
AC188	10p	BD375	35p	M103G MOSFET	30p	2N456A	71p	2SB156	60p
ACY20	30p	BD437	35p	MA393	25p	2N597	16p	2SB175	20p
ACY21	20p	BD438	28p	MD7000	£2.25	2N598	16p	2SB176	20p
ACY28	22p	BD597 60v 55w	36p	ME2	13p	2N601	£1.50	2SB187	25p
AD181 20v 6wt	40p	BD677 60v 40w	50p	ME0412	14p	2N644	22p	2SB457	25p
AD162 20v 6wt	40p	BD678 Pwr. Darl.	50p	ME8003	20p	2N706A	101p	2SC1061 50v 25w	50p
AF119	15p	BDX33B Pwr. Darl.	50p	MJ481 BDY23	23p	2N708	9p	2SD234 60v 25w	50p
AF124	27p	BDX42 60v. Darl.	50p	MJE371	40p	2N914	15p	2SD315D	50p
AF126	27p			MJE2371	80p	2N918 15v VHF	12p	353-3 40v 5wt	22p
AF139	23p	BDX77	36p	MJE2901T (Hlgain	17p	2N929	28p	362-4 300v 6wt A/F	30p
AF178	35p	BDY20	86p	2955)	50p	2N984	28p	Video Amp (BF459)	30p
AF180	35p	BF115	18p	MJE2955 70v 90w	45p	2N987	16p	868-01 Plast. 10wt	15p
AF181	33p	BF137	11p	M115 Russian	25p	2N1091	16p	1034 Plast. 10wt	15p
AF239 15v VHF	35p	BF164	18p	M141 Russian	25p	2N1302	16p	16120 (MPSU5/	19p
ASV60	35p	BF167	18p	MP6513 60v 3w	31p	2N1303	16p	BD238)	19p
ASV63	35p	BF178	23p	MPF131 Dual	15p	2N1395	25p	40235	50p
ASV73	35p	BF179	23p	MOSFET	15p	2N1484	36p	40250	36p
ASZ21	4p	BF180	12p	MPU131 Prog. Uni J.	15p	2N1485 60v 25w	36p	40250VI (2N3054 + Ht.	40p
AU110	£1.43	BF181	8p	MRF502 Improved	15p	2N1487	90p	40316 40v. 50w	36p
AU113	£1.03	BF182	18p	BFY90	50p	2N1490	20p	40372 (2N3054 + Ht.	40p
AU110	70p	BF183	18p	116A Russian	25p	2N1500	30p	sink)	40p
BC107A/B	7p	BF184	18p	142A Russian	25p	2N1507	18p	40349v2 160v 1w	30p
BC108A/B/C	7p	BF185	18p	NKT45	23p	2N1711	15p	40394 60v 1w	30p
BC109B	7p	BF194A/B	5p	NKTAS2	20p	2N1716	28p	40633 NPN 40w	36p
BC125B	3p	BF195C/D	5p	NKTB54	30p	2N1748	28p	40911 (2N6261 + Ht.	40p
BC140	15p	BF196	5p	NKT152	38p	2N2192A	15p	sink)	40p
BC141	11p	BF197 20v VHF	5p	NKT153	24p	2N2212A	8p		
BC147A/B/C	5p	BF198	5p	NKT154	26p	2N2369	10p		
BC148A/B/C	5p	BF200	13p	NKT251	18p	2N2401	7p		
BC149A/B/C/S	5p	BF224	4p	NKT775	16p	2N2412	27p		
BC154	7p	BF244 FET	7p	NKTME2	13p	2N2483	28p		
BC157A	5p	BF245	6p	NSD102 45v 10wt	23p	2N2484	10p		
BC158A/B	5p	BF256FET	8p	NSD129 Plastic 10wt	23p	2N2586	15p		
BC159B/C	5p	BF256B/LC FET	6p	NSD131 250v 10wt	30p	2N2514	4p		
BC159B/C	5p	BF257	20p	NSD134 300v 10wt	30p	2N2887	£2		
BC171B	4p	BF258 see 2N5058	23p	NSD151 30v 10wt	22p	2N2894	11p		
BC172	6p	BF262	29p	Darlington	22p	2N2904	9p		
BC172C	4p	BF263	29p	NSD457 160v 10wt	3p	2N2905 SW/AMP	15p		
BC173	4p	BF274	8p	NSD U45 40v 10wt	30p	2N3006	9p		
BC177A	10p	BF324	31p	Darlington	22p	2N3007/A	9p		
BC178A/B/C	10p	BF336	16p	NSD U51 30v 10wt	22p	2N3026	4p		
BC179B	14p	BF335	15p	OC41	22p	2N3020	25p		
BC182/AL	5p	BF394B	3p	OC42	21p	2N3053	16p		
BC182L	3p	BF451	3p	OC43	55p	2N3054	35p		
BC183A/AL/LC	3p	BF494	10p	OC44	4p	2N3055RCA 80v	68p		
BC184L	5p	BF495	5p	OC45	13p	115wt	24p		
BC186	21p	BF595c FM/AM/GP	9p	OC71	4p	2N3133	25p		
BC187	11p			OC72 (XK 120)	4p	2N3283	25p		
BC204	5p			OC75	15p	2N3418	15p		
BC212/L/B	5p			OC76	4p	2N3553	56p		
BC213L	5p			OC77	15p	2N3583	18p		
BC213LA	3p			OC81 (XK 122)	4p	2N3645	3p		
BC213LB	4p			OC84	30p	2N3703	3p		
BC214B	5p			OC88	30p	2N3704	4p		
BC214L	3p			OC200	41p	2N3707	3p		
BC237A	7p			OC201	66p	2N3711	3p		
BC238	5p			OC202	66p	2N3714	14p		
BC238B/C	7p			OC203	66p	2N3799	18p		
BC239C	7p			OC204	66p	2N3823 FET	25p		
BC251	3p			OC205	66p	2N3906	8p		
BC257B	7p			OC603	50p	2N4000	15p		
BC258B/C	7p			OC701	50p	2N4026	15p		
BC259C	7p			ON222	23p	2N4031	15p		
BC302	15p			P77 Plastic 10wt	15p	2N4062	4p		
BC304	15p			P345A	24p	2N4285	17p		
BC307	7p			P7029	30p	2N4891	10p		
BC308B/C	7p			PXB103	25p	2N4918	15p		
BC309B	7p			RCP701A/B/D 10wt	30p	2N5058 300v .5w	11p		
BC327	5p			R1039 (2010)	54p	2N5147	15p		
BC328	5p			R2008B	£1.18	2N5293 80v 36w	30p		
BC337	6p			R2010B	£1.18	2N5294 80v 36w	30p		
BC338	6p			R2306 100v 40w	26p	2N5295 60v 36w	30p		
BC382L	7p			R2540	£1.70	2N5296 60v 36w	30p		
BC384B	7p			S3017	25p	2N5297 80v 36w	36p		
BC546	5p			SB240	28p	2N5449	3p		
BC547A/B	5p			SFT357	26p	2N5484	37p		
BC548A/B/C	5p			SJE5039	8p	2N5492 75v 50w	36p		
BC549C	5p			SL102	40p	2N5494 60v 50w	36p		
BC558C	5p			TE886	£1	2N5915 (16068)	12v		
BC559	5p			TIP29 40v 30w	22p	450Mhz 6WT R.F.	£2.50		
BC612L	4p			TIP30	22p	2N5954 P. 80v 40w	36p		
BCX32	10p			TIP30C 100v 30w	26p	2N6028 PUJT	6p		
BCX33 60v .75w	10p			TIP31C 100v 40w	26p	2N6101 80v 75w	55p		
BCX34	10p			TIP32A 60v 40w	22p	2N6106 80v 40w	44p		
BCX36	10p			TIP32C 100v 40w	26p	2N6109 60v 40w	44p		
BCY11	28p			TIP41 40v 65w	26p	2N6111 40v 40w	36p		
BCY31	59p			TIP42C 100v 65w	30p	2N6124	24p		
BCY56	10p			TIP48	33p	2N6178 100v 25w	30p		
BCY70	8p			TIP110 60v 50w Darl.	30p	2N6180 100v 25wt	30p		
BCY71	8p			TIP112 100v 50w	45p	2N6181 75v 25w	30p		
BCY72	8p			TIP115 60v 50wt	30p	2N6254	36p		
BCY79B	15p			TIP121 100v 50w	45p	2N6288 30v 40w	36p		
BCZ11	32p			TIP129 40v 30w	22p	2N6290 60v 40w	30p		
BD113	57p			TIP30	22p	2N6292 80v 40w	30p		
BD115	35p			TIP30C 100v 30w	26p	2N6385 80v 100wt	30p		
BD(BRC)116	35p			TIP31C 100v 40w	26p	Darlington	55p		
BD131	15p			TIP32A 60v 40w	22p	2N6486 40v 75w	36p		
BD132	28p			TIP32C 100v 40w	26p	2N6488 90v 75w	36p		
BD133	28p			TIP41 40v 65w	26p	2S701	18p		
BD135 45v 13w	22p			TIP42C 100v 65w	30p	2SA12	42p		
BD136 45v 13w	14p			TIP48	33p	2SA50	36p		
BD137	28p			TIP110 60v 50w Darl.	30p	2SA80	36p		
BD138	28p			TIP112 100v 50w	45p	2SA83	36p		
BD137/8 mch pr	60p			TIP115 60v 50wt	30p	2SA141	36p		
BD140	24p			TIP121 100v 50w	45p	2SA142	36p		
BD142	35p			TIP129 40v 30w	22p	2SA234	50p		
BD156	50p			TIP30	22p	2SA236	50p		
BD182 70v 117w	44p			TIP30C 100v 30w	26p	2SA236	50p		
BD201	86p			TIP31C 100v 40w	26p	2SA354	38p		
BD202	86p			TIP32A 60v 40w	22p	2SA360	34p		
BD203	86p			TIP32C 100v 40w	26p	2SA367	56p		
BD204	86p			TIP41 40v 65w	26p				
BD232	34p			TIP42C 100v 65w	30p				
BD233	20p			TIP48	33p				
BD235	35p			TIP110 60v 50w Darl.	30p				
BD238	25p			TIP112 100v 50w	45p				

D45C2 40v. 30w	9p	2SA518	38p
220HFE 50MHz	50p	2SA634	80p
DS70 Darl. 10wt	22p	2SB75	25p
GET102	46p	2SB77	25p
GET111	45p	2SB135	25p
GET120	30p	2SB136	25p
M103G MOSFET	30p	2SB156	60p
MA393	25p	2SB175	20p
MD7000	£2.25	2SB176	20p
ME2	13p	2SB187	25p
ME0412	14p	2SB457	25p
ME8003	20p	2N706A	101p
MJ481 BDY23	23p	2N708	9p
MJE371	40p	2N914	15p
MJE2371	80p	2N918 15v VHF	12p
MJE2901T (Hlgain	17p	2N929	28p
2955)	50p	2N984	28p
MJE2955 70v 90w	45p	2N987	16p
M115 Russian	25p	2N1091	16p
M141 Russian	25p	2N1302	16p
MP6513 60v 3w	31p	2N1303	16p
MPF131 Dual	15p	2N1395	25p
MOSFET	15p	2N1484	36p
MPU131 Prog. Uni J.	15p	2N1485 60v 25w	36p
MRF502 Improved	15p	2N1487	90p
BFY90	50p	2N1490	20p
116A Russian	25p	2N1500	30p
142A Russian	25p	2N1507	18p
NKT45	23p	2N1711	15p
NKTAS2	20p	2N1716	28p
NKTB54	30p	2N2192A	15p
NKT152	38p	2N2212A	8p
NKT153	24p	2N2369	10p
NKT154	26p	2N2401	7p
NKT251	18p	2N2412	27p
NKT775	16p	2N2483	28p
NKTME2	13p	2N2484	10p
NSD102 45v 10wt	23p	2N2586	15p
NSD129 Plastic 10wt	23p	2N251	

PRICES SO LOW, THE POLICE INVESTIGATED ME TWICE
ALL ENQUIRIES, ETC. MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

VAT & POST PAID
 (UK 2nd Class or Parcel)
MINIMUM ORDER £3 (excluding catalogue) OTHERWISE ADD 50% FOR SMALL ORDER HANDLING COSTS (UNDER £1.00 TOTAL ALSO INCLUDE FIRST CLASS S.A.E.)

UK - Postal Orders for prompt service. Cheques require 8 days from a Monday banking to ensure clearance. Export - banker's draft (sterling) prompt service. Foreign currency not accepted. VAT content becomes documentation charge. Add additional postage.

OPTO ELECTRONICS
 Photo Diodes: 32F2, 33F2, BPX40, BPX42, BPY10, BPY68, BPY69, BPY77, CQY17 CQY77.
 All types 36p
 Wire end neons 4p.
 Photo transistors: BPX43, BP103, 2N5777, Darlington, 36p. LED's (Mullard Selmans) Red 2" 8p, 125" 9p; Green 2" 11p; 125" 12p; Micro Yellow LD481 7p.
 PHOTO SILICON CONTROLLED SWITCH BPX66 PNPN 10 amp 36p.
 CA3062 Photo Detector and power amp. £1

7 SEGMENT L.E.D. DISPLAYS
 3" Red com. anode 81p
 6" Green R.S.C.A. £1.77
 5082-7650 Red com. anode.
 5082-7653 Red com. cath
 5082-7600 Yellow com. anode.
 H.P. Highbrilliance 43" 72p

HEWLETT PACKARD MULTIPLEXED 12" 7 SEGMENT LED DISPLAYS
 3 Digit HP5082 7413 45p
 4 Digit HP 5082 7414 45p
 5 Digit HP 5082 7415 45p
 Infra red transmit diodes CQY11B or LD27 High power 1.6-2v or 3-3.5v Pulse 32p
 LD242 36p
 H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p
 CNY17/1 opto coupler 70p
 Cold cathode tubes I.T.T. G517A or 5870L 60p

SPECIAL OFFER
 IN4004 or IN4006 Sealed manufacturers carton of 300. £6.85

COPPER CLAD BOARD
 Glass fibre double sided 41" x 31" 37p
 7" x 5 1/2" 65p
 Glass fibre single sided 16 1/2" x 8 1/2" 1/8" thick £1.75p. (This one is heavy-costs only 87p collected)
 Paxoline single sided 8" x 4 1/2" 54p
 7" x 5 1/2" 54p
 10 1/2" x 11" 90p

Plain Paxoline board
 290mm x 160mm x 2mm 57p

Foot switch
 4yd twin mains flex fitted 5amp 2 pin plug, with foot switch in middle 85p

Tag Strips
 1 way 2p
 2 way 4p
 3 way 4p
 9 way 5p
 11 way 10p

Weather Proof speaker
 Rugged duty 3 1/2" diam 6 watt 15ohm. Copper cone sandwiched between stainless steel protective grids - sealing gaskets. £3.50p

DIODES

AA119	7p	OA5	25p
AA133	9p	OA7	25p
AA144 100v 5ma	4p	OA10	25p
AZ15	15p	OA7	7p
B1	11p	OA70	10p
BA116	30p	OA75	11p
BA128	21p	OA79	11p
BA145	21p	OA81	31p
BA148	12p	OA90	4p
BA182 Varicap	6p	OA91	6p
BAX13	3p	OA95 (IN50)	6p
BAX14	21p	OA200	21p
BAX20	3p	IGP7	11p
BAX21 50v 120ma	3p	IGP10	11p
BAX22	3p	IN63 (OA91)	4p
BAX22 100v 120ma	4p	IN337 200v 200ma	4p
BAX54	8p	IN447 40v 25ma	3p
BAY36P	21p	IN604 400v 300ma	4p
BY472 100v 400ma	4p	IN662	21p
BB103 Varicap	8p	IN914 75v 10ma	11p
BB104 Varicap	16p	IN916 75v 20ma	21p
BB109 Varicap	24p	IN935B	71p
BB110B Varicap	24p	IN936B	71p
BB113 3x Varicap	43p	IN937B	71p
BB139	£1	IN941B	71p
BR103 Diac.	15p	IN942B	71p
BY206	71p	IN943B	71p
BY207	23p	IN3062 75v 20ma	3p
BY402	21p	IN3063 (BAV10)	6p
BY403	21p	IN3064 75v 10ma	21p
Centercell	3p	IN4009	21p
CG651	9p	IN4148 75v 10ma	1p
CR HG/3	10p	IN4149 100v 10ma	3p
CSD117YLZ	40p	IN4150	21p
CV7095	21p	IN4151	21p
CV7098	21p	IN4152 40v 20ma	3p
D3202Y Diac.	11p	IN4446 100v 20ma	21p
DC2845 Microwave	20p	DOG53	11p
DOG53	11p	IN4449 100v 5ma	21p
FSY28A	40p	IN5154 25v 30ma	3p
HG1012	10p	IN5456	15p
HS2091	11p	5082 2900 RF Schotky Barrier	20p
MPN3401	30p		

RECTIFIERS

Type	Volt	Amp	Price
BY126	650	1	5p
BY127	1250	1	4p
BY212	15kv	500ma	6p
BY235	600	1 1/2	71p
BY236	900	1 1/2	71p
BY264	300	3	9p
BY265	600	3	11p
BY266	900	3	15p
BY274	300	5	14p
BY275	600	5	17p
BY277	1200	5	27p
BY299	800	2	4p
BY1202	2kV	10mA	6p
BYW55	800	2 (Oxide bead)	15p
BYW56	1000	2 (Oxide bead)	18p
BYX20-200	200	25	72p
BYX22-200	300	1 1/2	25p
BYX38 300R	300	2 1/2	48p
BYX38 600	600	2 1/2	52p
BYX38 900	900	2 1/2	60p
BYX38 1200	1200	2 1/2	65p
BYX42 300	300	10	36p
BYX42 600	600	10	46p
BYX42 900	900	10	42p
BYX42 1200	1200	10	£1.07
BYX46 300R	300	15	£1.19
BYX46 400R	400	15	Avalanche £1.75
BYX46 500R	500	15	£2.00
BYX46 600	600	15	£2.30
BYX48 300R	300	6	47p
BYX48 600	600	6	60p
BYX48 900	900	6	70p
BYX48 1200R	1200	6	92p
BYX48 300R	300	3	35p
BYX49 600	600	3	42p
BYX49 900R	900	3	47p
BYX49 1200	1200	3	60p
BYX52 300	300	40	£2.05
BYX52 1200	1200	40	£2.90
BYX70	500	1	4p
BYX72 150R	150	10	42p
BYX72 300R	300	10	52p
BYX72 500R	500	10	65p
BYX94	1250	1	6p
E250C50	250	1	14p
KS11394	800	3	23p
LT102	30	2	15p
M1	68	1	5p
MR56	600	3	24p
MSR5	800	3	29p
OA210	400	5	33p
RAS3 10AF	1250	1 1/2	Avalanche 48p
RAS508AF	1250	1 1/2	Avalanche 50p
REC53A	1250	1 1/2	16p
SKE4G	200	6	22p
SR100	100	1 1/2	9p
SR400	400	1 1/2	10p
SR1825	100	50	75p
IN3254	400	1	4p
IN4002	100	1	3p
IN4004	400	1	41p
IN4005	600	1	6p
IN4006	800	1	6p
IN4007	1250	1	6p
IN5059	200	1 1/2	10p
IN5401	100	3	10p
IN5406	600	3	15p
IS138	800	1	21p
25G100	100	60	£4.35
3052	200	3	11p
16094P	900	3	15p
16492	700	1 1/2	91p

BRIDGE RECTIFIERS

60V	BC30 C350	23p
1,600	BYX10	34p
110	EC433	20p
50V	W005	27p
140	OSH01-200	25p
200V	W02 Ex Equip	15p
400V	W04	28p
400V	MDA104	29p
800V	W08	27p
1000	W10	36p
75V	IBIBY234	111p
150V	IBIBY235	15p
100	I.R.	40p
350V	9F2	53p
500V	9E4	85p
50	KBS005	30p
100	KBS01	30p
200	KBS02	30p
400	KBS04	30p
600	KBS06	30p
100	B40C 3200	39p
400	Texas	85p
	Minilature Meter Type	34p

THYRISTORS

Amp	Volt	Type	Price
0.8	200	2N5064	18p
1	240	BTX18-200	35p
1	240	BTX30-200	35p
1	400	BTX18-300	41p
1	700	BT 106	70p
2	400	S2710D with heatsink	40p
3	600	T3N06C00	53p
3	100	T3N1C00	36p
4	50	S107F Sensitive Gate	36p
4	50	S2060F Sensitive Gate	36p
4	400	S2061D Sensitive Gate	38p
4	500	40505 with heatsink	58p
4	600	C106M Sensitive Gate	36p
4	600	2N3228	36p
4	600	GAK	36p
5	400	S3700D	44p
5	400	S5800D/R	36p
5	600	S5800M	44p
6.5	500	BT109/SCR957	71p
7	400	S2620D	45p
7	600	S2620M	45p
8	100	S2800A	36p
8	600	S122M	54p
12	1000	CR121103-RB	£8
15	800	BTX95-800 Pulse Modulated	£1
20	600	BTW92-600RM	£3.40
75	800	71CG80	£6
110	20	72RC2A	£3
150	1000	151RA100	£10
150	1200	151RA120	£11
BT 121	70p		
BT 107	£1		

ZENER DIODES
 4/500MW. BZY98, BZX97, etc. 5p
 2v, 2v7, 3v, 3v3, 3v6, 3v9, 4v3, 4v7, 5v1, 5v6, 6v2, 6v8, 7v5, 8v2, 9v1, 10v, 11v, 12v, 13v, 13v5, 15v, 18v, 20v, 22v, 24v, 27v, 30v, 33v, 43v.
 BZY61 Laboratory Standard 400MW 7v5. Voltage Regulator Diode 12p
 1.3/1.5WT BZX61, BZY97, etc. 11p
 2v4, 2v7, 3v, 3v6, 3v9, 4v3, 4v7, 5v6, 6v2, 6v8, 8v2, 10v, 11v, 12v, 15v, 18v, 20v, 27v, 33v.
 2.5WT BZX70, etc. 13p
 v75, 1v, 2v4, 3v6, 3v9, 5v6, 6v2, 7v, 7v5, 8v, 9v, 10v, 11v, 14v, 15v, (8p), 20v, 22v, 24v, 26v.
 5WT BZV40, etc. 15p
 3v3, 3v6, 3v9, 4v3, 4v7, 5v1, 5v6, 6v2, 6v8, 7v5, 8v2, 8v7, 9v1, 10v, 11v, 12v, 15v, 33v, 68v, 120v.
 10WT Z5D, ZX, IS50, etc.
 4v3, 4v7, 5v1, 5v6, 6v2, 6v8, 7v5, 8v2, 10v, 11v, 12v, 13v, 16v, 18v, 21v, 22v, 33v, 36v, 39v, 43v, 51v, 56v, 62v, 68v, 75v, 150v.
 15WT BZV15C 12R 12volt 37p
 20WT BZY93, etc. 44p
 8v2, 12v, 39v.

TRANSFORMERS
 Douglas auto 0 - 10 - 115 - 200 - 220 - 240v 150watt £4 350watt £7.50.
 Douglas 10 - 0 - 10volt in either 7amp, 10amp, or 15amp £8.00
 Mains to 12 - 15 - 18volt 21amp £5
 110 input to 450 - 0 - 450 + 6.3v 5a + 5v 3a £3, callers only due to weight.
 Mains to 9volt 4amp £3.50p
 Mains to 15 - 0 - 15volt 3amp £4.75p
 Mains to 20volt 4amp £6
 Mains to 30v 750ma, 180v 500ma plus 3v 500ma £4.80p.
 Valve output 30ohm 5watt £1
 Mains to 20v + 20v 250ma £1.20p
 Mains to 12.6v 50ma £1.10p
 Mains to 18 - 0 - 18v + 12v 1 1/2 amp fully shrouded £4.70p
 Mains to 12volt 4amp £3.30p
 Mains to 6volt 6amp £3.20p
 Mains to 27v 5amp twin bobbin £4.80p
 Mains to 20v 0.5a twin bobbin £1.35p
 Mains to 6volt 3a twin bobbin £2.20p
 Mains to 12volt 1amp £2.50p
 Mains to 18v + 6v.3a. thermal fuse. £3.90p

BRIAN J. REED

SEE PRECEDING PAGES FOR ORDERING INSTRUCTIONS
Cut out and keep these 3 pages. Over the months they will bring to you some of the 6,000 items stocked.

INTEGRATED CIRCUITS

326	2, 2, 3, 3, Input Nand	20p	74196	Pre-set 50MHz	36p	CD4063	4 bit magnitude comparator	72p	SN15845	50p		
371A1	(MC684) Decade count.	4p	74S196/82S90			CD4066	Quad Bilateral Switch	27p	SN15846	37p		
542	Servo Amp	18p		Decade Count/Latch	65p	CD4067	1.16 MULTIPLEXER	£2.12	SN15851	50p		
702	CL	25p	74LS221	Dual Monostable M/VIB	52p	CD4070	Quad 2 input exclusive or	15p	SN15858N	55p		
709/72709	OP Amp	19p	74285	dual Mono Multi. Schm. Trig.	72p	CD4071	quad 2 input or buffer	16p	SN15862	6p		
723	2v - 37v 150ma Regulator	36p	74LS290	binary 4 x 4 mult.	47p	CD4072	dual 4 input or	15p	SN75107	Interface	£1.15	
724		20p	74293		80p	CD4076	Quad D Flip-Flop	54p	SN75108	36p		
741	OP Amp	4p	74298		£1	CD4077	Quad Exclusive Nor	19p	SN75110	46p		
747-Dual	OP Amp	16p	74490		£1.30	CD4078	8 Input Nor	15p	SN75150	7 line Rec. Interface	72p	
930DC		4p	IM5623	prom 256 x 4 60ns	36p	CD4081	Quad 2 Input and Buffer	15p	SN75235N		11p	
933DC		4p	7905	-5v Reg. 1 Amp	54p	CD4082	Dual 4 Input and	15p	SN75451	interface	36p	
936DC		4p	8080A	C.P.U.	£3.60	CD4085	Dual 2 in. 2 wide and or inv.	72p	SN75463	dual periph. or driver	36p	
946DC		4p	8284	Binary up down synch.	36p	CD4086	4 Wide 2 Input and/or Inv.	54p	SN76001		36p	
949DC		4p	82S126	256 x 4 prom	90p	CD4093	quad 2 input Nand S.T.	54p	SN76003	5Wt. Amp	36p	
961DC	Dual 4in Ext. nand	4p	82S129	Tri state prom 256 x 4	£5	CD4094	8 bit ser. par. hold bus reg.	72p	SN76013	5Wt. Amp	36p	
963DC		4p	9093DC		4p	CD4095	JK. Gated flip flop non Inv.	72p	SN76023	5Wt. Amp	92p	
1315P2		36p	9112DC		4p	CD4096	gated JK flip flop	72p	SN76110P		35p	
2102	Memory 1024 static 450ns	73p	93S10		£1	CD4097	mux/demux 8ch.	£2.90	SN76115N	Stereo Decoder	35p	
2107B	see µPD411AC	-	9311		£1.20	CD4502	Strobed Hex Invertor	44p	SN76131		58p	
214/7116	see µPD416C	-	9316		36p	CD4511	BCD 7 seg. latch decr/driver	£1.78	SN76227		59p	
2125	1024x1 Static 125ns RAM	£1.25	9370		25p	CD4514	decoder	72p	SN76228N		£1.60	
2140	4 x S.P.D.T. for D/A	£1.83	93453	Schöttky prom 1024 x 4	£1.83	CD4515	decoder	£2.12	SN76396	(TBA396)	35p	
2708	Eprom	£2.60	930399	256 Bit Shift Register	4p	CD4517	2x64 bit Shift Register	£3.60	SN76620	AN F.M.I.F. Amp.+ Demod.	18p	
2716	Eprom	£5.00	930399	480 Bit Shift Register	4p	CD4519	MC14519	54p	SN76650N	stage video I.F. + A.G.C.	50p	
3351-2DC	40 x 9 Bit FIFO 2MHz	£1.07	930399	500 Bit Shift Register	4p	CD4520	4 Bit Binary	72p	SN76660N		35p	
4060	Dynmic RAM 300ns	£1.45				CD4522	8 rate multiplier	£1.20	SN76666N	Sound I.F. + Demod. + Driver	75p	
25 LS 374	Octal D edge Trig F/F 3st	£1.30				CD4532	8in Priority encoder	£1.08				
7400	Quad 2 Input	10p	AY5-3507	3 1/2 Digit DVM	£1.65	CD4555	decoder	56p				
74H00	Positive Nand	26p	AY5-8300	Ch/Time Display	36p	CD4556	Decoder	£1.45	SN158093		50p	
74LS00	Gates	13p	AY58300	Ch/Time Display	36p	CD22100		£1.78	SN158097		4p	
74S00		18p	BRCM300	Volt Regulator	£1.40	CD40100	32 bit L/R Shift Reg.	£1.08	SN158099		4p	
7401	Quad 2 input positive	71p	BT1822		£1.25	CD40101	9 bit Par. Gen. check	£1.20	SP4021	-64 VHF/UHF 50mv TTL Q/P	75p	
74H01	Nand + O/C out	26p	C50	Calculator	37p	CD40108	4 x 4 Multiport Reg.	£3.10				
7402	Quad 2 in pos nor	11p	CA139AG	Quad Volt Comparator	54p	CD40162	4 bit synch. Dec. Count R/S	72p				
7404	Hex. Inverter	11p	CA239G	Quad volt comparator	54p	CD40163	Bin. count synch. clear	72p	TAA263	Amp	.75p	
54/7406	Hex. Inv./Buff/Drive	15p	(T)CA270AE		£1	CD40181	BE Quad 2 Input and	£2.12	TAA550	Volt Reg.	101p	
74LS08	Quad 2 in pos. and	15p	(T)CA270CW/AW		35p	CD40182	look ahead carry block	72p	TAD100	AM Radio	£2.30	
7410	Triple 3 Input	10p	(T)CA270CE		36p	CD40192	Sync 4 bit BCD U/D count	72p	TBA120S/CQ/SB/B	TV Amp	£1.22	
74H10	Positive Nand	25p	CA758	(MC1311)	36p	CD40194	4 bit L/R SR	72p	TBA240		£3.90	
74H010	Gates	18p	CA920	TV Horiz. system	72p	CD40208BF		£2.12	TBA395Q		£1.50	
7411	Triple 3 in. Pos. and	8p	CA3001	RF Amp	86p	CD40287	4 Bit Selector	£1.15p	TBA396	Luminance and chrom.	35p	
7414	Hex. Schmitt trig. Invertor	29p	CA3028A	balanced OP. AMP.	£1.20	CDP1833	Cosmac Rom 1824 x 8	£3.60	TBA550Q	Synch. Sep. + A.G.C.	£1.25	
7420	Dual 4 input	11p	CA3044		£1.43	CT1012	C Frequency Synthesiser	75p	TBA560C	Lum/Chrom. control	52p	
74S20	Positive Nand Gates	19p	CA3045	Transistor Array (5)	40p	CT1115	Frequency Synthesiser	75p	TBA800	Amp 5 Watt Audio	52p	
74S22	Dual 4 in. Pos. Nand o/c	18p	CA3046	Variable Array	72p	CT1116	Frequency synthesiser	75p	TBA920	TV Line System	70p	
7425		18p	CA3060	Transistor AMP	72p	CT1119	Frequency synthesiser	75p	TCA270Q	SA/AE/QS Vid. Det.	£1	
7428	Quad 2 In 15v Interface	16p	CA3065		36p	D3624		36p	TCA440	A.M. Receiver	18p	
7428	4 x 2in + Nor Buf/CL. Drive	16p	CA3080	Prog. Transconduct. Amp.	59p	DM8214	Interrupt (8080 support)	36p	TCA830S	Ex. Equip A.F. Amp.	18p	
7430	8 In. Pos. Nand	12p	CA3083		65p	FCH111	8 input Nand/Nor	8p	TCA830S	A.F. Amp.	£1.25	
74L30		11p	CA3086		29p	FCH201		18p	TCEP100		£1	
54/7437	Quad 2 in. Pos. Nand. Buf.	11p	CA3089		54p	FCJ101		50p	TDA0470	Organ	37p	
7438		14p	CA3093		72p	FPO/MP03725	4 Tr. Array	45p	TDA2610	6 watt audio amp	71p	
74H40	Dual 4 in. Pos. Nand. Buffer	26p	CA3094	Proa. Sw. Pwr. OP Amp.	36p	FZ1151		18p	TDA2680	T.V. Signal processor	£1.83	
7442	BCD to Decimal Decoder	26p	CA3123	AM Radio RF/IF Amp.	73p	FZ191		18p	TDA2690		71p	
74LS42	BCD to Decimal Decoder	40p	CA3132EM		£2.22	FZL201		18p	TID25A	16 diode array	4p	
7445	BCD Decimal Decoder	42p	CA3146E		90p	K17103	4 1/2 Digit DVM/DPM	18p	TL441	Log-antilog amp	36p	
	Expandable Dual 2		CA3183		80p	LM5623	MPU	36p	TLµA720	AM Radio RF/IF Amp	73p	
74H50	Wide 2 Input and/or Inv.	26p	CA3189		73p	LM3407v	Regulator	36p	TMS 3409	memory 80 bit shift Reg.	£1.10p	
7454	4 Wide 2 in. and or Inv.	11p	CA3290	Comparator	58p	LM343	Amp	4p	TMS4034	Memory	£1.08	
74LS4		11p	CA3401	(LM3900) Quad OP Amp	36p	LM1303N	Dual Stereo Pre Amp	65p	µPD411AC	200ns Dynamic 4096 x 1	ram	£1.30
54/7472	And Gated JK Master	17p	CD2500E	30mA/Seg Demi Point Dvr	90p	LM1303N	Dual OP Amp	19p	µPD416C	16384 x 1 Dynamic MOS RAM	120ns	£1.30
74L72	Slave F.F. Preset + Clear	25p	CD4000	Dual 3 Bit Binary Full Adder	12p	LM3000	Volt Regulator	36p	XR215		£2	
5473	Dual JK Master	17p	CD4002	Dual 4 Input Nor	12p	MC833P	dual 4 input expander	4p	ZN414	AM Radio Receiver	79p	
74H73	Slave Flip Flops	12p	CD4004		56p	MC837P	Hex invert. fast rise	4p	ZST131A	5 Input Power NOR	8p	
74H73	with Clear	26p	CD4005	18 Stage Static Shift Reg.	36p	MC846P		4p				
7474	Dual D. Pos. Trigger	13p	CD4007	Dual Comp. Pair + Invert	12p	MC862P		4p				
74L74	FE 2/Pres + Clear	25p	CD4008	4 Bit Binary Full Adder	30p	MC863P		4p				
7475		24p	CD4010	Hex Buffers	30p	MC1306P		4p				
54/7476	Dual JK Mas./SL Flip Flop	19p	CD4012	Dual 4 Input Nand	13p	MC1307P		4p				
5480		22p	CD4013	Dual D Flip Flop	36p	MC/CA/BRC	1310P St. Decoder	40p				
7482	2 Bit Binary Full Adder	35p	CD4014	8 Bit Shift Register	36p	MC1312P	Stroge Decoder	40p				
7483	4 Bit Binary full	45p	CD4017	Decade Count/Divide	54p	MC1314P		35p				
74LS83	Add + Fast carry	47p	CD4018	Preset Divide N Count	43p	MC1315P		35p				
547986		18p	CD4019	Quad 2 Input Multiplex	25p	MC1350P	Video I.F. Amp + A.G.C.	35p				
5490/7490	Decade Counter	25p	CD4020	14 Stage Binary Counter	54p	MC1357P	sound I.F. + Demod.	35p				
7493	Binary Counter 4 Bit	25p	CD4021	8 Bit Shift Register	54p	MC3302L	Quad amp	75p				
54/74L95	4 Bit Ser./Par. In Out	25p	CD4022	Divide by 8 Count/Divide	19p	MC4044P	Phase/Frequency detector	£1				
74LS98		£1.25	CD4023	Triple 3 Input Nand	19p	MC4344P		£3.50				
74107	Dual JK Flip Flop Clear	20p	CD4024	2/3-Stage Binary Counter	36p	MC7C		25p				
74S112		38p	CD4025	Triple 3 Input Nor	14p	MK2586		36p				
74118		75p	CD4027	Dual JK Flip Flop + RS	30p	NK4012	Memory Static Shift Reg	38p				
74121	Monostable Multivibrator	12p	CD4028	MC14028 BCD/Decimal	42p	MM5335	Prom 256 x 8 80ns	36p				
74122		18p	CD4029	Synch. Preset Bin/Decode	54p	MM8008	M.P.U.	36p				
54/74123	Dual Retrigr. Multivibrator	35p	CD4030	Quad Exclusive or	36p	MP3202	3 1/2 Digit DVM	£1.45				
54S124	dual volt cont. osc.	£1.10	CD4031	64 stage static. shift reg.	£1.20	MT300	Volt Regulator	8p				
74132		44p	CD4032		72p	MT305	Volt Regulator	8p				
74141	BCD To Decimal Dec/Drive	42p	CD4033	Dec. Count. 7 Seg. Output	72p	MW4050D	Static Ram 200ns	£1.60				
74LS145		93p	CD4034	Static shift register	£1.48p	MWS5101	256x4 SOS CMOS RAM	£3.60				
74151	1 of 8 Data Sel./Multiplex	32p	CD4035	4 Bit Par. in/out Shift	54p	SAA661		36p				
74153	Dual 4 to 1 multiplexer	36p	CD4036	Word Buff. Store/decode	£2.90	SAA1010		34p				
74154	16 Way Distribution	35p	CD4037	triple and/or B1 Phase pairs	72p	SAA1025		£4				
74155		12p	CD4038	Triple serial adder	54p	SAA 5012	Teletext Binary Tuner	£2.75p				
74157	Quad 2 line to 1 Data	12p	CD4039	Quad clocked D type catch	54p	SAAS580	4 Ch. touch tune. + Disp.	18p				
74165		58p	CD4040	Quad clocked D type catch	54p	SAAS590	4 Ch. touch tune. + Disp.	18p				
74167	Synch. Dec. Rate Multivibrator	23p	CD4043	Quad Nor R/S Latch	54p	SGS300	Op. Amp	4p				
74173		44p	CD4044	Quad Nand R/S Latch	54p	SL403A	3 Wt. Amp.	38p				
74174	Hex D/F/F and clear	55p	CD4045	4 Bit Par. in/out shift	54p	SL442	Copper power supply	36p				
74S174	Hex D Flip Flop + clear	72p	CD4046	Micro Power PH. Lock Loop	36p	SN7528		11p				
74176/8280	Pre-set 35MHz Decode	30p	CD4047	monostable	36p	SN15836		25p				
74180		12p	CD4048	Exp 8 input gate	36p							
74181	Arith. Logic unit/funt. Gen.	56p	CD4049	Hex								

Self-Binder

for "Radio & Electronics Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.



PRICE £2.25 P. & P. 50p
including V.A.T.

For your other magazines


Plain-backed in Maroon or Green
(Please state colour choice)

PRICE £2.25 P. & P. 50p
including VAT

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

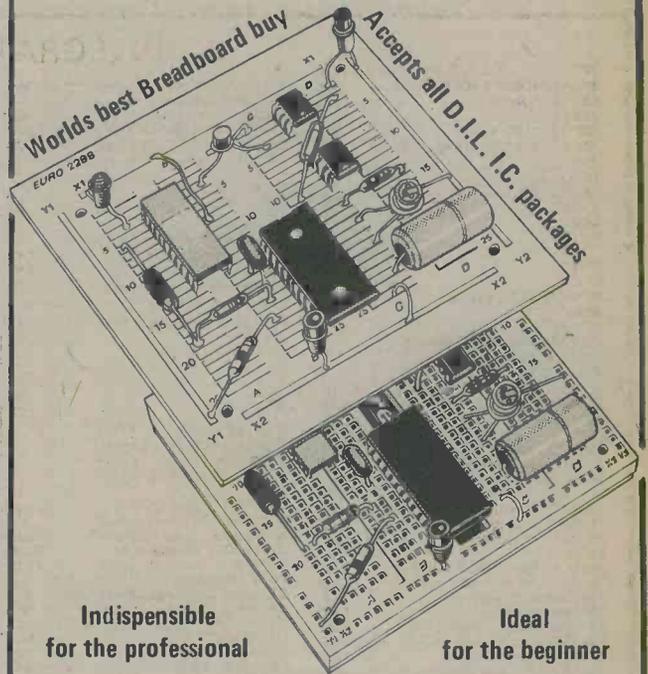First the EuroBreadBoard Now the EuroSolderBoard



Design on a EuroBreadBoard — Instal on a EuroSolderBoard

First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects) Long life, low resistance (<10m ohms) nickel silver contacts £6.20 each or £11.70 for 2

Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's

And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales,
Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales,
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.
Please send me:—

- | | | | |
|-----------------------|----------|-----------------------|--------|
| 1 EuroBreadBoard | @ £ 6.20 | <input type="radio"/> | |
| or 2 EuroBreadBoards | @ £11.70 | <input type="radio"/> | Please |
| or 3 EuroSolderBoards | @ £ 2.00 | <input type="radio"/> | Tick |
| or 1 EuroSolderSucker | @ £ 7.25 | <input type="radio"/> | |

All prices are applicable from Jan. 1st 1981 and include VAT & PP but add 15% for overseas orders.

Name

Company

Address

REC/2

Tel. No.

Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

AND THERE'S MORE WHERE THIS CAME FROM

It's a long time since one of our adverts was presented in 'list' form - but simply because we do not try to squeeze this lot in every time doesn't mean that it's not available. Our new style price list (now some 40 pages long) includes all this and more, including quantity prices and a brief description. The kits, modules and specialized RF components - such as TOKO coils, filters etc. are covered in the general price list - so send now for a free copy (with an SAE please). Part 4 of the catalogue is due out now (incorporating a revised version of pt.1).

LINEAR ICs - NUMERIC LISTINGS		TTL N and LSN		VARICAP		TRANSISTORS		CAPACITORS	
TLA120S	1.00	KB4413	1.95	7443N	1.15	74LS112	0.38	74LS169	2.00
L200	1.95	KB4417	1.80	7444N	1.12	74170N	2.30	74170N	2.30
U237B	1.28	TPA4220	2.25	7445N	0.94	74LS114	0.38	74LS170	2.00
U247B	1.28	KB4420B	1.09	7446N	0.94	74118N	0.83	74LS174	1.20
U257B	1.28	KB4423	2.30	7447N	0.89	74120N	1.15	74175N	0.87
U267B	1.28	KB4424	1.65	7448N	0.89	74121N	0.42	74LS175	1.10
LM301H	0.67	KB4431	1.95	7449N	0.99	74122N	0.46	74176N	0.75
LM301N	0.30	KB4432	1.95	7450N	0.99	74123N	0.73	74177N	0.78
LM308H	0.96	KB4433	1.52	7451N	0.17	74LS124	1.75	74181N	1.65
LM308N	0.65	KB4436	2.53	7452N	0.24	74LS125	0.38	74LS181	3.50
LM339N	0.66	KB4437	1.75	7453N	0.17	74LS126	0.44	74LS183	2.10
LM348N	1.86	KB4438	2.22	7454N	0.17	74LS128	0.74	74184N	1.35
LF351N	0.38	KB4441	1.35	7455N	0.26	74132N	0.73	74185N	1.34
LF352N	0.76	KB4445	1.29	7456N	0.17	74LS132	0.78	74192N	1.02
LM374N	3.75	KB4446	2.75	7457N	0.38	74LS136	0.40	74193N	1.05
LM380N-14	1.00	KB4448	1.65	7458N	0.28	74LS138	0.60	74LS193	1.80
LM380N-8	1.00	NE5044N	2.26	7459N	0.17	74141N	0.56	74194N	1.05
LM381N	1.81	NE5532N	1.85	7460N	0.38	74142N	2.65	74196N	0.99
LM391CE	1.95	SD6000	3.75	7461N	0.17	74143N	3.12	74196N	1.10
NE544N	1.80	SL6270	2.03	7462N	0.24	74144N	3.12	74198N	1.50
NE555N	0.30	SL6310	2.03	7463N	0.20	74145N	1.75	74199N	1.60
NE556N	0.50	SL6600	3.75	7464N	0.37	74147N	1.05	74LS247	0.93
NE560N	3.50	SL6640	2.75	7465N	0.24	74148N	1.75	74LS257	1.60
NE562N	4.05	SL6690	3.20	7466N	0.17	74149N	1.99	74LS260	1.53
NE564N	4.29	SL6700	2.35	7467N	0.38	74150N	0.99	74LS262	1.50
NE565N	1.60	ICL8038CC	4.50	7468N	0.48	74151N	0.55	74LS279	0.52
NE566N	1.60	MSL9362	1.75	7469N	0.28	74152N	0.80	74LS283	1.20
NE570N	3.85	MSL9363	1.75	7470N	0.37	74153N	0.64	74LS293	0.95
SL624	3.28	HALL1211	1.95	7471N	0.30	74154N	0.56	74LS365	0.49
THA651	1.81	HALL1223	2.15	7472N	0.16	74155N	0.54	74LS366	0.49
UA709HC	0.64	HALL1225	1.45	7473N	0.29	74156N	0.96	74LS367	0.43
UA709PC	0.36	HALL2002	1.45	7474N	0.33	74LS155	1.10	74LS368	0.49
UA710HC	0.65	HALL2017	0.80	7475N	0.27	74156N	0.80	74LS374	1.80
UA710PC	0.59	HALL2402	1.95	7476N	0.27	74157N	0.67	74LS377	1.95
UA741HC	0.66	HALL2411	1.20	7477N	0.27	74158N	0.56	74LS379	1.30
UA741CN	0.27	HALL2412	1.55	7478N	0.44	74159N	2.10	74LS393	1.40
UA747CN	0.70	LP13741	0.33	7479N	0.32	74160N	0.82		
UA748CN	0.36	SN76660N	0.80	7480N	0.37	74161N	0.92		
UA753	2.44			7481N	0.86	74162N	0.92		
UA758	2.35			7482N	0.69	74163N	0.92		
TBA810AS	1.09			7483N	0.99	74164N	1.04		
TBA820M	0.75			7484N	0.65	74165N	1.14		
TC9A04E	1.80			7485N	0.58	74166N	1.30		
TD1028	2.11			7486N	1.28	74167N	2.50		
TD1029	2.11			7487N	1.85				
TD1054	1.45			7488N	0.63				
TD1062	1.95			7489N	0.74				
TD1072	2.69			7490N	0.24				
TD1074A	5.04			7491N	0.76				
TD1083	1.95			7492N	0.38				
TD1090	3.05			7493N	0.32				
HALL137	1.20			7494N	0.80				
HALL196	2.00			7495N	0.65				
HALL197	1.40			7496N	1.14				
TD1120	1.00			7497N	0.58				
LM1303	0.99			7498N	0.24				
LM1307	1.55			7499N	0.74				
MC1310P	1.90			7500N	0.20				
MC1330	1.20								
MC1350	1.20								
HALL1370	1.90								
HALL388	2.75								
TD1490	1.86								
MCL496P	1.25								
MCL610P	1.60								
SLI611P	1.60								
SLI612P	1.60								
SLI613P	1.89								
SLI620P	2.17								
SLI621P	2.17								
SLI623P	2.24								
SL624C	3.28								
SLI625P	2.17								
SLI626P	2.44								
SLI640P	1.62								
SLI641P	1.89								
TR2002	1.25								
TR2020	3.00								
UDN2242A	1.00								
ULN2283B	1.00								
CA3380E	0.70								
CA3089E	1.84								
CA3090AQ	3.35								
CA3123E	1.80								
CA3130E	0.40								
CA3130T	0.90								
CA3140E	0.46								
CA3189E	2.20								
MC3357P	2.35								
LM3900N	0.60								
LM3909N	0.68								
LM3914N	2.80								
LM3915N	2.80								
KB4400	0.80								
KB4406	0.60								
KB4412	1.95								

Prices exclude VAT - PLEASE ADD 15%*
Postage 35p per order. CWO please. (*UK only)

Please send an SAE with all enquiries.
Access/Barclaycard (min £5 please)
Callers welcome

ambit

INTERNATIONAL

200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 95194 AMBIT G POSTCODE CM14 4SG

CWO PLEASE: Commercial MA terms on application. Goods are offered subject to availability, prices subject to change - so please phone and check if in doubt.

CATALOGUES
2 & 3...80p ea
4...76p
(4 inc. rev. of part 1)
ALL PARTS:
.....£1.75.....

BATTERIES NICAD rechargeable 1. (AA) £1.50 2. (C) £2.50 3. (D) £4.50		CAPACITORS Ceramic - Auto Insertion Types tol 10% 400V IN PFC 5mm		RESISTORS E12 IN OHMS 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82. 227A Carbon Film 1/8W5% 9 x 3mm 250V 10R-1 MEG E12 1p 227B Metal Film 1/2W5% 10 x 3mm 350V 10R-1 K E12 2p. By Electrofil/Welwyn When ordering resistors state qty, item no and resistance value. Minimum quantity per value, 10.																																																																																																																																																													
CABLE PVC round Grey 4. Audio screened overall 2 core 7.20mm 20p MTR. 5. Mains 3 core 3 amp 12p MTR. 8. TV Download 60p MTR. 7. 15/2mm x 15' 1 each in Black, Red, Yellow 5p tol.		CAPACITORS ELECTROLYTIC TOL - 10% + 60% IN MFDS SIZES IN MM AXIAL TUBULAR PLUG IN LEADS 7 x 5mm		BRIDGES By GI, ME 42. W005 18p 43. W02 20p 44. W04 24p																																																																																																																																																													
CAPACITORS POLYESTER PLUG IN RECT BOX STYLE TOL 10% IN MFDS BY EVOX MULL PLESSEY ROEDSTEIN SIEMENS		CONNECTORS 390 DIN plug 5 pin 180deg. 15p 391 DIN chassis SKT 15p 392 Jack plug stereo 15p 393 Jack chassis SKT Stereo J 38p 394 mains plug rubber white 3 pin 15p 395 3 pin 15p		SCRs 228 BT106 1 700 400 229 C106D 2.4 35p 231 2N5051 25 600 60 70p 230 2N4444 25 600 60 35p 231 2N5051 25 100 18p																																																																																																																																																													
CAPACITORS TANT BEAD TOL 20% IN MFDS PCM 5mm 64. 2/27v 9p. 65. 4/725v 9p. 66. 22/25v 12p. 67. 47/63v 18p.		TANT SOLID LARGE SELECTION AVAILABLE		TRANSISTORS all at 6p each <table border="1"> <tr><th>Case</th><th>VC EO</th><th>L</th><th>IC Max mA</th><th>P Tot mW</th><th>FT Min MHz</th></tr> <tr><td>234 BC134</td><td>TO106</td><td>45</td><td>N</td><td>200</td><td>200</td></tr> <tr><td>235 BC147</td><td>TO18</td><td>45</td><td>N</td><td>200</td><td>350</td></tr> <tr><td>236 BC148</td><td>SO725</td><td>30</td><td>N</td><td>200</td><td>350</td></tr> <tr><td>237 BC149</td><td>SO725</td><td>30</td><td>N</td><td>200</td><td>350</td></tr> <tr><td>238 BC157A</td><td>SO725</td><td>45</td><td>P</td><td>200</td><td>350</td></tr> <tr><td>239 BC158A</td><td>SO725</td><td>30</td><td>P</td><td>200</td><td>350</td></tr> <tr><td>240 BC159A</td><td>SO725</td><td>30</td><td>P</td><td>200</td><td>350</td></tr> <tr><td>241 BC171B</td><td>TO92</td><td>45</td><td>N</td><td>200</td><td>300</td></tr> <tr><td>242 BC172B</td><td>TO92</td><td>25</td><td>N</td><td>200</td><td>300</td></tr> <tr><td>243 BC182A</td><td>TO92</td><td>50</td><td>N</td><td>200</td><td>350</td></tr> <tr><td>244 BC183A</td><td>TO92</td><td>30</td><td>N</td><td>200</td><td>300</td></tr> <tr><td>245 BC184</td><td>TO92</td><td>30</td><td>N</td><td>200</td><td>300</td></tr> <tr><td>246 BC192B</td><td>TO92</td><td>30</td><td>P</td><td>200</td><td>300</td></tr> <tr><td>247 BC193B</td><td>TO92</td><td>30</td><td>P</td><td>200</td><td>300</td></tr> <tr><td>248 BC214B</td><td>TO92</td><td>30</td><td>P</td><td>200</td><td>300</td></tr> <tr><td>249 BC237A</td><td>TO92</td><td>45</td><td>N</td><td>100</td><td>625</td></tr> <tr><td>250 BC337</td><td>TO92</td><td>45</td><td>N</td><td>800</td><td>625</td></tr> <tr><td>251 BC447</td><td>TO92</td><td>60</td><td>N</td><td>200</td><td>625</td></tr> <tr><td>252 BF937</td><td>TO92</td><td>300</td><td>N</td><td>500</td><td>625</td></tr> <tr><td>253 TI990</td><td>TO92</td><td>40</td><td>N</td><td>800</td><td>625</td></tr> <tr><td>254 TI991</td><td>TO92</td><td>40</td><td>N</td><td>800</td><td>625</td></tr> <tr><td>255 2N3702</td><td>TO92</td><td>25</td><td>P</td><td>200</td><td>360</td></tr> <tr><td>256 2N3704</td><td>TO92</td><td>30</td><td>N</td><td>800</td><td>360</td></tr> <tr><td>257 2N3706</td><td>TO92</td><td>30</td><td>N</td><td>800</td><td>360</td></tr> <tr><td>258 2N3711</td><td>TO92</td><td>30</td><td>N</td><td>300</td><td>360</td></tr> </table>		Case	VC EO	L	IC Max mA	P Tot mW	FT Min MHz	234 BC134	TO106	45	N	200	200	235 BC147	TO18	45	N	200	350	236 BC148	SO725	30	N	200	350	237 BC149	SO725	30	N	200	350	238 BC157A	SO725	45	P	200	350	239 BC158A	SO725	30	P	200	350	240 BC159A	SO725	30	P	200	350	241 BC171B	TO92	45	N	200	300	242 BC172B	TO92	25	N	200	300	243 BC182A	TO92	50	N	200	350	244 BC183A	TO92	30	N	200	300	245 BC184	TO92	30	N	200	300	246 BC192B	TO92	30	P	200	300	247 BC193B	TO92	30	P	200	300	248 BC214B	TO92	30	P	200	300	249 BC237A	TO92	45	N	100	625	250 BC337	TO92	45	N	800	625	251 BC447	TO92	60	N	200	625	252 BF937	TO92	300	N	500	625	253 TI990	TO92	40	N	800	625	254 TI991	TO92	40	N	800	625	255 2N3702	TO92	25	P	200	360	256 2N3704	TO92	30	N	800	360	257 2N3706	TO92	30	N	800	360	258 2N3711	TO92	30	N	300	360
Case	VC EO	L	IC Max mA	P Tot mW	FT Min MHz																																																																																																																																																												
234 BC134	TO106	45	N	200	200																																																																																																																																																												
235 BC147	TO18	45	N	200	350																																																																																																																																																												
236 BC148	SO725	30	N	200	350																																																																																																																																																												
237 BC149	SO725	30	N	200	350																																																																																																																																																												
238 BC157A	SO725	45	P	200	350																																																																																																																																																												
239 BC158A	SO725	30	P	200	350																																																																																																																																																												
240 BC159A	SO725	30	P	200	350																																																																																																																																																												
241 BC171B	TO92	45	N	200	300																																																																																																																																																												
242 BC172B	TO92	25	N	200	300																																																																																																																																																												
243 BC182A	TO92	50	N	200	350																																																																																																																																																												
244 BC183A	TO92	30	N	200	300																																																																																																																																																												
245 BC184	TO92	30	N	200	300																																																																																																																																																												
246 BC192B	TO92	30	P	200	300																																																																																																																																																												
247 BC193B	TO92	30	P	200	300																																																																																																																																																												
248 BC214B	TO92	30	P	200	300																																																																																																																																																												
249 BC237A	TO92	45	N	100	625																																																																																																																																																												
250 BC337	TO92	45	N	800	625																																																																																																																																																												
251 BC447	TO92	60	N	200	625																																																																																																																																																												
252 BF937	TO92	300	N	500	625																																																																																																																																																												
253 TI990	TO92	40	N	800	625																																																																																																																																																												
254 TI991	TO92	40	N	800	625																																																																																																																																																												
255 2N3702	TO92	25	P	200	360																																																																																																																																																												
256 2N3704	TO92	30	N	800	360																																																																																																																																																												
257 2N3706	TO92	30	N	800	360																																																																																																																																																												
258 2N3711	TO92	30	N	300	360																																																																																																																																																												
DIODES BY ITT, MULL, SECOSEMI, TEXAS, etc. All coded. 68. AA119 35mA 45v 8p 76. BY255 3A 1300v 10p 84. IN4004 1A 400v 3p 69. BA182 100mA 35v 5p 77. OA47 48mA 30v 5p 85. IN4148 75mA 75v 1p 70. BA13 75mA 50v 1p 78. OA90 10mA 30v 5p 86. IN4151 150mA 75v 2p 71. BA16 200mA 150v 4p 79. OA91 50mA 115v 7p 87. IN404 3A 400v 10p 72. BA138 115mA 50v 4p 80. OA200 80mA 50v 6p 88. IN5407 3A 800v 12p 73. BY126 1A 650v 7p 81. IN814 75mA 100v 2p 89. IS932 200mA 200v 2p 74. BY127 2A 250v 11p 82. IN818 75mA 100v 2p 75. BY206 400mA 350v 20p 83. IN4002 1A 100v 2p		LEDs 2mm TIL 209C 90 GR 13p. 91. RED 9p. 92. YEL 15p.		all at 9p each <table border="1"> <tr><th>Case</th><th>VC EO</th><th>L</th><th>IC Max mA</th><th>P Tot mW</th><th>FT Min MHz</th></tr> <tr><td>259 BC107</td><td>TO18</td><td>45</td><td>N</td><td>100</td><td>300</td></tr> <tr><td>260 BC107B</td><td>TO18</td><td>45</td><td>N</td><td>100</td><td>300</td></tr> <tr><td>261 BC108</td><td>TO18</td><td>30</td><td>N</td><td>100</td><td>300</td></tr> <tr><td>262 BC108B</td><td>TO18</td><td>20</td><td>N</td><td>100</td><td>300</td></tr> <tr><td>263 BC109</td><td>TO18</td><td>30</td><td>N</td><td>100</td><td>300</td></tr> <tr><td>264 BC109C</td><td>TO18</td><td>20</td><td>N</td><td>100</td><td>300</td></tr> <tr><td>265 BC177</td><td>TO18</td><td>45</td><td>P</td><td>150</td><td>300</td></tr> <tr><td>266 BC178</td><td>TO18</td><td>45</td><td>P</td><td>150</td><td>300</td></tr> <tr><td>267 BC215A</td><td>TO18</td><td>45</td><td>P</td><td>150</td><td>300</td></tr> <tr><td>268 BC477</td><td>TO18</td><td>80</td><td>P</td><td>150</td><td>360</td></tr> <tr><td>269 BC478</td><td>TO18</td><td>50</td><td>P</td><td>150</td><td>360</td></tr> <tr><td>270 BC479</td><td>TO18</td><td>40</td><td>P</td><td>150</td><td>360</td></tr> <tr><td>271 708</td><td>TO18</td><td>40</td><td>P</td><td>200</td><td>350</td></tr> <tr><td>272 715</td><td>TO18</td><td>45</td><td>P</td><td>200</td><td>350</td></tr> <tr><td>273 727</td><td>TO18</td><td>25</td><td>P</td><td>200</td><td>350</td></tr> <tr><td>274 2N106</td><td>TO18</td><td>45</td><td>N</td><td>200</td><td>300</td></tr> <tr><td>275 2N3903</td><td>TO92</td><td>40</td><td>P</td><td>300</td><td>250</td></tr> <tr><td>276 2N3904</td><td>TO92</td><td>40</td><td>P</td><td>300</td><td>250</td></tr> <tr><td>277 2N3905</td><td>TO92</td><td>40</td><td>P</td><td>300</td><td>250</td></tr> <tr><td>278 2N3906</td><td>TO92</td><td>40</td><td>P</td><td>300</td><td>250</td></tr> </table>		Case	VC EO	L	IC Max mA	P Tot mW	FT Min MHz	259 BC107	TO18	45	N	100	300	260 BC107B	TO18	45	N	100	300	261 BC108	TO18	30	N	100	300	262 BC108B	TO18	20	N	100	300	263 BC109	TO18	30	N	100	300	264 BC109C	TO18	20	N	100	300	265 BC177	TO18	45	P	150	300	266 BC178	TO18	45	P	150	300	267 BC215A	TO18	45	P	150	300	268 BC477	TO18	80	P	150	360	269 BC478	TO18	50	P	150	360	270 BC479	TO18	40	P	150	360	271 708	TO18	40	P	200	350	272 715	TO18	45	P	200	350	273 727	TO18	25	P	200	350	274 2N106	TO18	45	N	200	300	275 2N3903	TO92	40	P	300	250	276 2N3904	TO92	40	P	300	250	277 2N3905	TO92	40	P	300	250	278 2N3906	TO92	40	P	300	250																														
Case	VC EO	L	IC Max mA	P Tot mW	FT Min MHz																																																																																																																																																												
259 BC107	TO18	45	N	100	300																																																																																																																																																												
260 BC107B	TO18	45	N	100	300																																																																																																																																																												
261 BC108	TO18	30	N	100	300																																																																																																																																																												
262 BC108B	TO18	20	N	100	300																																																																																																																																																												
263 BC109	TO18	30	N	100	300																																																																																																																																																												
264 BC109C	TO18	20	N	100	300																																																																																																																																																												
265 BC177	TO18	45	P	150	300																																																																																																																																																												
266 BC178	TO18	45	P	150	300																																																																																																																																																												
267 BC215A	TO18	45	P	150	300																																																																																																																																																												
268 BC477	TO18	80	P	150	360																																																																																																																																																												
269 BC478	TO18	50	P	150	360																																																																																																																																																												
270 BC479	TO18	40	P	150	360																																																																																																																																																												
271 708	TO18	40	P	200	350																																																																																																																																																												
272 715	TO18	45	P	200	350																																																																																																																																																												
273 727	TO18	25	P	200	350																																																																																																																																																												
274 2N106	TO18	45	N	200	300																																																																																																																																																												
275 2N3903	TO92	40	P	300	250																																																																																																																																																												
276 2N3904	TO92	40	P	300	250																																																																																																																																																												
277 2N3905	TO92	40	P	300	250																																																																																																																																																												
278 2N3906	TO92	40	P	300	250																																																																																																																																																												
DIODES ZENER BY MOTOROLA, MULLARD, SECOSEMI BZX79/BZ88C 400mW 5% <table border="1"> <tr><th>ITEM</th><th>3V3</th><th>4V7</th><th>5V1</th><th>6V6</th><th>6V8</th><th>8V1</th><th>10</th><th>15</th><th>18</th><th>5p</th></tr> <tr><td></td><td>53</td><td>54</td><td>55</td><td>56</td><td>57</td><td>58</td><td>59</td><td>100</td><td>101</td><td></td></tr> </table> <table border="1"> <tr><th>ITEM</th><th>102</th><th>103</th><th>104</th><th>105</th><th>106</th><th>107</th><th>108</th><th>109</th><th>110</th><th>8p</th></tr> <tr><td></td><td>6V8</td><td>9V1</td><td>10</td><td>12</td><td>16</td><td>18</td><td>20</td><td>22</td><td>24</td><td></td></tr> </table> BZX61/B8C 1W3 5%		ITEM	3V3	4V7	5V1	6V6	6V8	8V1	10	15	18	5p		53	54	55	56	57	58	59	100	101		ITEM	102	103	104	105	106	107	108	109	110	8p		6V8	9V1	10	12	16	18	20	22	24		FUSES DC 20mm x 5mm 395 100mA 4p. 396 500mA 4p. 397. 1A 4p. 398 2A 4p. MAINS 1" x 1" 399 3A 5p. 400 5A 5p. 401 13A 5p.		ICs DIL PINNING (-) <table border="1"> <tr><th>ITEM</th><th>111 301 (B)</th><th>112 380 (14)</th><th>113 555 (B)</th><th>144 709 (B)</th><th>115 723 (14)</th><th>116 741 (B)</th><th>117 CA130 (B)</th></tr> <tr><td></td><td>20p</td><td>45p</td><td>18p</td><td>18p</td><td>24p</td><td>18p</td><td>90p</td></tr> </table>		ITEM	111 301 (B)	112 380 (14)	113 555 (B)	144 709 (B)	115 723 (14)	116 741 (B)	117 CA130 (B)		20p	45p	18p	18p	24p	18p	90p																																																																																																
ITEM	3V3	4V7	5V1	6V6	6V8	8V1	10	15	18	5p																																																																																																																																																							
	53	54	55	56	57	58	59	100	101																																																																																																																																																								
ITEM	102	103	104	105	106	107	108	109	110	8p																																																																																																																																																							
	6V8	9V1	10	12	16	18	20	22	24																																																																																																																																																								
ITEM	111 301 (B)	112 380 (14)	113 555 (B)	144 709 (B)	115 723 (14)	116 741 (B)	117 CA130 (B)																																																																																																																																																										
	20p	45p	18p	18p	24p	18p	90p																																																																																																																																																										
ICs CMOS DIL 40 - N BUFF. <table border="1"> <tr><th>ITEM</th><th>121</th><th>122</th><th>123</th><th>124</th><th>125</th><th>126</th><th>127</th><th>128</th><th>129</th><th>130</th><th>131</th><th>132</th><th>133</th><th>134</th><th>135</th><th>136</th><th>137</th><th>138</th><th>139</th></tr> <tr><td></td><td>16p</td><td>48p</td><td>140</td><td>48p</td><td>54p</td><td>160</td><td>20p</td><td>140</td><td>24p</td><td>140</td><td>24p</td><td>140</td><td>24p</td><td>48p</td><td>208</td><td>01</td><td>210</td><td>02</td><td>211</td><td>03</td><td>212</td><td>04</td><td>213</td><td>05</td><td>214</td><td>10</td><td>215</td><td>15</td><td>216</td><td>27</td><td>217</td><td>51</td><td>218</td><td>73</td><td>219</td><td>00</td><td>220</td><td>02</td><td>221</td><td>04</td><td>222</td><td>08</td><td>223</td><td>10</td></tr> </table>		ITEM	121	122	123	124	125	126	127	128	129	130	131	132	133	134	135	136	137	138	139		16p	48p	140	48p	54p	160	20p	140	24p	140	24p	140	24p	48p	208	01	210	02	211	03	212	04	213	05	214	10	215	15	216	27	217	51	218	73	219	00	220	02	221	04	222	08	223	10	ICs TTL DIL 74 - N <table border="1"> <tr><th>ITEM</th><th>208</th><th>01</th><th>210</th></tr></table>		ITEM	208	01	210	02	211 <th>03</th> <th>212<th>04</th><th>213<th>05</th><th>214<th>10</th><th>215<th>15</th><th>216<th>27</th><th>217<th>51</th><th>218<th>73</th><th>219<th>00</th><th>220<th>02</th><th>221<th>04</th><th>222<th>08</th><th>223<th>10</th></th></th></th></th></th></th></th></th></th></th></th></th>	03	212 <th>04</th> <th>213<th>05</th><th>214<th>10</th><th>215<th>15</th><th>216<th>27</th><th>217<th>51</th><th>218<th>73</th><th>219<th>00</th><th>220<th>02</th><th>221<th>04</th><th>222<th>08</th><th>223<th>10</th></th></th></th></th></th></th></th></th></th></th></th>	04	213 <th>05</th> <th>214<th>10</th><th>215<th>15</th><th>216<th>27</th><th>217<th>51</th><th>218<th>73</th><th>219<th>00</th><th>220<th>02</th><th>221<th>04</th><th>222<th>08</th><th>223<th>10</th></th></th></th></th></th></th></th></th></th></th>	05	214 <th>10</th> <th>215<th>15</th><th>216<th>27</th><th>217<th>51</th><th>218<th>73</th><th>219<th>00</th><th>220<th>02</th><th>221<th>04</th><th>222<th>08</th><th>223<th>10</th></th></th></th></th></th></th></th></th></th>	10	215 <th>15</th> <th>216<th>27</th><th>217<th>51</th><th>218<th>73</th><th>219<th>00</th><th>220<th>02</th><th>221<th>04</th><th>222<th>08</th><th>223<th>10</th></th></th></th></th></th></th></th></th>	15	216 <th>27</th> <th>217<th>51</th><th>218<th>73</th><th>219<th>00</th><th>220<th>02</th><th>221<th>04</th><th>222<th>08</th><th>223<th>10</th></th></th></th></th></th></th></th>	27	217 <th>51</th> <th>218<th>73</th><th>219<th>00</th><th>220<th>02</th><th>221<th>04</th><th>222<th>08</th><th>223<th>10</th></th></th></th></th></th></th>	51	218 <th>73</th> <th>219<th>00</th><th>220<th>02</th><th>221<th>04</th><th>222<th>08</th><th>223<th>10</th></th></th></th></th></th>	73	219 <th>00</th> <th>220<th>02</th><th>221<th>04</th><th>222<th>08</th><th>223<th>10</th></th></th></th></th>	00	220 <th>02</th> <th>221<th>04</th><th>222<th>08</th><th>223<th>10</th></th></th></th>	02	221 <th>04</th> <th>222<th>08</th><th>223<th>10</th></th></th>	04	222 <th>08</th> <th>223<th>10</th></th>	08	223 <th>10</th>	10																																																														
ITEM	121	122	123	124	125	126	127	128	129	130	131	132	133	134	135	136	137	138	139																																																																																																																																														
	16p	48p	140	48p	54p	160	20p	140	24p	140	24p	140	24p	48p	208	01	210	02	211	03	212	04	213	05	214	10	215	15	216	27	217	51	218	73	219	00	220	02	221	04	222	08	223	10																																																																																																																					
ITEM	208	01	210																																																																																																																																																														

 ICs 74LS - N | ITEM | 208 | 01 | 210 | |------|-----|----|-----| |------|-----|----|-----| | | 02 | 211 03 | 212 04 | 213 05 | 214 10 | 215 15 | 216 27 | 217 51 | 218 73 | 219 00 | 220 02 | 221 04 | 222 08 | 223 10 || **ICs** CMOS DIL 40 - N BUFF. | ITEM | 118 556 (14) | 119 747 (14) | 120 324 (14) | 182 | 37 | 206 | 183 | |------|--------------|--------------|--------------|-----|-----|-----|-----| | | 60p | 30p | 60p | 183 | 30p | 206 | 183 | | | **ICs** TTL DIL 74 - N | ITEM | 208 | 01 | 210 | |------|-----|----|-----| |------|-----|----|-----| | | 02 | 211 03 | 212 04 | 213 05 | 214 10 | 215 15 | 216 27 | 217 51 | 218 73 | 219 00 | 220 02 | 221 04 | 222 08 | 223 10 | | | | | | | | | | | | | | **ICs** 74LS - N | ITEM | 208 | 01 | 210 | |------|-----|----|-----| |------|-----|----|-----| | | 02 | 211 03 | 212 04 | 213 05 | 214 10 | 215 15 | 216 27 | 217 51 | 218 73 | 219 00 | 220 02 | 221 04 | 222 08 | 223 10 || **POTS** Cermet 20 turn I' rest, plug in item 402 50R 70p. 403 100R 60p. 404 500R 60p. 405 1K 55p. 406 3K 55p. 407 10K 55p. | | **IC HOLDERS** LOW PROF 224 1491N 9p 225 1691N 9p 226 2491N 27p | | **FETS** 381 2N5457 18p 382 2N5458 16p | | **PuTs** 383 BRY39 18p 384 2N6076 16p | | **TRIODES** 385 MCR106-8 12p 386 2N4991 3p | | **UJTs** 387 2N2646 24p 388 2N2647 72p | | **PROM** 389 2716 54p 400 450m 72p | | | | | | | | | | | | | | | | | | | | | | | | | | | |

ORDER FORM CUT ALONG DOTTED LINE AND FOLD. PRICES FIRM UNTIL 31.3.81.

QTY _____ ITEM No. _____

NAME _____

A
D
D
R
E
S
S

Immediate despatch except Item 389 2 weeks.

Pay CASH WITH ORDER. £ _____

Carriage is free.


VAT 15% extra UK Only £ _____ TOTAL £ _____

CRIMSON COMPONENTS LTD.
 76 CASTLE VIEW
 ILFORD
 ESSEX

ENQUIRIES FOR PCB'S WELCOME

01-554 1834
 01-445 6645

MINIMUM ORDER CHARGE £4

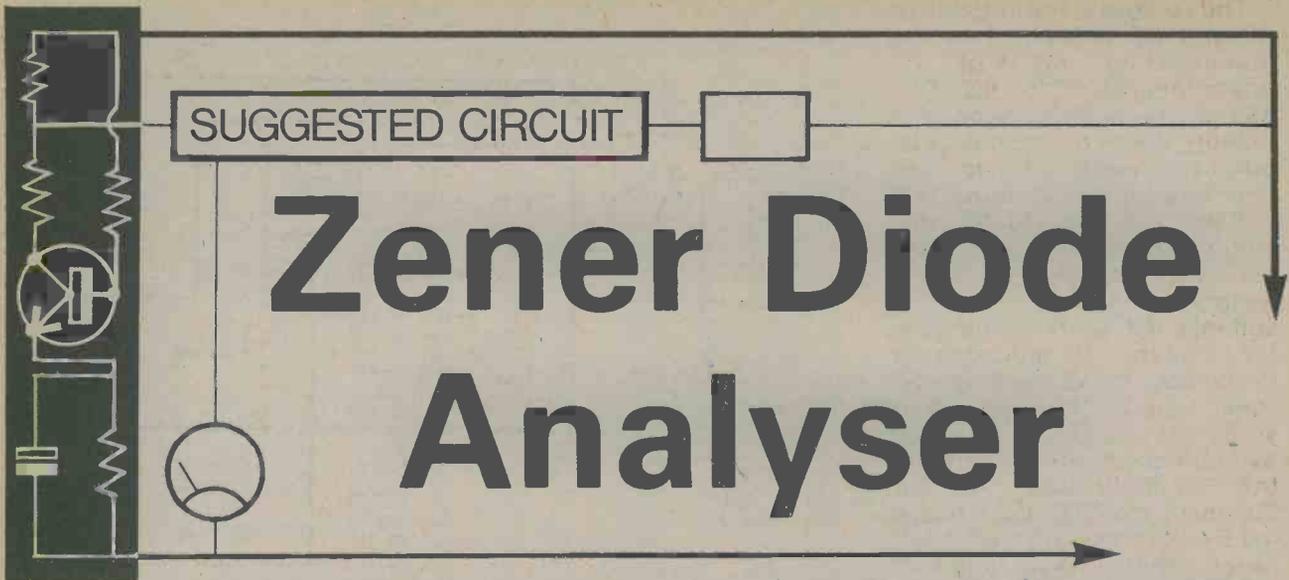

By G. A. French

Many of us fall into the habit of thinking that all zener diodes have voltage-current characteristics similar to that shown in Fig. 1. As soon as a small zener current is allowed to flow, the voltage across the zener diode stays constant at zener level for all higher currents. In practice such is by no means the case, this being particularly true of the lower voltage devices which, in many instances, have to pass a relatively high current before they approach the zener level and, even then, exhibit a marked slope in their characteristics.

This article describes a zener diode analyser which can evaluate the practical performance of a zener diode at five pre-set currents ranging from 0.1mA to 10mA. It can accommodate all zener diode voltages up to about 24 volts,

and voltage readings are given by a testmeter which is connected to the circuit only when required. In consequence, an expensive meter movement is not permanently tied to the unit. The analyser can check the performance of a zener diode which is to be employed in a new circuit and indicate the minimum zener current it requires for good voltage stabilising action. It can also be employed to sort out diodes which are salvaged from used equipment, and to find the zener voltage of diodes which have had their markings smudged or otherwise made illegible.


The analyser works on the simple principle of passing a known constant current through the zener diode under test and then measuring the voltage across it with a very high resistance voltmeter.

CIRCUIT OPERATION

The circuit of the analyser is given in Fig. 2. IC1 is an LM334Z constant current generator, and its output current flows through the test diode to the chassis rail. The three 9-volt batteries above the chassis rail give a positive supply to the i.c. of 27 volts. The constant current provided by IC1 is equal, in amps, to 0.0677 divided by the resistance, in ohms, which is connected between its pins 1 and 3. On position 5 of the range switch S1 the resistance is 6.8Ω, giving a constant current of almost exactly 0.01 amp, or 10mA. The resistance at positive 4 of the switch is 27Ω, whereupon the constant current calculates as 0.0025 amp, or 2.5mA. The current at position 3 of the switch is 1mA, at position 2 it is 0.25mA and at position 1 it is 0.1mA.

The voltage across the test diode is applied to the potential divider consisting of R6 and R7, with one-quarter of the voltage appearing across the second resistor. The current drawn by the potential divider is less than 2μA at a maximum zener voltage of 24 volts, and the low current flowing through it will have little effect on the accuracy of indications. ■

Fig. 1 A perfect zener diode voltage-current characteristic. Many practical diodes fall far short of this ideal

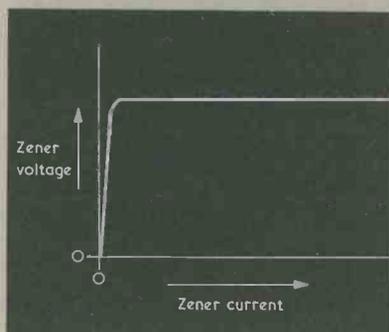

The voltage at the junction of R6 and R7 is passed to the non-inverting input of the operational amplifier, IC2. This has an input impedance of 1 million megohms and, with its output connected to its inverting input, functions as a voltage follower. Meter M1, connected between the output and the chassis rail, is a testmeter switched to a suitable d.c. volts range, and the voltage it indicates is multiplied by 4 to give the zener diode voltage. With some testmeters it may not even be necessary to carry out the multiplication. If, for instance, the testmeter has a 0-2.5 volt range and a 0-10 volt range, zener voltages below 10 volts can be measured with the meter switched to the 0-2.5 volt range, the readings being taken from the 0-10 volt scale.

The supply for IC2 is provided by BY3, the 9 volt battery immediately above the chassis rail, and by BY4, which is below the chassis rail. An offset null adjustment is given by the pre-set potentiometer VR1. Its slider is returned to the chassis rail and not to the lower negative rail, as is common with most offset null potentiometers. Because of the low voltage gain in the op-amp circuit the offset null adjustment is not critical.

On-off-switching is provided by S2(a) (b) (c). Since this requires 3 poles, it is a rotary switch. S1 is also, of course, a rotary switch. The current drawn by IC2 from BY3 and BY4 is approximately 1.2mA. Also flowing in BY3, and in BY1 and BY2, is the constant current selected by S1 when a test diode is connected.

Apart from R6 and R7, the fixed resistors may all be $\frac{1}{2}$ watt 5%. R6 and R7 should preferably be 5% as well, and will then normally be available in $\frac{1}{2}$ watt. VR1 is a 0.1 watt skeleton potentiometer. The four batteries can be any type, and a convenient size would be PP3. The two integrated circuits are available from Maplin Electronic Supplies. The lead-out inset for the LM334Z in Fig. 2 shows the lead-outs pointing at the reader.

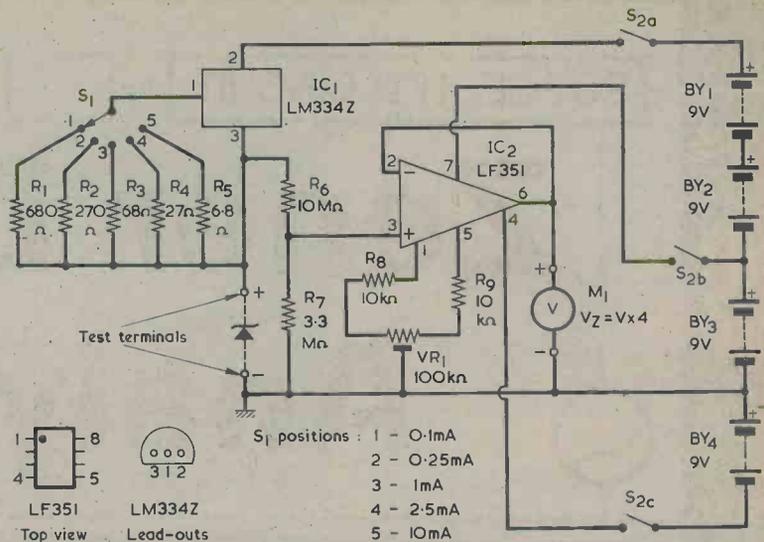


Fig. 2 The circuit of the zener diode analyser. S1 selects five different constant currents which flow through the test diode, the voltage across which is then measured.

CONSTRUCTION

The circuit can be assembled in a plastic or metal case with the two switches, the two test terminals and the two terminals for the external testmeter mounted on the front panel. When the case is metal it should be connected to the chassis supply rail. A chassis connection is not essential and if the case is all-plastic the chassis symbol in Fig. 2 can be ignored. S1 should be provided with a pointer knob and the front panel should be marked up to indicate the constant current it selects. Layout is not at all critical and the only wiring requirement is that all leads should be kept reasonably short. Ensure that pin 7 of IC2 cannot be accidentally connected to a supply potential higher than that provided by BY3.

After construction has been completed the two test terminals are connected together and the testmeter is connected up in the M1 position. VR1 is then adjusted for zero output voltage with the

meter switched to a low d.c. volts range.

In use the testmeter will normally be initially switched to a range whose maximum value is greater than 6 volts. It will then read a little in excess of this voltage when no diode is connected to the test terminals. S1 should be in position 1. If a zener diode is connected to the test terminals wrong way round the output voltage will correspond to about 0.6 volt. When the zener diode is connected correctly the voltage indication will be of zener voltage at 0.1mA. If necessary, the testmeter may then be switched to a lower volts range. S1 is next advanced, one step at a time, to position 5, whereupon an indication of the minimum current at which the zener characteristic starts to flatten out will be given. With some high voltage diodes the approximate zener voltage will be given at all positions of S1, or at positions 2 to 5 inclusive. Low voltage zener diodes may show a marked change in zener voltage at the different switch settings.

UNDERSTANDING TELEVISION



by

J. R. DAVIES

Over 500 pages

300 diagrams

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Introduction to colour TV

£3.95 P. & P. 80p

To:
DATA PUBLICATIONS Ltd.,
 57 Maida Vale, London W9

Please supplycopy(ies) of "Understanding Television", Data Book No. 17. I enclose cheque/crossed postal order for.....

Name

Address

.....

.....

.....

BLOCK LETTERS PLEASE

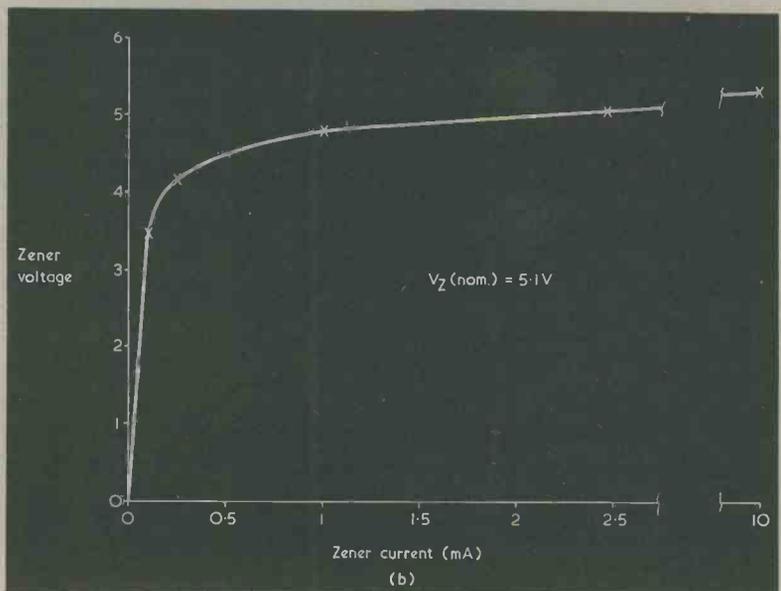
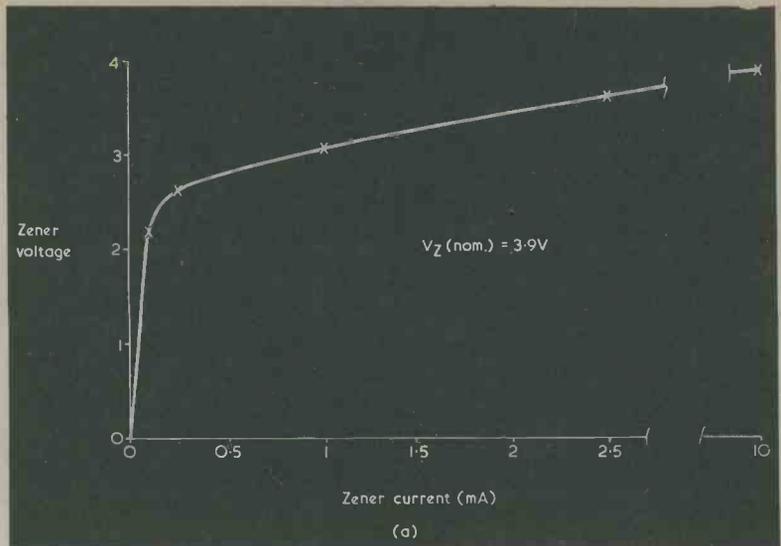


Fig. 3(a) A voltage-current characteristic, obtained with the aid of the analyser circuit, for a 3.9 volt zener diode.

(b) Another curve, given by a zener diode type BZY88C5V1

Fig. 3(a) shows the results obtained with a small 3.9 volt zener diode of unknown type and manufacture when checked with the prototype circuit. The crosses in the graph indicate the actual plotting points obtained by the analyser. A similar graph for a

BZY88C5V1 is given in Fig. 3(b). As can be seen, the first diode needs a zener current of at least 2.5mA if it is to provide an adequate zener performance, whilst the second diode should pass a zener current of at least 1mA.

ARE YOU MISSING COPIES?

Because of last summer's printing dispute and, subsequently to it, our then printers ceasing to trade, many readers have been unable to obtain some recent issues. For the time being we are still able to supply such numbers.

RECENT PUBLICATIONS



EARLY RADIO WAVE DETECTORS. By Vivian J. Phillips, B.Sc.(Eng), Ph.D., A.C.G.I., D.I.C., C.Eng., F.I.E.E., F.I.E.R.E. 238 pages, 215 x 140mm. Published by Peter Peregrinus Ltd. Price (UK) £18.00.

Nearly all of us tend to look upon the crystal and cat's whisker assembly as being probably the first radio signal detector of importance, and some of us may have heard vaguely of the coherer as preceding the crystal in this application. But there were many other types of radio detector in existence before and concurrent with the coherer, and this fascinating book describes them all in detail.

What is probably the most important detector of the pre-crystal era is nevertheless the coherer, and this worked on the principle that if a number of conductors were in loose contact with each other they exhibited a high resistance. When a radio signal was applied to them they "cohered" and offered a low resistance. Unfortunately, they did not "de-cohere" at the cessation of the radio signal and had to be tapped or agitated to return them to the high resistance state. Very many different coherers were developed and the metals could be in the form of filings, rods, balls, or virtually any other shapes which could be devised in those pioneering creative days.

They were also electrolytic detectors which offered the requisite non-linear resistance in the contact between a liquid and a metal electrode. Magnetic detectors were devised, the simplest being a very sensitive galvanometer and one of the more complicated being a rotating device incorporating 3-phase coils. Thin-film and capillary detectors were related to the coherer but took advantage of phenomena occurring in fluids. One of the more gruesome devices was the "Physiological Detector" in which electrodes were connected to the sciatic nerve of a newly killed frog, causing the frog's leg, to which were coupled a string and pointer, to twitch in response to the radio signal. The useful period of the detector came to an end when rigor mortis set in. . .

All these detectors and many more are described and illustrated in this book. It makes compulsive reading for anyone who wishes to rediscover the very early, and surprisingly successful, world of radio communication.

AUDIO CIRCUITS AND PROJECTS. By Graham Bishop. 192 pages, 215 x 125mm. Published by PAPERMAC (The Macmillan Press Ltd.) Price £4.95.

This book is the third in the PAPERMAC Electronic Projects series, and it presents nearly 100 tested circuits of amplifier and amplifier-related projects. Constructional details are given where necessary. All projects can be constructed on Veroboard, and ready-made printed circuit boards are available for designs which are better assembled in that way.

The book starts with a short treatise on human hearing, frequency range and the nature of sound, then carries on to microphones, pick-ups and speakers. Next dealt with are the basics of amplifiers. After this the main bulk of the book is devoted to working circuits. Covered first are pre-amplifiers, with attention being paid to filters, tone controls, mixers and electronic tone and attenuator control circuits. Veroboard layouts for many of the circuits are given. These are followed by power amplifier projects ranging from 1 watt to 70 watt designs. Again, Veroboard layouts are provided.

The book next turns to noise and rhythm projects, and these include attack and decay circuits, rhythm generators, envelope shapers, a reverberation unit and a peak overload detector, together once more with Veroboard assemblies. The following disco section describes sound-to-light modulators and a colour organ, and the final constructional pages deal with music circuits such as a stylus organ, organ generator and special effect oscillators. The components required for the projects, and sources of supply, are listed in two of the appendices at the end of the book.

NEWS . . . AND

10kHz to 100 MHz USB/LSB TRANSCEIVER BUILDING BLOCK


Ambit's 91600 receiver is based on an SL1600 series Plessey application design by James Bryant – modified to accept an 8-pole 10.7MHz SSB crystal filter to enable the frequency offset of the system to be used with the Ambit DFM7 LCD frequency read-out module for 1kHz resolution in the HF bands.

By using the correct first mixer, the range 10kHz to 100 MHz may be spanned – although for most users, the standard 1–500MHz range is quite sufficient. The unit provides approx. 10mW of SSB in transmit mode, and a complete SSB receiver with 1W output stage.

An external local oscillator and bandpass filter//preselector is required to cover the frequency band desired – full USB/LSB switching is provided on the board.

Price around £40.00 (in kit form), the 91600 offers a versatile basis for SSB TX/RX systems for HF to UHF.

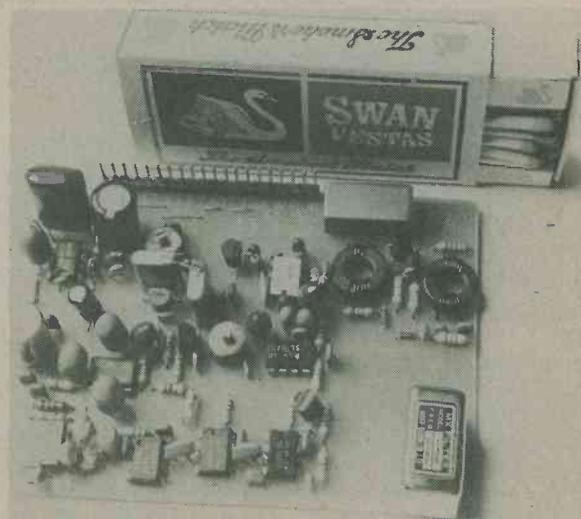Details from Ambit International, 200 North Service Road, Brentwood, Essex CM14 4SG.



HANDY PLANE FOR DO-IT-YOURSELFERS

In addition to their portable electric planes for heavy duty industrial use, SKIL have announced the birth of a handy plane for craftsmen and do-it-yourselfers. In designing this tool, SKIL wish to meet the ever growing demand for compact, practical tools with professional qualities, prevailing amongst home users.

Apart from edging and surfacing, the new plane will also do rabbeting jobs up to 7mm depth of cut. Planing jobs usually require a high degree of precision and for that reason the tool has a very high speed of 18,000 r.p.m., which also guarantees a fine, smooth finish of the workpiece. For chamfering jobs, a long V-notch has been designed in the base. A deflector removes chips away from the operator. The

powerful 480-watt motor is double insulated and radio/tv suppressed according to European safety requirements. The emphasis on handling ease has been consequently extended to easy depth and bevel adjustments and safe blade change.

The tool is equipped with a pair of blades that have HSS cutting edges and that can be resharpened many times. Two adjusting screws, a device for blade adjustment, a wrench and a locking pin to block cutterhead when changing blades, are also included in the standard equipment.

Enquiries to SKIL (Great Britain) Ltd., Fairacres Industrial Estate, Dedworth, Windsor, Berkshire, SL4 1QJ.


NEW THERMAL PRINTER

Bowmar Instrument Ltd., of 43 High Street, Weybridge, Surrey, have announced details of their newly available TP 3150 Thermal Printer.

Featuring: Full alpha-numeric 64 ASCII character set; complete interface electronics; 18 characters per line; over one line per second in parallel data mode for 18 column lines; TTL compatible 7 bit ASCII inputs that accept parallel or bit serial data; low stand-by power; quiet, non-impact thermal printing on white, bond-type paper; internal 32 character FIFO buffer; and left-to-right or right-to-left printing.

The printer is ideal for microprocessor terminal interfacing, test equipment, data recording devices, communications equipment or any alpha-numeric hard copy application where quiet, intermittent printing is required.

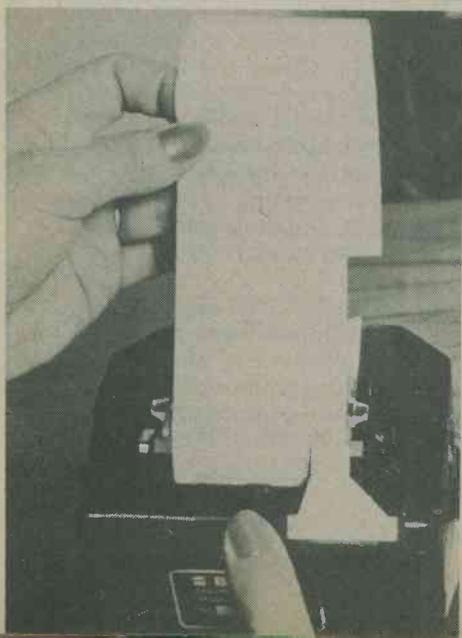The TP 3150 Thermal Printer's control function is implemented using a single chip microprocessor and it accepts 7-bit data in either synchronous parallel format with hand-shake signals or in asynchronous bit-serial format at a rate of 110 baud.



... COMMENT

PRESTEL FORGES AHEAD

'Prestel', the British system by which people can order goods and services through their home television sets, will shortly be available to over 60% of the population of the United Kingdom. This expansion is ahead of the schedule set by British Telecom (the new name for Post Office Telephones), and means that nearly every major city and town will have the service available, BBC World Service reported.

For Prestel, one's television set – specially designed or adapted – is also connected to the telephone. There is a push-button control unit rather like a pocket calculator. On pushing the appropriate button, the silicon chip circuits inside the set dial up a central computer over the 'phone line. This sends back signals to produce diagrams and text information on the screen of the TV set. The information capacity of the system is limited only by the capacity of the central computers.

Material available ranges from free information like transport timetables and catalogues for used cars and 'mail-order' goods, through cheap computer games and sports events to expensive specialist information about, say, trends in the stock market.

For some time now wine merchants have not only had their lists in Prestel, but also have permitted ordering, by tapping out the list numbers of the wine you want, the quantity and the number of your bank credit card. Then, within a day or two, a van turns up at your door with the wine you have ordered. There is no scope for practical jokers in this, because delivery is only to the credit card holder's address, and the system can record the identity of the 'phone line used for ordering.

The latest facility to be offered allows booking of theatre seats. The Royal Shakespeare Company's list of productions can be called up on the screen of your home or hotel TV, and by tapping the appropriate keys on the control unit, details of seats available for particular productions and days can be brought to the screen. You make your selection, give your credit card number – and the seats are booked by the computer.

So why do this, when you can book by 'phone? The answer is simple – it is much more like going to the theatre box-office in person. You can see the choice available set out on the screen in front of you at home or in your hotel bedroom and make a logical informed decision – not so easy when you are told at top speed by a busy box-office clerk on the 'phone, with others ringing in the background. And then when you get to the theatre you might find yourself behind a pillar, or that the seats have been sold twice. With the computer keeping tally, that is impossible.

BEGINNER'S BOX OF BITS

One of the snags for constructor beginners is that, unlike the old hand, they do not have a box of bits accumulated over the years. The experienced constructor can, with a bit of luck, find that he already has in his junk box, perhaps, half the components he needs for a new project – not so the beginner.

To overcome this snag for the newcomer Home Radio (Components) Ltd., P.O. Box 92, 215 London Road, Mitcham, Surrey, are now supplying a "Beginner's Constructional Hamper". Altogether the hamper contains 62 items covering 27 different components, from half-a-dozen assorted bulbs to a set of parts to make up a small chassis. Home Radio estimate the retail value of the hamper to be approximately £35 and yet it can be obtained from them for only £14, plus V.A.T.

WORLD'S SMALLEST HOME COLOUR VIDEO CAMERA



World's smallest home colour video camera, Hitachi's Model VK-C1000 incorporating a single chip MOS colour image sensor.

Using a MOS (metal oxide semiconductor) colour image sensor, Hitachi have manufactured the VK-C1000 home colour video camera, the smallest in the world. It will be marketed on the Japanese market from April 1981 at a price of around £690.

The recent improvements in functions and efficiency of home VTR equipment, together with its rising popularity has created a demand for a small lightweight and highly reliable colour video camera. The VK-C1000 has been developed by Hitachi to satisfy this demand, particularly for a video camera for outdoor use.

A single chip MOS image sensor of 2/3rds inch size has been developed using advanced VLSI (very large scale integrated circuit) technology and is used instead of a pick-up tube, and in addition the camera circuits are largely integrated. With these features, stability, long life, extremely high reliability and good picture are assured.

LOW CURRENT PILOT LAMP

By
F. L. Stephenson
Battery-saving flashing light

It is often desirable for battery powered equipment to have some form of pilot light to indicate when it is switched on. In the interests of battery economy the light should draw a low current only and a common approach is to have a light which flashes on for a short period at regular intervals. The average current then drawn from the supply is quite low, even when the light is brightly illuminated when it is turned on. The circuit to be described is for a flashing pilot lamp which can be added to equipment having a 9 volt battery supply.

CIRCUIT OPERATION

The circuit of the flashing pilot lamp appears in the accompanying diagram. An obvious choice for the timing device controlling the light is an ICM7555. This draws a very low supply current and can function with high value timing resistors.

The ICM7555 is employed in a standard astable oscillator configuration with capacitor C1 charging through R1 and R2, and discharging through R2 on its own. The i.c. output at pin 3 is high when the capacitor charges and is low when the capacitor discharges. The l.e.d. lights up when the output is low and a current of about 12mA flows through it, giving bright illumination.

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5% unless otherwise stated)

- R1 6.8M Ω 10%
- R2 750k Ω
- R3 100 Ω
- R4 470 Ω (see text)

Capacitors


- C1 1 μ F polyester
- C2 100 μ F electrolytic, 10 V. Wkg.

Semiconductor

IC1 ICM7555

Light-Emitting Diode

LED1 red l.e.d.

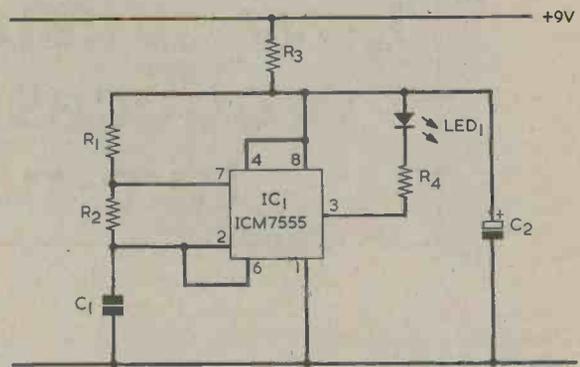

ICM7555
Top view

The low current pilot lamp circuit. The l.e.d. is brightly illuminated for half a second at 5 second intervals.

Since C1 has the value of 1 μ F it is an easy matter to calculate the charge and discharge times. The charge time in seconds is equal to 0.685 times the sum of R1 and R2 in megohms. This calculates as 5.2 seconds to 2 significant figures. The discharge time is equal to 0.685 times the value of R2, or 0.51 second. So, the l.e.d. is lit for approximately half a second at intervals of 5 seconds.

The current drawn from the 9 volt supply when the l.e.d. is lit is almost entirely the 12mA which flows through the l.e.d. The current when the l.e.d. is extinguished is a mere 60 μ A. The average current drawn from the supply is therefore about one-eleventh of 12mA, or 1.1mA. This current can, of course, be reduced by increasing the value of R4, at the expense of reduced light intensity in the l.e.d. A value of 2.7k Ω in this resistor, for instance, produces an l.e.d. current of approximately 3mA, whereupon the average current drawn from the supply is a little less than 0.3mA.

R3 and C2 decouple the ICM7555 circuit from the 9 volt supply and ensure that l.e.d. current pulses are not passed along the supply rails. ■

ELECTRONIC DOOR BUZZER


By A. P. Roberts

**Low consumption unit
produces distinctive
two-note tone**

This inexpensive door buzzer circuit produces a frequency modulated tone which is quite penetrating and attention-catching. The unit is powered by an internal 9 volt battery which is only connected into circuit when the bell-push is pressed. Even then, the current drawn from it is only 6mA and so, with normal usage, its life should be very nearly equal to its shelf life.

CERAMIC RESONATOR

The low current consumption is achieved by using a new type of component known as a "ceramic resonator". This is a piezo-electric transducer which produces an audible tone when fed with an electrical signal derived from an oscillator. Efficiency is very high and only a few mA of drive current are required to produce a loud audio tone. As the resonator is a high impedance device, the signal level should be at a fairly high voltage. The transducers are not intended to function as audio sound reproducers since they are

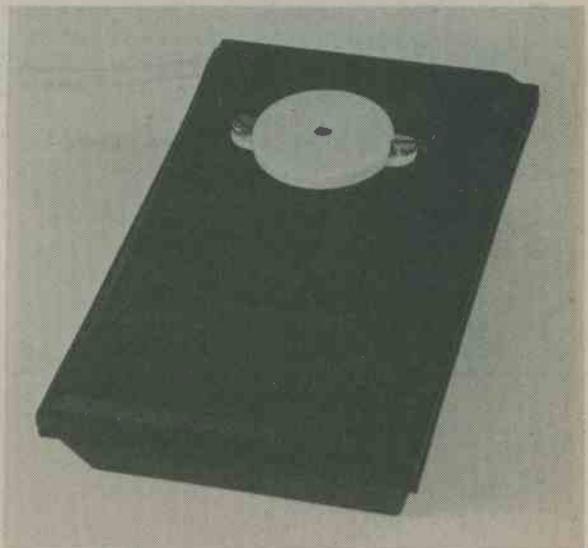

The ceramic transducer is mounted on the front of the case which holds the electronics

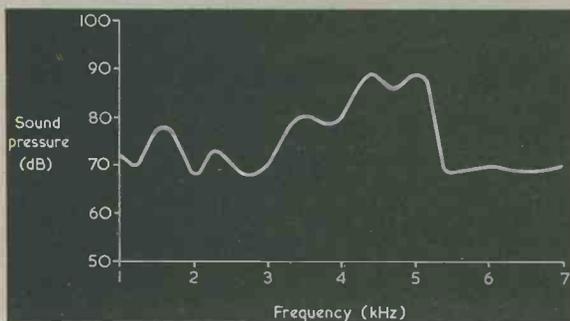


Fig. 1. The output response of the ceramic transducer type PBN-2720

not designed to give high quality. They are intended, instead, to be employed in alarm circuits where a flat response over the audio frequency spectrum is not required.

The ceramic resonator used in the present project is a type PBN-2720, and is available from Ambit International. It has the frequency response shown in Fig. 1. The graph covers the range from 1kHz to 7kHz, at which the transducer has greatest efficiency. There is a pronounced peak at about 4.5 to 5kHz due to the resonant performance of the transducer, but the audible output is quite high over the entire frequency range.

DOOR BUZZER CIRCUIT

The complete door buzzer circuit is given in Fig. 2. This is based on a dual amplifier i.c. type TL082CP, which can be obtained from Watford Electronics, 33/35 Cardiff Road, Watford, Herts.

The two sections of the amplifier are used in identical oscillation configurations. One oscillator produces an audio tone to drive the ceramic transducer whilst the other runs at a much lower frequency and frequency modulates the first. The point of using frequency modulation is that this gives an audible output having more than one frequency, which is much less likely to be masked by domestic sounds. The sound is also more pleasant and less monotonous than a single frequency tone. In the present circuit a square wave modulating signal is employed, giving a "warbling" effect since the output tone is switched continuously between two pitches. The result is not unlike the ringing sound given with a Trimphone.

The lower frequency oscillator employs IC1(a) and is used in an oscillator circuit which is nowadays becoming quite common. R1, R2 and R3 all have the same value, whilst R4 and C2 control the oscillation frequency. At switch-on, C2 is discharged, whereupon the inverting input is negative of the non-inverting input, and the amplifier output goes positive. This effectively puts R3 in parallel with R1, so that the non-inverting input is at two-thirds of the supply potential. C2 commences to charge via R4 until the voltage across it reaches the same voltage as that at the non-inverting input, whereupon the amplifier output starts to go negative, causing the non-inverting input to go negative as well. There is a regenerative effect which results in the amplifier output going fully negative and causing the non-inverting input to be at one-third of supply potential. C2 now discharges via R4 until the voltage across it reaches the same potential as the non-inverting input. A reverse regenerative effect takes place, resulting in the amplifier output going positive again, the non-inverting input being taken to two-thirds of supply voltage, and the capacitor charging once more through R4. The cycles repeat in

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

- R1 33k Ω
- R2 33k Ω
- R3 33k Ω
- R4 330k Ω
- R5 68k Ω
- R6 33k Ω
- R7 33k Ω
- R8 33k Ω
- R9 47k Ω pre-set potentiometer, 0.1 watt horizontal
- R10 39k Ω
- R11 6.8k Ω
- R12 3.9k Ω

Capacitors

- C1 4.7 μ F electrolytic, 10V. Wkg.
- C2 0.1 μ F polyester type C280
- C3 0.01 μ F polyester type C280

Semiconductors

- IC1 TL082CP
- TR1 BC109

Switch

- S1 bell-push

Transducer

- X1 ceramic resonator type PBN-2720

Miscellaneous

- Small plastic case
- Veroboard, 0.1in. matrix
- 9 volt battery type PP3
- Battery connector
- Nuts, bolts, wire, etc.


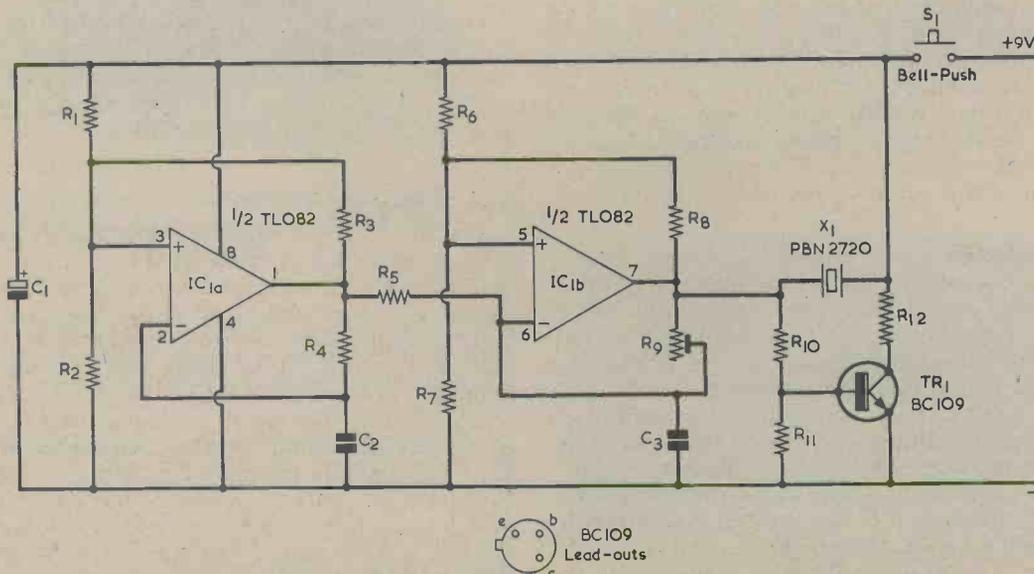


Fig. 2. The circuit of the electronic door buzzer. Low frequency oscillator IC1(a) frequency modulates the audio oscillator, IC1(b)

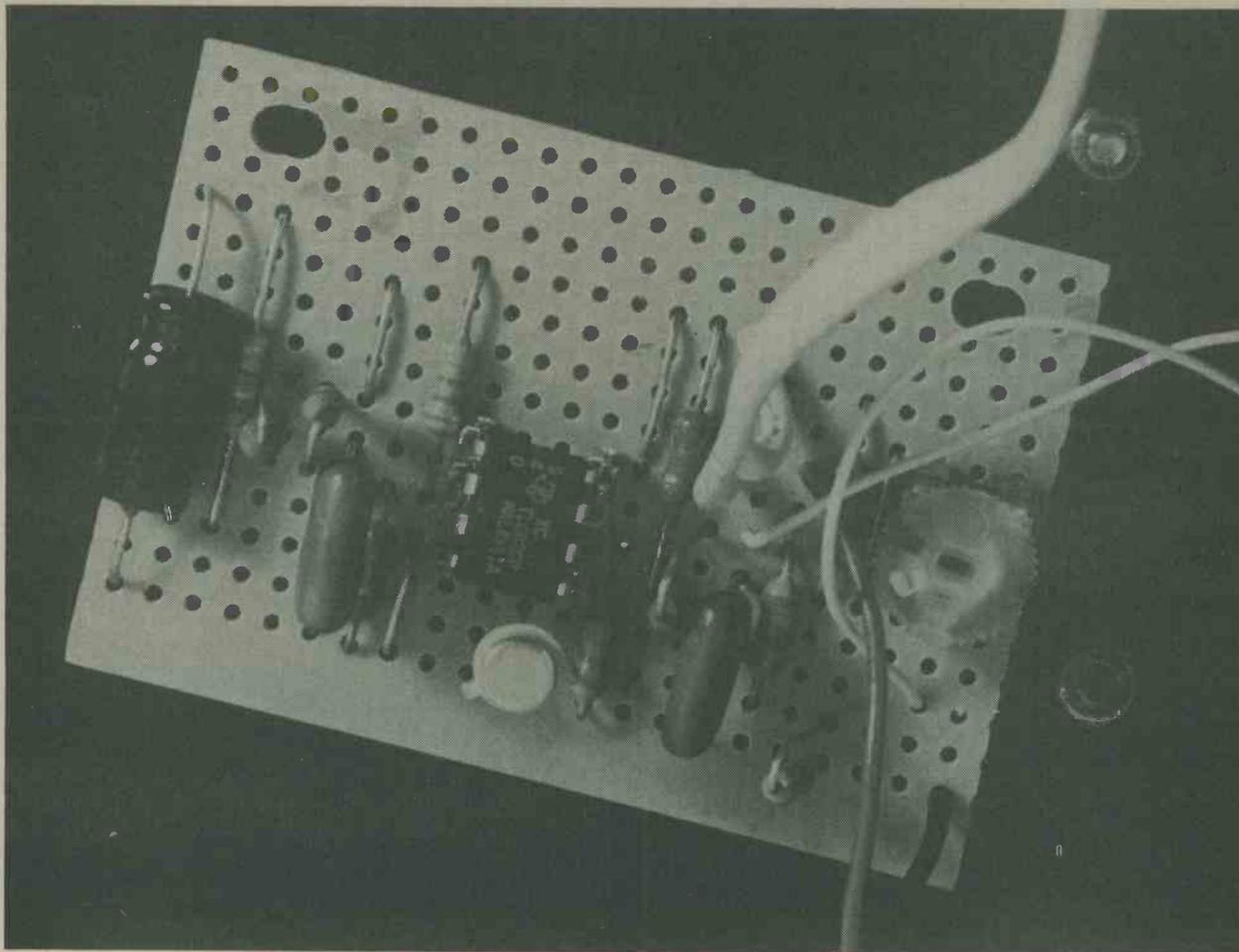

Close-up view of the Veroboard component panel

this manner with C2 alternately charging and discharging. A square wave is produced at the amplifier output.

Amplifier IC1(b) is used in the same type of oscillator circuit, but R9 and C3 have lower values to enable the oscillator to run at an audio frequency. This frequency can be varied by adjusting the resistance inserted into circuit by R9. The output of the lower frequency oscillator is coupled to the inverting input of IC1(b) via R5 and modifies its oscillation frequency according to whether IC1(a) output is positive or negative. The required frequency modulation of the audio oscillator is thus obtained.

OUTPUT STAGE

Since the ceramic transducer requires only a low drive current it can be driven directly from the output of IC1(b). However, the signal amplitude at this output is only about 6 to 7 volts peak-to-peak and a drive voltage higher than this is desirable. The higher voltage is achieved by connecting the output of IC1(b) to the transducer and also to the base of the inverting transistor, TR1. The collector of TR1 connects to the remaining terminal of the transducer. The result is that when IC1(b) output is positive the output from TR1 collector is negative, and vice versa, resulting in a peak-to-peak drive voltage for the transducer which is well in excess of battery voltage.

Since the output voltage of IC1(b) does not go fully

to negative rail potential when it goes negative, TR1 base is connected by way of the potential divider consisting of R10 and R11. The voltage drop provided by the potential divider ensures that TR1 is switched cleanly on and off, so that the voltage swing at its collector is the maximum possible.

On-off switching is provided by S1, which is of course the bell-push. C1 is a supply bypass capacitor and it is perfectly in order to use a component here which has a higher working voltage than that specified in the Components List.

ASSEMBLY

The unit can be assembled in virtually any small plastic case, since the component panel and the PP3 battery require little space. The ceramic transducer is mounted on the front panel of the case by two small bolts and nuts. The two holes required in the panel can be marked out by using the transducer as a template. A third small hole is needed to enable the two leads from the transducer to pass into the interior of the case. Two small terminals for connection to the bell-push could be positioned on one side of the case. A permanent connection was used with the prototype unit, however, and the 2-core cable which connects to the bell-push is passed through a hole drilled in the side of the case.

The component panel is a piece of Veroboard of 0.1in. matrix having 22 holes by 14 copper strips.

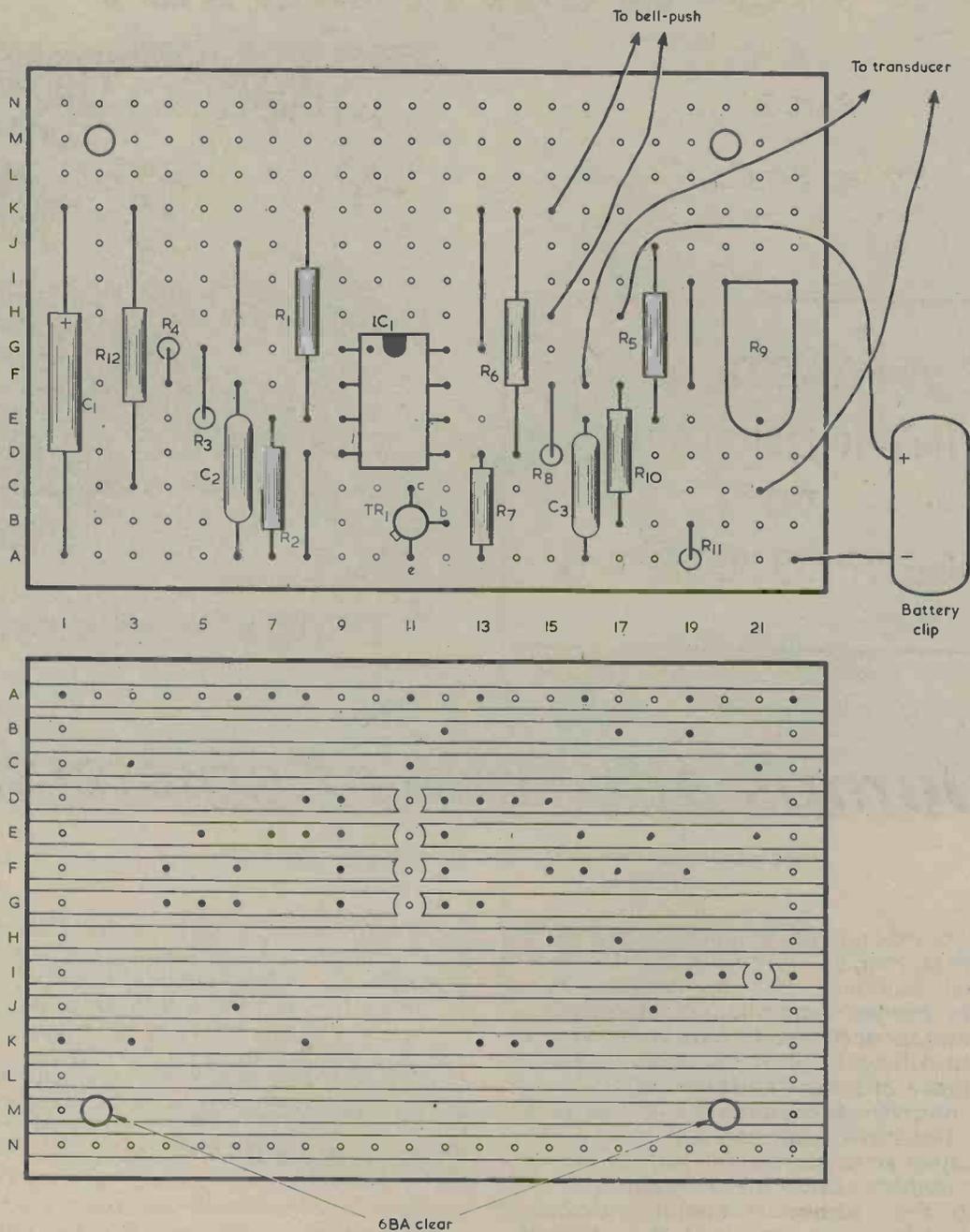


Fig. 3. Layout of components and wiring on the Veroboard panel

Details are given in Fig. 3. The board has to be cut from a larger size, after which the two mounting holes are drilled. The five breaks in the copper strips are next made, and then the components and link wires are soldered into place. Finally to be connected are the wires to the transducer, the bell-push and the battery clip. The board is secured inside the case by means of two 6BA bolts and nuts, with spacing washers to keep the board underside clear of the inside surface of the case.

ADJUSTMENT


R9 is adjusted with the bell-push pressed and it provides a wide range of output pitches. If the potentiometer is adjusted backwards and forwards over this range it will be found that there are noticeable peaks in the sound output level at several settings. R9 can be given any setting which coincides with one of these peaks, the one chosen being a matter of personal preference.

The INSTRUCTOR

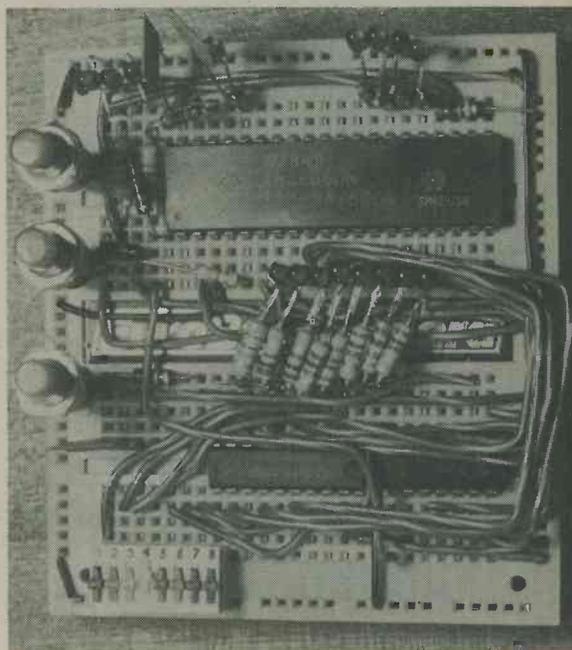Part 7

By Ian Sinclair

A PRACTICAL
INTRODUCTION
TO
MICROPROCESSORS



Jumps and Index Registers.

The program-counter relative displacement is one way of shifting a program momentarily out of its normal sequence, but the program count returns to normal immediately afterwards. A jump is another sort of shift. A jump is not made to pick up a byte of data, it's done to shift to another piece of program. There are four jump instructions on the 8060, and we'll look at all four of them. The most basic sort of jump, JMP, is what is called an unconditional jump.

That means that when the program says JMP, you jump! Fig.1 shows an example. We use a NOP to start things off, then JMP followed by the displacement 0000011, which places the prog-

ram three steps on. Now set the data switches back to NOP again and keep pressing GO. The count continues from 00000111; it doesn't return to where it was before the jump, which is an important difference between this type of instruction and the previous lot. To distinguish them, this is called a transfer function whilst the others are called memory reference instructions.

CONDITIONAL JUMPS

The JMP instruction has its uses, particularly if the 8060 is to be used at the end of a program to keep a number displayed, but the conditional jumps are even more useful. A conditional jump takes place only if some test is fulfilled. For example, the Jump-if-Zero instruction (JZ) means that the program will jump only if the byte in the accumulator is zero. Fig.2 shows examples of this, using a positive number, a negative number and then zero in the accumulator. If you keep an eye on the address l.e.d.'s you'll see that the jump occurs only when the accumulator is at zero.

The two other jumps are used to detect other conditions. The Jump-if-Positive (JP) instruction will cause a jump to take place if the byte in the accumulator has a zero in its D7 position - this means that a jump will also occur for a byte of zeros. The JNZ (Jump-if-Not-Zero) is as the name suggests - the jump will take place if there is any

RESET		
NOP	00001000	Note address
JMP	10010000	Note address
DISP	00000011	Note address
NOP	00001000	Note address

(Remember that the data bits are not important in this example, only the addresses. The same will be true of all the examples in this Part.)

Fig. 1.

RESET

LDI	11000100	Note address at each step
01	00000001	
jz	10011000	
03	00000011	
LDI	11000100	
-1	11111111	
JZ	10011000	
03	00000011	
LDI	11000100	
00	00000000	
JZ	10011000	
03	00000011	

Fig. 2

number, positive or negative but not zero, in the accumulator. Each one of these jumps, when we use the binary codes shown in Fig. 3, is program-relative, meaning that the instruction has to be followed by a displacement byte which can be up to +127 or -128 places from the program counter address.

THE INDEX REGISTERS

The method which is used in the INS8060 to change addresses by more than 128 steps is known as indexing, and the INS8060 uses three sixteen-bit registers (in addition to the program counter) to store addresses. These registers are called pointer registers, and the program counter itself is classed as one of these registers, being referred to as PO. The others are then numbered

P1, P2 and P3 respectively. So that we can specify which pointer register we want to use, these numbers are written in binary form as 00, 01, 10 and 11 and are used in this form in the instructions which make use of pointer registers.

Let's show what happens. Fig.4 shows a program which loads up pointer P1 with an address. Since the address is two bytes long and the accumulator can handle only one byte at a time, the pointer has to be loaded up in two groups of steps. We start with the number we want to load into the lower byte, in this example 00001010, and load-immediate this into the accumulator. The next instruction is a single byte instruction starting with 001100. Why "starting with" and why only six bits? The reason is that it can be completed by the two bits which specify which pointer we're using. If we finish it with 01 we shall load the byte into pointer P1, if we finish with 10 we shall load P2, and if the byte ends with 11 then P3 is loaded. This instruction is known in shortened form as XPAL - exchange the accumulator with the low byte of the pointer, and when it's used in a program we have to be careful to specify which pointer register is to be loaded. In this example, we're loading P1, so that the code is 00110001, with the final two bits indicating pointer 1. Note, by the way, that this is an **exchange**, so that if there has been a number in the pointer register, its lower byte will now be in the accumulator. Since we started by resetting, this should not cause any problems, and in any case can be cleared by loading another number into the accumulator. We do this, using load-immediate again, setting this byte to 00001111. This is shifted into the pointer register by using the single-byte instruction XPAH, binary code 00110101. This instruction exchanges the byte in the accumulator with the higher byte of the pointer and, once again, the last two bits of the code indicate the number of the pointer register. Since we've used the code 01 for the last two bits, we're transferring to pointer 1 as before.

The result of all this is that we have loaded up pointer 1 with two bytes. Now one of these is the AD11 bit and another is the AD1 bit, so that these l.e.d.'s should come on when we make the address change to the address in the pointer register, and we can use the spare l.e.d. to check for the 1's we expect to find in AD10, AD9 and AD8. The address isn't there yet, though - it's still loaded in the pointer and we have no connections to the pointer register. One way to exchange the

The JUMP instructions for jumps relative to the program counter

JMP	10010000	Unconditional jump
JP	10010100	Jump if accumulator is positive or zero
JZ	10011000	Jump if accumulator contains zero
JNZ	10011100	Jump if contents of accumulator are not zero

Fig. 3.

RESET		
LDI	11000100	
LBYT	00001010	
XPAL(1)	00110001	
LDI	11000100	
HBYT	00001111	
XPAH(1)	00110101	Note address
XPPC(1)	0111101	Note address
NOP	00001000	Note address
XPPC(1)	00111101	Note address
NOP	00001000	Note address

Fig. 4.

The pointer register codings.

Mnemonic	Code, P1	Code, P2	Code, P3
XPAL	00110001	00110010	00110011
XPAH	00110101	00110110	00110111
XPPC	00111101	00111110	00111111

Note that the last two bits of the code are used to show which pointer register is being used in each case.

Fig. 5.

The pointer-indexed jumps.

JMP	100100XX
JP	100101XX
JZ	100110XX
JNZ	100111XX

In each case XX means the pointer number 01 for P1, 10 for P2, and 11 for P3.

Fig. 6.

two is the final instruction on the list in Fig.5. This one, abbreviated to XPPC, has the effect of exchanging the bytes in the program counter (the present address) with the bytes in the pointer register. When this instruction, coded as 00111101, is set up and the GO button pressed, the result is to exchange the bytes so that the l.e.d.'s AD11 and AD1 light. The new address is actually one **more** than the address in the pointer register. The address which *was* about to appear on the l.e.d.'s (1000) is now stored in the pointer register, so that we can return to this address at any time by repeating the XPPC instruction. Try it - having exchanged, getting the AD11 and AD1 l.e.d.'s lit, and then using NOP to move the address on a bit. Then set up XPPC and, on pressing GO, you'll find the 1000 address (with l.e.d. AD11 out) back in business. This facility for hopping to a new address and then hopping back is extremely useful, and is found in all but the simplest of programs.

In this example, each of the instructions XPAL, XPAH, XPPC has referred to pointer 1, and the same instructions can be made to refer to any of the other pointer registers simply by modifying the two bits at the end of the binary code number. Fig. 5 shows these codes as they are used for each of the pointers.

INDEXED ADDRESSING

The use of indexed addressing, as this system is called, isn't confined to the XPPC instruction, and some very useful program tricks are available through the use of the pointer registers for other instructions. To take an example, Fig.6 shows the four JUMP instructions with their pointer-register variations. Once again, the binary instruction code consists of six bits, and two bits added on are used to specify which pointer register is used. When a pointer relative jump instruction is used, then, the address which is fetched is the sum of the address number stored in the pointer register plus the displacement byte which follows the jump instruction, plus 1. Fig.7 shows an example of this in use, employing pointer 2 this time. The first series of instructions load up pointer P2 with an address which will light up l.e.d. AD11, and display 1011

RESET		
LDI	11000100	
LBYT	00001000	
XPAL(2)	00110010	
LDI	11000100	
HBYT	00001000	
XPAH(2)	00110110	Note address
JMP(2)	10010010	Note address
02	00000010	Note address
NOP	00001000	Note address

Fig. 7.

List of instructions which can be indexed to a pointer. In the list, M is used to indicate the index bit, which will be set (1) for auto-indexing, reset (0) for normal pointer indexing. The XX symbols are used as in Fig. 6 to indicate the pointer number.

LD	11000MXX	Load accumulator from address
ST	11001MXX	Store contents of accumulator in address
AND	11010MXX	AND accumulator with address contents
OR	11011MXX	OR accumulator with contents of address
XOR	11100MXX	X-OR accumulator with contents of address
DAD	11101MXX	Decimal add contents of memory to accumulator
ADD	11110MXX	Binary add contents of memory to accumulator
CAD	11111MXX	Complement and add contents of memory to accumulator
ILD	101010XX	Increment memory and load to accumulator
DLD	101110XX	Decrement memory and load to accumulator

The JUMP and pointer exchange codes have been mentioned previously.

Fig. 8.

on the lower bits. The JUMP instruction uses the code relative to P2, and is followed by a displacement of two places. Run through this one, and check the address number before and after the displacement has been loaded into the microprocessor. As you might expect by this time, we can also jump to an address which is lower than the one loaded into the pointer register by using a negative displacement. Try the program again, but this time using a displacement of 11111110 (equal to decimal -2), and check the address before and after the GO switch is pushed.

Two more instructions which can make use of indexed addressing are the increment-and-load (ILD) and decrement-and-load (DLD) instructions. As usual, these consist of a basic six bits, which are completed by two bits which specify the correct pointer register. Remember that these two instructions change the data byte in the memory but not the address in the pointer register. What happens is that the GO action after the displacement byte causes the address lines to jump to an address equal to the pointer address plus the displacement. The data byte in this address is then incremented (+1) or decremented (-1) and loaded into the accumulator. The next time this byte is fetched, it will again be incremented or decremented, according to which instruction has been used. This is a convenient way of keeping a count, and the DLD instruction can, for example, be followed by a JZ, so that some new part of the program can be followed when the count is finished.

All the instructions shown in the table of Fig.8

RESET		
LDI	11000100	
01	00000001	
XPAL(3)	00110011	
NOP	00001000	
LD(3)	11000111	Note address
01	00000001	Note address
NOP	00001000	Note address
LD(3)	11000111	Note address
01	00000001	Note address
NOP	00001000	Note address

For a decrement, use 11111111 after the load instruction instead of 00000001.

Fig. 9.

can be used with pointer register indexing, and with yet another trick in store. Try the program in Fig. 9. This loads an easily recognisable address, into pointer P3 this time, and then, after a NOP, uses a load relative to P3, with a displacement of 1. This produces the expected address reading of 00000001, and following this with a NOP gets us

back to the normal address again. The next P3 relative load produces something unusual though, and when we use several more sequences of NOP and LOAD (relative P3), we can see what is happening. Each time the pointer register is used the starting address is incremented by one, so that each fetch from memory is from the address one higher than the one before. This type of system is called auto-indexing, and it's specified by an extra bit in the instruction. On all the instructions in Fig.8 the basic instruction consists of only five bits. The sixth bit is the auto index - 1 if the instruction is to be auto-indexed, 0 if not. The final two bits of the instruction are then used to specify which pointer register is to be used. Each instruction is then followed by a "displacement". When the instruction is used for the first time the displacement does *not* cause the address to change. The address which is fetched first time around is simply the address which is stored in the pointer register. At the end of this instruction, though, the pointer register has the "displacement" added to it, so that the next fetch from the pointer is to an address higher than before. The usual "displacement" or increment number is 1, but we could use any other number as we pleased. Now what happens if we use a negative number, such as 11111111 (decimal -1)? Try it out, using the program of Fig. 9. We load up the pointer as usual, NOP and then load, auto-indexed, relative to P3 with a - 1 displacement. What happens at each fetch?

STACK POINTER

This time, the pointer register is decremented by 1 before being fetched and used as an address. There's a very good reason for treating incrementing and decrementing in a different order. Suppose, for example, we want to preserve some constants, the numbers in various registers, while the microprocessor gets on with something different. We can load a number into the accumulator, store it with auto-indexing (using +1 for incrementing) and repeat this set of steps for each number we have to preserve. The result will be that each number is stored in order somewhere in the read/write memory. Now how do we get them back? At the end of the loading operation, the address in the pointer register will be one higher than the address which was used to store the last byte. This is because the address is incremented *after* the address has been used. If the same system were used when the index is decremented, then the first address fetched back would be empty or, worse still, nonsense, since we haven't written anything in that memory space. The system of decrementing the address before fetching ensures that we can fetch back the bytes in exactly the opposite order from that in which they were stored - first in, last out. This is the action of a "stack", and the register which is used in this way is often called the "stack pointer".

There are still a few secrets left. One is that in any memory - reference instruction (any in the table of Fig.8), the value 10000000 used as a displacement produces rather odd results, whether the instruction is PC relative, indexed or auto-indexed. The program of Fig.10 shows an example. The extension register is loaded with the byte

RESET


LDI	11000100	
BYT	11111110	
XAE	00000001	
NOP	00001000	
LD(P1)	11000000	Note address
- 128	10000000	Note address
NOP	00001000	Note address

Fig. 10.

11111110 (decimal -2), and after a NOP, the load-from-memory instruction is followed by the displacement 10000000, program relative. This number is decimal -128, but the program doesn't move 128 steps back, but only from 0110 to 0100. What has happened is that the number in the extension register has been used as a displacement relative to P1, which was reset to zero. Unless you've done some programming, it's difficult to appreciate the value of this, but one example may give you a glimmering. Usually, when we have a displacement, we have to specify it in the program, but this lets us use a displacement which isn't programmed! The outstanding example of this is a scanned keyboard.

There are two main ways of using a keyboard to input information to a microprocessor. One is to connect the keyboard to a digital circuit which will convert each key press into its appropriate digital circuit which will convert each key press into its appropriate digital code - that's a hardware solution. This type of method succeeds when each keyboard switch is separate. The other method uses a matrixed keyboard, where the keys are arranged in connected rows and columns. The action of a key is simply to short out one row to one column. With a system like this, converting the key-push into a digital code is not nearly so easy, and a method called "software scanning" is used, which is made much easier by the use of the extension register as we've described. Using the 5 x 4 matrix of Fig. 11 as an example, a counter is used to convert a few digits of an address into a logic 0, which is applied to one column of keys. If a key in this column is depressed, one data line is taken to logic 0. Note that only four data lines are affected - in this example the upper lines. This gives a number on the data line which can be loaded into the extension register. The number can then be used as a displacement in a load-from-memory, so reaching a memory address where the correct binary code for the number is stored. The beauty of this system is that the key action doesn't have to generate the correct binary number, simply *any* binary number, provided no two keys give the same number. If no key on the first column is pressed, the address increments, the lower four data lines are also incremented,

An example of a matrixed keyboard.

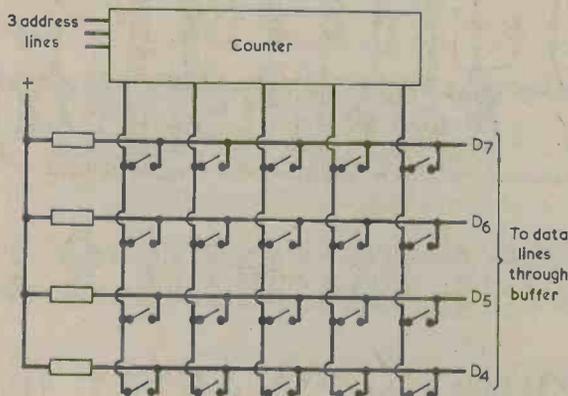

Programming: the keyboard program consists of putting out the keyboard addresses in sequence. If, when an address is put out, a zero is detected on the upper data lines, the byte is shifted into the extension register. If the data byte is still 1111XXXX, then the next address is put out, and so on until all the keyboard lines have been scanned. The program usually provides for "software debounce"—if a byte is returned on the data lines, the same address is scanned again a few milliseconds later to confirm the presence of a key pressed.

Fig. 11.

and the second column is activated. Even if the key which is now pressed is in the same row, the new number on the lower lines ensures that a different byte is loaded into the extension register.

NEXT MONTH

In next month's issue we shall look at the interrupt system, flags and sensing.

(To be concluded)

TRADE NOTE

ULTRASONIC TRANSDUCERS

Impectron Limited, of Foundry Lane, Horsham, W. Sussex, RH13 5PX, are now producing two new low cost matched ultrasonic transducers. These are small, light and highly sensitive, and they offer an excellent performance for applications such as industrial control and intruder detection systems.

The EFR-OCB25K5 and EFR-RCB25K5 are transmitter and receiver respectively, with a nominal centre frequency of 25kHz. The sensitivity is around -65dB per volt per microbar with a minimum bandwidth of 3kHz. Overall dimensions are 1 inch long

(body length being 0.37 inch) by 0.95 inch diameter for both receiver and transmitter. The internal construction of the transducers incorporates a compound vibrator consisting of a ceramic chip and conical aluminium resonator. This assembly provides sensitivity

and wide bandwidth, whilst the choice of body material and production methods ensure a long life in demanding environments.

Delivery is ex-stock, and application notes are available by return from Impectron to help circuit designers.



RADIO & ELECTRONICS CONSTRUCTOR

MARCH 1981

IN NEXT MONTH'S ISSUE

ROOM THERMOSTAT UNIT

Uncomplicated
robust circuitry

Temperature
control from
10 to 30°C

Switches currents
up to 8 amps




HIGH QUALITY COMPRESSOR

- Variable compression threshold
- High compression ratio without distortion
- Fast attack, slower decay

MEDIUM & SHORT WAVE RADIO

- ★ Medium waves plus 25, 39 and 49 metre bands
- ★ Low cost design
- ★ Special grade ferrite aerial

PLUS MANY OTHER ARTICLES

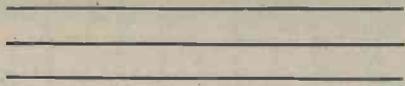


Reverbera

Self-contained self-powered unit

By

R. A. P.

Switching reverbera

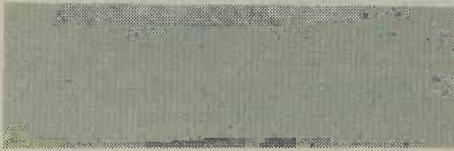

Natural reverberation of sound occurs in any room to some degree, but in rooms of normal domestic proportions and fitted with modern furnishings the reverberation time is usually only a small fraction of a second and is barely noticeable. Reverberation is caused by sounds being reflected around a room before they become attenuated to an inaudible level. Large halls usually have quite lengthy reverberation times, these often being as long as several seconds. When certain types of music are produced this reverberation results in a very rich sound.

There are a number of ways in which artificial reverberation can be added to an electrical audio signal in order to give a "big hall" sound to home produced music and recordings. One of the most simple, inexpensive and popular methods is to use a system based on a spring-line reverberation unit. Such a unit has input and output transducers with one or more springs under low tension between them. An electrical signal applied to the input transducer

produces an acoustical signal at one end of the springs, which then travels relatively slowly down the springs until it reaches the output transducer, whereupon it is re-converted to an electrical signal. The acoustical signal is not entirely absorbed by the output transducer and it is reflected back to the input end of the springs where it undergoes a further reflection. This process is repeated a number of times until the initial signal dies away to an insignificant level, and the effect is analogous with the reverberation of sounds in a large hall. The signal from the output transducer is mixed with the original signal to give the required amount of reverberation.

The reverberation unit described in this article employs a commercially manufactured spring-line unit and the only active component used is an integrated circuit. The unit is powered by a PP6 size 9 volt battery and is intended to operate with an input signal level of between 100mV and 1 volt r.m.s., although it can still be used effectively with signals somewhat outside these levels.



The completed reverberation unit is housed in an attractive ready-made metal case

ation Unit

Reverberation amplitude control

option for ation only

THE CIRCUIT

The complete circuit of the reverberation unit is given in Fig. 1. In this the integrated circuit is an LM389 which contains a small Class B audio power amplifier, with an output at pin 1, and three separate transistors. These are TR1 to TR3 and the numbers alongside them in the diagram are the i.c. pin numbers. The power amplifier section is used to drive the input transducer in the spring-line unit. This transducer requires a fairly strong signal as losses in the springs are high and a low input signal would produce a poor signal-to-noise ratio as well as an inadequate reverberation effect.

The inverting input of the amplifier, at pin 5, is connected to the negative rail, and the input signal is applied, via C2 and volume control VR1, to the non-inverting input at pin 16. There is no polarising

voltage for C2, but this capacitor still functions satisfactorily as a d.c. blocking component. C4 decouples the supply to an internal pre-amplifier inside the i.c. and prevents possible instability due to feedback along the supply rails. The amplifier output is coupled to the spring-line input transducer through R1 and C5. R1 is included to ensure that the amplifier cannot be driven to a level where current consumption is excessive.

The spring-line output transducer couples through C6 to the base of TR1 which, due to its unbypassed emitter resistor, has a voltage gain of about 12 times. The signal at its collector is passed via C7 and R5 to the base of TR2. Also coupled to this base, via C3, S2 and R6, is the original input signal. R6 has the same value as R5 and they provide a simple mixing circuit in which the original signal and the reverberation are


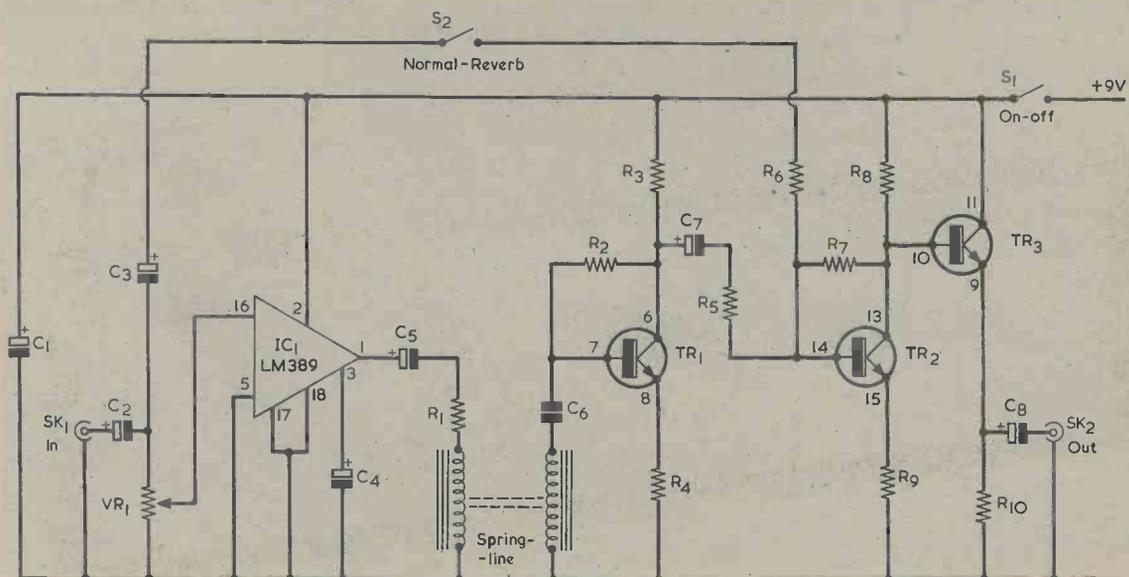


Fig. 1. The circuit of the reverberation unit. The power amplifier and the three transistors are all contained in a single i.c.

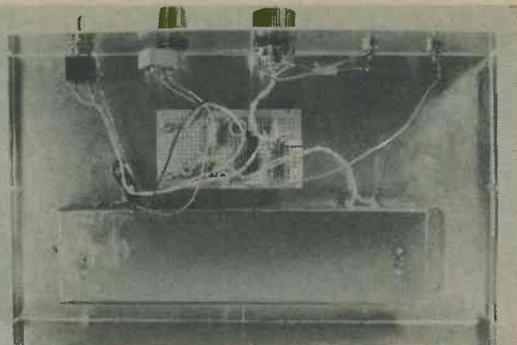The spring-line unit is mounted near the rear of the case. The Veroboard panel lies between the spring-line unit and the front panel components



mixed together. TR2 offers a small amount of gain and a high input impedance for the mixing circuit, and its output couples to the emitter follower, TR3. This last transistor gives the unit a low output impedance.


A wide range of control is provided by VR1 and S2. With S2 closed the amount of added reverberation is varied by VR1. With S2 open the original signal is switched out and only the reverberation signal is passed to the output of the unit.

S1 is the on-off switch and C1 the main supply bypass capacitor. The quiescent current consumption from the 9 volt battery is typically about 9 to 10mA, but the consumption rises to about two or three times this level when IC1 is driven hard.


COMPONENTS

The spring-line unit is available from Maplin Electronic Supplies, and is described in their catalogue as a "short spring-line unit". The LM 389 i.c. is also available from this source. The case used for the prototype unit was, again, obtained from Maplin Electronic Supplies. This is an aluminium case, type TP5, having a wood-grain finish on its cover and dimensions of approximately 279 by 159 by 76mm.

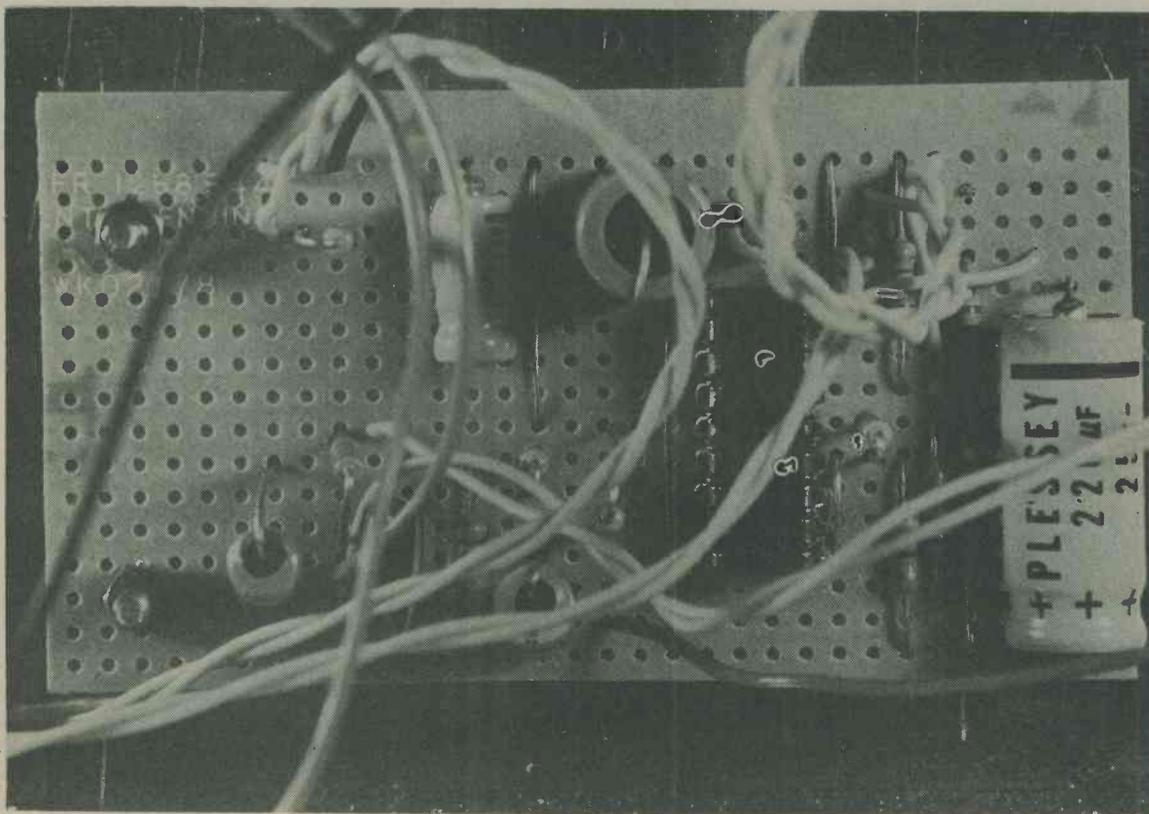The electrolytic capacitors are all specified as having working voltages of 10 volts. In practice it may be found very difficult to obtain $1\mu\text{F}$ capacitors with a working voltage as low as this and it will be perfectly in order to use $1\mu\text{F}$ components for C3 and C7 which



Close-up view of the Veroboard module

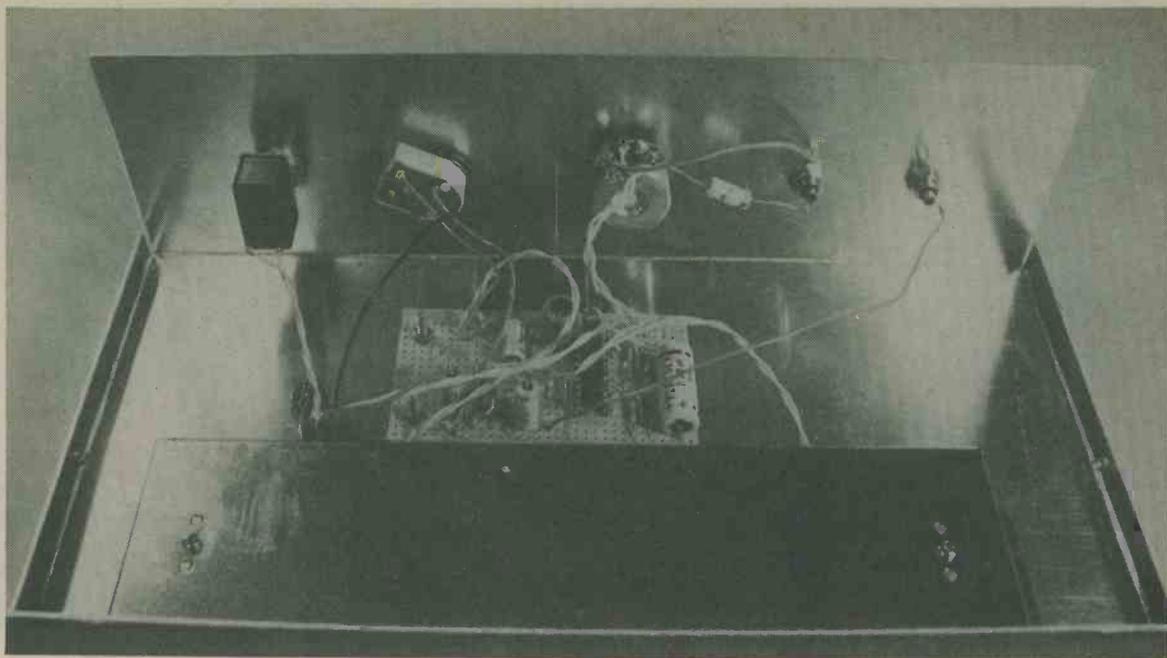

Rear view, illustrating the wiring to the components on the front panel

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated)

R1 33 Ω
 R2 1.2M Ω 10%
 R3 4.7k Ω
 R4 390 Ω
 R5 56k Ω
 R6 56k Ω
 R7 1.2M Ω 10%
 R8 4.7k Ω
 R9 1.5k Ω
 R10 2.7k Ω
 VR1 10k Ω potentiometer, log

Switches

S1 s.p.s.t. rotary toggle
 S2 s.p.s.t. toggle

Sockets

SK1 phono socket (see text)
 SK2 phono socket (see text)

Semiconductor

IC1 LM389

Capacitors

C1 220 μ F electrolytic, 10V. Wkg.
 C2 10 μ F electrolytic, 10V. Wkg.
 C3 1 μ F electrolytic, 10V. Wkg.
 C4 10 μ F electrolytic, 10V. Wkg.
 C5 100 μ F electrolytic, 10V. Wkg.
 C6 0.1 μ F polyester, type C280
 C7 1 μ F electrolytic, 10V. Wkg.
 C8 10 μ F electrolytic, 10V. Wkg.

Miscellaneous

Spring-line unit (see text)
 Metal case (see text)
 9-volt battery type PP6 (see text)
 Battery connector
 2 control knobs
 Veroboard, 0.1in. matrix
 Nuts, bolts, wire, etc.

have working voltages as high as 100 volts. Similarly, the 10 μ F capacitors can have working voltages up to some 25 volts.

CONSTRUCTION

The photographs show the general layout of the unit. From left to right on the front panel are the output socket, VR1, S1 and S2. The author used phono sockets for input and output, but alternative types can be used if these are more convenient. The

spring-line unit is mounted on the base panel of the case, well towards the rear and with the input and output terminals facing forwards so that they are readily accessible. The unit can be used as a template for marking out the two mounting holes required in the base panel, and it is secured by means of M3 bolts and nuts.

Situated between the spring-line unit and the front panel components is the Veroboard module, the component and copper sides of which are shown in



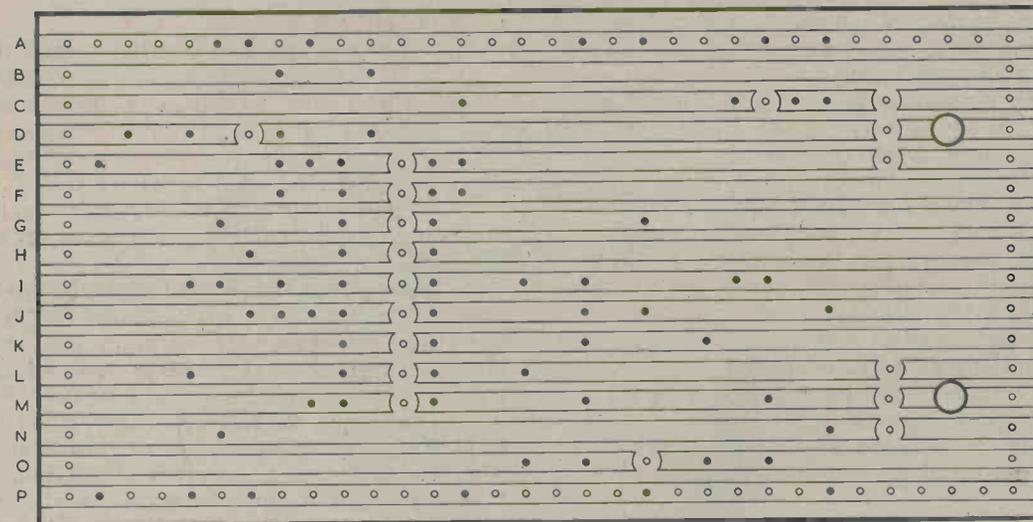
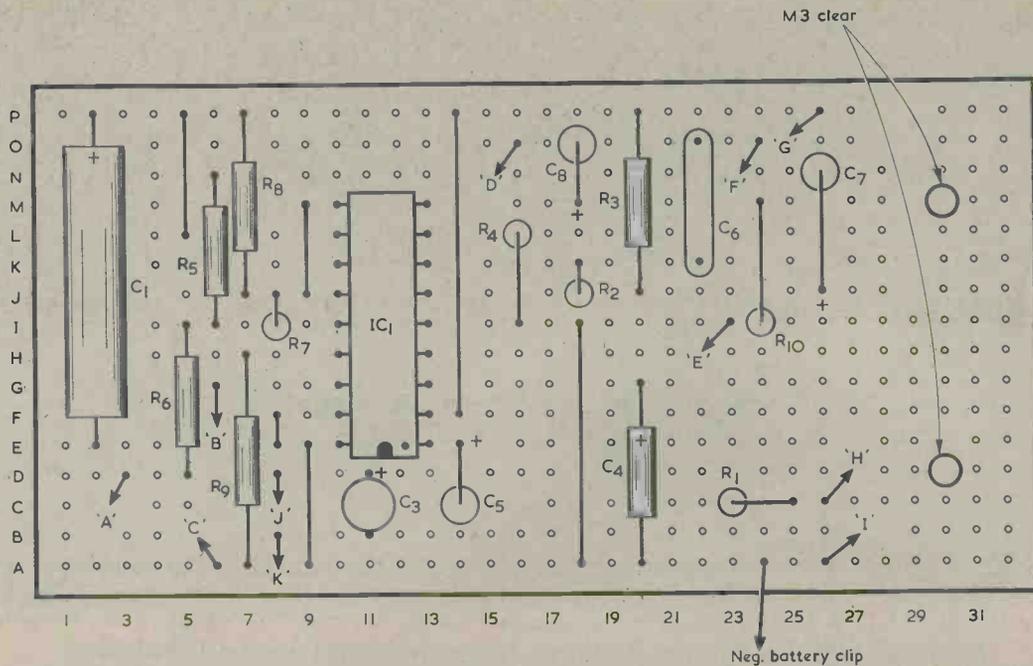


Fig. 2. Nearly all the small components are assembled on a Veroboard of 0.1in. matrix. Component positioning and layout are shown here

Fig. 3. Connections to the front panel components and to the spring-unit

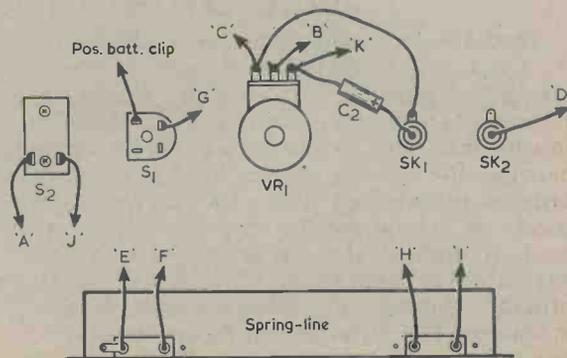

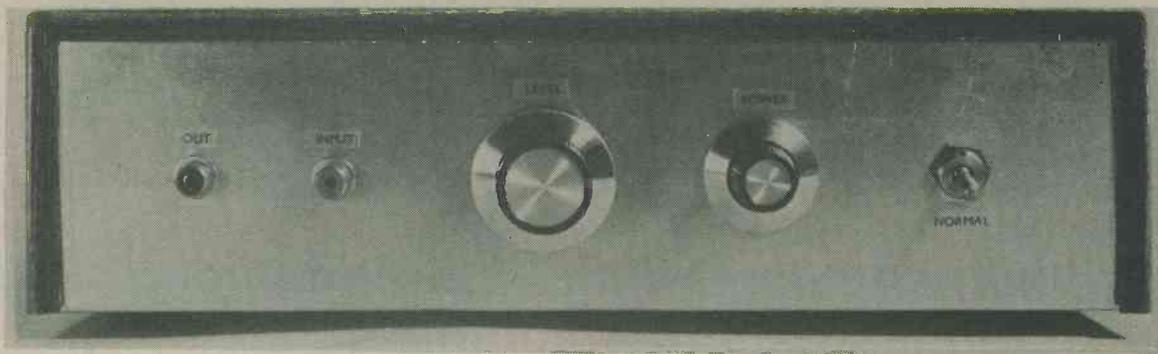

On the front panel, from left to right, are SK2, SK1, VR1, S1 and S2

Fig. 2. The Veroboard panel has 16 copper strips by 32 holes and has to be cut down from a larger piece. After filing the sawn edges to give a neat finish, the two mounting holes are drilled and the 18 breaks in the strips are made. The components and the 6 link wires are then soldered in place, taking care to ensure that IC1 and the electrolytic capacitors are fitted to the board right way round.

Flexible p.v.c. covered leads identified in Fig. 2 by the letters "A" to "K", are also soldered to the board. These leads can be longer than will finally be required and they can be cut to the correct length when the free ends are connected later. The board is secured to the base of the case by two M3 nuts and bolts, with spacing washers on the bolts to ensure that the underside of the board is well clear of the metal base panel surface. The board is oriented so that C3 and C5 are nearer the front panel.

The remaining wiring is illustrated in Fig. 3, where connections to the Veroboard are identified by the letters "A" to "K", which correspond with the same letters in Fig. 2. As can be seen, C2 is not mounted on the Veroboard and is positioned between SK1 and VR1.

There is plenty of space for the PP6 battery. Indeed, a larger PP9 type could be used, if desired, and this would probably give lower running costs if the reverberation unit is to be frequently employed

over long periods. With the prototype, a piece of foam plastic was glued to the underside of the case lid and this was quite sufficient to hold the battery in place when the lid was screwed on.

USING THE UNIT

The unit is simply connected between the signal source and the amplifier, employing screened leads. As described here, the unit can only be used with mono signals, but it is of course only necessary to construct two units for stereo, with each unit processing one channel. The voltage gain through the unit is roughly unity and it is therefore unlikely that any problems will occur when it is connected into a system.

As already mentioned, VR1 controls the amount of reverberation which is added to the original signal. Care must be taken when adjusting this component. Unless the input signal level is quite small, the power amplifier in IC1 will be driven to the point where the output becomes clipped well before VR1 is turned fully clockwise. Overdriving the power amplifier is undesirable because it gives distortion, reduced battery life and, in any case, an unrealistic amount of reverberation. VR1 must therefore be adjusted carefully and sensibly to give a good effect, and not simply set at maximum. ■

Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who have become the subject of liquidation or bankruptcy proceedings and who fail to supply goods or refund money. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.


For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

SHORT WAVE NEWS

FOR DX LISTENERS

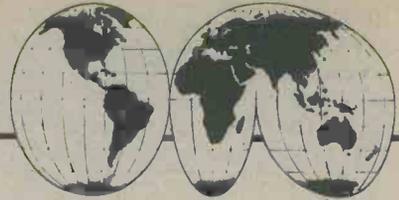

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

● AFGHANISTAN

Kabul on a measured **6231** at 1447, OM announcer, songs and music in the Urdu programme for nearby countries in the Domestic Service 2nd Programme. The Urdu transmission is scheduled from 1330 to 1530.

● NEW ZEALAND

Wellington on **15485** at 0538, OM and YL with a programme about New Zealand internal affairs in an English transmission for the Pacific area. At 0545 local sporting events and results were featured. (OM = Old Man = Male; YL = Young Lady = female).

● PAKISTAN

Islamabad on **21655** at 1040, YL announcer with local music and song programme in the Urdu service for Europe, scheduled from 0715 to 1100 on this particular channel.

● NORWAY

Oslo on **21730** at 1210, YL with station identification then OM and YL alternate with news items in the English programmed 'Norway this Week' radiated to Europe, the Far East, Pacific, South and South East Asia. This particular programme featured on Sundays only.

● AUSTRALIA

VLH9 Lyndhurst on **9680** at 1245, classical piano music, at 1250 OM announcer then choir and a religious programme, all for local consumption.

Melbourne on **11740** at 0745, OM with listeners letters in the English programme to Europe entitled 'Mailbag' (although some Pacific and Asian addresses were mentioned) scheduled from 0700 to 0800 on this channel and in parallel on **21680**, also logged.

Melbourne on **21570** at 0753, musical box version of 'Waltzing Matilda', the tuning and interval signal. At 0758 OM with details of frequencies and times, 0800 time-check pips then into a newscast of world events. Also logged in parallel on **15115**.

● UNITED ARAB EMIRATES

Dubai on **21700** at 0633, OM's and YL's with a drama in Arabic.

● SOUTH AFRICA

RSA (Radio South Africa) Johannesburg on **21535** at 0640, OM's with a newscast in English in the programme 'Looking into Africa', directed to Europe and West Africa from 0600 to 0700. All about African internal affairs - quite instructive.

● INDIA

AIR (All India Radio) Delhi on **3255** at 1549, OM with an English programme all about nuclear power in India. This is the Home Service, scheduled from 1400 to 1600.

AIR Lucknow on **3205** at 1534, YL with a newscast in English, a moderate signal but with some co-channel QRM (interference). This is the B Programme scheduled here from 1130 to 1740. The power is 10kW.

Radio Kashmir on a measured **3277** at 1535, YL with a newscast in English. At 1536, identification as AIR. Good clear signal. Scheduled from 1130 to 1740, the power being 7.5kW.

AIR Kurseong on **3355** at 1542, YL with news comment in English, a good clear signal on a clear channel. The schedule is from 1130 to 1700 and the power is 20kW.

AIR Delhi on **3365** at 1544, same programme as above in parallel. The schedule here is from 0025 to 00230 and from 1330 to 1830. The power is 10kW.

AIR Gahauti on **3375** at 1545, again the same programme as above but a weak signal although clear of QRM. Gahauti is scheduled from 1145 to 1740, the power is 10kW and the programmes are mostly in Assamese but with English newscasts at 1530 and 1730.

● NEPAL

Kathmandu (transmitter at Khumaltar) on **3425** at 1550, OM announcer in Nepalese, YL with local songs. The schedule is from 0020 to 0350 (Sundays to 0450), 0720 to 0950 and from 1150 to 1720. English programmes are radiated from 0220 to 0230 and from 1435 to 1520. The power is 100kW.

● CHINA

Radio Peking on **6430** at 1207, OM with the Mongolian programme in the Minority Language Service, scheduled from 1200 to 1255 on this channel.

Radio Peking on **11000** at 1135, local songs and music in the Tibetan programme in the Minority Language Service, scheduled on this channel in Tibetan from 1100 to 1155.

Radio Peking on **11375** at 1412, YL with the programme in Kazakh, scheduled from 1400 to 1455, in the Minority Language Service. Also logged in parallel on **11040**.

Radio Peking on **11650** at 1423, YL and OM with the English programme directed to South Asia and scheduled from 1400 to 1500 on this frequency.

Wulumqi, Xinjiang, on 5060 at 0055, Chinese music, YL with songs. A good signal when receiver on USB to escape utility QRM LF of channel. This one radiates both local programmes and those from R. Peking in Mongolian. This logging was made during the 2330 to 0555 schedule (February to September from 2400 or, to be correct, 0000 GMT). Wulumqi is also on the air from 1100 to 1625.

Nanning, Guangxi, on 4915 at 2138, YL in Chinese – the usual programming but signal somewhat muffled under co-channel heterodyne. This is Guangxi 1 which is on the air from 2105 to 0005 and from 0840 to 1600 relaying the Peking Domestic Service 1.

Kunming, Yunnan, on 2310 at 2319, YL with a talk in dialect. Yunnan 2A features programmes in Minority languages and is on the air from 2200 to 2400 and from 1225 to 1430.

Kunming, Yunnan, on 2460 at 2321, OM and YL alternate in Chinese. This is Yunnan 1, radiating in Chinese from 2150 to 1620. Can also be heard in parallel on 4760.

● INDONESIA

RRI (Radio Republik Indonesia) Bukittinggi, on a measured 4828 at 1522, OM in Indonesian, short musical interludes local-style. This one is scheduled from 2300 to 0300, from 0500 to 0715 and from 0930 to 1600. The power is 1kW and is listed on 4827.

RRI Yogyakarta on 5046 at 1536, slow rhythmic local music between acts of a drama, much clanging of cymbals. Good signal when tuned on a 1.2kHz bandwidth. The schedule is from 0100 to 0300, from 0455 to 0800 and from 0955 to 1700 and the power is 5kW. Yogyakarta is in Java (Indonesian = Jawa).

RRI Padang on a measured 4002 at 1542, 'When the Saints go Marching In' in local style! OM announcer, fair signal on a clear channel at this time. The schedule is from 2230 to 0100 and from 1000 to 1600, closing time variable. The power is 10kW and Padang is in Sumatra.

RRI Bukittinggi on 3232 at 1546, OM in Indonesian, religious chants at 1552. A poor signal but a clear channel. The schedule is from 1100 to 1600 (Saturdays until 1700); the power is 10kW and Bukittinggi is in Sumatra.

● MALAYSIA

Kuala Lumpur on 4845 at 1525, OM and YL with Indian songs and music, a good signal on USB. The schedule here is from 2130 to 0130 and from 0545 to 1530 Monday to Friday; from 2130 to 0330 and from 0545 to 1530 on Saturdays and from 2130 to 1530 continuous on Sundays. The power is 50kW.

● SINGAPORE

Radio Singapore on 5052 at 1534, OM with a newscast in English, both local and world events. All programmes are in English and they are timed from 2230 to 1630, Sundays until 1700. The power is 20kW and may also be heard in parallel on 5010. Experience shows however that it is often possible to hear them on one channel whilst the other is silent.

● BURMA

Rangoon on 5040 at 1539, local style music on records. A fair signal under co-channel hetero. Rangoon is timed from 0930 to 1430 in Burmese and from 1430 to 1600 in English. A piano solo in European style was featured from 1542. The power is 50kW.

● SRI LANKA

Colombo on 4870 at 1605, OM and YL in the Sinhala programme in the Home Service 2. The schedule is from 0000 to 0300 and from 1030 to 1730. The power is 10kW.

● SOCIETY ISLANDS

Papeete, Tahiti, on 15170 at 0517, OM with Polynesian songs, OM announcer in Tahitian. This is the Home Service scheduled from 1600 to 0730 and the power is 20kW. Tahiti is in France Regions 3.

● TAIWAN

Taipei on 9610 at 2130, OM with a newscast of local affairs in the English programme intended for Africa, the Middle East and Europe and scheduled from 2130 to 2230 on this frequency.

● PHILIPPINES

Tinang VOA (Voice of America) on 15410 at 1440, YL in Asian dialect, 'Yankee-Doodle' interval signal at 1500. Signal subject to interference from R. Moscow, co-channel.

Tinang VOA on 9630 at 1350, YL in Khmer to South Asia, scheduled from 1330 to 1400 when into the Burmese programme – at least according to the schedule!

Radio Veritas, Manila, on 11955 at 1517, OM and YL with the programme in Vietnamese to Vietnam, scheduled from 1500 to 1530.

● LESOTHO

Maseru on 4800 at 1744, OM and chorus with African songs and chants, YL announcer. This is the recently installed 50kW transmitter, a gift from the British Government. The schedule is irregularly from 0400 to 2030.

● BRAZIL

Radio Difusora Taubate, Taubate, on 4925 at 0220, YL with songs in Portuguese, OM announcer with announcements and commercials. The schedule is from 0830 to 0300 and the power is just 1kW.

Radio Tabajara, Joao Pessoa, on a measured 4796.8 at 0104, OM with sports commentary in Portuguese, a fair signal on USB to clear hetero. The schedule is from 0730 through to 0400 and the power is 2kW. Listed on 4797 but subject to slight variations at times.

Radio Capixaba, Vitoria, on 4935 at 2150, OM with commentary in Portuguese. The schedule is from 0730 to 0100 (Sundays until 2230 but reported to vary from 2200 to 0200). The power is 1kW.

● VENEZUELA

La Voz de Carabobo, Valencia, on 4780 at 0110, OM with an excited commentary on a local sporting event. The schedule of this one is from 1000 to 0400 and the power is 1kW.




OWIZZEE!!

By

David Arts

How to play cricket in comfort

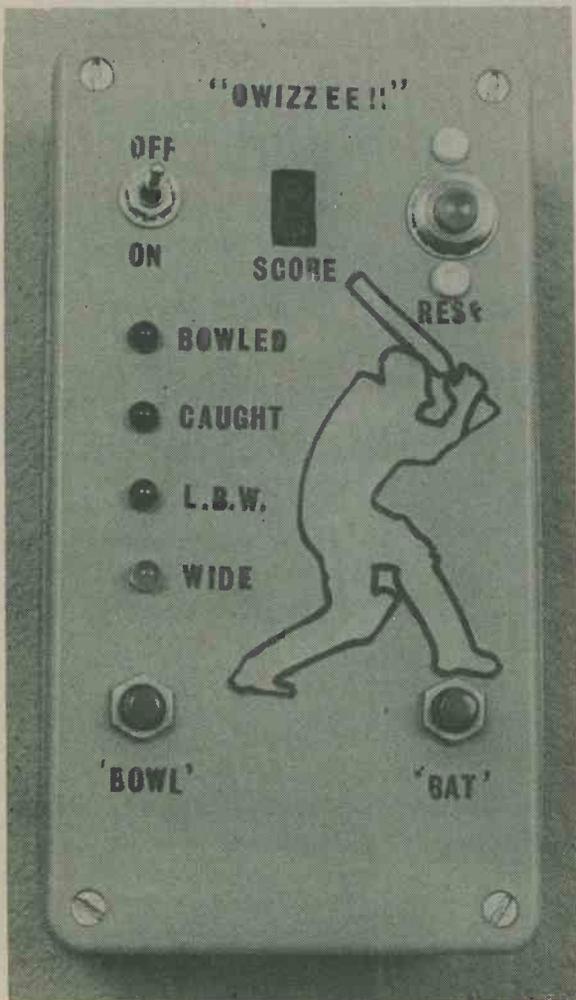

The prototype OWIZZEE! game is housed in a small plastic case with legends on the front panel indicating push-button and l.e.d. functions

OWIZZEE is an electronic game designed to simulate a game of cricket, albeit in a simple manner. The game has provided hours of amusement and can be extremely exciting, especially for the youngsters.

Four integrated circuits are used in the design, these being a 555, two 4017 decade counters and a 4013 type "D" dual flip flop.

CIRCUIT OPERATION

The circuit of the game is shown in Fig. 1. IC1 is the 555 connected as a table multivibrator having a frequency of around 550Hz. When the "Bat" push-button is depressed the 555 output is applied to the clock input of the decade counter, IC2, the ten outputs of which go high in turn with each clock pulse. When the push-button is released the counter stops with one of its outputs high and the remainder all low. No connections are made to four of the outputs and if the counter stops with any of these high the 7-segment display is not illuminated and no runs are scored. The remaining six outputs are fed via steering diodes and current limiting resistors to the display to indicate runs scored. Out of the six chances of making a score there are two chances of a single run, two chances of 2 runs, one chance of a 4 and one chance of a 6. This combination was found to be the most realistic after much experiment.

The bowling circuit operates on similar lines to the batting circuit. On depressing the "Bowl" push-button, clock pulses are fed into IC3, whose outputs similarly go high in turn. However, this time use is also made of the carry-out function on pin 12 which goes positive at the end of each decade count. This is used to clock one of the flip-flops in IC4, which is made to operate as a divide-by-two counter by coupling its not-Q output back to its data input. Each carry-out pulse then changes the state of the Q and not-Q outputs on alternate decades, with each output going high and low in turn.

Four of the IC3 outputs are used in conjunction with the Q and not-Q outputs of IC4 to light one of four l.e.d.'s. LED1 will light if IC3 pin 4 is high and IC4 pin 1 is low, LED2 will light if IC3 pin 5 is high and IC4 pin 1 is low. The other two l.e.d.'s will light when IC4 pin 2 is low. It can be seen that there are 4 chances in 20 of one of the l.e.d.'s lighting up when the "Bat" push-button is depressed and released. Three

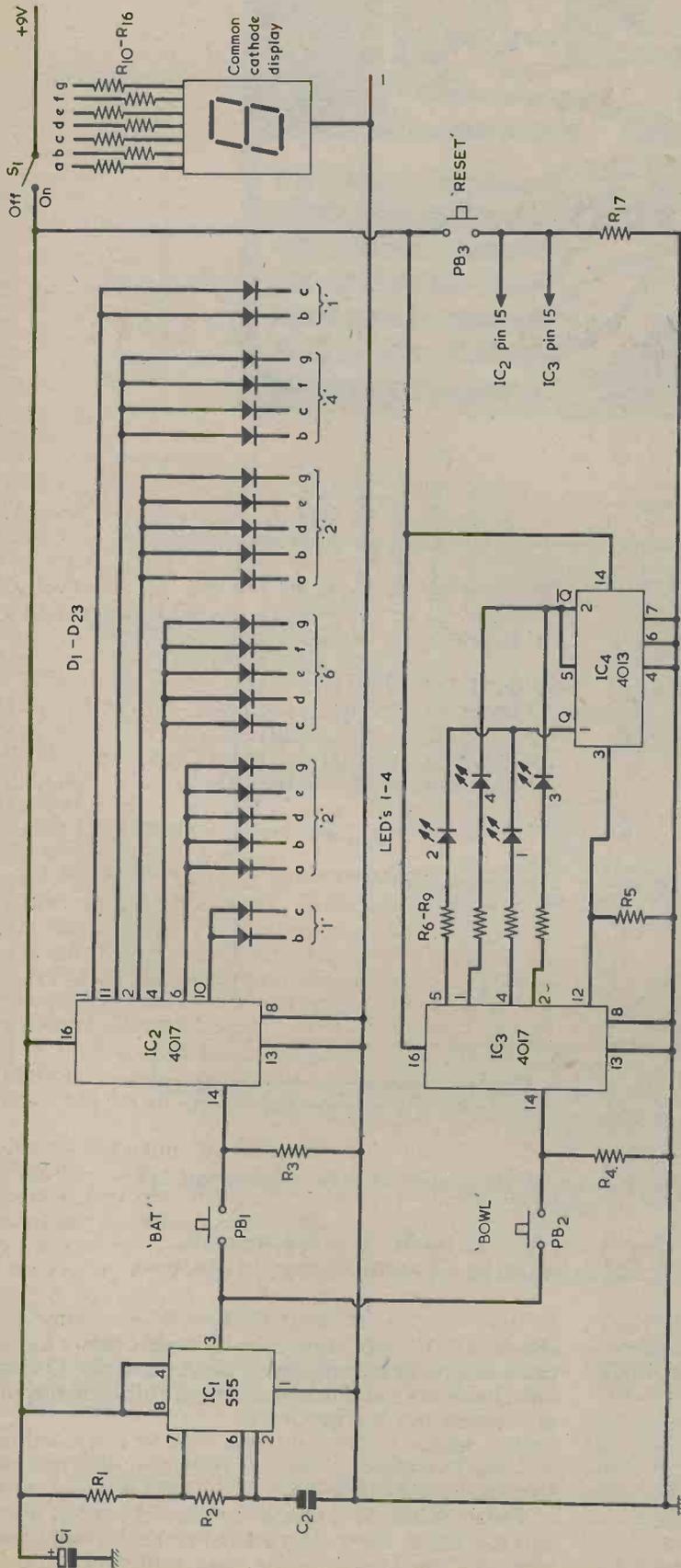


Fig. 1. The circuit of OWIZZEE! Batting scores are indicated by the 7-segment display and wickets, or wickets, by LED1 to LED 4

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5%)

- R1 8.2k Ω
- R2 56k Ω
- R3-R5 22k Ω
- R6-R16 680 Ω
- R17 22k Ω

Capacitors

- C1 100 μ F electrolytic, 10V. Wkg.
- C2 0.022 μ F

Semiconductors

- IC1 555
- IC2 4017
- IC3 4017
- IC4 4013
- D1-D23 1N4148

Light-Emitting Diodes

- LED1 green l.e.d., 0.2in. dia.
- LED2-4 red l.e.d., 0.2in. dia.
- Common cathode 7-segment display (see text)

Switches

- S1 s.p.s.t. miniature toggle
- PB1-PB3 push-button, push to make

Miscellaneous

- Plastic case (see text)
- 9 volt battery type PP3
- Battery connector
- Printed circuit board Veroboard, 0.1in. matrix
- Wire, etc.

Board size
2¹⁵/₁₆ x 4"

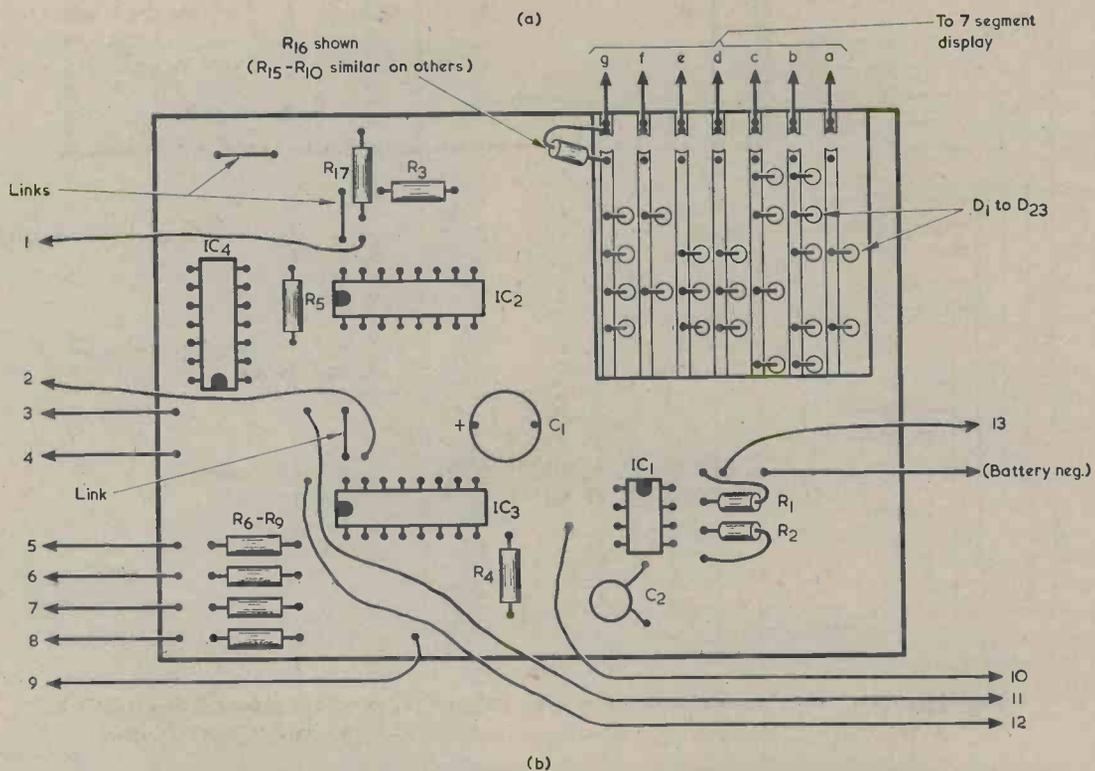
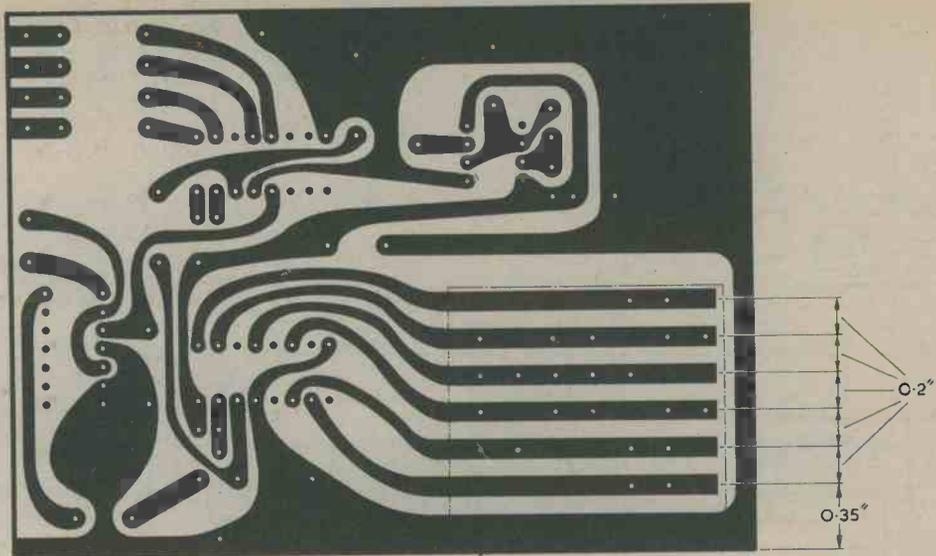


Fig. 2.(a). The copper side of the printed circuit board. This is reproduced full size

(b). The component side of the board. First to be fitted is the specially prepared Veroboard item of (c), which has to be correctly aligned in position

of the l.e.d.'s are labelled to indicate a wicket - "Bowled", "Caught" or "L.B.W". The fourth l.e.d. indicates a "Wide".


The game is provided with a Reset push-button which, when depressed, connects pins 15 of IC2 and IC3 to the positive rail. This returns both i.c.'s to the zero output condition. Since no connections are made to either of the zero output pins, both displays are thus cancelled.

No connections are made to the unused flip-flop in IC4, and this arrangement functions satisfactorily in practice. The current drawn from the 9 volt battery is


about 6mA with the display and the l.e.d.'s extinguished. It rises to about 20mA when the display indicates a score and to approximately 10mA if one of the four l.e.d.'s is alight.

CONSTRUCTION

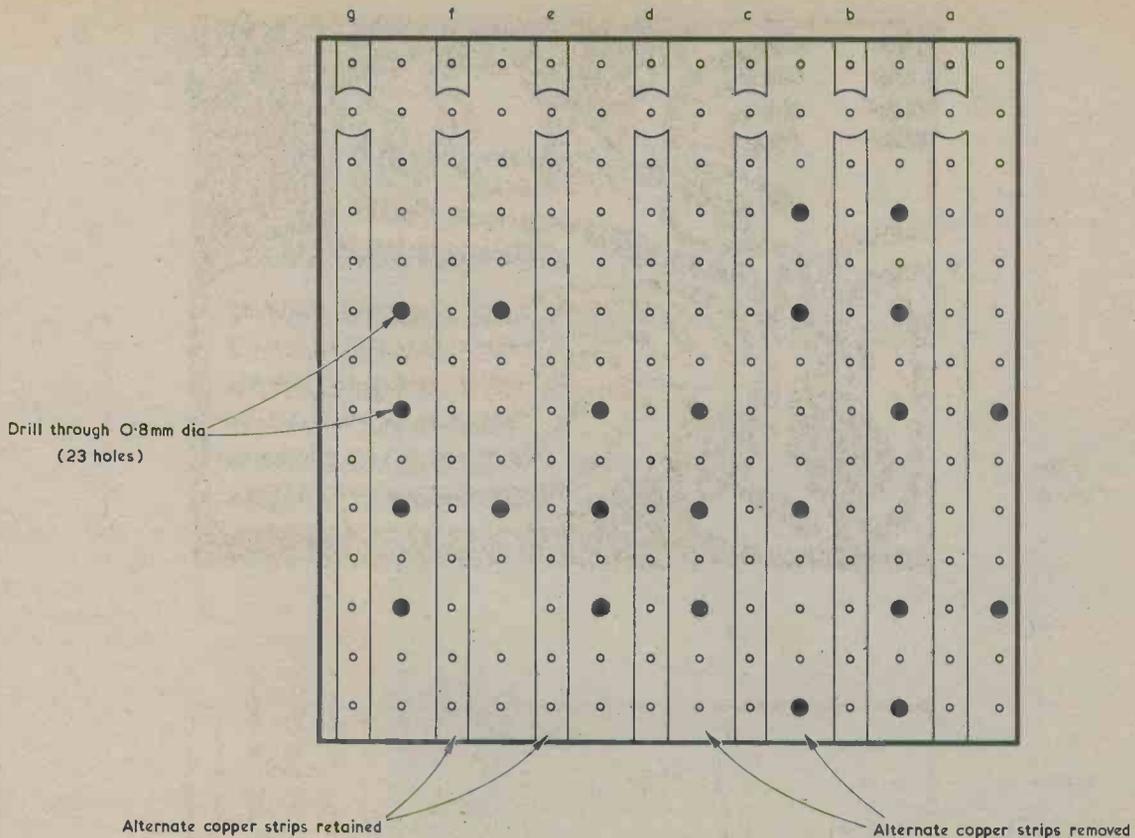The majority of components are assembled on a printed board, the copper side of which is shown full size in Fig. 2 (a). Before any components are mounted, however, it is necessary to fix, on the plain side of the board, the 0.1in. Veroboard item shown in



(c)

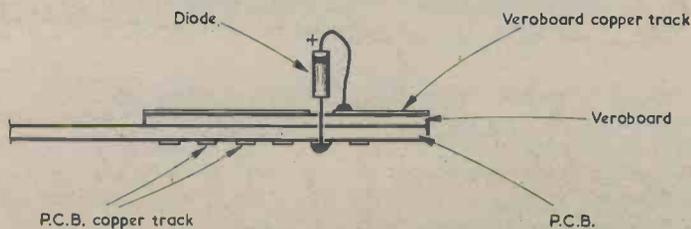

(d)

Fig. 2(c). How the Veroboard item is prepared. The holes are not drilled until after the Veroboard has been secured to the printed circuit board

(d). A side view of the Veroboard and printed circuit board assembly

Fig. 2 (c). Alternate copper strips are removed from the Veroboard, and this process can be carried out quite easily by using a sharp knife and carefully peeling back the copper. The 7 breaks in the copper strips are next made. The board is then glued on the plain side of the printed board, copper strips uppermost, to take up the position shown in Fig. 2 (b). Bostik or a similar adhesive may be used. After the glue has set, the holes illustrated in Fig. 2 (c) are next drilled, these being in the Veroboard areas from which the copper has been removed. If the Veroboard and printed board have been aligned accurately, the holes will pass through

the printed board in the positions shown in Fig. 2 (a). The diodes in the diode matrix can now be carefully soldered in place as illustrated in Fig. 2 (b). Each diode anode connects to the copper print, and each diode cathode connects to a Veroboard copper strip. Also soldered into place are the series resistors R10 to R16. These are soldered to the Veroboard copper strips. Fig. 2 (d) gives a side view of the Veroboard and printed board assembly. Wires from the end of the Veroboard connect to the 7-segment display.

The remaining components on the printed board can now be soldered in position. The prototype game was housed in a plastic case measuring about 6 by

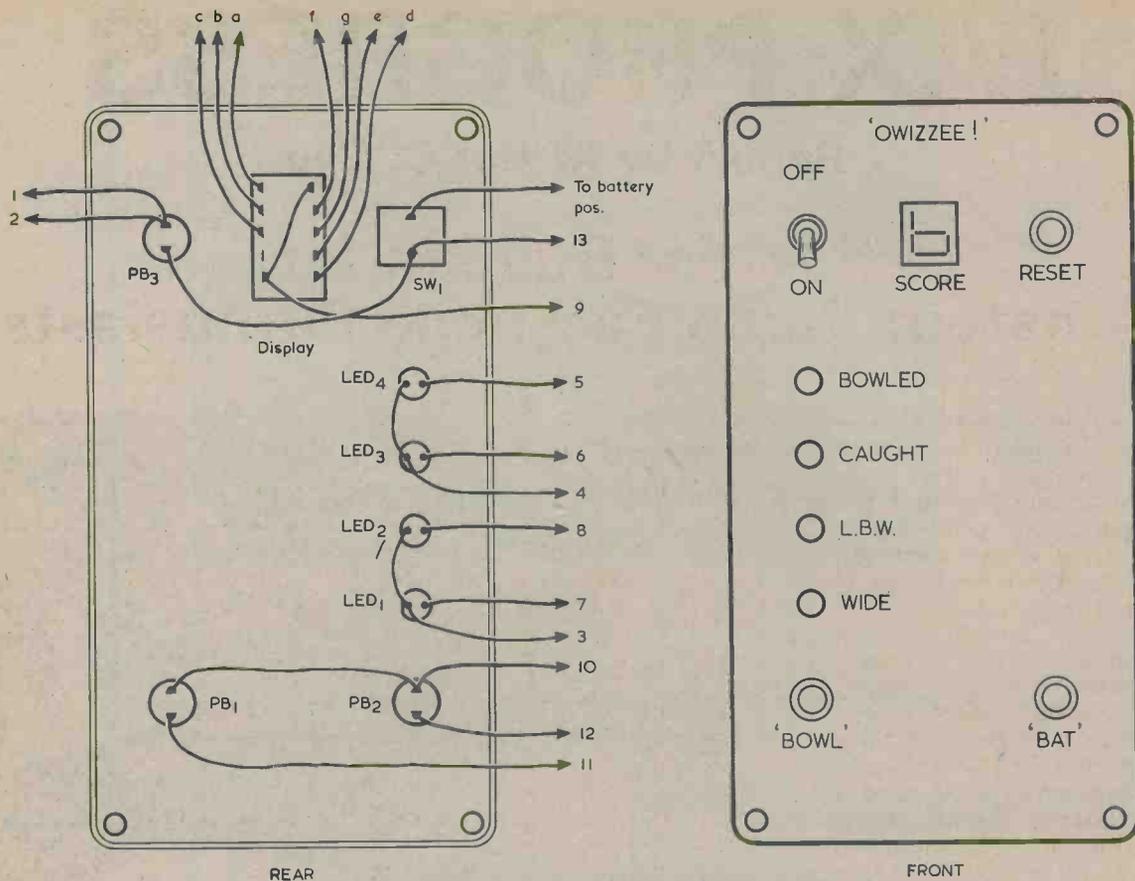


Fig. 3. The wiring and components on the front panel. The numbers from 1 to 13 correspond with those in Fig. 2(b)

3 1/8 in. and about 2 in. deep. Any small plastic case capable of taking the components and battery can of course be used. The printed board was secured to the base of the case with thin flexible leads coupling it to the front panel components, the leads being long enough to allow the front panel to be removed. The front panel is cut out and wired as shown in Fig. 3. The display was glued in place after having first glued a piece of red Cellophane over the aperture from the rear. The display used was an Archer type 276-062, and this should be available at Tandy dealers. An alternative display is the FND500, which is available

from a number of suppliers. The FND500 has the pin layout shown in Fig. 4.

The panel lettering should be carried out before mounting the panel components. In the prototype, the l.e.d.'s were push fits into the holes in the panel, but panel mounting bushes could be used if desired. Obviously, constructors will have their own ideas on layout and presentation.

THE PLAYING RULES

The author has drawn up a set of playing rules as "standard" but any variation can be played as a matter of personal choice. In the standard game each player has five wickets; this makes the game lively and interesting with players having a reasonably short turn-round time. The game can of course be played on more conventional lines with ten wickets per player, but it can then become rather frustrating for the bowler when for a long time he goes without taking a wicket and sees the cheery face of the batsman piling on the runs.

The bowler starts by depressing the "Bowl" push-button and if he fails to get a wicket the batsman presses the "Bat" button. The score, if any, is noted on a pad, and it is best to keep a running score as the game proceeds. The bowler then tries again and play alternates until the bowler takes a wicket or bowls a wide, in which case he bowls again. In the case of a wide, however, the batsman is credited with one run! When the fifth wicket has fallen the bowler takes his turn to bat and tries to beat the score. The game can be played over two innings, if preferred. ■

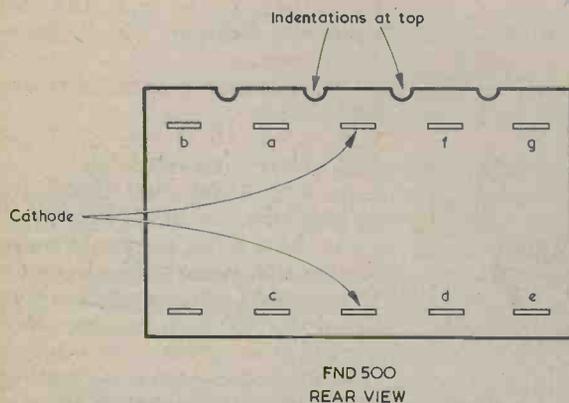


Fig. 4. An alternative display to that used in the prototype is the FND500. This has the pinning shown here

FAX PROGRESS

Report by Arthur C. Gee

Regular Bulletin for Amateur Radio Facsimile Enthusiasts

Facsimile transmission and reception is gradually catching on amongst the more experimentally minded radio amateurs, but progress has been slow since permission was granted recently to use this mode.

One step which may well help to encourage interest, is the establishment by Hans J. Schalk, DJ8BT, of Frankfurt, of a regular FAX Bulletin, transmitted on Saturdays and Sundays on the 80 and 20 metre amateur bands. Hans is reproducing in facsimile form the regular DARC News Bulletin, "DL-Rundspruch", so that those with FAX equipment, or those interested enough in this mode to be contemplating getting suitable equipment, have something to receive regularly, of an amateur radio interest.

The equipment used is a HELL HF 146 FAX Transceiver, which is a relatively modern and transistorised unit. The drum speed however, is a fixed



Hans J. Schalk in his shack.

one of 180 r.p.m., so that, to make it more versatile, Hans built a frequency divider and mixer unit, which now enables him to use all commercial drum speeds, viz., 60, 90, 120,


180 and 240 r.p.m. For his bulletins, a speed of 120 r.p.m. is used, but other drum speeds will be used if requested. The transmission time for one A4 sized page takes about ten minutes and the "DL-Rundspruch", which usually runs to two pages or so, takes about 25 minutes. A CQ and Test Chart transmission is run for ten minutes before the Bulletin transmission.

Transmission schedules are as follows:


Saturdays 1800 hrs GMT on 3605 MHz – F4/800 Hz.

Sundays 1000 hrs GMT on 14105 MHz – F4/800 Hz.

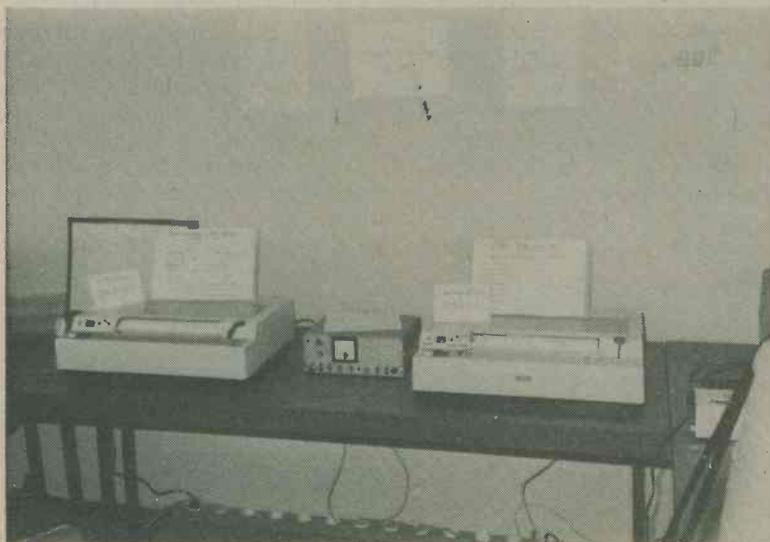As Hans says, now that there is a regular weekly FAX Bulletin this should encourage activity in this mode, as all FAX machine owners will have a weekly opportunity of testing out their equipment. Maybe this new service will give new life to some "long forgotten and dusty" FAX machines. ■



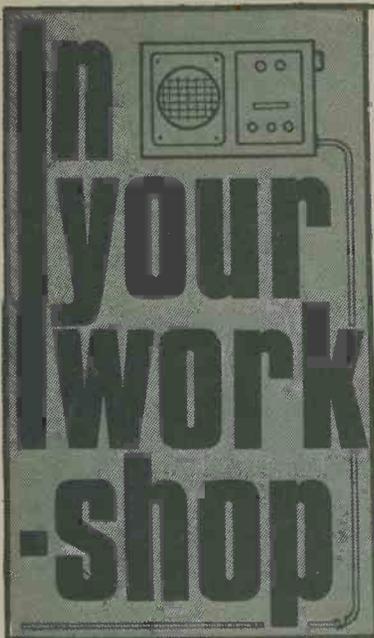The equipment used at a FAX demonstration at "HAM RADIO 80" held at Fridrickshafen/Badensee.



FIXING AN F.M. RADIO

Contentedly, Smithy watched his assistant as, leisurely, Dick brought the small f.m.-a.m. radio over to the bench. Yet another highly successful day could be chalked up in the favour of Dick and Smithy, and there were now at least two hours to go before they officially closed up shop for the day. The "Repaired" rack groaned under the weight of sets made serviceable by the indefatigable efforts of our talented pair. For most of the time they had proceeded along their own separate paths but on several occasions Dick had had to call in the aid of Smithy, who had instituted schemes of fault diagnosis and trouble-shooting which led to the successful location of Dick's snags. After this followed the triumphant installation, with impeccable solder joints on the part of Dick, of the replacement part which was needed to bring the set concerned back to its fully functional level. Dick would be the first to state that, whilst he might not be too hot on theory, he wielded a mean soldering iron.

F.M.-A.M. RADIO

Thus it was that the pair elected to work together on the very last set awaiting repair: the little f.m.-a.m. radio which Dick was now placing on the

surface of Smithy's bench. Dick settled himself comfortably on the stool he had brought over from his own bench and operated the volume control of the radio to switch it on. The sound of a punk rock group filled the Workshop. Dick adjusted the tuning control and was able to receive both Radio 2 and Radio 3. He had patently been tuned to Radio 1 when he first turned on the set and the tuning performance of the radio showed that it was switched to a.m., whereupon it was covering the medium wave band with no access to Radio 4. Dick looked at the back of the set, to find a small 2-way slide switch with its positions marked "AM" and "FM". With a.m. selected the receiver was limited to the medium wave band only, but it showed no signs of covering this band other than with a perfectly acceptable efficiency.

"It's okay on a.m.," Smithy," he announced. "I'll try it on f.m. now."

He moved the slide switch to the "FM" position, pulled out the telescopic aerial and tuned across the band. The set was silent.

"Well there's our snag," pronounced Smithy. "The set isn't working on f.m. I suppose we'd better do the obvious thing first and check battery voltage."

Dick removed the battery

cover, to reveal four HP7 cells. He was able to get his test prods to the end spring contacts for the cells and the meter on Smithy's bench indicated about 5.75 volts with the set switched on at a low volume setting and with either f.m. or a.m. selected.

"We can," said Smithy cheerfully, "take our time over this. The f.m. section in these sets is usually the first to stop working properly when the battery voltage falls, but it shouldn't go completely dead when the battery voltage is only a little below 6 volts. The fact that the same voltage was given with both a.m. and f.m. selected means that the loading on the battery is probably the same on both bands so that, at least, there isn't excessive battery current drawn when f.m. is selected. Get the back off, Dick, and I'll see if I can find the service sheet."

Some minutes later, Smithy returned to his bench with a service manual, to find Dick carefully examining the receiver printed board for obvious visible faults.

"Everything looks all right," stated Dick.

"Fair enough," responded Smithy, looking at the receiver circuit diagram. "This set has got two transistor amplifying stages which are common to both the a.m. intermediate

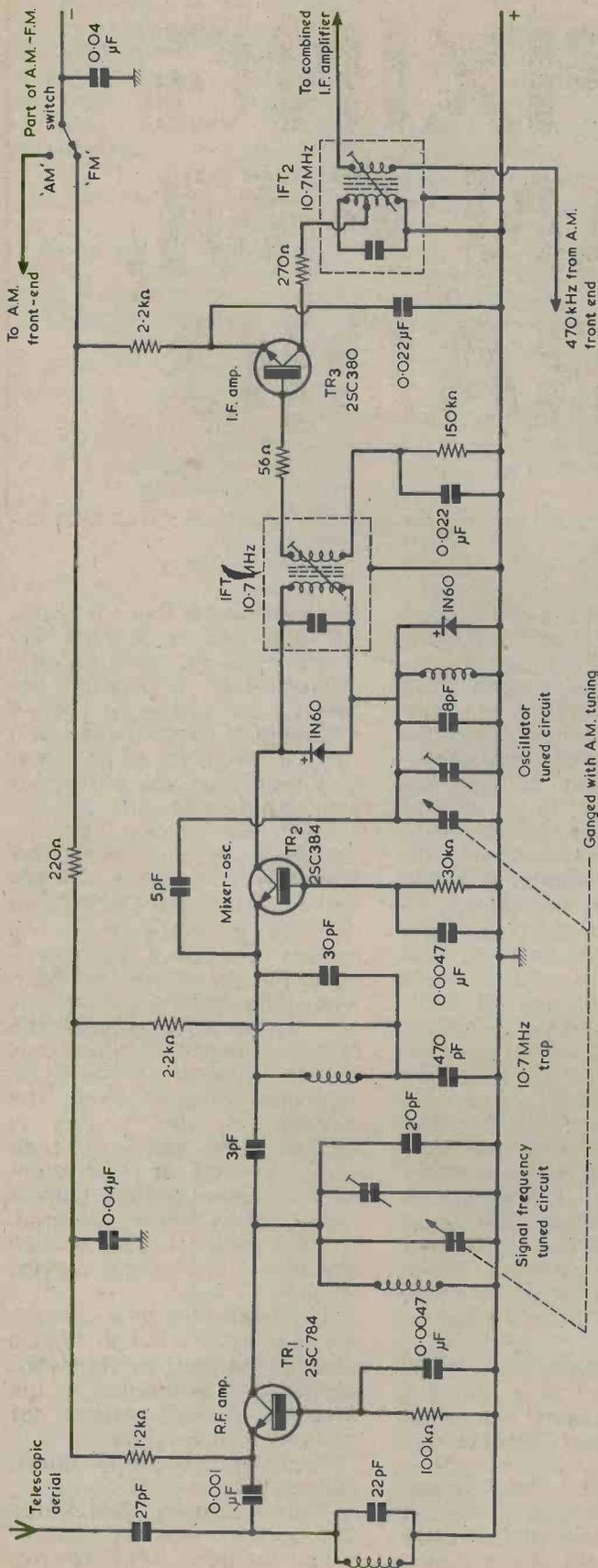


Fig. 1. The circuit of the r.f. amplifier, mixer-oscillator and first 10.7MHz i.f. amplifier in the f.m.-a.m. radio serviced by Dick and Smythy. This represents standard commercial practice and is a slightly simplified version of the circuit employed in the Ferguson portable radio model 3189.

frequency of 470kHz, and the f.m. i.f. of 10.7MHz. We're not in any hurry, so let's take things easy and just assume that, since these two stages are okay on a.m., they should also be okay on f.m. Which means that we might as well turn our attention first to the section of the radio which takes in the f.m. front-end and the f.m. first i.f. transistor."

Smithy pointed to the appropriate section of the receiver circuit. (Fig. 1.)

"Dear, oh dear," sighed Dick. "This is another of those circuits where the positive rail is common to chassis and the negative rail is at the top of the diagram. And we've got transistors with those Japanese type numbers, too."

"Look them up in **Towers**!" "Okeydoke," said Dick, as he stood up, reached to the shelf above Smythy's bench and took down the Workshop copy of **Towers' International Transistor Selector, Up-Date 2**. He turned through the pages and then found the transistor types which were employed in the circuit.

"All three transistors are n.p.n. silicon," he said. "TR1 and TR2 are v.h.f. amplifiers and TR3 is a general purpose type."

"Very good," said Smythy, "Well, the i.f. transistor, TR3, is obviously connected as a common emitter amplifier."

Dick looked at the circuit dubiously.

"If you say so." "I do say so." Smythy pulled his note-pad towards him and picked up a ball-point pen. "If I redraw the circuit with the positive rail at the top, you can see that it's a very straightforward common emitter stage."

Smythy busied himself with his pen, then showed the circuit he had sketched out to Dick. (Fig. 2.)

"That 0.022μF emitter bypass capacitor," objected Dick, "doesn't go to the negative rail, it goes to the positive rail."

"So what? Both rails are coupled together by a 0.04μF capacitor at the arm of the a.m.-f.m. switch, so that the emitter bypass capacitor can be returned to either."

"What about the 56Ω resistor

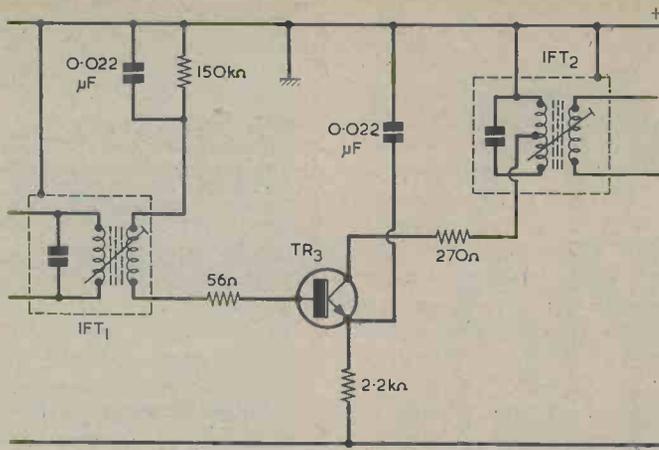


Fig. 2. TR3 is employed in the common emitter mode, as can be clearly seen if the circuit around it is redrawn with the positive supply rail at the top.

in the base circuit and the 270Ω resistor in the collector circuit?"

"You get these in f.m. i.f. stages," explained Smithy. "They help to reduce the effects of impulsive interference."

COMMON BASE AMPLIFIER

"Humph," grunted Dick. He turned his attention to the first stage in the front end. "Hey, what about TR1? Don't tell me that that's in a common emitter circuit as well."

"No, it isn't. It's in a common base circuit. Let me show you

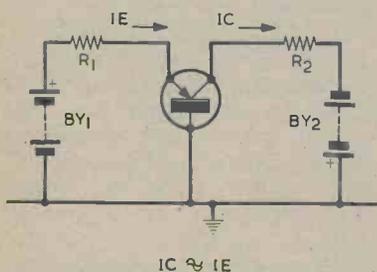


Fig. 3. The basic common base transistor configuration. Input and output signals may be applied to and obtained from the emitter and collector respectively via coupling capacitors. Current is assumed to flow from positive to negative. With an n.p.n. transistor, battery polarities and current directions are reversed.

the basic common base configuration."

Again, Smithy's pen passed quickly over the top sheet of his note-pad. (Fig. 3.)

"This is a common base amplifier," he went on. "I've used a p.n.p. transistor instead of an n.p.n. one because this makes it easier to visualise the currents which flow. The base is connected to a common rail which we can conveniently refer to as 'earth'. Battery BY1 and resistor R1 cause a forward current to flow in the emitter-base junction of the transistor. A collector current flows in resistor R2, which is supplied by battery BY2. As you can see, I've put in two little arrows and called the currents IE and IC."

"What's the relationship between these two currents?"

"They're virtually the same."

"The same?" repeated Dick incredulously. "Come on Smithy, you're having me on!"

"No, I'm not," replied Smithy. "Provided R2 is not too high in value, the current which flows in it is almost exactly the same as the current which flows in R1."

"But that can't be true," protested Dick. "You've got two separate circuits here. One circuit is given with BY1 and R1, and the other circuit is given with BY2 and R2. Are you telling me that if R1 has a value which causes 1mA to flow in it, there will be 1mA flowing in R2?"

"I am," said Smithy. "Or at least there will be very nearly 1mA in R2. If I reduced the value of R1 so that it passed 5mA, there'd be almost exactly 5mA in R2 as well. Similarly, if I increased R1 so that only 0.2mA flowed in it, then the current in R2 would also be virtually 0.2mA."

"Whatever," queried Dick "the value of R2?"

"Regardless of the value of R2," confirmed Smithy, "provided that it's low enough to allow the collector current to pass."

"Would that 0.2mA flow, even if R2 had as low a value as, say, 10Ω?"

"It would flow," Smithy assured him gravely, "if R2 were a short-circuit!"

Dick gazed at Smithy's circuit.

"I don't believe it!"

Smithy glanced at Dick's perplexed face.

"I suppose it does take a little imagination to see the effect," he said. "Let me see if I can show it you in a way you'll understand more easily."

He scratched his head thoughtfully, then picked up his pen as a thought occurred to him.

"Let me re-draw that common base circuit," he said slowly, "so that battery BY1 is above battery BY2."

He drew out a new circuit diagram and then showed it to Dick. (Fig. 4(a).)

"Does that," he asked, "make it clearer?"

Dick scowled down at the re-arrangement of the circuit symbols.

"I'm afraid not, Smithy. All you've done is move the batteries and resistors about a bit. I'm still baffled!"

"All right," said Smithy equably, "I'll now make another change. I'll keep BY1 and BY2 in series to give the same overall supply voltage that we had before. But I won't connect the junction of the two batteries to the transistor base. Instead, I'll feed that base by the steady voltage dropped across a zener diode having the same voltage as BY1. Here's the idea."

Smithy sketched out his new circuit then looked expectantly at his assistant. (Fig. 4(b).)

"That," said Dick frowning,

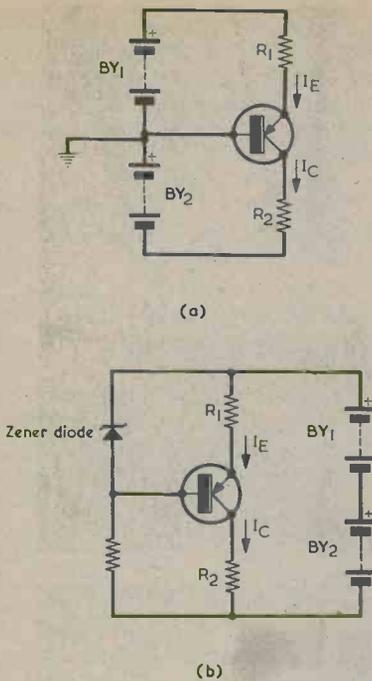


Fig. 4(a). Redrawing the circuit of Fig. 3 with battery BY1 above BY2. (b). Here, the connection between the batteries and the transistor base is removed and a zener diode added. The voltage across the diode is the same as that previously provided by BY1.

"looks very familiar to me."

"Think about it."

"Why, of course," exclaimed Dick. "It's the circuit of a constant current generator! The transistor base is held at a fixed potential by the zener diode, and the voltage across the diode, minus about 0.6 volt dropped in the transistor base-emitter junction, appears across R1. Since the voltage across R1 is fixed, the current which flows in it must also be fixed. The collector current is the same as the emitter current and so a constant current is given in R2 regardless of its value."

"Provided," stated Smithy, "that R2 has a value which is not too high to allow the current to flow. You should also have mentioned that the current in R2 is not precisely the same as that in R1, because the current in R1 is the collector current plus the very small base current which allows the collector current to flow. If the

transistor has a high current gain, though, the emitter and collector currents are nearly identical."

"I've got all that," said Dick quickly. "Let's go back to the circuit you drew just before. That's the first one where you put BY1 over BY2. I can see now how this gives the same sort of constant current performance as the circuit with the zener diode. The current which flows in R2 must be the same current, less the much smaller base current, as that which flows in R1. Gosh, it takes a bit of thinking about, though!"

"What you have to remember," said Smithy, "is that, with a common base amplifier stage, the actual supply voltage is given by BY1 and BY2 in series. The current which BY1 supplies is then virtually the same as that which BY2 supplies. We tend to think of bias current as being much smaller than collector current because we're so used to the common emitter circuit. But in the common base circuit the bias current to the emitter, provided by BY1 in our example, is actually a little higher than the collector current."

INPUT TRANSISTOR

"That's really cleared up this common base business for me," said Dick enthusiastically. "Wait a minute, though!"

"What's up now?"

"You said that the first transistor in this f.m. front-end was connected as a common base amplifier. But there's no BY1 and BY2 in the receiver circuit - there are just negative and positive supply rails."

Smithy busied himself once more with his pen. After some moments he showed a further circuit to his assistant. (Fig. 5.)

"Here's that r.f. amplifier transistor," he said. "An input from the aerial goes to its emitter, and an output from the collector goes to the signal frequency tuned circuit. A current is applied to the base via the 100kΩ resistor, with the result that virtually the same current flows through the 1.2kΩ emitter resistor and the coil in the collector tuned circuit. The important bit here is that the base is bypassed to

ELECTRONIC TUTOR KITS

Learn electronics the effective way by experiments. Each kit contains an illustrated handbook, which takes you step by step through the fundamentals of electronics, plus all the components needed. No soldering. Safe and instructive for even the young enthusiast. Kit 1, £5.85. Kit 2, £5.95. Kit 3, £6.15. SAE for leaflets on this and other RXG products.

RXG ELECTRONICS LTD.

15 Walnut Tree Crescent,

Sawbridgeworth, Herts, CM21 9EB.

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply:

Radio & Electronics Constructor Data Books Panel Signs Transfers

Also a postal service

PEATS

the world of electronics

25 Parnell Street, Dublin 1. Tel 749972

GAREX

RESISTOR KITS new extended range at old prices:

E12 series 10Ω to 1M, 61 values, 5% carbon film, 1/4W or 1/2W general purpose rating.

Starter pack 5 each value (305) £3.10

Standard pack 10 each (610) £5.55

Mixed pack, 5 each 1/4W plus 1/2W (610) £5.55

Giant pack 25 each (1525) £13.60

NICAD RECHARGEABLES physically as zinc carbon: AA(U7) £1.30, C(U11) £3.35; PP3 £5.55. Any 5 plus: less 10%; any 10 plus: less 20%

VHF FM MONITOR RECEIVERS

HF 12 POCKET SIZE 12 channel xtal controlled. 4MHz bandwidth in range 130-174MHz. With nicad & charger. £57.95 Xtals extra, see below.

SOUNDAIR 008 PORTABLE SCANNER 8 channel xtal controlled. With nicad & charger, £59 Xtals extra.

SR-9 top selling monitor: 2m FM with 144-146MHz full coverage VFO, plus 11 xtal controlled channels, ideal for fixed or mobile listening. 12V DC operation. £47.50

MARINE BAND version, 156-162MHz, same spec & price.

CRYSTALS FOR HF-12, NR-56, SR-9, SOUNDAIR 008, TM56B: all 2m channels in stock from 0(145.0) to 32(145.8) at £2.46 (plus 15p post). Over 40 popular marine channels at £2.85 (plus 15p post) Sae list.

AMPLIFIER MODULE new, fully assembled 6W IC unit, 12v DC. Low impedance (4-8:) input & output for extrn. speaker amplification, with circuit £2.75

CO-AXIAL CONNECTORS & ADAPTORS see list

PL259 UHF plug plus reducer 75p; 5 plus 67p

SO239 UHF socket panel mtd. 60p; 5 plus: 50p

We stock VHF & UHF mobile aeriels.

Access - Barclaycard

PRICES INCLUDE UK POST & VAT. CALLERS BY APPOINTMENT

GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH.

TRING, HERTS HP23 4LS

Cheddington (STD 0296) 668684

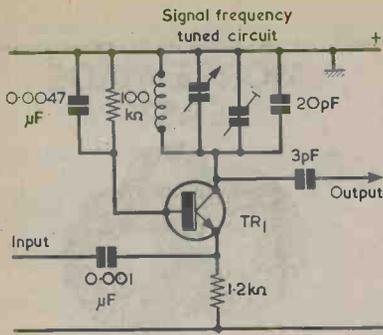


Fig. 5. TR1 in the receiver circuit functions as a common base amplifier at r.f. because of the 0.0047 μF capacitor coupling its base to chassis.

chassis via a 0.0047 μF capacitor. This means that so far as r.f. is concerned, that base is as common with chassis as it would be if there was a direct connection. Got it?"

"Blimey, yes. But there's something else I've thought of!"

"Go on."

"If the standing emitter and collector currents are virtually equal, an r.f. current in the base circuit will produce the same r.f. current in the collector circuit. What's the use of a transistor which provides no current gain?"

"The r.f. current gain the transistor provides," said Smyth, "is, as you rightly point out, just about unity. In fact, it's very slightly less than unity. On the other hand, the input impedance at the transistor emitter is low and the output impedance at the collector is very high. So, whilst the transistor may not offer any current gain it can, given the right components in the emitter and collector circuits, provide a considerable degree of voltage gain. As you can see, the collector of the transistor goes straight into the whole signal frequency tuned circuit. It doesn't go into a tap in the coil as would normally occur with a common emitter amplifier. There's another thing, too. When a transistor is connected in common base it maintains its amplification up to frequencies which are very

much higher than would be given when it is in common emitter. That's why common base transistors are so frequently found in the r.f. amplifier and mixer-oscillator stages of f.m. receiver front-ends."

Dick turned his attention to the receiver service manual.

"That mixer-oscillator transistor has to be in common base, too," he said. "Its base is bypassed to chassis by another 0.0047 μF capacitor."

"That's right," confirmed Smyth. "Now, another feature of transistors in the common base configuration is that, voltage-wise, the emitter and collector are in phase. If the emitter is taken negative of the base, the effect on collector current is the same as if, with a common emitter transistor, the base is taken positive of the emitter. In other words, taking the emitter of a common base transistor negative causes the collector to go negative, too. In the same way, taking the emitter positive causes the collector to go positive as well. So far as the mixer-oscillator transistor is concerned this means that a simple capacitive coupling from the collector back to the emitter is all that is required to make it oscillate. If you look at the service manual circuit again you'll see that the mixer-oscillator collector connects through the primary of the first 10.7MHz i.f. transformer to the top end of the oscillator tuned circuit. And the top end of that tuned circuit couples back to the emitter through a 5pF capacitor."

"Well," grinned Dick, "you couldn't have things much simpler than that. There's a 1N60 diode across the i.f. transformer primary. What's that for?"

"It's another component to reduce the effects of impulsive interference," replied Smyth. "The 1N60 is a germanium diode which is primarily intended as a video detector. In this circuit it turns on and damps the i.f. tuned circuit if there are any interference signal spikes. It also prevents excessively high signal levels getting into the i.f. amplifier."

"There's another 1N60 diode across the oscillator tuned circuit."

"That one does much the same sort of thing. It limits oscillator frequency amplitude to about the same level over the tuning range. Any more questions?"

"Nope."

"Good," pronounced Smyth. "Let's get down to some servicing then."

"You said earlier," commented Dick, "that the common i.f. amplifier stages should be all right."

"I only said that we'd start off by assuming they're all right. It's quite possible that the snag is in that common amplifier. But, as we're taking it easy, let's keep on playing hunches. If we continue with the assumption that it's the f.m. front-end which is at fault then a few unhurried voltage checks won't do any harm at all. Let's first check that the f.m.-a.m. switch is doing its job properly and is allowing power to get to the front-end. Perhaps you could keep an eye on the needle of my testmeter while I see what voltages are available."

Smyth turned to the printed circuit layout diagram in the service manual, and noted that his trusty analogue testmeter was switched to 0-10 volts d.c., as it had been when Dick used it to measure the battery voltage. He turned on the receiver, ensured that it was switched to f.m. and rested his positive test prod on the first i.f. transformer can to obtain a positive supply connection. After some scrutiny he applied the negative prod to the negative supply for the first transistor in the front-end. (Fig. 6(a).)

"Any reading?"

"Are you checking the supply rail voltage?"

"I am."

"Well," said Dick, "you're getting a reading of about 5 volts. Shouldn't it be the same as the battery voltage we measured earlier?"

"It will be lower than that," said Smyth. "There are several series decoupling resistors in the negative rail between the negative battery terminal and the point I'm checking now. I'll check the emitter of the first transistor next. Now, where is that on the board? Ah, here it is!"

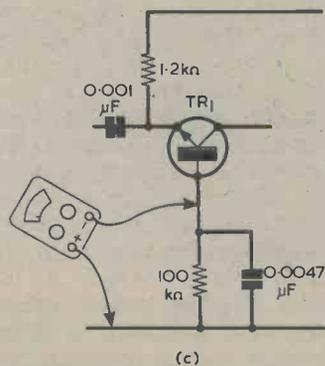
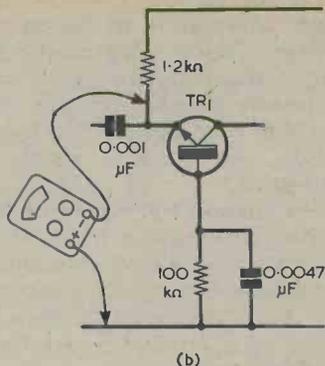
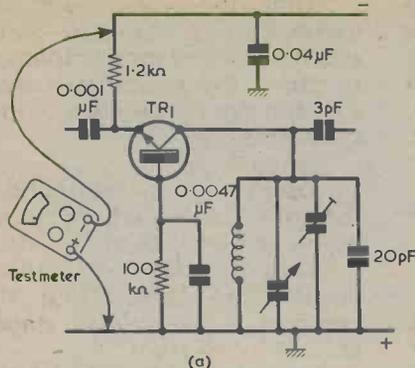


Fig. 6(a). Smithy first checked to ensure that a supply voltage was being passed to the f.m. front-end.

(b). He next measured the voltage at TR1 emitter.

(c). Finally, he applied his testmeter across the 100kΩ base resistor, with rather surprising results.

Smithy applied his test prod to the transistor emitter. (Fig. 6(b).)

"The meter's giving pretty well the same reading," stated Dick. "Just about 5 volts."

Smithy raised an eyebrow.

"Is it now?" he remarked.

"Don't tell me that I'm already on to something. I'll check the base of that first transistor next. Here we go!" (Fig. 6(c).)

Smithy placed the test prod end against the transistor base. There was a noticeable crackle from the receiver loudspeaker which then, to Dick's utter amazement, proceeded to give a distorted musical output.

"Blimey, Smithy, what did you do there?"

But Smithy was not yet ready to explain the phenomenon.

"See if you can tune in that station properly."

As Smithy kept the test prods in place, Dick adjusted the receiver tuning. This soon allowed the received signal to be heard clearly. Smithy removed his negative test prod and the music ceased. He re-applied the prod and the music once more became audible.

"Come on, Smithy! What the heck is happening there?"


"I've bridged the 100kΩ base resistor for the first transistor with the resistance of my

testmeter," said Smithy cheerfully. "My testmeter's got a resistance of 20,00 ohms per volt and so I'm putting 200kΩ across what is bound to be an open-circuit 100kΩ resistor. The meter resistance is enough to turn the transistor on, although it won't be passing the full current it ought to. The long testmeter leads won't upset matters, incidentally, because they're bypassed by the 0.0047μF capacitor between the base and chassis. So it looks as though all we need to do is to fit a new 100kΩ resistor in this set."

TAKING IT EASY

Contentedly, Smithy watched his assistant, leisurely, Dick proceeded to remove the faulty open-circuit 100kΩ resistor from the receiver printed board. The chalking up in their favour on this highly successful day had been further augmented by this final felicitous adventure in fault finding. Dick soldered in a replacement resistor, and they listened to the radio as it now gave a faultless performance on its f.m. range. Unhurriedly, Dick refitted the printed board in the cabinet, screwed on the back, gave the set a last check to make certain that all was well and carried it over to the "Repaired" rack.

MORSE MADE EASY

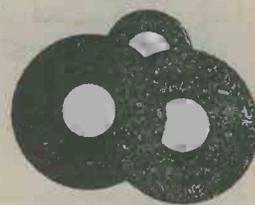

BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as Instruction books.

Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750gm). Details only s.a.e.

THE G3HSC MORSE CENTRE

S. Bennett, (Box 8), 45 Green Lane, Purley, Surrey.

Name

Address

.....

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET
LONDON W2 1NP

Tel: 01-402 9176

Please mention
Radio & Electronics Constructor

when replying to advertisements

SINGLE I.C. SIGNAL TRACER

By

M. V. Hastings

Inexpensive design with low component count

Traces a.f. and modulated r.f. signals

Two gain levels

This simple test instrument is suitable for tracing both audio frequency and amplitude modulated radio frequency signals, and is therefore suitable for fault-finding on audio and a.m. radio equipment. The unit is inexpensive since it incorporates only a single integrated circuit and a few passive components. The circuit is powered by a 9 volt battery and the output is applied to a crystal earphone. Two levels of voltage gain are available, one being 20dB (10 times) and the other 60dB (1,000 times). The tracer can in consequence detect very low level signals but need not be overloaded by higher level signals.

CIRCUIT OPERATION

Fig. 1 shows the circuit and, as will be apparent to many readers, the tracer is basically an operational amplifier used in the inverting mode. The LF351 has a very high resistance Jfet input and, in consequence, has a low noise level. This last factor is very important because weak signals must not be masked by noise generated in the amplifier.

To avoid the need for dual supply rails, the equal value resistors R3 and R4 bias the non-inverting input of the LF351 to a mid-supply voltage. There is 100% negative feedback at d.c. via R5 which causes the quiescent output voltage to be at the same level as the non-inverting input. This enables the output to

have what is virtually the maximum possible voltage output swing before clipping and serious distortion occur.


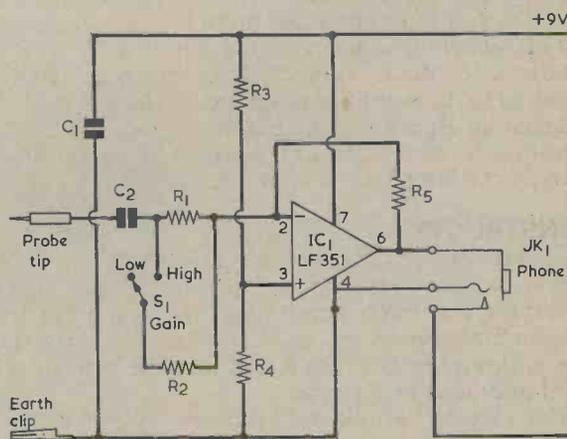


Fig. 1. The circuit of the signal tracer. This is switched on when the earphone plug is inserted into socket JK1.

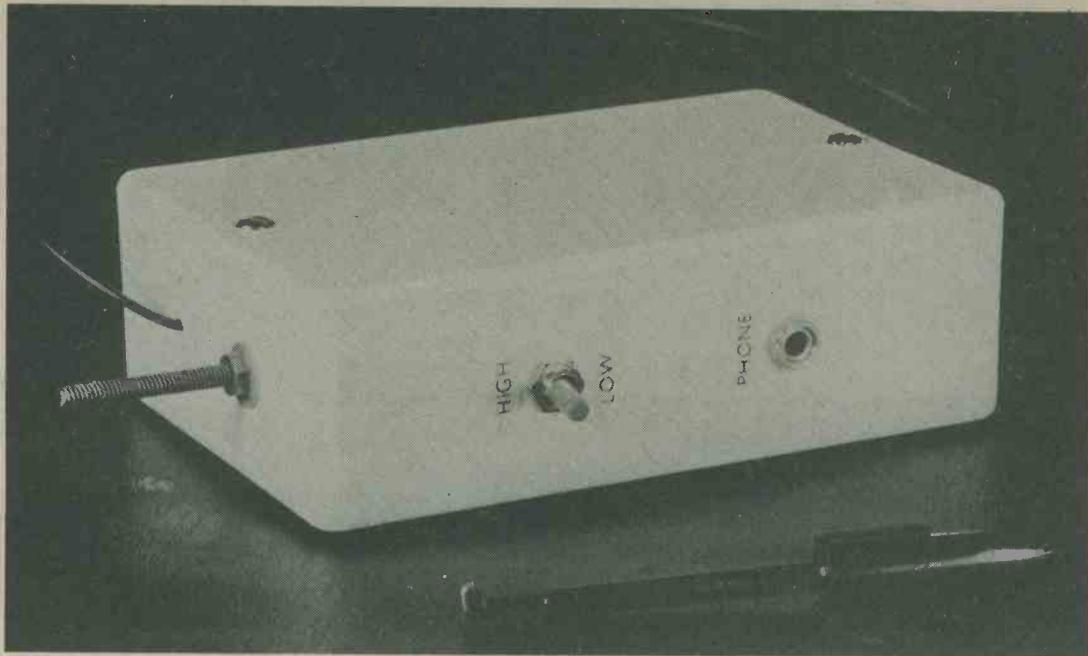

The signal tracer is housed in a small plastic case which can be held in the hand. The probe tip at the end is then applied to the test points in the equipment being checked.

Assuming a relatively low impedance at the point to which the signal tracer connects, the voltage gain is equal to the value of the feedback resistor divided by the value of the resistor in series with the inverting input. When S1 is in the "Low" position these two resistor values are $10\text{m}\Omega$ (R5) and $1\text{M}\Omega$ (R1) respectively and the voltage gain is therefore 10 times. Setting S1 to the "High" position connects the $10\text{k}\Omega$ resistor R2 across R1, so that the series input resistance is effectively $10\text{k}\Omega$ and the voltage gain is 1,000 times.

D.C. blocking is provided at the input by C2. No d.c. blocking is required at the output because a crystal earphone imposes no significant d.c. loading. It is quite in order, also, for the crystal earphone to have the amplifier quiescent output voltage across it. On-off switching is given at the output jack socket, where a contact connects the negative battery terminal to the amplifier when the crystal earphone is plugged in. Removing the earphone plug causes the amplifier to be switched off again. The circuit has a current consumption of approximately 2mA only.

CONSTRUCTION

A white plastic case measuring about 114 by 76 by 38mm is used to house the prototype signal generator, and this is a case type PB1, available from Maplin Electronic Supplies. A small case of about this size is desirable because it can then be held in the hand and used as a probe.

The layout employed can be seen in the photographs. A long 4BA or M4 bolt is mounted at one end of the case and is used as the probe tip. If desired, its end can be filed to a point. A solder tag is fitted under the bolt head inside the case to allow connection to be made to the bolt. A plain washer should be fitted outside the case under the securing nut. A small hole about 2mm in diameter is drilled at

COMPONENTS

Resistors

(All $\frac{1}{4}$ watt 5% unless otherwise stated)

- R1 $1\text{M}\Omega$
- R2 $10\text{k}\Omega$
- R3 $15\text{k}\Omega$
- R4 $15\text{k}\Omega$
- R5 $10\text{M}\Omega$ 10%

Capacitors

- C1 $0.1\mu\text{F}$ polyester type C280
- C2 $0.1\mu\text{F}$ polyester type C280

Integrated Circuit

- IC1 LF351

Switch

- S1 s.p.s.t. sub-miniature toggle


Socket

- JK1 3.5mm jack socket, modified (see text)

Miscellaneous

- Small plastic case (see text)
- 9 volt battery type PP3
- Battery connector
- Crystal earphone with 3.5mm jack plug
- Veroboard, 0.1in matrix
- Earth test clip (see text)
- Nuts, bolts, wire, etc.

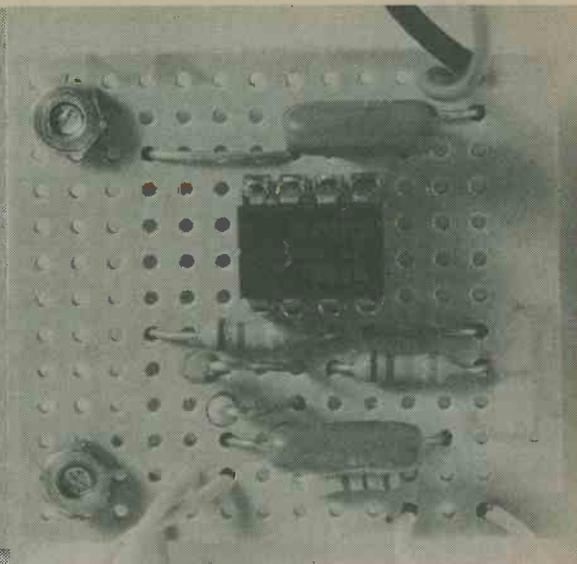The Veroboard assembly. This accommodates the single i.c. used in the tracer together with a small number of resistors and capacitors.



the same end of the plastic case, and this will eventually take the lead which connects to the earth clip. This can be a crocodile clip or any other convenient form of test clip. Switch S1 and socket JK1 are mounted on one side of the case, with the switch closer to the probe tip.

JK1 is an ordinary 3.5mm jack socket of open construction, normally having a contact which breaks when a plug is inserted. The socket is modified so that the contact makes with insertion of the plug. The unmodified socket has a contact set consisting of two pieces of metal, one fixed and the other springy so that it moves away from the fixed piece when the plug is inserted. The fixed piece is carefully bent downwards under the springy section so that the two are not normally in contact and only come together when the plug is fitted. The modified socket should have the appearance illustrated in Fig. 2. Make quite sure that the two parts of the contact set are not touching when the plug is not in the socket, as the unit will be permanently switched on if this should be allowed to happen.

COMPONENT PANEL

Most of the circuitry is assembled on a piece of 0.1in Veroboard having 13 holes by 13 copper strips. Fig. 3 gives details.


The board has first to be cut out from a larger piece, after which the two mounting holes are drilled. These can be clearance size for 6BA or M3 bolts. The 4

breaks in the copper strips are next made, using the special Vero tool or a small drill bit held in the hand. The components and link wires are next soldered in place, these being followed by the leads which connect to the components external to the board. The external wiring is finally completed, after which the Veroboard panel is mounted inside the case by two 6BA or M3 bolts with nuts. It takes up the position shown in the photograph of the case interior. Spacing washers should be fitted over the bolts to keep the panel underside clear of the inside surface of the case. The flexible lead which connect to the earth test clip can be about 18in long. A blob of glue can be used to secure it at the Veroboard hole at which it connects in order to reduce strain on the copper strip at the soldered joint. There is plenty of space for the PP3 battery. If a piece of sponge plastic is placed over the battery it will be held in position when the case lid is screwed on.

USING THE UNIT

There must, of course, be a signal fed into the input of the equipment being tested when the signal tracer is in use. This signal can be provided by a signal generator, but the normal signal source of the equipment is just as good. The earthing clip of the tracer is connected to the chassis of the equipment being checked and the probe tip is then applied to various points, starting at the input and working towards the output.

Fig. 2. Socket JK1 after modification. The fixed contact is carefully bent so that its end is below the springy contact instead of above it. The contacts should touch each other only when a jack plug is inserted.

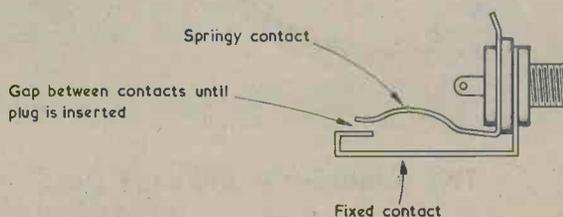



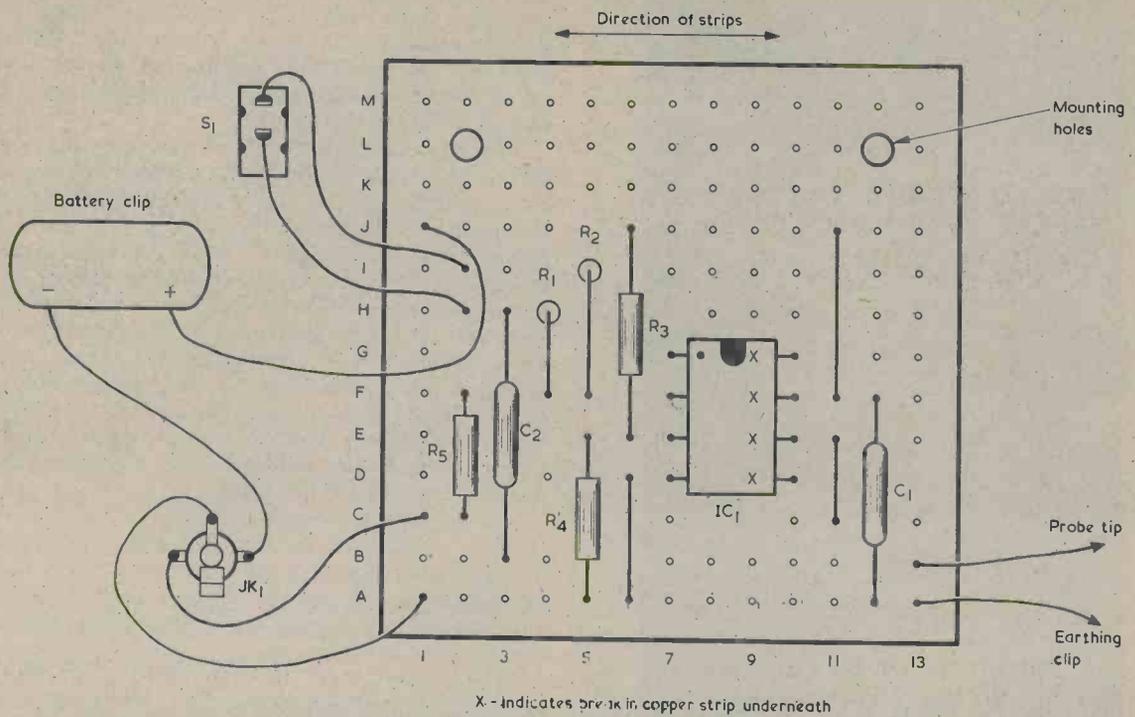


Fig. 3. Layout and wiring on the Veroboard panel. Also shown are the connections external to the panel.

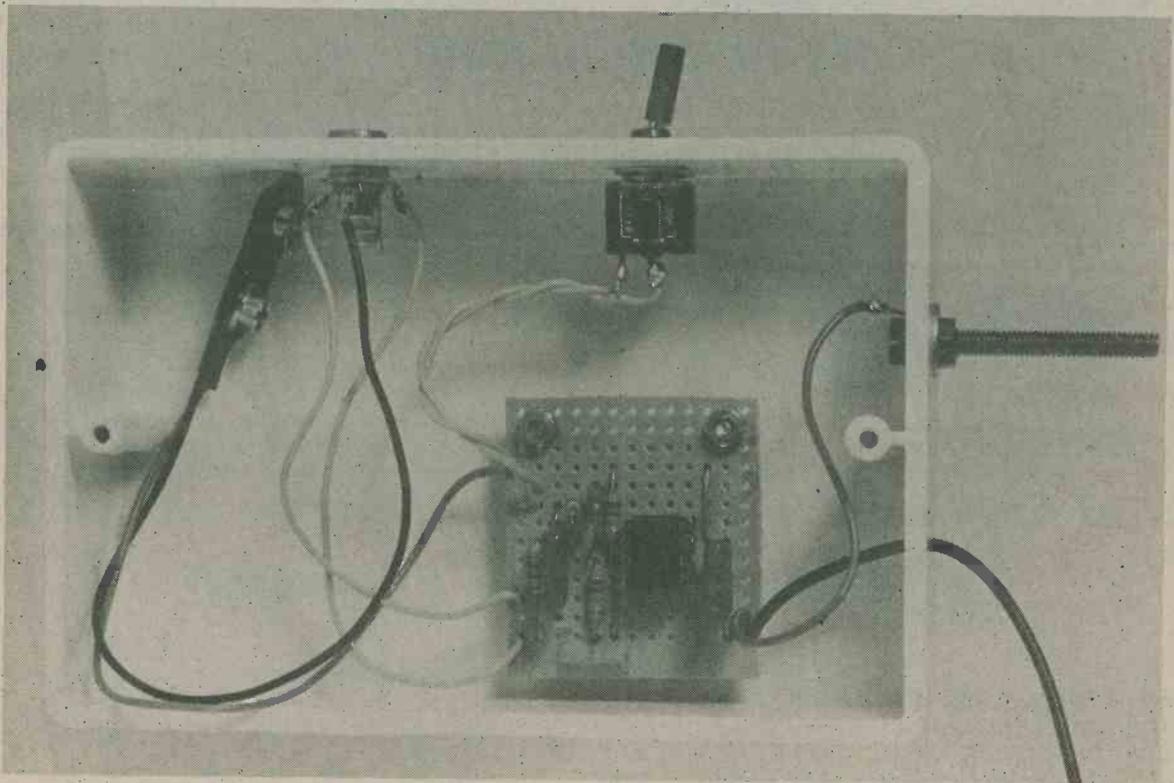

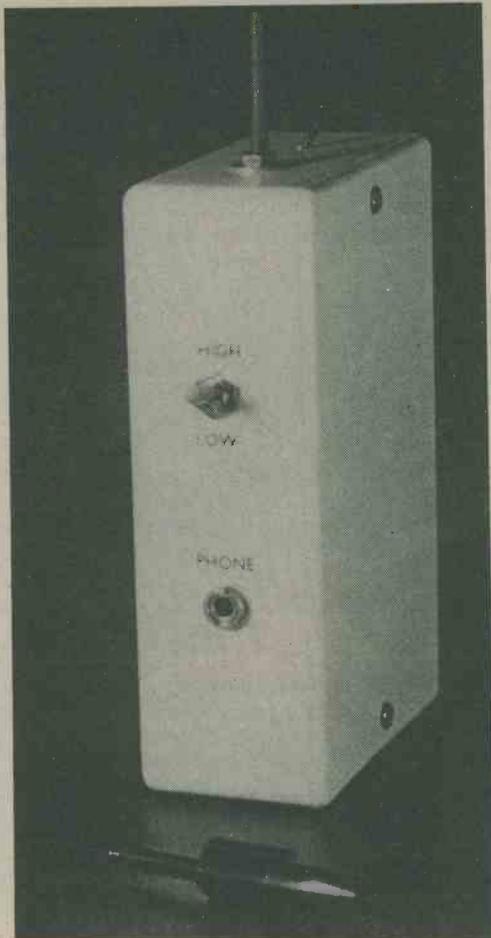The Veroboard is mounted inside the case near the probe tip. Note its orientation and positioning.



In this view the gain switch S1 is uppermost, with the jack socket below it.

Note that if the equipment is mains operated, the signal tracer may only be used when the equipment chassis is fully isolated from the mains supply by a double-wound mains power transformer. **The tracer must not be used with equipment having a direct connection between chassis and mains because of the risk of a dangerous shock.**

The person employing the signal tracer uses his own initiative in selecting test points. In general, the first test is made at the base of the input transistor, the second at its collector, the third at the base of the following transistor, and so on. If, say, there is a satisfactory signal at the base of a transistor and the signal is absent or is seriously distorted at its collector, then the fault obviously lies in the transistor or its associated circuitry. The transistor itself may be faulty or the collector load could, for example, have gone open or short-circuit. The primary function of a signal tracer is to find the area in which a fault lies. Component checks and/or voltage tests are then used to finally pin-point the fault.

Another use for the signal tracer is to check emitter bypass capacitors in circuits where a transistor emitter has a bias resistor connecting to chassis. If a significant signal level is present across the bypass capacitor this indicates that the bypass capacitor is not functioning correctly.

When tracing very low signal levels, as in the early i.f. stages of an a.m. radio receiver or the microphone input of a tape recorder, it will almost certainly be necessary to set S1 to the "High" position to obtain adequate sensitivity. However, for most tests the tracer will be overloaded unless S1 is switched to "Low". It is a good plan to use the signal tracer on serviceable equipment to obtain an idea of the signal level performance given at different stages.

On the face of it the unit is not suitable for r.f. signal tracing as there is no demodulation circuitry at the input. It is found in practice, however, that demodulation occurs within IC1, whereupon the unit is perfectly suitable for signal tracing in the i.f. stages of a.m. receivers. ■

Circular Hole Jig


by
D. M. Pitkin

Home-made jig cuts out large clean holes

Quite often an electronics project demands that fairly large circular holes need to be cut in a plastic panel to provide speaker apertures or to take meters or similar items. Faced with this problem recently, I discovered that a conventional hole saw produced sizes too small or too large for the particular item to be mounted.

WOODEN JIG

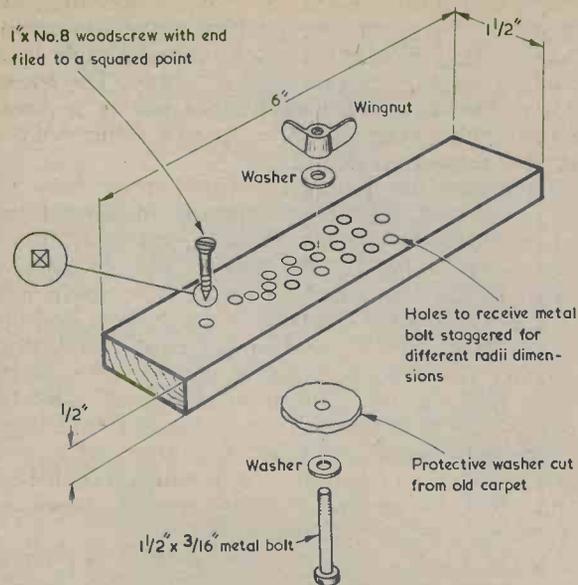The problem was solved quite simply by making up the jig shown in the diagram. The main section is a short length of scrap timber measuring about 6in. long, 1½in. wide and ½in. thick. Also required are a 1in. woodscrew, a 1½in. metal bolt of ⅜in. diameter, two ⅜in. plain metal washers, a protective washer cut



The home-made jig uses readily available parts and can be used to cut clean circular holes in plastic panels.

out from an old carpet and a wing nut which fits on the 1 1/2 in. bolt.

The end of the 1 in. woodscrew is filed to a squared point, and this point will cut cleanly through the plastic. Mark a centre line on the piece of wood and prick it about 1 in. from one end to receive the woodscrew. From this point mark out with a pair of dividers the required radius. Quite a number of radii can be accommodated on the single piece of wood to suit varying components by staggering the holes to be drilled.

When the marking out is complete, drill a threading hole for the woodscrew and an 3/16 in. hole at the radius point to be used. Fit the woodscrew, allowing the point to project through the timber a little more than the thickness of the plastic to be cut, and the jig is then ready for use.

To cut the circular hole in the plastic, locate and drill a 3/16 in. hole at its centre. Fit a plain washer over the 1 1/2 in. bolt and pass it through this hole from the underside. On the top of the plastic fit the protective washer, the wooden jig, a second plain washer and the wing nut. Tighten the wing nut with moderate pressure and turn the jig in a clockwise direction. The pointed woodscrew end will then cut through the plastic. Extra thick plastic can be tackled by reversing the jig and cutting from each side. Turning the jig in a clockwise direction maintains pressure on the cutting point.

RECIPROCAL WORKING

We regret that two obvious errors appeared in the article "Reciprocal Working", published in the December issue. The final term in the key sequence

on page 210 should, of course, be 0.047. Also, the frequency in the last calculation on page 211 should be 2.36Hz.

BOOK REVIEW

RADIO CONTROL FOR BEGINNERS. By F. G. Rayer, T.Eng. (C.E.I.), Assoc.I.E.R.E. 96 pages, 180 x 105mm. Published by Bernard Babani (Publishing) Ltd. Price £1.75.

The purpose of this book is to provide an introduction to radio control of models for beginners in this popular hobby. It commences by discussing the principles of radio control in various systems, including single and multi-channel, and then deals with licence conditions. Next to be described is a typical transmitter, with constructional notes, and a tone modulator. A mini transmitter is next dealt with as also is the question of transmitter aerials.

The book next proceeds to receiver aerials and takes in a super-regenerative receiver and a superhet receiver, again with constructional information. After this, relays and actuators are covered, together with other mechanical details and transistor switching of controlled devices. The book concludes with a consideration of the controlled model, which may be aircraft, boat or car.

"We used a mini-computer dateline service"





Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

- AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO DEPT REC
35/39 CHURCH STREET, WILMSLOW
CHESHIRE SK9 1AS.

Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits, etc.,

Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete speakers

MARCO TRADING

To obtain a free copy of our 35 page list simply send a 20p postage stamp or a large SAE. This advertisement shows only a part of our range. (Our new list includes Tants, Electrolytics, Disc ceramics, etc.)

400m/w ZENER DIODES

Low Price
3V6, 3V9, 4V3, 4V7, 5V1, 5V6, 6V2, 6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V, 13V, 13V5, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V
Price: 8p each 100 any mix £6.00

RESISTORS
1W at 40°C 5% tol., 2.2 Ω to 2M2, E12 2p each.
Resistor Pack — 2.2 Ω — 2M2, 10 each value (730 resistors) £6.00

1 watt ZENER DIODES

3V3 to 200V Full range
I.C. Sockets
Price 15p each, 100 any mix £12.50
8 DIL 10p 22 DIL 23p
14 DIL 13p 24 DIL 24p
16 DIL 15p 28 DIL 28p
18 DIL 18p 40 DIL 40p
20 DIL 22p

VEROBOARD (Copper Clad)

Size Inch 0-1" 0.15
2.5 x 1 20p N/A
2.5 x 5 55p 56p
2.5 x 3.75 46p 50p
Speakers 8" x 5" 3 ohm £1.50 each

CONNECTING CABLE

Black, Blue, Green, Grey, Orange, Pink, Red, White, Violet, Yellow, Brown.
Singles 5p per metre
7/0.2mm 5p per metre
15/0.2mm 8p per metre

SPECIAL OFFERS

BRAND NEW METAL SLIDER POTENTIOMETERS

60mm TRACK 1+ 100+ Mains Rocker switch with Neon 10A, D.P.S.T.
500 ohm Lin. Mono 35p 28p
50K Log. Stereo 40p 30p
100K Lin. Stereo 40p 30p
1 Meg Log. Stereo 40p 30p

BZY96 ZENERS (21W) — 5VZ 1 20p each
100 12p each

Other values available in 45mm track — send for list.

Send your orders to:

DEPT DP11, MARCO TRADING, THE OLD SCHOOL, EDSTASTON, Nr. WEM, SHROPSHIRE SY4 5RJ
Tel: Whixall (094872) 464/465

Please add 30p postage and packing to each order and add 15% VAT to your total order. Export add NO VAT but add postage. Air/Rex at cost

TANT. BEAD CAPS

0.1/35v	12p	4.7/35v	12p
0.22/35v	12p	33/6.3v	25p
1.0/35v	12p	47/10v	30p

SUB. MIN. TOGGLE SWITCHES

SPST — 70p
SPDT — 78p
DPDT — 82p
DPDT — 90p (C-OFF)



BRIDGE RECTIFIERS

2.5 Amp 50V	32p	400V	50p
400V	43p	6.0 Amp 50V	70p
800V	58p	200V	78p
2.0 Amp 50V	35p	400V	85p
100V	42p	25 Amp 100V	
25 Amp 50V	£2.38		£2.41

0.1W SUB. MINIATURE PRE-SETS

100 Ω to 1 Meg Vertical or Horizontal
Price: 6p each, 100 any mix £4.50

AC128	20p	BC125	10p	BC184	9p
AD149	58p	BC147	8p	ZN3055	48p
BC107	10p	BC153	10p	BY127	12p
BC108	10p	BC172	8p	IN4007	8p
BC109	10p	BC183	9p	IN4148	2p
BYF90	90p	BC212	9p	BC160	37p
BR101	32p	BC214	9p	CMOS	
741	20p	BC140	32p	4011	20p

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in the issue of RADIO & ELECTRONICS CONSTRUCTOR

➔			

15 words at 12p equals £1.80

ALL WORDING IN BLOCK LETTERS PLEASE

I enclose remittance being payment at 12p a word. MINIMUM £2.00
Box Number, if required, 30p extra.

NAME
ADDRESS

*Copy to be received four weeks prior to publication.
Published on the 3rd of every month, forward dated.*

SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge
£2.00
Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. Replies to Box Numbers should be addressed to: Box No. —, Radio and Electronics Constructor, 57 Maida Vale, London, W9 1SN.

LEARN ELECTRONICS FAST. New, unique, brilliantly simple Tutronik system. Selected by BBC TV. No-soldering, 30-kwikbuild electronics projects. Learn fast to identify components, read circuit diagrams, break the colour code and connect circuits that really work. Kit complete with simple-to-follow instructions, circuit plans, components and Tutronic connection system in compact presentation wallet. Only £12.95 plus 75p p. & p. UK (£2.75 p. & p. elsewhere). Available only from Dept. RE, Technocentre Ltd., 140 Norton Road, Stockton-on-Tees, TS20 2BG.


CONNECTING WIRE, single strand, PVC covered. Ideal for electronics experiments and Proto-Board work. 10 colours. 50 yds. £1.50. 100 yds. £2.50. J.D. Electronics, 69 Well Heads, Thornton. Bradford. W. Yorks.

ANY SINGLE SERVICE SHEET £1 plus S.A.E. Thousands of different service/repair manuals/sheets in stock. Repair data your named TV £6 (with circuits £8). S.A.E newsletter, price lists, quotations. (0698-883334). Ausrec, 76 Churches, Larkhall, Lanarkshire.

INTERESTED IN RTTY? You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk; NR32 3PJ.

BOOKS FOR SALE: *Experiments with Operational Amplifiers*, by George B. Clayton. £3.75. *Digital I.C. Equivalents & Pin Connections*, by Adrian Michaels, £1.20. *Experimenting with Electronic Music* by Brown & Olsen. £1.20. *Electric Model Car Racing* by Laidlaw-Dickson. 60p. *Electronics Unravalled* by Kyle, £1.10. *Easy Electronics Projects — Beyond the Transistor*, by Rufus p. Turner. £1.20. *Auto Electronics Simplified*, by Tab Books, £1.20. *Practical Solid-State DC Power Supplies*, by T. D. Towers. £1.00. Box No. G394.

(continued on page 381)

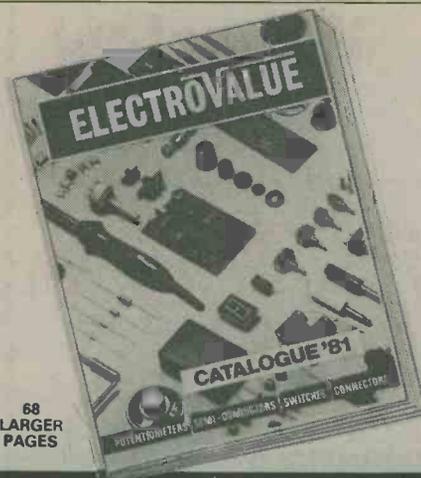

68
LARGER
PAGES

The larger
Catalogue
that means
FREE POSTAGE
IN U.K.

**ADDITIONAL
DISCOUNTS**

**GUARANTEED
SATISFACTION**

**GOOD STOCKS
GOOD DELIVERY**

We pay postage.

Semi-Conductors • I.C.s • Opto-
devices • Rs and Cs in great variety
• Pots • Switches • Knobs •
Accessories • Tools • Materials •
Connectors

ELECTROVALUE

**FREE
FOR THE
ASKING**

ELECTROVALUE LTD., 28 (RC2), St. Jude's
Road, Englefield Green, Egham, Surrey
TW20 0HB. Phone: 33603 (London 87) STD 0784. Telex 264475.
NORTHERN BRANCH (Personal shoppers Only): 680 Burnage Lane, Burnage,
Manchester M19 1NA. Phone (061) 432 4945.

A CAREER IN RADIO

Start training **today** and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for **you**.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
Radio TV Electronics Technicians'
Electrical Installations Technicians'
Electrical Installation Work
Radio Amateurs'

MPT Radio Communications Cert

EXAMINATION STUDENTS —

GUARANTEED COACHING

UNTIL SUCCESSFUL

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics. Including:

Electronic Engineering & Maintenance
Computer Engineering/Programming
Radio, TV & Audio Engineering
& Servicing
Electrical Engineering Installations
& Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name Age

Address

Occupation

ICS Accredited
by CACC
Member of
ABCC

To
International Correspondence Schools
Dept 278D, Intertext House, LONDON,
SW8 4UJ or phone 01-622 9911 (anytime)

**The MIGHTY MIDGETS
SOLDERING
IRONS AND ACCESSORIES**

18 WATT IRON FITTED WITH NO. 20 BIT AVAILABLE IN 12V, 110V, or 240V	RETAIL PRICE each inc. v.a.t	POSTAGE extra
SPARE BITS	69 ^p	—
STANDS	£4.49	80 ^p
SOLDER: SAVBIT 20	70 ^p	12 ^p
" 10"	40 ^p	8 ^p
LOWMELT 10"	80 ^p	12 ^p
I.C. DESOLDERING BIT	£1.27	12 ^p

BIT SIZES: NO. 19(1.5mm) NO. 20(3mm)
NO. 21(4.5mm) NO. 22(6mm)

From your Local Dealer or Direct from Manufacturers

**S & R. BREWSTER
LIMITED**

86-88 UNION ST. PLYMOUTH PL1 3HG
Tel: 0752 65011 TRADE ENQUIRIES WELCOME

PLEASE QUOTE YOUR NUMBER WHEN ORDERING

**BUILD YOUR OWN
P.A., GROUP & DISCO SPEAKERS** by R. F. C. Stephens
Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman
(full constructional details for versions using 15", 12" and 10" (drive units). £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens
This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING
5 Swan Street, Wilmslow, Cheshire-

**PRINTED CIRCUIT BOARDS FOR
"RADIO & ELECTRONICS CONSTRUCTOR"
PROJECTS.**

OCT. 20dB amp. Part 1 68p plus 25p P&P
NOV. 20dB amp. Part 2 62p plus 25p P&P
NOV. Basic Med. Wave radio 69p plus 25p P&P
DEC. Volume Expander £2.25 plus 25p P&P
All boards ready for use, roller tinned and drilled, glassfibre.

Trade enquiries welcome. Highly competitive prices.
Write now for quote To:
BRB PRINTED CIRCUITS (REC)
109, Potter Street, Worksop,
Notts. S80 2HL.

UNDERSTAND DATA PROCESSING

NEW FOURTH EDITION



DATA PROCESSING, by Oliver & Chapman, is now in its Fourth Edition

200 pages 9½" x 6½" **PRICE £2.95**
P.&P. 48p

PUBLISHED BY D.P. PUBLICATIONS

The primary aim of this outstanding manual is to provide a simplified approach to the understanding of data processing – (previous knowledge of the subject is not necessary).

The 40 chapters and appendices cover the following topics: Introduction to Data Processing; Organisation and Method; Conventional Methods; Introduction to EDP and Computers; Hardware; Computer Files; Data Collection and Control; Programming and Software; flowcharts and Decision Tables; Systems Analysis; Applications; Management of EDP, etc.

A Manual for Business and Accountancy Students

Available from: **DATA PUBLICATIONS LTD.,**
57 MAIDA VALE, LONDON W9 1SN.

SMALL ADVERTISEMENTS

(Continued from page 379)

BURGLAR ALARM EQUIPMENT. Top quality brand new free catalogue and price list. Sigma Security Systems, 13 St. John's Street, Oulton, Leeds, Yorks. LS26 8 JT.

FOR SALE: A number of "D & S" three pin, fused, mains plugs and fuses. S.A.E. for details. Box No. G396.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £6.00 per annum. (U.K. and British Commonwealth), overseas \$12.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

U.K. AIRCRAFT frequencies list £1. U.K. marine frequencies list £1. Including HF VHF. P.L.H. Electronics, 20 Vallis Road, Frome, Somerset.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.


2 WATT General Purpose I.C. Amplifier Module with volume and tone controls. Needs 9V-18V p.s.u. or battery. £4.00. R.H. Electronics. 119 Fraser Road, Sheffield, S8 0JH.

FOR SALE: Damaged repairable cassette recorder and 10 cassettes. £15.00. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

FOR SALE: Photographic enlarging equipment: Vivitar enlarger. Model E.36 with 50mm f. 3.5 and 75mm f.3.5 lenses. Kodak safety light. Kodak contrast filter set. 11 in. x 14 in. printing frame with copying facilities. Measuring flask. Three trays, three tweezers. Three plastic bottles. Clips. Printing paper. Antistatic brush for cleaning negatives. Kodak Photoguide Booklet. Man's protective apron. £75 o.n.o. Pair of Goodman's speakers 8 ohms, 15 watts, £50 o.n.o. R. L. Gee, 3 Longfellow Drive, Hutton, Essex, CM13 2QQ.

RADIO & ELECTRONICS CONSTRUCTOR 1969-1975, P.W./P.E. 1964-1970. 50p each. S.A.E. for refund if sold. C. Redwood, 45a Lulworth Avenue, Poole, Dorset, BH15 4DH.

(Continued on page 382)

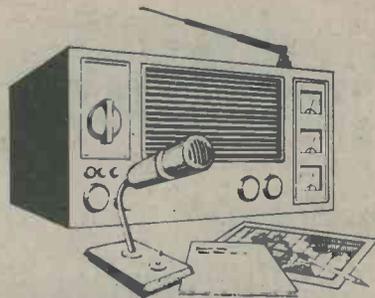

BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

Free!

Brochure without obligation to :-

British National Radio & Electronic School

4 Cleveland Road, Jersey, Channel Islands.

Name

Address

REC/2/815

BLOCK CAPS PLEASE

THE SPECTACULAR 1981 GREENWELD

Component Catalogue Bigger and better than ever!!!

- * 60p discount vouchers
 - * First Class reply paid envelope
 - * Free Bargain List
 - * Priority Order Form
 - * VAT inclusive prices
 - * Quantity prices for bulk buyers
- SEND 75p FOR YOUR COPY NOW!!

CALC CHIPS 60p!!!

New full spec. supplied with data. Type MK50321 - full function inc. memory. Only 60p.

DISPLAYS

8 and 9 digit 7-segment bubble type for above chips - most have minor faults dud segment etc. Mixture of 2 or 3 different types with data. 5 for £1.00

NICADS

Ex-equip size C approx. £1 each; 10 for £8.00

1N4006 DIODES

Special purchase of 1A rects, Russian made. Packed in boxes of 300, £8.50 per box; 4 boxes £30.00; 10 boxes £75.00

DISC CERAMICS

0.22uF 12V 9mm dia. Ideal for decoupling. 100 for £2.75; 1000 £20.00
0.05uF 12V 15mm dia. 100 £1.50; 1000 £12.00
Pack of disc ceramics, assorted values and voltages - 200 for £1.00

TRANSFORMERS

Mains primary, 50V 20A sec. £20.00
Mains pri. 110V 15A sec £30.00; 20A £40.00
FSRA60 relay. 2 x 10A contact, 1M, 1B. Coil is 250R, and rated 60V ac, but works on 12-24V DC. Solid Encapsulation with screw terminals makes it ideal for car use. £1.20

ALL PRICES INCLUDE VAT; JUST ADD 40p POST

SLIDER POT SCOOP!!!

Made by Piher, type PL40CP Silly prices for superb goods!!

PL40CP - 69 x 16 x 9mm, 40mm slide length. 220R, 2k2 or 10k lin only. Prices (any mix): 1-24 20p; 25-99 17p; 100+ 14p.

TTL LINEAR OPTO

All new full spec - Fairchild/SGS:
TTL: 5400 5401 5402 5403 5404 5405 5410 5421 5430 5450 5451 5453 5460
- All 12p ea. 5470 5472 5474 5475, 5476 5480 5486 5490 54107 54121 54122 - All 20p ea. 5482 54128 - 40p ea. Others (74S, H) on B/L 12 (SAE please)

LINEAR: 9665 or 9666, 7 x 50V Darlington in 16 DIL 60p; 75452 or 4 dual periph driver 70p; XK1444 7 CMOS P-channel buffers, 15V 16DIL 24p.

OPTO: Isolators, FCD831 60p; TIL115/118 60p; FPE100/106 Infra red LED £2.50; FND847 7 seg 0.8" CA £2.00; FND850 CC £2.00. (Data on request for linear & opto devices)

TRANSISTOR PACK K516

Take advantage of this unbelievable offer!! Small signal NPN/PNP transistors in plastic package at an incredibly low, low price!! Almost all are marked with type number - almost all are full spec devices, some have bent leads. Over 30 different types have been found by us, including BC184/212/238/307/328; BF196/7; ZTX107/8/9/342/450/550 etc. Only available as a mixed pack at £3/100; £7/250; £25/1000.

REGULATED PSU PANEL

Exclusive Greenweld design, fully variable 0-28V & 20mA-2A. Board contains all components except pots and transformer. Only £7.75. Suitable transformer and pots £6.00. Send SAE for fuller details.

GREENWELD

443G Millbrook Road Southampton SO1 0HX

BUY THIS BEST SELLER

T.V. FAULT FINDING

MONOCHROME
405/625 LINES



REVISED & ENLARGED

Edited by J. R. Davies

132 pages

PRICE £1.20

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

Price £1.20 from your bookseller.

or post this Coupon together
with remittance for £1.47
(to include postage) to

DATA PUBLICATIONS LTD.
57 Maida Vale, London, W9 1SN

Please send me the 5th revised edition of TV
Fault Finding. Data Book No. 5

I enclose cheque/crossed postal order for . . .

NAME

ADDRESS

.

.

BLOCK LETTERS PLEASE

SEPTEMBER

SMALL ADVERTISEMENTS

(Continued from page 381)

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ.

BURGLAR ALARM COMPONENTS. PVC coated steel bell box £8.74. 6in. masterbell £13.53. 106dB sounder £11.53. Latching personal attack button £2.95. Surface contact £1.28. Flush contact £1.28. Large pressure pad £2.85. Stair tread pad £2.00. 20m range infra red beam £46. Mains/battery alarm control module £17.20 or send for our free component catalogue and price list. All prices inclusive. Sigma Security Systems, 13 St. Johns Street, Oulton, Leeds, W. Yorks. LS26 8JT.

THE RADIO AMATEUR INVALID & BLIND CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey, KT6 4TE.

ZX80 PEOPLE. Free leaflet explains how to overcome load problems, ½-price memories, etc., supplied with four games on cassette. Send £3 or s.a.e. for details. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

BOOK CLEARANCE. Bound volumes *Radio & Electronics Constructor* Nos. 27, 28 and 29, £3.00 each. *Cost Effective Projects Around the Home* by John Watson, £1.50. *Talk-Back Tv: Two-Way Cable Television*, by Richard Veith, £1.00. *Acoustic Techniques for Home & Studio*, by F. Alton Everest, 75p. *Beginners Guide to Building Electronic Projects*, by R. A. Penfold, 60p. *Solid State Short Wave Receivers for Beginners*, by R. A. Penfold, 60p. *50 Simple LED Circuits*, by R. N. Soar, 50p. *Radio-Electronics Hobby Projects*, Foulsham-Tab, £1.00. *The Inventor of the Valve - Biography of Fleming*, by J. MacGregor-Morris, £1.00. *Understanding and Using Modern Electronic Servicing Test Equipment*, by Charles M. Gilmore, £1.30. *Using Electronic Testers for Car Tune-Up* by Albert Warringer, 75p. All prices include postage. Box No. G399.

25 MIXED I.C.'S £1.50. 100 mixed transistors £3.50. Valves. Early radios. Electronic bargains. Interesting lists 15p. Sole Electronics, REC, 37 Stanley Street, Ormskirk, Lancs, L39 2DH.

(Continued on page 383)

SMALL ADVERTISEMENTS

(Continued from page 382)

12 UNUSED RECHARGEABLE Gel type Lead Acid Batteries. 12V 1.5 A.H. £4 each. R. Garas, 147 Seaforth Avenue, New Malden, Surrey.

USE OPTICAL FIBRES TO CARRY LIGHT.

Tough, wire-like strands that are excellent for communications, lighting, electrical isolation, etc. Introductory pack totals sixteen feet of four assorted types, plus twenty page illustrated guide. Send £3.55 inclusive to Quantum Jump Ltd., 53 Marlborough Road, Tuebrook, Liverpool L13 8EA.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

SPONSORS required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NR8 8SS.

SITUATION VACANT

WANTED: Representatives to sell Electronic Components to shops and industries on good commission basis. Please send full details of experience to: Sunmit Electronics, 96 Peel Road, Wembley, Middlesex. Telephone: 01-904-6792.

RADIO & ELECTRONICS

Project Kits

LATEST KITS:

Coil Coupled S.W. Converter Nov 80	£24.65
Portable Short Wave Radio Aug 80	£16.00
"K" Tone Generator Dec 80	£11.00
Opto-Coupled Volume Expander Dec 80	£17.25
Add-on Clipping Monitor Dec 80	£8.00

(Postage 60p)

CATALOGUE 1981

Our brand new, fully illustrated catalogue is now available. A very wide range of components and accessories is detailed, including: resistors, i.c.s, transistors, aerials, cases, connecting leads, transformers, coils etc etc. For your copy send a cheque or postal order for 50p (post paid).

T & J ELECTRONIC COMPONENTS

98, Burrow Road, Chigwell, Essex. IG7 4HB.

Mail order only. No minimum order. VAT inclusive.

REVROR OPTICAL & TECHNICAL

6 SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536

PRICED
FROM
£148.75

Stereomaster

This microscope's working distance and field of view is relatively large; this feature ensures convenience to the operator who works with both hands while assembling precision mechanisms.

IDEAL FOR
PRINTED CIRCUITS
AND OTHER
DELICATE WORK.
COMES
COMPLETE WITH


built-in x 10 Mag.
Objectives x 20
Objectives x 35
At extra cost



We stock one of the largest selections of second hand microscopes and optical magnifiers, on and off stands. Please phone for details.


DIRECT SUPPLY SERVICE TO READERS

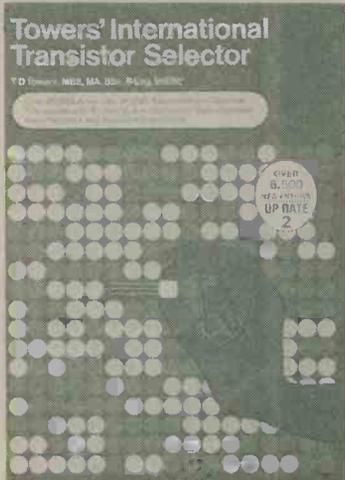TOWERS INTERNATIONAL TRANSISTOR SELECTOR (NEW REVISED EDITION)



This is dead! 

Would this replace it?

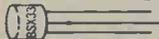

If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. It's one of the most useful working books you will be offered this year. And probably the cheapest!

In it, you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price £10-70 inc P&P

TOWERS INTERNATIONAL FET SELECTOR



If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price £4-60 inc P&P

(Please allow 21 days for delivery)

Tower's International Transistor Selector by T. D. Towers
MBE, MA, BSc, C Eng, MIERE
£10-70
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

.
.
.

(Block capitals)

Tower's International FET Selector by T. D. TOWERS
MBE, MA, BSc, C Eng, MIERE
£4-60
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below


NAME

ADDRESS


.
.
.

(Block capitals)


SEVEN SEGMENT DISPLAYS

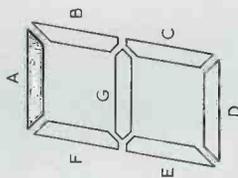


(a)

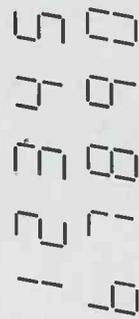

(b)

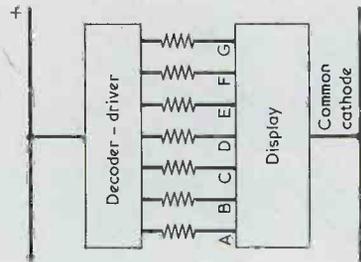

(d)

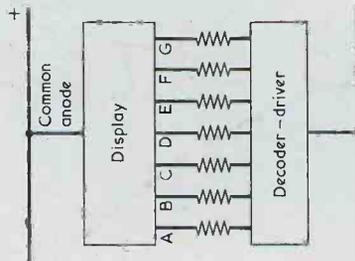

(e)

A seven segment numeric display is formed in the manner illustrated in (a), and the way in which the numbers 1 through to 0 are presented is shown in (b). 1 is given by segments B and C, 2 by segments A, B, D, E and G, 3 by segments A, B, C, D, 4 by segments B, C, F and G, and 5 by segments A, C, D, F and G. The number 6 is displayed with segments C, D, E, F and G, 7 with segments A, B and C, 8 by all seven segments, and 9 by segments A, B, C, F and G. Finally, 0 is represented by segments A, B, C, D, E and F.

Two alternative presentations for 6 and 9 appear in (c). Both have added "tails", the number 6 tail being given by segment A and the number 9 tail by segment D. Further provided in the display may be a decimal point segment. Plus and minus signs, colons, etc., can also be included.

Light-emitting diode displays, in which each segment is an i.e.d., are either common cathode or common anode types. With the first type the segment cathodes are made common and connect to one (or more) of the display terminals. The display is then driven as in (d), with a current limiting resistor in series with each anode. A common anode display is connected as in (e), with current limiting resistors in series with the seven segment cathodes. The decoder-driver i.c. may be either t.t.l. or CMOS (with which the current limiting resistors are sometimes omitted).

Liquid crystal displays are also very widely encountered, and are typified by requiring extremely low drive currents. This makes their use attractive in digital watches and other battery driven items.

The new MAPLIN CATALOGUE is out on December 5th

A massive new catalogue from Maplin that's bigger and better than ever before. If you ever buy electronic components this is the one catalogue you must not be without. Over 300 pages, it's a comprehensive guide to electronic components with thousands of photographs and illustrations and page after page of invaluable data. We stock just about every useful component you can think of. In fact, well over 5000 different lines, many of them hard to get from anywhere else. Hundreds and hundreds of fascinating new lines, more data, more pictures and a new layout to help you find things more quickly.

MAPLIN

Maplin Electronic Supplies Ltd.
 All mail to: P.O. Box 3, Rayleigh, Essex SS6 8LR.
 Telephone: Southend (0702) 554155. Sales (0702) 552911.
 Shops:
 159-161 King Street, Hammersmith, London W6. Telephone: (01) 748 0926.
 284 London Road, Westcliff-on-Sea, Essex. Telephone: Southend (0702) 554000.
 Both shops closed Mondays.



On sale
 in all branches
 of W H Smith
 from Dec 5th
 price £1

**PLUS
 LOW PRICES**
 such as
 Resistors from 1½p
 Multimeters from £4.25
 Ni-Cads from £1.15
 Stereo Headphones from £3.49
 Radios from £2.95
 Over 300 Books
 21 Different ranges
 of capacitors, etc.,
 etc., etc.,

Post this coupon now for your copy of our 1981 catalogue price £1.

Please send me a copy of your 320 page catalogue. I enclose £1 (Plus 25p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the UK send £1.68 or 12 International Reply Coupons.

I enclose £1.25

Name _____

Address _____

REC281