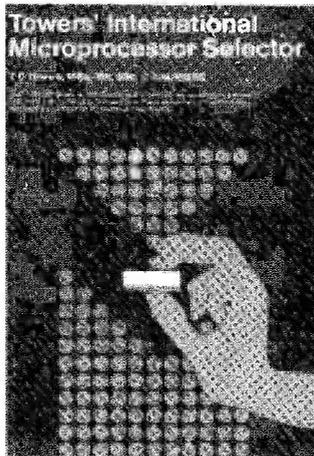


NEW! JUST PUBLISHED TOWERS INTERNATIONAL MICROPROCESSOR SELECTOR



**ONLY
£16.25
POST PAID**

If you come into contact with microprocessors (whether as hobbyist, student, circuit engineer, programmer, buyer, teacher, serviceman, or just humble reader) you often find you would like data information on a specific microcircuit element. Specifications apart, you may be even more interested in where you can get the device in question. And perhaps even more important still (particularly with obsolete devices), you may be looking for guidance on a readily-available second source or possible substitute.

This microprocessor selector (working on the same basis as the TRANSISTOR, FET, and OPAMP LINEAR-IC selectors already compiled by the author) is designed to provide in one handy reference volume a comprehensive body of readily-accessible, user-slanted essential information across the field of microprocessors.

In the data tabulations will be found set out the essential basic specifications of over 7,000 commercially-available microprocessor 'chips', including not only the microprocessor elements themselves (e.g. MPUs and CPUs) but also the many other LSI 'support' circuits (e.g. ROMs, RAMs, PROMs, clocks, UARTs, I/Os) normally used in harness with the microprocessors proper to produce complete microcom-

puters or microcontrollers. For ease of reference, the descriptions and control specifications of the individual circuits are set out in the detailed data tables on separate single lines, arranged in alpha-numeric order by type number.

For the newcomer to the very new field of microprocessors, the selector includes a full introductory note on these devices before the data tables.

Besides this, the tables are supplemented by separate appendices giving additional information on: (a) Microprocessor chip applications (and codings); (b) Microprocessor 'families'; (c) Microprocessor LSI chip manufacturers (and codings); (d) Semiconductor LSI technologies (and codings); (e) Microprocessor chip packages (and codings); (f) Microprocessor trainer and development systems; (g) Microprocessor bibliography; (h) Manufacturers' house codes; (i) Glossary of microprocessor terms; (j) Explanatory notes to tabulations.

This selector is fully international in scope and covers not only microprocessors and related devices from the USA and Continental Europe, but also from the UK and the Far East (Japan).

TO:- DATA PUBLICATIONS LTD, 57 MAIDA VALE, LONDON W9 1SN

Please send me copy/copies of

**TOWERS INTERNATIONAL
MICROPROCESSOR SELECTOR**

Price: £16.25 inc P&P

NAME

ADDRESS

(BLOCK CAPITALS PLEASE)

RADIO & ELECTRONICS CONSTRUCTOR

APRIL 1981
Volume 34 No. 8

Published Monthly

First published in 1947

Incorporating The Radio
Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone
01-286 6141

Telegrams
Databux, London

©Data Publications Ltd., 1981. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £9.50, Eire and Overseas £10.50 (U.S.A. and Canada \$30.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production – Web Offset.

NEWS AND COMMENT	462
VOLTAGE CALIBRATOR FOR OSCILLOSCOPES Suggested Circuit by G.A. French	464
SOLDERING IRON REMINDER – Unobtrusive audible device – by John Baker	466
TRADE NOTE – Ratchet-operated cable cutter	469
TIMER WITH TRIGGER ACTION by F. Craig	470
FURTHER NOTES ON SOME RECENT RECEIVERS – Part 2 (Conclusion) by Sir Douglas Hall Bt., K.C.M.G.	472
MODEL TRAIN CONTROLLER – low impedance "constant voltage" output, low cost mains operation by M.V. Hastings	474
GUITAR PRACTICE AMPLIFIER – Single i.c. design, 3 mixed inputs by R.A. Penfold	480
SHORT WAVE NEWS – For DX Listeners by Frank A. Baldwin	487
MEDIUM AND SHORT WAVE RADIO by I. M. Attrill	489
A SESSION OF PUZZLES – No. 1 In Your Workshop	494
AGILE TARGETS – Ministry of Defence contract	498
IN NEXT MONTH'S ISSUE	499
RADIO TOPICS by Recorder	500
ACTIVE TONE CONTROL MODULE by A. P. Roberts	502
LINEAR AMPLIFICATION Electronics Data No. 68	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by LSG Printers, Portland Street, Lincoln.

OUR NEXT ISSUE
WILL BE PUBLISHED
15th. APRIL

THE BI-PAK OPTO SHOW

LEDs

1501	£0.10	TIL209 Red LED .125"
1502	£0.16	TIL211 Green LED .125"
1503	£0.16	TIL213 Yellow LED .125"
1504	£0.10	FLV117 Red LED 2"
1505	£0.16	FLV310 Green LED 2"
1506	£0.16	FLV410 Yellow LED 2"
1507	£0.80	2nd Grade LED pack 10 assorted
1522	£0.12	MIL32 Clear Illuminating Red LED .125"
1523	£0.12	FLV111 clear illuminating Red LED 2"
1524	£0.65	COX21 Red Flashing LED
1525	£0.75	COX95 two colour LED

OPTO-ISOLATORS

1515	£0.55	Opto-isolator IL74 Single
1516	£1.16	Opto-isolator IL74 Dual
1517	£2.10	Opto-isolator ILQ74 Quad

7 SEGMENT LED DISPLAYS

1508	£0.80	BDL307 7 segment LED display .3"
1509	£1.80	BDL527 dual 7 segment LED display .5"
1510	£0.98	BDL707 7 segment LED display .3"
1511	£1.75	BDL747 7 segment LED display .6"
1512	£1.90	BDL727 dual 7 segment LED display .5"

MISCELLANEOUS

1514	£0.60	DRP12 Light Dependent Resistor
1518	£0.60	Photo transistor P20 NPN
1519	£0.26	Photo Darlingon MEL11 NPN
1520	£0.40	Photo transistor OCP71 PNP
1526	£0.38	FPE100 Infra Red Emitter
1527	£0.38	CQY89 Infra Red LED

Beginners Pak .no.1 - 100 Transistors

A pack of well known transistors, As used in many popular projects, A must for beginners (and very useful to experienced constructors too).

10	BC107/8 TO18 Metal	NPN
10	BC237 TO92 Plastic	NPN
5	BC177/8 TO18 Metal	PNP
5	BC251 TO92 Plastic	PNP
10	BFY61 BC141 TO39 Metal	NPN
5	BC160 TO39 Metal	PNP
5	2N3055 TO3 Metal	NPN
2	BD312/MJ2955 TO3 Metal	PNP
5	TIP29-31 TO220 Plastic	NPN
2	TIP30-32 TO220 Plastic	PNP
10	OC71-76 Germanium	PNP
5	AC128-188 Germanium Metal	PNP
5	AC127-187-188 Germanium Metal	NPN
5	OC44-45 Germanium	PNP
5	TIS43-UT46 Unijunction Plastic	
2	2N3819 F.T.	
2	MEL11 Photo Transistor Plastic	
2	BD131 TO126 Plastic	NPN
2	BD132 TO126 Plastic	PNP

100 TOTAL

ALL devices - brand new and full spec as per device coding. Data and lead out details included in pak.
Normal Retail Value £23.00
Our Special Offer Price £15.00

Beginners Pak .no.2 - 100 Rectifiers, SCR's, Triacs, Diodes.

20	IN4001-IN4007 1 Amp Silicon Rectifier
20	IN5401-IN5407 3 Amp Silicon Rectifier
20	IN4148 Fast switch diodes Silicon
10	OA200 BAX13-16 General Purpose Diode Silicon
5	C106D Thyristor 400v TO202 Case
2	10Amp Triacs 400v TO220 Case Isolated Tab
2	4Amp Triacs 400v TO220 Case Non-Isolated Tab
10	Assorted 3Amp Thyristors 50-600 volts TO64-T066 Case
5	Assorted 1Amp Thyristors 50-600 volts TO39 Case
6	OA81-91 General Purpose Germanium Diodes

100 TOTAL

ALL devices brand new and full spec. Data and lead out details included.
Normal Retail Value £17.00
Our Special Offer Price £11.00

UNTESTED SEMICONDUCTOR PAKS

U1	150 germ Gold Bonded Diodes OA47	£1.00
U2	150 germ Point contact Diodes OA81	£1.00
U3	150 Silicon G.P. 200mA Diodes OA200	£1.00
U4	150 Silicon Fast Switch Diodes IN4148	£1.00
U5	25 Stud type Silicon Rectifiers up to 10A	£1.00
U6	10 SCR's 5Amp T066	£1.00
U7	40 Sil Trans NPN TO18 Case BC107/8/9	£1.00
U8	40 Sil Trans PNP TO18 Case BC177/8/9	£1.00
U9	40 Sil Trans NPN TO18 Case 2N706/8	£1.00
U10	40 Sil Trans NPN TO39 2N697/2N1711	£1.00
U11	40 Sil Trans PNP TO39 2N2905/1132	£1.00
U12	30 Sil Trans NPN TO39 BFY51-BC141	£1.00
U13	30 Sil Trans PNP TO39 BC160-161 etc	£1.00
U14	10 Sil Trans NPN TO3 2N3055	£1.00
U15	10 Sil Trans NPN TO220 TIP29-31 33	£1.00
U16	10 Sil Trans PNP TO220 TIP30-32 34	£1.00
U17	30 Sil Trans NPN TO39 High Vits. BF258/115	£1.00
U18	40 Sil Trans TO92 BC237/8	£1.00
U19	40 Sil Trans TO92 BC251	£1.00
U20	40 Sil Trans NPN TO92 BC183-4	£1.00
U21	40 Sil Trans PNP TO92 BC257 BC212L	£1.00


Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

ELECTROLYTIC PAKS

A range of paks each containing 25 first quality, mixed value miniature electrolytics.

EC1	Values from .47mFD - 10mFD	£1.00
EC2	Values from 10mFD - 100mFD	£1.00
EC3	Values from 100mFD - 1000mFD	£1.00

NEW SHAPE LEDs

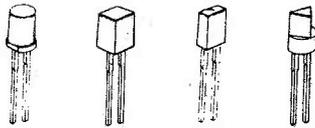

1561	£0.26	3mm Cylindrical LED Red
1562	£0.26	3mm Square LED Red
1563	£0.26	3mm Triangular LED Red
1564	£0.26	5mm Rectangular LED Red
1565	£0.26	5mm Cylindrical LED Red
1566	£0.26	5mm Square LED Red
1567	£0.26	5mm Triangular LED Red
1568	£0.28	3mm Cylindrical LED Green
1569	£0.28	3mm Square LED Green
1570	£0.28	3mm Triangular LED Green
1571	£0.28	5mm Rectangular LED Green
1572	£0.28	5mm Cylindrical LED Green
1573	£0.28	5mm Square LED Green
1574	£0.28	5mm Triangular LED Green
1575	£0.28	3mm Cylindrical LED Yellow
1576	£0.28	3mm Square LED Yellow
1577	£0.28	3mm Triangular LED Yellow
1578	£0.28	5mm Rectangular LED Yellow
1579	£0.28	5mm Cylindrical LED Yellow
1580	£0.28	5mm Square LED Yellow
1581	£0.28	5mm Triangular LED Yellow

CERAMIC PAKS

Containing a range of first quality miniature ceramic capacitors.

MC1	40 miniature ceramic capacitors: 5 of each value: 22pf, 27pf, 33pf, 39pf, 56pf, 68pf, 82pf.	£1.00
MC2	40 miniature ceramic capacitors: 5 of each value: 100pf, 120pf, 150pf, 180pf, 220pf, 270pf, 330pf, 390pf.	£1.00
MC3	40 miniature ceramic capacitors: 5 of each value: 470pf, 560pf, 680pf, 820pf, 1000pf, 1500pf, 2200pf, 3300pf.	£1.00
MC4	35 miniature ceramic capacitors: 5 of each value: 4700pf, 6800pf, .01uf, .015uf, .022uf, .033uf, .047uf.	£1.00

SPEAKERS AND CROSSOVERS

1901	Dome Tweeter 3 1/2" 8ohms 50w	£3.20
1902	Dome Tweeter 3" 8ohms 20w	£2.60
1903	Flared Horn Tweeter 8 ohms 30w	£3.80
1904	2 way crossover 15w 8ohms	£1.24
1905	2 way crossover 40w 8ohms	£2.70
1906	3 way crossover 60w 8ohms	£3.50
1907	Piezo Tweeter	£5.20
1914	70mm 8 ohm speaker	£1.20
1915	70mm 8 ohm speaker	£0.95
1916	56mm 8 ohm speaker	£0.65
1917	2 1/2" 8 ohm speaker	£0.75
1918	2 1/2" 64 ohm speaker	£0.82
1919	5 1/2" woofer 40hms 10w	£3.90
1920	5 1/2" woofer 80hms 10w	£3.90
1921	5 1/2" Dual cone wide range 8ohms	£5.80
1922	8" Dual cone long throw 8ohms 15w	£4.84
1923	8" woofer dual 4 plus 8ohms rubber edge 20w	£7.80

DIL SOCKETS:

1601	8 Pin 0.09	1605	20 Pin 0.20
1602	14 Pin 0.11	1606	22 Pin 0.24
1603	16 Pin 0.12	1607	24 Pin 0.28
1604	18 Pin 0.18	1608	28 Pin 0.32
		1609	40 Pin 0.36

LATE ADDITIONS - High Current Amps and switches

VCEO VCB0 IC Max			
BFT32	£0.60	60	3A
BFT33	£0.62	80	100 3A
BFT34	£0.65	100	120 3A
-BFT37	£0.95	100	120 3A
RPY76A			Infra Red Detector £0.65


POWER SUPPLIES

137	AC-DC Adaptor 6, 7, 9 & 12 volts	£3.50
138	DC-DC Adaptor 6, 7, 9 volts	£2.70

CABINETS

139	Teak 30 Case	£7.00
140	Teak 60 Case	£9.50

LED CLIPS AND HOUSINGS

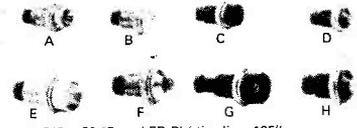

1548	£0.15	LED Plastic clips .125"
1549	£0.18	LED Plastic clips 2"
1550	£0.26	LED Housing (nickel plated) .125"
1551	£0.22	LED Housing (nickel plated) .125"
1552	£0.37	LED Housing (matt black) .125"
1553	£0.31	LED Housing (matt black) .125"
1554	£0.34	LED Housing (nickel plated) 2"
1555	£0.28	LED Housing (nickel plated) 2"
1556	£0.44	LED Housing (matt black) 2"
1557	£0.36	LED Housing (matt black) 2"

BULBS AND NEONS

1534	£0.24	LES Bulb 6v 0.36w
1535	£0.24	LES Bulb 6.5v 1w
1536	£0.24	LES Bulb 14v 0.75w
1538	£0.24	MES Bulb Round 6v .04A
1539	£0.20	MES Bulb Round 6.5v .15A
1540	£0.20	MES Bulb Round 6.5v .3A
1541	£0.20	MES Bulb Round 12.0v 1A
1542	£0.20	MES Bulb Round 12.0v 2.2w
1543	£0.34	Neon Red Round 240v
1544	£0.34	Neon Red Rectangular 240v
1545	£0.34	Neon Orange Rectangular 240v
1546	£0.34	Neon Green Rectangular 240v
1547	0.18	MES Batten Holder

CARBON FILM RESISTOR PAKS

These paks contain a range of Carbon Film Resistors, assorted into the following groups:

R1	80 Mixed jw 100ohms - 820ohms	£1.00
R2	80 Mixed jw 1Kohms - 8.2Kohms	£1.00
R3	80 Mixed jw 10Kohms - 82Kohms	£1.00
R4	80 Mixed jw 100Kohms - 1M	£1.00
R5	60 Mixed jw 100ohms - 820ohms	£1.00
R6	60 Mixed jw 1Kohms - 8.2Kohms	£1.00
R7	60 Mixed jw 10Kohms - 82Kohms	£1.00
R8	60 Mixed jw 100Kohms - 1M	£1.00

TANTALUM BEAD CAPACITORS

401	1.0uF	16v	0.11
402	0.22uF	16v	0.11
403	0.33uF	16v	0.11
404	0.47uF	16v	0.11
405	0.68uF	16v	0.11
406	1.0uF	16v	0.11
407	2.2uF	16v	0.12
408	3.3uF	16v	0.13
409	4.7uF	16v	0.14
410	6.8uF	16v	0.15
411	10.0uF	16v	0.16
412	22.0uF	16v	0.28
413	33.0uF	16v	0.50
414	47.0uF	16v	0.55
415	100.0uF	10v	0.55
416	.1uF	35v	0.12
417	.22uF	35v	0.12
418	.33uF	35v	0.12
419	.47uF	35v	0.12
420	.68uF	35v	0.12
421	1.0uF	35v	0.12
422	2.2uF	35v	0.13
423	3.3uF	35v	0.15
424	4.7uF	35v	0.18
425	6.8uF	35v	0.30
426	10.0uF	35v	0.38

FAIRCHILD/DARLINGTONS

TYPE	Pd	VCEO	VCB0	IC	HFE	CASE	£ p
2N6052	PNP	-100v	-100v	12A	750-18K	TO3	1.50
2N6282	PNP	-60v	-60v	20A	750-18K	TO3	1.25
MJ3000	PNP	60v	60v	10A	1KMN	TO3	1.00
SE9300	PNP	60v	60v	10A	1000	TO220	0.90
SE9311	PNP	80v	80v	10A	1000	TO220	0.95
SE9304	PNP	80v	80v	10A	1000	TO3	0.95
SE9305	PNP	100v	100v	10A	1000	TO3	1.00
SE9401	PNP	-80v	-80v	10A	1000	TO220	1.10
TIP115	PNP	-60v	-60v	2A	1K	TO220	0.40
TIP117	PNP	-100v	-100v	2A	1K	TO220	0.50
TIP120	PNP	60v	60v	5A	1K	TO220	0.60
TIP121	PNP	80v	80v	5A	1K	TO220	0.65
TIP122	PNP	100v	100v	5A	1K	TO220	0.68
TIP126	PNP	-80v	-80v	5A	1K	TO220	0.70
TIP127	PNP	-100v	-100v	5A	1K	TO220	0.72

Access and Barclaycards accepted - just telephone our Orderline - Ware (STD 0920) 3182.

All prices exclude V.A.T., add 50p. postage per order. Terms: C.W.O., cheques.

Postal Orders payable to Bi-Pak at address below.

BI-PAK


SEMICONDUCTORS

Dept. RC4 P.O. BOX 6, WARE, HERTS.

Tel: Ware (STD 0920) 3442. Telex: 817861.

Giro No. 3887006

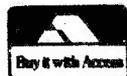Visit our shop at: 3, Baldock St, Ware, Herts.



THREE FOR FREE FROM GSC



Electronics by Numbers
Projects No 10, No 11, No 12

Available from selected stockists ELECTRONICS BY NUMBERS

No. 10 SOIL MOISTURE TESTER

No more wilting houseplants with this soil moisture test. Just place the probes into the soil and it will light up to tell you whether the soil is "too wet" or "too dry". You don't even need green fingers.


No. 11 DIGITAL ROULETTE

The suspense and excitement of the casino in your own home. Just press the button, the circle of lights go round and there is the sound of the roulette wheel as well, both gradually slowing down to reveal the winning number.

No. 12 EGG TIMER

How do you like your eggs done, hard or soft, just set the timer and it will sound when the egg is done to your liking. Long battery life because it switches itself off automatically. So get cracking now!

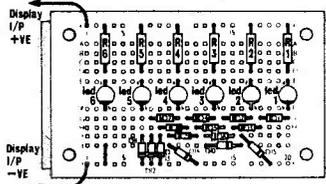Want to get started on building exciting projects, but don't know how? Now using EXPERIMENTOR BREADBOARDS and following the instructions in our FREE 'Electronics By Numbers' leaflets, ANYBODY can build electronic projects. For example, take one of our earlier projects, a L.E.D. Bar Graph;



You will need: One EXP 300 or EXP 350 breadboard 15 silicon diodes 6 resistors 6 Light Emitting Diodes Just look at the diagram, Select R1, plug it into the lettered and numbered holes on the EXPERIMENTOR BREADBOARD, do the same with all the other components, connect to the battery, and your project's finished. All you have to do is follow the large, clear layouts on the 'Electronics by Numbers' leaflets, and ANYBODY can build a perfect working project.

EXPERIMENTOR BREADBOARDS

No soldering modular breadboards, simply plug components in and out of letter number identified nickel-silver contact holes. Start small and simply snap-lock boards together to build a breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board, if you need more than 2 buses simply snap on 4 more bus-bars with the aid of an EXP 4B.

EXP 325 £1.60 The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22 pin ICs. Has 130 contact points including two 10 point bus-bars.



EXP 350 £3.15 Specially designed for working with up to 40 pin ICs perfect for 3 & 14 pin ICs. Has 270 contact points including two 20 point bus-bars.



EXP 300 £5.75 The most widely bought bread-board in the UK. With 550 contact points, two 40 point bus-bars, the EXP 300 will accept any size IC and up to 6 x 14 pin DIPS. Use this breadboard with Adventures in Microelectronics.



EXP 600 £6.30 Most MICROPROCESSOR projects in magazines and educational books are built on the EXP 600.



EXP 650 £3.60 Has '6" centre spacing so is perfect for MICROPROCESSOR applications.



EXP 4B £2.30 Four more bus-bars in "snap-on" unit.



The above prices are exclusive of P&P and 15% VAT.

THE GSC 24 HOUR SERVICE TELEPHONE (0799) 21682

With your Access, American Express, Barclaycard number and your order will be in the post immediately
GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Ltd, Dept. 16TT
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21662
Telex: 817477

For full detailed instructions and layouts of Projects 10, 11 and 12, simply take the coupon to your nearest GSC stockist, or send direct to us, and you will receive the latest 'ELECTRONICS BY NUMBERS' leaflet.

If you have missed projects, 1, 2 and 3, or 4, 5 and 6, or 7, 8 and 9, please tick the appropriate box in the coupon.


PROTO-BOARDS

The ultimate in breadboards for the minimum of cost. Two easily assembled kits.



PB6 Kit, 630 contacts, four 5-way binding posts accepts up to six 14-pin Dips.

PROTO-BOARD 6 KIT £9.20

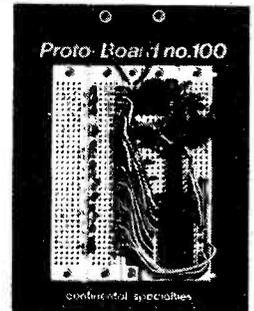

PB 100 Kit complete with 760 contacts accepts up to ten 14-pin Dips, with two binding posts and sturdy base. Large capacity with Kit economy.

PROTO-BOARD 100 KIT £11.80

IT'S EASY WITH G.S.C.

TO RECEIVE YOUR FREE COPY OF PROJECTS 7, 8 and 9

Just clip the coupon

Give us your name and full postal address (in block capitals). Enclose cheque, postal order or credit card number and expiry date, indicating in the appropriate box(es) the breadboard(s) you require.

For immediate action

The GSC 24 hour, 5 day a week service. Telephone (0799) 21682 and give us your Access, American Express or Barclaycard number and your order will be in the post immediately.

EXPERIMENTOR BREADBOARDS	CONTACT	IC CAPACITY 14 PIN.DIP.	UNIT PRICE INC. P&P & 15% VAT	Qty req.
EXP 325	130	1	£ 2.70	
EXP 350	270	3	£ 4.48	
EXP 300	550	6	£ 7.76	
EXP 600			£ 8.39	
EXP 650	270	use with 0.6 pitch Dip's Strip Bus-Bar	£ 5.00	
EXP 4B	Four 40 Point Bus-Bars		£ 3.50	
PROTO-BOARDS				
PB6	630	6	£11.73	
PB100	760	10	£14.72	

NAME

ADDRESS


I enclose cheque/P.O. for £.....
Debit my Barclaycard, Access,
American Express card No.
..... Expiry date

If you missed project No's 1 to 9 tick box.

For Free catalogue tick box

GSC (UK) Ltd., Dept. 16TT, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682. Telex: 817477.

LATEST BOUND VOLUME No. 33.

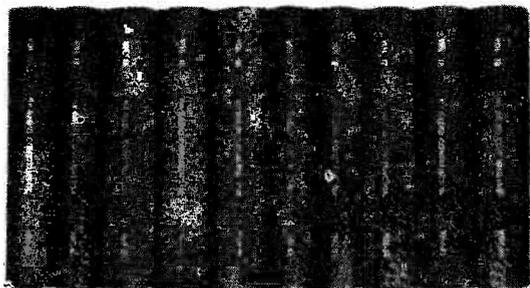

of "Radio & Electronics Constructor"

Comprising
752 pages
inc. index

SEPTEMBER 1979
to AUGUST 1980

PRICE £6.20 P&P £1.50

BOUND VOLUME No. 27 (August 1973 to July 1974)
BOUND VOLUME No. 28 (August 1974 to July 1975)
BOUND VOLUME No. 29 (August 1975 to July 1976)
BOUND VOLUME No. 30 (August 1976 to July 1977)
BOUND VOLUME No. 31 (August 1977 to August 1978)
BOUND VOLUME No. 32 (September 1978 to August 1979)

PRICE £3.00 p&p £1.50
PRICE £3.20 p&p £1.50
PRICE £3.50 p&p £1.50
PRICE £3.70 p&p £1.50
PRICE £5.20 p&p £1.50
PRICE £5.20 p&p £1.50

We regret all other volumes are now completely sold out.


Available only from:

DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON W9 1SN

RX 80 MkII - A DIY SOLID-STATE-OF-THE-ART MODULAR DUAL CONVERSION RECEIVER SYSTEM FOR THE ENTHUSIAST

AS DESCRIBED IN JAN/FEB/MAR 81 RADCOM BY TONY BAILEY-G3WPO : REPRINTS £1 inc

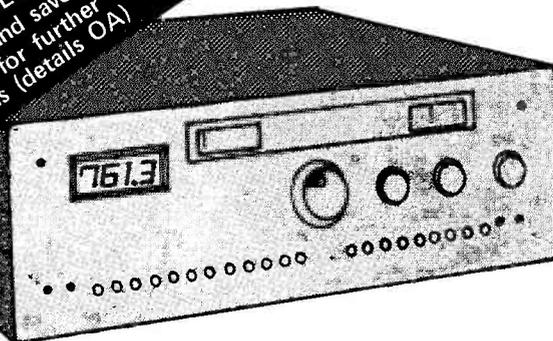CLUBS & COLLEGES:
Buy 5 kits and save 10%
Buy more for further
reductions (details OA)



- ★ LOW DRIFT VARICAP TUNING (READILY ADAPTABLE FOR SYNTHESISED/ HUFF&PUFF STABILIZATION)
- ★ DUAL CONVERSION BASED ON A 3-4 MHz SSB IF, WITH MECHANICAL IF FILTER, AUDIO DERIVED AGC, BALANCED MIXER, WITH ON-BOARD AF AMP AND VOLTAGE REGULATOR
- ★ CAPACITY FOR UP TO 12HF/VHF/UHF 1 MHz WIDE CRYSTAL CONTROLLED CONVERTERS WITH TRACKED RF TUNING
- ★ EACH CONVERTER SELF CONTAINED - SO MORE CAN BE USED EXTERNALLY IF REQUIRED. RF PATHS ARE DC SWITCHED AT LOW IMPEDANCE

PRICES

RX 80 Mk II tuneable 3-4MHz SSB receiver/IF with MFL series
2.4kHz mechanical SSB IF filter ..£42.66
A/A but with low cost 4kHz CFM2 series filter ..£32.42
HF Converters, including crystal for the following bands:
1-2MHz, 7-8MHz, 10-11MHz, 14-15MHz, 18-19MHz, 21-22MHz
24-25MHz, 28-29MHz, 29-30MHz ..£9.10 ea
Hardware: Case, meters, pots, knobs (exc. DFM) ..£25.00
Complete RX 80, 6 converters, switches, case, PSU ..£132.50

CURRENT OPTIONS INCLUDE

- ★ LCD DFM with built in IF offset, interface PCB ..£23.75
- ★ HUFF/PUFF vfo stabilizer ..£9.60
- ★ NBFM adapter inc 8kHz multielement ceramic IF filter ..£9.95
- ★ Constant Z PIN diode attenuator ..£4.95
- ★ 12v low RF noise mains PSU ..£7.95

PLANNED ADDITIONS TO THE SYSTEM

- 3-4MHz IF frequency synthesiser
- 'UP Conversion' front end system
- AM IF adapter ■ Noise blanker
- VHF/UHF converters with helical filters



PRICES EXCLUDE VAT (15%). Postage 50p on orders under £12. Free postage on orders over £12, except please note any order including HARDWARE should be accompanied with a £2 carriage charge. General price lists are available FOC with an SAE - full AMBIT catalogues including a multitude of radio parts/components £1.80 a set - or 70p per section.


AMBIT international 200 North Service Road, Brentwood, Essex

TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG


LINEAR ICS	LINEAR ICS	LINEAR ICS	LINEAR ICS	4000 series	4000 series	TTL	'N'	'LPSN'	TTL	'N'	'LPSN'	TTL	'N'	'LPSN'	TTL	'N'	'LPSN'	MICROMARKET	LEDS	LEDS		
LB120S	1.00	SL1610P	1.60	HA11223	2.15	4000	0.18	4068	0.25	TTL	'N'	'LSN'	TTL	'N'	'LSN'	TTL	'N'	'LSN'	8224	3.50	STD DOMED TYPES	
T200	1.95	SL1611P	1.60	HA11225	1.45	4001	0.18	4069	0.25	7400	0.13	0.20	7454	0.20	0.30	74128	0.74	74194	1.05	6.25	5mm RED 12p	
U2378	1.28	SL1612P	1.60	HA12002	1.45	4002	0.24	4070	0.30	7401	0.13	0.20	7455		0.30	74132	0.73	74196	1.34	5.40	3mm RED clr 15p	
U2478	1.28	SL1613P	1.99	HA12017	0.80	4007	0.30	4071	0.24	7402	0.14	0.20	7460	0.20		74136		74197	1.10	7.50	3mm RED 15p	
U2578	1.28	SL1620P	2.17	HA12402	1.95	4008	0.80	4072	0.80	7403	0.14	0.20	7463		1.24	74138		74198	1.80	6.810	5.95	5mm RED 17p
U2678	1.28	SL1621P	2.17	HA12411	1.20	4008AE	0.80	4073	0.24	7404	0.14	0.24	7470	0.40		74138		74198	1.80	6.820	7.45	5mm GRN 15p
LM301H	0.67	SL1623P	2.44	HA12412	1.55	4009	0.58	4075	0.25	7405	0.18	0.26	7472	0.30		74141	0.75	74198	1.60	6.850	4.90	3mm GRN clr 16p
LM301N	0.30	SL624C	3.28	LS13741	0.33	4010	0.58	4076	0.90	7406	0.36		7473	0.35	0.45	74143	3.12	74257		6.852	4.85	3mm GRN 16p
LM308TC	0.65	SL1625P	2.17	SN78660N	0.30	4011AE	0.24	4077	0.35	7407	0.38		7474	0.35	0.35	74145		74260		6.852	4.85	3mm GRN 16p
LM324	0.64	SL1626P	2.44			4011B	0.24	4078	0.30	7408	0.18	0.24	7476	0.56		74145		74260		6.852	4.85	3mm GRN 16p
LM339N	0.66	SL1630P	1.62	FREQ. DISPLAY		4012	0.55	4082	0.28	7409	0.21	0.24	7478	0.41	0.45	74148	1.75	74267		6.852	4.85	3mm GRN 16p
LM348N	1.86	SL1840P	1.89	AND SYNTH.		4013	0.55	4093	0.86	7410	0.18	0.24	7478	0.56		74148	1.09	74267		6.852	4.85	3mm GRN 16p
LF351N	0.48	SL1841P	1.89	DEVICES		4014	0.95	4175	1.15	7411	0.26	0.32	7478	0.56		74148	1.09	74267		6.852	4.85	3mm GRN 16p
LF353N	0.76	TDA2002	1.25	SA11056	3.75	4016	0.52	4503	1.15	7411	0.26	0.32	7478	0.56		74148	1.09	74267		6.852	4.85	3mm GRN 16p
LM374N	1.35	ULN2242A	3.05	SA11058	3.35	4017	0.80	4506	0.68	7413	0.32		7480	0.52		74150	0.99	74365		6.852	4.85	3mm GRN 16p
LM390N-14	1.00	ULN2283B	1.00	SA11059	3.35	4019	0.90	4510	0.99	7414	0.51		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
LM390N-8	1.00	CA3089E	0.70	11C90DD	14.00	4021	0.98	4511	1.49	7415	0.30	0.40	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
LM398N	1.21	CA3089E	1.84	LM1232	19.00	4021	0.82	4512	0.98	7416	0.30		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
ZM419CE	1.98	CA3090AQ	3.35	LM1242	19.00	4022	0.96	4514	2.55	7417	0.30		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
NE544N	1.80	CA3123E	1.40	MSL2318	3.84	4023	0.25	4518	1.03	7420	0.19	0.24	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
NE555N	0.30	CA3130E	0.80	MSM5523	11.30	4024	0.76	4520	1.09	7421	0.38	0.24	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
NE565N	0.50	CA3130T	0.90	MSM5524	11.30	4025	0.25	4521	2.36	7422	0.27		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
NE568N	0.50	CA3140E	0.46	MSM5525	7.85	4026	1.80	4522	1.49	7423	0.27		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
NE562N	4.05	CA3189E	2.20	MSM5526	7.85	4028	0.79	4529	1.61	7427	0.32	0.35	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
NE564N	4.25	CA3240	1.27	MSM5527	9.75	4029	1.04	4539	1.28	7428	0.35	0.35	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
NE565N	1.00	MC357P	2.85	MSM55271	9.75	4030	0.59	4549	3.50	7430	0.17	0.26	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
NE566N	1.80	LM3900N	0.60	MSL2312	3.94	4035	1.20	4564	1.73	7432	0.32	0.28	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
NE570N	3.85	LM3909N	0.68	SP8629	3.85	4040	0.93	4569	3.03	7441	0.74		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
SL624	3.28	LM3914AN	2.80	SP8647	6.00	4042	0.85	4566	1.59	7438	0.33	0.35	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
TB6851	1.81	LM3915N	2.80	98H09PC	7.90	4043	0.85	4568	2.18	7440	0.20	0.28	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
UA709HC	0.64	KB4400	0.80	HD10551	2.45	4043AE	0.93	4569	3.03	7441	0.74		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
UA709PC	0.65	KB4406	0.60	HD44015	4.45	4044	0.94	4572	3.00	7442	0.70	0.99	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
UA710HC	0.46	KB4412	1.85	HD12009	6.00	4046	1.30	4585	1.00	7443	1.15		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
UA710PC	0.59	KB4413	1.85	HD44752	8.00	4047	0.99			7444	1.12		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
UA741CH	0.65	KB4417	1.85	MC145151	12.45	4048	0.52			7445	1.05		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
UA741CN	0.27	KB4420B	1.09	MC145156	8.75	4051	0.55			7446	1.32		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
UA747CN	0.70	TDA4420	2.65			4051	0.78			7447	0.89		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
UA748CN	0.36	KB4423	2.30	M15C	4.05	4052	0.79			7448	0.56		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
UA753	2.44	KB4424	1.95	ICM7107CP	9.55	4053	0.78			7449	0.99		7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
UA758	2.35	KB4430	1.85	ICM72168P	19.50	4063	1.18			7453	0.20	0.25	7481	1.20		74151	0.95	74365		6.852	4.85	3mm GRN 16p
TB820M	0.78	KB4432	1.95	ICM7555	0.94	4066	0.57															
TC9A90E	1.80	KB4433	1.52																			
TDA1028	2.11	KB4436	2.53																			
TDA1029	2.11	KB4437	1.74																			
TDA1054	1.45	KB4438	2.22	32.76KHz	2.70	10.245	2.00															
TDA1062	1.95	KB4441	1.35	100KHz	3.85	10.6985	2.50															
TDA1072	2.69	KB4445	1.29	455KHz	5.00	10.700	2.00															
TDA1074A	5.04	KB4446	2.75	1.00MHz	2.75	10.7015	2.50															
TDA1083	1.60	KB4448	1.95	3.2768	2.70	11.011	2.00															
TDA1090	3.05	NE5044N	2.26	4.000	2.00	11.115	2.00															
HA1137	1.20	NE5532N	1.85	4.1934	2.00	11.520	2.00															
HA1196	2.00	SD6000	3.75	4.096	2.00	8.9985	2.50															
HA1197	1.00	SL6270	2.03	4.032	2.00	2.00	2.00															
TDA1220	1.40	SL6310	2.03	4.433619	2.00	21.000	2.00															
LM1303	0.99	SL6600	3.75	4.800	2.00	24.000	2.00															
LM1307	1.55	SL6640	2.75	5.000	2.00	25.000	2.00															
MC1310P	1.90	SL6440	3.00	6.000	2.00	26.000	2.00															
MC1330	1.95	MSL9363	3.70	7.000																		

DIRECT SUPPLY SERVICE TO READERS

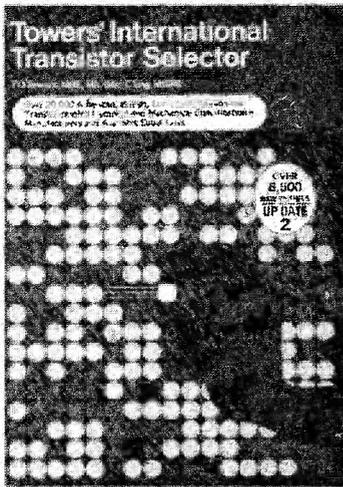TOWERS INTERNATIONAL TRANSISTOR SELECTOR (NEW REVISED EDITION)



This is dead! 
Would this replace it?

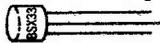


If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. It's one of the most useful working books you will be offered this year. And probably the cheapest!

In it, you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price **£10-70** inc P&P

TOWERS INTERNATIONAL FET SELECTOR

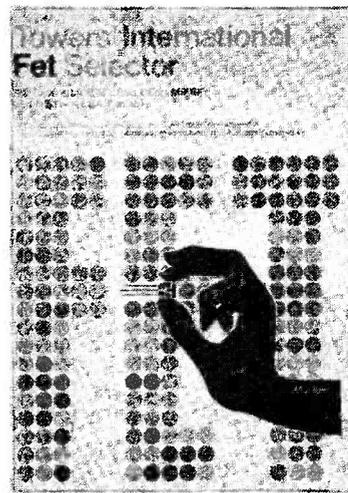

If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price **£4-60** inc P&P

(Please allow 21 days for delivery)

Tower's International Transistor Selector by **T. D. Towers**
MBE, MA, BSc, C Eng, MIERE
£10-70
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

.

.

. (Block capitals)

Tower's International FET Selector by **T. D. TOWERS**
MBE, MA, BSc, C Eng, MIERE
£4-60
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

.

.

. (Block capitals)

OSCILLOSCOPES

How to use them - How they work - by Ian Hickman

Oscilloscopes are essential tools for checking circuit operation and diagnosing faults, and an enormous range of models is available. But which is the right scope for a particular application? Which features are essential, which not so important? What techniques will get the best out of the instrument?

Ian Hickman, experienced in both professional and hobbyist electronics, has written this book to help all oscilloscope users - and potential users. After introducing basic principles for readers new to the subject, he explains in detail the features of typical simple and advanced real-time oscilloscopes, plus accessories such as probes and cameras. He advises on how to choose and operate scopes, and how to avoid common pitfalls; he also describes special-purpose instruments, from small portable scopes to storage scopes and spectrum and logic analysers. Finally, to give readers a better understanding of how oscilloscopes work, he explains the principles of the cathode-ray tube and basic scope circuitry.

**NEW
BOOK**

Illustrated with many photographs and two-colour diagrams, the book will appeal to everyone who needs to know about oscilloscopes, from the school student to the graduate, from the hobbyist to the technician.

Available from your local bookseller or in case of difficulty from the Publisher.

BROADEN YOUR SCOPE NOW!

Cut out this coupon and return it to Patricia Davies, Marketing Manager, at the address below.

Please send me copy/copies of Oscilloscopes (Hickman) 0 408 00472 X illustrated paperback 216 x 318mm 128 pages @ £3.45 each.

I enclose a cheque/PO for £..... in total payment

From

Address

.....

.....

.....

(REC 4/81)

Newnes Technical Books
Borough Green, Sevenoaks, Kent TN15 8PH

Conquer the chip.

Be it a career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

MASTER ELECTRONICS LEARN THE PRACTICAL WAY BY SEEING AND DOING

- Building an oscilloscope. ● Recognition of components.
- Understanding circuit diagrams. ● Handling all types Solid State 'Chips'.
- Carry out over 40 experiments on basic circuits and on digital electronics.
- Testing and servicing of Radio, T.V., Hi-Fi and all types of modern computerised equipment.


MASTER COMPUTERS

LEARN HOW TO REALLY UNDERSTAND COMPUTERS, HOW THEY WORK - THEIR 'LANGUAGE' AND HOW TO DO PROGRAMS.

- Complete Home Study library. ● Special educational Mini-Computer supplied ready for use. ● Self Test program exercise.
- Services of skilled tutor available.

MASTER THE REST

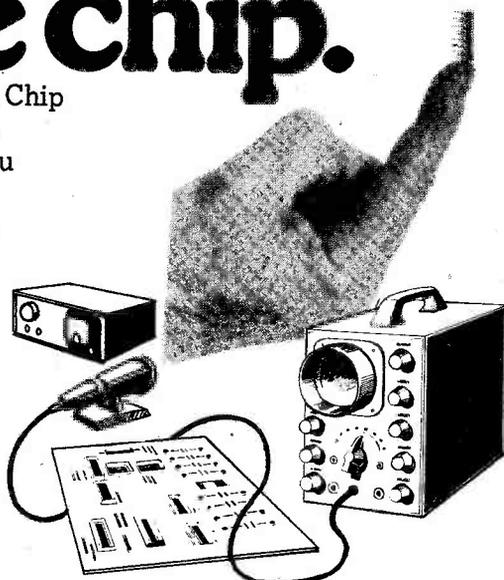- Radio Amateurs Licence. ● Logic/Digital techniques.
- Examination courses (City & Guilds etc.) in electronics.
- Semi-conductor technology.
- Kits for Signal Generators - Digital Meters etc.



FREE	Please send your FREE brochure without obligation to: REC/4/813	I am interested in --
	Name	PRACTICAL ELECTRONICS
	Address	COMPUTER TECHNOLOGY
	OTHER SUBJECTS
BLOCK CAPS PLEASE		(please state your interest)
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL		
4 CLEVELAND ROAD, JERSEY, CHANNEL ISLANDS.		

TRANSISTORS

BCY11	28p	BCY31 64v 6w	12p
AC122 30v 2w	12p	BCY56	10p
AC126 30v 2w	16p	BCY70 50v 35w	9p
AC127 32v 3wt	16p	BCY71 45v 35w	9p
AC128 36v 1wt	5p	BCY72 25v 3w	9p
AC153	11p	BCY79B 45v 3w	15p
AC176 32v 7w	11p	BD115	32p
AC179 20v 1.1w	40p	BD113	57p
AC188 25v 1w	10p	BD115	35p
ACY20 40v 3w	30p	BD(BRC)116	35p
ACY21 40v 3w	20p	BD131 45v 15w	15p
ACY28	22p	BD132 45v 15w	15p
AD161 20v 6wt	40p	BD133 90v 15w	28p
AD162 20v 6wt	40p	BD135 45v 13w	22p
AD164 25v 6w	40p	BD136 45v 13w	14p
AD165 25v 6w	40p	BD137 60v 8w	28p
AF119	35p	BD137/8 mtch pr	60p
AF124	27p	BD140 80v 8w	26p
AF126	27p	BD142	35p
AF127	27p	BD145	55p
AF139 22v 1w	23p	BD182 70v 117w	44p
AF178	35p	BD201 45v 60w	86p
AF180	35p	BD202 45v 60w	64p
AF181	33p	BD203 60v 60w	86p
AF239 20v 1w	35p	BD204 60v 60w	86p
ALZ10 50v 5w	37p	BD232 500v 15w	34p
ASV50	35p	BD233 45v 25w	20p
ASV63	35p	BD235 60v 25w	35p
ASV73	35p	BD238 80v 25w	25p
ASZ21	4p	BD239C	29p
AU110	£1.43	BD240	30p
AU113	£1.03	BD241 45v 40w	22p
AU110	70p	BD242B 90v 40w	30p
BC107A/B	7p	BD245	32p
BC108A/B/C	7p	BD253	32p
BC109/B/30v	7p	BD375	35p
BC125 50v 3w	7p	BD437 45v 36w	35p
BC125B 60v 3w	4p	BD438 45v 36w	28p
BC129A/B 50v 2w	7p	BD597 60v 55w	36p
BC130A/C 25v 2w	7p	BD677 60v 40w	50p
BC131C 25v 2w	7p	BD678 Pwr. Darl.	50p
BC139 40v 7w	11p	BDX33B Pwr. Darl.	44p
BC140 40v 7w	15p	BDX42 60v Darl.	36p
BC141 60v 7w	11p	BDX77 80v 60w	51p
BC143 60v 8w	11p	BDY20 60v 117w	86p
BC147A/B/C	51p	BF115 50v 2w	18p
BC148A/B/C	51p	BF137	11p
BC149A/B/C/S	51p	BF167 30v 15w	18p
BC154 40v 2w	7p	BF173 25v 2w	18p
BC157A 50v 4w	51p	BF178	23p
BC158A/B	51p	BF179	23p
BC159B/C	51p	BF180 30v 2w	12p
BC160/10 40v 3.2w	12p	BF181 30v 2w	8p
BC168B 20v 3w	71p	BF182	18p
BC171B	4p	BF183	18p
BC172	4p	BF184 20v 15w	18p
BC172c	71p	BF185 20v 15w	18p
BC173	4p	BF194A/B	51p
BC177A 45v 4w	101p	BF195/C/AM	51p
BC178A/B/C	101p	BF196/C/FM	51p
BC179B 20v 3w	14p	BF197 20v VHF	51p
BC182/AL 50v 3w	51p	BF198 30v 3w	51p
BC182L 50v 3w	3p	BF200 30v 2w	13p
BC183A/AL/LC	3p	BF224	4p
BC184	5p	BF244C FET 30v	71p
BC186	21p	BF245 FET	6p
BC187	8p	BF256FET	8p
BC196A 30v 50mw	100 for £3.65p	BF256B/LC FET	6p
BC196B 30v 50mw	100 for £3.65p	BF257 160v 5w	20p
BC197A 50v 50mw	4p	BF259 see 2N5058	29p
BC198B 30v 50mw	100 for £3.65p	BF262	29p
BC204 50v 3w	11p	BF263	29p
BC212B 50v 3w	5p	BF274	8p
BC213L 45v 3w	5p	BF324 30v 3w	31p
BC213LA 45v 3w	5p	BF336 185v 3w	15p
BC213LB 45v 3w	4p	BF355 300v 3w	15p
BC214L 45v 3w	5p	BF394B	3p
BC214L 45v 3w	31p	BF451 40v 3w	6p
BC237A 45v 3w	71p	BF494 20v 3w	10p
BC237B 50v 3w	71p	BF495 20v 3w	5p
BC238 20v 3w	5p	BF595c FM/AM/GP	91p
BC238B/C	71p	BF615	27p
BC239C 20v 3w	71p	BF617	27p
BC251	3p	BFQ35	15p
BC257B	71p	BFQ37	16p
BC258B/C	71p	BFR34A 12v 2w	£1
BC259C	15p	BFR38	68p
BC304	15p	BFR86	19p
BC307 45v 3w	7p	BFS21 FET pair	£3
BC308B/C 25v 3w	71p	BFS28 DualM/Fet	50p
BC309B 20v 3w	71p	BFT30	15p
BC327 45v 7w	5p	BFT39	15p
BC328 25v 7w	6p	BFT41	15p
BC337 45v 7w	6p	BFT60	6p
BC382L	71p	BFT61	15p
BC384B	71p	BFT70	15p
BC546 80v 6w	5p	BFT71	15p
BC547/A/B 45v	5p	BFW10 FET 30v	46p
BC548A/B/C	5p	BFW11 FET 30v	46p
BC549C 30v 5w	5p	BFW30 20v 25w	15p
BC556 80v 5w	5p	BFW31	15p
BC557/B	5p	BFW57	18p
BC558A 30v 5w	5p	BFW58	18p
BC559 30v 5w	5p	BFX12	23p
BC612L	4p	BFX29 60v 6w	11p
BCX32	10p	BFX30 60v 8w	16p
BCX33 60v .75w	10p	BFX37 60v 4w	16p
BCX34	10p	BFX48 100v 8w	20p
BCX36 60v 1.5w	10p	BFX85 100v 8w	14p
		BFX88 40v 6w	20p
		BFX89 30v 2w	20p
		BFY39	20p
		BFY50 25v 1wt	15p
		BFY51 60v 1w	15p
		BFY52 40v 1w	15p

BEY75	15p	P77 Plastic 10wt	15p
BFY90 30v 2w	5p	P346A	24p
BL101	23p	P7029	30p
BR110	20p	PXB103	25p
BR393	23p	RCP701A/B/D 10wt	30p
BRV56	29p	R1039J2010	54p
BSV60 45v 8w	30p	R2008B 660v 85w	£1.18
BSV64 100v 1w	36p	R2010B	£1.18
BSV79 40v 4w	50p	R2306 100v 40w	26p
BSV80 40v 4w	50p	R2540	£1.70
BSV81 Dep. Mos Fet	75p	S3017	25p
BSX19 40v 4w	50p	S240	26p
BSX20 40v 4w	7p	SBT37	26p
BSX21 120v 3w	10p	SL102	40p
BSY48	8p	TE886	£1
BSY49	8p	TIP29 40v 30w	22p
BSY95A 20v 3w	10p	TIP30 40v 30w	22p
BU105 1k5v 10w	64p	TIP30C 100v 30w	26p
BU105/04	78p	TIP31C 100v 40w	26p
BU204 1k3v 10w	75p	TIP32A 100v 40w	22p
BU208 1k5v 12w	£1.05	TIP32C 100v 40w	26p
		TIP41 40v 65w	15p
		TIP42C 100v 65w	33p
		TIP48 300v 40w	33p
		TIP 110 60v 50w Darl.	30p
		TIP112 100v 50w	45p
		TIP115 60v 50wt	22p
		TIP2955 100v 90w 45p	30p
		TIP3055 100v 90w 34p	30p
		TIS44 VHF switch	91p
		TIS60GY	9p
		TIS61	9p
		TIS619	3p
		TIS73L FET	7p
		TIS90	4p
		TIS91	6p
		TIS92GY	14p
		TIS98	3p
		TK24	20p
		V435	20p
		U14710	20p
		ZT403P	30p
		ZT1486	£1.10
		ZTX341	9p
		ZG103	33p
		ZG302	12p
		ZG309	30p
		ZG339A	20p
		ZG371	12p
		ZN388	71p
		ZN456A	71p
		ZN525 45v 3w	12p
		ZN527 45v 2w	12p
		ZN597	16p
		ZN598	16p
		ZN601	£1.50
		ZN644	27p
		ZN698 120v 8w	12p
		ZN699 120v 6w	12p
		ZN706A 25v 3w	101p
		ZN708 40v 4w	9p
		ZN718 60v 4w	10p
		ZN720A 120v 5w	12p
		ZN720 120v 5w	12p
		ZN736 80v 5w	71p
		ZN914	15p
		ZN918 15v 2w	12p
		ZN929 45v 3w	16p
		ZN930 45v 3w	7p
		ZN984	28p
		ZN987	45p
		ZN1091	16p
		ZN1132	23p
		ZN1132 25v 2w	16p
		ZN1303 30v 2w	16p
		ZN1395	28p
		ZN1484	36p
		ZN1485 60v 25w	36p
		ZN1487	90p
		ZN1490	90p
		ZN1500	30p
		ZN1507	18p
		ZN1711 75v 8w	13p
		ZN1716	15p
		ZN1724A 118wt RF 180v	£2.10
		ZN1748	28p
		ZN2192A	15p
		ZN2221A 40v 5w	9p
		ZN2222A 40v 5w	9p
		ZN2369 40v 4w	10p
		ZN2401	71p
		ZN2412	27p
		ZN2483	28p
		ZN2484 60v 4w	10p
		ZN2586	15p
		ZN2614	4p
		ZN2887	£2
		ZN2894	11p
		ZN2904 60v 6w	9p
		ZN2905 60v 6w	15p
		ZN2906 60v 4w	9p
		ZN2907A 60v 4w	9p
		ZN2926Y 25v 2w	9p
		ZN2926Z 25v 2w	9p
		ZN2926R 25v 2w	4p
		ZN3020 140v 8w 25p	41p
		ZN3054 90v 30w	35p
		ZN3055RCA 100v 115wt	68p

2N3133	24p	2SA12	42p
2N3283	25p	2SA50	36p
2N3645	30p	2SA80	36p
2N3418	15p	2SA83	36p
2N3442 160v 117w	75p	2SA141	36p
2N3583	30p	2SA142	36p
2N3663 30v 2w	6p	2SA234	50p
2N3702 40v 4w	4p	2SA236	50p
2N3703 50v 3w	3p	2SA354	34p
2N3704 50v 4w	4p	2SA360	38p
2N3707 30v 3w	4p	2SA367	38p
2N3714 80v 150w	54p	2SA518	59p
2N3794	14p	2SB77	20p
2N3799	18p	2SB135	25p
2N3823 FET 30v	25p	2SB136	25p
2N3904 60v 3w	71p	2SB156	60p
2N3905 40v 3w	71p	2SB175	20p
2N3906 40v 3w	8p	2SB176	20p
2N4000	15p	2SB187	25p
2N4026	15p	2SB457	25p
2N4031 80v 1w	15p	2SC1061 50v 25w	50p
2N4039 MOSFET	54p	2SD234 60v 25w	50p
2N4062 30v 4w	4p	2SD315D	80p
2N4285	17p	2SD34 40v 5wt	22p
2N4403 40v 3w	71p	382-A 300v 6wt A/F	30p
2N4891	30p	Video Amp (BF459)	30p
2N4918	15p	868-01 Plast. 10wt	15p
2N5058 300v 5w	11p	10	

PRICES SO LOW, THE POLICE INVESTIGATED ME TWICE

VAT & POST PAID

UK - Postal Orders for prompt service. Cheques require 9 days from a Monday banking to ensure clearance. Export - banker's draft (sterling) prompt service. Foreign currency not accepted. VAT content becomes documentation charge. Add additional postage for overseas mail.

OPTO ELECTRONICS
 Photo Diodes: 30F2, 31F2, 32F2, 33F2, BPX40, BPY10, BPY68, BPY69, BPY77, CQY17, CQY77, All types 38p
 Wire and neons 5p
 Photo transistors: BPX43, BP103, 2N5777, Darlington, 36p. LED's (Mullard Siemens) Red 5mm 8p, 3mm 13p; Green 5mm 13p, 3mm 13p; Micro Yellow LD481 7p.
PHOTO SILICON CONTROLLED SWITCH BPX66 PNP N 10 amp 36p.
 CA3062 Photo Detector and power amp. £1.05p

7 SEGMENT L.E.D. DISPLAYS
 3" Red com. anode 81p
 6" Green C.A. £1.77
 5082-7650 Red com. anode.
 5082-7653 Red com. cath
 5082-7600 Yellow com. anode.
 H.P. Highbrilliance .43" 72p

HEWLETT PACKARD MULTIPLEXED 12" 7 SEGMENT LED DISPLAYS
 3 Digit HP5082 7413 45p
 4 Digit HP 5082 7414 45p
 5 Digit HP 5082 7415 45p
 Infra red transmit diodes CQY11B or LD271 High power 1.6-2v or 3-3.5v Pulse 32p
 LD242 36p
 H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p
 CNY17/1 opto coupler 70p
 Cold cathode tubes I.T.T. G517A or 5870L 60p

SPECIAL OFFER
 IN4004 or IN4006 Sealed manufacturers carton of 300. £6.85

I. C. SOCKETS
 Low Profile
 8 Dii 9p
 14 Dii/Q 8p
 16 Dii 11p
 16 Dii/Q 10p
 22 Dii 20p
 24 Dii 29p
 28 Dii 29p
 40 Dii 36p
 Standard
 14 Dii 10p
 14 Dii/Q 8p
 16 Dii/Q 11p
 25 Pin Sil Pack of 10 £2.90

HC 33u CRYSTALS
 STC XF1000 £1.00
 Semitron ZS11.4 £1.00

LA 1216/D12 POT CORE
 5pair bubblepacked £2.80

DIODES
 AA118 90v 50ma 4p
 AA119 30v 35ma 7p
 AA133 100v 50ma 9p
 AA144 100v 5ma 4p
 AAZ15 100v 250ma 15p
 B1 11p
 BA101B varicap 10p
 BA116 30p
 BA127 60v 100ma 3p
 BA128 21p
 BA145 21p
 BA148 12p
 BA182 Varicap 6p
 BAX 13 50v 150ma 3p
 BAX14 21p
 BAX20 3p
 BAX21 50v 120ma 3p
 BAX22 100v 120ma 3p
 BAX54 8p
 BAY36P 21p
 BAY44 50v 250ma 4p
 BAY68 25v 115ma 3p
 BAY72 100v 400ma 4p
 BB103 Varicap 24p
 BB104 Varicap 16p
 BB109 Varicap 24p
 BB110B Varicap 24p
 BB113 3x Varicap 43p
 BB139 £1
 BR100 Diac. 15p
 BY206 300v 400ma 71p
 BY207 600v 400ma 23p
 BY402 21p
 BY403 21p
 Centercell 3p
 CG651 9p
 CR HG/3 10p
 CSD1117V LZ 40p
 CV7095 21p
 CV7098 21p
 D3202Y Diac. 11p
 DC2845 Microwave 20p
 DOG53 11p

RECTIFIERS

Type	Volt	Amp	Price
BY126	650	1	5p
BY127	1250	1	5p
BY212	15kv	500ma	6p
BY235	600	1 1/2	71p
BY236	900	1 1/2	71p
BY264	300	3	9p
BY265	600	3	11p
BY266	900	3	15p
BY274	300	3	14p
BY275	600	3	13p
BY277	1200	3	27p
BY289	800	2	4p
BY1202	2KV	10mA	6p
BYW55	800	2 (Oxide bead)	15p
BYW56	1000	2 (Oxide bead)	18p
BYX20-200	200	25	72p
BYX22-200	300	1 1/2	25p
BYX38 300R	300	6	48p
BYX38 600	600	6	52p
BYX38 900	900	6	60p
BYX38 1200	1200	6	65p
BYX42 300	300	12	36p
BYX42 600	600	12	46p
BYX42 900	900	12	92p
BYX42 1200	1200	12	107p
BYX46 300R	300	15	£1.19
BYX46 400R	400	15	Avalanche £1.75
BYX46 500R	500	15	£2.00
BYX46 600	600	15	£2.30
BYX48 300R	300	6	47p
BYX48 600	600	6	60p
BYX48 900	900	6	70p
BYX48 1200R	1200	6	92p
BYX49 300R	300	6	35p
BYX49 600	600	6	42p
BYX49 900R	900	6	47p
BYX49 1200	1200	6	60p
BYX52 300	300	48	£2.05
BYX52 1200	1200	48	£2.90
BYX70	500	1	4p
BYX72 150R	150	10	42p
BYX72 300R	300	10	52p
BYX72 500R	500	10	65p
BYX94	1250	1	14p
E250C50	250	3	6p
KS11394	800	3	23p
LT102	30	2	15p
M1	68	1	5p
MR856	600	3	24p
MSR5	800	3	12p
OA210	400	5	33p
RA53 10AF	1250	1 1/2	48p
RA5308AF	1250	1 1/2	50p
REC35A	1250	1 1/2	16p
SKE45	200	6	22p
SR100	100	1 1/2	9p
SR400	400	1 1/2	10p
SR1825	100	50	75p
IN3254	400	1	4p
IN4002	100	1	4p
IN4004	400	1	41p
IN4005	600	1	6p
IN4006	800	1	6p
IN4007	1250	1	15p
IN5059	200	1 1/2	10p
IN5401	100	3	10p
IN5402	200	3	11p
IN5406	600	3	15p
IN5408	1000	3	19p
IS027	800	1 1/2	11p
IS138	800	1	21p
25G103	100	60	£4.35
3052	200	2	11p
1604P	800	2	15p
16492	700	1 1/2	9p

BRIDGE RECTIFIERS

AMP	VOLT	Model	Price
1/2	60VOLT	BC30 C350	23p
1/2	1,600	BYX10	34p
0.6	110	EC433	20p
1	140	OSH01-20n	25p
1	400V	MDA104	29p
1 1/2	50V	WO05	27p
1 1/2	200V	WO2 Ex Equip	15p
1 1/2	400V	WO4	28p
1 1/2	400V	UE4R1	12p
1	100V	B40C800	12p
1	800V	WO8	27p
1 1/2	1000	W10	36p
1 1/2	75V	IBIBY234	111p
1 1/2	150V	IBIBY235	15p
2 1/2	100	I.R.	40p
2 1/2	350V	9F2	53p
2 1/2	500V	9E4	85p
3	50	KBS005	30p
3	100	KBS01	30p
3	200	KBS02	30p
3	400	KBS04	30p
3	600	KBS06	30p
3 1/2	100	B40C 3200	39p
5	400	Texas	85p

Miniature Meter Type

THYRISTORS

Amp	Volt	Model	Price
0.8	200	2N5064	18p
1	240	BTX18-200	35p
1	240	BTX30-200	35p
1	400	BTX18-300	41p
1	700	BT 106	70p
2	400	S2710D with heatsink	42p
3	600	T3N06C00	53p
3	100	T3N1C00	36p
4	50	S107F Sensitive Gate	36p
4	50	S2060F Sensitive Gate	36p
4	50	S2061D Sensitive Gate	38p
4	400	40506 with heatsink	58p
4	600	C106M Sensitive Gate	37p
4	600	2N3228	36p
4	600	GAK	36p
4	400	S3700D	44p
5	400	S5800D/R	36p
5	600	S5800M	44p
6.5	500	BT109/SCR957	71p
7	400	S2620D	45p
7	600	S2620M	45p
8	100	S2800A	36p
8	600	S122M	54p
12	1000	CR121103-RB	£8
15	800	BTX95-800 Pulse Modulated	£1
20	600	BTW92-600RM	£3.40
75	800	71CG80	£6
110	20	72RC2A	£3
150	1000	151RA100	£10
150	1200	151RA120	£11
BT 121		70p	
BT 107		£1	

ZENER DIODES
 4/500MW. BZY88, BZX97, etc. 51p
 2v. 2v7. 3v. 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 9v1. 10v. 11v. 12v. 13v. 13v5. 15v. 18v. 20v. 22v. 24v. 27v. 30v. 33v. 43v.
 BZY61 Laboratory Standard 400MW 7v5. Voltage Regulator Diode 12p
 1.3/1.5WT BZX61, BZY97, etc. 11p
 2v4. 2v7. 3v. 3v6. 3v9. 4v3. 4v7. 5v6. 6v2. 6v8. 8v2. 10v. 11v. 12v. 15v. 18v. 20v. 27v. 33v.
 2.5WT BZX70, etc. 13p
 2v4. 3v6. 3v9. 5v6. 6v2. 7v. 7v5. 8v. 9v. 10v. 11v. 14v. 15v. (8p). 20v. 22v. 26v.
 5WT BZV40, etc. 15p
 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 8v7. 9v1. 10v. 11v. 12v. 15v. 20v. 33v. 68v. 120v.
 10WT Z5D, ZX, IS50, etc. 20p
 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 10v. 11v. 12v. 13v. 16v. 18v. 21v. 22v. 33v. 36v. 39v. 43v. 51v. 56v. 62v. 68v. 75v. 150v.
 15WT BZV15C 12R 12volt 37p
 20WT BZY93, etc. 44p
 8v2. 12v. 39v.

TEMPERATURE COMPENSATED REFERENCE
 IN935B, IN936B, IN937B 9volt
 IN941B, IN942B, IN943B 11.7volt 8p

ELECTROLYTIC CAPACITORS (Wire ended)

Value	25 Volt	Price
1.6	6p	40
4.7	7p	47
6.4	4p	50
6.4	4p	64
10	4p	80
12	4p	100
16	4p	150
22	7p	160
25	4p	200
30	4p	220
33	4p	250

300 15p
470 8p
640 27p
680 11p
750 27p
1000 20p
3,300 46p

JUNCTION BOXES
 G.P.O. 12 way 60p
 4 pole 30 amp. mains. 45p

Value	40 Volt	Price
1	3 1/2p	47
8	7p	50
10	7 1/2p	64
15	3p	100
16	7p	150
25	5p	220
32	5p	250

400 12p
470 10p
680 8p
1000 39p
2200 35p

BRIAN J. REED

SEE PRECEDING PAGES FOR ORDERING INSTRUCTIONS
Cut out and keep these 3 pages. Over the months they will bring to you some of the 6,000 items stocked.

INTEGRATED CIRCUITS

343 4 bit comparator	4p	74196 Pre-set 50MHz	36p	CD4071 quad 2 input or buffer	16p	SN15862	6p
326 HINIL 2, 2, 3, 3, Input Nand	20p	74S196/82S90 Decade Count/Latch	65p	CD4072 dual 4 input or buffer	15p	SN75107 Interface	£1.15
371AJ (MC684) Decade count. HINIL	5p	74LS221 Dual Monostable M/VIB	52p	CD4076 Quad D Flip-Flop	54p	SN75108	36p
542 Servo Amp	18p	74221 dual Mono Multi. Schm. Trip	72p	CD4077 Quad Exclusive Nor	30p	SN75110 Dual line driver	46p
702 CL OP AMP	25p	74285 binary 4 x 4 mult.	72p	CD4078 8 Input Nor	19p	SN75125 7 line Rec. Interface	72p
709/72709 OP Amp	18p	74LS290 Decade counter	47p	CD4081 Quad 2 Input and Buffer	15p	SN75150	72p
723 2v - 37v 150ma Regulator	36p	74293 4 bit binary counter	80p	CD4082 Dual 4 Input and	15p	SN75235N	11p
724	20p	74298 Quad 2 in multi plus store	£1	CD4085 Dual 2 in. 2 wide and/or inv.	72p	SN75451 interface	36p
733 diff. wide band video amp	40p	74490 dual decade ripple count	£1.30	CD4086 4 Wide 2 Input and/or Inv.	54p	SN75463 dual periph. or driver	36p
741 OP Amp	17p	74490	£1.30	CD4093 quad 2 input Nand S.T.	54p	SN76001	36p
747 Dual OP Amp	44p	7905 - 5v Reg. 1 Amp	54p	CD4094 8 bit ser. par. hold bus reg.	72p	SN76003 5Wt. Amp	36p
930DC	4p	8080A C.P.U. 8 bit	£3.60	CD4095 JK. Gated flip flop non Inv.	72p	SN76013 5Wt. Amp	36p
933DC	4p	8284 Binary up down synch.	36p	CD4096 gated JK flip flop	72p	SN76013N 5 Wt. Amplifier	92p
936DC	4p	82S126 256 x 4 prom	90p	CD4097 mux/demux 8ch.	£2.90	SN76023 5Wt. Amp	36p
937DC	4p	82S129 Tristate prom 256 x 4	£5	CD4502 Strobed Hex inverter	44p	SN76110P	35p
946DC	4p	9093DC	4p	CD4508BF dual 4 bit latch	£1.78	SN76115N Stereo Decoder	59p
949DC	4p	9112DC	4p	CD4511 BCD 7 seg. latch dec/driver	72p	SN76121	59p
961DC Dual 4in Ext. nand	4p	93S10	£1	CD4514 decoder	£1.45	SN76228N	£1.60
963DC	4p	9311	£1.20	CD4515 decoder	£2.12	SN76396 (TBA396)	35p
1315P2	36p	93L16	36p	CD4517 2x64 bit Shift Register	£3.60	SN76620 F.M.I.F. Amp. + Demod.	18p
2102 Memory 1024 static 450ns	73p	9370	£1.83	CD4519/MC14519 4 bit and/or Set.	54p	SN76650N stage video I.F. + A.G.C.	50p
2107B see JPD41 AC	-	93453 Schottky prom 1024 x 4	25p	CD4520 quad 2 Bit Binary	72p	SN7666N	35p
2125 1024x1 Static 125ns RAM	£1.25	930399-256 Bit Shift Register	4p	CD4527 8cd rate multiplier	£1.20	SN76666N Sound I.F. + Demod. + Driver	50p
2140 4 x S.P.D.T. for D/A	£1.83	930399-480 Bit Shift Register	4p	CD4532 BCD Priority encoder	£1.08	SN158093	50p
25 LS 374 Octal D edge Trig F/F 3st	£1.30	930399-500 Bit Shift Register	4p	CD4555 decoder	72p	SN158097	4p
2708 Eprom 1024 x 8	£2.60	AYS-3607 3/8 Digit DVM	£1.65	CD4555 decoder	56p	SN158099	50p
2716 Eprom 2048 x 8	£5.00	AYS-8300 Ch/Time Display	38p	CD22100 cross point switch	£1.45	SP4021 ±64 VHF/UHF 50mv TTL O/P.	75p
3351-2DC 40 x 9 Bit FIFO 2MHZ	£1.07	BRCM300 Volt Regulator	£1.40	CD40100 32 bit L/R Shift Reg.	£1.78	TAA263 Amp (low level)	75p
3624-4 prom 512x8 90ns	£1	BT7822	£1.25	CD40101 9 bit Par. Gen. check	£1.08	TAA320 Integrated most AMP.	35p
4060 Dynamic RAM 300ns	£1.45	CA139A Quad Volt Comparator	54p	CD40108 4 x 4 Multiport Reg.	£3.10	TAA550 Volt Reg.	10p
74H00 Quad 2 Input	26p	CA239G Quad volt comparator	54p	CD40160 Dec. Count. Async. clear	72p	TAA700	£2.30
74LS00 Positive Nand	13p	(T)CA270AE	£1	CD40162 4 bit synch. Dec. Count R/V	72p	TAD100 AM Radio	£1.22
74S00 Gates	18p	(T)CA270CW/AW	35p	CD40163 Bin. count synch. clear	72p	TBA1205/CQ/5B/B TV Amp	36p
7401 Quad 2 input positive	73p	(T)CA270CE	35p	CD40182 logic ahead carry block	72p	TBA395Q	£1.50
74H01 Nand + O/C out	26p	CA920 7V Horiz. system	72p	CD40192 Sync 4 bit BCD U/D count	72p	TBA396 Luminescence and chrom.	35p
7404 Hex. Inverter	11p	CA3001 RF Amp	86p	CD40194 4 bit L/R SR	72p	TBA550Q Synch. Sep. + A.G.C.	£1.25
54/7406 Hex. Inv./Buff/Drive	15p	CA3028A balanced OP. AMP.	£1.20	CD40208BF 16 bit multi port RAM	£2.12	TBA560C Lum/Chrom. control	52p
74LS08 Quad 2 In. Pos. And	15p	CA3044	75p	CD40257 Data Selector	£1.15p	TBA800 Amp 5 Watt Audio	52p
7410 Triple 3 Input	10p	CA3045 Transistor Array (5)	£1.43	CDP1833 Cosmac Rom 1824 x 8	£3.60	TBA920 TV Line System	70p
74L10 Positive Nand	25p	CA3046 Transistor Array (5) NPN	40p	CDP1834 Cosmac Rom 1024 x 8	£3.60	TC2700/SAE/AE/QS Vid. Det.	£1
74H10 Gates	18p	CA3080 Prog. Transconduct. Amp.	59p	CT1012 C Frequency synthesiser	75p	TC2700/SB synch. demodulator	55p
7411 Triple 3 In. Pos. and	8p	CA3083 NPN transistor array	65p	CT1115 Frequency synthesiser	75p	TC4440 A.M. Receiver	£1.25
7414 Hex. Schmitt trig. Inverter	29p	CA3086 NPN 5 transistor array	29p	CT1116 frequency synthesiser	75p	TC4830S Ex. Equip A.F. Amp.	18p
7420 Dual 4 Input	11p	CA3089 FM I.F. amp plus detector	1.10p	CT1119 Frequency synthesiser	75p	TC4830S A.F. Amp.	37p
74S20 Positive Nand Gates	19p	CA3090 Q/AQ FM decoder	£1.72p	FCH111 8 input Nand/Nor	8p	TC4440	£1.25
74S22 Dual 4 In. Pos. Nand o/c	18p	CA3093	36p	FCH201	18p	TCEP100	£1
7425 dual 4in nor strobe	18p	CA3094 Prog. Sw. Pwr. OP Amp.	36p	FCJ101	50p	TDA0470 Organ	37p
7426 Quad 2 In 15v Interface	16p	CA3123 AM Radio RF/IF Amp	73p	FCQ/MPQ3725 4 Tr. Array	45p	TDA1003 Pre-amp and record	£1
7428 4 x 2in + Nor Buff/CL. Drive	16p	CA3126E	£2.22	FZ1151	18p	TDA2610 6watt audio amp	71p
5430 8in. Pos. Nand	12p	CA3146E Hi-volt 5 transistor array	90p	FZ1191	18p	TDA2680 T.V. signal processor	£1.83
7430 8in. Pos. Nand	11p	CA3183 NPN transistor array	80p	FZ201	18p	TD25A 16 diode array	4p
74L30 11p	11p	CA3189 FM receive IF. system	£1.40	ICL7103 4 1/2 Digit DVM/DPM	£2.04	TL41 Log-antilog amp	36p
54/7437 Quad 2 In. Pos. Nand. Buf.	13p	CA3230 Comparator	59p	IM5623 Prom. 256 x 4.60ns	36p	TLu A720 AM Radio RF/IF Amp	73p
7438 Quad 2in nand buf O/P	14p	CA3401 (LM3900) Quad OP Amp	36p	LM3623 Prom. 256 x 4.60ns	36p	TMS 3409 memory 80 bit shift Reg.	£1.10p
74H40 Dual 4 In. Pos. Nand. Buffer	26p	CD4000 Dual 3 input Nor + Invert	12p	LM3001 Volt Regulator	42p	TMS4034 Memory	£1.08
7442 BCD to Decimal Decoder	26p	CD4002 Dual 4 Input Nor	12p	LM3007 Volt Regulator	36p	µPD411AC 200ns Dynamic 4096 x 1 ram	£1.30
74LS42 BCD to Decimal Decoder	40p	CD4004	56p	LM10411N Do. by system	£1.00	XR215 Hi-freq. phase lock loop	£2
7445 BCD Decimal Decoder	42p	CD4006 18 Stage Static Shift Reg.	36p	LM1303N Stereo Pre Amp low noise	65p	ZN414 AM Radio Receiver	78p
Expandable Dual 2		CD4007 Dual Comp. Pair + Invert	12p	LM3900 (See CA3401)		ZST131A 5 Input Power NOR	8p
74H50 Wide 2 Input and/or Inv.	26p	CD4008 4 Bit Binary Full Adder	54p	MC830P	4p		
7454 4 Wide 2 In. and/or Inv.	11p	CD4009 Hex 3 Buffers	39p	MC833P dual 4 input expander	4p		
74L54 11p	11p	CD4010 Hex 3 Input Nand	39p	MC837P Hex invert. fast rise	4p		
54/7472 And Gated JK Master	17p	CD4012 Dual 4 Input Nand	36p	MC846P	4p		
74L72 Slave F.F. Preset + Clear	25p	CD4013 Dual D Flip Flop	36p	MC852P	4p		
5473 Dual JK Master	12p	CD4014 8 Bit Shift Register	36p	MC1306P	40p		
7473 Slave Flip Flops	17p	CD4016 Quad Bi-Lateral Switch	36p	MC1307P	35p		
74H73 with Clear	26p	CD4017 Decade Count/Divide	54p	MC/CA/BRC 1310P St. Decoder	35p		
7474 Dual D. Pos. Trigger	13p	CD4018 Preset Divide N Count	54p	MC1211 see CA758	40p		
74L74 FF 2/Preset + Clear	25p	CD4019 Quad 2 Input Multiplex	54p	MC1312P Stereo Decoder	40p		
7475 Quadlatch	24p	CD4020 14 Stage Binary Counter	54p	MC1314P	35p		
54/7476 Dual JK Mas./SL Flip Flop	19p	CD4022 Divide by 8 Count/Divide	36p	MC1315P	35p		
5480 gated 5 input	22p	CD4023 Triple 3 Input Nand	19p	MC1350P Video I.F. Amp + A.G.C.	35p		
7482 2 Bit Binary Full Adder	35p	CD4024 7-Stage Binary Counter	36p	MC1357P sound I.F. + Demod.	35p		
7483 4 Bit Binary full	45p	CD4025 Triple 3 Input Nor	14p	MC3302L Quad amp (volt comparator)	75p		
74LS83 Add + Fast carry	47p	CD4027 Dual JK Flip Flop + RS	30p	MC4044P Phase/Frequency detector	£1		
54/7486 Quad exclusive or	18p	CD4028/MC14028 BCD/Decimal	42p	MC4344P	£3.50		
5490/7490 Decade Counter	25p	CD4029 Synch. Preset Bin/Decade	54p	MIC7C	25p		
7493 Binary Counter 4 Bit	25p	CD4030 Quad Exclusive or	36p	MK2686	36p		
54/7495 4 Bit Ser./Par. In Out	25p	CD4031 64 stage static. shift reg.	£1.20	MK4012 Memory Static Shift Reg	38p		
74LS98 4 bit storage register	£1.25	CD4032 Trip. Ser. Add Neg	72p	MM237B (6108) 6 channel tuner	£1		
74107 Dual JK Flip Flop Clear	20p	CD4033 Dec. Count. 7 Seg. Output	72p	MM5335 Prom 256 x 8 80ns	36p		
74S112 Dual JK N.E.T. Flip Flop	38p	CD4034 Static shift register	£1.45p	MM8008 C.P.U.	36p		
74118 Hex Reset latch	75p	CD4035 8 Bit Par. In out Shift	54p	MP3202 3/8 Digit DVM	£1.45		
74121 Monostable Multivibrator	12p	CD4036 Word Buff. Store/decode	£2.90	MT300 Volt Regulator	8p		
74122 Mono stable multivibrator	18p	CD4037 triple and/or B1 Phase pairs	72p	MT305 Volt Regulator	8p		
54/74123 Dual Retrigger. Multivibrator	35p	CD4038 Triple serial adder	54p	MW4050D Static Ram 200ns	£1.60		
54S124 dual volt cont. osc.	£1.10	CD4040 12 stage binary counter	80p	MWS5101 256x4 SOS CMOS Ram	£3.60		
74132 Quad 2 in nand schmitt	44p	CD4041 Quad True/Comp. Buffer	54p	SA4661	36p		
74141 BCD To Decimal Dec/Drive	42p	CD4042 Quad clocked D type catch	56p	SA1010	34p		
74LS145 BCD to decimal Dec/Drive	93p	CD4043 Quad Nor R/S Latch	54p	SA1025	£4		
74151 1 of 8 Data Sel/Multivibrator	32p	CD4044 Quad Nand R/S Latch	54p	SAA5012 Teletext Binary Tuner	£2.75p		
74153 Dual 4 to 1 multiplexer	36p	CD4045 4 Bit Par. in out shift	54p	SAS580 4 Ch. touch tune. + Disp.	18p		
74154 16 Way Distribution	35p	CD4046 Micro Power PH. Lock Loop	36p	SAS590 4 Ch. touch tune. + Disp.	18p		
74155 Dual 2 to 4 line decoder	12p	CD4047 monostable	72p	SGS308 4 diode array	4p		
74157 Quad 2 line to 1-Data	12p	CD4048 Exp 8 input gate	36p	SL403A 3 Wt. Amp.	38p		
74165 8 bit shift reg. Piso	58p	CD4049 Hex Inverter Buffers	36p	SL442 Copper power supply	36p		
74167 Synch. Dec. Rate Multivibrator	23p	CD4051 Analogue Multi/Demulti	36p	SN15836	11p		
74173 Quad 3 state latch	44p	CD4052 Analogue Multi/Demulti	56p	SN15845	25p		
74174 Hex D/F/E and clear	55p	CD4053 Analogue Multi/Demulti	54p	SN15846	50p		
74S174 Hex D Flip-Flop + clear	72p	CD4054 4 LINE LCD driver/count	72p	SN15851	37p		
74176/8280 Pre-set 35MHz Decode	30p	CD4055 BCD7SEG. Decode/Drive.	72p	SN15858N	55p		
74180 8 bit parity gen.	12p	CD4061 256 X 1 Bit Static RAM	£5.30				
74181 Arith. Logic unit/funt. Gen.	56p	CD4063 4 bit magnitude comp.	72p				
74H183 Dual full adder	36p	CD4066 Quad Bilateral Switch	27p				
74192 Synch. Dec. Up/Down	36p	CD4067 1.16 MULTIPLEXER	£2.12				
74LS192 Count + Dual Clock	60p	CD4069 Hex inverter	16p				
74193 reversible binary count.	38p						

Electrolytic capacitors (wire ended)						
75 volt						
1	10p	3	10p	100	15p	
2	10p	64	15p	220	22p	
			100 Volt			
3	9p	25	13p	330	11p	
5	10p	47	16p	680	11p	
20	13p	50	16p			
22	13p	60	7p			
			160 Volt			
1	15p	8	15p	32	23p	
4	15p	10	16p	50	23p	
4.7	15p	15	7p	80	26p	
6.8	15p	16	18p			
			200 Volt			
2	15p					
			250 Volt			
22	18p	47	23p			
			275 Volt			
32	32p					
			300 Volt			
2	26p	8	13p	10	£1.05p	
			(Pack of 5)			
			350 Volt			
1	6p	4	6p	10	8p	

MOTORS

1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3rpm Motors 32p. 6 volt standard cassette motors new £1.20. 8 track 12V Replacement Motors 55p. Ex. Equip. BSR record player motors, C129, C197 type, £1.20.

SEMICONDUCTORS


LM340 80p. BY103 10p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. CA3020 45p. 741 22p. 741S 35p. 723 35p. NE555 24p. 2N3773 £1.70. NE556 50p. 2N414 75p. BD238 28p. BD438 28p. CB4069 15p. 4" Red Led Displays, c.c. or c.a. 95p. TIL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p. BY223 20p.

PROJECT BOXES

Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

MOTOROLA PIEZO CERAMIC TWEETERS

No crossover required

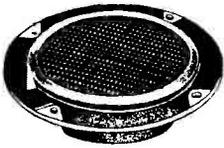

2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65

TOOL SALE

Small side cutters 5" insulated handles £1. Radiopliers, snipe nosed insulated handles £1. Heavy duty pliers insulated handles £1.10. Draper side cutters spring loaded £1.

HANDY BENCH VICE

1" Jaw opening, £2.95.



Hand drill, double pinion with machine cut gears, 5/16", only £2.75p plus 50p p&p.

MORSE KEYS

Beginners practice key £1.05. All metal full adjustable type. £2.60

MINIATURE LEVEL METERS

1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

TRANSFORMERS

All 240VAC Primary (post-age per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 24 volt 2 Amp £2.45 (54p).

TRIAC/XENON PULSE TRANSFORMERS

1:1 (gpo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.

MICROPHONES

Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95, ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. DYNAMIC stick microphone dual imp., 600 ohms or 20K, 70-kHz., attractive black metal body £7.75. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromed copper body, £12.95 CASSETTE replacement microphone with 2.5/3.5 plugs £1.35 GRUNDIG electric inserts with FET pre amp, 3-6VDC operation £1.00

LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic swich on when dark £4.50

RIBBON CABLE

8 way single strand miniature 22p per metre.

SPECIAL OFFER TAPE HEAD DEMAGNETIZER



240VAC with curved probe suitable for reel to reel or cassette machines, £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p

MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50




20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £975.

40kHz Transducers. Rec/ Sender £3.50 pair.

TELEPHONE PICK UP COIL

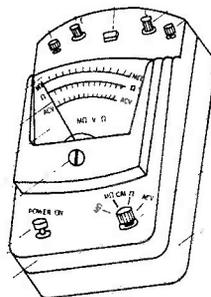Sucker type with lead and 3.5mm plug 62p.



500v electronic megger, push button operation. Ranges- LO ohm Range 0 - 100Ω (MW scale 5Ω) 0 - 100MΩ Mid scale 5MΩ) £48.75p

Stabilized power supplies, 240V A.C. input output 13.8 volts at 3/5 amps D.C. £14.75p

TERMS:

Cash with order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive.

S.A.E. for illustrated lists

MULTI-TESTER



KRT5001 50k/v range doubler multimeter, 0-1kv (125mv LO range) 0 - 1kv AC. 0 - 10amp DC. 0 - 20MΩ res. (LO ohm Ω - 2k range) 170 x 124 x 50mm £15.50.

YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts, 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

CRIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

POWER SUPPLIES

SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 40 0mA, switchable £3.45. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.

BUZZERS

MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, voltage operating 4-15VDC, 75p each. LOUD 12VDC BUZZER, with metal case. 50mm diam. x 30mm high 63p. Carters 12 volt Minimize Alarm sirens £7.65p. 12VDC siren, all metal rotary type, high pitched wail, £6.25.

TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

All Antex irons still at pre increase prices, order now as new stock will be going up next month.

Antex Model C 15 watt soldering irons, 240VAC £3.95

Antex Model CX 17 watt soldering irons, 240VAC £3.95

Antex Model X25 25 watt soldering irons, 240VAC £3.95

ANTEX ST3 iron stands, suits all above models £1.65

Antex heat shunts 12p each. Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 59p each.

Miyarna IC test clips 16 pin £1.95

SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p. DPDT (8 x 7 x 7mm) 55p. DPDT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

TEI Mobile SWR metre, with field strength, PL259 connection, £8.35.

RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.



Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz. R.F., output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95 BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10 tape head assembly - 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20

PROGRESSIVE RADIO

31 CHEAPSIDE, LIVERPOOL 2.

ALL ORDERS DESPATCHED BY RETURN POST

BATTERIES NICAD rechargeable 1. 1AA 2pc (C) £1.90 3. (D) £2.90		CAPACITORS Ceramic - Auto Insertion TOL 10% 100v IN PFS PCM 5mm		RESISTORS E12 IN OHMS 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82		SCRs ITEM (IT/A) V 70p 330 BT106 1 700 331 C106D 2 4 400 332 2N444 3 600 333 2N5061 25 60					
CABLE PVC round Grey 4. Audio screened overall 2 core 7/2mm 20p MTR. 5. Comm. wire 18/2mm x 15' 1 each in Black Red Yellow 5p lot. 6. Mains 3 core 3 amp 12p MTR. 7. TV Downloaded 20p MTR.		BRIDGES 4S. KBPC105 2A 30p By GMR, W005 1A 20p MROLA MULLARD 47 W02 1A 20p 48. W04 1A 20p 49. 2KB40R 2A 20p 42. BY18 1.4A 50p 43. BY17 1A 80p 44. BY261 400 2.5A E3 50. 10DB1A 1.8A 20p		SWITCHES 334 Push button PCB mounting pins PCM 4mm push to make/push to break 19p. 335. Rocker panel mounting fits 1 1/4" x 1" hole on/off 15A 250v 19p. 336 Toggle panel mounting fits 10mm hole on/off 5A 250v chrome 59p.		TERMINAL BLOCK 337 10 way 5A 112 x 22mm red 29p.					
CAPACITORS ELECTROLYTIC TOL 10% 50% IN MFDS SIZES IN MM AXIAL TUBULAR (ALL 5mm) PLUG IN		CONNECTORS 30. DIN plug 5 pin 180deg 15p 31. DIN chassis SKT 5 pin 180deg 15p 32. Jack plug stereo J 15p 33. Jack chassis SKT Stereo J 39p 34. Mains plug rubber white 3 pin 13a 5p sq. pin 13p		TRANSISTORS all at 6p each		all at 19p each					
CAPACITORS POLYESTER ALL IN RECT BOX STYLE TOL 10% BY EVOK MULL PLESSEY ROEDSTEIN SIEMENS		POLYESTER AXIAL STYLE TOL 10% 71. .1/160v 311 31104 9p 72. .22/400v M312 9p 73. .33/160v KT1853 12p 74. .47/250v MKT122 15p 75. .68/400v MKT1813 15p		STOCK LISTS SAE 15p TANT SOLID AXIAL U. CARBIDE KJ VAL TOL VAL TOL 80 1.5 10 20p 85 10 20 10 40p 81 2.2 5 35 40p 86 22 20 10 20p 82 3.3 20 15 20p 87 47 20 5 20p 83 4.7 5 10 30p 88 100 5 20 70p 84 6.8 10 10 30p 89 220 10 10 50p		all at 39p each					
CAPACITORS TANT BEAD TOL 20% IN MFDS PCM 5mm 76. 2.2/200v 9p 77. 4.7/25v 9p 78. 22/25v 15p 79. 47/6v3 18p		DIODES by IIT, MULL, SECOSEM, TEXAS, etc. All coded. 95. BA155 100mA 150v 5p 105. OA67 48mA 75v 5p 115. IN4148 75mA 75v 11p 96. BA133 75mA 50v 5p 106. OA80 10mA 30v 5p 116. IN4141 150mA 75v 3p 97. BA116 200mA 150v 5p 107. DA91 50mA 115v 7p 117. IN4004 3A 400v 11p 98. BA717 75mA 35v 5p 108. RGF108 1A 100v 5p 118. IN5407 3A 800v 13p 99. BY127 2A 125v 5p 109. TA550 50mA 100v 11p 119. IS44 75mA 40v 5p 100. BY206 400mA 350v 15p 110. IA30 10mA 3KV 9p 101. BY255 3A 13v 5p 111. IN914 15mA 100v 3p 102. BYX10 360mA 16v 5p 112. IN616 75mA 100v 2p 103. BYX55/600 1A2 500v 20p 113. IN4002 1A 100v 2p 104. CV8790 200mA 150v 5p 114. IN4004 1A 400v 3p		LEDs .125" TIL 209C SERIES 155. GR13p 156. RED 9p 157. YEL 15p 158. GR 14p 159. RED 10p 160. YEL 16p		all at 19p each					
DIODES ZENER by MOTOROLA, MULL, SECOSEM etc BZ79/BZ88C 400mW 5% ITEM 3V 3V3 4V7 5V1 5V6 6V8 9V1 10 15 18 5p 120 121 122 123 124 125 126 127 128 129 5p		DIODES ZENER by MOTOROLA, MULL, SECOSEM etc BZ79/BZ88C 400mW 5% ITEM 3V 3V3 4V7 5V1 5V6 6V8 9V1 10 15 18 5p 120 121 122 123 124 125 126 127 128 129 5p		all at 19p each		all at 89p each					
FUSES DC 20mm x 5mm 16A 100mA 4p. 16A 500mA 4p. 16A 5p. 16A 2A 5p.		HOLDER 167. F297 24p		all at 19p each		all at 19p each					
ICs DIL PINNING (-) 172 380(14) 175 556(14) 178 709(14) 181 741(8) 184 1458(8) 187 3800(14) 56p 26p 16p 36p 56p 56p 188 301(8) 170 324(14) 173 381(14) 176 565(14) 179 710(14) 182 747(14) 185 3048(14) 188 3914(18) 76p 36p 76p 76p 56p 56p 169 308(8) 171 348(14) 174 555(8) 177 567(8) 180 723(14) 183 1316(14) 186 3080(8) 189 13600(16) 76p 86p 86p 86p 86p 86p		ICs MROLA NATIONAL T M CMOS DIL 40 - N BUFF 15p 52p 190. 00 214. 29 52p 84p 191. 01 215 30 192. 02 06 216 35 40 193. 07 08 217 41 40 194. 09 218 41 40 195. 10 219 42 40 196. 08 220 43 40 197. 10 221 44 40 198. 11 222 46 40 199. 12 223 47 40 200. 13 224 48 40 201. 14 225 50 60 202. 15 226 60 60 203. 16 227 69 80 204. 17 228 71 80 205. 18 229 81 93 206. 19 230 93 207. 20 253 25 277 157 153 208 21 254 27 278 209 22 255 30 278 210 23 256 32 280 211 24 4500 - N 257 37 281 212 25 258 38 282 213 26 259 40 283		ICs TIL DIL 74 - N M 15p 52p 84p 236. 00 260 42 45 237. 01 261 42 45 238. 02 262 47 239. 03 263 70 240. 04 264 72 241. 05 265 73 242. 06 266 74 243. 07 267 75 244. 08 268 75 245. 09 269 85 246. 10 270 80 247. 11 271 93 248. 12 272 96 249. 14 273 121 96 250. 16 274 145 251. 17 275 151 252. 20 276 157 253. 25 277 157 254. 27 278 255. 30 278 256. 32 280 257. 37 281 258. 38 282 259. 40 283		ICs FCHILD NAT SIGNETICS T M 74LS - N 15p 52p 284. 00 299 84p £1.68 285. 01 300 123 286. 02 301 138 287. 03 302 139 288. 04 303 155 160 289. 05 304 160 290. 08 305 161 291. 11 306 292. 23 307 193 170 293. 27 308 294. 28 309 295. 74 310 296 311 297 311 298 93		LOW IC HOLDERS 312 00 26p 313 02 26p 314 04 26p 315 06 26p 316 10 27p		all at 29p each	
POTS Cermet 20 turn 1/2" rect. plug in item 320. 50R 70p. 321. 100R 60p. 322. 500R 60p. 323. 1K 55p. 324. 5K 55p. 325. 10K 55p. Cermet Horiz. round plug in 326. 50R 9p. 327. 100R 11p. 328. 100K 15p.		DUALS 516 BFY81 £1.89 FETS 518 2N3818 20p 519 2N3820 40p 520 2N6457 30p 521 2N5459 40p PUTS 522 BRV39 36p 523 2N6028 12p 524 2N6466 48p V REGS 525 LM309K £1.20 526 LM317K £2.40 527 CA3085 40p		all at 19p each		all at 11.39 each					
ICs MROLA NATIONAL T M CMOS DIL 40 - N BUFF 15p 52p 190. 00 214. 29 52p 84p 191. 01 215 30 192. 02 06 216 35 40 193. 07 08 217 41 40 194. 09 218 41 40 195. 10 219 42 40 196. 08 220 43 40 197. 10 221 44 40 198. 11 222 46 40 199. 12 223 47 40 200. 13 224 48 40 201. 14 225 50 60 202. 15 226 60 60 203. 16 227 69 80 204. 17 228 71 80 205. 18 229 81 93 206. 19 230 93 207. 20 253 25 277 157 153 208 21 254 27 278 209 22 255 30 278 210 23 256 32 280 211 24 4500 - N 257 37 281 212 25 258 38 282 213 26 259 40 283		ICs FCHILD NAT SIGNETICS T M 74LS - N 15p 52p 284. 00 299 84p £1.68 285. 01 300 123 286. 02 301 138 287. 03 302 139 288. 04 303 155 160 289. 05 304 160 290. 08 305 161 291. 11 306 292. 23 307 193 170 293. 27 308 294. 28 309 295. 74 310 296 311 297 311 298 93		all at 11.39 each		all at 11.81 each					

ORDER FORM CUT ALONG DOTTED LINE AND FOLD.

PRICES FIRM UNTIL 30.8.81


NAME	QTY	ITEM No.
ADDRESS		
CRIMSON COMPONENTS LTD.		
76 CASTLE VIEW		
ILFORD		
ESSEX		
ENQUIRIES		
FOR		
PCBS		
WELCOME		
01-554 1834		
01-445 6645		
Immediate despatch except item 389 2 weeks.		
Pay CASH WITH ORDER. £		
Carriage is free.		
VAT 15% extra UK Only £		
TOTAL £		

Self-Binder

for "Radio & Electronics Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

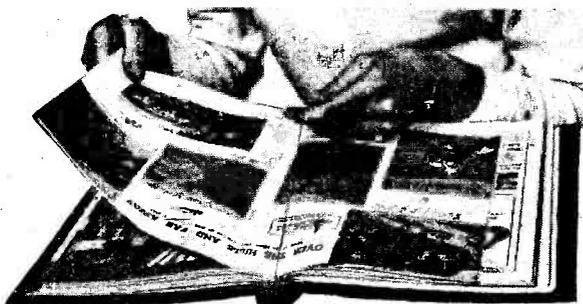

PRICE £2.25 P. & P. 60p
including V.A.T.

For your other magazines


Plain-backed in Maroon or Green
(Please state colour choice)

PRICE £2.25 P. & P. 60p
including VAT

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

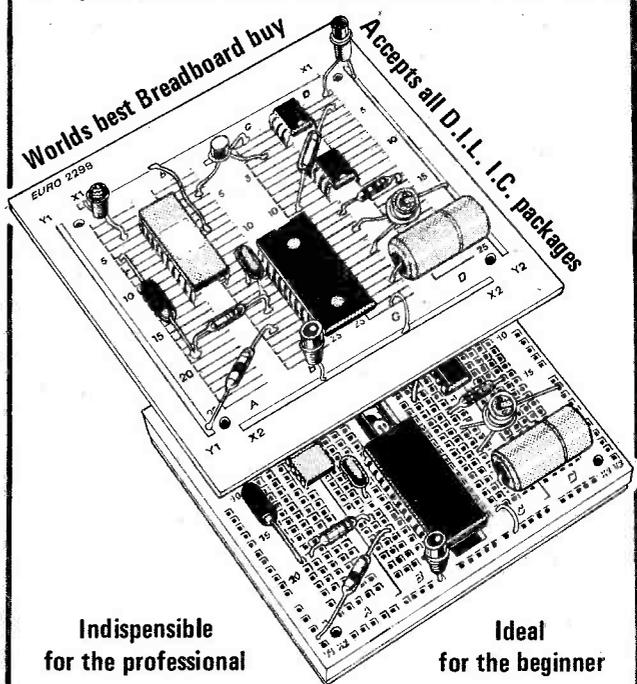First the EuroBreadBoard Now the EuroSolderBoard



Design on a EuroBreadBoard — Instal on a EuroSolderBoard

First the EuroBreadBoard

Will accept 0.3" and 0.6" pitch DIL IC's, Capacitors, Resistors, LED's, Transistors and components with up to .85mm dia leads. 500 individual connections PLUS 4 integral Power Bus Strips along all edges for minimum inter-connection lengths. All rows and columns numbered or lettered for exact location indexing (ideal for educational projects) Long life, low resistance (< 10m ohms) nickel silver contacts £6.20 each or £11.70 for 2

Now the EuroSolderBoard

New 100mm square, 1.6mm thick printed circuit board with pre-tinned tracks identically laid out, numbered and lettered to EuroBreadBoard pattern. Four 2.5mm dia fixing holes. £2.00 for set of three ESB's

And don't forget the EuroSolderSucker

Ideal for tidying up messy solder joints or freeing multi-pin IC's, this 195mm long, all metal, high suction desoldering tool has replaceable Teflon tip and enables removal of molten solder from all sizes of pcb pads and track. Primed and released by thumb, it costs only £7.25 including VAT & PP



Snip out and post to David George Sales,
Unit 7, Higgs Industrial Estate, 2 Herne Hill Road, London SE24 0AU

David George Sales,
Unit 7, Higgs Ind. Est., 2 Herne Hill Rd., London SE24 0AU.
Please send me:—

- | | | | |
|-----------------------|----------|-----------------------|--------|
| 1 EuroBreadBoard | @ £ 6.20 | <input type="radio"/> | |
| or 2 EuroBreadBoards | @ £11.70 | <input type="radio"/> | Please |
| or 3 EuroSolderBoards | @ £ 2.00 | <input type="radio"/> | Tick |
| or 1 EuroSolderSucker | @ £ 7.25 | <input type="radio"/> | |

All prices are applicable from Jan. 1st 1981 and include VAT & PP but add 15% for overseas orders.

Name

Company

Address

.


Tel. No.

Please make cheques/P.O. payable to David George Sales and allow 10 days for cheque clearance and order processing

REC/4

NEWS . . . AND

NEW TRADE MARK WITH NEW RANGE OF DRILLS

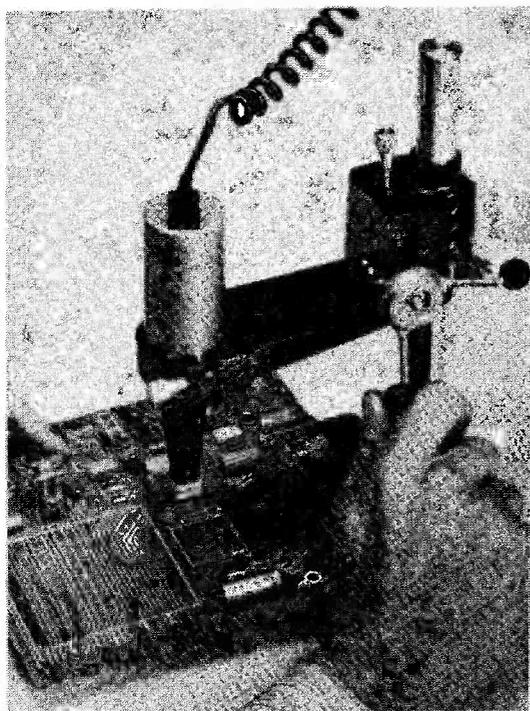

Microflame (UK) Limited, Vinces Road, Diss, Norfolk IP22 3HQ have recently announced the birth of a brand-new trademark and range of low-voltage mini-Drills.

The 'Drillmaster' range embraces two drills – 'Drillmaster' Junior and 'Drillmaster' Senior – and a comprehensive range of accessories for drilling, grinding, polishing, cutting, shaping, carving, engraving, de-burring and similar operations. Both drills are fitted with the latest telephone-type, "curly-tail" flexible cords, and are suitable for battery or transformer operation.

'Drillmaster' Junior has a unique, "curved triangular" shaped body which fits comfortably into the angle between the base of the user's thumb and forefinger, and close control is aided by the provision of a detachable chuck finger-shield. A chuck with 4 precision cut steel collets, 0.6mm, 1.2mm, 1.8mm and 2.4mm is fitted as standard.

'Drillmaster' Junior Drill Stand has a powerful magnifying glass attachment built-in.

'Drillmaster' Senior is supplied with an automatic 3-jaw chuck as standard, and a precision chuck with a set of 5 steel collets, 0.6mm, 1.2mm, 1.8mm, 2.4mm and 3.2mm is available as an optional extra.

In addition to a robust Drill Stand for the 'Drillmaster' Senior, over 100 accessories are available for use with either the Junior or Senior Drill.

Leaflets and Price Lists are available.

SOLDERING IRONS TO BE BETTER DISPLAYED

S. & R. Brewster Ltd., of 86-88 Union Street, Plymouth PL1 3HG, are sending their famous soldering irons to retail outlets in a different form of packing.

Previously packed for shelf display, the soldering irons can now be seen in very attractive boxes using the more modern hang-up display style. Instead of viewing the soldering irons end-on they can now be

seen full length.

The green boxes house the standard Type 1 mains voltage iron, the brown ones contain Type 1 12 volts iron and the yellow one their Model D.

The soldering irons can be supplied direct to individual customers as well as to the trade and the irons can, of course be obtained from many retail outlets.

TECHNICAL STANDARDS FOR TV AND LOCAL RADIO STATIONS

"Standards for Television and Local Radio Stations" – has recently been published by the Independent Broadcasting Authority.

This 72-page book with many two-colour illustrations brings together the current IBA Technical Codes of Practice relating to television studio centres and to ILR studios and OB operations. These are mandatory codes for ITV and ILR programme companies and have special importance also to equipment suppliers and the broadcasting industry generally. For television, these codes will apply to the new ITV contracts from January 1982.

The book is intended for engineers, firms and students directly involved in the field of broadcasting.

IBA Technical Review No. 13, "Standards for Television and Local Radio Stations", technical editor John Lovell, published by IBA, London.

THE RADIO AMATEUR INVALID AND BLIND CLUB

We recently received the up-to-date membership list of the R.A.I.B.C.

The total membership is now 615 of whom 324 are licensed members and 291 short wave listeners. Due to helpful publicity by the R.S.G.B., during the past year, nearly 30 additional clubs and societies have promised their help.

Those of our readers not previously aware of the good offices of R.A.I.B.C. in assisting shortwave enthusiasts who are invalids, or blind, and feel that they could probably help should write to the Honorary Secretary, Mrs. Frances Woolley, 9 Ranoch Road, Adelaide Road, Surbiton, Surrey KT6 4TE, for details.

The club was founded in 1954 and is affiliated to the R.S.G.B. and publishes 6 News Letters per year.

... COMMENT

AMSAT NEWS

With this year's AMSAT Membership Renewal Subscription Form, comes a message from Tom Clark, AMSAT's President. As he points out, last year the Phase III Satellite was nearing completion at the beginning of the year, when subscription renewal forms were being sent out; the first issue of AMSAT's magazine ORBIT was on the boards and everyone was looking forward to the dawn of a new era in the amateur radio satellite field. The loss of the Phase III satellite on May 23rd., last year, seemed at first to be a calamity from which AMSAT might well not have recovered, but the support which followed appeals for financial and practical help, enabled a second Phase III to be got on the stocks and AMSAT to come back stronger than ever. As Tom Clark points out, a lot is going on, as the following list of projects shows:-

In September 1981, the University of Surrey's UoSAT, Amateur Scientific Satellite will be launched. Much help for this project has come from AMSAT.

In February 1982, the replacement Phase III satellite will be launched.

In mid-1983, another Phase III type amateur radio satellite will be launched, which at the moment is designated Phase III C.

Sometime in 1984, SYNCART, the first synchronous amateur radio satellite will be launched.

With such a list of projects in the pipe-line, AMSAT is still appealing for more subscribers and donations. The Overseas Subscription is now \$20 and a Life Membership subscription can be had for \$200. For those who would find it easier to pay into an account in this country, AMSAT-UK has agreed to accept the AMSAT Corporation subscriptions and donations and forward them on to Washington. They should contact AMSAT-UK's Secretary, Mr. Ron Broadbent, at 94, Herongate Road, Wanstead Park, London, E12 5EQ.

May we take this opportunity of congratulating Dr. Tom Clark, on the recent award to him, by NASA, of a NASA Exceptional Performance Award, for work he has carried out in his professional capacity as a professional radio astronomer. Dr. Clark was leader of a team doing work on "long base-line" radio space surveys.

SONY'S GUIDE TO VIDEOGRAPHY

With UK sales of video recorders forecast to pass the 300,000 mark by the end of the year, Sony has recognised the need both to assist existing owners in utilising their equipment to its best advantage, and also to explain to potential customers the full range of home entertainment which videography now provides.

The company has produced a 48 page full colour handbook containing comprehensive details not only

of the best ways to exploit all the facilities of video recorders, but also how to make home video movies, the use of sound and lighting and even the creation of professional style, special effects and titling.

Amplly illustrated and using simple non-technical language the handbook - entitled 'How to Video' - is currently on sale at Sony London Showroom, 134 Regent Street, London W.1., price 60 pence. It is also available by post from the Showroom (30 pence extra).

50 MHz QUAD TRACE OSCILLOSCOPE


The new leader LBO-517 has all the features expected on a professional 50MHz oscilloscope plus an extremely useful quad trace facility.

Sensitivity is 5mV/DIV for 50MHz, 1mV/DIV (with MAG x5) for 10MHz, and maximum sweep rate is 5nS/DIV with MAG x10.


Comprehensive triggering and synchronisation facilities, a full specification calibrated timebase and variable hold off functions (including B ends A) make the LBO-517 ideal for a wide range of applications in R & D, or for servicing TVs, VCRs, computer peripherals, etc.

Performance is further enhanced by the quad trace facility, channels 3 and 4 being accessed via rear panel sockets and controls, and various alarm indicators to eliminate mis-operations.

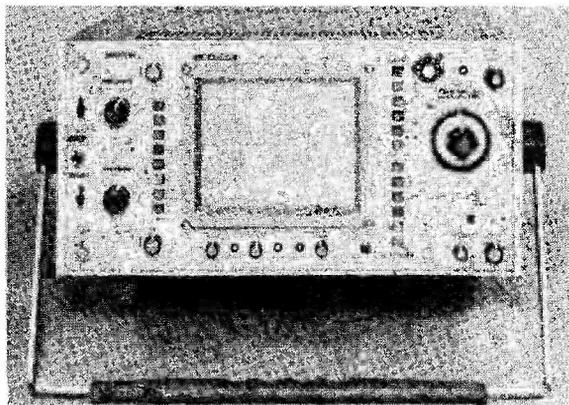The 10 x 8cm high brightness display has an internal graticule to eliminate parallax errors, graticule illumination, and additional 10% and 90% scales to facilitate pulse measurements.



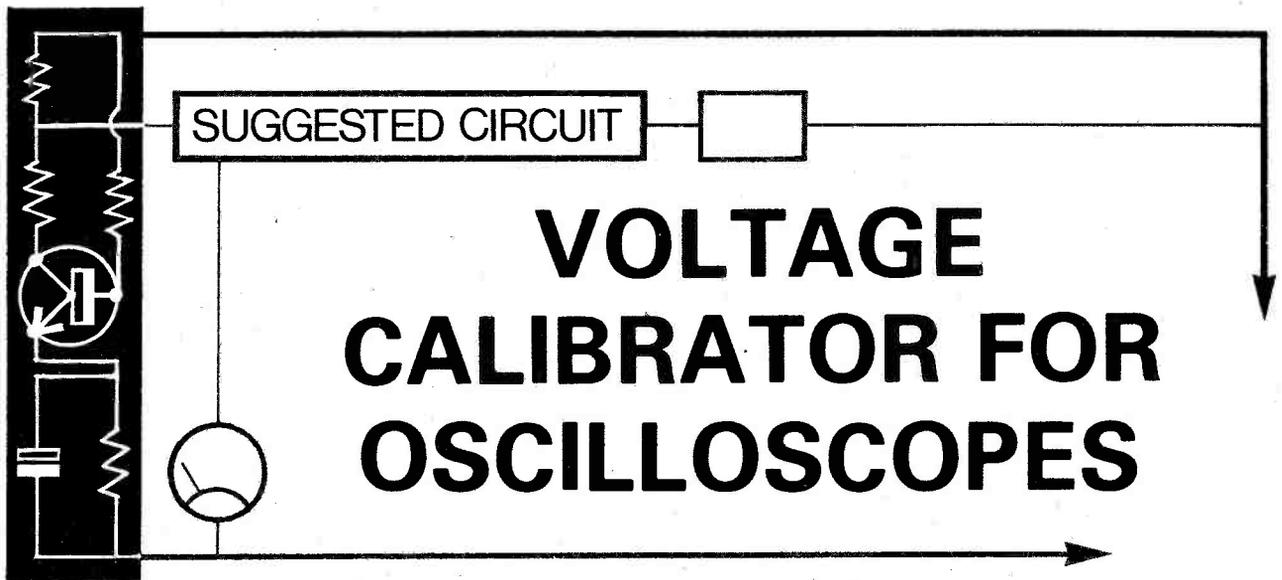Further details can be obtained from: Sinclair Electronics Ltd., London Road, St. Ives, Huntingdon, Cambs. PE17 4HJ.



VOLTAGE CALIBRATOR FOR OSCILLOSCOPES

By G. A. French

From time to time we receive requests from readers for oscilloscope voltage calibrating units. Only a small proportion of home-constructors possess oscilloscopes, of course, and it is for this reason that voltage calibrator circuits appear less frequently than do circuits for more commonly employed items of amateur-built test equipment. On the other hand, oscilloscope voltage calibrator circuits represent an interesting branch of hobby electronics because they demonstrate how high degrees of accuracy can be achieved with only a few components in quite simple designs. Also, an oscilloscope voltage calibrator can double as an audio frequency signal generator!

CALIBRATOR CIRCUIT

The calibrator circuit appears in Fig. 1. In this, IC1 runs as an astable multivibrator whose frequency is controlled by R1, R2, R3 and C1. Because R2 is equal to R3, and R1 is equal to 4 times R2, the multivibrator produces a 50 : 50 square wave. The presence of R1 causes the oscillator frequency to be slightly higher than the calculated value taken from the values of R2, R3 and C1, and in practice it is approximately 1kHz.

The 555 output, at its pin 3, is applied via the constant current device IC2, to the potential divider chain consisting of R5, R6 and R7. A constant current flows through the chain when the 555 output is high, and there is zero current in the chain when the 555 output is low. Thus, a positive going square wave is built up across

the chain, its voltage magnitude depending upon the constant current and the resistance values in the chain.

The required constant current is 5mA. It will be seen that the sum of the values of R5, R6 and R7 is 200Ω whereupon, from Ohm's Law, a constant current of 5mA will cause 1 volt to appear across the three

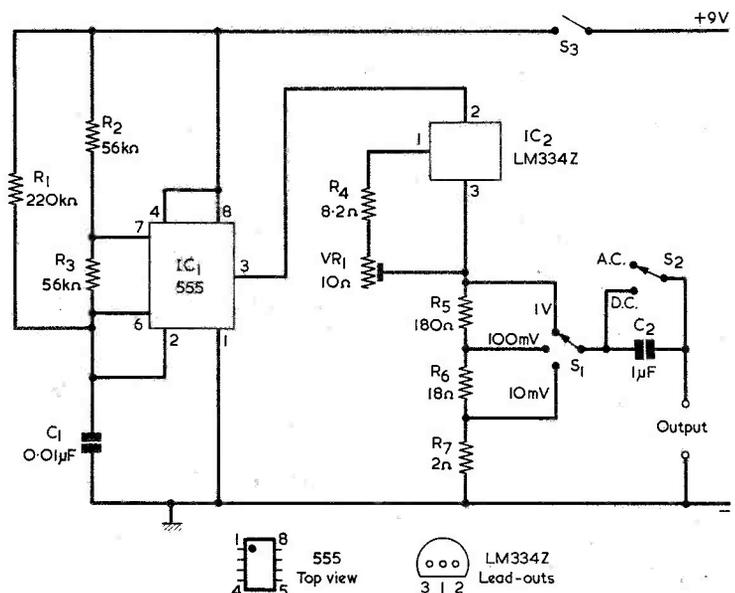


Fig. 1. The circuit of the voltage calibrator. A constant current of 5mA passes through R5, R6 and R7 when the 555 output is high. No current flows through these resistors when the 555 output is low.

resistors. The values of R6 and R7 add up to 20Ω , so that the constant current of 5mA produces a voltage of 100mV across these two resistors. The value of R7 is 2Ω , allowing a voltage of 10mV to appear across it. One of these three voltages is selected by S1 and passed to the calibrator output. The use of a relatively high constant current through the potential divider chain enables the calibrator output impedance to be low, and the d.c. output resistance is 200Ω maximum.

IC2 is an LM334Z and the constant current it passes is controlled by the external resistance between its pins 1 and 3. The current, in amps, is approximately equal to 0.0677 divided by the external resistance in ohms, and the calculated resistance value is equal to 13.54Ω . There is, however, a tolerance of 3% on the current value and it is necessary to make the external resistance adjustable about the calculated value. In Fig. 1 the external resistance is given by R4 in series with the pre-set potentiometer, VR1.

The square wave selected by



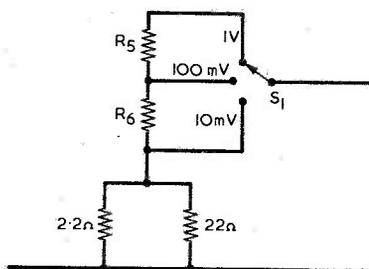


Fig. 2. If difficulty is experienced in obtaining a close tolerance 2Ω resistor for R7, a 2.2Ω resistor and a 22Ω resistor connected in parallel will provide the required resistance.

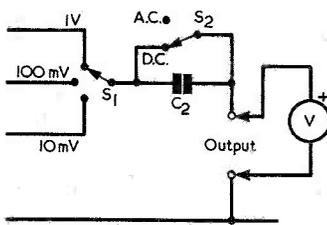

(a)

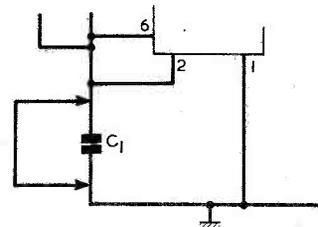

(b)

Fig. 3(a). For setting-up purposes, a voltmeter is connected to the output terminals, and S1 and S2 are put to the positions shown here.

(b). A temporary short-circuit is then placed across C1 to drive the 555 output high.

S1 is passed directly to the output terminals when S2 is in the "D.C." position. Setting S2 to "A.C." allows a capacitive output coupling via C2. S3 is the on-off switch, and the current drawn from the 9 volt supply is approximately 9mA.

COMPONENTS

The 555 required for IC1 is, of course, widely available. It should be noted that the CMOS version, the ICM7555, is not suitable for this circuit because it cannot provide the output source current required. The LM334Z required for IC2 is available from Maplin Electronic Supplies. In the inset showing its lead-outs, these lead-outs are pointing towards the reader.

R1, R2, R3 and R4 are all $\frac{1}{4}$ watt 5% resistors. R5, R6 and R7 are close tolerance $\frac{1}{4}$ or $\frac{1}{2}$ watt resistors, and these should be 2% or, better, 1% types. If difficulty is experienced in obtaining a 2Ω resistor in close tolerance for R7, a 2.2Ω and a 22Ω resistor can be connected in parallel, as shown in Fig. 2. These give a combined value of almost exactly 2Ω .

S1 is, of course, a 3-way rotary switch. Both S2 and S3 can

be s.p.s.t. toggle components. S2 is shown as s.p.d.t. in Fig. 1 for ease of circuit presentation. The two capacitors may be polyester.

Because of its low value, VR1 is not normally available in the usual range of miniature pre-set potentiometers. A small wire-wound component should be employed here.

The calibration unit can be housed in a small metal case which is common with the negative supply rail. Alternatively a plastic case may be employed and the chassis connection shown in Fig. 1 is then ignored.

SETTING UP

A voltmeter, which can be a multimeter switched to a low volts range, is required for setting up. This is connected to the output terminals with S1 set to the "1V" position and S2 set to "D.C.", as shown in Fig. 3 (a). A short-circuit, as illustrated in Fig. 3(b), is then applied across C1. This causes the 555 output to go high. VR1 is next adjusted for a reading of exactly 1 volt in the meter.

The voltmeter and short-circuit are then removed, after which the voltage calibrator is ready for use. ■

OBITUARY

It is with deep regret that we have to inform readers that our Technical Editor, Mr. J. R. Davies, died on 7th. February after a very short illness.

Mr. Davies was 57 years of age and, prior to becoming a technical journalist, he was engineer in charge of the television component and sub-assembly factory of Ferguson Radio Corporation Ltd., (now Thorn Electric) at Enfield, Middlesex. Before being appointed Technical Editor of this magazine he had frequently written articles which appeared in these pages and his writing and his editing were notable for their thoroughness and accuracy. All of us who worked with him at Data Publications looked upon him as a personal friend and regarded him with affection - he will be greatly missed.

The funeral service took place at Taunton Crematorium on Wednesday 11th. February at which we were represented by the Production Editor and Advertisement Manager.

To his daughter we extend our deep sympathy and condolences.

J.H.B.

SOLDERING IRON REMINDER

By John Baker

UNOBTRUSIVE AUDIBLE DEVICE

Functions when iron is switched on

A common problem for radio and electronics constructors is that of inadvertently leaving a soldering iron switched on. This usually results in the iron running continuously for many hours before the oversight is discovered, with a consequent reduction in the life of the bit and element. Probably of greater importance is the fact that the soldering iron can present a fire hazard, and the author has some scorched circuit diagrams and carbon papers to illustrate this point. Yet another factor is that one can burn one's fingers or hand by touching an iron which is supposedly switched off. All these points led to the development of the very simple unit which is described in this article.

AUDIBLE REMINDER

In the author's experience there are no difficulties in remembering whether an iron is switched on if it is one of the thermostatically controlled types having an internal bi-metal strip temperature controller. An iron of this nature produces a quiet but clearly audible "clicking" as the bi-metal thermostat switches on and off. The sound helps to remind the user that the iron is switched on, and he is in consequence much more liable to remember to switch off the iron before leaving it.

One solution to the problem, therefore, is to have some form of audible reminder circuit connected in parallel with the iron, so that the user is frequently given a signal that the iron is switched on. Such a

reminder can be employed with ordinary irons which are not thermostatically controlled.

It is not necessary for the audible reminder signal to be especially loud or complex, since the unit will be in very close proximity to the user and it would be difficult to miss even a quiet and simple signal. In fact, a loud and complex sound is undesirable because it would soon become very tiresome and irritating! In practice a very suitable signal is a fairly quiet "click" produced at about 10 second intervals – the same sort of sound, in fact, as is given with a temperature controlled iron.

THE CIRCUIT

The circuit finally developed is extremely simple, and is shown in Fig. 1. The unit is permanently connected in parallel with the soldering iron so that it is powered whenever the iron is plugged into the mains supply. The live and neutral mains lines are coupled to the primary of mains transformer T1. The secondary voltage is full-wave rectified by D1 and D2, causing a smoothed voltage to appear across C1. This voltage, unloaded, is of the order of 17 volts. Since the main part of the circuit only consumes some 3mA, the loaded supply voltage is not significantly different.

The rectified supply voltage is by no means critical, and the unit will work just as well with a mains transformer having a secondary voltage of 9-0-9 volts or 6-0-6 volts. It is quite in order to use one of these alternative transformers if the construc-

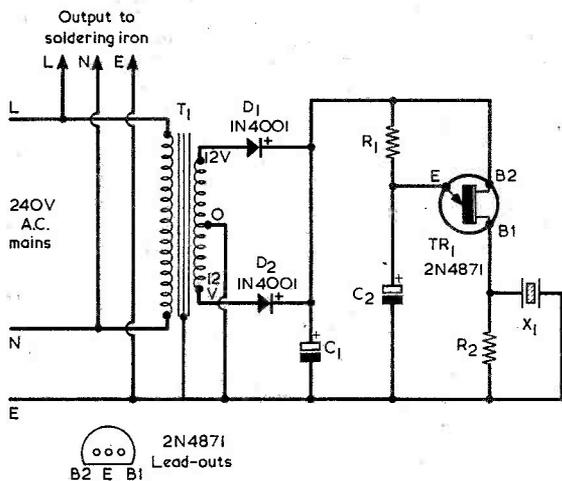


Fig. 1 The circuit of the soldering iron reminder. X1 is a piezoelectric acoustic transducer.

COMPONENTS

Resistors

(Both $\frac{1}{4}$ watt 5%)

R1 680k Ω
R2 120 Ω

Capacitors

C1 10 μ F electrolytic, 25V. Wkg.
C2 10 μ F electrolytic, 25V. Wkg.

Transformer

T1 mains transformer, secondary 12-0-12V at 50mA (see text)

Semiconductors


TR1 2N4871
D1 1N4001
D2 1N4001

Transducer

X1 ceramic transducer type PB-2720 (Ambit International)


Miscellaneous

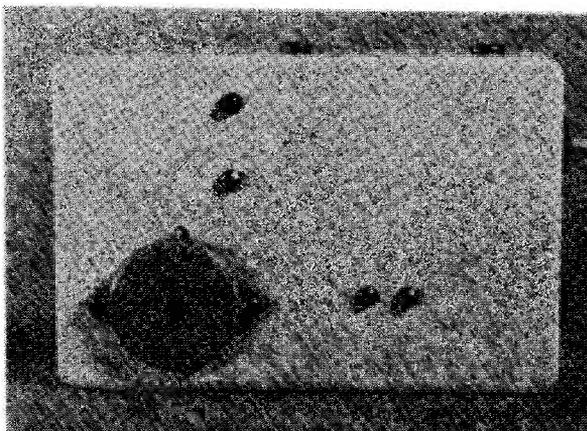Plastic case
Veroboard, 0.1in. matrix
3-way connector block
3-core mains lead
2 grommets
Nuts, bolts, wire, etc.



The soldering iron reminder in its plastic case. The ceramic transducer is fitted on the outside.

The 3-way connector block and Veroboard assembly are mounted on the other side of the panel to which the transducer is fitted. The mains transformer is bolted to one side. The mains input lead was not fitted when these photographs were taken.

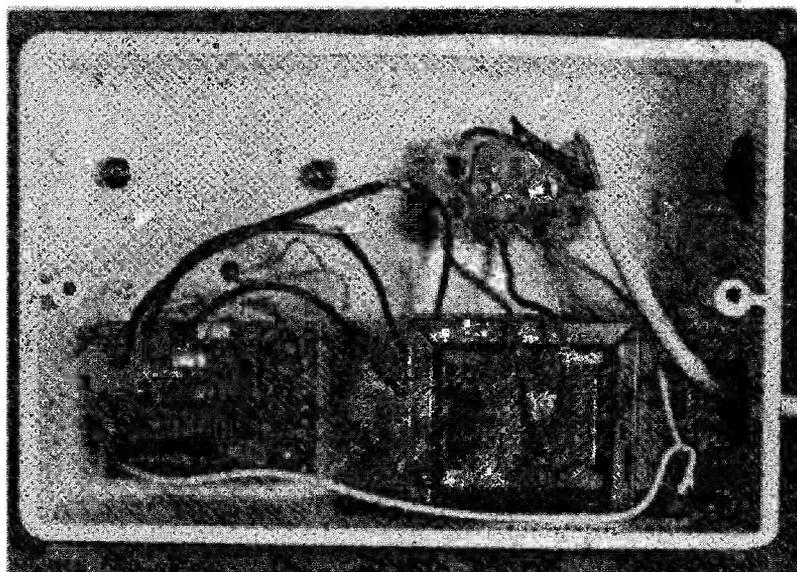


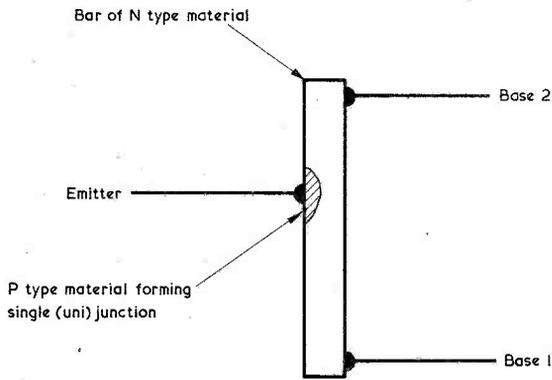


Fig. 2. Basic construction of a unijunction transistor.

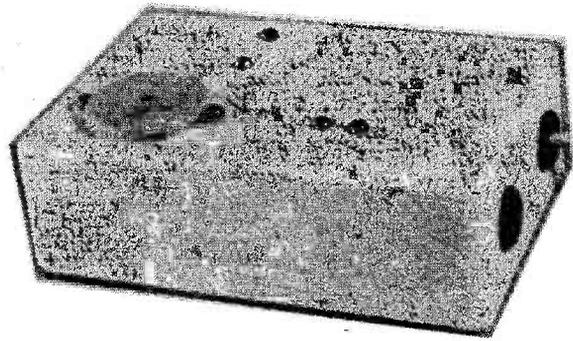

The reminder can be positioned at any convenient point on the work bench.

tor happens to have one in the spares box.


A unijunction transistor relaxation oscillator generates the reminder signal. For those unfamiliar with the unijunction transistor, this has the basic construction shown in Fig. 2. There is a bar of silicon between the base 1 and base 2 terminals with an emitter junction nearer the base 2 end of the bar. Normally, the bar is N-type material and the emitter material is P-type. When the base 2 and base 1 are connected into circuit as in Fig. 1, and the voltage at the emitter is low, the bar presents a resistance in the order of 4 to 9k Ω . It therefore functions as a potential divider with a proportion of the voltage between the two bases appearing between the emitter junction and the base 1. This proportion is known as the "intrinsic stand-off ratio".

When the emitter is below the intrinsic stand-off level the only emitter current which flows is reverse leakage current in the emitter PN junction. This situation is maintained if the emitter is taken positive, but it changes abruptly when the emitter potential reaches intrinsic stand-off level plus about the 0.5 to 0.6 volt needed for a silicon diode to conduct. The device then exhibits a very low resistance between the emitter and the base 1.


Turning back to Fig. 1, capacitor C2 is discharged at switch-on, and it then commences to charge via R1. The voltage on the unijunction transistor emitter is, in consequence, going positive. When the voltage reaches triggering level the transistor exhibits the very low resistance between the emitter and base 1, causing the capacitor to rapidly discharge into R2. The voltage across the capacitor falls to a low level before the transistor reverts to its previous state, after which the capacitor once more commences to charge through R1.

A sharp pulsed voltage is produced across R2 at each discharge of C2, and this is applied to the piezoelectric transducer, X1. The transducer produces a quiet "click" with each pulse, and the volume was found to be adequate for the application.

The values of R1 and C2 are chosen to give a nominal operating frequency of 0.1Hz, or to produce one "click" every 10 seconds. However, the actual frequency will vary significantly between different units built to the circuit due, mainly, to the wide tolerance in the value of C2, and in the intrinsic stand-off ratio of the transistor. The latter is specified as 0.7 to 0.85 for the particular transistor

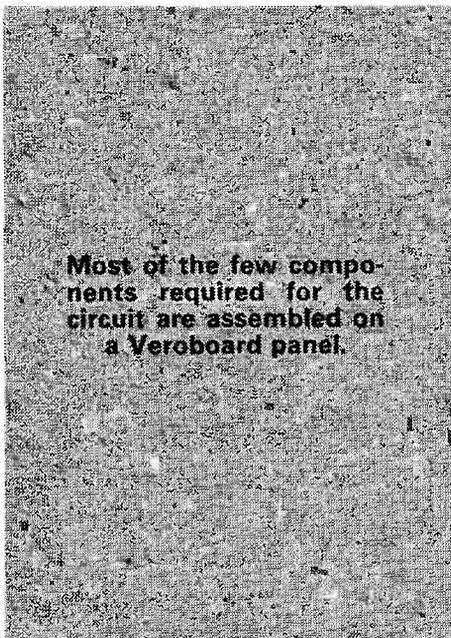

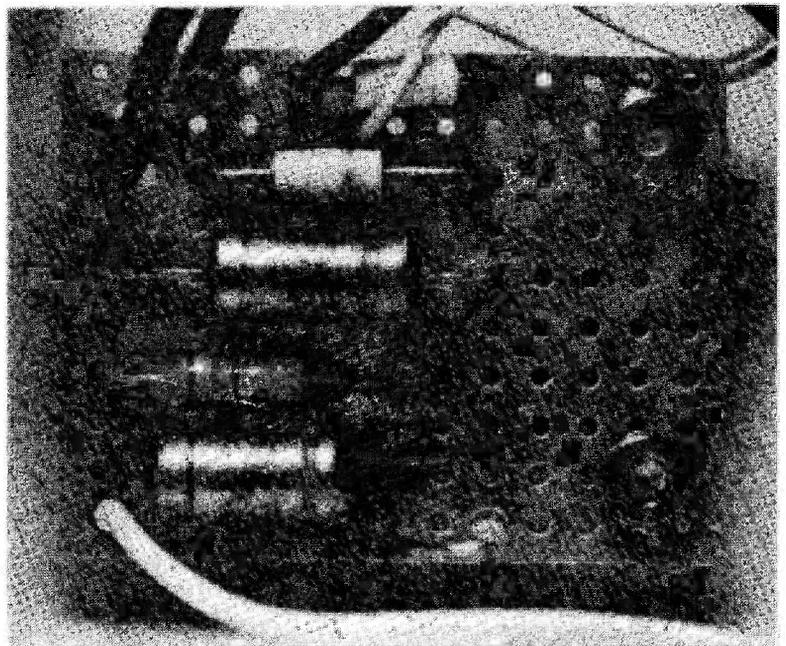Most of the few components required for the circuit are assembled on a Veroboard panel.



employed here. The operating frequency of the circuit is obviously of no great importance and a variation from the nominal value of 0.1Hz presents no disadvantage.

CONSTRUCTION

The prototype was assembled in a small plastic case measuring 114 by 76 by 38mm. This case is a type PB1, available from Maplin Electronic Supplies. Any other small plastic case which can accommodate the components can, of course, be used and there are many suitable types available. The general layout used for the prototype can be seen in the photographs. The transducer is mounted on the case exterior and can be used as a template when marking the positions of the two mounting holes in the case. The transducer mounting holes are very small but they can be enlarged slightly to take 8 or 6BA mounting bolts. A small hole must also be drilled just below the transducer to allow its leads to pass through.

A 3-way connector block is used to take the mains wiring and this is secured to the plastic case with suitable nuts and bolts. These connector blocks are usually sold in 12-way strips, and the 3-way block is cut from one of these with a sharp knife. Two holes fitted with grommets are required in one of the case sides. One takes a 3-core lead from the mains plug and the other takes the lead from the soldering iron.

Apart from T1, which is bolted to one side of the case, the remaining components are assembled on a small piece of 0.1in. Veroboard having 13 copper strips by 10 holes. Fig. 3 shows this board and the other wiring. No breaks in the copper strips are required. Note that there is a solder tag under one of the transformer mounting nuts. The mains earth connects to this tag, as also does the oscillator negative rail. Take care to ensure that all the mains wiring is properly carried out.

When it has been wired up, the Veroboard panel is secured inside the case with two 6BA bolts and

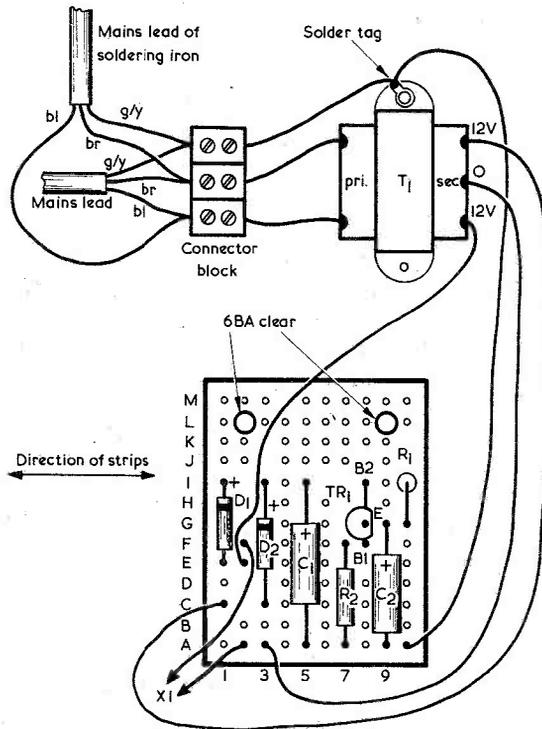


Fig. 3. Wiring up the soldering iron reminder.

nuts, spacing washers being employed to keep the board underside clear of the inside surface of the case. After the wiring has been completed and checked, the soldering iron reminder unit is ready to start "clicking". The lid of the plastic box must always be firmly screwed on when the unit is in use.

TRADE NOTE

RATCHET-OPERATED CABLE CUTTER


A new hand-held cable cutter, introduced by Klippon, features an integral ratchet mechanism to ensure positive gripping and cutting action when used with a range of copper or aluminium cables with an outer diameter up to 32mm.

The KT 3's unique design enables cables to be cut with a fraction of the pressure normally associated with cable cutters whilst a cutting blade release lever enables the cutting process to be interrupted in any position. A grip locking/unlocking device is provided just below the cutter.

Weighing just 590 grammes, the KT 3 is manufactured from high-quality steel with heavy-duty vinyl protecting the handles and providing a firm grip. Finger-guards are provided on the handles to increase the safety aspects of the tool.

Replacement blades are available.

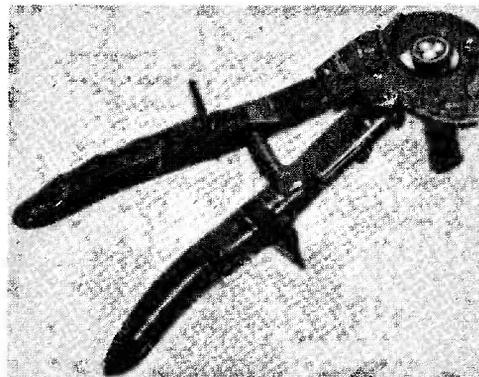For further details, contact:- Klippon Electricals Ltd., Power Station Road, Sheerness, Kent ME12 3AB.



The ratchet-operated cable cutter.

Timer With Trigger Action

By F. Craig

Positive feedback gives snap switching.

Electronic timers normally employ a resistor and capacitor to provide the timing period. A typical timer circuit is illustrated in Fig. 1(a), in which R_A and C_A are the timing components. Some form of voltage comparator is required to sense the voltage across the capacitor and this can be an operational amplifier with one input connected to the junction of the capacitor and resistor and the other input connected to a reference voltage which could, conveniently, be half the supply voltage.

CHARGING CAPACITOR

At the start of the timing period the capacitor is discharged. In our example the capacitor is connected to the non-inverting input of the op-amp and so the op-amp output is low and the transistor following the op-amp is cut off.

The capacitor is then allowed to charge. When its voltage closely approaches the reference voltage at the op-amp inverting input the op-amp output starts to go high. Due to the very high level of voltage gain

in an operational amplifier the relatively slow rise in voltage across the capacitor is translated into a much more rapid voltage swing at the op-amp output, whereupon the transistor is turned on and the relay is energised. The timing period is then at an end.

The arrangement of Fig. 1(a) is acceptable for long timing periods with heavy duty relays and can be employed for periods up to about a minute or two with lightweight relays such as the popular 410 Ω "Open Relay" which is available from Maplin Electronic Supplies and other sources. When longer periods with a lightweight relay are required, the change in op-amp output voltage at the end of the timing period, although reasonably fast, is still too slow for reliable relay operation. With the Open Relay just referred to, the gradually increasing relay current at the end of the timing period can cause noticeable relay "chatter", with the armature moving irregularly between its two contacts.

This problem can be overcome by introducing positive feedback as shown in Fig. 1(b), where the feedback is provided by the two resistors R_B and R_C . When, during the timing period, the voltage across the capacitor is low and the op-amp output is similarly low, the voltage applied to the non-inverting input is equal to the fraction of the capacitor voltage which is given at the junction of R_C and R_B . As, with the capacitor charging, this voltage closely approaches the reference voltage at the inverting input the op-amp output starts to go positive. In doing so it causes the voltage at the non-inverting input to go positive as well, making the op-amp output more positive again. This positive feedback results in the op-amp output swinging rapidly high and thereby causing the relay to energise quickly without risk of chatter or any other similar effect.

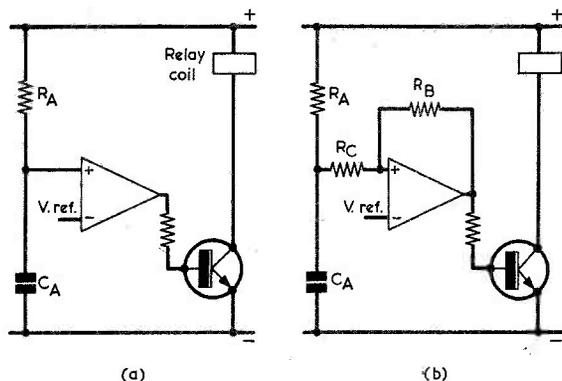


Fig. 1(a). A typical electronic timer. Capacitor C_A is discharged at the start of the timing period, the length of which is controlled by the values of C_A and R_A

(b). Irregular relay operation at the end of very long timing periods can be eradicated by incorporating positive feedback around the voltage comparator

WORKING CIRCUIT

The full working circuit of the timer is shown in Fig. 2. The operational amplifier is a CA3140E, which has very high resistance MOSFET inputs. A reference voltage equal to half the supply voltage is given at the junction of the equal value resistors R_4 and R_5 , and this voltage is applied to the inverting input at pin 2. The timing resistance is given by R_2 and VR_1 in series, and the timing capacitance consists of whichever capacitor is switched into circuit by S_1 . The feedback resistors, R_B and R_C of Fig. 1(b), are now given

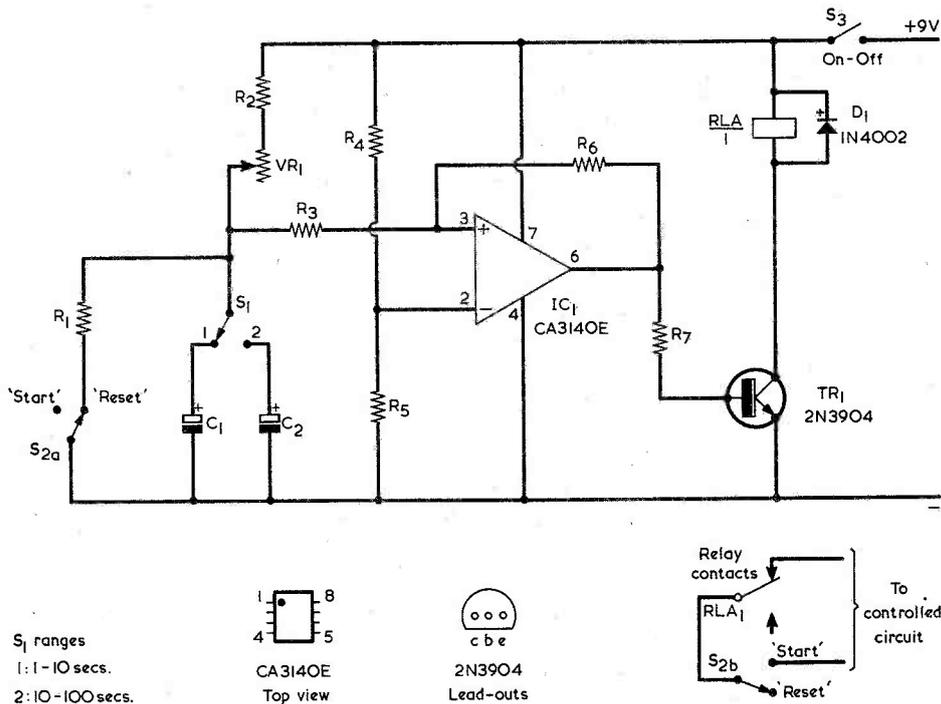


Fig. 2. Full working circuit of the timer with trigger action. The ranges selected by S1 are nominal, but should be within the travel of VR1 with most electrolytic capacitors

by R6 and R3 respectively. The op-amp output is coupled to TR1 base by way of R7, and the relay coil is connected in the transistor collector circuit. D1 is the usual protective diode which prevents the formation of a high back-e.m.f. when the relay de-energises.

S2(a) (b) is the Start - Reset switch. When this is in the Reset position, S2(a) short-circuits the timing capacitor selected by S1 via the current limiting resistor, R1. At the same time, S2(b) keeps the controlled circuit open. Setting S2(a) (b) to Start takes the short-circuit off the timing capacitor. Also, S2(b) completes the controlled circuit by way of the break contacts of the relay.

The timing capacitor now charges. After a period dependent upon the value of the capacitor and the resistance inserted by VR1, the voltage at the non-inverting input of the CA3140E closely approaches that at the inverting input. The positive feedback effect just described comes into action and the relay energises rapidly. Its break contacts break the controlled circuit and the timing period is over.

TIMING COMPONENTS

Due to the presence of R6 and R3 the timing period comes to an end when the voltage across the capacitor is 0.55 times the supply voltage. This calculates as 0.8 times the time constant of the timing components. However, since the timing capacitors are electrolytic with a typical tolerance on value of -10 + 50%, it can be expected that the actual values of C1 and C2 will be in excess of their nominal values. Because of this fact, it can be assumed that the length of a timing period is roughly equal to the time constant of the timing resistance and capacitance (which, in seconds, is equal to megohms multiplied by microfarads). Timing ranges can then be calculated by

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated)

- R1 10 Ω
- R2 6.8k Ω
- R3 1M Ω
- R4 100k Ω
- R5 100k Ω
- R6 10M Ω 10%
- R7 10k Ω
- VR1 100k Ω potentiometer, linear

Capacitors

- C1 100 μ F electrolytic, 10V. Wkg.
- C2 1,000 μ F electrolytic, 10V. Wkg.

Semiconductors

- IC1 CA3140E
- TR1 2N3904
- D1 1N4002

Relay

- RLA Open Relay, 410 Ω coil, changeover contacts

Switches

- S1 s.p.d.t. toggle or rotary
- S2 d.p.d.t. toggle
- S3 s.p.s.t. toggle

Miscellaneous

- 9 volt battery
- Pointer control knob
- Wire, solder, etc.

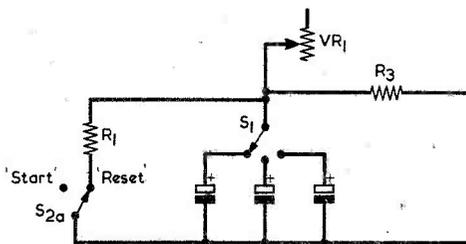


Fig. 3. Alternative ranges can be incorporated by simply choosing different values of timing capacitor. Here, S1 is changed to a 3-way switch, offering three timing ranges

assuming that the minimum timing resistance is 10k Ω and the maximum timing resistance is 100k Ω . Since R2 is considerably lower in value than 10k Ω , it should be possible to obtain, within the travel of VR1, the ranges quoted with most electrolytic capacitors. It is unlikely that C2 will be precisely 10 times C1, whereupon it will be necessary to provide two scales for VR1. To make up the scales some four well spread out calibration points are found on each range, and the scales are then marked out from these. The calibration points are found by checking timing periods

with a watch having a sweep second hand or a digital display.

Any capacitance values other than those specified can be employed. If desired, there could be three ranges, as illustrated in Fig. 3, with S1 being 3-way rotary. When there are two ranges, S1 can be rotary or toggle. S2(a) (b), on the other hand, must be toggle.

To withstand initial charging currents, VR1 should be a $\frac{1}{2}$ watt potentiometer. This is the normal rating for a standard sized linear carbon track potentiometer. Because of its MOSFET inputs, care should be taken to ensure that the CA3140E is not damaged by high static voltages, and it should be soldered into circuit with an iron having a reliably earthed bit. Alternatively, an 8-way d.i.l. holder can be used, and the CA3140E plugged into this after all wiring has been completed and checked.

The 410 Ω relay specified for RLA has contacts with a maximum rating of 5 amps at 24 volts d.c. or 240 volts a.c.

The current drawn from the 9 volt supply is approximately 1.5mA during the timing period. This increases to some 23mA when the relay energises at the end of the period. The prototype timer was checked with a temporary timing capacitance which produced a period in excess of 5 minutes. The relay energised quickly and properly at the end of this period. ■

Further Notes on Some Recent Receivers

Part 2 (Conclusion)

by Sir Douglas Hall, Bt., K.C.M.G.

More modifications to enhance the performance of recent receivers.

THE "DORIC"

This multi-band receiver appeared in the four issues between August and November 1979. The only problem encountered with this design has been that the volume control on the amplifier, when adjusted very nearly at its maximum position whilst listening on the short wave bands, has an effect on reaction. The snag is easily overcome by putting a 3.3k Ω resistor between the short wave tuner and the amplifier as shown in Fig. 3.


In some circumstances on some of the short wave bands it may prove advantageous to set the length of the aerial to suit selectivity, adjust VR3 to a suitable setting and use VR1 as a very smooth vernier reaction control.

"LISA"


The article describing this receiver appeared in the magazine issues for September and October 1980. If for any reason it is found that the wavebands are not

Fig. 3(a). The "Doric" receiver can have a 3.3k Ω resistor added to prevent slight interaction between volume and reaction controls on short waves.

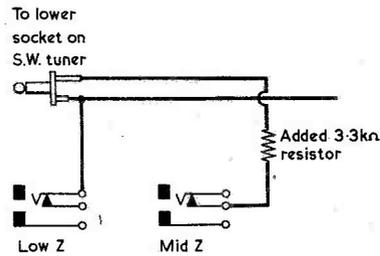(b). Showing how the added resistor is wired into circuit.



(a)

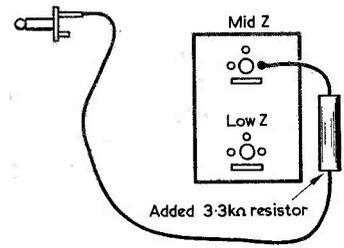

(b)

properly covered the values of C3 and C4 can be altered accordingly.

C10 and C11 are included in the interests of stability. In most cases C10 may be removed and C11 changed to 0.1 μ F (using the C10 component), giving equal stability and a slight improvement in output quality.

Provided that it has proved possible to set up the receiver so that the reaction control does not have to be moved through more than about 20 degrees to maintain the receiver on the threshold of oscillation throughout the whole of the medium wave band it is worth carrying out the following modification. Change the value of VR3 from 2.2k Ω to 1k Ω and wire the slider of this new component to the outer unused tag of S1 (b) instead of to the centre tag. When this 1k Ω component is properly adjusted it should be found that reaction comes in extremely gradually. The altered wiring causes a little extra resistance to be included in the reaction circuit when switched to long waves, in order to maintain proper control on this band with the new pre-set potentiometer.

F.M. BANDS IN GENERAL


Finally, it might be useful to provide a few notes on problems which can arise when listening on the f.m. band with the "Jubilee," the "Band II Portable" or the "Doric". The comments also apply to any of the earlier receivers described by the author which provides an f.m. band and use a self-contained telescopic aerial, and to many similar non-superhet receivers in addition.

Excessive hiss or hand-capacitance effects nearly always mean that there is insufficient signal, either due to distance from the transmitter or screening. Different positions should be tried for the receiver. Sometimes there is one part of a room where the reception is much better than in other parts. Also, try different lengths of aerial, as well as different angles

and changes in the direction in which the aerial points. Aerial length can sometimes be quite critical in bad reception areas. The only other likely cause of excessive hiss and hand-capacitance effects is a faulty transistor. In the author's designs the culprit will be the Spontaflex amplifier – the one with the diode in its emitter circuit. This transistor is more critical than the input amplifier, to which the aerial is connected through a capacitor. On at least one occasion a marked improvement has been effected by swapping the two transistors round.

Other problems can arise when the receiver is in a very strong signal area, close to the transmitter. Here again the length of the aerial can be quite critical, this time to avoid overloading. Sometimes the receiver will work best in these conditions with the aerial completely closed or even removed altogether. Generally, however, some 12in. of aerial, carefully orientated, will give best results.

(Concluded)

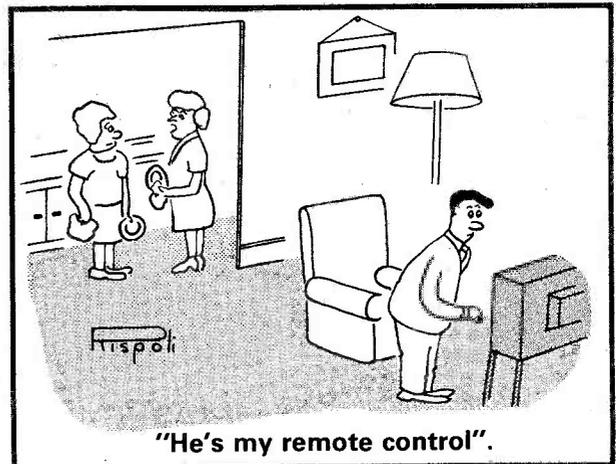

Mail Order Protection Scheme

The publishers of this magazine have given to the Director General of Fair Trading an undertaking to refund money sent by readers in response to mail order advertisements placed in this magazine by mail order traders who have become the subject of liquidation or bankruptcy proceedings and who fail to supply goods or refund money. These refunds are made voluntarily and are subject to proof that payment was made to the advertiser for goods ordered through an advertisement in this magazine. The arrangement does not apply to any failure to supply goods advertised in a catalogue or direct mail solicitation.

If a mail order trader fails, readers are advised to lodge a claim with the Advertisement Manager of this magazine within 3 months of the appearance of the advertisement.

For the purpose of this scheme mail order advertising is defined as:

"Direct response advertisements, display or postal bargains where cash has to be sent in advance of goods being delivered."

Classified and catalogue mail order advertising are excluded.

MODEL TRAIN CONTROLLER

By M. V. Hastings


*Low impedance
"constant voltage"
output.*

* * *


*Continuously vari-
able voltage control.*

* * *

*Low cost mains
operation.*

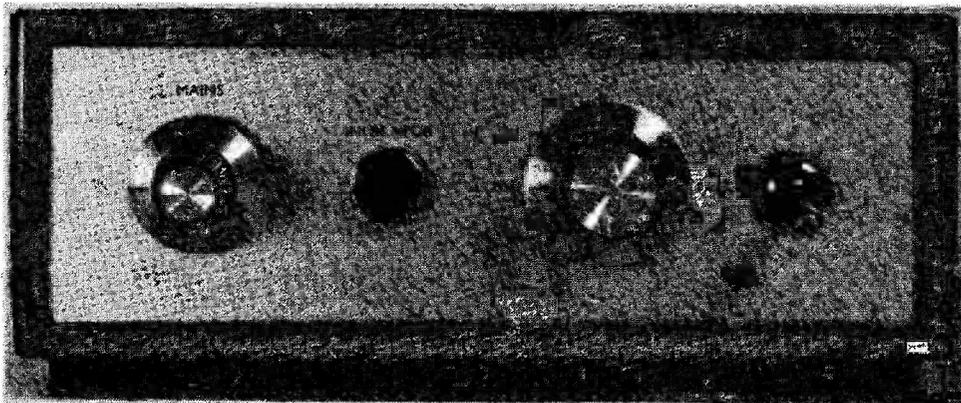

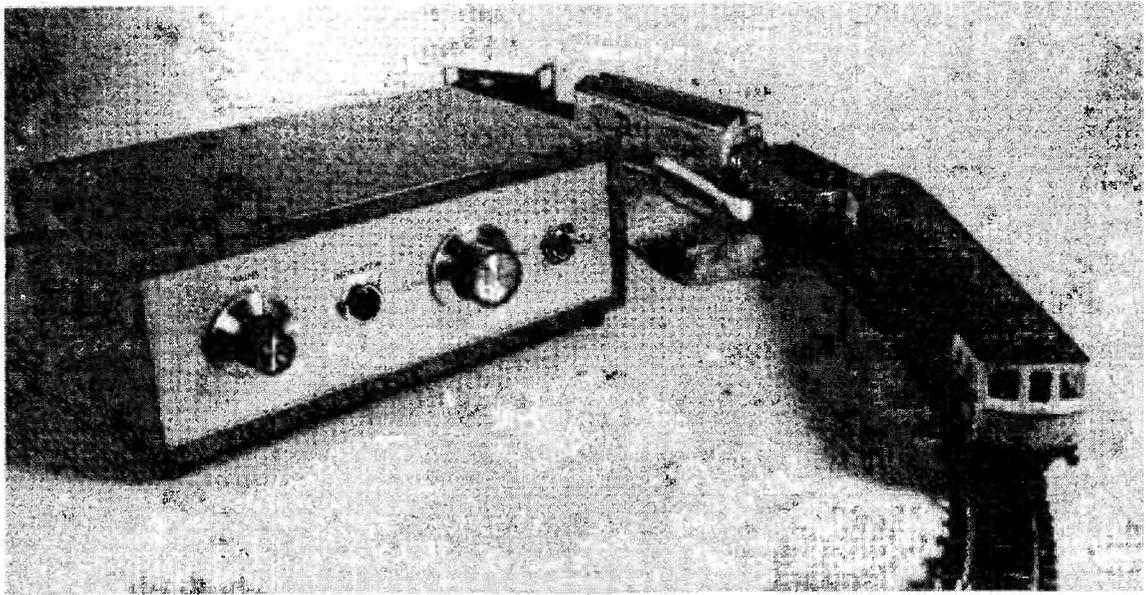On the front panel, from left to right, are the mains on-off switch, the pilot lamp, the output voltage control and the Forward-Reverse switch.



The train controller in action as the 10.55 from Waterloo negotiates a bend in the tracks.

This simple model train controller has been designed for use with an inexpensive train set which was originally supplied with a combined battery box and controller. This employed six HP11 cells and, while their cost was not too high initially, the expense soon started to mount up as replacement sets became necessary. Battery operation became, in consequence, uneconomic in the long term. The controller section also had the initial advantage of being very inexpensive but the control it exerted was rather limited, in that it only had three speed settings. These were "Stop", "Slow" (with four cells switched into circuit) and "Fast" (all six cells switched in).

These factors led to the design and construction of the mains powered controller which is described here. This can be built at reasonable cost and provides a continuously variable full range of speeds. It also gives a low output impedance at all output voltages, whereupon a good performance is given even at low running speeds.

TYPES OF CONTROLLER

The simplest type of mains driven controller giving a full range of speeds merely consists of a transformer to give isolation and step down the mains voltage to the required level, a rectifier to produce a pulsating d.c., and a large variable resistor in series with the output to vary the output current and act as a speed control. Some form of polarity reversal switching is usually incorporated so that the direction of the train can be altered.

A serious problem with this arrangement is that the output impedance of the controller becomes high at low speeds due to the relatively high resistance inserted by the variable speed controller. This is apt to lead to the train running fast down slight gradients

and stalling when trying to climb a gradient.

The reason for this effect is that the output impedance of the controller and the impedance of the train motor effectively form a potential divider. When the train attempts to climb a gradient its motor impedance reduces with the increased loading, and the voltage across it falls. Whilst this causes the current fed to the motor to be increased, the high output impedance of the controller results in the actual power applied remaining roughly the same or even decreasing! With the train requiring increased power, but getting the same or decreased power, it is not surprising that it should stall and come to a halt.

An opposite effect is given when the train runs down a gradient, with the motor requiring less current and having increased impedance. This results in a small decrease in the supply current which is counteracted by a rise in the voltage across the motor. The power fed to the motor therefore remains much the same or increases slightly, resulting in the train accelerating.

Another, related, problem with this type of controller is a poor starting performance. Slowly advancing the speed control from zero does not result in the train starting off smoothly, and gradually accelerating up to full speed. Instead, nothing happens at first and then the train suddenly starts off at high speed.

This last effect is caused by the motor having a very low impedance when it is stationary and a comparatively higher impedance when it is running. Thus, there is very little voltage across the motor at first, and when the train does begin to move the voltage across the motor rises dramatically, resulting in a start at a fast rate.

One way of obtaining improved performance is to use a controller of the so-called constant voltage

type. This employs a variable voltage regulator in place of the variable resistor, so that the voltage across the motor does not vary when its current consumption changes due to loading. If the motor tries to draw more current when the train is climbing a gradient it is therefore able to do so, and the increased power causes the risk of stalling to be greatly reduced. Conversely, if the motor tries to consume less current and power it is again able to do so. Improved starting is also given, and with a little skill and practice it is possible to have quite realistic starting. It is a train controller of this type which is described in this article.

CONTROLLER CIRCUIT

By taking advantage of an integrated circuit power amplifier it is possible, as is shown in Fig. 1, to make up a controller having only a small number of components.

S1(a) (b) is the on-off switch, and it controls the mains supply to the isolation and step-down transformer, T1. PL1 is a pilot lamp, and consists of a panel-mounting neon indicator with integral series resistor suitable for 240 volt a.c. operation.

The rectified output from D1 and D2 is smoothed by C1. It is not necessary to have a smoothed d.c. supply for a d.c. electric motor, but the voltage control circuitry requires a reasonably well smoothed supply, and it is for this reason that C1 is included.

IC1 is primarily intended to function as an audio power amplifier, but it is quite suitable for a wide range of other applications. It is very much like an operational amplifier, and has both inverting and non-inverting inputs. Unlike an operational amplifier which, in most cases, can provide an output current in the order of milliamps, the TDA2006 specified for IC1 can provide output currents up to a few amps. The i.c. is available from Maplin Electronic Supplies.

The output of the TDA2006 is connected directly to its inverting input, and the consequent 100% feedback causes it to function as a voltage follower. The output voltage, which is at low impedance, is then (within limits) equal to the voltage at the non-inverting input. The voltage at the non-inverting input can be varied from zero to the full supply potential by adjusting VR1. The output of the

COMPONENTS

Resistor

VR1 10k Ω potentiometer, linear

Capacitors

C1 1,000 μ F electrolytic, 16V. Wkg.

C2 10 μ F electrolytic, 16V. Wkg.

C3 10 μ F electrolytic, 16V. Wkg.

Transformer

T1 mains transformer, secondary 9-0-9V, 1A

Semiconductors

IC1 TDA2006

D1-D4 IN4001

Switches

S1(a) (b) d.p.s.t., mains rotary switch

S2(a) (b) d.p.d.t., toggle

Fuse

FS1 1A fuse, quick blow, 20mm. cartridge

Lamp

PL1 panel-mounting neon indicator with integral series resistor

Socket

SK1 4mm. insulated socket, red

SK2 4mm. insulated socket, black

Miscellaneous

Verocase type 75-1411-D (see text)

2 control knobs

Chassis mounting fuseholder, 20mm.

Veroboard, 0.1in. matrix

18 s.w.g. aluminium (for heat sink)

Nuts, screws, wire, etc.


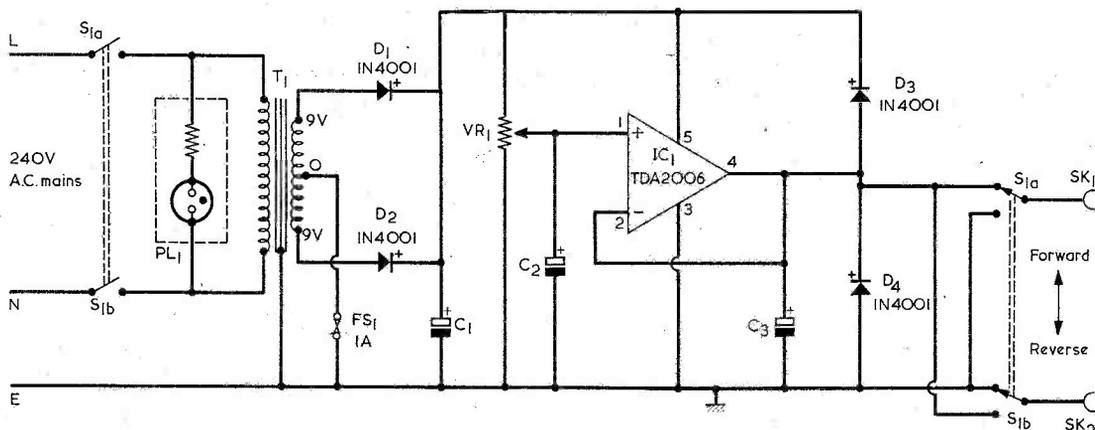
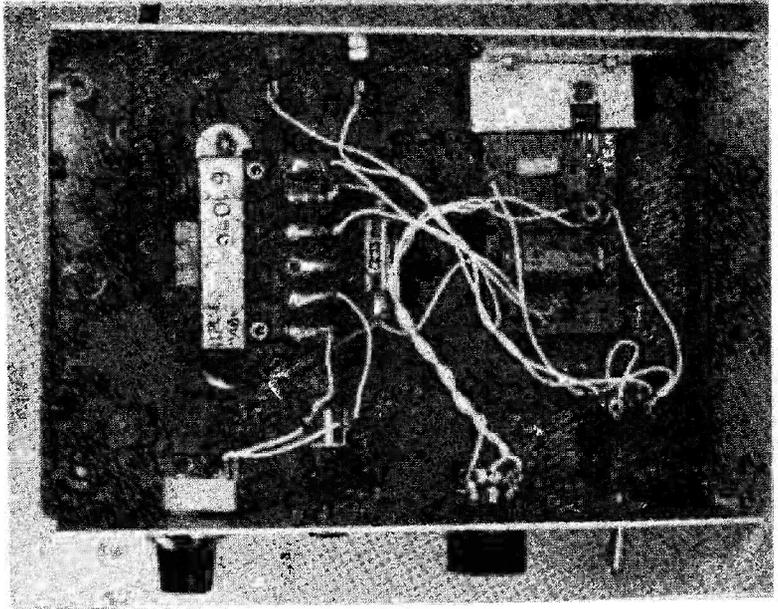


Fig. 1. The circuit of the model train controller. The rectified variable voltage output is given at sockets SK1 and SK2.

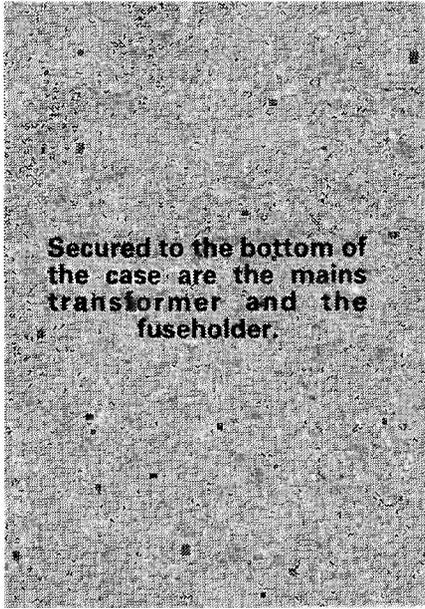


TDA2006 cannot quite reach either of these extremes, but it comes close enough for satisfactory results in the present application. VR1 thus operates as the speed control.

C2 and C3 are needed to aid circuit stability. D3 and D4 are protection diodes. S2 is the forward/reverse switch, and it alters the polarity of the supply fed to the output sockets when it is changed from one position to the other.

In common with most units of this type, a truly constant output voltage is not provided since loading

of the output causes the rectified voltage across C1 to fall. This results in a slight drop in the voltage at VR1 slider. However, the output impedance of the unit is still quite low, and the output voltage is more than stable enough to give good results.

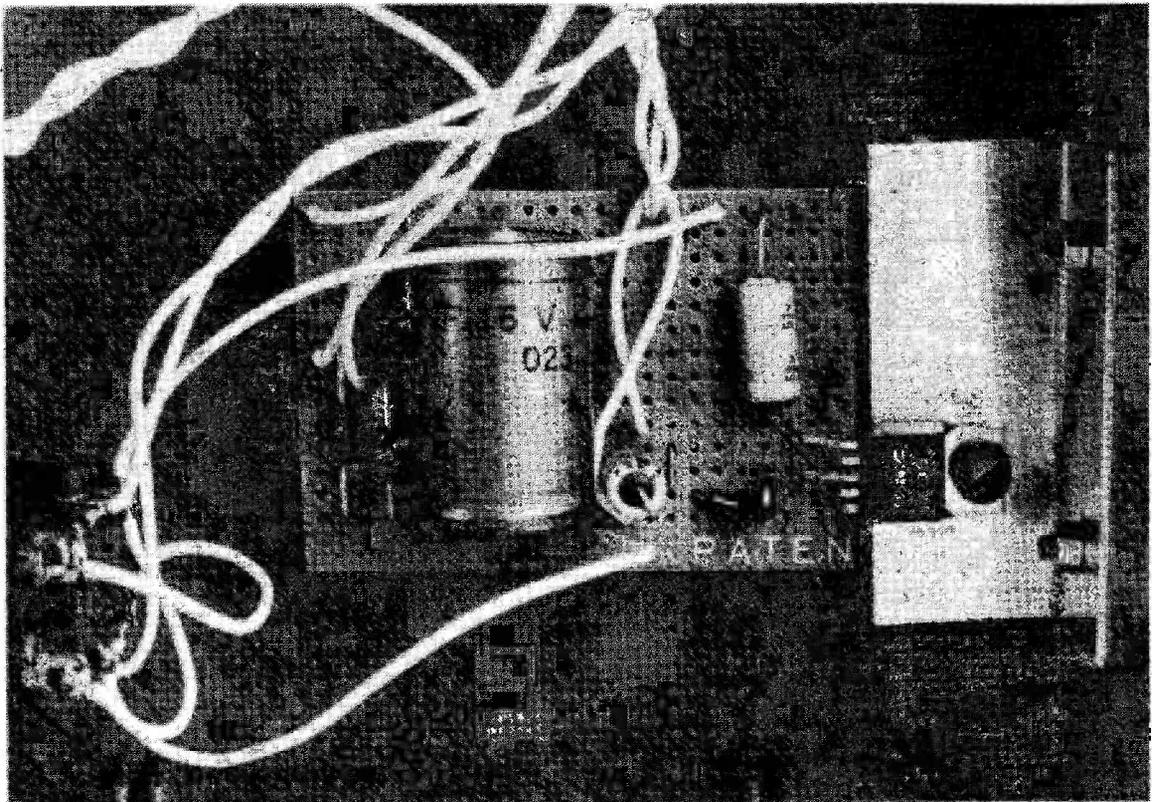
IC1 incorporates output short-circuit protection circuitry which prevents damage in the event of most overloads. A prolonged overload will cause fuse FS1 to blow and protect the components from damage. IC1, incidentally, also has built-in thermal shutdown protection.




The Veroboard component assembly. The L-shaped bracket bolted to IC1 heat tab is secured to the rear panel of the case.

Fig. 2(a). The L-shaped bracket before bending. The material is 18 s.w.g. aluminium and the bend is at right angles, with the upper section being bent towards the reader.

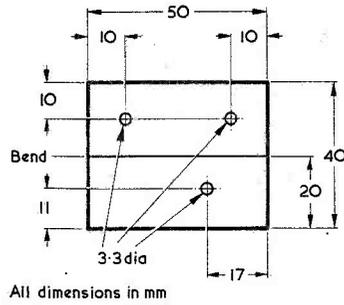(b). After bending, IC1 heat tab is secured to the bracket section having one hole. The remaining section, with two holes, is bolted to the rear panel of the case. Bolts and nuts are 6BA or M3.



(a)

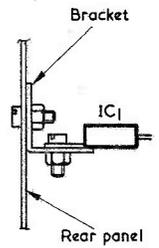

(b)


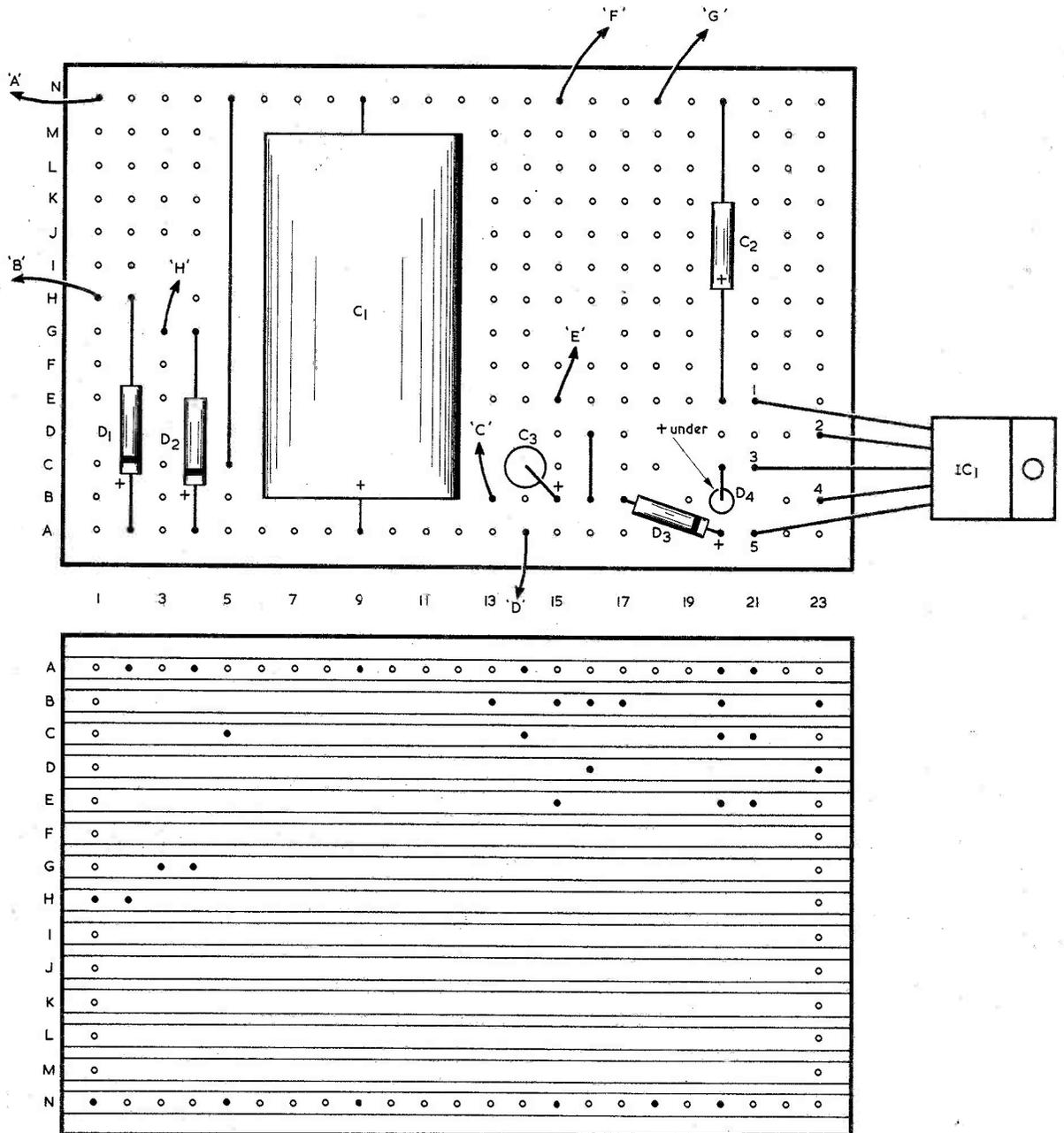


Fig. 3. Wiring up the components on the Veroboard panel. The letter references from "A" to "H" correspond with the similar references in Fig. 4.

CONSTRUCTION

The prototype is housed in a Verocase type 75-1411-D, which has dimensions of 205 by 140 by 75mm. Before obtaining the case it is advisable to check the dimensions of the particular transformer to be employed, to ensure that the case height is adequate.

Layout details are shown in the photographs. On the front panel, from left to right, are switch S1(a) (b), PL1, VR1 and S2(a) (b). The output sockets are 4mm. insulated types and are mounted on the rear panel. The component panel is also secured to the rear panel by way of an L-shaped bracket which functions as a heat sink for IC1. This bracket is made from 18 s.w.g. aluminium and has the dimensions shown in Fig. 2(a). The bracket is fitted to IC1, after the component panel has been wired up, in the manner illustrated in Fig. 2(b). Also required in the rear panel is a hole, fitted with a grommet, for the mains lead.

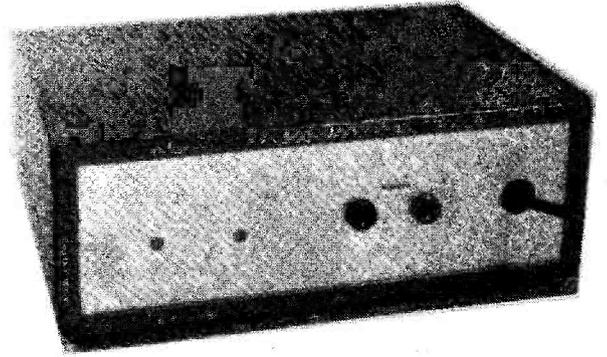

The two output sockets are mounted on the rear panel. This also has a hole, fitted with a grommet, for the mains lead.

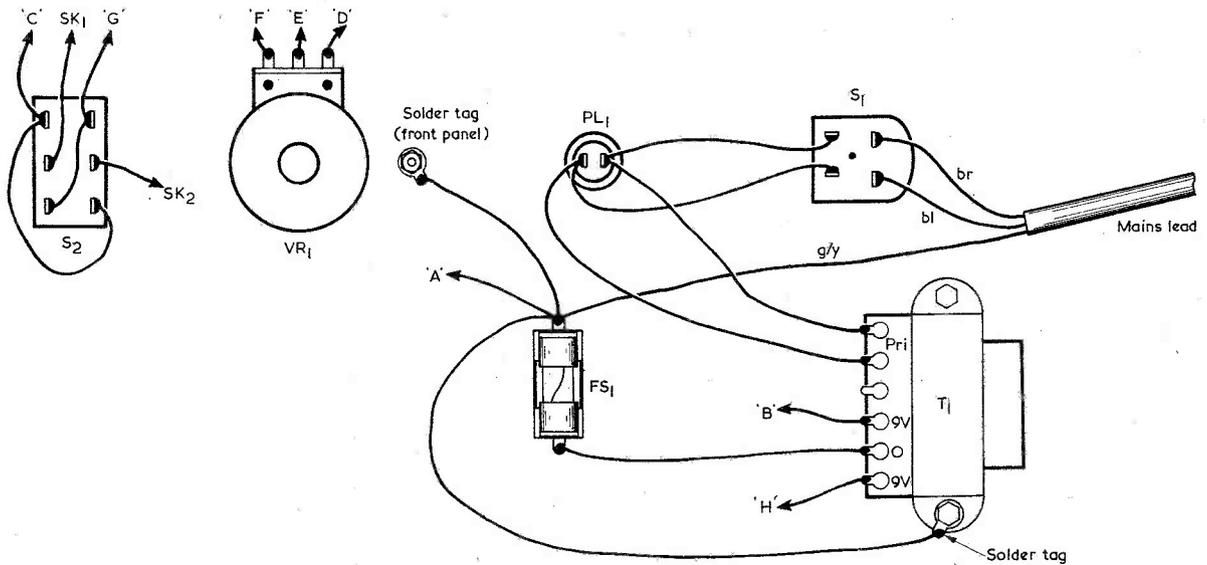


Fig. 4. Wiring external to the Veroboard. Check the tag positioning of S1 with a continuity tester before wiring to this component.

The mains transformer is secured to the base of the case behind S1(a) (b), with the fuseholder alongside it on the component panel side. A solder tag is held under one of the transformer mounting nuts to allow its frame to be earthed. A solder tag, secured with a countersunk 6BA bolt and nut, is fitted to the front panel at any unobtrusive point to allow this to be earthed as well. The rear panel is automatically earthed by way of IC1 heat tab, which is common with its negative supply pin.

VEROBOARD PANEL


The remaining components are fitted to a 0.1in. matrix Veroboard having 14 copper strips by 23 holes. This has to be cut down from a larger board, using a small hacksaw. The Veroboard layout is illustrated in Fig. 3, and there are no breaks in any of the copper strips. IC1 has preformed lead-outs and these have to be opened out somewhat to fit into the appropriate Veroboard holes. After wiring on the Veroboard is completed the heat sink bracket is

secured to IC1 as already described. The component panel is not finally secured to the rear panel of the case until the wiring illustrated in Fig. 4 has been completed. It will be found that the Veroboard is held in place quite adequately by the heat sink, and no further mounting arrangements are required.

The train controller is then ready for use.

SHORT-CIRCUITS

Model train systems are prone to short-circuits from time to time due to derailments and similar mishaps. Since the controller incorporates a 1 amp fuse it might be thought that this fuse would blow for short-circuits of this nature. In practice the fuse does not blow with derailments, partly because the resulting short-circuits are too short in duration and partly because of the current limiting effect of IC1. The prototype controller has had quite a lot of use and, although derailments have occurred, the original fuse is still fitted and has not needed to be replaced. ■

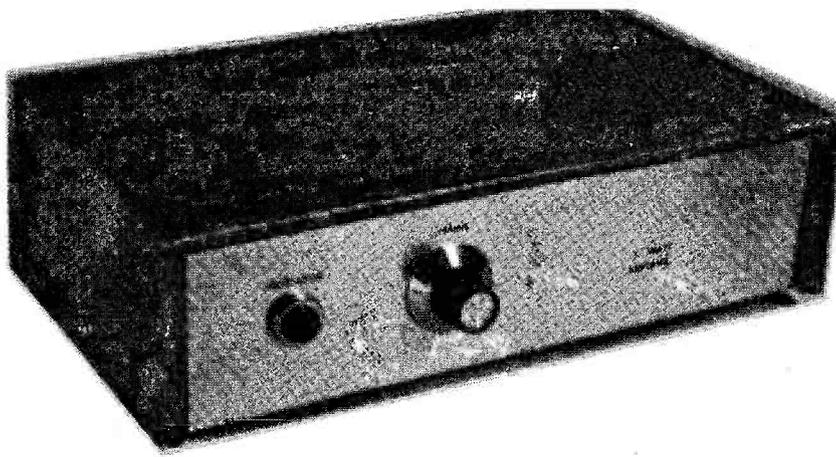

Gui Am

The practice amplifier as seen from the front. The only items mounted on the front panel are the on-off switch and the neon pilot light.

- **Single i.c. design**
- **3 mixed**

The acoustic sound output of solid electric guitars is quite small, and it is necessary to use an amplifier and speaker to boost the sound even when practicing, especially if two or more people are playing together. Stage equipment can be used when practicing at home, but it is better in most instances to use a low power amplifier specifically designed for this application.

Such an amplifier is described here, and it has an output power of up to about 3 watts r.m.s. into an 8Ω speaker. The circuit has a built-in mixing facility and has inputs for three guitars. Since normal electric guitars are fitted with volume and tone controls such controls are not provided with the amplifier, giving a consequent simplification in design.

MIXING CIRCUIT

The amplifier employs an integrated circuit which is rather like an operational amplifier having a Class AB output stage, and which has inverting and non-inverting inputs. Fig. 1(a) shows an operational amplifier working in the inverting mode. The non-inverting input is biased to a mid-supply voltage by R_B and R_C . The input signal is applied to the inverting input via d.c. blocking capacitor C_A and R_A . R_D provides feedback from the output to the inverting input. An inherent feature of an operational amplifier is that, in a circuit of this nature, it functions to keep the inverting input at the same voltage as the non-inverting input. Because of this action, the voltage gain of the amplifier is equal to R_D divided by R_A . If,


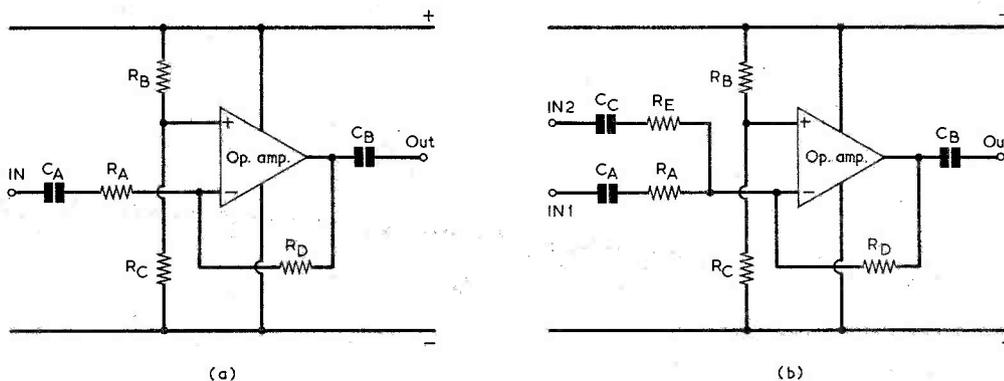


Fig. 1(a). An operational amplifier connected in the inverting mode. Voltage gain is equal to R_D divided by R_A , and there is a virtual earth at the inverting input.

(b). A second input can be mixed with the existing input by simply adding another d.c. blocking capacitor and input series resistor. The virtual earth at the op-amp inverting input prevents interaction between the two inputs.

The winning of the war...

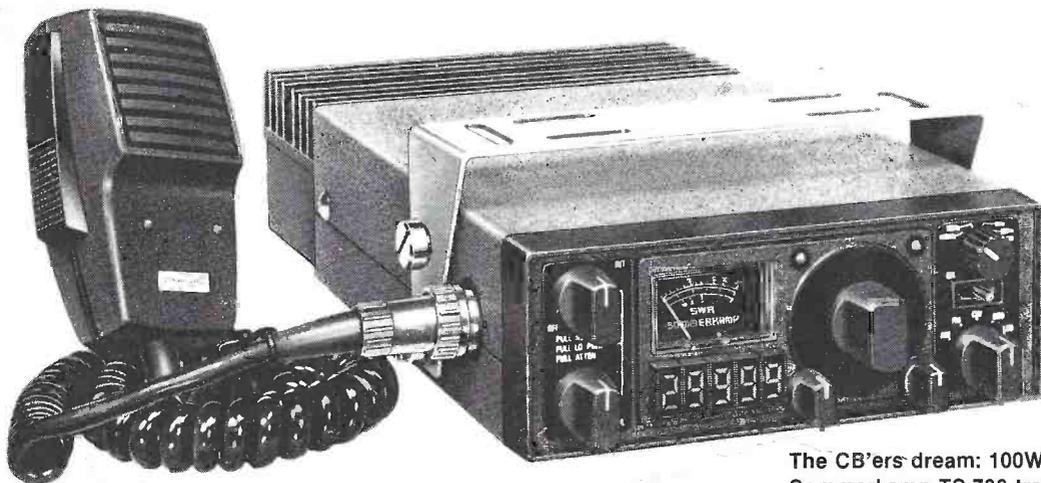Following Eire's decision to adopt 27MHz, 40 channel FM for the basis of its CB system, the much delayed decision from the UK seems to have been arrived at for the worst possible reasons:



The CB'ers dream: 100W all modes Sommerkamp TS-788 transceiver

The Voice of the People

Depending on your viewpoint, it is not at all clear whether or not the UK CB phenomenon of the past year has been a gratifying example of beaurocracy overcome by sheer practical commonsense — or yet another unedifying example of the irresistibility of large scale organised civil disobedience.

The practical realization of a personal communication facility with a minimum of administrative beaurocracy is a logical extension of any 'libertarian' democracy — provided it conforms to the usual criteria by which democratic 'freedom' has been established.

Namely, CB radio should not interfere with the freedom of any other citizen to pursue his legally established rights. The fact that 27MHz CB radio (particularly AM mode operation) has grossly undermined the safety and confidence of the aero modelling fraternity was grudgingly recognized at the start of the year, when the Home Office allocated the almost universal 'Euro' band of 35.005 to 35.205MHz to UK radio modellers — although restricting its use to airborne applications only. At the same time, the first step towards CB was taken by the broad deregulation of the erstwhile 27MHz model control band.

A victory for commonsense, but what a shame so many Cbers are/were so badly informed on the subject of their responsibility to aero modellers in the first place. It's not enough to simply stay away from a channel when the characteristic buzz of digital proportional RC can be heard in the receiver — since the aircraft can hear a Cber over a range many times that which can be covered from the RC transmitter to the CB receiver (Fig. 1). The airborne antenna of the aircraft receiver can hear an enormous number of additional groundwave transmissions — so the answer is to stay clear of the RC spot channels at the very least. (Table 1). The use of intermediate or split frequencies is not really very common, and will probably die out as serious users migrate to 35MHz.

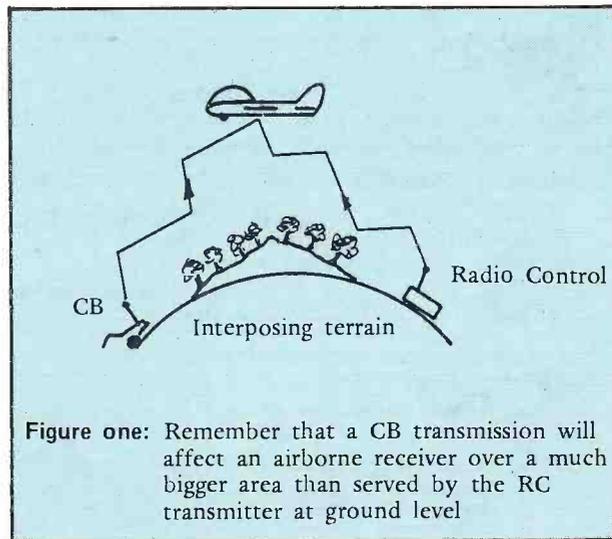


Figure one: Remember that a CB transmission will affect an airborne receiver over a much bigger area than served by the RC transmitter at ground level

RC colour code	CB channels to avoid	Freq. MHz
Black	(1)	26.945
Black/brown	2	26.975
Brown	(2/3)	26.995
Red/brown	6	27.025
Red	(7/8)	27.045
Orange/red	10	27.075
Orange	(11/12)	27.095
Yellow/orange	14	27.125
Yellow	(15/16)	27.145
Green/yellow	18	27.175
Green	(19/20)	27.195
Blue/green	22	27.225
Blue	23	27.255

(Channel numbers in brackets indicate adjacent channels)

Table one: RC versus CB




Interference to other TV/Radio/Audio equipment

Public enemy number one for the CBer and the Home Office is/will be interference to the democratic right of the public to watch TV. Even if the CB set is fully approved and in accordance with the regulations laid down, there will still be a great deal of scope for the inadequacy of most types of 'front end' used in UK TV sets to be brought into relief by the presence of a large number of strong RF fields. (Fig. 3) The fact that the RF field is at a frequency far removed from UHF band 4 TV makes little difference. The basic problems results from simple overloading of the input of the TV, and is not as a result of harmonically related spurii (multiples of the 27MHz frequency).

Figure two: Know your broadcast frequencies.....

Broadcast bands above 27MHz:

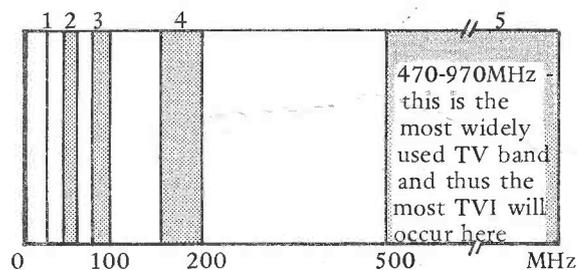

- 1: 27MHz 2: 45-68MHz Band 1 VHF TV
 3: 88-108MHz Band 2 FM broadcasting
 4: 175-230MHz Band 3 TV 5: Band 4 UHF TV

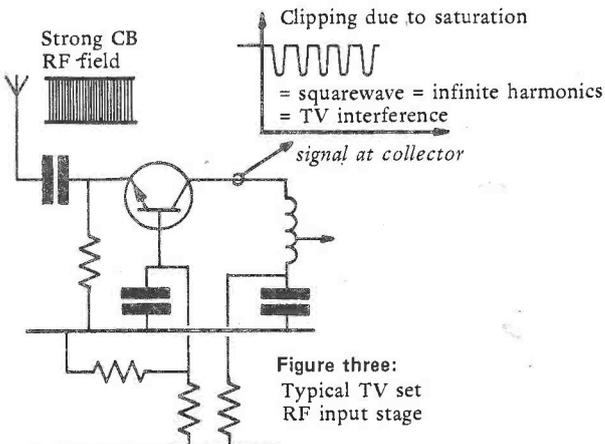


Figure three:
Typical TV set
RF input stage

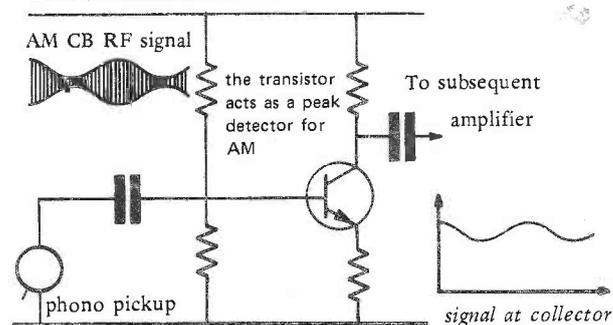


Figure four: AM CB in an audio amplifier

Table two: Harmonics of the 27MHz band to 1000MHz

Number	Reference	Upper limit	Lower limit
1	27.000 MHz	27.405 MHz	26.965 MHz
2	54	54.81	53.93
3	81	82.215	80.895
4	108	109.62	107.86
5	135	137.025	134.825
6	162	164.43	161.79
7	189	191.835	188.755
8	216	219.24	215.72
9	243	246.645	242.685
10	270	274.050	269.650
11	297	301.455	296.615
12	324	328.860	323.580
13	351	356.265	353.545
14	378	383.670	377.510
15	405	411.075	404.475
16	432	438.480	431.440
17	459	465.885	458.405
18	486	493.290	485.370
19	513	520.695	512.335
20	540	548.100	539.300
21	567	575.505	566.265
22	594	602.910	593.230
23	621	630.315	620.195
24	648	657.720	647.160
25	675	685.125	674.125
26	702	712.530	701.090
27	729	739.935	728.055
28	756	767.340	755.020
29	783	794.745	781.985
30	810	822.150	808.950
31	837	849.555	835.915
32	864	876.960	862.880
33	891	904.365	889.845
34	918	931.770	916.810
35	945	959.175	943.775
36	972	986.580	970.740
37	999	1013.985	997.705

Exact details of UK broadcast frequencies are obtainable from the IBA and BBC:

IBA Eng. Inf. Dept.,
 Crawley Court,
 Winchester,
 Hants SO21 2QA

B.B.C. Engineering
 Information Dept.,
 Broadcasting House
 London W1A 1AA

The use of AM and SSB (both basically modes of speech that vary the transmitted output power in accordance with speech level) will also lead to interference in such unlikely things as HiFi and ordinary domestic MW receivers, where a powerful RF field can readily be rectified and amplified in the audio stages — regardless of what the RF selectivity may do. (Fig. 4).

FM modulation at least alleviates the problem of interference with HiFi — but it doesn't necessarily eradicate it altogether. An FM transmission can still drive an audio stage into non-linearity (and hence distortion), but the reason the CBer gets away with it, is that there is no actual speech coming from the amplifier since the RF carrier level is constant. FM CB will still give TV sets the 'wobblers', but since the match of the set to its antenna is not so critical as with AM, the scope for really grotesque interference arising from the mismatch of an AM transmitter is rather less.

In fact, FM CB has many advantages from a technical viewpoint, although the predominance of AM and SSB CB equipment as the historical result of the USA's policy has left a legacy that will be hard to 'phase out'.




Euro-CB on 27MHz

The fact that most of Europe already uses 27MHz for CB was obviously an influential force in the UK choice - but as you will see as we unwind each country in the course of this series - actual standards vary widely.....

No.	Country	Channels	Mode(s)	Output
1	UK	(?)40	FM	(?)4W
2	Eire	40	FM	4W
3	Holland	22	FM	0.5W
4	W. Germany	22	AM/FM	0.5W
5	Belgium	22	AM/FM/SSB	0.5W
6	France	22	FM	2W
7	Switzerland	12	AM	0.1W
8	Italy	23	AM	5W
9	Spain	22	AM	5W
10	Portugal	40	AM/FM/SSB	5W
11	Greece	40	AM/FM/SSB	5W
12	Sweden	25	(SSB)/AM/FM	2-5W
13	Yugoslavia	32	AM	2W
14	Poland	40	AM/SSB	4W
15	Denmark	23	AM/FM	0.5W
16	Austria	12	AM/FM	0.5W
17	Norway	23	AM/FM	0.5W
18	Finland	24	AM/FM	0.5W

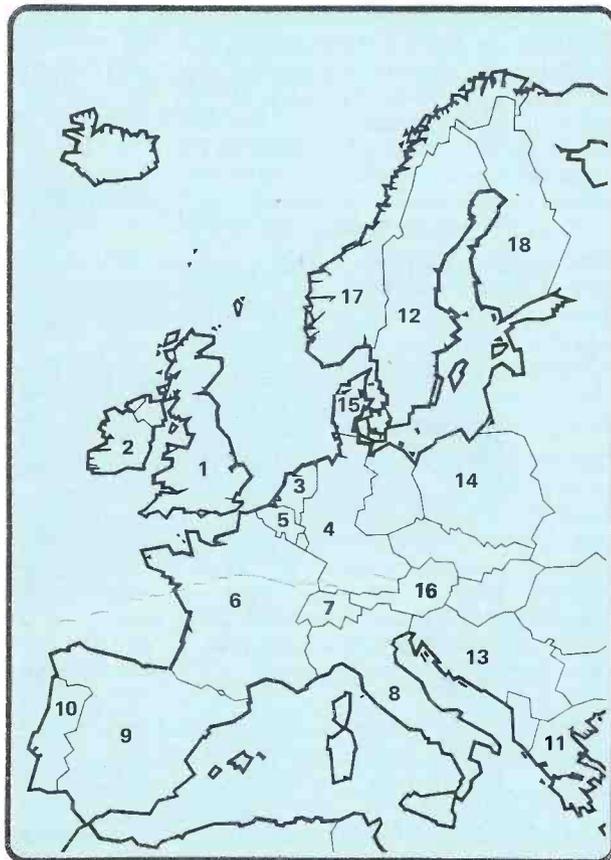Please note that one country's channels do not necessarily relate to those of another. A much more detailed analysis of Euro-CB will follow in subsequent issues.



CHANNEL v FREQUENCY — FOR THE STANDARD 40 CHANNEL SYSTEM USE 'LOW' COLUMN

CH	FREQUENCY IN MHZ		
	HI	MID	LOW
1	28.500	27.415	26.965
2	28.510	27.425	26.975
3	28.520	27.435	26.985
4	28.540	27.455	27.005
5	28.550	27.465	27.015
6	28.560	27.475	27.025
7	28.570	27.485	27.035
8	28.590	27.505	27.055
9	28.600	27.515	27.065
10	28.610	27.525	27.075
11	28.620	27.535	27.085
12	28.640	27.555	27.105
13	28.650	27.565	27.115
14	28.660	27.575	27.125
15	28.670	27.585	27.135
16	28.690	27.605	27.155
17	28.700	27.615	27.165
18	28.710	27.625	27.175
19	28.720	27.635	27.185
20	28.740	27.655	27.205

CH	FREQUENCY IN MHZ		
	HI	MID	LOW
21	28.750	27.665	27.215
22	28.760	27.675	27.225
23	28.790	27.705	27.255
24	28.770	27.685	27.235
25	28.780	27.695	27.245
26	28.800	27.715	27.265
27	28.810	27.725	27.275
28	28.820	27.735	27.285
29	28.830	27.745	27.295
30	28.840	27.755	27.305
31	28.850	27.765	27.315
32	28.860	27.775	27.325
33	28.870	27.785	27.335
34	28.880	27.795	27.345
35	28.890	27.805	27.355
36	28.900	27.815	27.365
37	28.910	27.825	27.375
38	28.920	27.835	27.385
39	28.930	27.845	27.395
40	28.940	27.855	27.405

R&EC and CB

Now that CB is here to stay, REC will ensure that all the adherents enjoy the maximum benefit — with minimum interference to the liberty of others. Which broadly means that your neighbours should be able to watch Crossroads without crosshatch — whilst you are able to hook the DX, without resorting to the sheer brute force and ignorance of illegal power boosters.

Contributors to this regular monthly supplement include the most knowledgeable people in the business of world CB. But furthermore, we think that CB will be an introduction to the broader spectrum of interests in Radio and Electronics for a good many CB enthusiasts who find the topics of a CB-only publication just a little restrictive and subjective. Write and tell us what you want — and what you think.



The Evolution of CB

AM CB grew up in Europe (and much of the rest of the world) from the purely commercial expedient that a lot of surplus gear was available at very low cost as a result of the Boom and Bust of the US CB market in the 1977/8/9 period. The whole point of CB is that the user frequently doesn't care much about the technicalities of his rig — as long as it is cheap and enables him to talk to a passable number of other enthusiasts.

And the other reason is the naive reluctance of the Post Office (as it then was) followed by the Home Office (who took over the Post Office's responsibility for radio spectrum usage), to recognize that CB existed. Or even acknowledge the inevitability of a formal CB system in the UK — if only as a result of the frequently repeated experiences of the rest of the world.

The Post Office greedily guarded its communications monopoly; and the Home Office uttered dark things about the potential for illegal use of CB. It's hardly likely any criminal would be stupid enough to use the most populated frequency on the airwaves, when it is nearly as simple to obtain far more discrete amateur or private mobile/portable radio equipment. The experience of the USA bears out the simple fact that CB is a far more constructive medium than the UK authorities would like to admit.

After a while, the interminable buck passing in the Home Office during the last Labour administration led to the attraction of CB as an election issue. The Conservative Party — being nominally the party of individual freedom and against state monopoly agreed to the idea 'in principle' — and thus won the support of the CB Association. Not surprisingly, with the election in the bag and more pressing matters afoot, the CB lobby was conspicuously ignored while the Home Office replayed its usual round of worn out excuses:

Number one: *"There isn't a demand for the service....."*
Not to anyone's great surprise, this old chestnut quickly passed into disuse.

Number two: *"There is no suitable frequency....."*
This was one that the 'boffins' used most successfully to bamboozle the politicians. After all, the average MP will probably admit to having his scientific acumen strained when asked to change the batteries in a torch — so the 'blind 'em with science' ploy was very successful. The fact that the rest of the world found a frequency eventually got the better of the argument, although the wimpering continues with talk of the 'special factors' that apply to the British Isles.

Number three: *It would be impossible to regulate the illegal misuse of CB, and people might say Rude Things.."*
Oh dear, oh dear. The BBC and IBA somewhat preempted this argument by the saturation broadcast coverage of just the sort of thing that the anti-CB brigade claimed would undermine the nation's morality. Even the so-called responsible radio amateur fraternity have been thoroughly disgraced by the behaviour of some moronic souls on the 2 metre band in particular. Never mind, there is always that quaint switch marked 'Off'.

Number four: *"The problems of interference to other users will be insurmountable....."*

Now even the most ardent CB proponent must concede some ground here. Technical advances over the past couple of years have certainly reduced the chance of the CB set causing problems — and the ease with faults and problems can be identified and rectified. Nevertheless, the problem of simple overload cannot be ignored. The answer is to provide sufficient revenue from the CB licence to pay the relevant authority to go out and settle problems. Existing CB groups are already well organized, so that trouble shooting such problems should be quite an orderly affair. Most such problems conform with very standard phenomena, that are cured by equally standard solutions. With 2.4 million unemployed persons, the shortage of manpower to handle these situations is scarcely a convincing argument — albeit a fairly minimal degree of training will be required.

But all these were all eventually ground down to the point at which Mr. Whitelaw made the infamous 'Open Channel' green paper available for discussion. The almost universal derision that this attracted from practical realists (be they fans of CB or otherwise) clearly underlined that 928MHz was ludicrously inadequate as an answer to the growing band of illegal 27MHz CB operators — hence the first crack in the facade appearing with the 35MHz aero modellers' allocation. 928MHz was simply the next most negative suggestion the Home Office could come up with compared to 'No CB at all'.

As country after country in Europe adopted the 27MHz band, it was inevitable that the UK could not pretend it could avoid the question any longer. Cars and trucks fitted with CB from the continent simply could not be regulated, and the underground movement had acquired nearly 250,000 illegal sets. Not as the result of any careful planning or consideration, 27MHz has simply happened.

The availability of another as yet unused 928MHz frequency offers some opportunity for the future, when equipment for these frequencies will become more viable and attractive as 27MHz clogs up.

Conclusions

No one can really be proud of the way CB has arrived here. There is very little scope for UK manufacturing to benefit — and we have a very indifferent technical solution compared to the system we could have had if the decision had been just two years ago. The capitulation to mass disobedience will lead to further erosion of public respect for politicians and the 'good sense' of authority.

In such circumstances there can be no victory — we have all lost something in this unseemly affair. Gleeful CBers might like to reflect on the other Great American 'democratic right' supported by a similar campaign of public obstinacy in the shape of the ludicrous gun laws. The ownership of firearms is a fait-accomplis, enshrined in as much law as can feasibly be enforced — and stoked along by some unashamedly commercially biased considerations.

Next month AM to FM conversions examined
928MHz — our objective assessment

tar Practice plifier

By R. A. Penfold

inputs


• Ideal for solo or
group practice. •

for instance, R_D has twice the value of R_A , an input signal going 1 volt positive would cause the operational amplifier output to swing 2 volts negative. The actual voltage change at the inverting input itself would be very small and it can be looked upon as providing a "virtual earth." The input impedance of the circuit is then equal to R_A .


To obtain a mixing action at the inverting input it is merely necessary to add a second d.c. blocking capacitor and series input resistor, as are given by CC and RE in Fig. 1(b). The output now corresponds to

the sum of the two input signals and the required mixing is obtained. Also, since the inverting input provides a virtual earth there is negligible interaction between the two inputs. In the present application, this ensures that adjustments to the volume and tone controls of one guitar will have no effect on the output of another guitar connected to the second input.

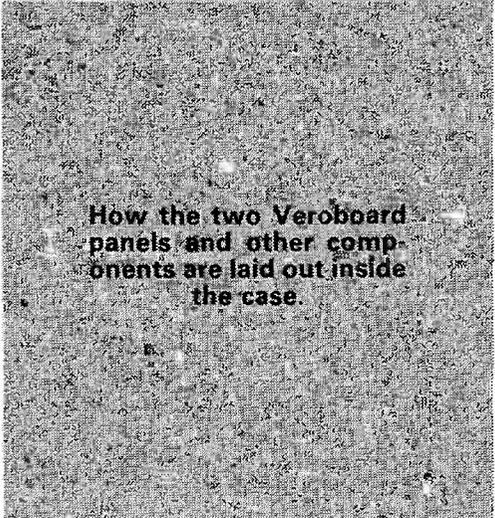Another advantage with this type of circuit is that it can accept any number of inputs within reason, without any adverse effect on performance. It is merely necessary to add a d.c. blocking capacitor and series resistor for each input required.



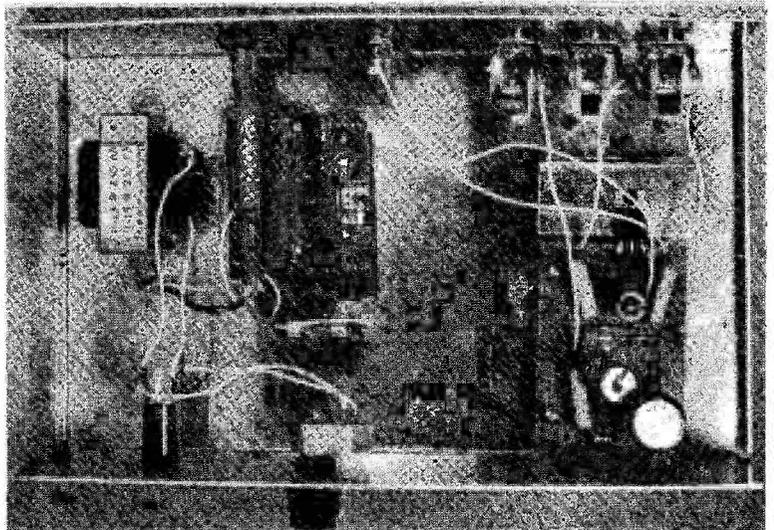How the two Veroboard panels and other components are laid out inside the case.



AMPLIFIER CIRCUIT

The circuit of the guitar practice amplifier is given in Fig. 2. This is basically similar to Fig. 1(b), but there are now three inputs. Guitar pick-ups need to work into a reasonably high impedance and they do not provide a very high output signal level. R1 to R3 give the circuit an input impedance of 33k Ω at each input, and the value of feedback resistor R7 is chosen to give a voltage gain of about 46dB, or 200 times.

This gives an input sensitivity of about 24mV for full output, and any normal guitar pick-up will provide an output of adequate magnitude.

Unlike the operational amplifier in Figs. 1(a) and (b), the input impedance of the i.c. employed in the amplifier is not very high, and is comparable with the value of R7. Because of this, the non-inverting input cannot be biased to a mid-supply voltage by simply connecting it to the junction of two equal value resis-

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated)

- R1 33k Ω
- R2 33k Ω
- R3 33k Ω
- R4 8.2k Ω
- R5 47k Ω pre-set potentiometer, 0.1 watt horizontal
- R6 22k Ω
- R7 6.8M Ω 10%

Capacitors

- C1 0.47 μ F polyester type C280
- C2 0.47 μ F polyester type C280
- C3 0.47 μ F polyester type C280
- C4 330 μ F electrolytic, 25V. Wkg.
- C5 2,200 μ F electrolytic, 16V. Wkg., single-ended (see text)
- C6 100 μ F electrolytic, 25V. Wkg.
- C7 0.1 μ F polyester type C280
- C8 2,200 μ F electrolytic, 25V. Wkg. (see text)

Semiconductors

- IC1 TDA2006
- D1-D6 1N4001

Transformer

T1 mains transformer, secondary 15V at 500mA (see text)

Fuse

FS1 500mA cartridge fuse, 20mm.

Switch

S1 d.p.s.t. rotary mains switch

Lamp

PL1 panel-mounting neon, with integral series resistor

Sockets

SK1-SK3 $\frac{1}{4}$ in. jack socket
SK4 3.5mm. jack socket (see text)

Miscellaneous

Metal case (see text)
Control knob
Chassis-mounting fuseholder, 20mm.
Veroboard, 0.1in. matrix
Aluminium, 18 s.w.g. (for IC1 heat sink)
3-core mains lead
Nuts, bolts, wire, etc.

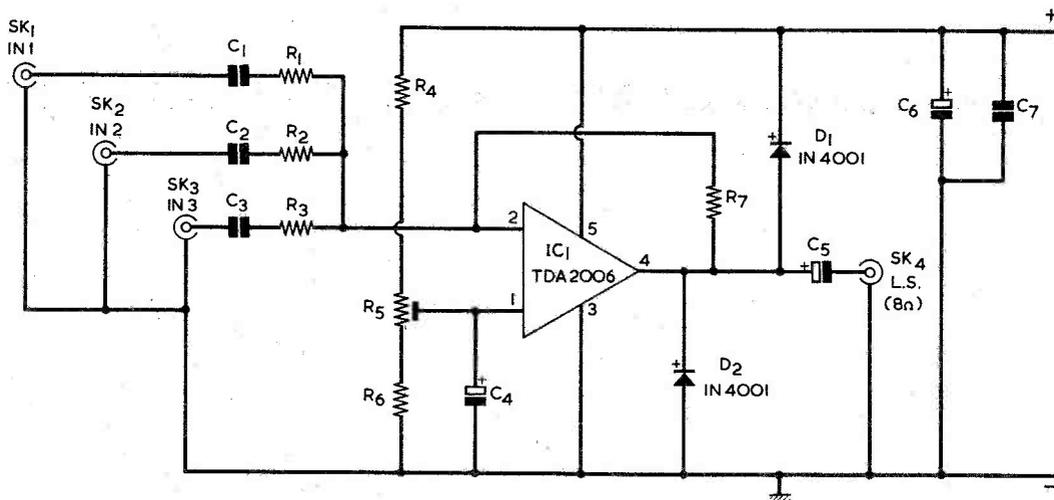


Fig. 2. The circuit of the a.f. section of the guitar practice amplifier.

tors, and it is necessary to provide an adjustable bias voltage here. The bias voltage is given at the slider of pre-set potentiometer R5, which is adjusted for a mid-supply voltage at the amplifier output.

The non-inverting input is bypassed to chassis by way of C4. This capacitor is given a relatively high value to ensure that no hum or noise from the power supply is passed into the non-inverting input. The amplifier is designed for use with a non-stabilized supply, and the high value of C4 causes quite a stable bias voltage to be given even when there are substantial fluctuations in supply voltage with high level signals. C4 prevents a form of positive feedback which could cause the biasing to be forced well off centre by strong sudden signals, resulting in clipping of one set of half-cycles.

D1 and D2 are protection diodes, and C6 and C7 are supply decoupling components. The amplifier has a quiescent current consumption of about 40mA, but this rises to some 300 to 350mA at full output.

POWER SUPPLY

The supply current required by the amplifier is much too high to be provided economically by batteries, and a mains power supply is required. The circuit of the supply used with the amplifier is shown in Fig. 3.

S1 is the on-off switch and is, incidentally, the only control for the unit. PL1 is a neon indicator with integral series resistor intended for operation from the 240 volt a.c. supply. T1 provides isolation from the mains supply and offers a secondary voltage of 15 volts at 500mA. (Some important notes concerning this transformer are given later under the heading "Components").

The secondary voltage is applied via fuse FS1 to the bridge rectifier consisting of D1 to D4, and the rectified voltage is smoothed by capacitor C8. It might be thought that the initial surge of current at switch-on, as C8 charges, could cause the fuse to blow, but it has been found in practice that a quick-blow fuse withstands this surge, and there is no necessity to employ an anti-surge fuse for FS1.

COMPONENTS

The amplifier is assembled in a vinyl covered metal instrument case having dimensions of 229 by 133 by 63.5mm, and this is a case type TP4 available from Maplin Electronic Supplies. Also available from Maplin Electronic Supplies is the integrated circuit type TDA2006 and suitable electrolytic capacitors for C5 and C8. C8 is an axial lead capacitor whilst C5 is a single-ended (i.e. both lead-outs are at one end) capacitor intended for printed circuit mounting. Both the Maplin capacitors will fit into the layout and case specified.

As will be evident from Fig. 3, the mains transformer has its two 15 volt secondaries connected in parallel. Mains transformer secondaries with the same nominal voltage should never be connected in parallel unless the transformer manufacturer states that it is safe to do so. This is because the transformer can overheat if one secondary should happen to have one or more turns in excess of the other. The author employed a transformer having two 250mA secondaries, but this may be difficult to obtain and a satisfactory alternative is a 10VA Miniature Transformer with two 15 volt 330mA secondaries which is listed by Maplin Electronic Supplies. It is also in order, with this particular transformer, to connect the two secondaries in parallel. It would also be in order,


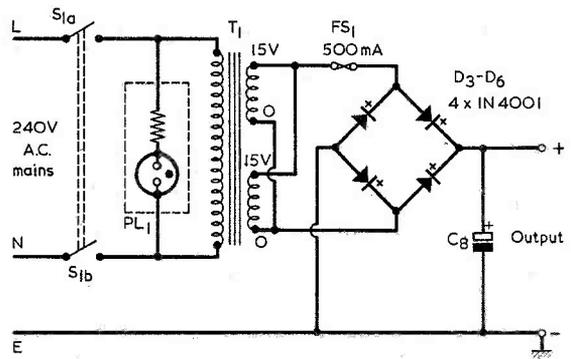


Fig. 3. The power supply section. There is no necessity for a stabilized supply.

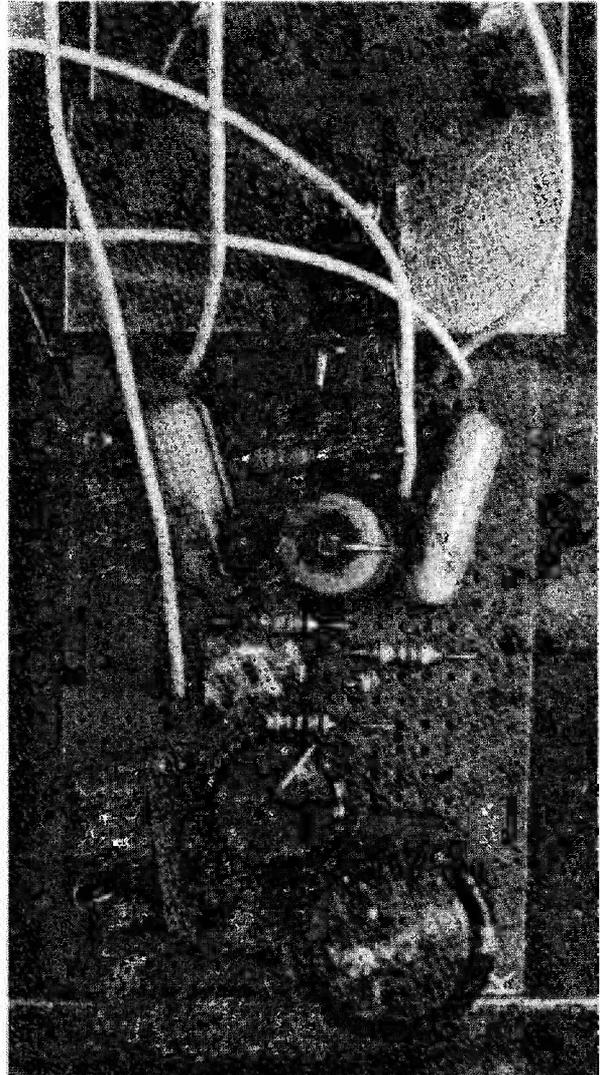

The amplifier section. The three input leads do not need to be screened.

of course, to use a mains transformer having a single 15 volt secondary rated at 500mA or more. Such a transformer may require a metal case of greater height than that used for the prototype unit.

CONSTRUCTION

As can be seen from the photograph of the internal layout, the use of a relatively large case allows the mains transformer to be mounted well away from the amplifier board, thereby causing minimal stray pick-up of hum in the amplifier circuitry. Looking into the case from the front, the mains transformer is to the rear at the extreme left, with the power supply board to its right. On the right hand side of the case is mounted the amplifier board. On the front panel, to the left, is PL1 with S1 to its right. The chassis-mounting fuseholder is secured to the case bottom between S1 and the power supply board.

Output socket SK4 is fitted to the centre of the rear panel. A 3.5mm jack socket was used in the prototype but any other type of 2-way socket or connector which may be preferred can be used instead. SK1, SK2 and

SK3 are all $\frac{1}{4}$ in. jack sockets and are mounted behind the amplifier board. A hole with a grommet for the mains lead is provided at the power supply end. The mains lead should be secured inside the case with a plastic or plastic-faced clip.

SUPPLY BOARD

Many of the power supply components are assembled on a piece of 0.1in. Veroboard having 19 copper strips by 18 holes, and this is shown in Fig. 4. There are no breaks in the copper strips. The two mounting holes are 3.3mm, in diameter and take 6BA or M3 screws.

As is shown in Fig. 4, a solder tag is secured under one of the mounting nuts for the transformer, and this provides the chassis connection for the mains earth lead as well as the negative output of the power supply. Before connecting to S1, confirm relative tag positioning with a continuity tester in case the particular switch employed has a different tag layout to that shown in the diagram. An insulated lead about 150mm. long is soldered to the Veroboard at the

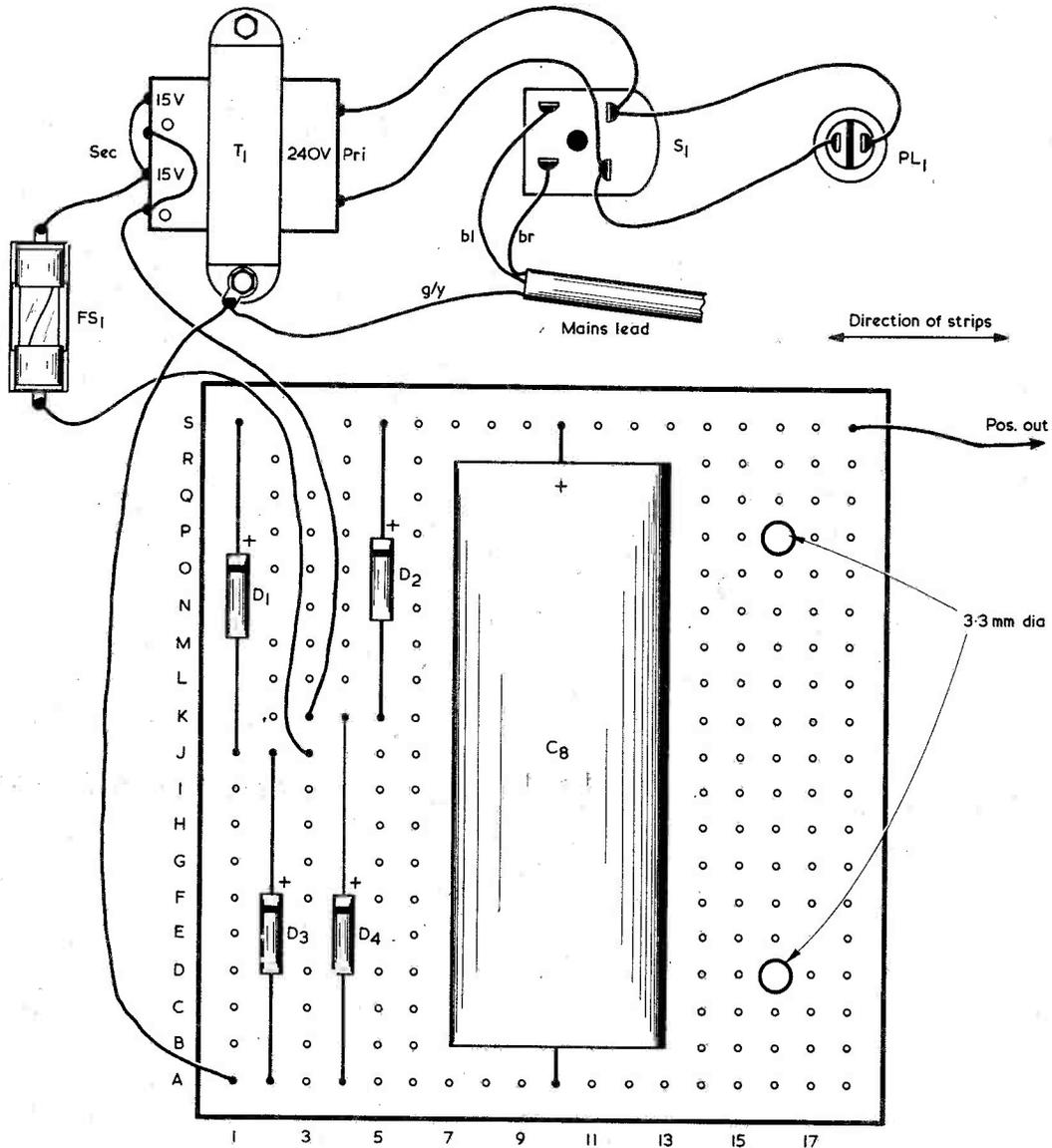


Fig. 4. Wiring up the power supply. There are no breaks in the Veroboard copper strips.

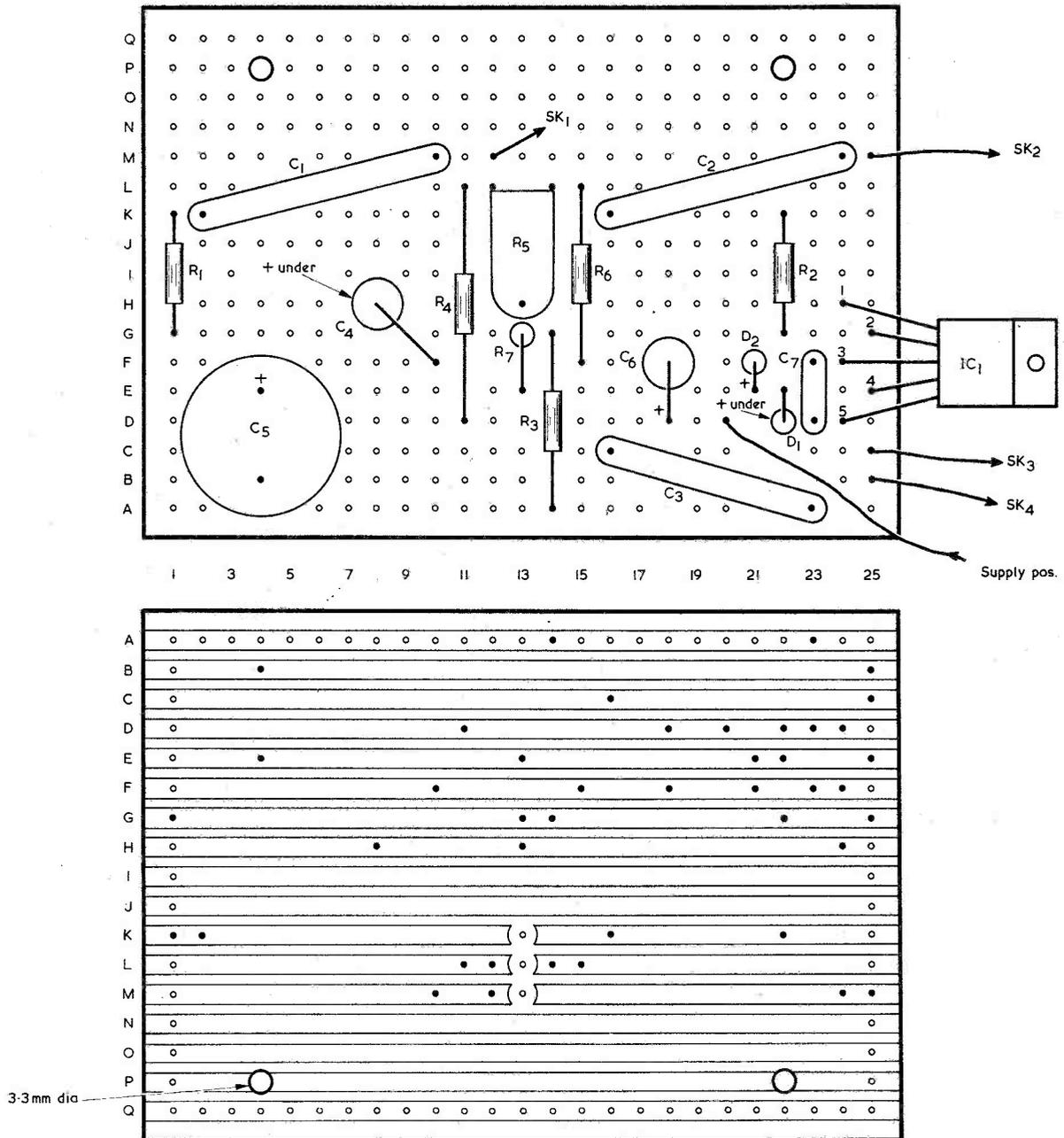


Fig. 5. Component layout on the amplifier Veroboard.


positive output, for later connection to the amplifier board. The power supply board is secured to the case bottom with strip "A" towards the front of the case. Spacing washers 12.5mm. long on the mounting bolts keep the board underside well clear of the inside metal surface of the case.

AMPLIFIER BOARD

A second 0.1in. Veroboard is used for the amplifier, and details of this are given in Fig. 5. The board has 17 copper strips by 25 holes and there are three breaks in the strips. The lead-out wires of the TDA2006 are preformed, but will not fit the 0.1in. matrix board unless they are splayed out slightly. The


i.c. requires a small heat sink which is made up as shown in Fig. 6. Fig. 7 gives a side view, illustrating how the heat sink is bolted to the i.c. and to the bottom of the metal case. The heat sink is made of aluminium of about 18 s.w.g., and it also provides the negative supply connection to the amplifier by way of the i.c. heat tab.

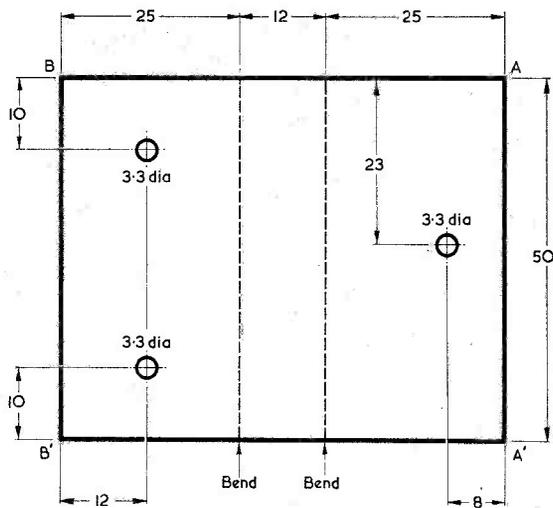The completed amplifier board assembly is mounted at the extreme right hand end of the case, so that it is well away from the mains transformer and the mains wiring. Spacing washers 12.5mm. long are used on the screws securing the board. If this is temporarily mounted in place the two holes for the heat sink can then be marked out using the heat sink itself



All dimensions in mm

Fig. 6. The heat sink for IC1 is made from a piece of 18 s.w.g. aluminium. The two bends are at right angles and the sink is shown, after bending, in Fig. 7.

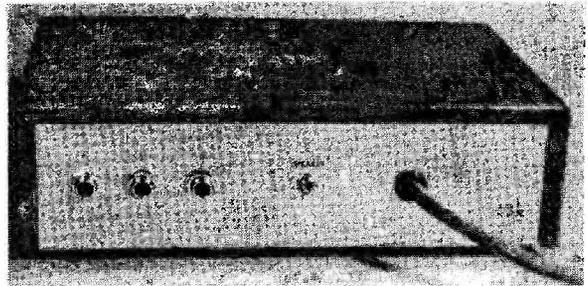


The rear panel. The three input sockets are to the left, and the output socket is positioned centrally.

as a template. The assembly is mounted with the heat sink to the rear.

The positive supply lead is connected to the amplifier board, as also are the leads to the four sockets. Because the amplifier is in a metal case the leads to SK1, SK2 and SK3 do not need to be screened, but they should be kept as short as is reasonably possible. All the jack sockets pick up their chassis connection by way of their mounting bushes and nuts. The non-earthly tags of the sockets can be determined by visual inspection.

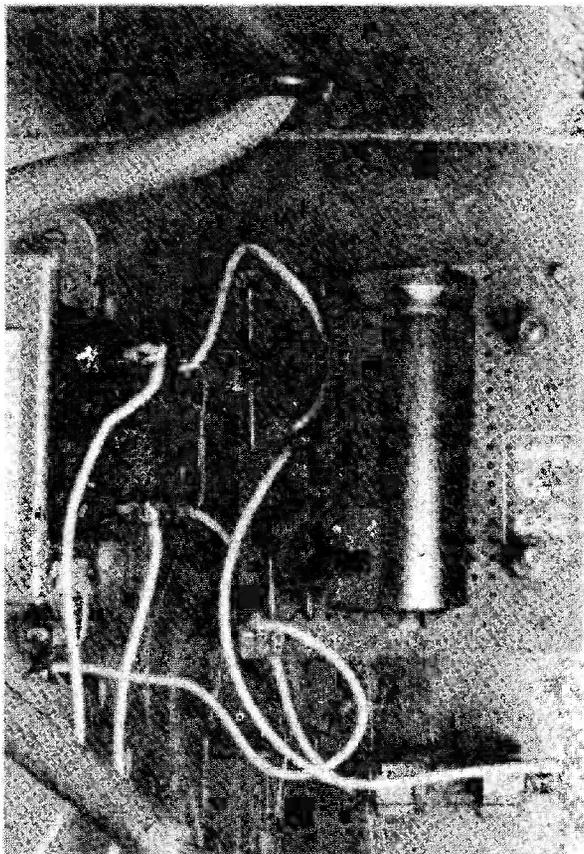If an alternative output socket is employed it may require a wired chassis connection. This can be provided by a solder tag under the nearer nut securing the heat sink to the case bottom.



The mains transformer and power supply panel.

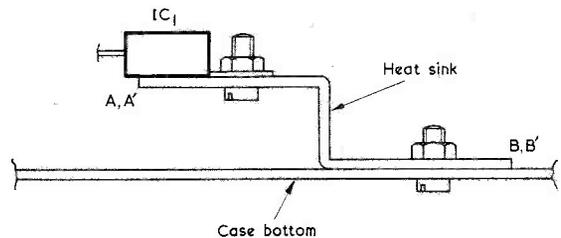


Fig. 7. How the heat sink is secured to the integrated circuit heat tab and to the bottom of the metal case.

ADJUSTMENT

After the amplifier has been completed it needs to be checked and R5 has then to be adjusted. Initially, R5 should be given a central setting. A guitar is connected to one of the inputs and an 8Ω speaker to the output socket. Note that there is a short delay of a second or two after switch-on before the amplifier becomes fully operational, since some of the capacitors have to charge to their working levels. In its present state the amplifier should function reasonably well.


Next, set a multimeter to a suitable d.c. volts range (25 volts f.s.d. or more), connect its negative lead to chassis and its positive lead to the output of the TDA2006. A suitable point is the lower wire of R7 as shown in Fig. 5. R5 is then adjusted for an output voltage of 11 volts.

If a multimeter is not available, it is quite acceptable to simply adjust R5 to the setting which gives the highest audible output before clipping and consequent severe distortion occur.

After R5 has been adjusted the case lid is fitted. The amplifier should always be employed with the lid firmly screwed in position. ■

SHORT WAVE NEWS

FOR DX LISTENERS

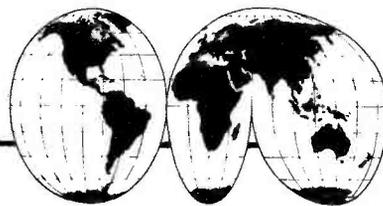

By Frank A. Baldwin

Times — GMT

Frequencies — kHz

As the winter period comes to an end, signals from the Far East will fade out and those from the Latin American area will tend to build up – at least that is the usual pattern of events for those of us here in the U.K. and Europe. Instead of listening from around 1500 and 2200GMT for those elusive transmissions from the East, we must instead strain our ears for the African signals from 1730 onwards and the Latin American transmissions from around 2200 through to 0600 or so – providing one has trouble with sleeping at nights! Insomniacs make good LA specialists!

Some LA signals heard of late have been –

● COLOMBIA

La Voz del Norte, Cucuta, on **4875** at 0415, OM identification in Spanish followed by local announcements in which Cucuta was mentioned several times. The schedule is from 0930 to 0500 variable, reportedly closing sometimes at 0630. The power is 5kW.

Radio Guatapuri, Valledupar, on **4815** at 0722, local-style music, OM with station identification at 0726 and again at 0736. Local announcements, some with the echo-effect much beloved by the LA's. Still on the air as late as 0745. The schedule is from 0930 to 0600 and the power is 10kW. Reportedly identifying as "Radio Favorita" it was "Radio Guatapuri" on both the above occasions.

● ECUADOR

Radio Federacion, Sucua, on **4960** at 0319, OM with announcements in Spanish, YL with folk songs. The schedule is from 1030 (Sundays from 1100) to 0300 (Saturdays until 0400, Sundays until 0100). The power is 5kW.

● SURINAM

Radio Apintie, Paramaribo, on a measured **5006** at 0305, light music European-style non-stop through to 0330 when announcements in Dutch. The schedule is from 0830 to 0430 and the power is unknown.

● ALGERIA

Algiers on a measured **15033** at 2057, OM (Old Man = Male announcer) with announcements in French, local-style music. At 2100, 5 pips time-check, OM with station identification and details of frequencies with transmission times (this channel not mentioned) in English. Algerian frequencies are

subject to constant variations.

● PORTUGAL

Radio Renascenca, Lisbon, YL (Young Lady = Female announcer) in Portuguese with the programme for Portuguese catholics abroad, scheduled from 1830 to 2230 on this particular channel.

● YEMEN ARAB REPUBLIC

Radio Sana'a on **9780** at 1950, Arabic-type music, YL with songs in the Home Service which is entirely in Arabic. The schedule on this frequency is from 0300 to 0700 and from 1000 to 2130, on Fridays additionally from 0700 to 1000. The power is 50kW.

● KUWAIT

Radio Kuwait on **11650** at 1830, OM with station identification followed by news of the Arabic world in the English programme intended for Europe, scheduled on this channel from 1800 to 2100. Also directed to the Arabian Gulf area.

● BULGARIA

Radio Sofia on **9700** at 1954, YL with the English programme for the U.K. and Eire, scheduled from 1930 to 2000 – all about mineral springs in Bulgaria on this occasion.

● EAST GERMANY

Radio Berlin International on **21500** at 1839, OM with station identification, frequencies and times details in the English programme for Europe and West Africa, scheduled from 1800 to 1845.

● ETHIOPIA

Addis Ababa on **7165** at 1512, xylophone music. At 1515, OM with a talk in English until 1520 then into a programme of European-style dance music until pips time-check at 1530 and a newscast after station identification by YL. All in the English programme, scheduled on this channel from 1500 to 1600.

● SOMALIA

SBS Mogadishu on **9585** at 1932, OM with news of African affairs in Somali (place names identified) then local music and songs by YL chorus. Lots of co-channel QRM (interference). This is the External Service which is scheduled from 1000 to 1930 (extended on this occasion). Domestic Service programmes are carried on this channel from 1530 to 1630.

●ROMANIA

Radio Bucharest on **9690** at 1957, OM with a talk about the libraries of Romania in the English programme for Europe, scheduled from 1930 to 2030.

●KENYA

Mombasa on a measured **4934** at 0341, OM with a religious service in vernacular, choir with hymns in the North Eastern and Coastal Service, scheduled on this frequency from 0330 to 0630 and from 1400 to 2005. The power is 20kW.

●MALI

Bomako on a measured **4838** at 2207, African-type orchestra, YL with songs, OM's with chants. The schedule is from 0600 to 0800 and from 1800 (Friday to Sunday inclusive from 1830) to 2400. The power is 18kW and this one is listed on **4825**.

●NETHERLANDS

Radio Nederland on **9895** at 0948, OM with the English programme intended for Europe and scheduled on this channel from 0930 to 1020.

●INDONESIA

RRI (Radio Republik Indonesia) Ujung Padang on a measured **4719** at 1520, OM in Indonesian with Sousa march interludes. The schedule here is from 0830 to 1230 but has been noted here closing as late as 1532 on several occasions. The power is 50kW.

RRI Jakarta on a measured **4774** at 1526, OM in Indonesian, short interludes of military music, almost certainly in parallel with Ujung Padang on this occasion. Jakarta transmits special events on this channel and is scheduled from 2200 to 0200 and from 0830 to 1600. The power is 50kW.

RRIBukittinggi on a measured **4828** at 1528, OM in Indonesian, signal just audible. This one operates from 2300 to 0300, 0500 to 0715 and from 0930 to 1600, is listed on **4827** and has a power of just 1kW.

RRI Yogyakarta on **5045** at 1535, OM's with a discussion in Indonesian. The schedule is from 0100 to 0300, from 0455 to 0800 and from 0955 to 1700. The power is 5kW.

●CHINA

Radio Peking on **9860** at 1920, OM with the English programme for Europe, scheduled from 1900 to 2000. All about the mistakes made during the "Great Cultural Revolution."

Radio Peking on **9880** at 1918, Chinese music in the Portuguese programme for Europe and Africa, scheduled from 1900 to 2000.

Radio Peking on **9920** at 1915, OM with the Cantonese programme to Europe, scheduled from 1900 to 2000.

Radio Peking on **9945** at 1912, OM with the Romanian programme, scheduled from 1900 to 1930.

Radio Peking on **3220** at 2150, OM in Chinese in the Domestic Service 1 programme scheduled from 2000 to 2300 and from 1318 to 1733.

●CHINA - REGIONALS

Kunming, Yunnan on **4760** at 1524, YL in Chinese, piano music. This is Yunnan 1 operating from 2150 to 0600 (Tuesdays until 0800) and from 0920 to 1600. An English language lesson is radiated from 2200 to 2230. (Yunnan People's

Broadcasting Station = "Yunnan Ren-min Guangbo Dian-tai" as identified in Standard Chinese).

PLA (People's Liberation Army) Fuzhou on **4045** at 1514, OM and YL alternate in Chinese. This transmitter radiates the Network 1 programme to Taiwan and other offshore islands from 2100 to 0145 and from 1000 to 1800.

Lanzhou, Gansu on **4865** at 2215, YL in Chinese. The schedule is from 2145 to 0100 (Sundays until 0600), from 0320 to 0600 and from 1000 to 1600.

Xizang, Tibet on **4750** at 1544, OM in Chinese, local-type classical music. The schedule is from 2230 to 0645 (March to September from 2300) and from 1000 to 1545. "Hsi-Tang Ren-min Guang-bo Dian-tai."

Haerbin, Heilongjiang on **4840** at 2226, OM and YL in Chinese, OM with songs. The schedule is from 2040 to 0630 (Thursdays until 0510) and from 0830 to 1530.

●THAILAND

Bangkok on **4830** at 1530, OM song in Thai with local orchestral music. Radio Thailand operates from 2240 to 1630 on this channel. The power is 10kW.

●NORTH KOREA

Pyeongyang on **9977** at 1315, OM with a newscast, YL with a song in Korean in the English programme for South East Asia, scheduled from 1300 to 1450.

●VIETNAM

Hanoi on a measured **9986** at 1345, YL with announcements in the Cambodian programme for South East Asia, scheduled from 1300 to 1400.

Hanoi on a measured **4944** at 2208, OM in Vietnamese in the Home Service 1 programme, scheduled on this channel from 2100 to 1615 (variable closing time, reported closing sometimes at 1630).

●MONGOLIA

Ulan Bator on a measured **4763** at 2221, OM and YL alternate in Mongolian, also logged in parallel on **4830**. This transmitter radiates the Home Service 1 from 2200 to 0100 and from 1030 to 1500; relays the R. Moscow Mongolian programme from 0600 to 0650, 0930 to 1000 and from 1200 to 1245; the Foreign Service in Russian from 1330 to 1400. Although scheduled to open at 2200, it has always been noted here as opening at 2202 with the National Anthem (the tuning signal commences at 2200). The power is 50kW.

●IRAQ

Radio Baghdad on **9745** at 2130, YL with station identification and opening announcements in the English programme for Europe, scheduled from 2130 to 2230. This item according to one of our regular readers, A. Dupres of Cardiff, an enthusiast just 16½ years of age - have we any younger fans? I must listen to Baghdad sometime, I lived there for some time and know it well - but I never saw any magic carpets!

Alastair also logged AIR Delhi on **11620** at 1915, at which time every Saturday he listens to "Quiz Time" and has sent in some questions of his own.

Another of his regular loggings is United Nations Radio on **15230** at 0800 when they transmit a newscast in English to Africa.

Medium and Short Wave Radio

By
I.M. Attrill

Medium waves plus 25, 39 and 49 metre bands. Special grade ferrite aerial. Low cost design.


This unusual 3-transistor radio covers the standard medium wave band and the short wave broadcast bands within a frequency range of approximately 5 to 12MHz. This range takes in the 25, 39 and 49 metre bands. The output is intended for high impedance magnetic headphones (2,000 Ω or 4,000 Ω) or a crystal earphone, and there is plenty of volume from any reasonably strong signal.

Medium and short wave receivers usually employ a ferrite aerial for medium wave reception and a telescopic aerial for short waves, but this design uses a ferrite aerial for both wavebands. The ferrite rod grade normally encountered in portable receivers has a useful range for efficient reception from around 150kHz to 2MHz and covers the medium and long wave bands. The ferrite rod used in the design to be described is a special F16 grade, with a range from 500kHz to 12MHz. This allows the receiver to cover the medium wave band and the short wave range just mentioned.

THE CIRCUIT

The receiver employs a t.r.f. circuit in which all amplification before the detector stage is carried out at signal frequency. This is as opposed to a superhet which first converts the received signal to an intermediate frequency, this being passed into an i.f. amplifier before detection. Since the i.f. amplifier works at a fixed frequency it can provide a high level of sensitivity and selectivity, and the performance of a superhet is superior to that of a t.r.f. receiver in these respects. On the other hand a superhet is much more complicated than a basic t.r.f. receiver and, on completion, requires careful alignment. As can be seen from Fig.1, the circuit of the t.r.f. receiver to be described is quite simple and it requires only a small number of components. A further advantage is that, after completion, it requires no alignment whatsoever and is ready for immediate use.

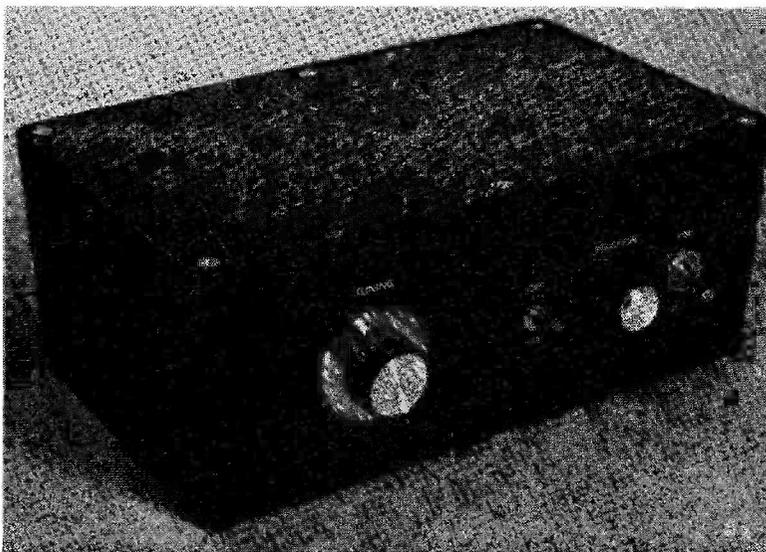L1 and L2 are the medium and short wave aerial coils respectively, and they are connected by



The prototype medium and short wave receiver is housed in a plastic case with the controls mounted on one of the longer sides.

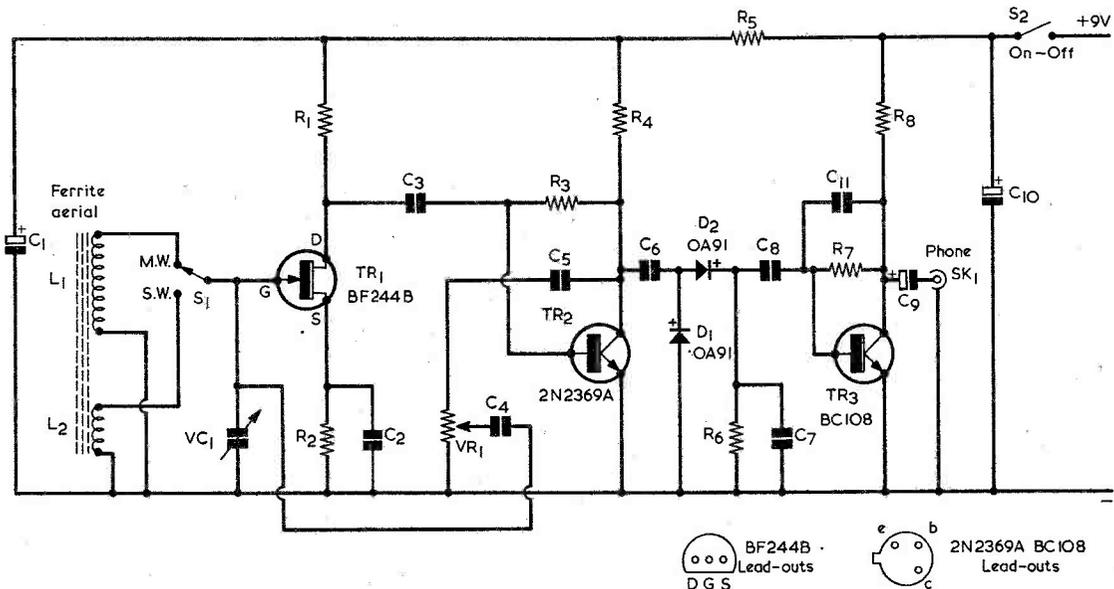


Fig.1. The circuit of the medium and short wave radio. The aerial uses a special grade ferrite rod which is suitable for short wave reception.

wavechange switch S1 to tuning capacitor VC1 and the gate of TR1. This is a Jfet having a very high input impedance, with the result that the aerial tuned circuit can be connected directly to the gate and there is no necessity for coupling windings. The coil specified for L1 has a coupling winding which is not shown in Fig.1. and no connections are made to this winding.

C3 couples the amplified signal from TR1 drain to the base of TR2, which functions as a broadband, untuned r.f. amplifier. The aerial signal is inverted both by TR1 and by TR2, so that the signal at the

collector of TR2 is in phase with the signal at TR1 gate. This allows positive feedback (known as reaction or regeneration in this application) to be provided from TR2 collector, through C5, VR1 and C4, back to TR1 gate, the level of feedback being controlled by VR1. This feedback increases the effective Q of the aerial tuned circuit by an extremely high level, allowing the receiver to have good selectivity and sensitivity. For normal reception, VR1 is advanced to the stage where TR1 and TR2 are just short of going into oscillation.

COMPONENTS

Resistors

(All fixed values ¼ watt 5%)

- R1 330Ω
- R2 1.5kΩ
- R3 680kΩ
- R4 330Ω
- R5 1kΩ
- R6 22kΩ
- R7 1MΩ
- R8 3.3kΩ
- VR1 100kΩ potentiometer, linear

Capacitors

- C1 100μF electrolytic, 10V. Wkg.
- C2 0.01μF polyester type C280
- C3 0.0068μF ceramic plate
- C4 2.2pF ceramic
- C5 100pF ceramic plate
- C6 0.047μF polyester type C280
- C7 0.015μF ceramic plate
- C8 0.1μF polyester type C280
- C9 10μF electrolytic, 10V. Wkg.
- C10 100μF electrolytic, 10V. Wkg.
- C11 560pF ceramic plate
- VC1 variable air-spaced (see text)

Inductors

- L1 medium wave aerial coil type MWC2 (Ambit)
- L2 see text

Semiconductors

- TR1 BF244B
- TR2 2N2369A
- TR3 BC108
- D1 OA91
- D2 OA91

Switches

- S1 s.p.d.t. toggle
- S2 s.p.s.t. toggle

Socket

- SK1 3.5mm. jack socket

Miscellaneous


- F16 grade ferrite rod, 200mm. x 9.5mm. (Ambit)
- 2 clips type FRPC (Ambit)
- Plastic case (see text)
- 9-volt battery type PP3
- Battery connector
- 1 large control knob
- 1 small control knob
- Crystal earphone or high impedance headphones with 3.5mm. jack plug
- Wire for L2 (see text)
- Nuts, bolts, wire, solder etc.

The signal at the collector of TR2 passes through C6 to the detector circuit comprising D1, D2, R6 and C7, and the detected audio signal is fed via C8 to the audio amplifier, TR3. C11, between the collector and base of TR3, provides negative feedback at the higher audio frequencies and thus rolls these off. The result is a lower noise level and a reduction in adjacent channel interference. C9 is the output d.c. blocking capacitor.

Supply decoupling is provided by C1, R8 and C10. The current consumption of the receiver is only about 3.5mA, and a small PP3 battery is adequate.

COMPONENTS

The F16 grade ferrite aerial rod has a length of 200mm. and a diameter of 9.5mm. and is available, together with two mounting clips type FRPC, from Ambit International. Ambit International also supply the medium wave coil type MWC2. The BF244B required for TR1 is available from several retailers as are the 0.0068 μ F and 0.015 μ F ceramic plate capacitors, C3 and C7. Tuning capacitor VC1 can be any air-spaced variable component having a value between 200 and 250pF. The author used the front (208pF) section of a 208pF plus 176pF 2-gang capacitor. The receiver has to be housed in a plastic case to ensure that the ferrite aerial is not screened, and this has to be large enough to take the rather long ferrite rod. The case employed by the author has dimensions of 215 by 130 by 85mm. and is a case type MB4 available from Maplin Electronic Supplies.

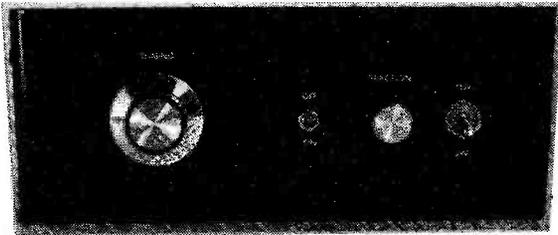


On the front panel the tuning control is on the left. S2 is mounted approximately central with the potentiometer and S1 to its right.

SHORT WAVE COIL

The short wave aerial coil is wound by the constructor using multi-strand p.v.c. covered connecting wire. The author used 7 x 0.2mm. wire and this is listed by Maplin Electronic Supplies as "Hook-up Wire". However any similar wire should give practically identical results provided that the length of the coil is about 10m. The winding is illustrated in Fig.2.

Start by anchoring the wire to the end of the ferrite rod by a length of insulating tape 19mm. ($\frac{3}{4}$ in.) wide, leaving a lead-out wire of adequate length, say about 200mm. Then wind exactly 8 turns of wire around the rod, closely spaced so that the winding is about 10mm. long. A second piece of insulating tape is then used to anchor the free end of the coil to the rod and to prevent the coil from unwinding. The free wire is then cut to a suitable length. The two lead-outs of the coil can be cut to their final length during the wiring of the receiver.

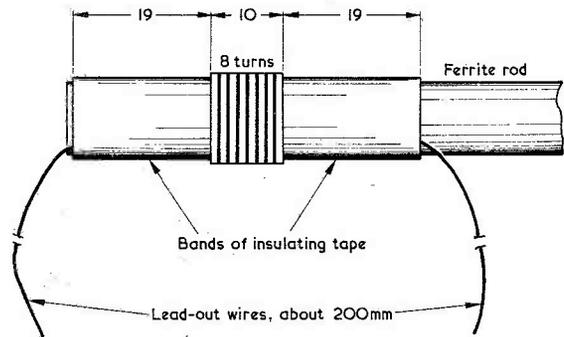

All dimensions in mm

Fig.2. The short wave coil is home-wound and uses ordinary stranded connecting wire as described in the text.

PRINTED BOARD

Most of the components are assembled on a printed circuit board, which is shown full-size in Fig.3. The board is prepared in the usual way.

The ferrite aerial is fitted to the board after the other components have been soldered in place. The two mounting clips are secured to the board by means of short 6BA bolts and nuts. The short wave coil takes up the position relative to the board which is shown in Fig.3. and the medium wave coil is fitted to the other end of the ferrite rod. It is positioned so that only about 2mm. of the rod protrudes outside the end of the coil former and is then taped in this position.

The parts are mounted in the plastic case referred to earlier. This is rather larger than is really required, but it is necessary for it to have a dimension which will accommodate the ferrite aerial rod.

The front panel controls are laid out as shown in the photographs. The tuning capacitor is to the left, and on its right, slightly right of centre, is the on-off switch S2. The next control is VR1 with S1 on its right. The precise positioning of these controls is not critical. The tuning capacitor requires a hole of about 16mm. diameter for its spindle and bush. It will have 4BA tapped holes on its front plate and corresponding 4BA clear holes are needed in the front panel. A piece of paper with a $\frac{1}{4}$ in. hole in it is passed over the spindle of the capacitor and the positions of the three holes marked on it in pencil. The paper can then be used as a template to mark out the corresponding holes in the panel. The three 4BA bolts holding the capacitor in place must be very short since their ends must not pass more than fractionally beyond the inside surface of the capacitor front plate. Should the bolt ends pass too far into the capacitor the moving or fixed vanes may be damaged.

The printed board is fitted to the case bottom by means of two 6BA bolts and nuts, with spacing washers to keep the board underside clear of the inside surface of the case. The board is not finally fitted in place, however, until it has been connected to the controls, output socket and battery clip. The wiring should be kept reasonably short and direct. Try to keep the two non-earthly leads to VR1 fairly well spaced and not running closely side by side, otherwise



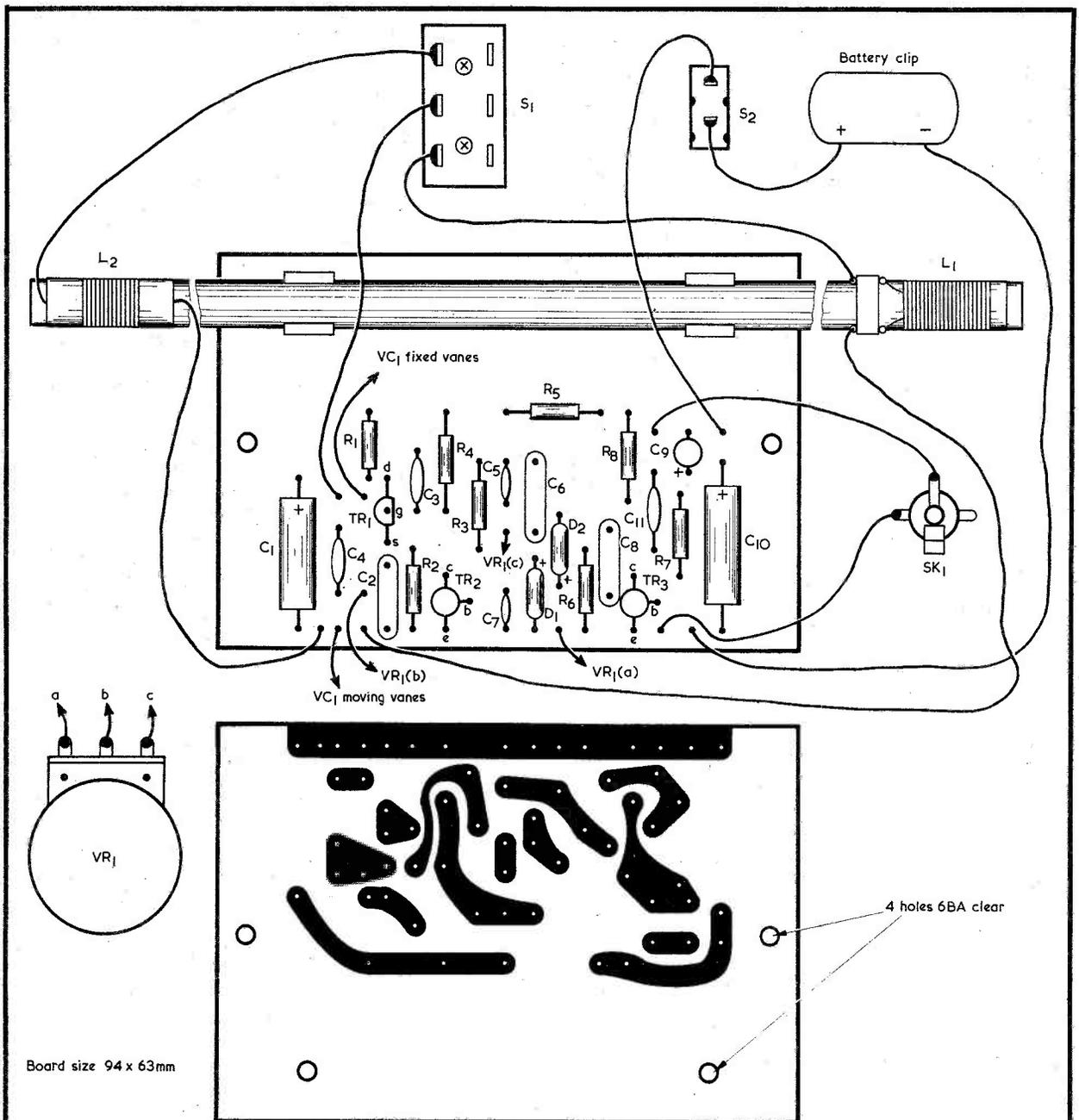


Fig.3. The majority of the components are assembled on a printed circuit board which is reproduced full size.

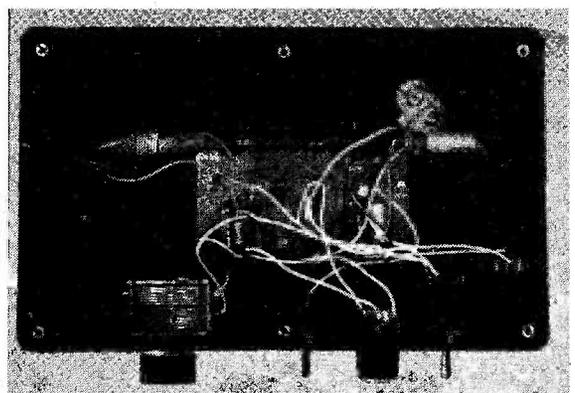The printed board assembly is fitted to the bottom of the case with the ferrite rod aerial away from the panel controls.



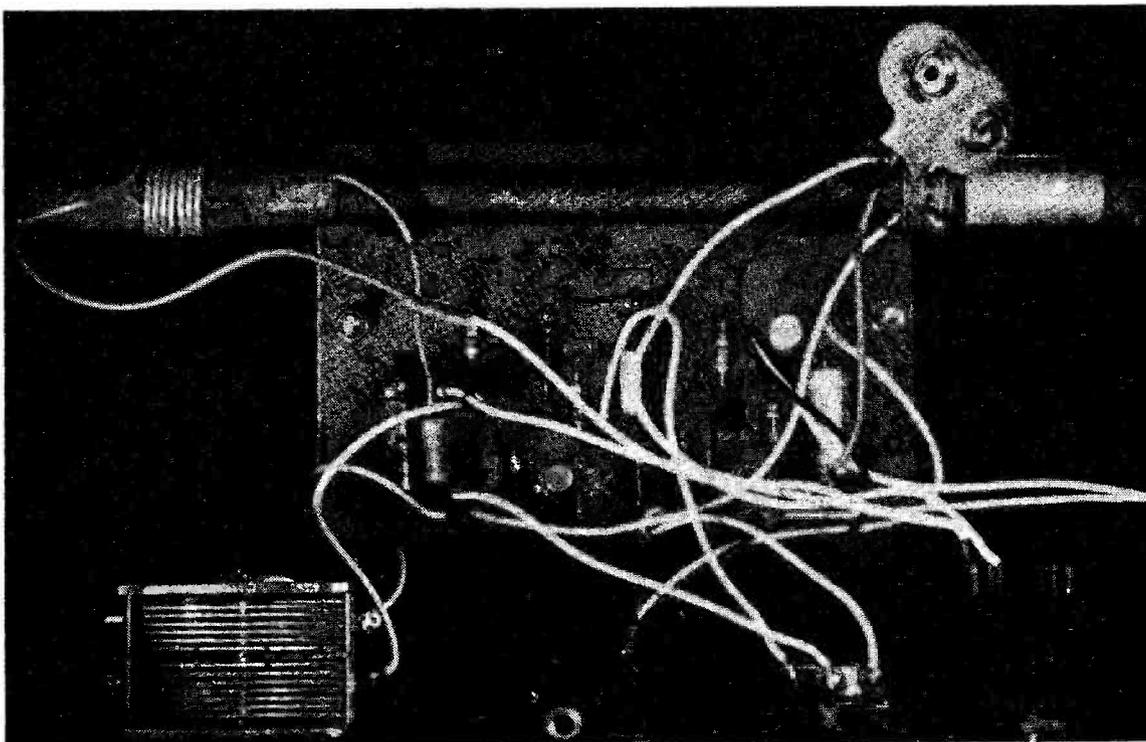

A closer look at the printed board assembly

stray capacitance between them may render VR1 unable to control the level of regeneration properly. These are the two wires which connect to tags B and C of the potentiometer, as shown in Fig.3.

On the front panel, VC1 should be fitted with a large control knob. A smaller knob will suffice for VR1.

USING THE SET

With a crystal earphone or high impedance headphones plugged into SK1, VR1 backed well off (i.e. turned anticlockwise) and S1 set to the medium wave position, it should be possible to tune in a few stations by means of VC1. Sensitivity and Selectivity will probably both be rather poor, and advancing VR1 clockwise will give improved results. If VR1 is advanced too far the circuit will oscillate, causing beat notes to be produced when tuning through a station, and satisfactory reception will be impossible. For optimum results, VR1 should be backed off slightly from the point at which oscillation starts. The best setting required for VR1 will alter slightly after any significant adjustment of VC1. It will probably be found that, with VR1 advanced as far as possible without oscillation occurring at any setting of VC1, quite good results will be obtained over the entire medium wave band.

The receiver is operated in the same way when S1 is set to select short waves. The short wave broadcast bands are quite easy to locate as they provide what are normally the strongest signals, but reception on each band will vary somewhat according to the prevailing conditions. It is unlikely that there will be a single setting for VR1 which will give good results over the whole short wave tuning range, but it should be possible to find a setting for each broadcast band which gives good results over that band.

If, at some point on one of the tuning ranges the level of regeneration is excessive even with VR1 fully backed off, the gain of the r.f. amplifier must be slightly decreased. This can be achieved by increasing the value of R3 to $1M\Omega$.



In your workshop

A Session of Puzzles.

No. 1.

Puzzle along with Dick and Smithy.

"But there's nothing to flaming well do!"

"We could," suggested Smithy, "have a game of swear-words Scrabble."

"No, thank you," replied Dick bitterly. "You know more dirty words than I do and most of the ones I do know I don't know how to spell."

"How about tidying up your bench?"

"I've tidied it up."

"Couldn't you knock up some little gadget to pass the time?"

"I can't think of anything to knock up."

A FEW PUZZLES

Dick squatted morosely on his stool and scowled at the Serviceman.

"Well," said Smithy, "I have to agree that things have been pretty quiet for the last few days and that we've completely cleared up everything that's in for repair."

"Exactly," confirmed Dick moodily, "and now there's nothing whatsoever to flaming well do. I'm bored rigid!"

Smithy pondered for a moment, then brightened.

"I've just had an idea," he said cheerfully. "I'll set you a little puzzle and we'll see if you can solve it."

"A puzzle? What sort of a puzzle?"

"An electronics puzzle."

"That doesn't sound a bad idea at all," stated Dick, quickly enthusiastic. "What's the puzzle going to be?"

Smithy pulled his note-pad towards him.

"Come over here," he said, taking a ball-point pen from his pocket, "and I'll show you."

Dick carried his stool over to Smithy's bench and perched on it while the Serviceman carefully drew out a circuit. (Fig. 1).

"There you are," said Smithy, putting down his pen. "Here's a simple circuit with four batteries and eight resistors in it."

"What am I supposed to do?"

"Find out the current which

flows in the circuit. Everything is in series and so the same current flows through all the resistors and all the batteries."

(Would you, gentle reader, like to puzzle along with Dick and Smithy? If so, read no further and see if you can determine the current which flows in Smithy's circuit. Then come back to the events of the Workshop and discover whether your answer is the same as that reached by our servicing pair).

"I could start simplifying things a bit, I suppose," said Dick doubtfully, "by changing the four pairs of resistors to single resistors. For instance I could replace R1 and R2 by a single 3Ω resistor."

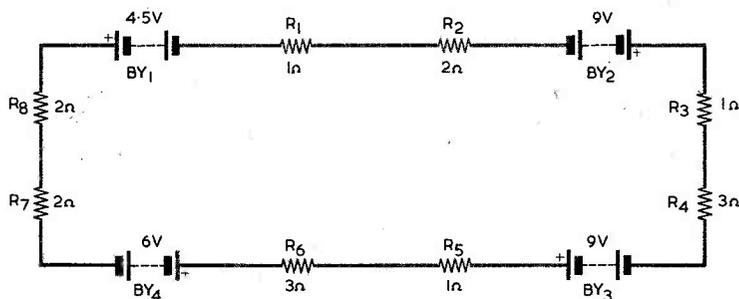


Fig. 1. If, this month, you would like to puzzle along with Dick and Smithy, avert your eyes from the following diagrams and their captions and proceed straightaway to the start of the text. This is the first puzzle which Smithy put to Dick.

"You could do that," agreed Smithy, "but it wouldn't help you much."

"It's those darned batteries," complained Dick. "You've got no less than four of them distributed throughout the circuit."

"If the batteries are worrying you, try simplifying them."

"How can I?"

"Think about it. To give you a hint I said just now that the same current flows through all the resistors and all the batteries."

"Which must of course be true," mused Dick. "Hang on a jiff! Will the same current flow if I take a battery out of one part of the circuit and insert it at another place?"

"Of course it will. Provided, that is, you don't reverse its polarity."

Dick picked up Smithy's pen and proceeded to draw in Smithy's note-pad.

"Then," he said excitedly, "I could move BY2 to the left so that it's next to BY1. And I could also move BY3 to the left so that it connects directly to BY4."

He quickly completed the new version of the circuit and

showed it to Smithy. (Fig. 2(a)).

"Keep at it," said Smithy. "You're on the right lines."

"I think I'm nearly there now. Well, BY1 and BY2 have their two negative ends together, which means that BY1 subtracts 4.5 volts from the 9 volt BY2. So I can replace them with a single 4.5 volt battery having the same polarity as BY2. There's the same sort of thing with BY3 and BY4, and these can be replaced by a single 3 volt battery with its negative end connecting to R6." (Fig. 2(b)).

"That's perfectly correct. Now shift the lower battery so that it's next door to the upper battery. Be careful with its polarity."

"I'll bring it round to the left hand side of the upper battery," said Dick. "Now, the positive side of the lower battery points in the clockwise direction so, when I bring it round, its positive end will be to the right."

Dick scribbled out the new rearrangement of the circuit. (Fig. 2(c)).

"And that," said Smithy, "is very nearly the final step. The

two batteries are series-aiding and so they provide a total voltage of 7.5 volts. The next thing to do is to add up the values of the resistors."

"I'll do that next," said Dick. "Let's see what it is. Ah yes, the grand total comes to 15Ω."

"Which means that we've got 7.5 volts pushing a current through 15Ω. What will that current be?"

"It will be 7.5 volts divided by 15Ω. Which works out at half an amp?"

"Correct," confirmed Smithy. "The current which flows in the circuit is half an amp."

CIRCUIT ERROR

"This is great," said Dick, pleased at his success. "Let me try out one on you."

"Okay," said Smithy equably. "See if you can catch me out."

Dick walked over to his bench and returned with a sheet of paper.

"Here we are," he said. "I was making up a transistor phase splitter the other day and I got some very funny voltage readings. I made a note of them, and here they are."

Dick showed the paper to


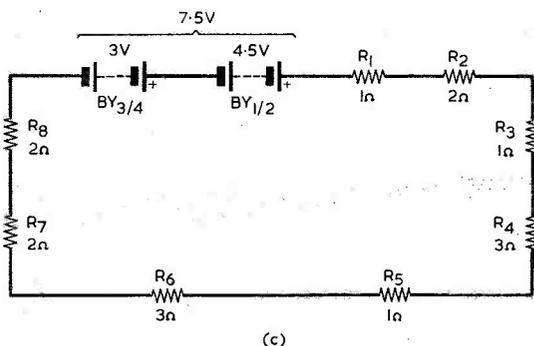
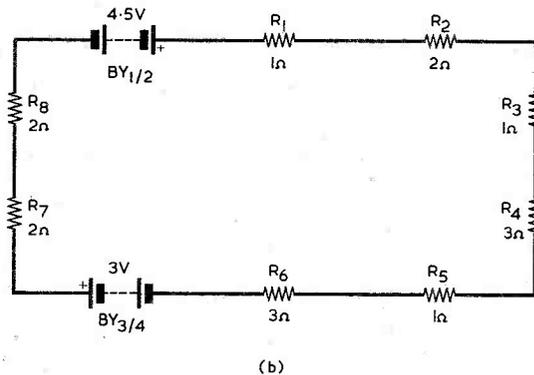
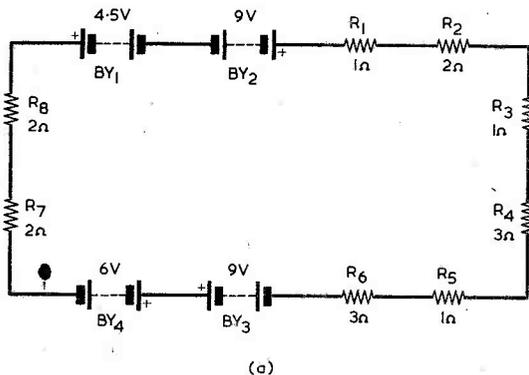


Fig. 2(a). First stage in simplifying the circuit. BY2 and BY3 are moved left to connect directly to BY1 and BY4 respectively.

(b). The circuit is now effectively powered by two batteries.

(c). The final simplification consists of bringing round the lower battery. (Some solvers may have simply added and subtracted battery voltages, according to polarity, to arrive at the same solution as results from this diagram).

MORSE MADE EASY

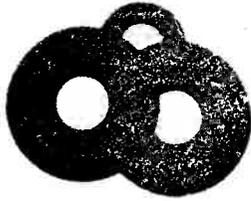

BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books. Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750gms). Details only s.a.e.

THE G3HSC MORSE CENTRE
S. Bennett, (Box 8), 45 Green Lane,
Purley, Surrey.

Name

Address

THE

MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET
LONDON W2 1NP
Tel: 01-402 9176

Please mention

Radio & Electronics Constructor

when replying to advertisements

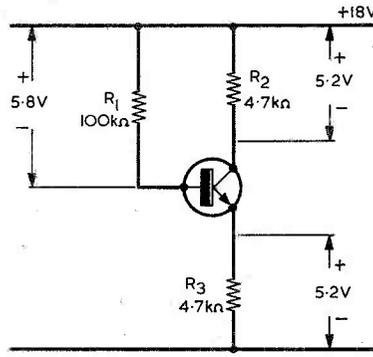


Fig. 3. There is a single error in this diagram.

Smithy. (Fig. 3).

"Dear me," stated Smithy. "I must say that those voltages are very peculiar."

"There is one single error in that circuit drawing," said Dick. "I found out what it was later."

"Did you use an incorrect value resistor?"

"No."

Were the queer voltage readings due to a low resistance voltmeter?"

"No. I used a very high resistance voltmeter."

"Is it a silicon transistor?"

"It is," stated Dick, "and its base connects to R1, its collector to R2 and its emitter to R3. What you have to find is the single error which exists in the circuit."

(Can you, as you read this, spot the single error? You already know that all resistor values are correct. See if you can find the error before Smithy does).

Smithy gazed thoughtfully at Dick's circuit.

"Do you know what caused these funny voltages?"

"I know what the error was because I was able to put it right," said Dick a little uncomfortably. "But I don't know why the error caused the voltages to appear!"

"What happened," stated Smithy with complete certainty, "is that you made up the circuit with a p.n.p. transistor instead of an n.p.n. transistor."

Dick looked crestfallen at Smithy's quick solution to his problem.

"Yes," he said sheepishly, "That's exactly what I did do. After I got these queer voltages I checked the transistor marking and I found I'd soldered in the wrong type."

"So the error in the circuit

drawing," said Smithy, "is that the emitter arrow is pointing in the wrong direction. To get the voltages shown, the emitter arrow should be pointing inwards instead of outwards."

"That's exactly right. Now you tell me why the voltages appeared!"

"All right," said Smithy. "Well, if it had been an n.p.n. transistor there would have been a voltage drop of 0.6 volt only between the base and the emitter. But in your drawing there are 5.8 volts across R1 and 5.2 volts across R3. Subtract the sum of these from the 18 volts supply voltage and you're left with 7 volts across the base emitter junction. So that junction must be reverse biased. From which it follows that you used a p.n.p. transistor instead of an n.p.n. one."

"If the base-emitter junction is reverse biased," queried Dick, "why does it pass any current at all?"

"Because" replied Smithy, "the base-emitter junction of most silicon transistors has a breakdown voltage in the region of 6 to 10 volts. When that breakdown voltage is reached the junction acts like a zener diode. The transistor you used happened to have a breakdown voltage of 7 volts. Now, because the transistor was p.n.p. instead of n.p.n. the collector-base junction was forward biased, and that explains the 0.6 volt difference between the voltage across R1 and the voltage across R2. Let's redraw the circuit using zener diode and ordinary diode symbols. This is how it looks."

Smithy picked up his pen and drew the equivalent circuit. (Fig. 4).

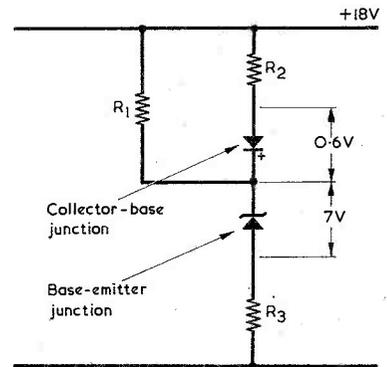


Fig. 4. An equivalent circuit incorporating diodes.


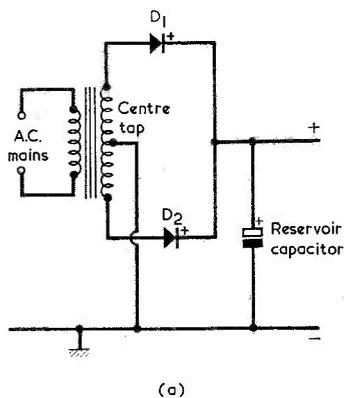


Fig. 5(a). A standard full-wave rectifying circuit in which the mains transformer has a centre-tapped secondary.

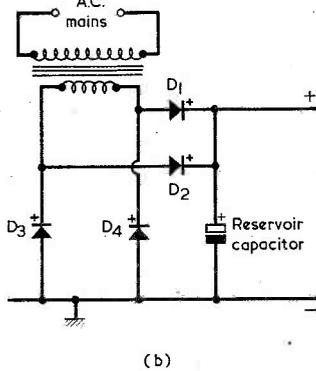

(b). By adding two rectifier diodes it is possible to obtain the same rectified voltage with only half the secondary winding.

STRANGE RECTIFIER

"Well," said Dick. "You've answered my little puzzle, so how about setting me another one?"

"All right," replied Smithy obligingly. "What I'll do is introduce you to an unfamiliar power supply rectifier circuit."

Dick settled himself more comfortably on his stool.

"Righty-ho," he said cheerfully. "Fire away!"

"As you know," said Smithy, drawing once more on his note-pad, "the usual full-wave rectifier circuit has two rectifier diodes connected to the outside ends of a mains transformer secondary. The secondary is centre-tapped, and the centre tap goes to the negative rectified supply rail. Like this."

He pointed to the circuit which he had now completed. (Fig. 5(a)).

"That's basic enough," commented Dick. "On half-cycles when the upper end of the secondary is positive diode D1 conducts, and on half-cycles when the lower end is positive diode D2 conducts. Both diodes cause the reservoir capacitor to charge and stay charged."

"Fair enough," said Smithy. "Now, it's possible to get the same full-wave rectifying action and the same rectified voltage with only half the secondary winding which is

required in the ordinary full-wave circuit. All you have to do is to add two more rectifier diodes, giving you a circuit like this."

Smithy drew a further circuit. (Fig. 5(b)).

"How does that work?"

"It works like this," said Smithy. "We've got our original two diodes, D1 and D2. And I've now added two more diodes, D3 and D4. Let's see first what happens on half-cycles when the right-hand side of the transformer secondary is positive. Diode D3 prevents the left-hand side of the secondary going negative of chassis by any significant voltage, so virtually the full secondary voltage is applied through D1 to the reservoir capacitor. On the alternate half-cycles the left-hand end of the secondary is positive. This time, diode D4 prevents the right-hand end going negative of chassis, and virtually all the secondary voltage is applied through diode D2 to the reservoir capacitor. So, just by adding two diodes we get the same full-wave rectifier action as we had with the centre-tapped transformer secondary, and we only need half the secondary winding to give the same rectified voltage."

"But that's a marvellous rectifier circuit," stated Dick. "Why don't we see it used in practice?"

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply:

Radio & Electronics
Constructor Data Books
Panel Signs Transfers

Also a postal service

PEATS

the world of electronics

25 Parnell Street, Dublin 1. Tel 749972

ELECTRONIC

TUTOR KITS

Learn electronics the effective way by experiments. Each kit contains an illustrated handbook, which takes you step by step through the fundamentals of electronics, plus all the components needed. No soldering. Safe and instructive for even the young enthusiast. Kit 1, £5.85. Kit 2, £5.95. Kit 3, £6.15. SAE for leaflets on this and other RXG products.

RXG ELECTRONICS LTD.

15 Walnut Tree Crescent,

Sawbridgeworth, Herts, CM21 9EB.

GAREX

RESISTOR KITS new extended range at old prices:

E12 series 10Ω to 1M, 61 values, 5% carbon film, general purpose ratings ½W or ¼W (please extra).

Starter pack 5 each value (305) £3.10

Standard pack 10 each (610) £5.55

Mixed pack, 5 each ½W plus ¼W (610) £5.55

Giant pack 25 each (1525) £13.60

NICAD RECHARGEABLES physically as zinc carbon: AA(U7) £1.30, CU(U11) £3.35; PP3 £5.55.

Any 5+; less 10%; any 10+; less 20%.

VHF FM MONITOR RECEIVERS

HF 12 POCKET SIZE 12 channel xtal controlled. 4MHz bandwidth in range 130-174MHz. With nicad & charger. £57.95 Xtals extra, see below.

SOUNDAIR 008 PORTABLE SCANNER 8 channel xtal controlled. Nicad, charger. £59. Xtals extra.

SR-9 top selling monitor: 2m-FM with 144-146MHz full coverage VFO, plus 11 xtal controlled channels, ideal for fixed or mobile listening. 12V DC operation. £47.50. Xtals extra.

MARINE BAND SR-9, 156-162MHz £47.50.

CRYSTALS FOR HF-12, NR-56, SR-9, SOUNDAIR 008, TM56B: all 2m channels in stock from 0(145.0) to 32(145.8) at £2.46 (plus 15p post). Over 40 popular marine channels at £2.85 (plus 15p post) Sae list.

AMPLIFIER MODULE new, fully assembled 6W IC unit, 12V DC. Low impedance (4-8) input & output for extn. speaker amplification, with circuit £2.75

CO-AXIAL CONNECTORS & ADAPTORS see list

PL259 UHF plug plus reducer 75p;

SO239 UHF socket panel mtd. 60p;

2xSO239 Inline coupler £1

2xPL259 Inline coupler £1

Co-ax fitting - any 5+; less 10%

MAINS P.S.U. 12v 1A regulated. British made by GAREX £15.95.

Main distributor of Revco aerials and special products.

Access - Barclaycard

PRICES INCLUDE UK POST & VAT

CALLERS BY APPOINTMENT

GAREX ELECTRONICS

7 NORVIC ROAD, MARSWORTH.

TRING, HERTS HP23 4LS

Cheddington (STD 0296) 668684

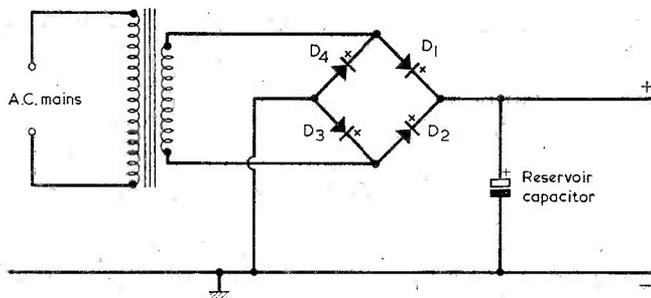


Fig. 6. The familiar bridge rectifier.

"There's the mystery," replied Smithy. "See if you can fathom it out!"

(And can you fathom it out? On the face of it, Smithy's rectifier circuit cannot help but work. Can you remember it being used in a practical application? Be warned, there's a catch).

"There's something fishy

here," said Dick suspiciously. "I think you're reverting to your usual devious tactics."

Smithy presented an expression of utter innocence to his assistant.

"No, I'm not," he said. "I've drawn out a working rectifier circuit and it functions exactly as I've described it."

"Then why," queried Dick

scowling, "haven't I seen it used in practice? Or have I?"

Smithy remained silent.

"Four rectifier diodes and an untapped mains transformer secondary," muttered Dick. "Now let me think about this."

He picked up Smithy's pen and traced the lines in the rectifier circuit. Suddenly his brow cleared and, decisively, he drew another rectifier circuit. (Fig. 6).

"You crafty devil," he grinned. "You really had me there! That circuit of yours is just a standard full-wave bridge rectifier!"

"It had you fooled for a bit though, didn't it?"

"I'll say it did," agreed Dick.

"It just shows how you get used to seeing circuits drawn out in a standard fashion. Now let's see if I can dream up another puzzle for you."

Dick and Smithy complete their session of puzzles next month.

AGILE TARGETS

Under a contract from the Ministry of Defence, EASAMS Limited, a member of the GEC-Marconi group of companies, is studying the feasibility of providing highly manoeuvrable and realistic "agile" targets for anti-tank weapons training.


Using a practical knowledge of the terrain, training programmes and support facilities on each of the Army's firing ranges, the EASAMS commission is to bring an imaginative approach to new and existing target system concepts. This will take into account the financial and logistic limitations within which the target system is to operate. EASAMS' task is to determine whether technically and economically feasible compromises can be reached among a number of conflicting requirements.

Anti-tank weapons are now able to engage modern armoured vehicles which are fast and highly manoeuvrable. New moving targets capable of varying speed and direction during a target run are required to train tank crews, anti-tank gunners and missile operators in the use of the new weapons.

Many training techniques, such as simulators and non-firing manoeuvres are available, but there is no substitute for live firing against realistic targets in the appropriate environment.

An ideal target should look and behave like the armoured

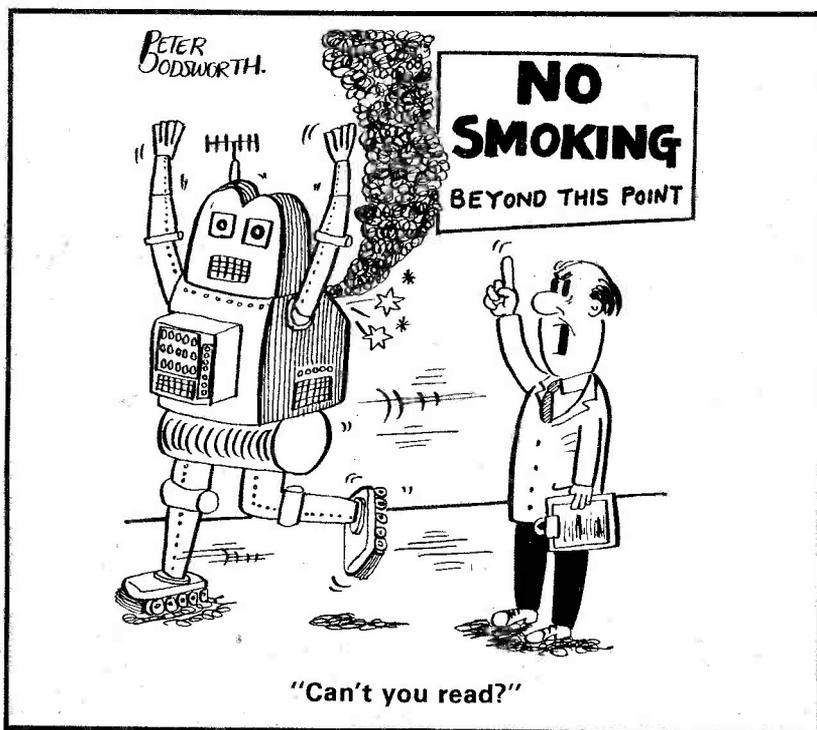vehicle it represents and react realistically when hit. It should provide a cheap easily controlled solution, immune to intentional weapon strikes and to adverse range conditions. Also, it should make minimal demands on range facilities and manpower.




RADIO & ELECTRONICS

CONSTRUCTOR

MAY 1981

IN NEXT MONTH'S ISSUE

CRYSTAL CALIBRATOR

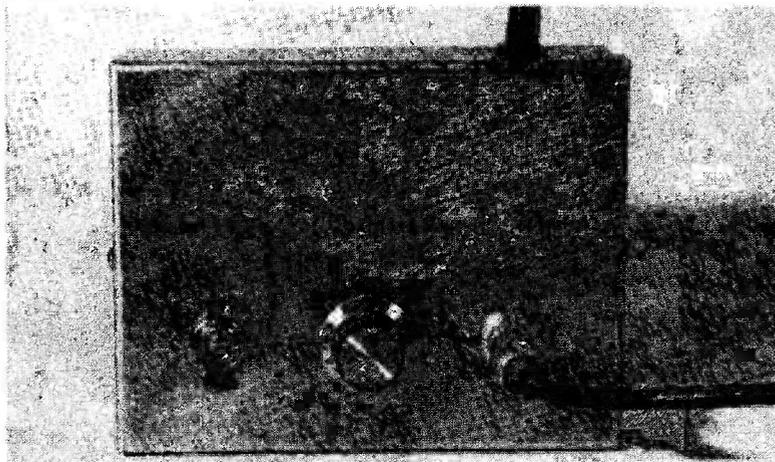

Eight frequency decades – 1Hz to 10MHz
Harmonic-rich square wave outputs.
Receiver calibration and digital applications.

3-STAGE M.W. SUPERHET

Two high gain transistors and an integrated a.f. amplifier.

Low component count.

Full speaker output.

**BURGLAR ALARM
WITH
ENTRANCE DELAY**
Suggested Circuit

**A SESSION
OF PUZZLES No. 2.**
In Your Workshop

• CB •
AM to FM conversions examined
—an objective assessment

PLUS MANY OTHER ARTICLES

Radio Topics

By Recorder



Molex Electronics Limited announce a touch switch with a difference. Instead of controlling circuits by way of electronic semiconductor devices, the Molex switch simply causes two electrical surfaces to come into physical contact with each other. Touch pressure to operate the switch is only 6 to 10 ounces.

The switch has been made feasible by the development of a special process which allows a conductive silver polymer ink to be deposited on a flexible substrate. Two sections of thin flexible polyester sheet with conductive surfaces facing each other are separated by a thin insulated spacer layer with holes, and the whole assembly is sealed. It may be mounted on a flat surface whereupon, when the outer layer is lightly touched, the two conductive surfaces come into contact with each other and complete the circuit in which they appear.

The outer surface can be covered by a graphic overlay showing numbers, letters or words printed in an attractive design. As many individual switches as may be required can be provided in a given area, so that touching, say, the printed figure 1 on the overlay causes circuit 1 to be actuated, touching number 2 completes circuit 2, and so on.

The new product is known as the 10900 Membrane Switch and is intended for low energy logic level switching applications. Switch systems can be custom designed for any particular function, and the manufacturers are Molex Electronics Limited, Holder Road, Aldershot, Hampshire.

PROBES AND PULSES

Of assistance in servicing and developing digital circuitry are two new probes available from OK Machine & Tool (UK) Limited, Dutton Lane, Eastleigh, Hants, SO5 4AA. Both items are housed in narrow diameter cylindrical casings which can be held in the hand, and are provided with prod tips for connection to digital equipment on either side of the printed board.

The first item is the PRB-1 Digital Logic Probe, which costs less than £30 but has all the features of much more expensive units. It detects pulses as short as 10 nanosecond, has a frequency response of better than 50MHz and automatic pulse stretching to 50 nanosecond. The Logic Probe is compatible with r.t.l., d.t.l., h.t.l., t.t.l., MOS, CMOS and microprocessor logic families, and it also features 120K Ω input impedance, power lead reversal protection and over-voltage protection up to 200 volts positive or negative. The supply voltage range is 4 to 15 volts, and an adaptor type PA-1 can be supplied for use with voltages from 15 to 25 volts.

The PLS-1 is the second item. This is a multi-mode high current pulse generator. It will superimpose a dynamic pulse train at 20 p.p.s. or a single pulse onto the circuit points under test, without having to unsolder pins or cut printed circuit traces, even when the circuit points are being clamped by digital outputs. It can source or sink sufficient current to force saturated output transistors in digital circuits into the opposite logic

state. Signal injection is by means of a pushbutton switch near the probe tip. When the button is depressed a single high-going or low-going 2 microsecond pulse is delivered to the circuit under test. Pulse polarity is automatic, and high level points are pulsed low and low level points are pulsed high. Holding the button down causes a series of pulses at 20 p.p.s. to be delivered to the digital circuit. The PLS-1 is ideally suited for use in conjunction with the PRB-1 probe and it also costs less than £30.

LONG SCALE MULTIMETER

The photograph shows the new 4½ digit multimeter Model 1503 which has been introduced by Thurlby Electronics. This has an unusually long scale of 32,768 (2 to the power of 15) counts or 15 bits on d.c. voltage and resistance, 16,384 counts or 14 bits on a.c. voltage and 8,192 counts or 13 bits on current. It is stated that the long scale length gives the 1503 much greater resolution and higher accuracy than competitive 3½ and 4½ digit meters.

Thirty measuring ranges are provided, covering the five basic functions of d.c. and a.c. voltage, d.c. and a.c. current, and resistance. In addition a diode test and crystal controlled frequency measurement up to 3.9999MHz are included. Resolution is within 0.1kHz, and frequency measurements can be extended to 7MHz with display overflow. The 1503 has very high sensitivity figures of 10 μ V, 10M Ω and 0.001 μ A, and an input impedance of

The Model 1503 digital multimeter manufactured by Thurlby Electronics. This has an exceptionally long scale length of 15 bits on d.c. voltage measurements, providing very high resolution and accuracy.



1,000M Ω can be selected for low voltage readings as an alternative to the standard 10M Ω . Maximum voltage input is 1,200 volts and currents can be measured up to 25 amps.

The multimeter combines a clear liquid crystal display with low power circuitry to give hundreds of hours of operation from a set of batteries. The casing is tough knock-proof ABS plastic and the multi-tilt stand doubles as a carrying handle. In the laboratory the 1503 can be operated from its a.c. mains adaptor, or from batteries for near infinite common mode rejection.

The manufacturers are Thurlby Electronics Limited, Coach Mews, St. Ives, Huntingdon, Cambs, PE17 4BN.

LOW COST MICROCOMPUTER

A low cost Z80-based microcomputer system, the

Video Genie EG3000 Series, is now being offered by Cambridge Micro Computers Limited, Cambridge Science Park, Milton Road, Cambridge, CB4 4BN. The system hardware is shown in the second photograph and it is accompanied by software and support which make it ideally suited for industrial and educational applications. Designed to plug into a video monitor or u.h.f. television receiver, the Video Genie costs £330 (plus VAT), and Cambridge Micro Computers is also making available a Microsoft Z80 editor/assembler package on magnetic tape cassette, at a price of £24 (plus VAT).


The Video Genie EG3000 Series is a fully self-contained system with its own built-in power supply, u.h.f. modulator and cassette tape unit. Software is based on the well established BASIC interpreter used on the TRS-80, and the

standard system is supplied with a 16K random-access memory plus 12K of Microsoft BASIC in read-only memory. A 51-key typewriter-style keyboard with 10-key rollover facility is also included.

The system is ideally suited for education, particularly the teaching of BASIC software, as well as providing a low cost approach to Z80 microprocessor system development. In addition to the wide range of software available on cassette, the Video Genie's interface capability allows it to be expanded with the use of flexible-disc stores and printers into a comprehensive microprocessor system.

The Video Genie comes complete with a BASIC demonstration tape, a video lead and a second cassette lead, as well as a user's manual, BASIC manual and beginner's programming manual.

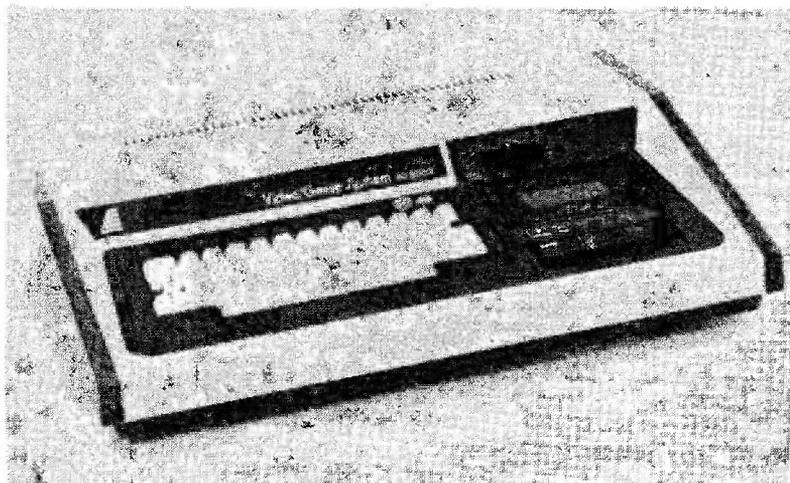The Video Genie EG3000 Series, offered with industrial and educational support by Cambridge Micro Computers Limited.



Active Tone Control Module

By A. P. Roberts

Very low distortion and noise


Treble boost and cut • Bass boost and cut

The tone control circuit to be described is primarily intended for those who are constructing their own amplifier systems, either from scratch or by using some of the excellent pre-amplifier and power amplifier modules which are currently available. The performance of the circuit is very good, the t.h.d. level being less than 0.05% over the audio frequency range provided the output is kept to about 1 volt r.m.s. or less, and this should be more than adequate to fully drive any normal power amplifier. The output has to reach about 5 volts r.m.s. before serious distortion occurs. The unweighted signal-to-noise ratio is better than -80dB relative to an output of 1 volt r.m.s. The circuit has an input impedance of 500k Ω , so that there is minimal loading on the stage which drives the

circuit. An emitter follower output stage gives the circuit a low output impedance, whereupon the output should not be significantly loaded by the following power amplifier.

BASS AND TREBLE

Both bass and treble controls are included, and these can each provide about 12dB of boost and cut (at 100Hz for the bass control and at 10kHz for the treble control) relative to 1kHz. The circuit contains resistors which "tame" the response at the highest and lowest audio frequencies, so that the levels of boost and cut at these frequencies are little more than the figures just quoted for 100Hz and 10kHz. In practice this gives good results, and reduces the risk of

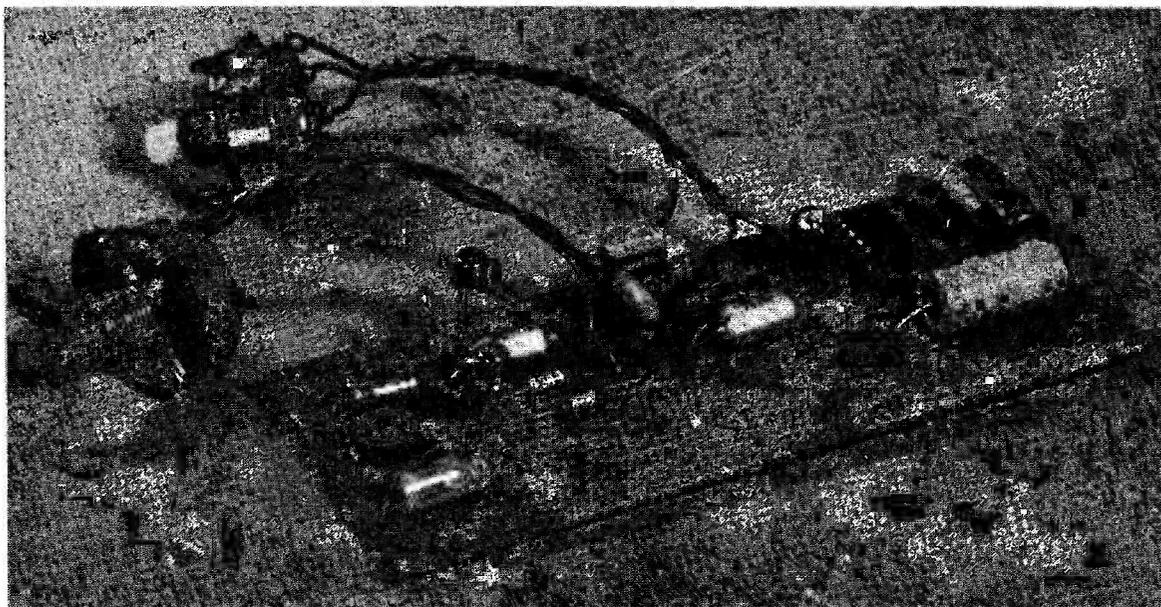

The prototype tone control circuit, assembled on its printed board

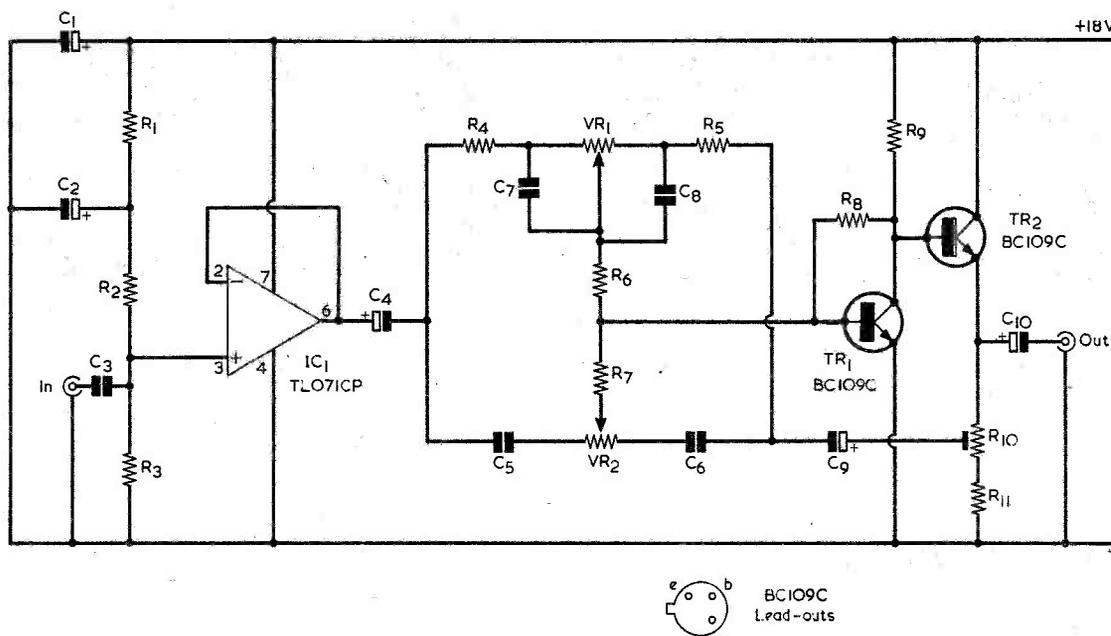


Fig. 1. The circuit of the active tone control module. VR1 provides base boost and cut, whilst VR2 gives treble boost and cut

the complete audio system becoming unstable due to excessive high or low frequency gain.

The circuit is designed for use with an 18 volt supply and has a current consumption of only about 5mA. However, it will work well with any supply voltage between 12 and 24 volts, the supply current varying from about 4 to 7mA over this range.

THE CIRCUIT

Fig. 1 shows the full tone control circuit. This is only for one channel, and two such circuits, with ganged potentiometers for the bass and treble controls, would of course be required for stereo operation.

The tone control circuitry proper should be fed from a low impedance source, and this is provided by the buffer amplifier IC1. This i.c. also allows the circuit to have its high input impedance. IC1 has 100% negative feedback from its output to its inverting input and therefore gives a voltage gain of unity. R2 and R3 bias the non-inverting input to about half the supply voltage, whilst R1 and C2 prevent hum and noise from the positive supply rail reaching this input. C3 is the input d.c. blocking capacitor.

IC1 is a low noise and distortion operational amplifier having a Jfet input stage, and it can be obtained from Watford Electronics, 33/35 Cardiff Road, Watford, Herts. However, similar devices, such as the TLO81CP, LF351 and even the standard 741C will all give a good performance in this design.


The tone control circuitry is based on the amplifier given by TR1 and TR2, and operates by simply increasing negative feedback at frequencies where cut is required, or by reducing feedback at frequencies where boost is needed. TR1 is a straightforward common emitter amplifier directly coupled to emitter follower TR2. TR2 merely serves to give a low impedance output.

TREBLE CONTROL

Detailed operation of the circuit is quite complex and it helps to look upon it in the light of an operational amplifier working in the inverting mode. If, with such an amplifier, a feedback resistor is connected from the output back to the inverting input, and a series resistor is connected between the signal source and the inverting input, the voltage gain of the amplifier is equal to the feedback resistance divided by the input series resistance. In Fig. 1 the output is at the slider of R10 and the inverting input is at the base of TR1. The voltage gain is then controlled by the feedback impedance given by the tone control components, and by the input series impedance which these components also give.

We can consider first the functioning of the treble section, which employs VR2, C5 and C6. The feedback impedance is through C6 and the right-hand section of VR2 track (i.e. right of the slider) and the input series impedance is given by C5 and the left-hand section of VR2 track. At low and middle frequencies, C5 and C6 have a reactance which is high in comparison with the track resistance of VR2. Therefore, adjustment of VR2 has little effect on the relative values of the feedback and input series impedances which, since C5 and C6 have equal values, remain virtually the same.

At higher frequencies the situation is very different because C5 and C6 start to have a reactance which is comparable with VR2 track resistance, and at the highest frequency this reactance is considerably lower than the track resistance of VR2. Thus, with the slider of VR2 towards the C6 end of its track the feedback impedance becomes much lower than the input series impedance, giving significantly reduced gain, or treble cut. When the slider of VR2 is moved to the C5 end of the track the feedback impedance is much larger than the series input impedance, producing

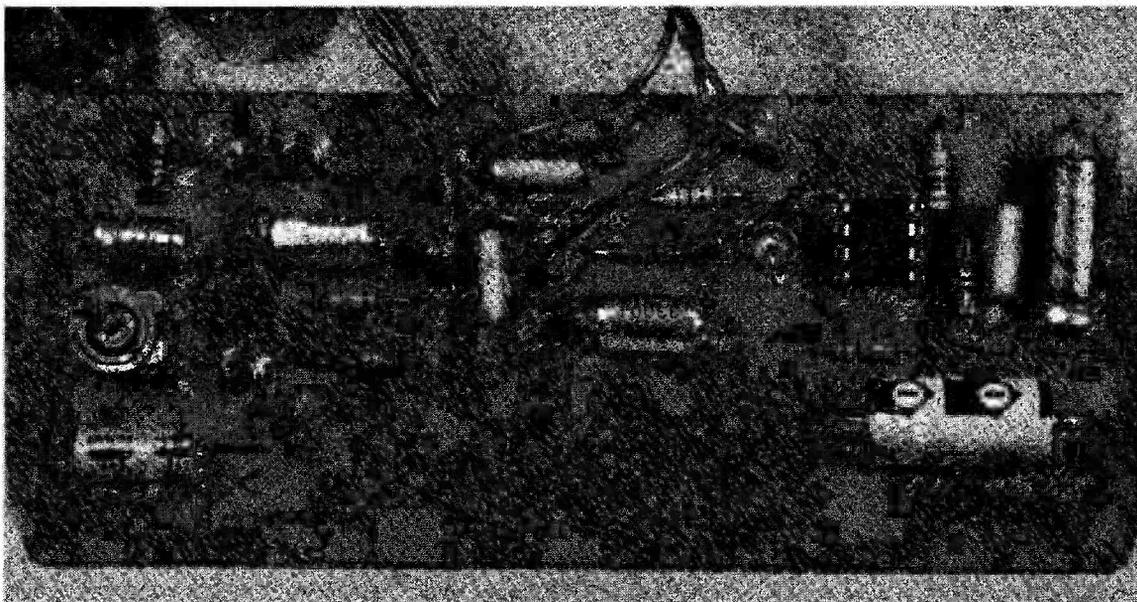

Looking down on the printed board. Input, output and supply leads were not fitted when these photographs were taken

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated)

R1	10k Ω
R2	1M Ω
R3	1M Ω
R4	10k Ω
R5	10k Ω
R6	12k Ω
R7	5.6k Ω
R8	3.9M Ω 10%
R9	10k Ω
R10	2.2k Ω pre-set potentiometer, 0.1 watt horizontal
R11	1k Ω
VR1	47k Ω potentiometer, linear
VR2	47k Ω potentiometer, linear

Capacitors

C1	100 μ F electrolytic, 25V. Wkg.
----	-------------------------------------

C2	100 μ F electrolytic, 25 V. Wkg.
C3	0.047 μ F polyester type C280
C4	4.7 μ F electrolytic, 25 V. Wkg.
C5	3,300pF polystyrene
C6	3,300pF polystyrene
C7	0.047 μ F polyester type C280
C8	0.047 μ F polyester type C280
C9	4.7 μ F electrolytic, 25 V. Wkg.
C10	10 μ F electrolytic, 25 V. Wkg.

Semiconductors

IC1	TL071CP
TR1	BC109C
TR2	BC109C

Miscellaneous

Printed circuit board
2 control knobs
Wire, solder, etc.

increased gain and treble boost. With VR2 slider at the centre of its track the two impedances are equal, a flat response is obtained and the high frequency amplifier gain becomes unity. In consequence, VR2 can provide a flat treble response, or any degree of treble cut or boost within its range which is required.

BASS CONTROL

The bass control, VR1, operates in a similar manner. At high and middle frequencies C7 and C8 have a low reactance and virtually short-circuit VR1. Since R5 and R4 have the same values, the feedback impedance at these frequencies is equal to the series input impedance, and adjustment of VR1 has no significant

effect. At bass frequencies, the reactances of C7 and C8 are high in comparison with the track resistance of VR1, and they have little effect on the circuit. In this low frequency range, moving VR1 slider towards R5 makes the feedback impedance lower than the series input impedance, causing voltage gain to be reduced and giving bass cut. When VR1 slider is at the R4 end of its track the feedback impedance is greater than the series input impedance, resulting in bass boost. Since the bass control circuitry, like the treble circuitry, is symmetrical, unity gain and a flat bass response is achieved when VR1 slider is at the centre of its track.

VR1 can thus provide a flat response or the desired level of bass cut or boost, with R4 and R5 limiting the

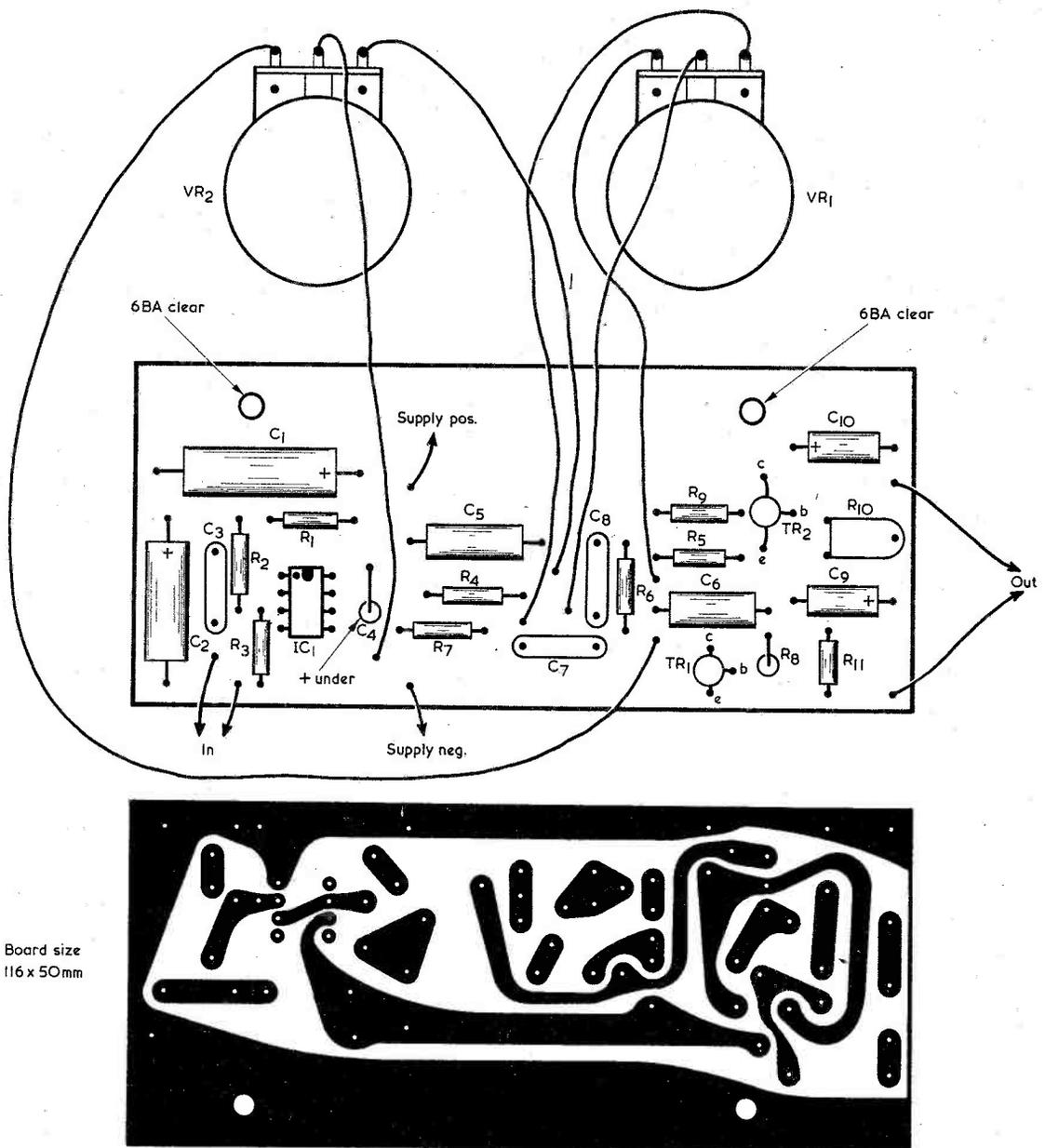


Fig. 2. The prototype circuit was assembled on a printed board which is reproduced here full size





maximum amounts of boost and cut respectively. R7 performs a similar limiting task in the treble control circuit and, together with R6, it also helps to minimise any interaction between the two controls.

When the slider of R10 is at the top of its track (and disregarding any cut or boost introduced by VR2 and VR1) the overall circuit has a nominal gain of unity. If required, the amplifier feedback can be reduced by adjusting the slider down the track, so that the circuit provides a small amount of voltage gain. The maximum gain available is a little over three times, or approximately 10dB. The gain could be boosted still further by reducing the value of R11 but, in the

interests of obtaining good noise, distortion and overload performances, this is not recommended.

CONSTRUCTION

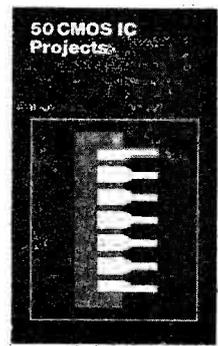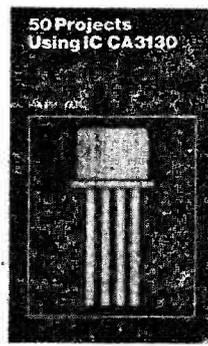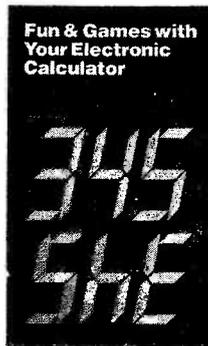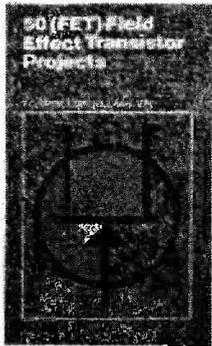Any normal method of construction can be employed for this circuit; the prototype was built using the printed circuit design shown in Fig. 2. The layout is not particularly critical if some other method of construction is used, but the components should obviously be kept away from hum fields in order to minimise pick-up. The input connection should be made by way of screened cable. ■



DIRECT READER SERVICE RADIO & ELECTRONICS BOOKS

18. 50 Projects Using IC CA3130	£1.25	40. Projects in Opto-Electronics	£1.25
19. 50 CMOS IC Projects	£1.25	41. Radio Circuits Using IC's	£1.35
20. A Practical Introduction to Digital IC's	95p	42. Mobile Discotheque Handbook	£1.35
22. Beginners Guide to Building Electronic Projects	£1.25	43. Electronic Projects for Beginners	£1.35
23. Essential Theory for the Electronics Hobbyist	£1.25	44. Popular Electronic Projects	£1.45
26. 52 Projects Using IC741	95p	45. IC LM3900 Projects	£1.35
28. Two Transistor Electronic Projects	85p	46. Electronic Music and Creative Tape Recording	£1.25
29. How to Build Your Own Metal and Treasure Locators	£1.00	47. Practical Electronic Calculations and Formulae	£2.25
30. Electronic Calculator Users Handbook	95p	48. Radio Stations Guide	£1.45
31. Practical Repair and Renovation of Colour TVs	£1.25	49. Electronic Security Devices	£1.45
32. Handbook of IC Audio Preamplifier and Power Amplifier Construction	£1.25	50. How to Build Your Own Solid State Oscilloscope	£1.50
33. 50 Circuits Using Germanium, Silicon and Zener Diodes	75p	51. 50 Circuits Using 7400 Series IC's	£1.45
34. 50 Projects Using Relays, SCR's and TRIACS	£1.25	52. Second Book of CMOS IC Projects	£1.50
35. Fun and Games with your Electronic Calculator	75p	53. Practical Construction of Pre-Amps, Tone Controls, Fitters & Attenuators	£1.45
36. 50 (FET) Field Effect Transistor Projects	£1.25	54. Beginners Guide to Digital Techniques	95p
37. 50 Simple L.E.D. Circuits	75p	55. 28 Tested Transistor Projects	£1.25
38. How to Make Walkie-Talkies	£1.25	56. Digital IC Equivalentents and Pin Connections	£2.50
39. IC 555 Projects	£1.75	57. Linear IC Equivalentents and Pin Connections	£2.75

POSTAGE: 20p PER BOOK. IF MORE THAN 3 BOOKS ORDERED: 10p PER BOOK

To: Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please send me within 21 days copy/copies

Book Nos:

.

I enclose Postal Order/Cheque for £

Name

Address

.

(Block Letters Please)

(We regret this offer is only available to readers in the U.K.)

SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge
£2.00
Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the **bona fides** of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. Replies to Box Numbers should be addressed to: Box No. —, **Radio and Electronics Constructor**, 57 Maida Vale, London, W9 1SN.

WIRELESS, VALVES, PRE-WAR ONWARD S.A.E. Modern bargains list 15p. Sole Electronics, (REC), 37 Stanley Street, Ormskirk, Lancs., L39 2DH.

BOOKS FOR SALE: *Experiments with Operational Amplifiers*, by George B. Clayton. £3.75. *Experimenting with Electronic Music* by Brown & Olsen. £1.20. *Electric Model Car Racing* by Laidlaw-Dickson. 60p. *Electronics Unravelled* by Kyle. £1. *Auto Electronics Simplified*, by Tab Books. £1.20. Box No. G394.

ANY SINGLE SERVICE SHEET £1 plus S.A.E. Thousands of different service/repair manuals/sheets in stock. Repair data your named TV £6 (with circuits £8). S.A.E. newsletter, price lists, quotations. (0698-883334). Ausrec, 76 Churches, Larkhall, Lanarkshire.

ALMAG INDOOR TV AERIAL. New design. All groups. £2.50 + 50p P. & P. Refundable. Murphy, 6 London Road, Dalkeith, Midlothian.

FOR SALE: A number of "D & S" three pin, fused, mains plugs and fuses. S.A.E. for details. Box No. G396.

PARCELS ASSORTED COMPONENTS: 100 £2.50. 200 £3.50. Superpack 400 £4.75. All post paid. C.W.O. only. Transway Services, P.O. Box 197, Ingatestone, Essex, CM4 OAR.

OSCILLOSCOPE, Calscope, (Scopex) Super 6, single beam 6MHz. Little used, now surplus. £100. Telephone: Tonbridge (0732) 832923 after 6 p.m.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

(Continued on page 509)



The larger Catalogue that means **FREE POSTAGE** IN U.K.

ADDITIONAL DISCOUNTS

GUARANTEED SATISFACTION

GOOD STOCKS GOOD DELIVERY

We pay postage.


Semi-Conductors • I.C.s • Opto-devices • Rs and Cs in great variety • Pots • Switches • Knobs • Accessories • Tools • Materials • Connectors

ELECTROVALUE

FREE FOR THE ASKING

ELECTROVALUE LTD., (RC4), St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB. Phone: 33603 (London 87) STD 0784. Telex 264475.

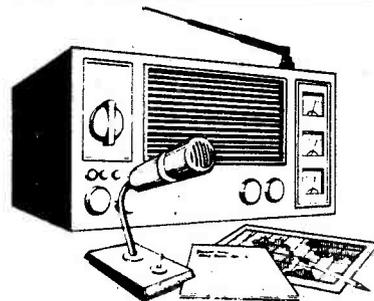NORTHERN BRANCH (Personal shoppers Only): 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.



BECOME A RADIO AMATEUR

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

No previous knowledge required.

Brochure without obligation to :-

British National Radio & Electronic School

4 Cleveland Road, Jersey, Channel Islands.

Name
Address

REC/4/815

BLOCK CAPS PLEASE

THE SPECTACULAR 1981 GREENWELD

Component Catalogue Bigger and better than ever!!!

- * 60p discount vouchers
 - * First Class reply paid envelope
 - * Free Bargain List
 - * Priority Order Form
 - * VAT inclusive prices
 - * Quantity prices for bulk buyers
- SEND 75p FOR YOUR COPY NOW!!**

CALC CHIPS 60p!!!

New full spec. supplied with data. Type MK50321 - full function inc. memory. Only 60p.

DISPLAYS

8 and 9 digit 7-segment bubble type for above chips - most have minor faults dud segment etc. Mixture of 2 or 3 different types with data. 5 for £1.00

NICADS

Ex-equip size C approx. £1 each; 10 for £8.00

1N4006 DIODES

Special purchase of 1A rects, Russian made. Packed in boxes of 300, £8.50 per box; 4 boxes £30.00; 10 boxes £75.00

DISC CERAMICS

0.22uF 12V 9mm dia. Ideal for decoupling. 100 for £2.75; 1000 £20.00
0.05uF 12V 15mm dia. 100 £1.50; 1000 £12.00

Pack of disc ceramics, assorted values and voltages - 200 for £1.00

TRANSFORMERS

Mains primary, 50V 20A sec. £20.00
Mains pri. 110V 15A sec. £30.00; 20A £40.00
FSRA60 relay. 2 x 10A contact, 1M, 1B. Coil is 250R, and rated 60V ac, but works on 12-24V DC. Solid Encapsulation with screw terminals makes it ideal for car use. £1.20

ALL PRICES INCLUDE VAT; JUST ADD 40p POST

GREENWELD

443G Millbrook Road Southampton SO1 0HX

SLIDER POT SCOOP!!!
Made by Piher, type PL40CP Silly prices for superb goods!!
PL40CP - 69 x 16 x 9mm, 40mm slide length. 220R, 2k2 or 10k lin only. Prices (any mix): 1-24 20p; 25-99 17p; 100+ 14p.

TTL LINEAR, OPTO

All new full spec - Fairchild/SGS:
TTL: 5400 5401 5402 5403 5404 5405
5410 5421 5430 5450 5451 5453 5460
- All 12p ea. 5470 5472 5474 5475
5476 5480 5486 5490 54107 54121
54122 - All 20p ea. 5482 54126 - 40p ea. Others (74S, H) on B/L 12 (SAE please)

LINEAR: 9665 or 9666, 7 x 50V Darlington in 16 DIL 60p; 75452 or 4 dual periph driver 70p; XK1444 7 CMOS P-channel buffers, 15V 16DIL 24p.

OPTO: Isolators, FCD831 60p; TIL115/118 60p; FPE100/106 Infra red LED £2.50; FND847 7 seg 0.8" CA £2.00; FND850 CC £2.00 (Data on request for linear & opto devices)

TRANSISTOR PACK K516

Take advantage of this unbelievable offer!! Small signal NPN/PNP transistors in plastic package at an incredibly low, low price!! Almost all are marked with type number - almost all are full spec devices, some have bent leads. Over 30 different types have been found by us, including BC184/212/238/307/328; BF196/7; ZTX107/8/9/342/450/550 etc. Only available as a mixed pack at £3/100; £7/250; £25/1000.

REGULATED PSU PANEL

Exclusive Greenweld design, fully variable 0-28V & 20mA-2A. Board contains all components except pots and transformer. Only £7.75. Suitable transformer and pots £6.00. Send SAE for fuller details.

BUY THIS BEST SELLER

T.V. FAULT FINDING

MONOCHROME
405/625 LINES



REVISED & ENLARGED

Edited by J. R. Davies

132 pages

PRICE £1.20

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

Price £1.20 from your bookseller.

or post this Coupon together with remittance for £1.50 (to include postage) to

DATA PUBLICATIONS LTD.
57 Maida Vale, London, W9 1SN

Please send me the 5th revised edition of TV Fault Finding. Data Book No. 5

I enclose cheque/crossed postal order for . . .

NAME

ADDRESS

BLOCK LETTERS PLEASE

APRIL

LATEST PROJECT KITS

Double Output Test Oscillator Jan 81	£5.95
Car Voltage Monitor Jan 81	£2.75
Fuzz Box Jan 81	£7.15
Reverberation Unit Feb 81	£16.85
Single IC Signal Tracer Feb 81	£3.80
"Owizzee" Feb 81 (excludes p.c.b.)	£11.30

Complete list of kits available on receipt of an S.A.E.

A selection from our new catalogue (45p post paid)

P.C.B. transfers (13 different sheets)	300p
5W amplifier module	530p
Small insulated crocodile clip	9p
Mains square lens neons, red or green	35p
Telephone pick up coil	75p
0.125" leds, red 12p green/yellow 21p. 0.2" 13p & 22p	
Small 2½" screwdrivers 18p 4" screwdrivers 22p	
Set of 10 test leads with crocodile clips	125p
2.5" x 1" 0.1" Veroboard	16p
+ transistors, i.c.s. diodes, resistors, books, panel meters, nuts & bolts, component packs etc etc.	

T & J ELECTRONIC COMPONENTS

98 Burrow Road Chigwell Essex IG7 4HB

Mail order only. Prices include VAT. No minimum order. Postage: components 40p, kits 65p. Orders are despatched same day as received. Catalogue 45p post paid.

SMALL ADVERTISEMENTS

(Continued from page 507)

BURGLAR ALARM EQUIPMENT. Top quality brand new free catalogue and price list. Sigma Security Systems, 13 St. John's Street, Oulton, Leeds, Yorks. LS26 8 JT.

JOIN THE INTERNATIONAL S.W. LEAGUE.

Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazine etc., £9-00 per annum U.K. Overseas rates on request, Secretary Grove Road, Lydney, Glos., GL15 5JE.


TELEPHONE ANSWERING MACHINE. Build your own for under £10 plus any cassette recorder. Send £3 for circuit and plans. S. D. Cross, 24 Thorney Road, Streetly, Sutton-Coldfield, West Midlands.

BOOK CLEARANCE. Bound volumes *Radio & Electronics Constructor* Nos. 27, 28 and 29, £3.00 each. *Cost Effective Projects Around the Home* by John Watson, £1.50. *Talk-Back TV: Two-Way Cable Television*, by Richard Veith, £1.00. *Solid State Short Wave Receivers for Beginners*, by R. A. Penfold, 60p. *50 Simple LED Circuits*, by R. N. Soar, 50p. All prices include postage. Box No. G399.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from: Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

(Continued on page 510)

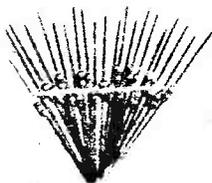METALFILM RESISTORS 1% Tolerance, 1/4 Watt



ONLY 3P EACH

Minimum order £10
Minimum 5 pcs per value
89 Values (E24)

100R	1k	10k	100k
110R	1k1	11k	110k
120R	1k2	12k	120k
130R	1k3	13k	130k
150R	1k5	15k	150k
160R	1k6	16k	160k
180R	1k8	18k	180k
200R	2k	20k	200k
220R	2k2	22k	220k
240R	2k4	24k	240k
270R	2k7	27k	270k
300R	3k	30k	-
330R	3k3	33k	330k
360R	3k6	36k	-
390R	3k9	39k	-
430R	4k3	43k	-
470R	4k7	47k	470k
510R	5k1	51k	-
560R	5k6	56k	560k
620R	6k2	62k	-
680R	6k8	68k	680k
750R	7k5	75k	-
820R	8k2	82k	820k
910R	9k1	91k	910k

Special Offer: 5 PCS of EACH (445 RESISTORS) ONLY £11.50.
High Quality, High Stability, High Strength.
VAT inclusive. Add £1.00 p&p all areas.

ORION SCIENTIFIC PRODUCTS LTD.
10 Wardour St., London W1.



Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN'S ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO DEPT REC
35/39 CHURCH STREET, WILMSLOW
CHESHIRE SK9 1AS.

Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits, etc.,

Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete speakers

A CAREER IN RADIO

Start training **today** and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs - they can do the same for **you**.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
Radio TV Electronics Technicians'
Electrical Installations Technicians'
Electrical Installations Work
Radio Amateurs'

MPT Radio Communications Cert

EXAMINATION STUDENTS -

GUARANTEED COACHING

UNTIL SUCCESSFUL

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:

Electronic Engineering & Maintenance
Computer Engineering/Programming
Radio, TV & Audio Engineering
& Servicing
Electrical Engineering Installations
& Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name Age

Address

..... Occupation

ICS Accredited by CACC Member of ABCC

To International Correspondence Schools
Dept 278F, Intertext House, LONDON
SW8 4UJ or phone 01-622 8911 (anytime)

RECHARGEABLE BATTERIES

**TRADE ENQUIRIES
WELCOME**

FULL RANGE AVAILABLE SEND SAE
FOR LISTS. £1.45 for Booklet Nickel
Cadmium Power" plus Catalogue.
Write or call:

*NEW SEALED
LEAD RANGE AVAILABLE*

SANDWELL PLANT LTD

2 Union Drive, Boldmere,
Sutton Coldfield, West Midlands,
021-354 9764.

REVOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536



**PRICED
FROM
£148.75**

Stereomaster

This microscope's working
distance and field of view is
relatively large; this feature
ensures convenience to the
operator who works with both
hands while assembling
precision mechanisms.

**IDEAL FOR
PRINTED CIRCUITS
AND OTHER
DELICATE WORK.**

**COMES
COMPLETE WITH**

built-in x 10 Mag.
Objectives x 20
Objectives x 35
At extra cost

We stock one of the largest selections of second
hand microscopes and optical magnifiers, on
and off stands. Please phone for details.

SMALL ADVERTISEMENTS

(Continued from page 509)

CONNECTING WIRE, single strand, PVC
covered. Ideal for electronics experiments and
Proto-Board work. 10 colours. 50 yds. £1.50.
100 yds. £2.50. J.D. Electronics, 69 Well Heads,
Thornton. Bradford. W. Yorks.

LEARN ELECTRONICS FAST. New, unique,
brilliantly simple Tutronik system. Selected by
BBC TV. No-soldering, 30-kwikbuild electronics
projects. Learn fast to identify components,
read circuit diagrams, break the colour code and
connect circuits that really work. Kit complete
with simple-to-follow instructions, circuit plans,
components and Tutronic connection system in
compact presentation wallet. Only £12.95 plus
75p p. & p. UK (£2.75 p. & p. elsewhere).
Available only from Dept. RE, Technocentre
Ltd., 140 Norton Road, Stockton-on-Tees,
TS20 2BG.

FOR SALE: Oscilloscopes, Tektronix 545 with
CA plug-in, double switched beam 15MHz.
£110. Solartron CD1017 (CT436) compact
double beam, 6MHz. £80. Signal generators:
RF/AM 100kHz-25MHz £20. Audio, Advance
20Hz - 50kHz £10. Avo electronic multimeter
(CT38) £20. Avo 7 £20. 500V megger £15.
Large auto transformer 240/115V £10. All
working order with handbooks. S.A.E.
enquiries please. Carriage extra. Box No.
(Middlx.) G400.

WANTED: FAX equipment, manuals, service
sheets, etc. G2UK, 21 Romany Road, Oulton
Broad, Lowestoft, Suffolk. NR32 3PJ.

FOR SALE: Photographic enlarging equipment:
Vivitar enlarger. Model E.36 with 50mm f. 3.5
and 75mm f.3.5 lenses. Kodak safety light.
Kodak contrast filter set. 11 in. x 14 in. printing
frame with copying facilities. Measuring flask.
Three trays, three tweezers. Three plastic bot-
tles. Clips. Printing paper. Antistatic brush for
cleaning negatives. Kodak Photoguide Booklet.
Man's protective apron. £75 o.n.o. Pair of
Goodman's speakers 8 ohms, 15 watts, £50
o.n.o. R. L. Gee, 9 Glanmead, Shenfield,
Essex.

2 WATT General Purpose I.C. Amplifier Module
with volume and tone controls. Needs 9V-18V
p.s.u. or battery. £4.00. R.H. Electronics. 119
Fraser Road, Sheffield, S8 0JH.

**THE RADIO AMATEUR INVALID & BLIND
CLUB** is a well established Society providing
facilities for the physically handicapped to enjoy
the hobby of Amateur Radio. Please become a
supporter of this worthy cause. Details from the
Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch
Court, Adelaide Road, Surbiton, Surrey, KT6
4TE.

(Continued on page 511)

SMALL ADVERTISEMENTS

(Continued from page 510)

100 1N4148 £1. 150 Resistors £1. 100 Capacitors £1. P. & P. 25p. S.A.E. Lists. Dept. R, D. B. Products, P.O. Box 8, York, YO1 1FT.

FOR SALE: Damaged repairable cassette recorder and 10 cassettes. £15.00. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

INTERESTED IN RTTY? You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk, NR32 3PJ.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: - The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NR8 85S.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

SPONSORS required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary; 195 White Woman Lane, Old Catton, Norwich, Norfolk.


SITUATION VACANT

WANTED: Representatives to sell Electronic Components to shops and industries on good commission basis. Please send full details of experience to: Summit Electronics, 96 Peel Road, Wembley, Middlesex. Telephone: 01-904-6792.

PURE GOLD!

Top-quality, low-profile, gold-plated contacts, **IC SOCKETS**

8 pin	8p
14 pin	14p
16 pin	16p
18 pin	18p
20 pin	20p
22 pin	22p
24 pin	24p
28 pin	28p
40 pin	40p

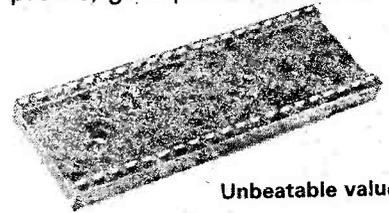

Unbeatable value!

Minimum order £10. Add £1 P & P

500+ and 1 type lens 5%
1000+ any mix lens 10%

Special Offer: 10 x 8 pin, 20 x 14 pin, 20 x 16 pin, 5 x all others £11.50

ORION Orion Scientific Products Ltd.,
10 Wardour St., London, W.1

BUILD YOUR OWN

P.A., GROUP & DISCO SPEAKERS by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman

(full constructional details for versions using 15", 12" and 10" (drive units). £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING

5 Swan Street, Wilmslow, Cheshire

PRINTED CIRCUIT BOARDS FOR "RADIO & ELECTRONICS CONSTRUCTOR" PROJECTS.

OCT 20dB amp. Part 1 **68p** plus 25p P&P

NOV. 20dB amp. Part 2 **62p** plus 25p P&P

NOV. Basic Med. Wave radio **69p** plus 25p P&P

DEC. Volume Expander **£2.25** plus 25p P&P

All boards ready for use, roller tinned and drilled, glassfibre.

Trade enquiries welcome. Highly competitive prices.

Write now for quote to:

BRB PRINTED CIRCUITS (REC)

109, Potter Street, Worksop,
Notts. S80 2HL.

VARI WIPE

WIPER DELAY CONTROL

The Vari Wipe provides intermittent operation of the windscreen wipers with adjustable control to delay each wipe between 3 and 60 seconds. Set the control to suit the conditions to clear light drizzle, fog, snow, sleet or spray. Easily fitted to British, Continental & Japanese cars with 12 volt self park wipers. Complete kit contains all components, including timer chip, PCB, case, mounting panel, wire, etc., with full instructions.

VARI WIPE KIT £6.95 inc. P & P
ASSEMBLED £9.25 inc. P & P

or send large s.a.e. for details

Spimin

DEVELOPMENTS

Dept R1

Card Holders Phone
0253 27244

FREEPOST Thornton Cleveleys, Blackpool FY5 2BR

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 60p each, p&p 20p
Issue(s) required

Annual Subscription

Price £9.50 inland, £10.50 overseas (including Eire)
post free, commence with issue

Bound Volumes:

Vol. 27.	August 1973 to July 1974	Price £3.00, post & pkg £1.50
Vol. 28.	August 1974 to July 1975	Price £3.20, post & pkg £1.50
Vol. 29.	August 1975 to July 1976	Price £3.50, post & pkg £1.50
Vol. 30.	August 1976 to July 1977	Price £3.70, post & pkg £1.50
Vol. 31.	August 1977 to August 1978	Price £5.20, post & pkg £1.50
Vol. 32.	September 1978 to August 1979	Price £5.50, post & pkg £1.50
Vol. 33	September 1979 to August 1980 (Available Mid-March)	Price £6.20 post & pkg. £1.50

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only Price £2.25, post & pkg 60p
With no title on spine, maroon Price £2.25, post & pkg 60p
With no title on spine, green Price £2.25, post & pkg 60p
Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages Price £1.20, P.&P. 30p
DB6 Radio Amateur Operator's Handbook,
New edition in course of preparation
DB17 Understanding Television, 504 pages Price £3.95, P. & P. £1.20
DB19 Simple Short Wave Receivers Price 80p, P. & P. 30p
140 pages

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording - White - 6 sheets Price £1.50, P. & P. 13p
Set 4: Wording - Black - 6 sheets Price £1.50, P. & P. 13p
Set 5: Dials - 6 sheets Price £1.50, P. & P. 13p
Prices include V.A.T.

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

*Overseas customers please pay by International Money Order.
All publications are obtainable through your local bookseller*

Data Publications Ltd., 57 Maida Vale, London W9 1SN


PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS

LINEAR AMPLIFICATION


Most integrated circuits are categorised as linear or digital devices. The operational amplifier in (a) is classed as linear whilst the NOR gate of (b) is classed as digital. All the i.c.'s in the t.t.l. and CMOS logic families are described as digital.

In practice, digital devices exhibit linear amplification whilst some linear devices can be employed in simple digital applications. The transistor in (c) has its base bias resistor returned to an input voltage which is a fraction, say one-quarter, of the supply voltage. Resistor values are such that the transistor collector has a voltage half-way between the supply rails. In this state the transistor is capable of linear amplification: an increase in input voltage causes a fall in collector voltage and a decrease in input voltage causes a rise in collector voltage. In (d) the base bias resistor is returned to the positive rail and the transistor is turned fully on, producing a collector voltage which is virtually zero. The base resistor connects to the negative rail in (e), whereupon the transistor is turned off and the collector voltage is the same as that of the positive rail.


In (f) the transistor and base resistor follow a CMOS NAND gate. The transistor acts as a digital inverter, producing a low collector voltage when the gate output is high and a high collector voltage when the gate output is low. Since the output of the NAND gate does not change states instantaneously, there is a brief moment during a change of state when the transistor exhibits linear amplification. The same applies to all digital devices which are driven by other digital devices.

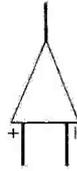


(a)

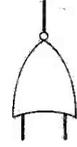


(b)

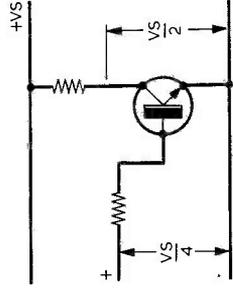


(c)

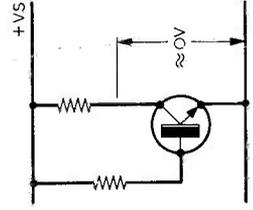

(d)

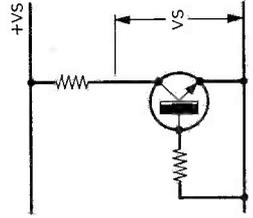

(e)

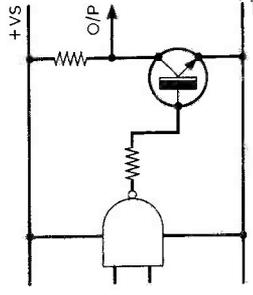

(f)

