



## **DIODE AND TRANSISTOR AMPLIFIER RECEIVER**

- Place the schematic diagram over the peg board.
- Put the component assemblies in the positions indicated.
- Complete the circuit by joining up wires as indicated.











