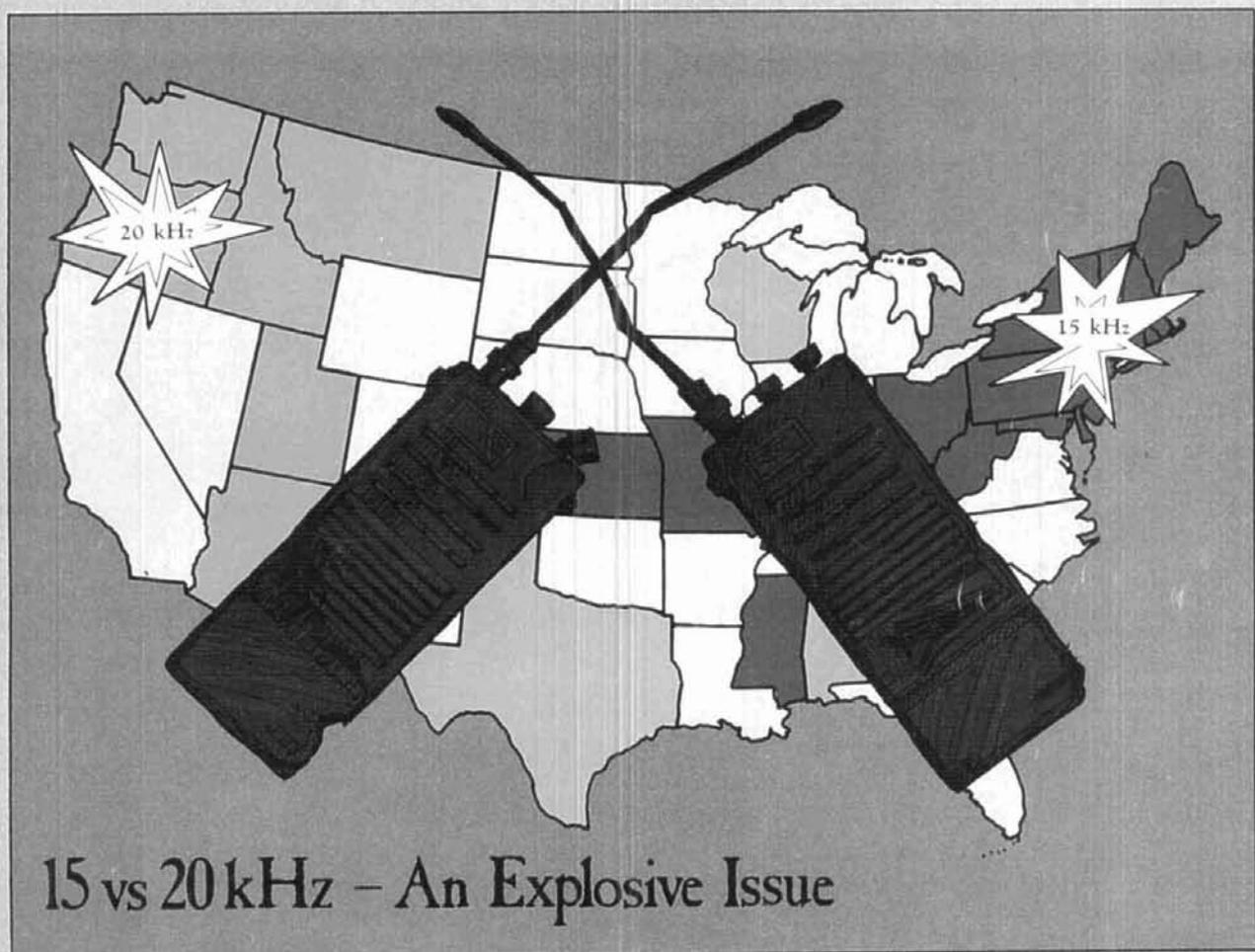


# ham radio magazine



**hr**  
focus  
on  
communications  
technology

*calculate the input impedance of tapered verticals • design toroidal tank circuits • stop blowing finals in the GLA-1000 • build a pulsed NiCad battery charger • run full power with a 3CX1200A7 amplifier • plus W1JR, W6SAI, W6MGI, and K0RYW*

ICOM VHF Transceiver

# IC-271H



## The Versatile 100 Watt 2 Meter Base System

For the ultimate in 2-meter communications, ICOM presents the IC-271H transceiver with a high dynamic range receiver and a 100 watt transmitter...And all the advanced functions of the latest CPU controlled radios.



IC-PS30  
Power Supply

### Exceptional Standard

#### Features:

- 143.800 - 148.199MHz, expandable for MARS operation
- 32 full-function Memories with lithium battery backup
- 100 Watts, fully adjustable on all modes
- Variable Tuning Steps, FM 5KHz and 1KHz; SSB 10Hz, 50Hz and 1KHz

- 32 built-in Subaudible Tones
- High Visibility Display
- S-Meter and Center Meter
- Scanning Systems Memories, Modes and Programmable Band
- IC-HM12 Microphone with Up/Down Scan
- 11¼"W x 4¾"H x 12½"D

### Optional Features:

AG-25 switchable preamp, UT-15S CTCSS encoder/decoder (encoder is standard), IC-EX310 voice synthesizer, IC-SM8 two-cable desk mic and IC-SM6 desk mic. PLUS a variety of power supplies... IC-PS30 system power supply, IC-PS15 external or IC-PS35 internal power supplies.

The IC-271A. The 25 watt IC-271A has the same outstanding features as the IC-271H, including an internal power supply, IC-PS25.



IC-271H  
Shown with internal  
power supply, IC-PS35

See the IC-271A(H) and other fine ICOM equipment. your local ICOM dealer today.



# ICOM

First in Communication

ICOM America, Inc., 2380-116th Ave NE, Bellevue, WA 98004 / 3331 Towerwood Drive, Suite 307, Dallas, TX 75234

All stated specifications are approximate and subject to change without notice or obligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions. 271H1084

## What To Look For In A Phone Patch

The best way to decide what patch is right for you is to first decide what a patch should do. A patch should:

Give complete control to the mobile, allowing full break in operation.

Not interfere with the normal operation of your base station. It should not require you to connect and disconnect cables (or flip switches!) every time you wish to use your radio as a normal base station.

Not depend on volume or squelch settings of your radio. It should work the same regardless of what you do with these controls.

You should be able to hear your base station speaker with the patch installed. Remember, you have a base station because there are mobiles. **ONE OF THEM MIGHT NEED HELP.**

The patch should have standard features at no extra cost. These should include programmable toll restrict (dip switches), tone or rotary dialing, programmable patch and activity timers, and front panel indicators of channel and patch status.

**ONLY SMART PATCH HAS ALL OF THE ABOVE.**

## Now Mobile Operators Can Enjoy An Affordable Personal Phone Patch...

Without an expensive repeater.

Using any FM transceiver as a base station.

The secret is a SIMPLEX autopatch, The **SMART PATCH.**


## SMART PATCH is Easy To Install

To install **SMART PATCH**, connect the multicolored computer style ribbon cable to mic audio, receiver discriminator, PTT, and power. A modular phone cord is provided for connection to your phone system. Sound simple? ... IT IS!

# With SMART PATCH You are in CONTROL



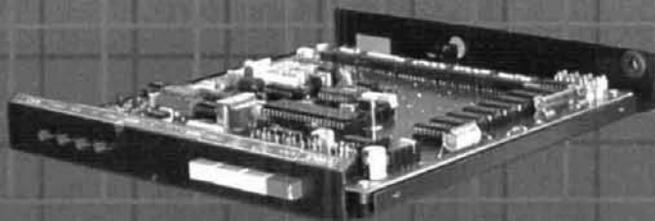
## With CES 510SA Simplex Autopatch, there's no waiting for VOX circuits to drop. Simply key your transmitter to take control.



**SMART PATCH** is all you need to turn your base station into a personal autopatch. **SMART PATCH** uses the only operating system that gives the mobile complete control. Full break-in capability allows the mobile user to actually interrupt the telephone party. **SMART PATCH** does not interfere with the normal use of your base station. **SMART PATCH** works well with any FM transceiver and provides switch selectable tone or rotary dialing, toll restrict, programmable control codes, CW ID and much more.
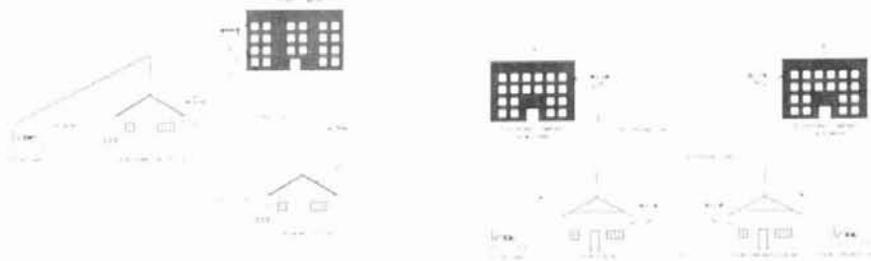
## To Take CONTROL with Smart Patch — Call 800-327-9956 Ext. 101 today.



**Communications Electronics Specialties, Inc.**  
P.O. Box 2930, Winter Park, Florida 32790  
Telephone: (305) 645-0474 **Or call toll-free (800)327-9956**

## How To Use SMART PATCH

Placing a call is simple. Send your access code from your mobile (example: \*73). This brings up the Patch and you will hear dial tone transmitted from your base station. Since **SMART PATCH** is checking about once per second to see if you want to dial, all you have to do is key your transmitter, then dial the phone number. You will now hear the phone ring and someone answer. Since the enhanced control system of **SMART PATCH** is constantly checking to see if you wish to talk, you need to simply key your transmitter and then talk. That's right, you simply key your transmitter to interrupt the phone line. The base station automatically stops transmitting after you key your mic. **SMART PATCH** does not require any special tone equipment to control your base station. It samples very high frequency noise present at your receiver's discriminator to determine if a mobile is present. No words or syllables are ever lost.

## SMART PATCH Is All You Need To Automatically Patch Your Base Station To Your Phone Line.

Use **SMART PATCH** for:

- Mobile (or remote base) to phone line via Simplex base. (see fig. 1.)
- Mobile to Mobile via interconnected base stations for extended range. (see fig. 2.)
- Telephone line to mobile (or remote base).
- **SMART PATCH** uses **SIMPLEX BASE STATION EQUIPMENT**. Use your ordinary base station. **SMART PATCH** does this without interfering with the normal use of your radio.

## WARRANTY?

YES, 180 days of warranty protection. You simply can't go wrong. An FCC type accepted coupler is available for **SMART PATCH**.

# KENWOOD

...pacesetter in Amateur radio

## “Digital DX-terity!”



### TS-430S

**Digital DX-terity—that outstanding attribute built into every Kenwood TS-430S lets you QSY from band to band, frequency to frequency and mode to mode with the speed and ease that will help you earn that dominant DX position from the shack or from the mobile!**



- Covers all Amateur bands 160 through 10 meters, as well as the new 30, 17, and 12 meter WARC bands. High dynamic range, general coverage receiver tunes from 150 kHz to 30 MHz. Easily modified for HF MARS operation.
- Superb interference reduction. Eliminate QRM with the IF shift and tuneable notch filter. A noise blanker suppresses ignition noise. Squelch, RF attenuator, and RIT are also provided. Optional IF filters may be added for optimum interference reduction.

- **Reliable, all solid state design.** Solid state design permits input power of 250 watts PEP on SSB, 200 watts DC on CW, 120 watts on FM (optional), or 60 watts on AM. Final amplifier protection circuits and a cooling fan are built-in.
- **Memory channels.** Eight memory channels store frequency, mode and band data. Channel 8 may be programmed for split-frequency operation. A front panel switch allows each memory channel to operate as an independent VFO or as a fixed frequency. A lithium battery backs up stored information.
- **Programmable, multi-function scan.**
- **Speech processor built-in.**
- **Dual digital VFOs.**
- **VOX circuit, plus semi break-in with sidetone.**

#### Optional accessories:

- PS-430 compact AC power supply
- SP-430 external speaker
- MB-430 mobile mounting bracket
- AT-130 compact antenna tuner covers 80-10 meters, incl. WARC bands
- AT-250 automatic antenna tuner covers 160-10 meters, incl. WARC bands
- AT-230 base station antenna tuner
- FM-430 FM unit
- YK-88C (500 Hz) or YK-88CN (270 Hz) CW filters
- YK-88SN (1.8 kHz) narrow SSB filter
- YK-88A (6 kHz) AM filter
- MC-42S UP/DOWN hand mic.
- MC-60A deluxe desk mic., with UP/DOWN switch
- SW-2000 SWR/power meter
- SW-100A SWR/power/volt meter
- PC-1A phone patch
- HS-4, HS-5, HS-6, HS-7 headphones



## KENWOOD

TRIO-KENWOOD COMMUNICATIONS  
1111 West Walnut Street  
Compton, California 90220

Complete service manuals are available for all Trio-Kenwood transceivers and most accessories. Specifications and prices are subject to change without notice or obligation.

# ham radio

magazine

**AUGUST 1985**

**volume 18, number 8**

**T. H. Tenney, Jr., W1NLB**  
publisher

**Rich Rosen, K2RR**  
editor-in-chief  
and associate publisher

**Dorothy Rosa, KA1LBO**  
assistant editor

Joseph J. Schroeder, W9JUV  
Alfred Wilson, W6NIF  
associate editors  
Susan Shorrock  
editorial production

#### editorial review board

Peter Bertini, K1ZJH  
Forrest Gehrke, K2BT  
Michael Gruchalla, P. E.  
Bob Lewis, W2EBS  
Mason Logan, K4MT  
Ed Wetherhold, W3NQN

#### publishing staff

**J. Craig Clark, Jr., N1ACH**  
assistant publisher

**Rally Dennis, KA1JWF**  
director of advertising sales

**Dorothy Sargent, KA1ZK**  
advertising production manager

**Susan Shorrock**  
circulation manager

**Therese Bourgauf**  
circulation

cover:  
**Anne Fleming**  
Map details represent latest information  
available at presstime.

ham radio magazine is published monthly by  
Communications Technology, Inc.  
Greenville, New Hampshire 03048-0498  
Telephone: 603-878-1441

#### subscription rates

United States:  
one year, \$19.95; two years, \$32.95; three years, \$44.95  
Canada and other countries (via surface mail):  
one year, \$22.95; two years, \$41.00; three years, \$58.00  
Europe, Japan, Africa (via Air Forwarding Service): one year, \$28.00  
All subscription orders payable in U.S. funds, via international  
postal money order or check drawn on U.S. bank

international subscription agents: page 122

Microfilm copies are available from  
University Microfilms, International  
Ann Arbor, Michigan 48106  
Order publication number 3076

Cassette tapes of selected articles from ham radio  
are available to the blind and physically handicapped  
from Recorded Periodicals,  
919 Walnut Street, Philadelphia, Pennsylvania 19107

Copyright 1985 by Communications Technology, Inc.  
Title registered at U.S. Patent Office

Second-class postage paid  
at Greenville, New Hampshire 03048-0498  
and at additional mailing offices  
ISSN 0148-5989

Send change of address to ham radio  
Greenville, New Hampshire 03048-0498



## contents

**12 FM repeater separation**  
— 20 kHz Yes, 15 kHz No  
Chris Kelly, WD5IBS

**24 calculating the input impedance**  
**of a tapered vertical**  
Walter J. Schulz, K3OQF

**29 design a toroidal tank circuit**  
**for your vacuum tube amplifier**  
Robert E. Bloom, W6YUY

**39 VHF/UHF world:**  
**medium power amplifiers**  
Joe Reisert, W1JR

**59 stop blowing finals**  
**in the GLA-1000 amplifier**  
A.J. Nailer, G4CFY, and G.J. Morgan, G3ROG

**67 a pulsed, constant current**  
**NiCad battery charger**  
Alan Lefkow, K2MWU


**75 3CX1200A7 10 to 80-meter amplifier**  
Jerry Pittenger, K8RA

**90 ham radio techniques:**  
**big signals from the north**  
Bill Orr, W6SAI

**124 the Guerri report**  
Ernie Guerri, W6MGI

**126 advertisers index**  
**and reader service**  
**8 comments**  
**100 DX forecaster**  
**122 flea market**

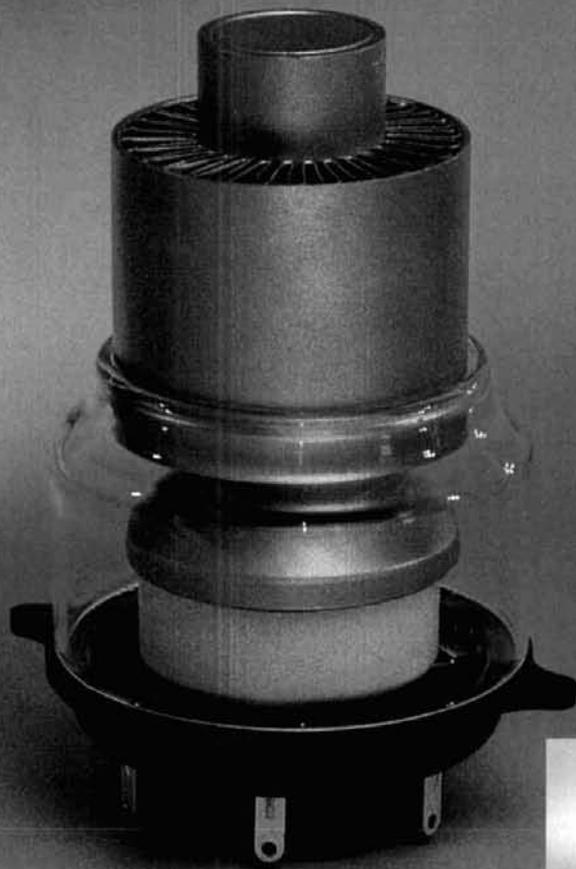**120 ham mart**  
**86 ham note**  
**110 new products**  
**6 presstop**  
**27 short circuit**



## When the FCC changed the rules, EIMAC was prepared for continuing HAM operations.

The FCC changed the allowable output power for linear amplifiers in amateur radio service. Hams can now run at 1500 watts PEP into an antenna. EIMAC was right there to meet requirements with its 3CX1200A7 tube.

### Low-cost replacement for small spaces.

RF cabinets of many linear amplifiers currently use the EIMAC 3-500-Z tubes. The new 3CX1200A7 for design takes size into consideration and, by design, is recommended as a single, low-cost replacement for a pair of EIMAC 3-500-Z tubes for new amplifier designs.

### General Specifications

The EIMAC 3CX1200A7 is a high- $\mu$ , compact, forced air cooled triode for zero-bias class AB2 amplifiers.

- 2.9" dia. x 6.0" long
- Plate dissipation: 1200 watts
- Glass chimney SK-436 available
- Standard EIMAC SK-410 socket available

More information is available on the new EIMAC 3CX1200A7 tube from Varian EIMAC, or any Electron Device Group worldwide sales organization.


Varian EIMAC  
1678 S. Pioneer Road  
Salt Lake City, Utah 84104  
Telephone: 801 • 972-5000

Varian AG  
Steinhauserstrasse  
CH-6300 Zug, Switzerland  
Telephone: 042 • 23 25 75






R.F. Power Monitoring

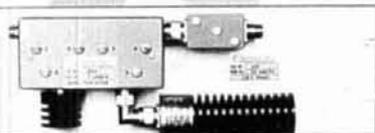

IM Suppression Panels

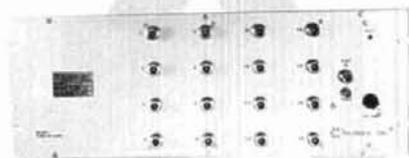

Receiver Multicoupling

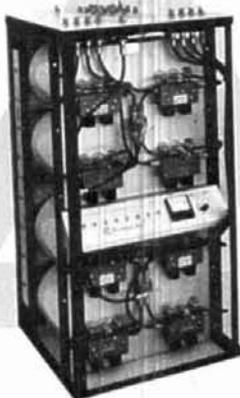
# The Problem Solvers



Duplexers & Preselectors



Bandpass, Pass-Reject  
and Notch Cavity Filters



Transmitter Combining  
150 - 900 MHz

**\*COMPLETE SYSTEM ENGINEERING ASSISTANCE\***



# TELEWAVE, INC.

1155 TERRA BELLA, MOUNTAIN VIEW, CA 94043  
(415) 968-4400 • TWX 910-379-5055

STILL ANOTHER THREAT AGAINST 220 MHZ HAS BEEN MOUNTED by an oil exploration-related firm in Illinois. LAOAD Radio and Microwave Communications Consultants petitioned the FCC to allocate 216-220 MHz for use as 1033 ASCB data and voice channels, AND provide a 350 kHz segment of 220-222 MHz to be shared with Amateur Radio. Under terms of the proposal, LAOAD would advise the ARRL of pending operations, and the League would then alert Amateurs.

Little, If Any, Interference To Amateurs Would Result, the petitioner (W9GT, whose Norwegian call LAOAD inspired his company name) claims, as operations would be very short-lived and typically well removed from populated areas. However, 220 MHz users and others are very concerned that any such incursion could set a dangerous precedent for the future.

The Original Comment Period On RM-4983 Had Closed by presstime, but there has been considerable pressure to reopen it. Though the recent upsurge in interest in providing Novices with 220 MHz privileges (see below) certainly tends to diminish or at least postpone threats such as this one, it is still quite serious and should be challenged.

ARRL'S PETITION TO EXPAND NOVICE PRIVILEGES HAS RECEIVED its FCC Rule Making number, RM-5038, along with several other related petitions. In brief, the League proposal would give Novices limited 10-meter SSB and data privileges plus full privileges (with reduced power) on 220 and 1246-1260—see July Presstop for specific details. Somewhat similar petitions filed by KC50Q include giving Techs and Novices ASCII (RM-5022) and phone (RM-5032) on part of 10 meters, some 30 meter privileges (RM-5024), and 220 MHz phone (RM-5025). The Comment period closed for KC50Q's petitions July 11; a date hadn't been set for ARRL's at presstime, but its cutoff date should fall sometime in late July.

BROADCAST STATIONS MAY RETRANSMIT AMATEUR TRANSMISSIONS or use what they hear on the Amateur bands on the air, but any direct involvement between Amateurs and a broadcast station is expressly forbidden. In its June 7 Report and Order on BC Docket 79-47, the Commission agreed that the content of an Amateur transmission is not protected against reuse by others, but that to have, for example, an Amateur station at a broadcast studio to solicit traffic information during rush hours would be against the rules.

AMATEURS MAY BE ALMOST TWICE AS PRONE TO LEUKEMIA as the general population, a study reported June 23 by the New York Times News Service suggests. Underscoring ham radio Editor K2RR's July editorial, Washington state epidemiologist Dr. Samuel Milham, Jr. found the death rate from various forms of leukemia for 1691 California and Washington Amateurs who died between 1971 and 1983 was just about twice as high as would normally be expected. The increase was in myeloid and unspecified forms of leukemia; lymphatic and monocytic forms of the disease had no higher incidence among Amateurs than among others.

COMMENT DEADLINE FOR FCC'S NATIONAL REPEATER COORDINATION proposal (PR Docket 85-22) has been extended to August 15 in response to an ARRL request. The new Reply Comment date is September 30. Comments received thus far by the FCC have almost all been endorsements of the concept of national coordination, with few specific ideas on how to make it work.

VEC MAINTENANCE OF AMATEUR QUESTION POOLS WAS PROPOSED by the FCC in a Notice of Proposed Rule Making issued June 12. VEC-developed questions would have to follow the Commission's syllabus, and each pool would have to include at least 10 times the number of questions asked in that particular exam. At the same time the FCC also proposed moving up the date at which VECs may begin preparing their own exams. Comments on PR Docket 85-196 are due at the Commission by August 30, and Reply Comments by September 30.

One Regional VEC Has Already Dropped Out Of The Program, and another has said it plans to when the ARRL gets fully up to speed. Still another VEC has asked his Senator to look into the fee structure, as he feels his club isn't getting enough money for its efforts. For comparative purposes, NABER's fee for administering an exam for certification under its commercial examination program is \$38!

The FCC's August VEC Meeting In Gettysburg Had Relatively Few signed up at presstime, despite a very promising program. Planned topics include improving speed of service, decreasing paperwork errors, and improving the integrity—real and perceived—of the program. Attendees will also meet the FCC people they've been dealing with and see the FCC's licensing facilities and procedures in operation.

Volunteer Examiners Are Now Averaging About 4000 Exam Elements Monthly, compared to a high of about 2750 exams a month when the FCC was still giving exams. However, the U.S. Amateur population is still well under its March, 1983, all-time high of 414,973; latest (May 30) figures show 410,846 individual FCC-licensed Amateurs.

U.S. AMATEURS MAY FINALLY USE OSCAR 10'S MODE "L" TRANSPONDER, under an FCC STA issued June 12. The Special Temporary Authorization permits uplink transmissions to OSCAR 10 from 1269.05 to 1269.85 MHz; an editorial error in the initial FCC release limited the STA to Extras only, but that was later corrected to include Technicians and above.

# You may not be able to solve the world's problems. But at least you can listen.



## The Panasonic Command Series™. With double superheterodyne tuning, you'll hear the world loud and clear.

Now it's easy to listen in on the world's hot spots. With the Panasonic RF-B600 Command Series FM/LW/MW/SW receiver.

Its advanced microcomputer-controlled tuner lets you preset up to nine different frequencies. And reach them at the touch of a button. Or, press the appropriate buttons and tune in any desired frequency with direct-access digital tuning. It'll lock right in to every signal with a PLL quartz-synthesized tuner. Once tuned in, the Panasonic double superheterodyne system helps deliver a clean, consistent signal.

There's even built-in auto-tuning to let you scan the shortwave band automatically, as well as manually. All this means you can tune in Berlin, pick up Paris, or locate London in an instant. Without dialing all over the band.

Both the RF-B600 and the RF-B300 are packed with features and built to go anywhere.

The Panasonic Command Series offers something for everyone. With equipment sophisticated enough to impress the most avid enthusiast, and automatic features that get you where you want to be. Fast.

There's a whole world out there that's waiting to be heard. Tune in to it with the Panasonic Command Series.



Batteries not included.

**Panasonic**  
just slightly ahead of our time.™



## comments

### can we talk?

Dear HR:

In the May, 1985, editorial it was noted that we Amateurs can't really communicate. I find this statement to be offensive, but in many respects accurate....

I find it offensive because I think it comes from a narrow perspective. It seems the persons making such statements see only one aspect of our hobby. I would agree that at times we really don't communicate much of anything interesting or important. The hard work and learning that made such contacts possible can't be judged on this evidence alone.

The major reason for this lack of ability to communicate clearly and effectively is a failure of our society and its education system, not the fault of Amateur Radio. We in Amateur Radio are only a reflection of the society which makes our hobby possible. Everywhere one looks these days, one can find someone writing about the deplorable state of our schools. We have students who can't read or write properly receiving diplomas and college degrees. To correct this sad state of affairs, we as a society will have to change our approach to education and discipline....

One last issue before I close. I don't think that many people, when they judge our ability to communicate, listen to 2 meters FM. This activity is one really bright spot in Amateur Radio when it comes to communication. Here you find truly local activity being

carried out. In the case of my area, Southern New England, we have many fine activities taking place on repeaters and on simplex. We have a computer net on the W1XJ repeater that meets on Mondays at 8:30 PM, local time, where hams communicate ideas and educational information concerning this aspect of our hobby. We have several MSO-type RTTY bulletin board systems up and running, distributing Amateur information of all kinds. We now have active packet radio systems in operation with all sorts of bulletin boards, message systems, and other features that promote real communication.

**Kenneth E. Stringham, Jr., AE1X**  
Attleboro, Massachusetts

### service — not hobby

Dear HR:

Congratulations on an outstanding May issue!

It was especially interesting to read the editorial, "The Readers Speak," (page 4) regarding the problems and solutions before us. Let me call to your attention one of the problems that seems to have escaped your attention. It is one of perception, and it is reflected by you in your editorial by the use of the word "hobby" no fewer than five times. Of course, you are referring to the Amateur Radio "Service." It is, you know, a federally regulated "service" and not a "hobby."

Stamp collecting is a hobby. Model building is a hobby. Woodcraft is a hobby. Amateur Radio is a federally regulated *service* — even though it is perceived as a hobby by all too many hams and would-be hams.

Typically, hobbies don't require formal exams and licenses and involvement with federal regulations. One has only to read Part 97 to see that the purpose and intent of Amateur Radio was not to establish a hobby, but rather a federally regulated communications service for the public interest, convenience, and necessity. Indeed, too many of us are overly involved in contesting and card-collecting — the hobby aspects of ham radio. But if it's presented to us as a hobby, why not?

Our organization, the Wireless Institute of New Orleans, was established by a group of dedicated hams to preserve the original principles of Amateur Radio and to promote the state of communications art. We continue to observe the degradation of ham radio into what appears to be an expanded version of the Citizen's Band. But what the hell? It's just another hobby, isn't it?

**A.J. ("Buddy") Massa, W5VSR**  
New Orleans, Louisiana

### matching dipoles

Dear HR:

Even though George A. Wilson, Jr., W1OLP, in "Matching Dipole Antennas," (May, 1984, page 129) made at least 24 separate references to GDO (Grid Dip Oscillators) and Grid Dipping, someone is certain to try substituting a solid-state dipper, (such as the Heathkit HD-1250 or one of several factory assembled versions) when exciting the RF Bridge discussed in the article. In fact, with the solid-state dipper far more prevalent today than the old vacuum tube grid dip oscillator (and interchangeable in most applications), no doubt a large number of hams who build the RF bridge will end up frustrated and with no discernible "dip."


While the solid-state dippers can be used to determine resonance, per the first part of George's article, it is not likely to provide enough excitation to obtain a reading with the RF bridge unless overcoupled, with sensitivity set at maximum, and with an extremely sensitive  $\mu\text{A}$  meter used as the detector. Even a 50  $\mu\text{A}$  meter will probably not allow a discernible "dip" to be obtained!

A rough idea of a dipper's suitability can be obtained by connecting a germanium diode and a small 2 to 3-turn link in series across the  $\mu\text{A}$  meter's terminals. Coupling the link to the dipper's coil should easily produce a full-scale reading. If it does not, the dipper cannot be used to excite the RF bridge.

**Robert G. Wheaton, W5XW**  
San Antonio, Texas

# NEW FROM MFJ

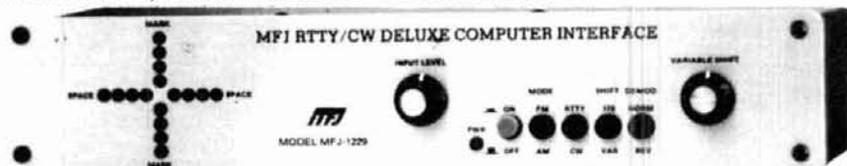**MFJ'S MOST ADVANCED RTTY/ASCII/AMTOR/CW COMPUTER INTERFACE HAS FM, AM MODES, LED TUNING ARRAY, RS-232 INTERFACE, VARIABLE SHIFT TUNING, 170/850 Hz TRANSMIT, MARK-SPACE DETECTION.**



MFJ RTTY/ASCII/CW software on tape, cables for C-64/VIC-20.

**MFJ-1229** Engineering, performance, value and features sets MFJ's most advanced RTTY/ASCII/AMTOR/CW computer interface apart from others. **FM (limiting) mode** gives easy, trouble-free operation. Best for general use, off-shift copy, drifting signals, and moderate signal and QRM levels. **AM (non-limiting) mode** gives superior performance under weak signal conditions or when there are strong nearby stations. **Crosshair mark-space LED tuning array** simulates scope ellipse for easy, accurate tuning even under poor signal-to-noise conditions. Mark and space outputs for true scope tuning.

**MFJ MULTI-FUNCTION TUNING INDICATOR** MFJ-1221 **\$79.95**



Greatly improve your RTTY copying capabilities. Add a crosshair LED Tuning Indicator that makes tuning quick, easy with pin-point accuracy. Add mark and space outputs for scope tuning. Add LEDs that indicate 170, 425, 850 Hz shifts. Great for copying RTTY outside ham bands. Add sharp mark and space filters to improve copy under crowded/weak conditions. 170, 425, 850 Hz shifts. Add Normal/Reverse switch to check for inverted RTTY without retuning. Add output level control to adjust signal into your terminal unit. Add a limiter to even out signal variation for smoother copy. Unit plugs between your tuner and receiver. Mark is 2125 Hz, space is 2295, 2550 or 2975 Hz. Measures 10x2x6 in. and uses floating 18 VDC or 110 VAC with AC adapter, MFJ-1312, \$9.95.


**24/12 HOUR CLOCK/ID TIMER**

Switch to 24 hour UTC or 12 hour format! Battery backup. ID timer alerts every 9 minutes after reset. Red .6 in. LEDs. Synchronizable to WWW. Alarm, Snooze function. PM, alarm on indicators. Gray/Black cabinet. 110 VAC, 60 Hz.



MFJ-106 **\$19.95**

**MFJ 24 HOUR LCD CLOCKS**

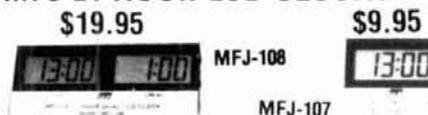

**\$19.95**

MFJ-108

**\$9.95**

MFJ-107

Transmits on both 170 Hz and 850 Hz shift. Built-in RS-232 interface, no extra cost. Variable shift tuning lets you copy any shift between 100 and 1000 Hz and any speed (5-100 WPM RTTY/CW and up to 300 baud ASCII). Push button for 170 Hz shift. Sharp multi-pole mark and space filters give true mark-space detection. Ganged pots give space passband tuning with constant bandwidth. Factory adjusted trim pots for optimum filter performance. Multi-pole active filters are used for pre-limiter, mark, space and post detection filtering. Has automatic threshold correction. This advanced design gives good copy under QRM, weak signals and selective fading.

**MFJ ELECTRONIC KEYS**

MFJ-407 **\$69.95**



MFJ-407 Deluxe Electronic Keyer sends Iambic, automatic, semi-auto or manual. Use squeeze, single lever or straight key. Plus/minus keying. 8 to 50 WPM. Speed, weight, tone, volume controls. On/Off, Tune, Semi-auto switches. Speaker. RF proof. 7x2x6 inches. Uses 9 V battery, 6-9 VDC or 110 VAC with AC adapter, MFJ-1305, \$9.95.

**MICROPHONE EQUALIZER**

MFJ-550 **\$49.95**



Greatly improves transmitted SSB speech for maximum talk power. Evens out speech peaks and valleys due to voice, microphone and room characteristics that make speech hard to understand. Produces cleaner, more intelligible speech on receiving end. Improves mobile operation by reducing bassy peaks due to acoustic resonances. Plugs between mic and rig. 4 pin mic jack, shielded output cable. High, mid, low controls provide ±12 db boost or cut at 490, 1170, 2800 Hz. Mic gain, on/off/bypass switch. "On" LED. 7x2x6 inches. 9 V battery, 12 VDC or 110 VAC with adapter, MFJ-1312, \$9.95.

Has front panel sensitivity control. Normal/Reverse switch eliminates retuning while checking for inverted RTTY. Speaker jack. +250 VDC loop output.

Exar 2206 sine wave generator gives phase continuous AFSK tones. Standard 2125 Hz mark and 2295/2975 Hz space. Microphone lines: AFSK out, AFSK ground, PTT out and PTT ground.

FSK keying for transceivers with FSK input. Has sharp 800 Hz CW filter, plus and minus CW keying and external CW key jack.

Kantronics software compatible socket. Exclusive TTL/RS-232 general purpose socket allows interfacing to nearly any personal computer with most appropriate software. Available TTL/RS-232 lines: RTTY demod out, CW demod out (TTL only), CW-ID in, RTTY in, PTT in, key in. All signal lines are buffered and can be inverted using an internal DIP switch.

Metal cabinet. Brushed aluminum front. 12½x2½x6 inches. 18 VDC or 110 VAC with optional AC adapter, MFJ-1312, \$9.95.

Plugs between rig and C-64, VIC-20, Apple, TRS-80C, Atari, TI-99 and other personal computers. Use MFJ, Kantronics, AEA and other RTTY/ASCII/AMTOR/CW software.

**MFJ ANTENNA BRIDGE** MFJ-204 **\$79.95**

Trim your antenna for optimum performance quickly and easily. Read antenna resistance up to 500 ohms. Covers all ham bands below 30 MHz. Measure resonant frequency of antenna. Easy to use, connect antenna, set frequency, adjust bridge for meter null and read antenna resistance. Has frequency counter jack. Use as signal generator. Portable, self-contained. 4x2x2 in. 9 V battery or 110 VAC with adapter, MFJ-1312, \$9.95.



**MFJ PORTABLE ANTENNA**

MFJ's Portable Antenna lets you operate 40, 30, 20, 15, 10 meters from apartments, motels, camp sites, vacation spots, nearly any electrically clear location where space for a full size antenna is a problem.

A telescoping whip (extends to 54 in.) is mounted on self-standing 5½x6¼x2¼ inch Phenolic case. Built-in antenna tuner. Field strength meter. 50 feet RG-58 coax. Complete multi-band portable antenna system that you can use nearly anywhere. Up to 300 watts PEP.

MFJ-1621 **\$79.95**



Huge 5/8 inch bold black LCD numerals make these two 24 Hour clocks a must for your shack. Choose from a dual clock that features separate UTC and local time display or a single clock that displays 24 Hour time. Mounted in a brushed aluminum frame, these clocks feature huge 5/8 inch LCD numerals and a sloped face for across the room viewing. Easy set month, day, hour, minute and second function. Clocks can be operated in an alternating time-date display mode. MFJ-108, 4½x1x2 inches; MFJ-107, 2¼x1x2 inches. Battery included.



MFJ ENTERPRISES, INC.  
Box 494, Mississippi State, MS 39762

TO ORDER OR FOR YOUR NEAREST DEALER, CALL TOLL-FREE  
**800-647-1800**. Call 601-323-5869 in Miss and outside continental USA  
Telex 53-4590 MFJ STKV



# HAM RADIO OUTLET

## 6 STORE BUYING POWER!

■ TOLL-FREE PHONE: 800-854-6046

INCLUDING ALASKA AND HAWAII CALIF. AND ARIZONA CUSTOMERS CALL OR VISIT STORE NEAREST YOU

■ FREE SHIPMENT

MOST ITEMS. U.P.S. SURFACE.

 **ICOM**

SIMPLEX-REPEATER-SATELLITE



**IC-271H**

2 METERS • 100 WATTS  
• ALL-MODE



**IC-471H**

430-450MHz • 75 WATTS  
• ALL-MODE

CALL FOR YOUR SPECIAL PRICE

 **TOWER**  
CORPORATION  
Formerly Tristao Tower Co.

**MA-40 40' tubular**

Regular \$745

**SALE! \$549**

**MA-550 55' tubular**

Will handle 10 sq. ft.  
antennas at 50 MPH winds.

Regular \$1245

**SALE! \$899**

**IN STOCK FOR  
IMMEDIATE DELIVERY**

CALL FOR INFORMATION  
ON ALL OTHER MODELS



**FT-209RH**

**FT-757GX**

**FT-2700H**



**NEW!**  
2M/70CM  
TRANSCEIVER

CALL FOR GREAT PRICES

 **ICOM** **IC-27A**



**SUPER-COMPACT  
2 METER MOBILE**

ALSO \*IC-27H HIGH POWER VERSION  
AND IC-37A, 220MHz  
IC-47A, 70CM **SAVE!**

**BIRD**



**MODEL  
43**

THE LONG  
TIME STANDARD  
FOR ACCURACY

**SLUGS**



MOST ITEMS IN STOCK

**NEW! KENWOOD TS-940S**

TOP-OF-THE-LINE HF TRANSCEIVER



- General coverage receiver.
- 40 memories.
- 250W pep. Runs cooler, longer.
- Additional LCD readout.
- Optional ant. tuner, 160 thru 10M.
- Plus, plus, plus.

**NEW!**

CALL FOR PRICE  
AND INFORMATION



**Tri-Ex**

**SALE!**

W-51 SALE \$899  
LM-354 SALE \$1599

**IMMEDIATE DELIVERY**

THE VERY BEST DEAL ON EVERY COUNT!



# FM repeater separation — 20 kHz Yes, 15 kHz No

## Proving the point through VHF FM receiver selectivity measurements

**Amateur use of the 2-meter (144-148 MHz) band** is now under nationwide scrutiny in an effort to determine whether the channel spacing for FM sections of the band should be set at 15 kHz or 20 kHz. The original 30 kHz spacing was divided, as band use increased, into 15 kHz channels to allow more channels; this division led to increased adjacent channel interference in many areas, which in turn resulted in the current proposal to increase the channel spacing to 20 kHz.

Changing to the 20 kHz spacing will, of course, change the frequencies of some of the channels and change the overall number of repeater "pairs" in the band. Only the technical — not the political or emotional issues implicit in these changes — will be addressed in this article.

In trying to become better informed on the issue and thus establish a more substantial foundation for our decision in northern Colorado, we examined the nature of frequency modulation and its transmission and reception, and then made some measurements on several popular transceivers. We hope this information will be useful to other repeater groups and coordinators as they weigh this issue for themselves.

Our measurements were made to establish the actual performance levels of Amateur ("consumer") and professional ("commercial") receivers, with respect to adjacent channel rejection and variation of sensitivity with transmitter deviation setting.

### frequency modulation


One factor that complicates any discussion of FM

channel spacing is the varied levels of the understanding from one person to another of just how FM works. The following brief review may help to clarify the subject and shed some light on interpretation of our data.

In FM operation, the radio frequency output spectrum components vary as a function of the modulating (voice) signal amplitude. The resulting signal consists of a varying amplitude carrier and sideband pairs. (In narrow-band FM-only, the first sideband pair and carrier are significant in amplitude.) The amplitude of the carrier and sidebands is described by a mathematical term called a Bessel function of the first kind. The only thing we need to understand here is how much power is spread over how much spectrum, and what determines the signal (spectrum) width. Note that regardless of individual sideband or carrier amplitude, the *total* power of the FM signal is constant.

A simplified FM signal spectrum is illustrated in **fig. 1**. With no modulation applied, a single carrier term at a frequency  $f_c$  is visible. As the amplitude of the modulating signal is increased (from zero), a sideband pair displaced  $\pm f_m$  from the carrier frequency appears. In this simplified version, we have assumed that a single-tone modulating signal (at frequency  $f_m$ ) is used. Further increases in modulating signal amplitude cause additional sideband terms (pairs) to appear. At the same time, the amplitude of the carrier decreases. It is worthwhile reiterating that the total power of the FM signal is constant. This power distribution is a function of the modulation index  $\beta$ , which is defined as the ratio of frequency deviation (swing from carrier frequency) to modulating frequency ( $f_m$ ). For small values of  $\beta$ , the bandwidth occupied by an FM signal is simply  $2 \times f_m$ . As  $\beta$  increases, more sidebands appear (separated  $f_m$  in frequency from each other). A natural further complication is that voice modulation can be considered to consist of many tones of varying

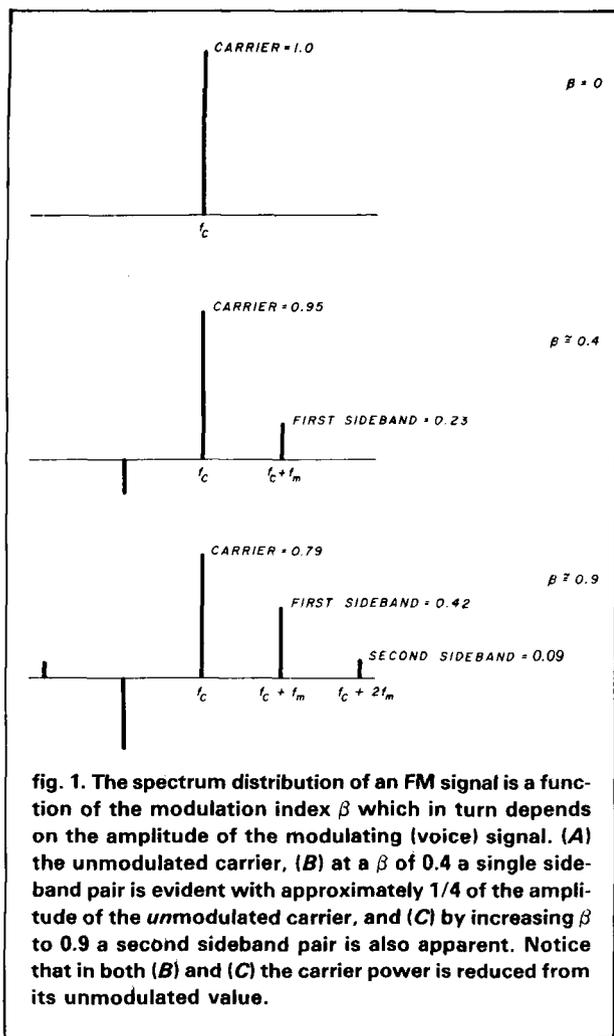By Chris Kelly, WD5IBS, 1220 East Stuart #14, Fort Collins, Colorado 80525, and Virgil Leenerts, W0INK, 1007 W. 30th, Loveland, Colorado 80537




amplitudes. Consequently the total FM signal spectrum is quite complex.

For most VHF FM communications transceivers, this is 5 kHz deviation over 3 kHz maximum voice (modulation) frequency, or a  $\beta$  of 1.7 for high-pitched tones. Notice that lower deviation causes a lower modulation index. Using these figures, we find that 99.99 percent of the power in an FM signal will be contained in about 22 kHz of spectrum.<sup>2</sup> Depending on the assumed voice characteristics, this figure will change, and the older EIA specifications say that 99.99 percent of the power will occupy 19 kHz of spectrum.<sup>3</sup>

In the case of several FM signals, we do not have just narrow carriers that must be separated — we have finite bandwidth modulated signals occupying some spectrum.

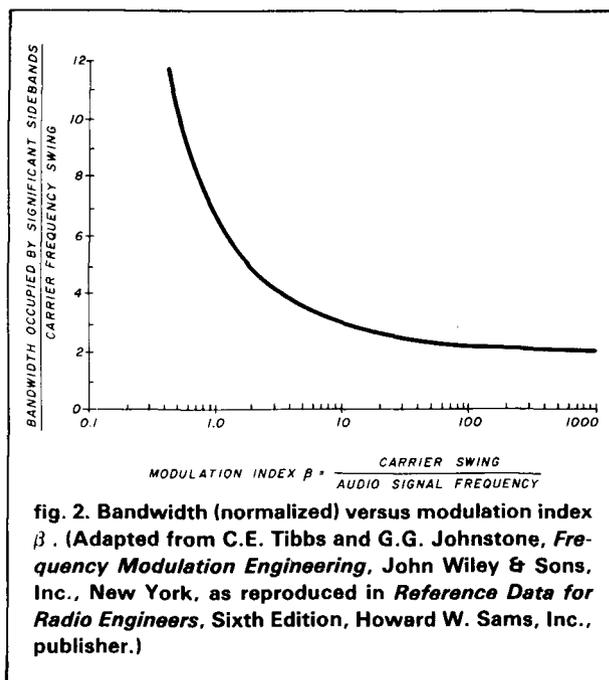For any given modulation frequency, we can decrease the modulation index, and thereby decrease the spectrum occupied, but not always in an exactly linear way. By increasing or decreasing the transmitter deviation control, the power ratios in the various sidebands will change, causing various effects on the radio channel and on the receiver.



## effect of transmitter deviation on system performance

The Amateur 2-meter FM system is based on the commercial 5 kHz deviation FM system. System performance depends on the design and adjustment of the transmitters and the receivers used. However, design tradeoffs do exist.

Amateurs often discuss the effect of changing the deviation setting of ham transmitters, both in bandwidth and in effects on the receiver. We examined these two issues and made measurements of consumer gear and test equipment.

Figure 2 shows a curve of normalized significant bandwidth versus modulation index. Most Amateur transmitters adjusted for 5 kHz deviation will operate at a modulation index ranging between 3 and 6, depending on the operator's individual voice characteristics. The curve shows that in this range the curve begins to flatten, and that increasing deviation has less effect on bandwidth than at lower modulation indices. The "rules of thumb" used to roughly describe the bandwidth of FM signals involve a limited range where the slope of this curve can be considered constant. This is because as you decrease transmitter deviation, the modulation index for a given tone rises, changing the relative energy in each sideband.

Figure 3 illustrates the effect of the modulation index on the relative amplitude of FM sideband pairs. Consider the case of a 1 kHz tone, with the operator varying the deviation control on the transmitter. When the deviation control is at zero, all the RF power is contained in the unmodulated carrier. When the deviation rises to 1 kHz, the modulation index equals 1, and we

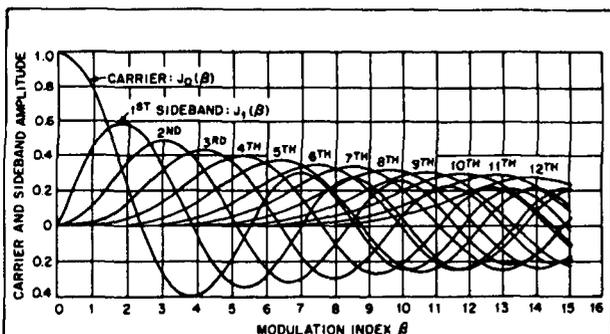


fig. 3. Plot of Bessel function of first kind as a function of argument  $\beta$ . (From P.F. Panter's *Modulation, Noise, and Spectral Analysis*, as reproduced in *Reference Data for Radio Engineers*, Sixth Edition, Howard W. Sams, Inc., publisher.)

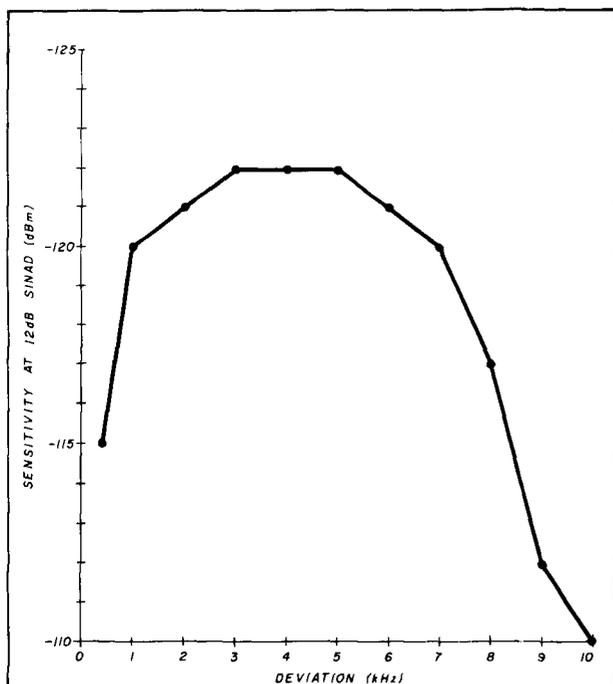


fig. 4. Effect of deviation on sensitivity for a popular Amateur 2-meter transceiver.

see a decrease in carrier power and increases in the first and second sidebands. In fact, there are increases in every sideband, but they are too small to show on this chart. At 1 kHz deviation, we see that the amplitude of the first sidebands has risen to about 0.44 times the original carrier level, and each sideband contains about 19 percent (0.44 squared) of the RF power. Now each of the second sidebands has about 1 percent (0.11 squared) of the RF power, and the carrier has only about 60 percent of the power.

As we raise the deviation to 5 kHz, the modulation index rises to 5 (5 kHz deviation/1 kHz modulation) and we can see that significant energy is now found

in almost all sidebands up to the eighth. (Actually, there is energy present in other sidebands, but this chart cannot illustrate that.) The sidebands are spaced at intervals corresponding to the frequency of the modulating tone (1 kHz).

Note also how the modulation index varies with the modulating tone. Consider what would happen if we left the transmitter at 5 kHz deviation, but raised the modulating tone to 2000 Hz. The modulation index would drop to 2.5, and we would have to examine fig. 3 at this new point to determine the relative amplitude of sidebands at the new index. Here, only the first five sidebands are noticeable — but remember, these sidebands are now 2 kHz apart. The bandwidth of the signal has increased, but it has not doubled.

It should be noted that this discussion of single-tone modulation is a very simplified version of what happens when voice is used to modulate the carrier. The voice is composed of many frequencies, and the composition changes with time. The components of the FM signal are many, and not just the sum of the voice frequencies. Consider a case of just two tones modulating the carrier. There will be carriers with amplitude of the Bessel function ( $J_0$ ) at the deviation ratio of the first tone, the Bessel function ( $J_0$ ) of the second tone, and sidebands having lines of all Bessel functions of  $f_1$ ,  $f_2$ ,  $f_1 + f_2$ ,  $f_1 - f_2$ ,  $f_1 + 3f_2$ ,  $3f_1 + f_2$ , and so on.

If you now consider the complexity of the human voice, the problem of mathematically describing the bandwidth becomes unmanageable, at least for this author. For this reason the discussions here are limited to single-tone modulation.

The second aspect of performance affected by the deviation adjustment of the transmitter is how well the receiver is able to demodulate these signals. This is a very easily measured parameter. We checked the performance of an Amateur receiver when receiving signals at different deviation values. In this test, we used a Hewlett-Packard 8640B signal generator and a SINADder. We measured the sensitivity of the receiver at the 12 dB SINAD point at deviations of 500 Hz, and 1 kHz through 10 kHz deviation in steps of 1 kHz. The results of the test are shown in fig. 4.

Notice that maximum sensitivity (–122 dBm at 12 dB SINAD) occurs at 3, 4, and 5 kHz deviation. The sensitivity is not affected by changes in deviation within this range. But above 5 kHz and below 3 kHz deviation, the sensitivity actually decreases. This result contradicts the popular notion that increasing the deviation of a transmitter increases range, and further indicates that reduction of transmitter deviation below 5 kHz does not reduce range (down to no less than 3 kHz, that is).

### receiver selectivity

Although the performance of a receiver in rejecting

**table 1. Level of isolation from interference experienced on channels separated from 10 to 30 kHz from an adjacent FM source.**

**Kenwood TW-4000A.** On channel signal: - 115 dBm, ± 3 kHz deviation, 1000 Hz modulation.

interference modulation	30 kHz (dB)	20 kHz (dB)	15 kHz (dB)	10 kHz (dB)
400 Hz (EIA)	86	80	45	0
800 Hz	86	80	40	0
1200 Hz	86	80	33	0
2000 Hz	86	68	25	0

**Kenwood TR-7800.** On channel signal: - 114 dBm, ± 3 kHz deviation, 1000 Hz modulation

400 Hz (EIA)	87	82	65	2
800 Hz	87	83	57	0
1200 Hz	87	83	48	0
2000 Hz	87	79	37	0

**Handheld 1.** On channel signal: - 115 dBm, ± 3 kHz deviation, 1000 Hz modulation

400 Hz (EIA)	69	52	35	0
800 Hz	69	52	34	0
1200 Hz	69	52	30	0
2000 Hz	69	52	25	0


**Motorola Syntor-X, 460.425 MHz.** On channel signal: - 107 dBm, ± 3 kHz deviation, 1000 Hz modulation.

400 Hz (EIA)	93	85	53	13
800 Hz	93	85	53	13
1200 Hz	93	85	50	20
2000 Hz	93	84	43	8

off-channel signals is something that cannot be adjusted easily, it is a major element of any radio communications system. A receiver consists of RF, IF, discriminator, and audio sections with most of the selectivity provided by the IF filter section. Intermodulation products and images can be generated in the RF and mixer stages. However, these are not directly related to the problem of adjacent channel interference — the IF filter and discriminator are.

Most FM receivers use crystal or ceramic filters to narrow the IF bandwidth before the signals reach the discriminator, where they are demodulated (back) to audio frequencies. While it would be nice if we could build ideal filters that would pass all signals in the desired passband and completely stop all off-channel signals, this isn't possible. Filters actually have finite passbands with "skirts" that roll off signals more the further away from the channel center frequency they are. The filters are usually specified by their bandwidth at the - 6 dB and the - 60 dB points; this is also how most ham transceivers are specified for selectivity.

Because the actual performance of the radio depends on this and other, less easily described factors — including discriminator performance — commercial manufacturers have therefore elected to specify their receiver selectivity with a functional test that actually challenges the receiver with a signal in the ad-

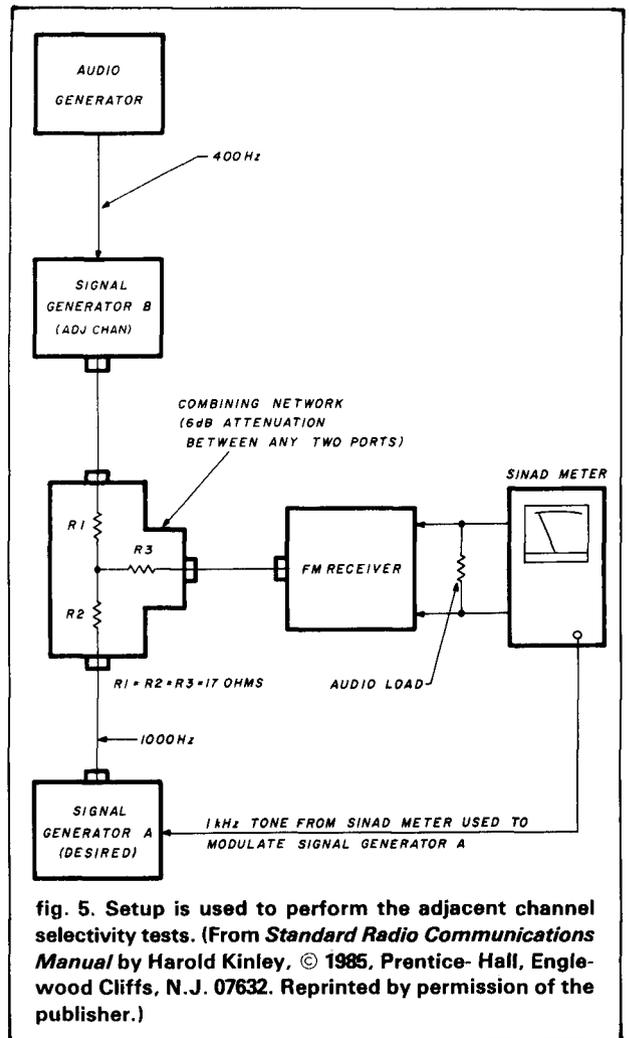

**fig. 5.** Setup is used to perform the adjacent channel selectivity tests. (From *Standard Radio Communications Manual* by Harold Kinley, © 1985, Prentice-Hall, Englewood Cliffs, N.J. 07632. Reprinted by permission of the publisher.)

acent channel and measures the result. This is the test we selected and performed to determine selectivity.

The Electronic Industries Association (EIA) has established an adjacent channel rejection test based on the ratio between the on-channel to off-channel signal strengths when the received signal-to-noise and distortion (SINAD) ratio becomes degraded by 3 dB by the adjacent channel signal. This test, part of the RS 204-C test, is performed by mixing the signals from two signal generators and measuring the SINAD of a 1000 Hz tone modulating the on-channel signal at 3 kHz deviation.<sup>4</sup>

The test setup used to perform the selectivity test is shown in fig. 5. The on-channel signal level is raised to obtain a 12 dB SINAD, then raised an additional 3 dB. The off-channel signal is modulated at 3 kHz deviation by a 400 Hz tone, and its signal level is raised until the SINAD is degraded back down to 12 dB. Then the ratio of the two signals' strength is calculated in dB. When this measurement is made for both the next higher and the next lower adjacent channels, the lower of the two figures is used.

When the EIA established these tests for selectivity, they also established standards they consider "mini-

## the action is at the IF — not the RF — stages

When the problem of adjacent channel interference is examined, attention is focused on the filtering that takes place at the intermediate frequency (IF) stages of the receiver, not at the radio frequency (RF) stages. The reason the IF gets the attention is the very narrow bandwidth required to allow separation of channels within the receiver's radio frequency input bandwidth.

At the RF frequencies, cavity resonators are usually used by repeaters and helical resonators are found in commercial and some consumer receivers. These filters are used to control the receiver's RF bandwidth to improve performance in terms of sensitivity and reduction of out-of-band signal strength. By this filtering, desensitization ("desense") and intermodulation distortion ("intermod") are reduced. However, these filters are typically 50 kHz to several Megahertz wide, and match the input RF stages to the intended operating range of the receiver. These filters are therefore very wide compared to the spacing of the channels (15 or 20 kHz), and will not have any significant filtering effect on those adjacent channels signals.

In the IF amplifier chain, however, the very narrow filters required become practical, due to both the lower frequency used in the IF (typically from 0.455 to 10.7 Megahertz) and the fact that the intermediate frequency does not have to be varied as the radio changes operating frequencies. In the IF stages, crystal filters are most commonly used to obtain very high "Q" (resonant frequency divided by bandwidth), frequency stability and shape factor (bandwidth at -60 dB divided by -6 dB bandwidth). These filters are commonly built with very narrow passbands (12 to 20 kHz wide for FM, and as little as 250 Hertz wide for CW applications). Even these filters do not act as "brick-walls," passing all signals in the passband and completely stopping all signals outside of the passband; since their out-of-band attenuation increases as the off-channel signal moves farther away from the passband. The slope of this attenuation is another factor in the response of a receiver to the adjacent channel rejection test, and together with the filter bandwidth (3 dB bandwidth) is a major factor in determining receiver performance in the test.

The IF filter, then, plays a key part in determining the receiver's response to adjacent channel interference, while the filtering at the RF stages of the receiver has little or no effect on this problem.

imum acceptable" performance. For this test, performed on the adjacent channels, the minimum acceptable standard is 70 dB isolation from the adjacent channel.

In these tests, we used a pair of HP 8640B VHF generators, chosen for their spectrally pure output signals (SSB phase noise below -130 dBc), as the signal sources. The SINAD was measured using a Helper Instruments "SINADder 5."

After the normal RS-204-C tests, we also measured selectivity with different frequencies of modulating tone on the adjacent channel signal. We did this because we believed that the choice of a 3 kHz deviation and a 400 Hz modulation tone may not be realistic for direct comparison with the ham environment, since our DTMF tones and voices contain higher frequency components than 400 Hz, and our transmitters may be adjusted for greater deviation. While we did not change the deviation setting, we made additional measurements with tones of 800, 1200, and 2000 Hz at 3-kHz deviation.

We measured receiver performance in this way, at channel spacings of 10 kHz, 15 kHz, 20 kHz, and 30 kHz. The seven units we tested included one commercial and three consumer mobile transceivers as well as three handhelds.

### results with consumer gear

The results with consumer equipment are shown in **figs. 6A, B, and C**. Note that at 10 kHz spacing, little or no adjacent channel rejection is evident, and signals within 10 kHz of the channel center frequency are treated as "on-channel" by the receivers. This gives some idea of the bandwidth of each receiver's IF filter.

At 15 kHz separation, the adjacent channel isolation (of an unmodulated carrier) is about 45 to 70 dB. With the introduction of modulation, the interfering signal component is up by as much as 30 dB from ideal.

At 20 kHz, the adjacent channel isolation is about 80 dB, and some adjacent channel modulation is still detected. In most cases, the 20 kHz measurement was within a few dB of the receiver's ultimate rejection (as measured at 30 kHz separation).

At 30 kHz, the adjacent channel isolation is about 85 dB, and there is no change in this figure because of modulation frequency change. This figure shows little variation among the mobile rigs, but the handheld unit shows slightly lower performance (70 dB). (See appendix for further details.)

### results with commercial gear

Motorola loaned us a commercial UHF "SYNTOR-X" which tuned to 460 MHz. (A VHF unit was not available.) At UHF, commercial manufacturers and Amateurs use 25-kHz channel spacing, but shop personnel believe that both VHF and UHF radios have similar specs and IF designs. *We believe this test is*

COM 144, 220 and 440MHz

# MOBILES



## The World's Most Compact Mobiles

ICOM's three ultra compact mobiles...the IC-27A 220MHz, the IC-37A 220MHz and the IC-47A 440MHz... are the smallest mobiles available.

Even in such a small package the 25 watt mobiles contain an internal speaker which makes them fully self-contained and easy to mount.

Size. The ICOM compacts measure only 5½"W x 1½"H x 9"D (IC-47A is 9" deep)... which allows them to be mounted in various "compact" locations. Yet the compacts have large operating knobs which are easy to use in the mobile environment.

More Features. Other IC-27A/37A/47A standard features include a mobile mount, IC-HM23 DTMF mic with up/down scan and memory scan, and internally adjustable transmit power. An optional IC-PS45 slim-line external power supply and IC-SP10 external speaker are also available.

Internal Speaker




32 PL Frequencies. The IC-27A/37A/47A come complete with 32 PL frequencies.

9 Memories. The compact mobiles have 9 memories which will store the receive frequency, transmit offset, offset direction and PL tone. All memories are backed up with a lithium battery.

Speech Synthesizer. To verbally announce the receive frequency, an optional UT-16 voice synthesizer is available.

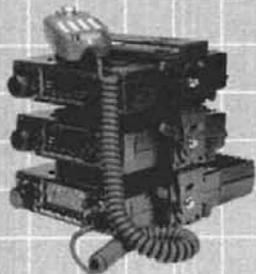Scanning. The ICOM compacts have four scanning systems...memory scan, band scan, program scan and priority scan. Priority may be a memory or a VFO channel...and the scanning speed is adjustable.



Stacking Mobile Mounts. The IC-27A/37A/47A can be stacked to provide a three band mobile station. Each band is full featured and will operate even when another band is in use.

The IC-27A/37A/47A provide superb performance in the mobile radio environment. See them at your local ICOM dealer.



# ICOM

First in Communications

ICOM America, Inc., 2380-116th Ave NE, Bellevue, WA 98004 / 3331 Towerwood Drive, Suite 307, Dallas, TX 75234

All stated specifications are approximate and subject to change without notice or obligation. All ICOM radios significantly exceed FCC regulations limiting spurious emissions. MOBILES385

therefore representative of commercial receiver performance at VHF.

At 10 kHz, the SYNTOR showed slight rejection (see fig. 7), about 10 dB, of the interfering signal, indicating a slightly narrower IF filter than found in the consumer gear. Still, the low value means that receiver bandwidth is approximately 15-20 kHz total.

At 15 kHz, the SYNTOR showed 53 dB isolation, which was degraded by 10 dB when the modulating tone was increased to 2000 Hz. This again indicates, as in the case of the consumer gear, that we are on the skirts of the IF filter.

At 20 kHz, the isolation increased to 85 dB and was degraded only 1 dB by increasing the modulating tone to 2000 Hz.

At 30 kHz the SYNTOR showed 93 dB isolation, actually better than its specifications by several dB. Varying the modulating tone made no difference during the measurements.

### discussion

Two major results are evident in this data. First, while commercial radio gear offers higher performance

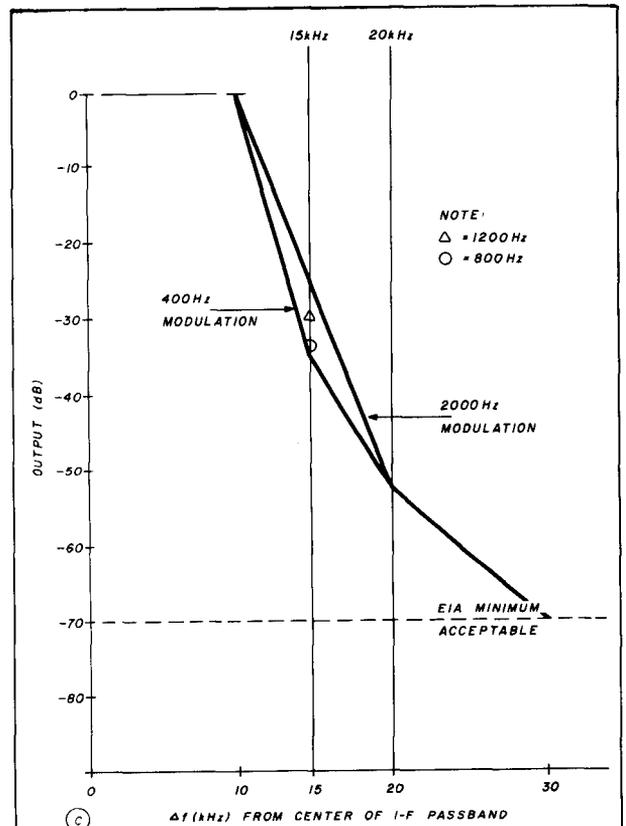
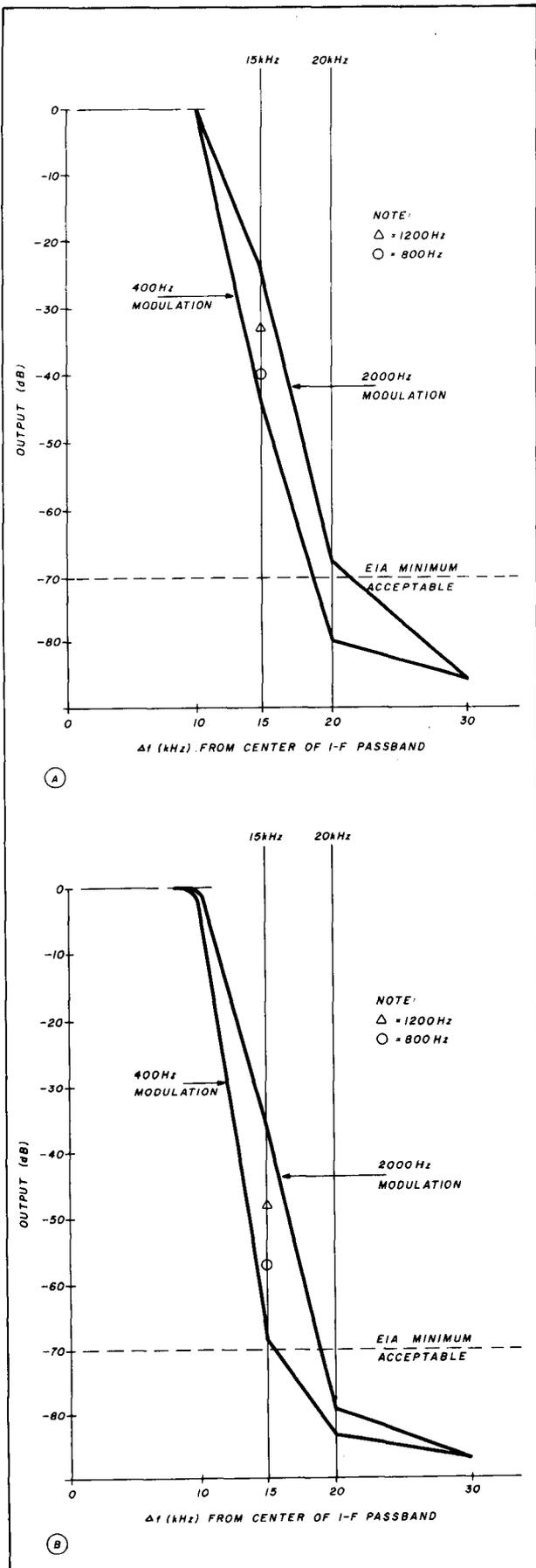



fig. 6. Effect of modulating frequency on selectivity test. Performed on three consumer (Amateur band) transceivers using 3 kHz deviation and 400 Hz (RS-204-C test), 800 Hz, 1200, and 2000 Hz modulation tones. (A) Kenwood TW-4000A, (B) Kenwood TR-7800, and (C) Handheld, HT1.

# John J. Meshna Jr., Inc.

P. O. Box 62 19 Allerton St. E. Lynn, Ma. 01904 Tel: (617) 595-2275

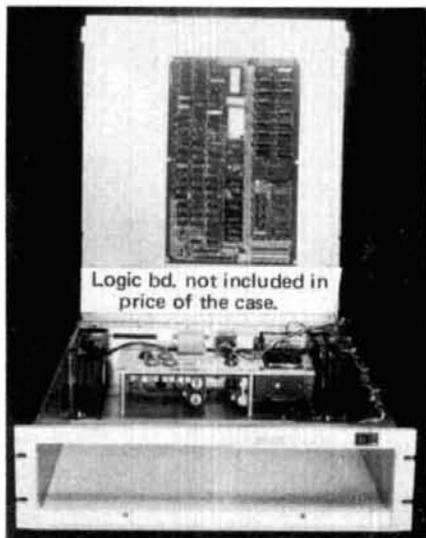
## Dual 8" F. D. D. Case by SMS w/ POWER ONE Power Supply & Cooling Fans

We were very fortunate to find these beautifully designed & constructed rack mount disc drive cases in the surplus field. These cases were made for Scientific Micro Systems for their FT Series of equipment. They are manufactured from heavy gauge steel w/ a cast metal designer bezel. They were designed to house 2 8" floppy or hard drives. We offer you the case with the following components & features: hinged cover with restraining cable for simplified servicing of the interior components, 2 muffin fans for assured cool operation, studs for mounting the controller card listed below, and a heavy duty Power One power supply (their model no. CP 281A). The outputs of the power supply are as follows: +5 vdc 11 amps, +24 vdc 3.5 amps, +12 vdc .25 amps, -12 vdc .25 amps, & -5 vdc .25 amps. The input to the power supply is 115/230 vac 50/60 Hz. and is both filtered and fused. This assembly must have originally sold for well over \$300.00 each! Only 25 on hand, so order early or be left out on this super bargain! Shpg. wt. 38 lb. SPL-479-35 \$135.00 each


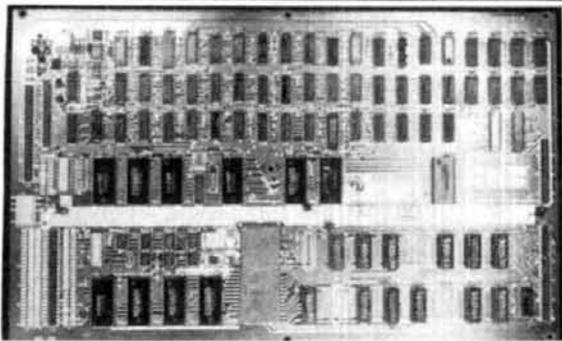
## Scientific Micro Systems IBM 3740 Compatible 8" FDD Controller Card

The SMS FD 0502 8" floppy disc drive controller is a complete preprogrammed controller for single or double density recording on either single or dual headed disc drives. It performs control functions required to transfer data between 1 to 4 drives and a host system, performs all formatting functions required to read and write data and utilizes both IBM single and double density standards to achieve up to 630 Kilobytes of storage per disc surface. Some features are: programmable sector size, 128, 256, 512, or 1024 bytes, jumper selectable drive type, block transfer mode, sector buffer, overlapped head seek, on board General Purpose Host Interface with asynchronous 19 TTL signal lines for eight bit host system and input of only 5 vdc 6 amps. This board provides a direct interface to the following drives: Shugart 800-2/850, Pertec 511, Memorex 550/552, MFE 751B, Qume Data Trak and similar drives. These boards were removed from the above cabinets which were in service prior to our reception of them. The manufacturers price on these IBM compatible boards is currently \$900.00 each. These boards all appear to be in excellent condition. If more information is needed, please call us. Shpg. wt. 3 lb. SPL 480 \$150.00



## SEAGATE TECHNOLOGY ST 506 5 1/4" HARD DRIVES

The Seagate Technology ST 506 hard disc drive utilizes proven Winchester technology for reliable storage of up to 5 megabytes of formatted data. Some features of this very popular drive are: 5 megabit/second data transfer rate, simple floppy like interface, high speed band actuator & stepper head positioning, requires only +5 & +12 vdc, and same physical size and mounting parameters as a mini floppy drive. This Shugart compatible drive is the same as used on many home personal computers. Each drive is checked out prior to shipment. Comes with data. Only a few on hand, so order early. Will run with OMTI controller card listed below. Shpg. wt. 8 lb. ST-506 ~~\$225.00~~ \$175.00




## 5 1/4" HARD DRIVE CONTROLLER CARD

Finally, affordable, intelligent disc drive controllers are available at low, low surplus prices. The OMTI 20C controller boards we offer are unused, late style, surplus from a now defunct system house. OMTI is a division of Scientific Micro Systems. These boards will handle up to (2) 5 1/4 inch Winchester type hard drives that utilize a standard 34 pin SASI interface. Perfect for using with the above Seagate ST 506 drive, or other hard drives from 5 megabytes of storage on up. The controllers have buffered slew/seek modes, overlapped seeks, auto seek & verify, extensive fault detection, auto head & cylinder switching, full sector buffering, 256/512 bytes/sector, 33 or 18 sectors/track (jumper selectable), programmable disc parameters and much more. The board runs on +5 vdc & +12 vdc. We supply users manual & pinout data. Guaranteed O. K.. Shpg. wt. 3 lb. OMTI 20 C \$150.00 each 2/\$275.00 Qty. pricing available.


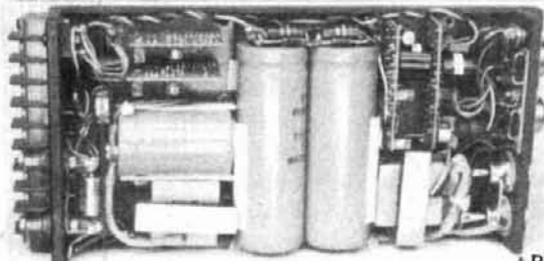
## 5 VDC 25 AMP SWITCHING POWER SUPPLY

We just got in a small lot of ruggedly built, lightweight (4 lb.), compact (11" x 5" x 1 1/2"), fully enclosed (cover removed for pic.), regulated, switching, power supplies made by RO Industries. Input of 115/230 vac is attached thru convenient, clearly marked screw terminals. The hefty 5 vdc 25 amp output is via heavy duty, brass lugs with a Red LED status indicator. All appear to be unused and in excellent condition. Shpg. wt. 6 lb. PS-8 \$50.00



Free 72 page catalogue available or send \$1.00 for 1st class service to P. O. Box 62 E. Lynn, Ma. 01904.

Phone (617) 595-2275 to place your order by phone. MC, VISA or American Express charge cards accepted.



## why do we use FM?

Considering the ongoing discussions of channel spacing and FM bandwidth, one might ask why hams use FM, which occupies such a large bandwidth compared with AM or single sideband (SSB). The answer lies in the improved signal-to-noise ratio (S/N) gained by the demodulator in an FM receiver. If you compare the signal-to-noise ratio of the demodulated signal with the carrier to noise ratio (C/N) of the radio wave before demodulation, you find that above a certain threshold, the demodulated signal shows a significant enhancement in S/N. The measurement of C/N must be made in a bandwidth equivalent to the IF bandwidth of the receiver, but within these constraints, we find an enhancement factor of:  $E = 6\beta^2(\beta + 1)$  where  $\beta$  is the modulation index of the FM signal.\*

To see how significant this enhancement is, consider the case of a 1000 Hz tone modulating a carrier at 4.5 kHz deviation, and a beta of 4.5, not unusual in Amateur voice systems. In this case, the enhancement is 668 times the carrier to noise ratio, or about 28 dB.

This enhancement, seen only above a threshold C/N, is one reason FM is popular for both commercial broadcasting and communications. Below this threshold, FM actually provides lower S/N than other modes, which is why weak-signal work is seldom done using FM.

\*Simon Haykin, *Communications Systems*, John Wiley & Sons, 1983.

than consumer radios, the differences are not particularly large. Secondly, when operated at 15 kHz spacing, all these receivers will exhibit considerably degraded performance when compared to their use at 20 kHz.

On the first result, we wish to note that in the last several years, commercial radio suppliers have changed their radio designs from a relatively limited coverage radio to one that can cover channels separated by many Megahertz. This has been done by reducing filtering at the RF stages and enhancing the IF filters to maintain performance. While this reduction of the  $Q$  of the RF portion of the receivers does not alter the adjacent channel rejection, the enhancement of the IF stages does. The SYNTOR-X model is capable of covering the entire 450 MHz commercial band without retuning the RF stages, and represents first-class commercial radio equipment, with a price near \$2800.


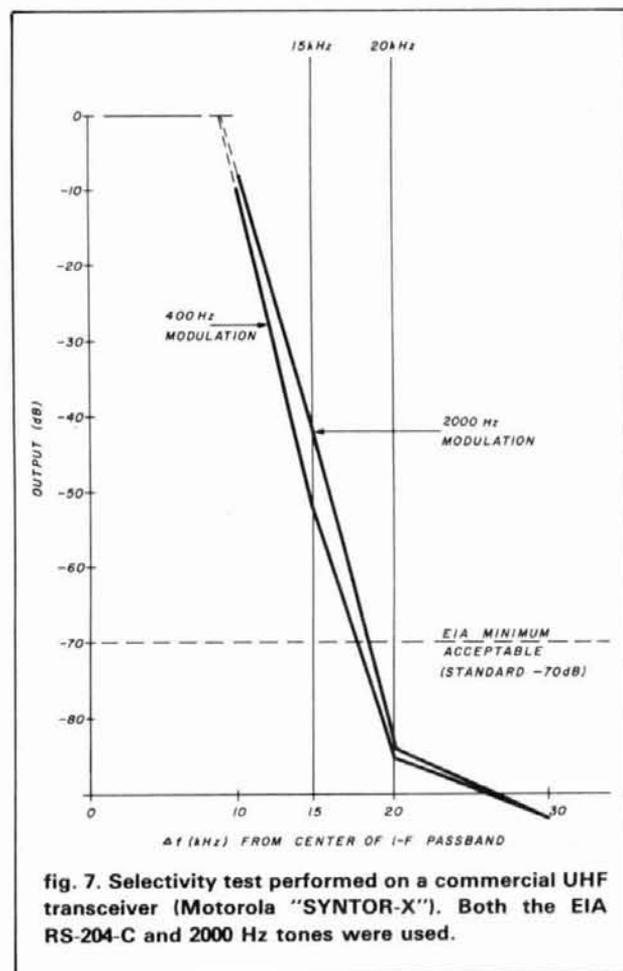


fig. 7. Selectivity test performed on a commercial UHF transceiver (Motorola "SYNTOR-X"). Both the EIA RS-204-C and 2000 Hz tones were used.

We expected, and found, excellent IF performance in the Motorola gear. The surprise was that the IF performance of the consumer gear was *actually quite similar*, and for most Amateurs the difference would not be significant — this was a surprise to us because we suspected that by adopting commercial standards for Amateur purposes, the interference problem could be solved. But the answer is clearly not that simple.

On the second result, we believe that when these radios are operated with 20 kHz channel spacing, they demonstrate performance which is near their ultimate design goal (as defined by their 30 kHz performance). At 15 kHz spacing, these radios *all* demonstrated very similar degradations in performance, and these degradations amounted to 30 to 40 dB. Furthermore, this degradation was significantly affected by the *bandwidth* of the interfering signal. Considering the conservative settings (3 kHz deviation, 400 Hz modulation) we believe the 15 kHz isolation numbers are generous compared to the Amateur environment, where 4.5 to 6 kHz deviation seems more common.

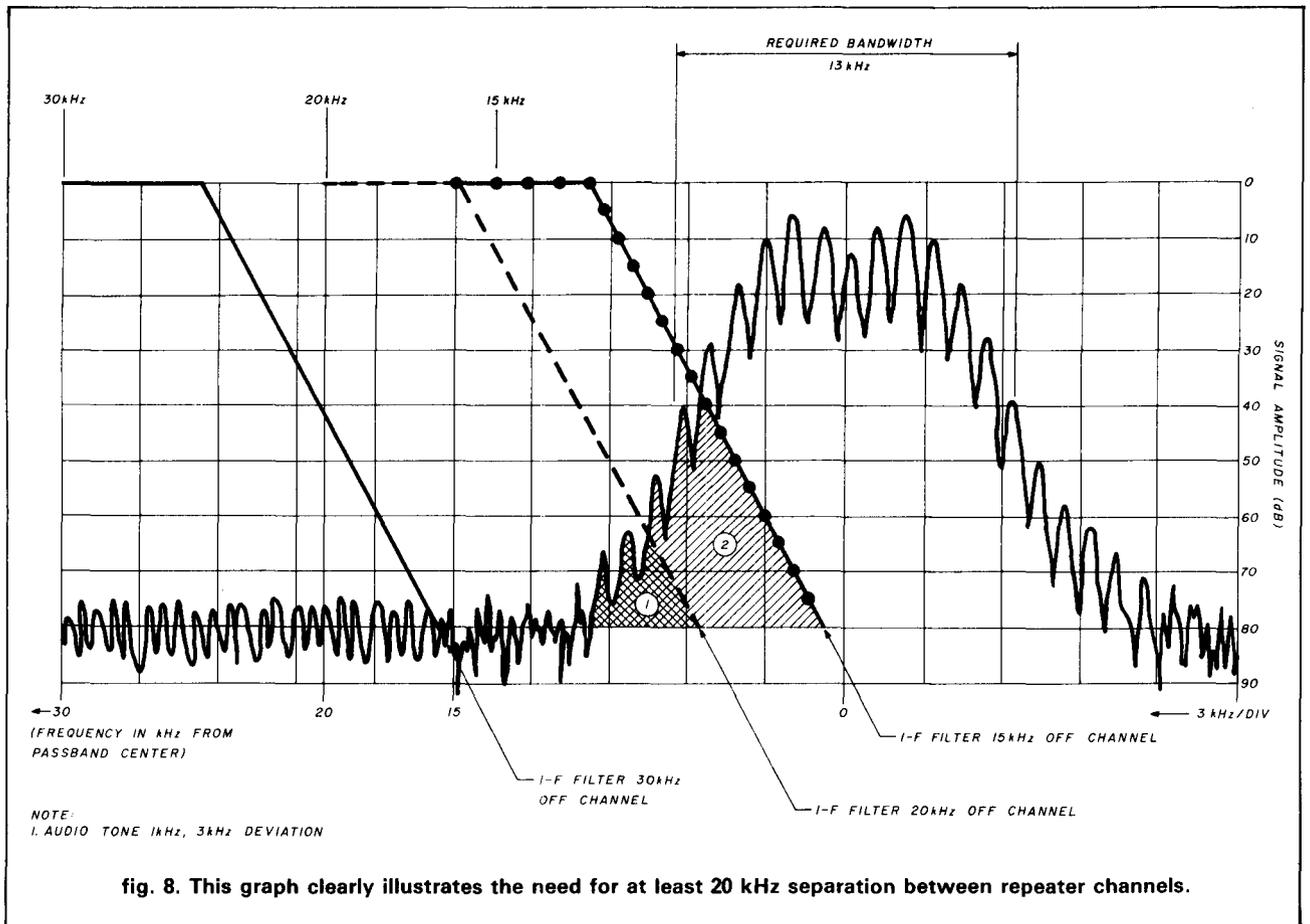

Finally, when these results are compared with the EIA specification for minimum acceptable adjacent channel rejection, we see that all the receivers failed the test at 15 kHz spacing, and all but the handheld unit passed the test at 20 kHz spacing (see appendix).

The mechanism for this adjacent channel interference depends on both the nature of FM itself and the design of the receiver IF filters. What we believe is happening is shown in fig. 8. In this diagram, we have illustrated the shape of the FM signal resulting from a 1 kHz tone modulating a transmitter at 3 kHz deviation. First note the zone called "required bandwidth," which is the legendary 13 kHz wide. This zone shows the sidebands down to -40 dB from the carrier's unmodulated level. It is evident that some remaining sidebands are present, down to the -80 dB level, with the noise floor of the test instrument, an HP8568B spectrum analyzer.

On the left of the diagram, we have illustrated the filter shapes of typical consumer receivers spaced 30, 20, and 15 kHz away from the carrier frequency of the signal. Notice that at 30 kHz spacing, no power from the signal is entering the receiver's passband, down

to the resolution of the instrument. At 20 kHz spacing, the edge of the receiver passband intersects a small portion of the signal, indicated by the area labeled 1. At 15 kHz spacing, more of the signal is in the receiver passband, as noted by areas 1 and 2. While it would be difficult to quantify the difference from this diagram, our tests have shown that this difference is in the range of 30 to 45 dB. If the more liberal EIA RS-204-C test were performed, using a 400 Hz tone, the receivers would pass at 20 kHz separation and fail at 15 kHz spacing.

We hope this report is informative and will be useful as you make your decisions on coordinating repeaters, both in frequency and geographical separation.

### references

1. *Reference Data for Radio Engineers*, Sixth Edition, ITT and Howard W. Sams, Indianapolis, Indiana 46268, 1981, pages 23-7 to 23-9.
2. Carleton Maylott, W2YE, "Close Look at Amateur FM," *ham radio*, August, 1979, page 46.
3. R. Harold Kinley, *Standard Radio Communications Manual*, Prentice Hall, 1985.
4. *EIA Standard RS-204-C*, Electronic Industries Association, Washington, D.C., page 16, paragraph 14.2



# AMATEUR TELEVISION



## KPA5 1 WATT 70 CM ATV TRANSMITTER BOARD

- **APPLICATIONS:** Cordless portable TV camera for races & other public service events, remote VCR, etc. Remote control of R/C airplanes or robots. Show home video tapes, computer programs, repeat SSTV to local ATVers. DX depends on antennas and terrain typ. 1 to 40 miles.
- **FULL COLOR VIDEO & SOUND** on one small 3.25x4" board.
- **RUNS ON EXTERNAL 13.8 VDC** at 300 ma supply or battery.
- **TUNED WITH ONE CRYSTAL** on 426.25, 434.0, or 439.25 mHz.
- **2 AUDIO INPUTS** for a low Z dynamic and line level audio input found in most portable color cameras, VCRs, or home computers.
- **APPLICATION NOTES & schematic** supplied for typical external connections, packaging, and system operation.
- **PRICE ONLY \$159** delivered via UPS surface in the USA. Technician class amateur license or higher required for purchase and operation.

**WHAT IS REQUIRED FOR A COMPLETE OPERATING SYSTEM?** A TV set with a TVC-2 or TVC-4 420-450 mHz to channel 3 downconverter, 70 cm antenna, and coax cable to receive. Package up the KPA5, add 12 to 14 vdc, antenna, and any TV camera, VCR, or computer with a composite video output. Simple, eh?

**CALL OR WRITE FOR OUR COMPLETE CATALOG & more info** on atv downconverters, antennas, cameras, etc., or who is on in your area.

**TERMS:** Visa, Mastercard, or cash only UPS COD by telephone or mail. Telephone orders & postal MO usually shipped within 2 days, all other checks must clear before shipment. Transmitting equipment sold only to licensed amateurs verified in 1984 Calbook. Calif. include sales tax.

(818) 447-4565 m-f 8am-6pm pst.

**P.C. ELECTRONICS**  
Tom W6ORG Maryann WB6YSS



2522 Paxson Lane  
Arcadia CA 91006

## appendix

Of the three handhelds tested (HT1, HT2, and HT3 — see **table A1**) variation existed from one unit to the other and also from the better side to the worse side of the filter. Because this test is made on the side of the filter (response) and not farther away from the passband, *the results will be very sensitive to the frequency to which the receiver is tuned.* Therefore, if the receiver drifts, it will change the better and worse isolation figures even more. There is also something else at work here: notice that HT3 shows considerable variation at 15 kHz from one side of the filter to the other, but its figures are more nearly equal at 20 and 30 kHz than HT1's. This is a dramatic demonstration of why a performance test like this is so much more revealing than merely quoting the nominal specification of the filter element.

**table A1. RS-204-C test results for three handhelds (interfering signal, 400 Hz).**

Channel Spacing:	15 kHz	20 kHz	30 kHz
dB isolation (HT1)	32/50	48/70	69/77
(HT2)	58/69	76/80	83/83
(HT3)	23/66	70/73	76/77

This table is not meant to compare one brand name against the other (thus the anonymity) since none of the units are at their brand-new performance levels, but have been in use for varying lengths of time. Variation between individual units of a given model may also be considerable. To compare given models fairly, we would have to test several of each type to obtain a sample large enough to be considered representative of its series.

More important, though, is the difference in readings between the upper and lower adjacent channel tests and its effect on performance. Remember, the EIA (specification) procedure calls for using the lower of the two figures.

Finally, perhaps the EIA-70 dB specification is not meant for HTs; considering their intended use, it may be acceptable for HTs to have a lower isolation value since they are typically operated closer to the repeater and use a much lower gain and altitude antenna than found on most home or mobile installations.

ham radio

✓ 114

**ICOM  
SPECIAL  
IC-745  
\$789.00  
Plus shipping**

MA. ★

# TEL-COM ★

*Electronic Communications*

Authorized Dealers For

**KENWOOD & ICOM**

Also displaying the popular accessories needed to complete a HAM STATION . . .

- ARRL PUBLICATIONS • AEA PRODUCTS • AMPHENOL
- ALPHA DELTA • ASTRON • AUSTIN ANTENNAS • AVANTI
- BELDEN • BENCHER • B & W • DAIWA • HAM-KEY
- HUSTLER • KLM • LARSEN • MIRAGE • ROHN
- TELEX/HY-GAIN • VIBROPLEX • WELZ • ETC.

OPEN SIX DAYS A WEEK

✓ 113

**KENWOOD  
SPECIAL  
NEW  
TS-940S  
with automatic  
tuner**

**\$1765.00  
Plus shipping**

**Telephone 617/486-3400, 3040**


**675 Great Rd., (Rte. 119) Littleton, MA 01460  
1/4 miles from Rte. 495 (Exit 31) toward Groton, Mass.**

# THE MOST AFFORDABLE REPEATER

ALSO HAS THE MOST IMPRESSIVE PERFORMANCE FEATURES

(AND GIVES THEM TO YOU AS STANDARD EQUIPMENT!)

Band	Kit	Wired
10M,6M, 2M,220	\$680	\$880
440	\$780	\$980


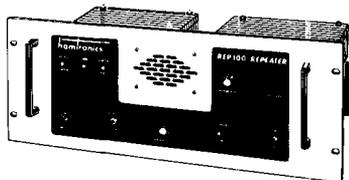


## FEATURES:

- SENSITIVITY SECOND TO NONE; 0.15 uV (VHF), 0.2 uV (UHF) TYP.
- SELECTIVITY THAT CAN'T BE BEAT! BOTH 8 POLE XTAL FILTER & CERAMIC FILTER FOR > 100 dB AT ± 12KHZ. HELICAL RESONATOR FRONT ENDS TO FIGHT DESENSE & INTERMOD.
- OTHER GREAT RECEIVER FEATURES: FLUTTER-PROOF SQUELCH, AFC TO COMPENSATE FOR OFF-FREQ TRANSMITTERS, SEPARATE LOCAL SPEAKER AMPLIFIER & CONTROL.
- CLEAN, EASY TUNE TRANSMITTER; UP TO 20 WATTS OUT (UP TO 50W WITH OPTIONAL PA).
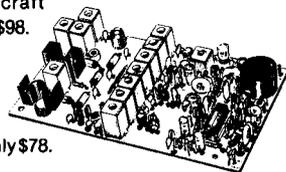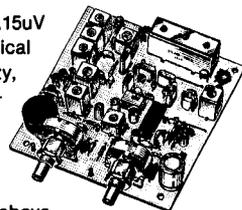
## HIGH QUALITY XMTR & RCVR MODULES FOR REPEATERS, LINKS, TELEMETRY, ETC.

- **R144/R220 FM RCVRs** for 2M or 220 MHz. 0.15uV sens.; 8 pole xtal filter & ceramic filter in i-f, helical resonator front end for exceptional selectivity, > 100 dB at ± 12kHz, best available today. Flutter-proof squelch. AFC tracks drifting xmtrs. Xtal oven avail. Kit only \$138.
- **R451 FM RCVR** Same but for uhf. Tuned line front end, 0.3 uV sens. Kit only \$138.
- **R76 FM RCVR** for 10M, 6M, 2M, or 220. As above, but w/o AFC or hel. res. Kits only \$118. Also avail w/4 pole filter, only \$98/kit.
- **R110 VHF AM RECEIVER** kit for VHF aircraft or ham bands or Space Shuttle. Only \$98.
- **T51 VHF FM EXCITER** for 10M, 6M, 2M, or 220 MHz. 2 Watts continuous, up to 3W intermittent. \$68/kit.
- **T451 UHF FM EXCITER** 2 to 3 Watts. Kit only \$78. Xtal oven avail.
- **VHF & UHF LINEAR AMPLIFIERS.** For either FM or SSB. Power levels from 10 to 45 Watts to go with exciter & xmtg converters. Several models. Kits from \$78.



NOW—FCC TYPE-ACCEPTED TRANSMITTERS & RECEIVERS AVAILABLE FOR HIGH-BAND & UHF. CALL FOR DETAILS.

## RECEIVING CONVERTERS

Models to cover every practical rf & if range to listen to SSB, FM, ATV, etc. NF = 2dB or less.



### VHF MODELS

Kit with Case	\$49
Less Case	\$39
Wired	\$69

### UHF MODELS

Kit with Case	\$59
Less Case	\$49
Wired	\$75

Antenna Input Range	Receiver Output
28-32	144-148
50-52	28-30
50-54	144-148
144-146	28-30
145-147	28-30
144-144.4	27-27.4
146-148	28-30
144-148	50-54
220-222	28-30
220-224	144-148
222-226	144-148
220-224	50-54
222-224	28-30

SCANNER CONVERTERS Copy 806 MHz band on any scanner. Wired/tested ONLY \$88.

## TRANSMIT CONVERTERS

For SSB, CW, ATV, FM, etc. Why pay big bucks for a multi mode rig for each band? Can be linked with receive converters for transceive. 2 Watts output vhf, 1 Watt uhf.

For VHF,  
Model XV2  
Kit \$79  
Wired \$149  
(Specify band)

Exciter Input Range	Antenna Output
28-30	144-146
28-29	145-146
28-30	50-52
27-27.4	144-144.4
28-30	220-222*
50-54	220-224
144-146	50-52
50-54	144-148
144-148	28-30


For UHF,  
Model XV4  
Kit \$99  
Wired \$169

Exciter Input Range	Antenna Output
28-30	432-434
28-30	435-437
50-54	432-436
61.25	439.25
144-148	432-436*

\*Add \$20 for 2M Input

VHF & UHF LINEAR AMPLIFIERS. Use with above. Power levels from 10 to 45 Watts. Several models, kits from \$78.

## LOW-NOISE PREAMPS

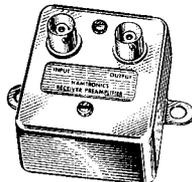

### Hamtronics Breaks the Price Barrier!

No Need to Pay \$80 to \$125 for a GaAs FET Preamp.


### FEATURES:

- Very Low Noise: 0.7 dB VHF, 0.8 dB UHF
- High Gain: 18 to 28 dB, Depending on Freq.
- Wide Dynamic Range for Overload Resistance
- Latest Dual-gate GaAs FET, Very Stable

MODEL	TUNES RANGE	PRICE
LNG-28	26-30 MHz	\$49
LNG-50	46-56 MHz	\$49
LNG-144	137-150 MHz	\$49
LNG-160	150-172 MHz	\$49
LNG-220	210-230 MHz	\$49
LNG-432	400-470 MHz	\$49
LNG-800	800-960 MHz	\$49
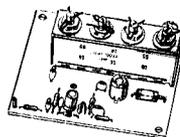
## HELICAL RESONATOR PREAMPS

Low-noise preamps with helical resonators reduce intermod and cross-band interference in critical applications. 12 dB gain.



Model	Tuning Range	Price
HRA-144	143-150 MHz	\$49
HRA-220	213-233 MHz	\$49
HRA-432	420-450 MHz	\$59
HRA-( )	150-174 MHz	\$54
HRA-( )	450-470 MHz	\$64

## ACCESSORIES

- **MO-202 FSK DATA MODULATOR.** Run up to 1200 baud digital or packet radio signals through any FM transmitter. Automatically keys transmitter and provides handshakes. 1200/2200 Hz tones. Kit only \$45.
- **DE-202 FSK DATA DEMODULATOR.** Use with any FM receiver to detect packet radio or other digital data in "202" modem format. Provides audio conditioning and handshakes. Kit only \$38.
- **COR-2 KIT** With audio mixer, local speaker amplifier, tail & time-out timers. Only \$38.
- **COR-3 KIT** as above, but with "courtesy beep". Only \$58.
- **CWID KITS** 158 bits, easily field programmable, clean audio. Kit only \$68.
- **A16 RF TIGHT BOX** Deep drawn alum. case with tight cover and no seams. 7 x 8 x 2 inches. Designed especially for repeaters. \$20.
- **DTMF DECODER/CONTROLLER KITS.** Control 2 separate on/off functions with touchtones®, e.g., repeater and autopatch. Use with main or aux. receiver or with Autopatch. Only \$90
- **AUTOPATCH KITS.** Provide repeater autopatch, reverse patch, phone line remote control of repeater, secondary control via repeater receiver. Many other features. Only \$90. Requires DTMF Module.
- **SIMPLEX AUTOPATCH.** Use with your FM transceiver. System includes DTMF & Autopatch modules above and new Timing module to provide simplex autopatch and reverse autopatch. Complete patch system only \$200/kit. Call or write for details.

- **SEND \$1.00 for 40 page CATALOG** (Send \$2.00 or 4 IRC's for overseas mailing)
- **Order by phone or mail • Add \$3 S & H per order** (Electronic answering service evenings & weekends)
- **Use VISA, MASTERCARD, Check, or UPS COD.**

# hamtronics, inc.


65-E MOUL ROAD • HILTON NY 14468

Phone: 716-392-9430

Hamtronics® is a registered trademark
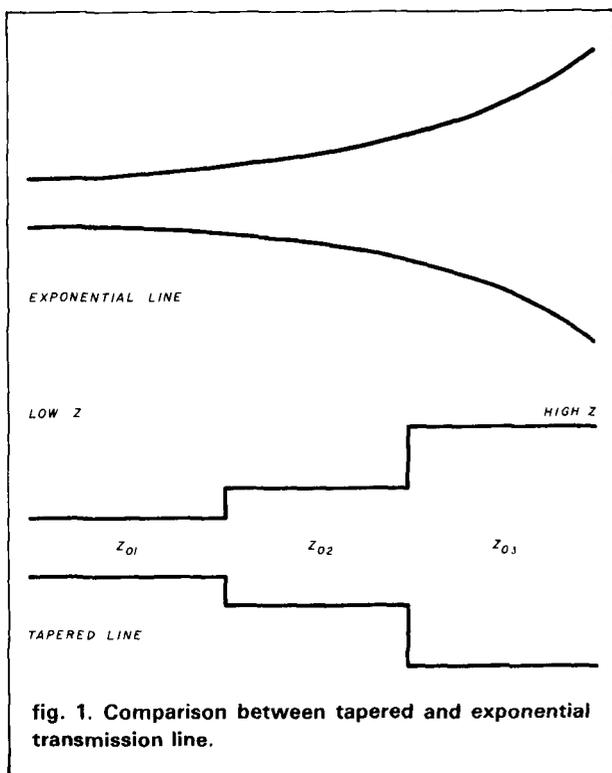
# calculating the input impedance of a tapered vertical

Schelkunoff procedure  
— best method to use



In the last decade there has been a tendency among Radio Amateurs to use vertical whip antennas on 80 and 160 meters. One clear advantage of using tapered whip elements, constructed of aluminum tubing, is their durability under severe weather conditions. But the fundamental question and the main obstacle to even more widespread Amateur use of the antenna is the problem of accurately determining the antenna feedpoint impedance for various tapers.

For cylindrical element length-to-diameter ratios, the feedpoint impedances are readily solvable by analytical methods such as Hallen's integral equation,<sup>1</sup> the induced EMF method,<sup>2</sup> and Schelkunoff's input impedance equation.<sup>3</sup> Using a computer and the "method of moments" approach, employing matrix algebra techniques,<sup>4</sup> will also provide answers.

## which approach to use?

The basic question to be answered is what method should be employed to solve for the feedpoint impedance of a tapered vertical before its actual construction begins. Perhaps a clue is provided in the analytical method described by James Lawson, W2PV, in his well-known *ham radio* series on Yagi-Uda antennas.<sup>5</sup> Lawson stated that the inductance to capacitance ( $L/C$ ) ratio of a tapered element is related to a geometrical mean diameter. Each cylindrical section has its own  $L/C$  ratio, or more specifically, its own surge impedance  $Z_0 = \sqrt{L/C}$ . This formula is used to describe an exponential (Collins) transmission

By Walter J. Schulz, K3OQF, 3617 Nanton Terrace, Philadelphia, Pennsylvania 19154

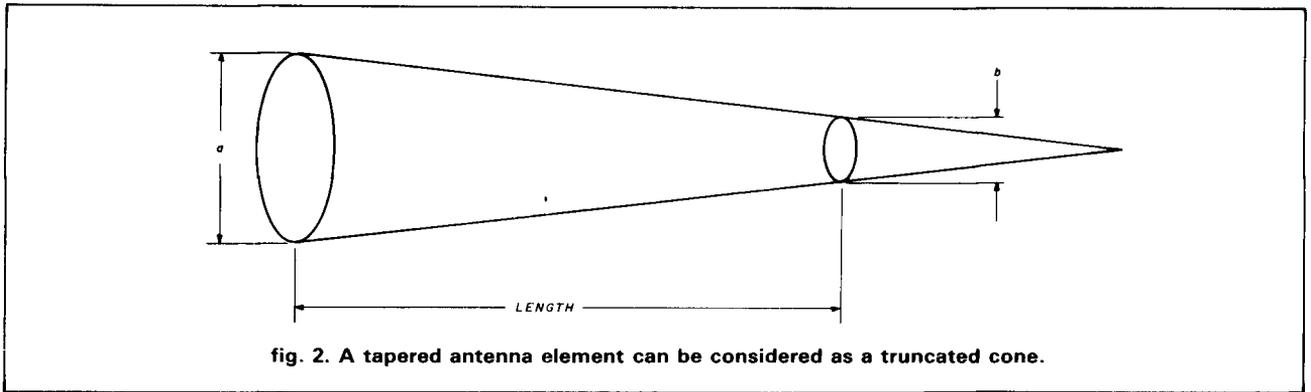


fig. 2. A tapered antenna element can be considered as a truncated cone.

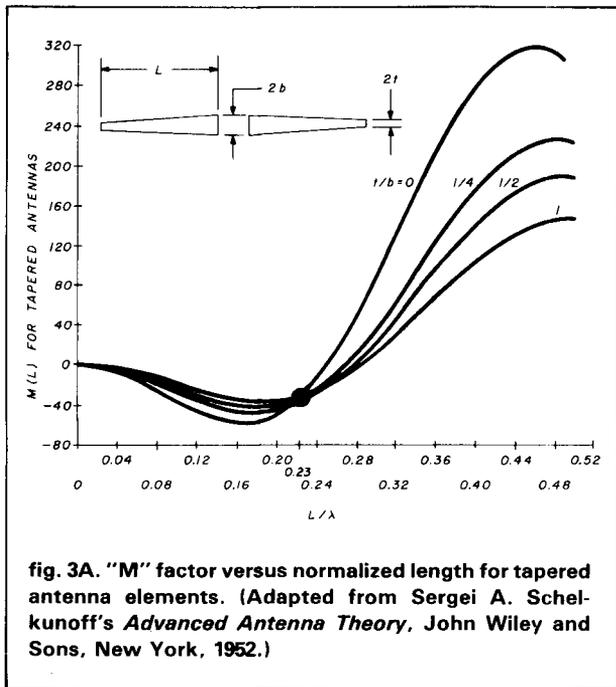


fig. 3A. "M" factor versus normalized length for tapered antenna elements. (Adapted from Sergei A. Schelkunoff's *Advanced Antenna Theory*, John Wiley and Sons, New York, 1952.)

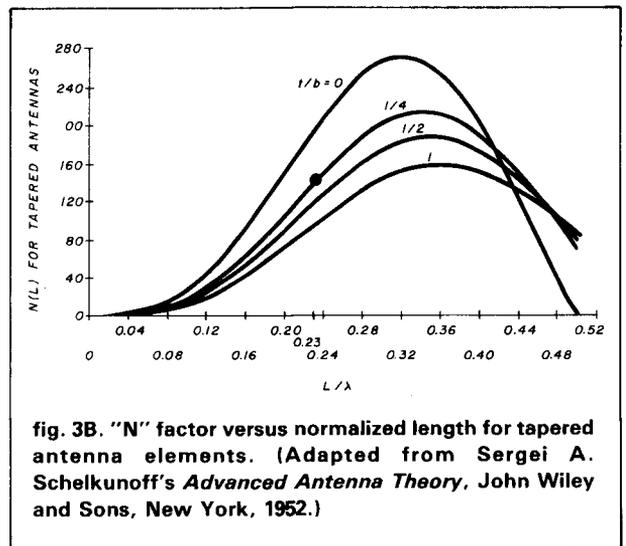


fig. 3B. "N" factor versus normalized length for tapered antenna elements. (Adapted from Sergei A. Schelkunoff's *Advanced Antenna Theory*, John Wiley and Sons, New York, 1952.)

line used for matching two different impedances (see fig. 1). Notice that each section of the exponential transmission line has its own surge or characteristic impedance. An impedance transformation occurs in either direction as a result of the taper. Consequently a tapered antenna element can be considered as a tapered exponential transmission line that has an average characteristic impedance described as a geometrical mean of its diameter.

W2PV took note of this physical relationship, applied that relationship to Yagi elements, and developed a method to evaluate the taper. An even earlier method, developed by Sergi A. Schelkunoff at Bell Labs is easier to work out — with either a pencil and paper or with a handheld calculator — yet still provides accurate results.

### describing a tapered vertical

A tapered vertical element may be thought of as a truncated cone, as shown in fig. 2, with specific base and tip diameter and length, using cylindrical elements that telescope into one another, exhibiting impedance discontinuities at each section boundary. Consequently, eq. 1 can be used to describe a tapered vertical element shape factor.<sup>7</sup>

$$Z_0 = 60 \ln(2L/b) + 60 t/b - t \ln(t/b) \quad (1)$$

where  $L$  = length (inches)

$b$  = base radius (inches)

$t$  = tip radius (inches)

Not only was Schelkunoff able to determine the shape factor, but he was also successful in making the necessary engineering approximations to equate antennas to transmission line behavior. This resulted in the modification of the basic transmission line formula for the solution of feedpoint impedance values for arbitrarily shaped antennas.<sup>3</sup>

$$Z_{in} = Z_0 \frac{R_a \sin G + j(X_a - N) \sin G - j(2Z_0 - M) \cos G}{(2Z_0 + M) \sin G + (X_a + N) \cos G - jR_a \cos G} \quad (2)$$

$$R_a = 60(\gamma + \ln 2G - Ci 2G) + 30(\gamma + \ln G - 2 Ci 2G + Ci 4G) \cos 2G + 30(Si 4G - 2 Si 2G) \sin 2G \quad (3)$$

$$X_a = 60 Si 2G + 30(Ci 4G - \ln G - \gamma) \sin 2G - 30 Si 4G \cos 2G \quad (4)$$

where  $M$  and  $N$  values are taken from **figs. 3A** and **3B**

$G$  = antenna height in radians

$\gamma$  = 0.5772

$Si$  = sine integral

$Ci$  = cosine integral

### example

It is desired that a vertical whip antenna is to operate on 3.8 MHz. Its height is 60 feet (18.29 meters) or 720 inches (1829 cm). The base diameter is 3 inches (7.62 cm) and its tip diameter measures 3/4 inch (2 cm). What is the vertical feedpoint impedance at this operating frequency? It is assumed that the vertical sits on a perfect ground radial system that has a minimum resistance.

**Step 1.** Find the shape factor ( $Z_0$ ).

$$Z_0 = 60 \ln 2 \cdot \frac{720}{1.5} + 60 \frac{0.375}{1.5} - 0.375 \cdot \ln \frac{0.375}{1.5} = 384.3$$

**Step 2.** Find the  $M$  and  $N$  values from **figs. 3A** and **3B**.

$$\text{with } t/b = \frac{0.375}{1.5} = 0.25$$

$$M(1) = -38 \text{ and } N(1) = +125$$

**Step 3.** Express fractional wavelength of antenna in degrees or radians.

$$\text{fractional wavelength} = \frac{\text{height}}{984/\text{Freq (MHz)}}$$

$$= \frac{60}{(984/3.8)} = 0.2317$$

$$0.2317 \cdot 360^\circ = 83.4^\circ$$

$$\text{or } \frac{83.4^\circ}{57.3} = 1.4557 \text{ radians}$$

**Step 4.** Calculate  $R_a$  value.

$$R_a = 60[0.5772 + \ln 2.9114 - (+0.15)] + 30[0.5772 + \ln 1.4557 - 2(+0.15) + (-0.10)] \cos 2.9114 + 30(1.4356 - 2 \cdot 1.8431) \sin 2.9114 = 58.2$$

**Step 5.** Calculate  $X_a$  value.

$$X_a = 60(1.8431) + 30(-0.10 - \ln 1.4557 - 0.5772) \sin 2.9114 - 30 \cdot 1.4356 \cdot \cos 2.9114 = 145.31$$

**Step 6.** Calculate the vertical feedpoint impedance.

$$Z_{in} = 384.3 \left[ \frac{58.2 \sin 1.4557 + j(145.3 - 125) \sin 1.4557 - j(2 \cdot 384.3 + 38) \cos 1.4557}{(2 \cdot 384.3 - 38) \sin 1.4557 + (145.3 + 125) \cos 1.4557 - j58.2 \cos 1.4557} \right]$$

$$Z_{in} = (384.3 + j0) \left[ \frac{57.8 - j72.5}{756.8 - j6.7} \right] = (384.3 + j0)(0.0772 - j0.0951) = 29.7 - j36.5$$

$$= 29.7 \text{ ohms} - j36.5 \text{ ohms}$$

Using an HP-41C calculator eliminated the manual labor and produced answers more quickly (see **Appendix**).

This program can be used not only on tapered vertical antennas, but on tapered Yagi elements as well. To do this, calculate half the dipole length just as if it were a vertical, and then multiply the answer by two. This new product is the feedpoint impedance for a tapered dipole element.

## appendix

### HP-41C calculator program for finding feedpoint impedance of tapered vertical antenna

#### HP-41C instructions

- Execute SIZE and key in 020.
- Key in ZB program and subroutines  $Z_0$ , O,  $R_a$ ,  $X_a$ .
- Key in functions memory register 01 to 11.
- Execute program ZB.
- Each subroutine answer will be displayed, to continue program depress R/S key.

functions	memory registers
Si 2G	STO 01
Si 4G	STO 02
Ci 4G	STO 03
2G	STO 04
G	STO 05
Ci 2G	STO 06
M function	STO 07
N function	STO 08
base radius	STO 09
tip radius	STO 10
length	STO 11

#### references

1. Erik Hallen, *Theoretical Investigations into the Transmitting and Receiving Qualities of Antennae*, Nova Acta Regiae Soc. Sci. Upsaliensis, 1938, Serial IV, 11 No. 4, pages 1-44.
2. Kai Fong Lee, *Principles of Antenna Theory*, John Wiley and Sons, New York, 1984, pages 98-101.
3. Sergei A. Schelkunoff, "Theory of Antennas of Arbitrary Size and Shape," *Proceedings of the IRE*, September, 1941, pages 493-520.
4. Roger F. Harrington, *Field Computation by Moment Methods*, Robert E. Krieger Publishing Company, Malabar, Florida, 1968, pages 64-75.
5. James L. Lawson, W2PV, *ham radio*, January, February, May, June, July, September, October, November, December, 1980. (For limited time only a set of nine back issues containing W2PV's series of articles on yagi antenna design will be made available at the reduced price of \$9.86 postpaid to U.S. addresses, \$16.95 to addresses outside the U.S. Foreign payment accepted in U.S. funds drawn on U.S. bank only. Address request to Ham Radio's Bookstore, Greenville, NH 03048. Supplies are limited; order promptly.)
6. James L. Lawson, W2PV, "Yagi Antennas: Practical Designs," *ham radio*, December, 1980, page 33.
7. Sergei A. Schelkunoff and Harald T. Friis, *Antennas: Theory and Practice*, John Wiley and Sons, New York, 1952, pages 425-431.

#### ham radio

### August 1985 short circuit

In "Voltage Controlled Oscillator Uses Ceramic Resonators," (K2BLA, June 1985, page 23), two base bias resistors for the 2N3904 were inadvertently omitted from fig. 8. Add a 2.2k resistor from base to ground and a 10k resistor from the same base to +15 VDC.

```

01*LBL "ZB"      55 CLX      01*LBL "0"      01*LBL "Xa"
02 XEQ "Ra"      56 RCL Z      02 XEQ "Z0"     02 RCL 03
03 RCL 05        57 STO 19     03 2            03 RCL 05
04 SIN          58 CLX      04 *            04 LN
05 *            59 0          05 RTN         05 -
06 STO 16       60 ENTER↑    06 END         06 .5772
07 CLX          61 XEQ "Z0"   07 -           07 -
08 XEQ "Xa"     62 RCL 19     08 30          08 30
09 RCL 06       63 RCL 18     09 *           09 *
10 -            64 XROM "C*"   10 RCL 04      10 RCL 04
11 RCL 05       65 "ZB IN=R"  11 SIN         11 SIN
12 SIN          66 AVIEW      12 *           12 *
13 *            67 RCL X      13 ENTER↑     13 ENTER↑
14 ENTER↑      68 STOP      14 RCL 01      14 RCL 01
15 XEQ "0"     69 CLX      15 60          15 60
16 RCL 07       70 "J="      16 *           16 *
17 -            71 AVIEW      17 +           17 +
18 RCL 05       72 RCL Z      18 ENTER↑     18 ENTER↑
19 COS          73 STOP      19 RCL 04      19 RCL 04
20 *            74 END      20 COS        20 COS
21 -            01*LBL "Z0"  21 RCL 02     21 RCL 02
22 STO 17       02 RCL 04     22 *           22 *
23 CLX          03 LN         23 30          23 30
24 XEQ "Ra"    04 .5772     24 *           24 *
25 RCL 05       15 +         25 CHS        25 CHS
26 COS          16 RCL 06   26 +           26 +
27 *            17 2         27 STOP       27 STOP
28 -1           18 *         28 RTN        28 RTN
29 *            19 CHS        29 END         29 END
30 STO 14       20 +         30 CHS        30 CHS
31 CLX          21 RCL 03    31 2           31 2
32 XEQ "0"     22 +         32 *           32 *
33 RCL 07       23 RCL 04    33 CHS        33 CHS
34 +            24 COS        34 RCL 02     34 RCL 02
35 RCL 05       25 *         35 +           35 +
36 SIN          26 30        36 RCL 04     36 RCL 04
37 *            27 *         37 SIN        37 SIN
38 ENTER↑      28 +         38 *           38 *
39 XEQ "Xa"    29 ENTER↑   39 30          39 30
40 RCL 08       30 RCL 01    40 *           40 *
41 +            31 2         41 +           41 +
42 RCL 05       32 *         42 STOP       42 STOP
43 COS          33 CHS        43 RTN        43 RTN
44 *            34 RCL 02   44 END         44 END
45 +            35 +         45 +           45 +
46 STO 15       36 RCL 04    46 STO 15     46 STO 15
47 CLX          37 SIN        47 CLX        47 CLX
48 RCL 17       38 *         48 RCL 17     48 RCL 17
49 RCL 16       39 30        49 RCL 16     49 RCL 16
50 RCL 14       40 *         50 RCL 14     50 RCL 14
51 RCL 15       41 +         51 RCL 15     51 RCL 15
52 XROM "C/"   42 STOP      52 XROM "C/"  52 XROM "C/"
53 RCL X        43 RTN        53 RCL X      53 RCL X
54 STO 18       44 END        54 STO 18     54 STO 18

```

fig. A1. HP41C calculator program for finding feedpoint impedance of tapered vertical antenna.

# TIME FOR AN AEA BREAKTHROUGH

The high quality of AEA products is appreciated long after the price paid is forgotten.

**No Antenna  
No Radio  
No TV!**



**\$99.95**

## THE FANTASTIC DOCTOR DX™ CW Band Simulation That Is So Real You Won't Believe It!

- Will improve the operating skills of ANY CW operator!
- More fun than ANY Morse Code trainer yet devised.
- Use with a C-64, TV set, and key (or keyer).
- Experience the thrill of a "DXpedition" to anywhere in the world.
- Operate anytime you want, ideal for travelers.
- Impressive award certificates available for verified performance.
- On-going contests: 8-hour sprint and 24-hour marathon.

## HOT ROD™

½ Wave Telescope Antenna **\$24.95\***

- Fewer telescopic sections than any ½ wave whips.
- Shorter and lighter than all ½ wave whips
- Better performance than a ½ wave whip when mounted on a handie talkie.
- Special matching network designed by Professor D.K. Reynolds (co-inventor of Isopole™ antenna).

- Most gain attainable for length of antenna—3dBd(0dBd for JR models).
- Best decoupling of any commercial VHF base station antenna available.
- More gain than many antennas claiming up to 7 dB gain—don't be fooled by misleading claims!
- Zero degree angle of radiation
- Factory-tuned matching network.
- Greater bandwidth than any competitive product.
- DC grounded for static discharge protection.
- Documented cases of wind survival in 140+ mph hurricanes.
- Easier than any competitive antenna to assemble.

**Mast  
Not  
Included**

ISO = 144 or 220—\$49.95

ISO = 440—\$69.95

## ISOPOLE ANTENNA™



## CP-1 \$239.95\* Computer Patch™ Interface

- Better performance than any competitive product
- Dual channel filtering with auto threshold correction
- Variable shift
- 117 VAC power supply included



## DOCTOR QSOT™ \$79.95 Morse Code Trainer

- Makes Morse Training Fun, Fun, Fun!!!
- Plug-in Cartridge For C-64 Computer
- Simulates Real Morse Raghews
- Can Operate With Only C-64 and TV Set



## PKT-1 Packet Controller \$499.95

- Multitasking - Can receive information from the keyboard and off the air at the same time.
- Uses TAPR circuitry and firmware.
- Senses squelch to detect busy channel.
- Send computer files error free.
- Data detect (DCD) for HF operation.
- Digital radio communications for computer to computer.
- Every PKT-1 is a digipeater
- Operates from 9-15 VDC

## GET YOUR FIRST HAM RADIO LICENSE, OR INCREASE YOUR CODE SPEED SO YOU MAY UPGRADE!



+



=

## AMATEUR RADIO STARTER KIT \$39.95

- Includes Morse University™, Morse code training software.
- Morse training routine teach you the Morse code a character at a time.
- Proficiency routine helps you increase code speed, and upgrade your license class.
- Receiving audio/video game gives you code practice under pressure.
- Sending analysis routine helps you improve your sending ability.

- Keyboard input allows you to compose your own code practice sessions.
- More complete than any Morse code trainer now available.
- Includes the ARRL book "Tune in the World" to help you get your first license.
- Club and license information for your area.
- Use with a C-64 (or C-128) & T.V. set.

**NEW!** MP-1  
MICROPATCH™  
\$159.95\*



- Morse/Baudot/ASCII/AMTOR
- Use any AEA software
- Compact and Economical
- Operates from 12-16 VDC.

**NEW!** ATU-1000  
ADVANCED  
TERMINAL UNIT



\$1195

- World's most advanced terminal unit/computer interface
- 32 poles, active filtering
- Set filters & AFSK tones to one Hertz
- TTL, RS-232, loop keyer incl

**NEW!** CP-100 COMPUTER  
PATCH™  
\$369.95\*



- 170/425/850 or variable shift
- Front-panel squelch
- Built-in monitor speaker
- Discriminator-style tuning for AMTOR

## Unmatched Software For C-64 And VIC-20 Computers

**MBA-TOR™**—The most advanced software written for Morse-Baudot-ASCII-AMTOR including mail drop.  
**MARSTXT™**—A special Morse-Baudot-ASCII package written especially for MARS and other traffic operators.  
**SWLSTXT™**—The most sophisticated software available for the shortwave listening enthusiast. Automatic data analysis: Morse, Baudot, ASCII, AMTOR, and SITOR.

AEA also offers Morse, Baudot, and ASCII software for the following computers: Apple II, II+, IIe; IBM-PC.

## \*Retail Prices MIDWEST AMATEUR RADIO SUPPLY

3456 Fremont Avenue, North  
Minneapolis, MN 55412

Store Hours: Mon.-Fri. 9-6, Saturday 9-3

For service call: (612) 521-4662

For orders call: 1-800-328-6365

115



**Brings you the  
Breakthrough!**

# design a toroidal tank circuit for your vacuum tube amplifier

No engineering  
degree required  
for this  
practical approach

Sooner or later every ham experiences three common desires: to build a big low-band power amplifier covering all of the ham bands, including 160 meters; to acquire (without benefit of an EE degree) sufficient knowledge to determine the exact number of turns and placement of taps for the tank coil therein; and to see, sometime soon — preferably within the limits of this century — the shrinking of the tank circuit to an acceptably small size.

Good news! With no more than a high school student's understanding of math, you can easily fulfill all three desires described. How? By simply using a powdered iron toroidal core network in the vacuum tube tank circuit in place of the huge conventional air dielectric coil.

Many solid state amplifiers, by virtue of their extremely low load impedances, use this technique; this is one reason for their reasonably small size. Yet only a few experimenters have actually tried using the toroid in the high impedance circuits of the vacuum tube.

After reading this article, you'll be able to either modernize the amplifier you have on the shelf or start from scratch, building one from the many excellent schematics available in periodicals, in Bill Orr's *Radio Handbook*,\* or in the various ARRL publications.

What effect does continuous high power have on the core? The high impedance of vacuum tubes causes the toroid core to become hot, causing its characteristics to change. The core would also saturate at the higher frequencies, causing instability and destruction of its composition. But the core described in this article will easily handle in excess of 2 kW maximum peak power, with no instability or saturation. (When I finished testing, the core was barely warm to the touch. Before you touch the coil, be sure the B+ is off and capacitors fully discharged to avoid shock.)

The toroid used was an Amidon T-400-2A. A nearly exact substitute for this is two Amidon T-400-2 units sandwiched together. If the amplifier you want to build is less than the 2 kW class, then a single T-400-2 core can be used. Even more space can be saved by using a pair of 3-inch (7.6 cm) T-300-2 toroids. These, however, will require five or six more turns of wire.

## choosing the right tube is an important first step

You must now decide on the type tube or tubes you intend using in your amplifier. Grounded grid operation in class AB1 is a favorite for single sideband. Let's suppose you have a number of 4CX300A tubes and sockets or 4CX250Bs or Fs that were obtained surplus. The very first number you must come up with is the operating plate load impedance. This you determine

By Robert E. Bloom, W6YUY, 8622 Rubio Avenue, Sepulveda, California 91343

\*Available from Ham Radio's Book Store, Greenville, New Hampshire 03048, \$12.95 plus \$3.50 shipping and handling.

from the level of plate voltage and current you'll be running. This information can be obtained from the sources previously mentioned or from data sheets from the tube manufacturer.

Suppose, for example, that SSB is your main interest and a pair of 4CX300A tubes is available. We've already stated that grounded grid would be the choice. But the 4CX series of tubes requires screen and grid bias voltages, so to call the operation "grounded grid" would be inaccurate. The tubes would really be running in a cathode driven circuit with the grids at RF ground potential, but above ground at DC so that the necessary voltages could be applied.

With drive applied in class AB operation, each tube draws 250 mA at a plate voltage of 2000 volts. This translates to a total input power level of 1000 watts. Output efficiency in this class of service is between 60 and 65 percent, or just over 650 watts. A circuit  $Q$  of 12 is needed to sustain the proper energy storage in the tank circuit.

### determining plate load resistance

We now have all of the information necessary to calculate one of the more important values needed, and that is the load impedance,  $R_p$ , the tubes will present to the input of the Pi network. For class AB operation

$$R_p = \frac{V_p}{1.8 \cdot I} \quad (1)$$

where  $V_p$  = plate voltage  
 $I$  = total plate current

$$\frac{2000}{1.8 \times 0.5} = \frac{2000}{0.9} = 2222 \text{ ohms}$$

For class "B" operation the formula becomes

$$R_p = \frac{V_p}{2 I_p} \quad (2)$$

Values of components  $C_1$ ,  $C_2$ , and  $L_1$  in a pi configuration are readily available.<sup>1</sup> An abbreviated version of it is provided in **table 1**. The data is divided into columns headed by the various values of plate load resistance in increments of 250 ohms. The tables are usually calculated for a  $Q$  of 10 or 12.  $C_1$  is called out as the plate tuning capacitor and  $C_2$  as the loading capacitor. The purpose of the pi networks is to step down the high level of plate load impedance to some value between 25 and 100 ohms to match the load, which is usually an antenna or possibly a dummy termination.

### pi values for other load impedances

The plots provided in **figs. 1, 2, and 3** can be used to find component values for intermediate load impe-

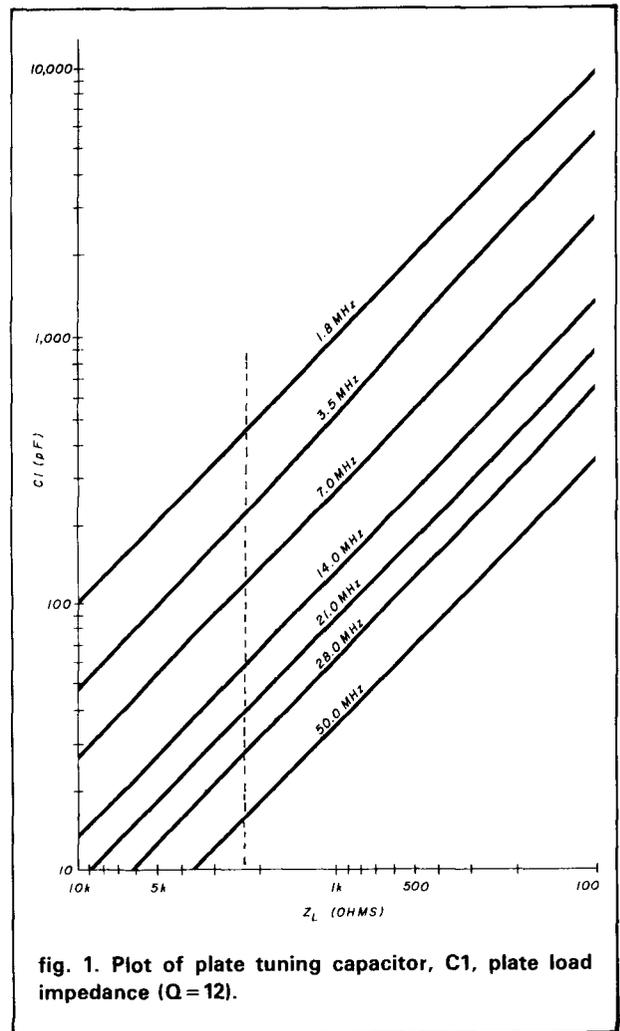


fig. 1. Plot of plate tuning capacitor,  $C_1$ , plate load impedance ( $Q = 12$ ).

dances simply by linearly interpolating. For example, if the value of capacitor  $C_1$  is needed for a load impedance half way between 1500 and 2000 ohms on the 160 meter band, take the arithmetic mean:

$$C_1 = \frac{531 + 430}{2} = 481 \text{ pF}$$

The same holds true for determining the values of  $C_2$  and  $L_1$ . The same interpolation method can be used to find pi values for the WARC band frequencies.

### effective pi-network capacitance

The two capacitors,  $C_1$  and  $C_2$ , in the pi-network, are effectively in series and shunt the coil so that the resultant capacity ( $C_T$ ) of the pair determines the resonant frequency (see **fig. 4**). Knowing  $C_T$  and the required resonant frequency, the coil value can be calculated. Evaluating:

$$C_T = \frac{C_1 \cdot C_2}{C_1 + C_2} = \frac{481 \times 2652}{481 + 2652} = 407 \text{ pF}$$

remember this, because we'll be using it later.

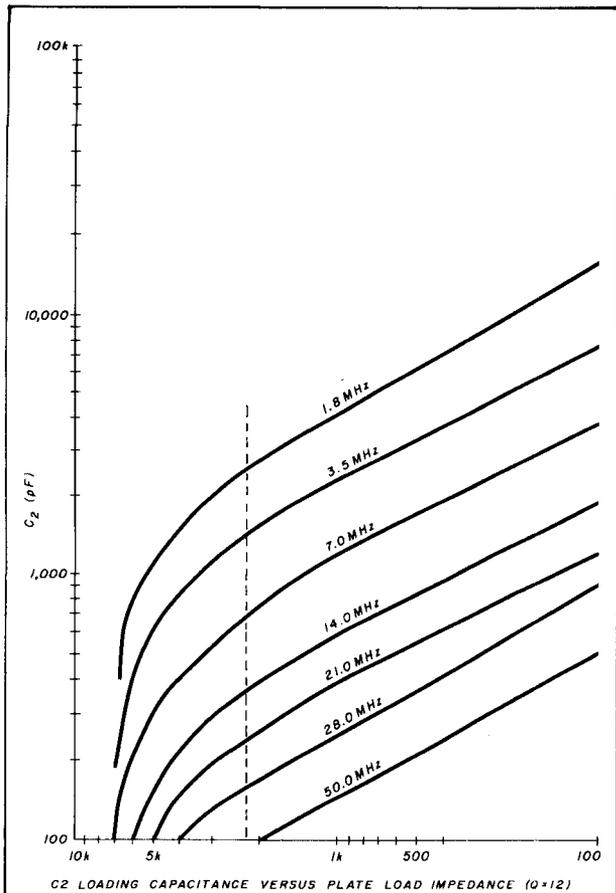


fig. 2. Loading capacitance versus plate load impedance (Q = 12).

## toroids in general

Information about toroidal cores and coils is available in many handbooks. Amidon's catalog, "Iron and Ferrite Cores," also includes general information about core characteristics.

Toroidal cores are basically of two types: powdered iron and ferrite. The permeability of the core ( $\mu$ ) helps determine the number of turns of wire required on a given physical size core; the larger the  $\mu$ , the fewer the number of turns required to provide the given inductance. Powdered iron cores generally have permeabilities from 1 up to 125, while ferrite cores have permeabilities ranging from 40 to 5000. Worthwhile noting is that with toroids, there is no such thing as a partial turn. If the wire goes through the hole, you have one turn and you do not get a second turn until the wire goes through the window once more.

The core size is another factor that affects the number of turns needed for a given inductance. This is directly related to the cross sectional area and consequently the flux density of the core. It sounds complicated, but is simplified by combining everything into

table 1. PI-network component values versus plate load impedance. (Capacitors C1, C2 in pF and inductance L1 in microhenries.)

Z <sub>L</sub> plate load impedance (ohms)				
capacitor C1				
band	1750 ohms	2000	2250	2500
160	610	531	481	430
80	318	273	246	220
40	159	136	123	110
30	120	102	93	83
20	80	68	62	55
15	53	45	41	37
10	40	34	32	30
capacitor C2				
160	3176	2865	2652	2440
80	1628	1473	1368	1263
40	815	737	684	632
30	610	492	457	422
20	407	368	342	316
15	272	246	229	211
10	204	184	171	158
inductor L1				
160	14.94	16.61	18.36	20.10
80	7.56	8.54	9.72	10.90
40	3.78	4.27	4.89	5.50
30	2.52	2.84	3.24	3.64
20	1.89	2.14	2.42	2.70
15	1.26	1.42	1.62	1.82
10	0.95	1.07	1.21	1.36

what is called the "A<sub>L</sub>" value, and this alone can be plugged into a simple formula resulting in the number of turns required for a given inductance. Although the ferrite material has a much higher  $\mu$  than the powdered iron core, ferrite is not as stable and saturates easily when used in power circuits.

Certain factors must be known in order to select the proper core for a specific job; first, we need the frequency range and permeability. Like resistors, all cores are marked according to a universal color code representing the compound mix number (table 2). The compound mix determines the core's frequency range. For the HF range, compound mix number 2 with a permeability of 10 is best. The core is powdered iron and is colored red.

Toroidal cores are prefixed either with a T for powdered iron or an FT for ferrite. The number following the T or FT identifies the diameter of the core. One of the more popular cores — because of its extensive application in antenna baluns — is the T-200-2, which is short for "toroidal powdered iron, 2 inches (5 cm) in diameter, No. 2 compound mix." Table 2 lists core colors and mixes versus frequency.

## selecting the core

The core I chose is a T-400-2A, which has an A<sub>L</sub>

# RAMSEY


# THE FIRST NAME IN ELECTRONIC TEST GEAR



## 20 MHz DUAL TRACE OSCILLOSCOPE

Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features include a component testing circuit for resistor, capacitor, digital circuit and diode testing • TV video sync filter • wide bandwidth & high sensitivity • internal graticule • front panel trace rotator • Z axis • high sensitivity x-y mode • regulated power supply • built-in calibrator • rock solid triggering • USA — add \$10.00 per unit for postage, overseas orders add 15% of total order for insured surface mail.

**\$399<sup>95</sup>\***

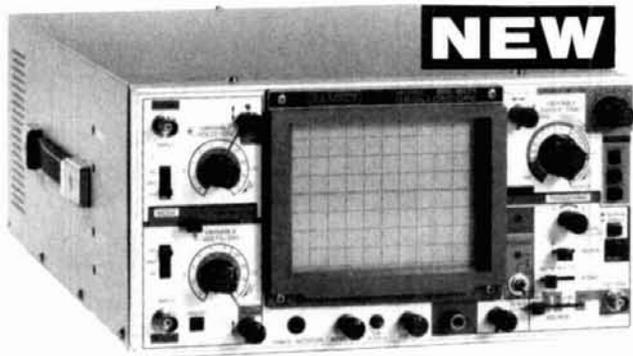

**NEW**

## 45 MHz DUAL SWEEP OSCILLOSCOPE

The Ramsey 625 is a dual time base, delayed sweep unit that includes a built-in signal delay line to permit clear viewing during very short rise times of high frequency waveforms. Other features include: variable trigger holdoff • 20 calibrated sweep time ranges from 0.5 ns/div. to 0.2 s/div. • fully adjustable sweep time • X5 sweep magnification • five trigger sources: CH1, CH2, LINE EXTERNAL and INTERNAL (V mode) • front panel x-y operation, Z axis input • sum difference of CH1, and CH2 waveforms displayed as single trace • sweep gate and sweep output • auto focus • single sweep. \*USA — add \$10.00 per unit for postage, overseas orders add 15% of total order for insured surface mail.

**\$799<sup>95</sup>\***



## RAMSEY D-1100 VOM MULTITESTER

Compact and reliable, designed to service a wide variety of equipment. Features include • mirror back scale • double-jeweled precision moving coil • double overload protection • an ideal low cost unit for the beginner or as a spare back-up unit.


**\$19<sup>95</sup>** test leads and battery included


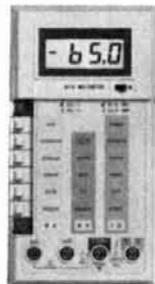
## NEW RAMSEY 1200 VOM MULTITESTER

Check transistors, diodes and LEDs with this professional quality meter. Other features include: decibel scale • 20K volt metering system • 3 1/2" mirrored scale • polarity switch • 20 measuring ranges • safety probes • high impact plastic case.

**\$24<sup>95</sup>** test leads and battery included



## RAMSEY D-3100 DIGITAL MULTIMETER

Reliable, accurate digital measurements at an amazingly low cost • in-line color coded push buttons, speeds range selection • abs plastic tilt stand • recessed input jacks • overload protection on all ranges • 3 1/2 digit LCD display with auto zero, auto polarity & low BAT indicator.

**\$49<sup>95</sup>** test leads and battery included



## CT-70 7 DIGIT 525 MHz COUNTER

Lab quality at a breakthrough price. Features • 3 frequency ranges each with pre amp • dual selectable gate times • gate activity indicator • 50mV @ 150 MHz typical sensitivity • wide frequency range • 1 ppm accuracy.

**\$119<sup>95</sup>** wired includes AC adapter

CT-70 kit ..... \$99.95  
BP-4 nicad pack ..... 8.95



## CT-90 9 DIGIT 600 MHz COUNTER

The most versatile for less than \$300. Features: 3 selectable gate times • 9 digits • gate indicator • display hold • 25mV @ 150 MHz typical sensitivity • 10 MHz timebase for WWV calibration • 1 ppm accuracy.

**\$149<sup>95</sup>** wired includes AC adapter

CT-90 kit ..... \$129.95  
OV-1 0.1 PPM oven timebase ..... 59.95  
BP-4 nicad pack ..... 8.95



## CT-125 9 DIGIT 1.2 GHz COUNTER

A 9 digit counter that will outperform units costing hundreds more. • gate indicator • 24mV @ 150 MHz typical sensitivity • 9 digit display • 1 ppm accuracy • display hold • dual inputs with preamps.

**\$169<sup>95</sup>** wired includes AC adapter

BP-4 nicad pack ..... 8.95



## CT-50 8 DIGIT 600 MHz COUNTER

A versatile lab bench counter with optional receive frequency adapter, which turns the CT-50 into a digital readout for most any receiver. • 25 mV @ 150 MHz typical sensitivity • 8 digit display • 1 ppm accuracy.

**\$169<sup>95</sup>** wired

CT-50 kit ..... \$139.95  
RA-1 receiver adapter kit ..... 14.95



## DM-700 DIGITAL MULTIMETER

Professional quality at a hobbyist price. Features include 26 different ranges and 5 functions • 3 1/2 digit, 1/2 inch LED display • automatic decimal placement • automatic polarity.

**\$119<sup>95</sup>** wired includes AC adapter

DM-700 kit ..... \$99.95  
MP-1 probe set ..... 4.95



## PS-2 AUDIO MULTIPLIER

The PS-2 is handy for high resolution audio resolution measurements, multiplies UIP in frequency • great for PL tone measurements • multiplies by 10 or 100 • 0.01 Hz resolution & built-in signal preamp/conditioner.

**\$49<sup>95</sup>** wired

PS-2 kit ..... \$39.95



## PR-2 COUNTER PREAMP

The PR-2 is ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for shifting RF • ideal receiver/TV preamp.

**\$44<sup>95</sup>** wired includes AC adapter

PR-2 kit ..... \$34.95



## PS-1B 600 MHz PRESCALER

Extends the range of your present counter to 600 MHz • 2 stage preamp • divide by 10 circuitry • sensitivity: 25mV @ 150 MHz • BNC connectors • drives any counter.

**\$59<sup>95</sup>** wired includes AC adapter

PS-1B kit ..... \$49.95

## ACCESSORIES FOR RAMSEY COUNTERS

- Telescopic whip antenna—BNC plug .. \$ 8.95
- High impedance probe, light loading ... 16.95
- Low pass probe, audio use ..... 16.95
- Direct probe, general purpose use ..... 13.95
- Tilt ball, for CT-70, 90, 125 ..... 3.95



PHONE ORDERS CALL  
**716-586-3950**

TELEX 466735 RAMSEY CI

TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased, return in original form for refund • add 6% for shipping and insurance to a maximum of \$10.00 • overseas add 15% for surface mail • COD add \$2.50 (COD in USA only) • orders under \$15.00 add \$1.50 • NY residents add 7% sales tax • 90 day parts warranty on all kits • 1 year parts & labor warranty on all wired units.

**RAMSEY**

RAMSEY ELECTRONICS, INC.  
2575 Baird Rd.  
Penfield, N.Y. 14626

of 360. As stated previously, two T-400-2 are a nearly exact equivalent; each 400-2 has an  $A_L$  of 185. Two stacked, therefore, would have an  $A_L$  of 370, because two of these together are a little thicker than a single 400-2A. You've probably guessed that a suffix letter relates to a core with a somewhat thicker than standard width and consequently a higher  $A_L$ . (Why the  $A_L$  number? This number represents the inductance in microhenries that 100 turns will produce on any given core.) From this important factor one can determine the number of turns required for a specific inductance.

The  $A_L$  number is used in a simple formula:

$$\text{Turns} = 100 \sqrt{\frac{\text{desired inductance } (\mu H)}{A_L \text{ value}}} \quad (3)$$

The coil number of turns is calculated for the lowest band we are to use, which is 160 meters. Referring to the capacity (inductance data) we find, under 2250 ohms, that the inductance for 160 meters will be 18.36 — let's say 18  $\mu H$ . Plugging in the numbers,

$$100 \sqrt{\frac{18}{360}} = 100 \sqrt{0.05} = 22 \text{ turns}$$

In case of a fraction, round out the number, since there are no partial turns in winding a toroid.

As a point of interest, I noticed that Amidon now has a 3.048 inch (7.8 cm) core called a T-300; A-2 mix would have an  $A_L$  of 115. The core is 0.5 inch (12.7 mm) thick. Stacking one on top of the other would make up a 1 inch thick core with an  $A_L$  of 230. The required number of turns in this case is equal to

$$100 \sqrt{\frac{18}{230}} = 27.975 \text{ or } 28 \text{ turns.}$$

For those of you thinking of an amplifier in the 1 kW input class, the coil should be wound with No. 12-gauge enamel covered wire. If you contemplate 2 kW, use No. 10-gauge wire.

### coil preparations

Obtain a roll of glass cloth electrical tape No. 27. It costs approximately \$3.50 for 66 feet, or about 20 meters (there'll be plenty left over). If you're going to stack cores, use Eastman 910 super glue or equivalent. Align the cores, applying a small quantity of the glue — possibly only a few drops — around the side of one core. Work swiftly; super glue hardens quickly. The glue prevents the cores from moving out of alignment while they're being prepared for winding.

Now wrap two layers of glass tape around the core. Apply a heavy layer of Polystyrene Q-dope (available from Radio Shack for less than \$2 per 2-ounce bottle) to the glass-taped core. Set the core on a sheet of waxed paper or plastic wrap. After 20 minutes or so the Q-dope will have hardened sufficiently for another

table 2. Color code identifies core mix and frequency range.

frequency range (MHz)	color	mix
0.05- 0.5	gray	3
0.1 - 1.5	red/white	15
0.5 - 5.0	blue	15
1.0 -30.0	red	2


layer to be applied. (The core can easily be separated from the waxed paper or plastic wrap for full coverage.) When you're finished, no one — not even you — will know if it's one core or two.

Apply coat after coat until you've practically exhausted the contents of one 2-ounce bottle of Q-dope; you'll probably have about ten layers, which will add about 1/8 inch (.32 cm) or more to the thickness of the core. Now you'll need to add some insulation to the sides of the toroid. Some 1/16 to 1/8-inch (16 mm to 32 mm) polystyrene or fiberglass will be needed. (Don't use plexiglass.) In my search I ended up using 1/16-inch (16 mm) G-10 epoxy glass printed circuit board.

Use a propane torch to remove the copper foil. Place the board in a vise and apply the heat, stripping off the copper foil with a long-nose pliers. It takes only a few minutes to strip both sides when using a torch. Use of a fly cutter (circle cutter) to cut two identically-sized donut washers out of the epoxy board. The outside diameter should be 1/4-inch (6.4 mm) wider than the epoxied core, and the inside window or center hole 1/4-inch (6.4 mm) smaller.

Using some of the remaining coil dope, coat one side of each of the donuts you've prepared and place one on each side of the powdered iron core. Let it set. Now when you place the wire winding on the core, the wire will clear the core by 1/16 inch (1.6 mm) or 1/8 inch (3.2 mm) and there'll be plenty of insulation on the sides of the core. The Q-doped glass tape and end plates are the instruments that prevents RF from arcing to the core. If you prepare the core as directed, this will be no problem.

If you're using a deep chassis the coil can be held in place by the wire leads and mounted directly to the switch, wheel fashion. My chassis was not deep enough, since it was subdivided with the input of the RF amplifier on one side and the output on the other. I prepared two more pieces of G-10 epoxy as large washers, cutting a small hole in the center of each so that the core could later be mounted from a long stud secured to the chassis. One recommended step you can take is not absolutely necessary, but does make

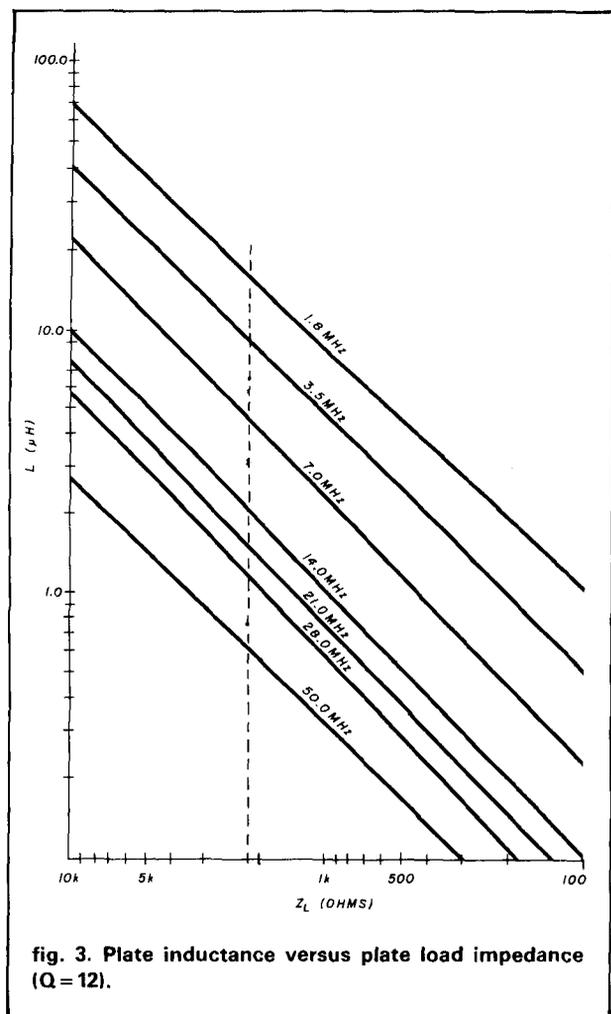

a neater package. The core does not include a 10-meter winding. As is conventional, this coil is almost always separate and is made up of about three or four turns of 1/4-inch (6.4 mm) copper tubing 2 to 2-3/4 inches (5 to 7 cm) in diameter. I mention it at this point because you may already have such a coil and the toroid core should be wound in the same direction as the turns of 10-meter coil, in order to prevent possible problems later. Take the core and determine the direction of winding, applying a sample of small wire to determine how the wire will lie in the core. With a Swiss file, file notches for the winding, making them about 3/64 inch (1.58 mm) deep. If you have 20 turns, there will be 40 notches on the inside window circumference and another 40 on the outside diameter of the G-10 epoxy donut sides.

Some pointers on winding the core: don't put the core between the jaws of a vise; it may break. Apply a test turn of wire to the core, observe the point at which a full turn is completed, remove and measure the test turn, multiply that figure by 20 and add 1 foot

(30.48 cm). This is the length of wire you'll use to wind the core. Place one end of the wire in a vise, go to the far end and get a good grip on the end with large pliers, stretch the wire taut and tug sharply to remove any kinks. (I didn't have anyone to help me at this point, but I suggest you get someone to hold the core while you wind it.) Put the end of the wire through until the core is close up to the vise. (Ask your helper to hold it.) In placing the notches around the core for the wire, wind till no gap remains. Leave a space between the beginning and end of the winding equal to at least the space of 1 or 2 turns of wire. This also provides a starting point for the winding. If you start on the notches for the second turn you can get the last turn on at the beginning from the end of the wire that was held in the vise. Start threading the wire. The person holding the core can assist in holding the wire in place. When finished, tie the ends together temporarily so they will not unravel or become loose. Some coil dope can be used to secure the wire in the notches.

### determining the tap positions

As the wire is spaced from the core, it's easy to scrape the enamel from the wire. Use the  $A_L$  formula to determine the tap placement. I'll take you through the first tap determination — that of 80 meters. Referring to the inductance data for L1, 80 meters = 9.72  $\mu$ H.

$$100 \sqrt{\frac{9.72}{3600}} = 100 \sqrt{0.0027} = 16.43 \text{ so the tap is } 6.5$$

turns from the 160 meter end or 16.5 turns from the load end. It can be placed at 16 turns. Calculate the location of each tap for the remaining bands.

If you wish — and it might be a wise thing to do — prove you have made all the correct calculations. How? You'll need a grid dipper for this part. Most of this can be done prior to winding the coil in its finished form. You can wind a more manageable wire size of No. 14 or 16 to test for the correct value of inductance.

At the beginning of this article we determined that 407 pF was needed for C1 and C2. With 22 turns of No. 14 or 16 wire on the core, make the last turn loose so that you can couple a grid dipper to it. Using capacitors from your junkbox, make up a capacitor of approximately 350 pF (300 and 50 pF are standard values of dog bone dipped micas). Connect the capacitor across the two ends of the winding — making sure the coil is not placed on a metal bench — couple it to the last turn, and dip the meter. If the dip is broad, de-couple by backing the dipper away until you get a sharp dip. Read the dipper frequency. If the scale has poor resolution, couple it to a counter or a receiver.

Many dippers only go down to 2 MHz. Wrap the leads of a 10 or 20 pF capacitor around the pins of the dipper coil. This will extend the range of the dipper, but the readout will be null and void so listen for the dipper oscillator on your receiver reading the receiver dial or digital readout. If this is not possible, compute the resultant capacitance for 80 meters and just place the equivalent capacitance across the 14 turns, dip the meter, and read the dial. Then place a one-turn link through the coil and tie the ends of the one turn together. Couple the dipper to this one turn. It will get you close to the frequency. It won't be as accurate as coupling to a loosely wound turn of the coil itself because a shorted turn loads the coil somewhat.


### tricks of the trade

Looking at the capacitor values of C1 and C2 for 160 and 80 meters makes one gasp. I used a four-gang capacitor from a surplus Hewlett Packard audio oscillator in my 800 watt output amplifier for C2. This has a total capacity of 2100 pF. I used two positions on the bandswitch for 160 and switched in 2000 pF on the lower frequency and 1000 on the higher end. The fixed capacitors used were the Hi-Q CRL-850 series 5000 volt DC.

For the plate capacitor C1, I also switch in parallel capacitors. Let's take a second look at the C1 values for 160, 80, and 40 meters 481, 246, and 123 pF respectively. We'd like to keep the physical size of the amplifier down, so let's say that a realistic practical maximum value is 250 pF. If one is to use vacuum variables, 350 becomes practical but for an air dielectric variable 250 pF seems high enough.

### combining capacitors

How can we get by with using 250 pF when we need 481 pF for 160 meters and 246 for 80? How would one cover the band? We may need two positions on the bandswitch if we plan to tune the whole 160 meter band, but let's see what it takes. For an accurate frequency plot it would be nice to have a reactance slide rule, but we can come close enough by interpolating between 3.5 MHz and 1.8 MHz in **figs. 1 and 2**. We know the 160-meter inductance is 18.4  $\mu$ H and the resultant capacitance ( $C_T$ ) of C1 and C2 is 410 pF for the low frequency end (1.8 MHz). What capacitance is required for 2.0 MHz? We find that it will take 340 pF. This is a change in the resultant capacity ( $C_T$ ) of 70 pF over the band. If  $C_T = 340$  pF, what will be the capacity remaining in the plate tuning capacitor C1? Let's go back to the plot in **fig. 2** for C2 at 2250 ohms load impedance. Extending a line through this impedance point, we find that 2400 pF will be required at 2.0 MHz — the high end of the band. Let's now look at the chart for C1; it looks like 400 pF. Let's see when

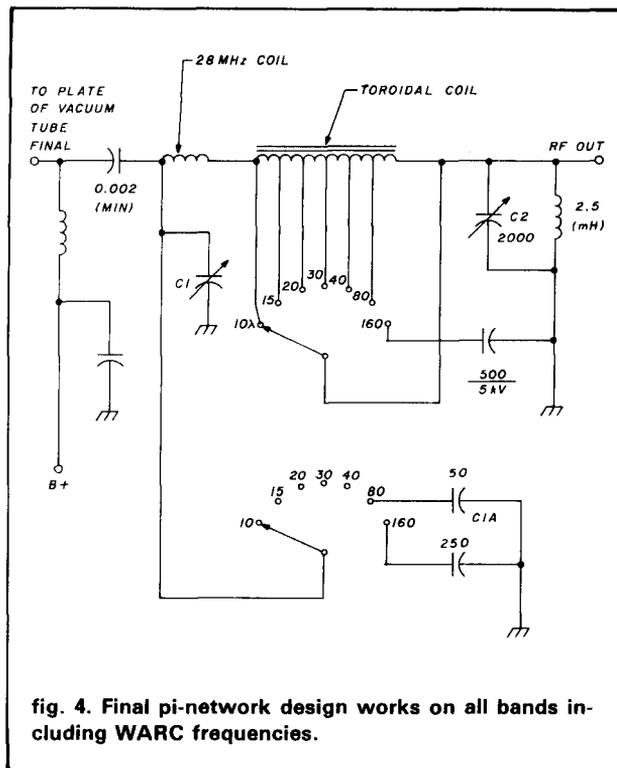

**fig. 4.** Final pi-network design works on all bands including WARC frequencies.

evaluating for the series capacitance how close we come to the required 340 pF.  $\frac{2400 \times 400}{2400 + 400} = 342.9$  pF.

That's close enough.

This indicates that C1 must be variable from a high of 481 pF for 1.8 MHz to a low value of 411 pF for 2.0 MHz. From this, if we switch in 250 pF fixed capacity across our 250 pF C1 selected variable, there will result a 500 pF total maximum capacitance which is 19 pF more than needed. For the high frequency end, if we tune out, say, 70 pF of the 250, there will be 430 remaining in the circuit. We still have a 180 pF of variable capacity remaining. It looks as if we can do the entire 160-meter band with just one band position by switching in 250 pF of CRL-850 series capacitance.

Let's now look at 80 meters and evaluate it the same way. 246 pF is required for C1 and 1368 pF is necessary for C2. We have plenty of C2 with 2100 pF of variable, but we may need more C1 — about 50 pF more. First let's see the minimum we need to cover 4.0 MHz. The capacitance chart at 2250 ohms, although poor in resolution, looks like 230 or possibly 240 pF. Let's say we switch in 50 pF of the CRL-850 series capacitance. This will provide a variable capacitance of 300-250 + 25 (about 25 pF for minimum capacitance in the capacitor and circuit capacity). This equates to a minimum available capacitance of 75 pF and a maximum of 300. We need only 246, so we have an excess of 54 pF; we need

State  
of the art



by  
**K.V.G.**

### 9 MHz CRYSTAL FILTERS

MODEL	Applica-tion	Band-width	Poles	Price
XF-9A	SSB	2.4 kHz	5	\$53.15
XF-9B	SSB	2.4 kHz	8	72.05
XF-9B-01	LSB	2.4 kHz	8	95.90
XF-9B-02	USB	2.4 kHz	8	95.90
XF-9B-10	SSB	2.4 kHz	10	125.65
XF-9C	AM	3.75 kHz	8	77.40
XF-9D	AM	5.0 kHz	8	77.40
XF-9E	FM	12.0 kHz	8	77.40
XF-9M	CW	500 Hz	4	54.10
XF-9NB	CW	500 Hz	8	95.90
XF-9P	CW	250 Hz	8	131.20
XF910	IF noise	15 kHz	2	17.15

### 10.7 MHz CRYSTAL FILTERS

XF107-A	NBFM	12 kHz	8	\$67.30
XF107-B	NBFM	15 kHz	8	67.30
XF107-C	WBFM	30 kHz	8	67.30
XF107-D	WBFM	36 kHz	8	67.30
XF107-E	Pix/Data	40 kHz	8	67.30
XM107-SO4	FM	14 kHz	4	30.15

Export Inquiries Invited.

Shipping \$3.75

### MICROWAVE MODULES VHF & UHF EQUIPMENTS

Use your existing HF or 2M rig on other VHF or UHF bands.

### LOW NOISE RECEIVE CONVERTERS

1691 MHz		MMk1691-137	\$249.95
1296 MHz GaAsFET		MMk1296-144G	149.95
432/435		MMc432-28(S)	74.95
439-ATV		MMc439-Ch x	89.95
220 MHz		MMc220-28	74.95
144 MHz		MMc144-28	59.95

Options: Low NF (2.0 dB max., 1.25 dB max.), other bands & IF's available

### LINEAR TRANSVERTERS

1296 MHz	1.8 W output, 2M in	MMI1296-144-G	\$299.95
432/435	10 W output, 10M in	MMI432-28(S)	269.95
144 MHz	10 W output, 10M in	MMI144-28	179.95

Other bands & IFs available.

### LINEAR POWER AMPLIFIERS

1296 MHz	20 W output	UP1296-20-L	439.95
432/435	100 W output	MML432-100	369.95
	50 W output	MML432-50	199.95
	30 W output	MML432-30-LS	209.95
144 MHz	200 W output	MML144-200-S	374.95
	100 W output	MML144-100-LS	239.95
	50 W output	MML144-50-S	149.95
	30 W output	MML144-30-LS	109.95

All models include VOX T/R switching.  
"L" models 1 or 3W drive, others 10W drive.

Shipping: FOB Concord, Mass.

### ANTENNAS

#### 420-450 MHz MULTIBEAMS

28 Element	70/MBM28 12 dBd	<del>\$49.95</del>	\$39.95
48 Element	70/MBM48 15.7 dBd	<del>75.75</del>	59.95
88 Element	70/MBM88 18.5 dBd	<del>105.50</del>	89.95

#### 144-148 MHz J-SLOTS

10 + 10 Twist	10XY/2M 11.3 dBd		69.95
---------------	------------------	--	-------

#### UHF LOOP YAGIS

1250-1350 MHz	29 loops 1296-LY 20 dBi		\$49.95
1650-1750 MHz	29 loops 1691-LY 20 dBi		59.95

Order Loop-Yagi connector extra:

Type N \$14.95, SMA \$5.95

Send 44¢ (2 stamps) for full details of all your VHF & UHF equipment and KVG crystal product requirements.



**si**

(617) 263-2145  
**SPECTRUM**  
INTERNATIONAL, INC.  
Post Office Box 1084  
Concord, MA 01742, U.S.A.

a minimum of 230 or 240, and we have 175 — so we're well in on 80 meters by switching in 50 pF. All the other bands are OK without additional capacitance. This should be enough data to enable you to draw up a switching circuit — see fig. 4.

### bandswitch connections

The bandswitch should be of ceramic or porcelain material, of high quality and capable of handling the RF power. The switch will need two decks to accommodate the additional C1 capacitance required to be switched in and out. The number of positions will depend on the number of bands.

Some final thoughts: keep in mind that if the load impedance of the vacuum tube or tubes selected calculates out to be 1500 ohms or less, the required L1 is somewhat less, so C1 and C2 become larger. This means there will be more capacitance to switch in. With such high values of fixed capacitance there may not be enough variable capacitance left to cover the 160-meter band. If this is the case, two positions will have to be provided on the bandswitch in order to cover both the low and high frequency segments of the band.

Note that only seven positions are shown on the switch in fig. 2 and the bands for 18 or 24.5 MHz are omitted. Also note that to provide enough Q on the 10-meter band, a separate coil will be required the same as in any and all amplifiers on the market. This usually requires about three or four turns of 2 to 2-1/2 inch (5 to 7 cm) diameter 1/4-inch (6.4 mm) copper tubing.

The last item is the plate blocking capacitor. This 0.002 μF capacitor is an important item and must handle high current, is high Q like the CRL-850 series capacitors and also is high voltage about 10,000 volts in amplifiers of 2 kW. This value capacitor has a 45-ohm reactance on 160 meters. The 0.004 μF capacitors reactance value is 25 ohms on 160 meters. The 858 capacitors are rated at 5000 volts and require two 1000 pF units in parallel. The 2000 pF capacitors are only rated at 1.5 kV. The 5000-volt 858 is just marginal at 2500 volts and should you be running approximately 1 ampere of plate current you'll have to series-parallel eight of these just to produce 0.002 at 10 kV.

There you have it. Should you need further assistance, drop me a line (enclose an SASE).

### bibliography

- "Solid State Exciter," Robert E. Bloom, W6YUY, 73, December, 1970.
- "Linear Amplifier Design," Bill Orr, W6SAI, ham radio, July, 1979, page 34.
- "Modular Linear Amplifier for the High-Frequency Amateur Bands," Jerry Pittenger, K8RA, ham radio, January 1981, page 12.
- "A 3CX800A7 Linear Amplifier," Jerry Pittenger, K8RA, ham radio, August, 1984, page 17.

ham radio

## Free Antenna Accessories Catalog



### ◀ Coaxial Antenna Relays

Remotely select up to 9 antennas from your transmitter, using only one coaxial cable. Environmentalized, high power and low loss.

### W2AU and W2DU Baluns▶

Our baluns, center insulators and insulators have been preferred for 20 years by Hams, industry, and the armed forces. Protect against TVI and lightning 1.8-200 MHz.



### ◀ W2VS Antenna Traps

Add these traps to your dipole and get low SWR on 2 to 6 bands, depending on how many you add. Antenna wire and custom kits also available.

### Send For Yours Today▶

Don't delay. Call or write today, and we will send you free literature which fully describes our Ham antenna accessory product line. Dealer inquiries also welcome.



**UNADILLA/REYCO/INLINE**


A Division of Microwave Filter Co., Inc.

6743 Kinne St., East Syracuse, NY 13057  
Toll Free 1-800-448-1666 TWX 710-541-0493  
NY/HI/AK/Canada (Collect) 315-437-3953

✓ 118
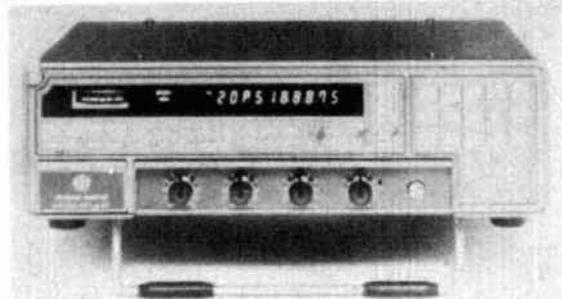
## J.I.L. SX-400

Uninterrupted  
Frequency  
Coverage  
100 kHz to 1400 MHz  
with Optional Converters



- A professionally created scanner for the serious listener
- Wide frequency coverage 26 to 520 MHz (with optional converters 100 kHz to 1400 MHz)
- Continuous coverage. You'll hear everything.
- Birdie-Free, no internal 'signals' to interfere with scanning
- 20 Channel memory, AM-FM Mode memory, Priority memory
- Carrier Operated Relay (COR) permits automatic start/stop of a recorder
- Four low-noise front end converters for optimum performance
- 12 Volt DC operation (120 Volt AC power supply optional)
- Check JIL's ad in this issue for further details

Sale Price \$549.95 List \$739.90

P-1A Power Supply \$34.95

Other options call

**HOT SUMMER SPECIAL**  
**\$499.95**



### Electronic Equipment Bank

516 Mill Street  
Vienna, Virginia 22180

800-368-3270  
✓ 119 (703) 938-3350



**DICK SMITH ELECTRONICS  
NOW OPEN IN THE U.S.A.**

# OUT NOW

**132 PAGES  
PACKED WITH  
ELECTRONIC  
GOODIES AT  
INCREDIBLY LOW  
PRICES PLUS**

- DATA ○ HIGH TECH KITS
- BOOKS
- COMPONENTS

**AND MUCH  
MUCH MORE - AS  
WELL AS \$2  
VOUCHER**



**PASSING BY  
OUR STORE?  
390 CONVENTION WAY  
REDWOOD CITY CA 94063  
DROP IN PICK UP  
A CATALOG  
WE'D LOVE TO MEET YOU!**

**FROM AUSTRALIA'S  
LEADING  
ELECTRONICS RETAILER  
THE 1985  
DICK SMITH ELECTRONICS  
CATALOG**


**RUSH \$2.00 PLUS \$1.00 SHIPPING FOR  
YOUR COPY TODAY AND GET YOUR MONEY  
BACK ON YOUR FIRST ORDER. THAT'S  
RIGHT! EACH CATALOG CONTAINS \$2.00  
WORTH OF VOUCHERS REDEEMABLE ON  
YOUR FIRST ORDER.**

### MAIL THIS COUPON TO:

DICK SMITH ELECTRONICS, Inc.  
P.O. BOX 2249 REDWOOD CITY CA 94063  
PHONE: (415) 368 1066

NAME.....  
ADDRESS.....  
CITY.....  
STATE..... ZIP.....

## AIR-WOUND INDUCTORS

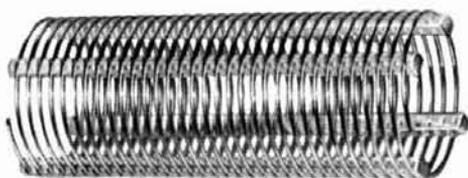

B&W Miniductors® and Air-Dux® have been the industry standard for over 50 years, wherever radio-frequency coils are used.

- For the experimenter, the radio amateur, the manufacturer
  - Available in diameters from 1/2" to 6"
  - Wire sizes from #24 to #8 AWG
  - Also edge-wound and tubing coils for high-power applications.
- Call or write for complete specifications.

ALL OUR PRODUCTS MADE IN USA



**BARKER & WILLIAMSON**

Quality Communication Products Since 1932

At your Distributors. Write or Call.

10 Canal Street, Bristol PA 19007

(215) 788-5581



## GLB PACKET RADIO CONTROLLER

Now you can get in on the fun in packet radio!

MODEL PK1



**SPECIAL PACKAGE DEAL!!!**

**Amateurs Only**

Includes PK1 installed in cabinet w/cable set & pwr. supply

**\$229.95**

(if purchased separately \$241.85)

- \* Ready to operate - wired and tested.
- \* Operates with Voice Transceivers.
- \* Easy to learn, easy to operate.
- \* Built in Packet Modem and CW Identification.
- \* Use with a computer, terminal or Teletype Machine.
- \* Terminal: ASCII or BAUDOT; 45 to 9600 Baud.
- \* Radio Link Speeds of 300, 600 or 1200 Baud.
- \* Automatically selects AX.25 or VADC-1.
- \* Remote Repeater Command Lockout.
- \* Full 8-digipeater operation in AX.25.
- \* Over 90 Commands.
- \* Stores received messages for delayed reading.
- \* Able to display other calls while connected.
- \* "Block" and "transparent" modes for data files.
- \* Operates as an unattended digipeater.
- \* "Beacon" mode.
- \* Signals available for Teletype Motor Control.
- \* Standard memory is 4K, expandable to 14K.
- \* 48K RAM available on special order.
- \* Can be customized for LAN's.
- \* Squelch input for sharing of voice channels.
- \* Call sign, SSID & VADC # programmed in ROM.

Dimensions: 2.3 X 11 X 5 (inches).  
Power Requirement: 12 volts DC at 200 ma.

- PK1 - FCC CERTIFIED - wired and tested in cabinet **\$209.95**
- PK1S - Subassembly board - wired and tested **\$164.95**
- PKDOC - Documentation only - Refundable on first PK1 purchase **\$ 9.95**

Please specify Call Sign, SSID Number, and Node Number when ordering  
Contact GLB for additional info and available options.

We offer a complete line of transmitters and receivers strips, preselector preamps, CWID's and synthesizers for amateur & commercial use.

Request our FREE catalog. MC & Visa welcome.

✓ 121

**GLB ELECTRONICS, INC.**

151 Commerce Pkwy., Buffalo, NY 14224  
716-675-6740 9 to 4

# SPECIAL OFFER

**CALLBOOKS NOW INCLUDE A FREE MAP**

VALUE \$2.50 each

### NORTH AMERICAN CALLBOOK

Includes free map of North America.

The New North American Callbook now contains Canadian and Mexican as well as all US Radio Amateurs. Fully updated with all the latest callsigns and addresses. Edited to ensure accuracy. Includes handy station aids. ©1984.

CB-US85

**Softbound \$25**

(\$21.95 + \$3.05 s & h)

### FOREIGN CALLBOOK

Includes free World Wide Prefix map.

The **only** source of DX calls and addresses available. Fully updated and has helpful QSL information. ©1984.

CB-F85

**Softbound \$24**

(\$20.95 + \$3.05 s & h)

Order Both and SAVE even more — Regular Price \$45


**HAM RADIO SPECIAL \$39.95 POSTPAID**

**ham  
radio** magazine

GREENVILLE, NH 03048

**BOOKSTORE**

(603) 878-1441

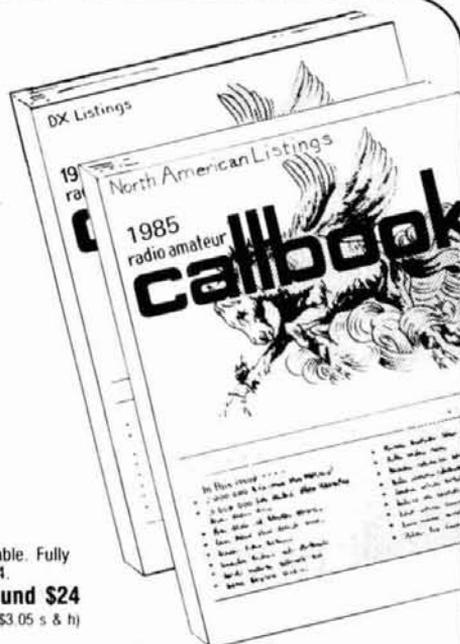

**SAVE \$5**

## medium power amplifiers

In one of my earlier columns I described VHF/UHF excitors, with the emphasis on transverters.<sup>1</sup> These transverters are primarily designed for 2 meters and 135 and 70 cm, but only at lower power — typically 0.5 to 1 watt output. In last January's and February's columns, I discussed high-power amplifiers, with the goal of attaining the legal power limit.<sup>2,3</sup>

But many VHFers need intermediate power level amplifiers, typically at 10 to 100 watts, for use as either a final stage or to drive a high-power amplifier. With this in mind, I've decided to dedicate this column to that subject.

### amplifier types and classes

There are two major types of medium-power amplifiers: vacuum tube and solid-state. Each has its advantages and disadvantages. Generally speaking, tube amplifiers have higher gain, are more linear, are larger in size, and require at least two or more voltages. Solid-state amplifiers, on the other hand, are generally more compact and more physically rugged than tube-type amplifiers and usually require only a single voltage power supply.

Both types can usually be run in class C, which is all that's required for CW and FM operation. However, nowadays most Amateurs prefer a linear amplifier, since it works equally well on CW and SSB at the flip of the mode switch and is less likely to cause key clicks when operating on CW.<sup>1,2</sup>

**Medium-power vacuum tube amplifiers.** Vacuum tube amplifiers have been around for a long time. They're usually quite reliable and rugged. Mis-

matches and mistuning — all too familiar to users of solid-state amplifiers — seldom cause catastrophic failures.

However, this type of amplifier can be bulky. It generally requires several voltages such as filament, plate, and possibly control and screen grid as well. And while it's not usually a problem, a warmup period of 1/2 to 5 minutes is usually necessary. Therefore, they're not particularly popular — especially for portable or mobile operation!

Regardless of their shortcomings, vacuum tube amplifiers are still quite plentiful and are often available at low prices. If you already have one anyway, why throw out or sell a perfectly good amplifier that's still functioning properly?

Many single-tube 2C39 amplifiers — often from the old Motorola T44 units — are still in operation on 70 cm. They make fine output amplifiers for low-power operation and serve well as drives from typical legal-limit amplifiers. There are also many single tube 4X150/4CX250B types of amplifiers still in use. They also make excellent moderate power amplifiers. Many modern high-power amplifiers use grounded grid circuitry and often have only 10-13 dB of gain. Hence they may require 75 to 150 watts of drive to achieve the full legal Amateur power limit. This is a great application for such an amplifier.

So don't dismiss the idea of using a vacuum tube amplifier as either a moderate output power amplifier or as a driver. (See references 2 and 3 for further information on the subject.)

**Medium-power solid-state amplifiers.** Solid-state amplifiers can be designed for either class C or linear

operation. Both bipolar transistors and MOS power FETs are commonly used. There's no doubt that the compact solid-state amplifier has done wonders to increase VHF/UHF activity as well as reduce the size of the necessary equipment.

Power bipolars are presently the most common type of device used in Amateur medium-power solid-state amplifiers. They've been available for over 15 years and are moderately priced. Most work well at 12 volts DC and are therefore convenient for mobile operation. But they're usually quite fragile, and their transistors may burn out if subjected to a high VSWR load.

More recent power amplifier designs employ high-power MOSFETs, which became available about ten years ago. Manufactured by Siliconix, the first commercially available power FETs were called VMOS (Vertical Metal Oxide Semiconductors). Soon after, other manufacturers started making and improving on their performance, power, and reliability.

The original MOS power devices, primarily designed as switches, are generally called enhancement FETs, since they have to be biased "ON" to operate — just the opposite of the way vacuum tubes work. Because they had a high input impedance, they were subject to burnout when not connected in a circuit. Therefore, the manufacturers frequently placed a zener diode across the gate, thus reducing the frequency response and limiting use to HF and down.

Siliconix introduced the VMP-1 and VMP-4 devices in RF packages without the input protection zener diode. I've been using the same VMP-4 in a 10-watt 135-cm linear amplifier since

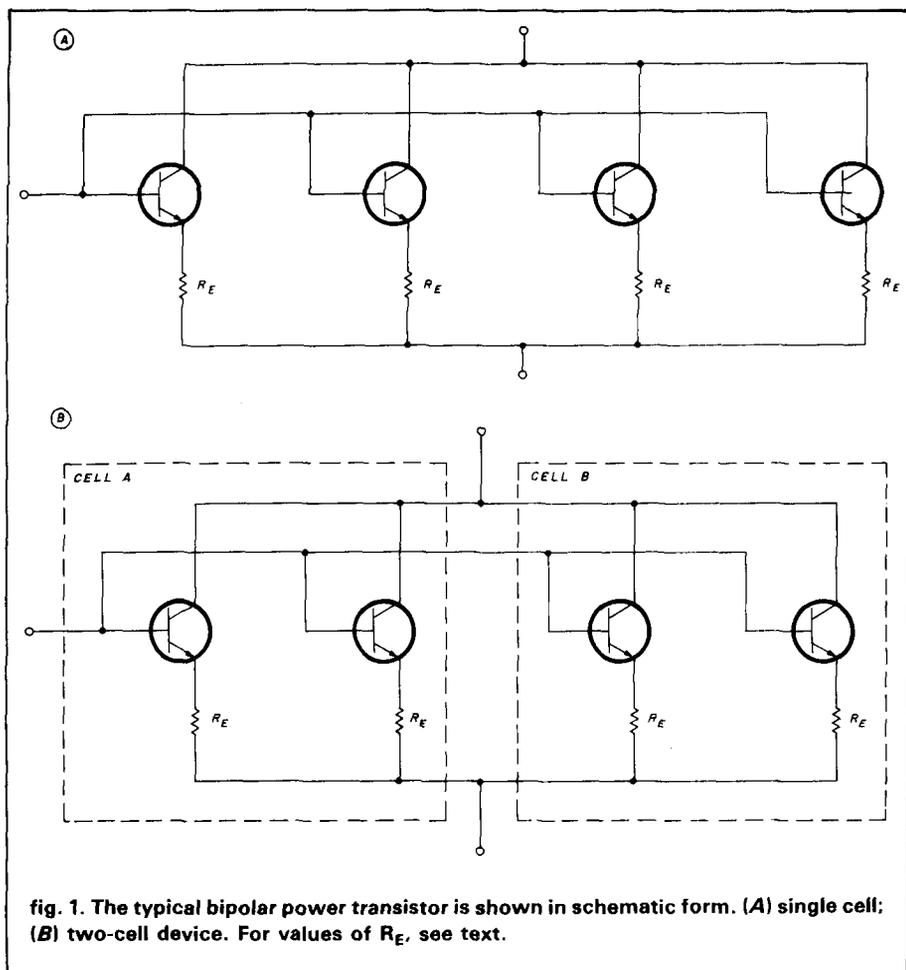


fig. 1. The typical bipolar power transistor is shown in schematic form. (A) single cell; (B) two-cell device. For values of  $R_E$ , see text.

1976! First it was my output stage and later my high-power amplifier driver.

Power MOSFETs are not as likely to be destroyed even if their output VSWR is high. When heated, many of these devices will just shut down rather than "self-destruct!" Power FETs generally have higher input/output impedances than bipolar power transistors, making them easier to impedance match (more on this later). However, the linear power MOSFET devices generally require higher operating voltage — 28 volts or more. For this reason, they're not as likely to be used in mobile or Amateur applications, where 12 volts is usually the only supply voltage available.

Power MOS devices stand an excellent chance of overtaking bipolar devices in many applications in the future. Although there may be some interest in the use of power MOS

devices for Amateur applications, I'll limit this discussion to bipolar transistors because they're by far the most widely used solid-state devices in medium power amplifiers.

Before we can design and build a medium power amplifier, we must first know some of the basic properties of the bipolar transistor devices to be used. The most important parameters are the DC voltages, the power dissipation, recommended operating frequencies, RF input/output impedances and recommended circuitry for bipolar power devices.

The typical bipolar power transistor consists of many individual transistor junctions in parallel (fig. 1A). This configuration is chosen to increase current handling and distribute the heat within each junction. In the larger devices, there may even be multiple identical "cells" which are paralleled in

the semiconductor itself to further increase the power and current handling (fig. 1B).

Resistance  $R_E$  (fig. 1C) is typically 5-30 ohms and is determined by the design requirements, manufacturing process, and material. The value chosen is very important, since the lower the resistance, the higher the gain of the transistor. This is frequently referred to as the ballasting resistor.

However, if heat increases in the junction, the typical bipolar transistor starts to draw more current and therefore heats up. If there's any potential difference between the junctions of the different transistors in parallel, the emitter current (and hence the collector current) may divide unevenly — and in an instant, there can be a chain reaction.

First one junction starts to "hog" current. It heats up until it's destroyed. Then the current is diverted to the remaining transistors, which may in turn be destroyed. The higher the resistance of  $R_E$ , the better the chances of equal current distribution (especially when heated) and the less possibility of (thermal) runaway destruction. Therefore the designer must carefully choose the optimum emitter resistance for the application and trade off gain versus power distribution and stability. Generally speaking, linear devices have higher  $R_E$ , while class C devices have lower  $R_E$ .

Power dissipation is a very serious consideration in the design of a power bipolar transistor. The junction area is quite small and the only way to cool it is with a good heat conducting package that is well heatsinked. This is in great contrast to power tubes where a large area is used and the power dissipation can usually be raised by increasing the air or water flow through the tube's plate radiator. Furthermore, the typical power bipolar transistor operates at a lower collector efficiency than its vacuum tube counterpart. While class C operation efficiency may approach 50 to 60 percent, typical linear service is usually between 33 and 50 percent.

DC voltages are most important.

However power bipolar manufacturers have made it easier for the user by optimizing the breakdown voltage and other parameters to suit the market. For example, there are power transistors for the 12 to 15, 24 to 30, and 50-volt markets. These markets are for the land mobile, aircraft/commercial and the pulse industries, respectively.

Current limits, also specified by the manufacturers, increase more or less in direct proportion to the power of the device and its application. In contrast to power tubes, the typical power bipolar transistor can be easily destroyed if the collector current rating is exceeded, even for an instant. Therefore, a current limited power supply is highly recommended. Fuses just may not operate fast enough to prevent burnout.

Most transistors are very frequency sensitive. For instance, the typical maximum gain of a bipolar power transistor usually decreases 6 dB every time the frequency is doubled. This means that if the transistor is operated at lower frequencies, it will have very high gain — typically enough to go into oscillation or “self destruct!”

Manufacturers work around this problem by designing each type of transistor to have a typical gain of 6 to 12 dB at the recommended operating frequency, much lower than that of a typical power tube! *Operation below the recommended frequency range is strongly discouraged.*

However, this is typically not a problem for Amateurs since most of us use a different power amplifier on each band. Also, power bipolar transistors are readily available for the Amateur 2-meter, 135 and 70-cm bands since they are also available for the commercial VHF, military and UHF bands, respectively.

**RF input/output impedance.** Unlike tubes, the input and output impedances of bipolar power transistors are extremely low and often have a significant reactive component. Input impedances of 1 to 10 ohms are quite common and the higher the power level, the lower the impedances will be. Typical input impedances are usually speci-

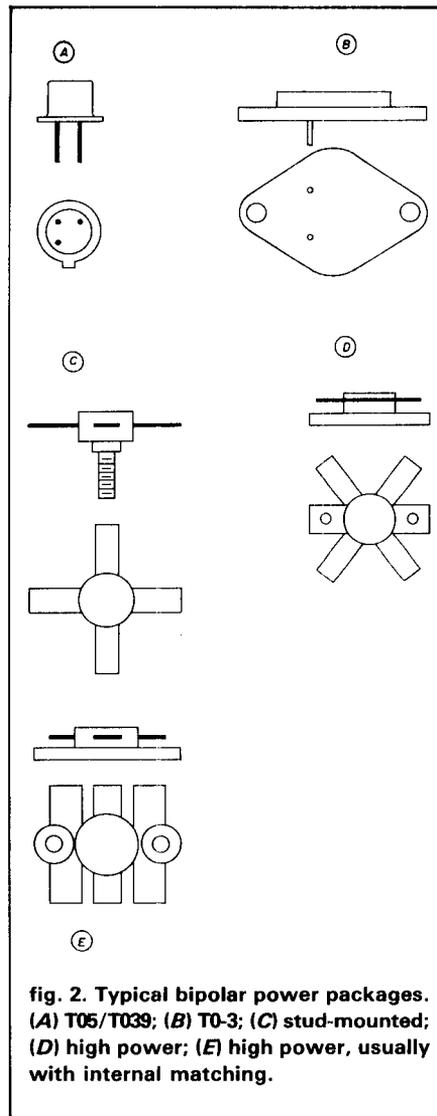


fig. 2. Typical bipolar power packages. (A) TO5/TO39; (B) TO-3; (C) stud-mounted; (D) high power; (E) high power, usually with internal matching.

fied by the manufacturers either at midband or over the specified frequency band as plotted on a Smith chart. The output impedance of a power bipolar transistor is usually specified differently than the input impedance since it is a function of the internal device parameters, the operating power level, and the class of operation. Furthermore, the output or collector of a power bipolar transistor is usually not operated in a matched condition (often called “conjugate matched”). If the output were matched, this would mean that at least 50 percent of the power would have to be dissipated in the circuit, output efficiency and power would be lowered, and the device would have to dissipate

more power. (This will be discussed shortly.)

Therefore, bipolar power transistors are often specified when operating into a *conjugate of the optimum load impedance* at a given frequency and power level. To simplify matters, most manufacturers usually show a typical or recommended circuit with the optimum components.

## transistor configurations

Bipolar power transistors are usually operated in either a grounded emitter or grounded base configuration. Most modern devices operating below 500 MHz are specified for grounded emitter circuitry. Gain is usually slightly lower than in grounded base operation and the input impedance is higher, making it easier to match impedance. Grounded emitter configurations are also easier to bias and stabilize for linear operation.

Grounded base operation is still popular, especially above 500 MHz and where class C operation is used. Devices operating in grounded base circuits typically have higher gain (typically 1 to 3 dB), especially at the maximum frequency of operation. Another advantage is that the gain of a device increases only a moderate amount (10 to 15 dB) and flattens out as frequency decreases. Hence this circuit is less likely to oscillate at a lower frequency.

## packages

Choosing the package for a high power bipolar transistor is almost as important to the device designer as designing the chip itself. At the higher power levels, heat dissipation is a complex problem. Because the area of the chip itself is usually quite small, manufacturers have selected packages with extremely low thermal resistance.

The typical three or four-lead TO-5 and TO-39 cans (fig. 2A) cannot dissipate heat efficiently. TO-3 packages (fig. 2B) are generally not suitable at VHF/UHF frequencies because of package parasitics.

Many power packages have been designed to handle power dissipation

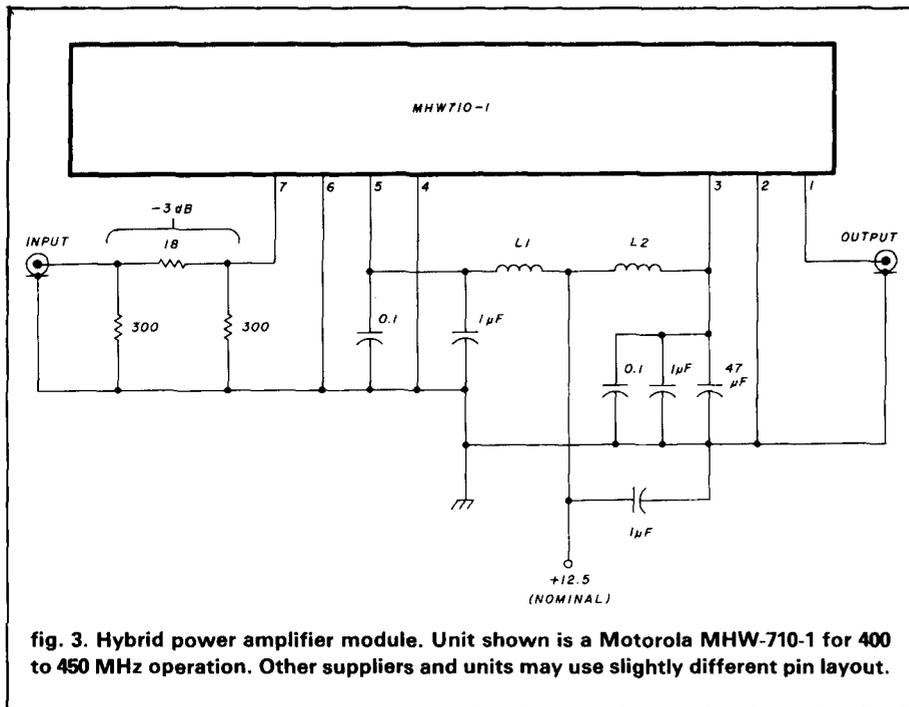


fig. 3. Hybrid power amplifier module. Unit shown is a Motorola MHW-710-1 for 400 to 450 MHz operation. Other suppliers and units may use slightly different pin layout.

while keeping the leads short. Furthermore, these packages usually have very wide leads to keep internal lead inductance at a minimum. At the lower power levels, 1 to 10 watts, stud-mounted packages are sometimes used (fig. 2C). However, at higher power levels, larger flat packages — generally with two mounting holes — are more common (figs. 2D and 2E). In all cases, the manufacturer uses a package commensurate with the power level of the device and specifies the thermal resistance and/or the type and size of heat sink required.

To further lower the internal parasitic load inductance, the common lead (either the base or emitter) is often attached to opposing leads on the package. Thus the package can be grounded on both sides. Not only does this improve gain but it often improves circuit stability.

*Caution: Many UHF power transistors use a special low thermal resistance ceramic package containing beryllium oxide. If the package is crushed, ground, or abraded, the dust resulting from such action may be hazardous if inhaled. Therefore, never try to work with packages that may contain this material. To dispose of*

*damaged or unwanted packages, enclose in an appropriate container for burial in an approved landfill, well away from ground water supplies.*

### linear versus class C operation

The first bipolar transistors were almost always operated in class C. To a great extent, this is still true today on FM. Class C design is rather straightforward and, as mentioned earlier, many devices are available with good gains.

However, most of the early devices available were not suitable for linear operation since they were highly non-linear and tended to self-destruct if even a small biasing current was applied. Therefore, manufacturers typically redesigned their devices by adding higher ballasting resistors in the emitters, as discussed above. Careful attention to frequency response, stability, and gain lead to a whole new category of devices suitable for linear operation.

Nowadays most Amateurs use linear power amplifiers since they can be placed on CW, FM, or SSB. Ample information is available on class C operation, both in the literature and from

manufacturers' data sheets. In addition, most suppliers have application notes available in their data manuals.

Before we leave class C operation, there is one type of commercially available unit that's particularly well suited for certain applications. Often referred to as the "brick" or "hybrid power amplifier module," this device is typically available at the 5 to 25 watt output power level for various frequency ranges from 144 to 940 MHz. They usually have high gain (2 or 3 internal stages) and therefore require only 0.1 to 1 watt of drive. Typically they are usable over 5 to 25 MHz of bandwidth (depending on operating frequency) with 30 to 50 percent overall efficiency.

Furthermore, these modules typically require a single 12 to 14 volt power supply and a few bypass capacitors. I particularly like them for driving frequency multipliers, which are more reliable if driven from a stable power source. Quite often I see these modules listed in surplus advertisements. Amperex, Motorola, RCA, NEC, and TRW are some of the major suppliers.

A typical 70-cm hybrid amplifier is shown in fig. 3. A good heat sink is required because efficiencies are low (30 to 40 percent). The 3 dB pad improves input match. However, hybrid modules are not suitable for linear service, and all the attempts to linearize them that I've heard of have been unsuccessful.

### linear operation

Modern bipolar power transistors are still not capable of class A operation above a few watts because their power dissipation is too high for the packages and device geometries available. Most Amateurs prefer 12-volt power transistors because they're more compatible with the power supplies available (especially in mobile operation), moderately priced, and fairly rugged. However, if good linearity is required, the 24 to 28 volt devices are usually superior, even though they are less rugged and cost more.

When good linearity is required at power levels exceeding 5 watts, class

**★ QUALITY PARTS ★ DISCOUNT PRICES ★ FAST SHIPPING!**

**SEND FOR FREE FALL 1985 CATALOG... 48 PAGES!**

**ALL ELECTRONICS CORP.**

**EDGE CONNECTORS**

ALL ARE 1.56" SPACING.



**22/44 EDGE CONNECTOR**  
PC style \$2.00 each  
10 for \$18.00

**22/44 EDGE CONNECTOR**  
solder lug style \$2.50 each

**28/56 EDGE CONNECTOR**  
PC style \$2.50 each  
10 for \$22.00

**36/72 EDGE CONNECTOR**  
PC style \$3.00 each

**43/86 EDGE CONNECTOR**  
PC style \$4.50 each

**TRANSISTORS**

2N706	4 for \$1.00
2N2222A	3 for \$1.00
PN2222A	4 for \$1.00
2N2904	3 for \$1.00
2N2904	3 for \$1.00
2N2905	3 for \$1.00
MJ2855	\$1.50
2N3055	\$1.00
PMD 10K40	\$1.00
TIP 121	75¢
TIP 125	75¢

**TRANSFORMERS**

120 volt primaries	
5.6 volts @ 750 ma.	\$3.00
6 volts @ 150 ma.	\$1.25
12 v.c.t. @ 200 ma.	\$2.00
18 volts @ 650 ma.	\$3.50
18 volts @ 1 amp	\$4.50
24 v.c.t. @ 200 ma.	\$2.50
24 v.c.t. @ 400 ma.	\$3.00
28 v.c.t. @ 15 amps	\$20.00
30 v.c.t. @ 2 amps	\$5.00

**WALL TRANSFORMERS**

all plug directly into 120 vac outlet	
4 VDC @ 70 ma.	\$2.00
6 VAC @ 500 ma.	\$3.50
6 VDC @ 750 ma.	\$6.50
9 VDC @ 500 ma.	\$5.00
12.5 VAC @ 265 ma.	\$3.00
24 VAC @ 250 ma.	\$3.00
MULTI-VOLTAGE @ 500 ma.	
3.4, 5, 6.7, 8 or 12 VDC	\$7.50

**SPRING LEVER TERMINALS**

Two color coded terminals on a sturdy 2 1/4" x 3 3/4" bakelite plate. Great for speaker enclosures or power supplies.  
\$1.00 each 10 for \$9.00

**SOUND AND VIDEO MODULATOR FOR T.I. COMPUTER**



T.I. # UM1381-1. Designed for use with T.I. computers. Can be used with video sources. Built-in A/B switch. Channel 3 or 4 selection switch. Operate on 12 vdc. Hook-up diagram included.  
**\$10.00 EACH**

**SLIM LINE COOLING FAN**




Etri # 99XM182 low noise fan. Measures 3 3/8" square x 1" deep. 21 cfm. 23 db. 1700 rpm.  
**SPECIAL PRICE ... \$12.50 each**

**2K 10 TURN MULTI-TURN POT SPECTROL #MOD 534-7161 \$5.00 EACH**

**SOLID STATE BUZZER**  
Star #SMB-06L 6vdc TTL compatible \$1.00 each 10 for \$9.00

**REVERBERATION UNIT**  
Accustronics coil spring type units. Used in electronic organs to provide acoustic delay sound effects. Input impedance 8 ohms. Output Impedance 2200 ohms. Measures 4 1/2" x 16 3/4" x 1 1/2".  
**\$7.50 EACH**

**SUB-MINIATURE D TYPE CONNECTORS**

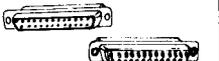

DB-15 PLUG	\$2.75
DB-15 SOCKET	\$4.00
DB-15 HOOD	\$1.50
DB-25 PLUG	\$2.75
DB-25 SOCKET	\$3.50
DB-25 HOOD	\$1.25

**PARALLEL PRINTER CONNECTORS**



Solder style 36 pin used on parallel data cables.  
**\$5.50 each**

**MALE CONNECTOR \$5.50 each**  
**FEMALE CONNECTOR \$5.50 each**


**I.D.C. CONNECTORS**

Will press fit on standard ribbon cable

DB-25 PLUG	\$6.25
DB-25 Socket	\$6.75
36 PIN MALE	\$5.50
36 PIN FEMALE	\$5.50

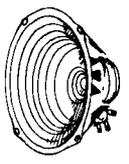**8" P.A. SPEAKER**

C.T.S. Model 8B3079 8 ohms coil 3.0 oz. ferrite magnet Typical response range: 100 - 10,000 Hz Power rating 15 watts max. Drilled to mount line matching transformers.  
**\$5.00 each**  
**CASE OF 8 SPEAKERS \$32.00**



**LINE CORDS**



**TWO WIRE**  
6 18/2 SPT-1 flat 3 for \$1.00  
6 18/2 SPT-2 flat \$1.25 each  
6 16/2 SJT round \$1.25 each

**THREE WIRE**  
6 18/3 flat \$1.50 each  
6 18/3 round \$2.00 each  
6 16/3 round \$4.00 each

**RELAYS**

**5 AMP SOLID STATE**  
Heinemann Electric #101-5A-140-5AMP CONTROL 3-32 vdc LOAD: 140 vac 5 amp SIZE 2 x 1 x 3/4 h  
**\$5.00 each 10 for \$45.00**

**ULTRA-MINIATURE 5 VDC RELAY**  
Fujitsu # FBR211NED005M20 High sensitivity COIL: 120 ohms CONTACTS: 1 amp Mounts in 14 pin DIP socket  
**\$1.25 each 10 for \$10.00**

**MINIATURE 6 VDC RELAY**  
Aromat # RSD-6V Super Small S P D T relay GO!O!colt contacts rated 1 amp @ 30 vdc. Highly sensitive. TTL direct drive possible. 120 ohm coil. Operate from 4.3 - 6 vdc. COIL: 120 ohms 1 1/16 x 1 1/32 x 7/16"  
**\$1.50 each 10 for \$13.50**

**TI SWITCHING POWER SUPPLY**

Compact, well-regulated switching power supply designed to power Texas Instruments computer equipment.  
INPUT: 14 - 25 vac @ 1 amp  
OUTPUT: 12 vdc @ 350 ma  
5 vdc @ 1.2 amp  
5 vdc @ 200 ma  
SIZE: 4 1/4" x 4 1/4" x 1 1/4" high  
**\$5.00 each**

**13.8 VDC REGULATED POWER SUPPLY**

These are solid state, fully regulated 13.8 vdc power supplies. Both feature 100% solid state construction, fuse protection, and L.E.D. power indicator U.L. listed.  
2 amp constant, 4 amp surge \$18.00 each  
3 amp constant, 5 amp surge \$25.00 each

**D.C. CONVERTER**

Designed to provide a steady 5 vdc @ 240 ma. from a battery supply of 3.5 to 6.25 volts.  
2 1/16" x 1 1/4" x 1 1/16"  
**\$1.50 each**

**7 CONDUCTOR RIBBON CABLE**

Spectra-strip red marker strip, 28 ga. stranded wire.  
**\$5.00 per 100' roll**

**\*SPECIAL PRICE\* DUAL L.E.D. DISPLAYS**



.560 high, 7 segment L.E.D. read-outs. Mount in 24 pin DIP sockets.  
MAN-6640 orange, c.c 75¢ each  
FND-5148 red, c.c 75¢ each  
DL-527 red, c.a 75¢ each

**3 1/2" SPEAKER**  
8 ohm impedance Full range speaker 8 oz magnet 4 diagonal mounting centers  
**\$2.50 each 10 for \$20.00**

**STANDARD JUMBO DIFFUSED T 1 1/2**

RED 10 for \$1.50 100 for \$13.00  
GREEN 10 for \$2.00 100 for \$17.00  
YELLOW 10 for \$2.00 100 for \$17.00

**FLASHER LED**  
5 volt operation red jumbo T 1 1/2 size \$1.00 each

**BI-POLAR**  
jumbo T 1 1/2 size 2 for \$1.70

**LED HOLDERS**  
Two piece holder for jumbo LED 10 for 65¢ 100 for \$5.00

**CLEAR CLIPLITE LED HOLDER**  
Make LED a fancy indicator. Clear 4 for \$1.00

**MINIATURE TOGGLE SWITCHES ALL ARE RATED 5 AMPS @ 125 VAC**

<b>S.P.D.T. (on-on)</b> PC style non-threaded bushing 75¢ each 10 for \$7.00	<b>S.P.D.T. (on-on)</b> Solder lug terminals \$1.00 each 10 for \$9.00 100 for \$80.00	<b>S.P.D.T. (on-off-on)</b> Solder lug terminals \$1.00 each 10 for \$9.00 100 for \$80.00
<b>S.P.D.T. (on-off-on)</b> PC style non-threaded bushing 75¢ each 10 for \$7.00	<b>S.P.D.T. (on-on)</b> PC lugs threaded bushing \$1.00 each 10 for \$9.00 100 for \$80.00	<b>D.P.D.T. (on-on)</b> Solder lug terminals \$2.00 each 10 for \$18.00 100 for \$180.00

**COMPUTER GRADE CAPACITORS**

2,000 mfd. 200 VDC 1 1/4" DIA. x 5" HIGH	\$2.00
3,600 mfd. 40 VDC 1 1/4" DIA. x 3 3/4" HIGH	\$1.00
6,400 mfd. 60 VDC 1 1/4" DIA. x 4 1/4" HIGH	\$2.50
9,700 mfd. 50 VDC 1 1/4" DIA. x 4 1/2" HIGH	\$3.00
31,000 mfd. 15 VDC 1 1/4" DIA. x 4" HIGH	\$2.50
72,000 mfd. 15 VDC 2" DIA. x 4 3/4" HIGH	\$3.50
185,000 mfd. 6 VDC 2 1/2" DIA. x 4 1/2" HIGH	\$1.50

**D.P.S.T. LIGHTED ROCKER SWITCH**

115 vac lighted rocker, snap mounts in 7/8" x 1 1/8" hole. Orange lens. 16 amp contact.  
**\$1.50**

**MINI-PUSH BUTTON**  
S.P.S.T. momentary normally open 1/4" bushing. Red button.  
35¢ each 10 for \$3.00

**KEY ASSEMBLY**  
5 KEY \$1.00 each  
contains 5 single-pole normally open switches. Measures 3/4" long.

**6 KEY** \$1.25 each  
contains 6 single-pole normally open switches. Measures 4 1/4" long.

**METAL OXIDE VARISTOR**

Popular GE # 130L10A varistor 1/4" diameter.  
**\$1.25 each**


**ALL ELECTRONICS CORP.**  
LOS ANGELES, CA STORE  
905 S. Vermont Ave  
213-380-8000  
VAN NUYS, CA STORE  
6228 Sepulveda Blvd  
818-997-1806

MAIL ORDERS TO  
P.O. BOX 24006  
Los Angeles, CA 90006  
TWX - 5101010163 ALL ELECTRONIC  
EASYLINK MBX - 62887748



TOLL FREE ORDERS ONLY  
1-800-826-5432  
(ORDER ONLY)  
(IN CALIFORNIA: 1-800-258-6666)  
ALASKA, HAWAII, OR INFORMATION  
(213) 380-8000 NO C.O.D.!

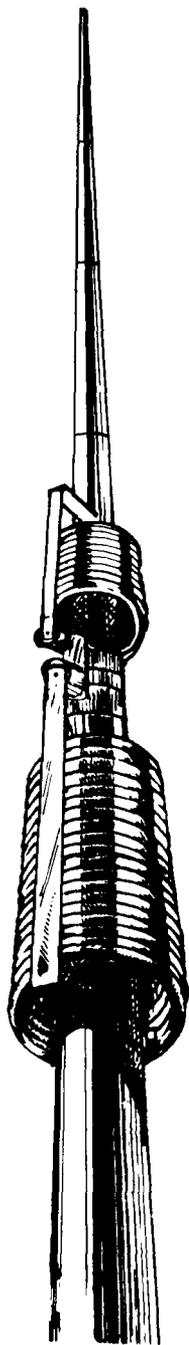QUANTITIES LIMITED  
MINIMUM ORDER \$10.00  
USA \$3.00 SHIPPING  
FOREIGN ORDERS  
INCLUDING SUFFICIENT SHIPPING  
CALIF RES. ADD 6% TAX



# New From Butternut® HF2V DX The 80 & 40 Meter Bands

The HF2V is the perfect complement for the Ham who already has a beam antenna for 10-15-20 meters. Add 80 and 40 meters (160 meters with an optional resonator kit) with a trim-looking vertical that can be mounted almost anywhere.

With the decline in sunspot activity, the HF2V's low angle of radiation will get you DX on the low bands -- even when 10-15-20 meters are "dead."

Automatic bandswitching. No lossy traps. Double wall tubing on the bottom section. Stainless steel hardware. Full 1/4 wavelength on 40 meters.

Height: 32 ft. --Self supporting

Power rating: legal limit


VSWR: 2:1 or less

40 Meters: Full CW & Phone band

80 Meters: 90 kHz

Add-on resonator kits available for 160-30-20 meters.

Write for our **FREE CATALOG.**

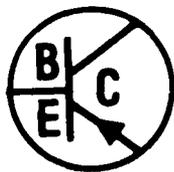

## BUTTERNUT ELECTRONICS

405 East Market Street  
Lockhart, Texas 78644  
(512) 398-9019

### Our Very-Hard to Find Components List

#### Semiconductors

MRF-208	\$12.00	MRF-901	\$ 1.75	MPSH-81	\$ .50	1N6263	\$ .75
MRF-240	18.40	MHW-710-1	61.00	MV2205	.58	2N2907	.60
MRF-247	34.80	2N5944	10.35	LM380N	1.90	2N4401	.75
MRF-309	33.81	MC1330P	1.60	LM565CN	1.65	2N5190	1.50
MRF-421	37.00	MC1350P	1.20	LM741CN	.65	2N5192	1.50
MRF-422	41.40	MC1358P	1.25	1N756A	.55	2N5194	1.50
MRF-429	46.00	MC1458P	.65	1N4001	.25	2N5989	2.80
MRF-454	26.00	MC1723G	2.80	1N4148	.30	2N5990	2.80
MRF-644	27.60	MC3405	2.50	1N4997	1.50	2N5991	3.00
MRF-646	29.90	MC78L08CP	.50	1N5400	.35	2N6486	1.25
MRF-648	33.50	MPS-2222	.35	1N5363A	2.00		

#### Kemet Chip Capacitors

NPO C1210 Size - .50 ea		NPO C1210C Size - .75 ea		NPO C1813 Size - \$1.00 ea		BX C2225 Size	
10 pf	75 pf	470 pf		3300 pf	5600 pf	6800 pf	33µf \$1.90
39 pf	82 pf	560 pf	4.7 pf	.1µf BX			68µf \$3.90
51 pf	100 pf	680 pf					
56 pf	390 pf	1000 pf					

We also carry a line of VHF, UHF amplifiers and ATV equipment. Call or write for our free catalog.

**CCI Communication Concepts Inc.**  
2648 North Aragon Ave. • Dayton, Ohio 45420 • (513) 296-1411

### POPULAR PA 19 Wideband Preamp

- Over 8,000 sold
- 0.5 - 200 MHz
- 19 dB gain
- 50 Ω in/output
- For receivers, counters, transmitter amp stages
- Built, tested & ready-to-go

**ONLY \$9.95 + \$1 shipping**

### NEW POCKET SIZED 500 MHz Freq. Counter

- Fits in your shirt pocket
- Uses 1 9-volt battery
- 4 digit LED readout, 7 digit resolution
- 1 MHz - 500 MHz
- Great addition to shack and toolbox

**ONLY \$34.95 + \$2 shipping**

✓ 123

### DIGITREX

1005 BLOOMER  
ROCHESTER, MI 48063

## MOVING?

KEEP HAM RADIO COMING...

If possible let us know four to six weeks before you move and we will make sure your HAM RADIO Magazine arrives on schedule. Just remove the mailing label from this magazine and affix below. Then complete your new address (or any other corrections) in the space provided and we'll take care of the rest.

**ham  
radio**  
Magazine

Greenville, NH 03048

Allow 4-6 weeks for correction.

Thanks for helping us to serve you better.

Here's my new address:

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

**AFFIX  
LABEL  
HERE**

B biasing is preferred. Since linear devices are so sensitive to heat, special biasing techniques that "track" the heat within the transistor junction and readjust the bias voltage accordingly are required. Furthermore, these biasing techniques must be able to supply high base or emitter current on demand and from a low impedance DC bias source.

The first biasing circuits developed for bipolar linears consisted of a forward biased diode connected to ground and strapped to the package or heat sink as shown in fig. 4A. The series resistor to the power supply was adjusted until the proper collector current, usually designated as  $I_{CQ}$ , was attained. The power transistor idling current is typically 20 to 100 mA and is dependent on the device type and power level. It's usually not critical and often specified by the device manufacturer. Increasing the idling current rarely improves IMD, except on higher order products.

The idling current drawn by this biasing circuitry can be considerable, with 250 to 500 mA a typical value. In addition, this circuit is somewhat sensitive to power supply variations. Many designers, therefore, use 3-terminal voltage regulators in the supply circuit to keep the voltage constant (fig. 4B). The resistor is still used, but it dissipates less power (depending on the regulator voltage). A lower value resistor can be used with one of the newer low voltage adjustable regulators.

In 1973, Communications Transistor Corporation (CTC) introduced the "byistor," a self-contained regulator that incorporated temperature tracking (fig. 4C).<sup>4</sup> This device is actually a diode similar to the base emitter junction of a power transistor in series with a silicon resistor. The final DC source impedance is less than 1.0 ohm. Mounted in a studded package similar to medium power bipolar transistors, it can be attached to the heat sink, close to the transistor being regulated, for very close temperature tracking.

The byistor, like the diode biasing scheme, typically requires 300 to 350 mA of idle current. Some applications

require low power drain. Therefore, in 1976 CTC introduced an alternative device, the Z0-28.<sup>5</sup> This device is actually a power bipolar transistor with two internal diodes (see fig. 4D). The diodes track the bias regulator and the transistor being regulated. The regulator transistor acts like a source follower. Hence this device has very low output impedance and draws high current only on demand.

To set up the Z0-28, a single low-power resistor is placed externally across the device as shown in fig. 4D. This resistor value is adjusted to set the power amplifier idling current. Some Amateurs have reported satisfactory operation by duplicating this device and circuit using discrete diodes (1N4001 types) and a power transistor. Close attention must be paid to adequate coupling to the heat sink to assure temperature tracking.

Other bias circuits have been used. When choosing a bias regulator, remember the following guidelines: the bias regulator circuit must track the temperature of the transistor being regulated and the output impedance of the bias source should be low, typically less than 1 ohm.

### impedance matching

As mentioned earlier, the input and output impedances of bipolar power transistors are very low and often reactive. The typical "L" and "Pi" networks often used with vacuum tubes do not lend themselves to these impedances and devices, since losses may be significant.

The most frequently used matching schemes for high-power bipolar transistors are called "T" networks.<sup>6,7,8</sup> Several are shown in fig. 5. They are particularly adaptable if the input and output impedances of the amplifier itself are 50 ohms, the most common case. Each network has its advantages and disadvantages. Usually only one of the elements has to be varied. However, I prefer the schemes with two variable capacitors because they seem to be the easiest to tune and optimize properly, especially in narrow band

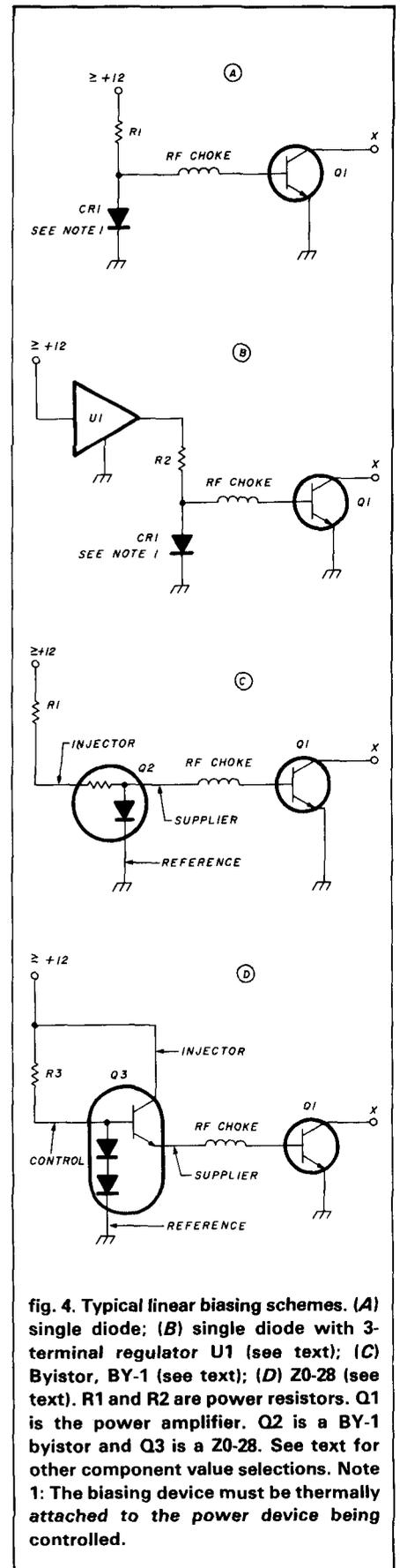


fig. 4. Typical linear biasing schemes. (A) single diode; (B) single diode with 3-terminal regulator U1 (see text); (C) Byistor, BY-1 (see text); (D) Z0-28 (see text). R1 and R2 are power resistors. Q1 is the power amplifier. Q2 is a BY-1 byistor and Q3 is a Z0-28. See text for other component value selections. Note 1: The biasing device must be thermally attached to the power device being controlled.

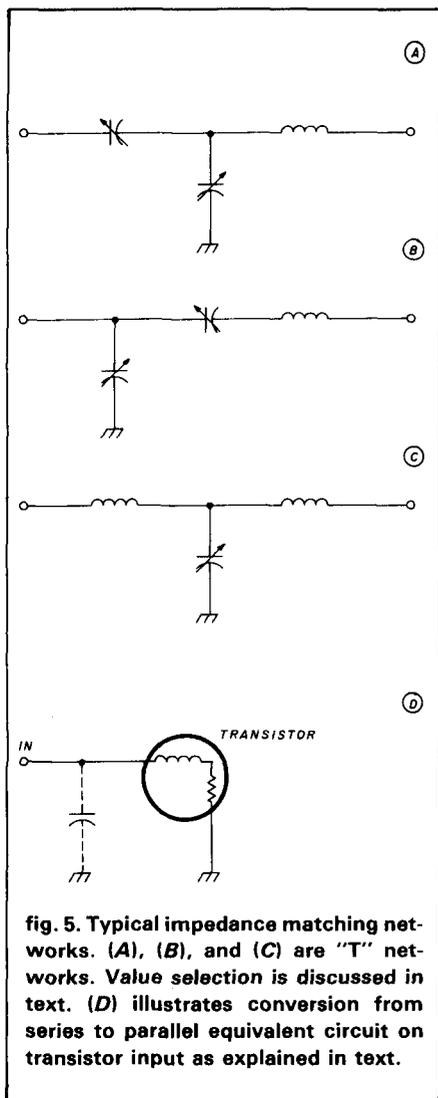


fig. 5. Typical impedance matching networks. (A), (B), and (C) are "T" networks. Value selection is discussed in text. (D) illustrates conversion from series to parallel equivalent circuit on transistor input as explained in text.

applications, and have a built-in DC block.

There is one rather sophisticated trick that is used extensively, especially in the wider bandwidth amplifiers. If the transistor series input impedance has an inductive reactance component (noted by a +j component such as the popular CM10-12A with an input impedance of  $1.5 + j3.5$  ohms), it can be mathematically converted from a series to an equivalent parallel network. Then an appropriate parallel capacitance can be placed at the input of the devices to tune out the inductive reactance as shown in fig. 5D. The transformed input impedance is higher and resistive. This makes the impedance matching network easier to design and with a smaller transforma-

tion ratio. Such techniques have been described elsewhere.<sup>8</sup>

This matching technique is also used extensively by the commercial suppliers of UHF transistors. First they adjust the series inductive reactance by adjusting the lengths of the bonding wires used to attach to the chip. Then they place the appropriate shunt capacitors internally in the package. The net result is more efficiency and greater bandwidth, as well as increased convenience for the circuit designer.

The output network is a function of the output power and the device. First the load impedance must be calculated using eq. 1:

$$RI = \frac{V_{cc}^2}{2P_o} \quad (1)$$

where  $RI$  is the desired output impedance,  $V_{cc}$  is the voltage across the transistor (usually the supply voltage less the saturation voltage of the transistor) and  $P_o$  is the output power in watts. For example, with a 13-volt supply, a 1-volt saturation voltage (typical for most transistors), and a desired output power of 10 watts,  $RI$  is approximately 7.2 ohms. This impedance is then converted in conjunction with the internal device impedance to the desired amplifier output impedance (usually 50 ohms).

Remember that the input network chosen is primarily matching the source (usually 50 ohms) to the power transistor. The output network is designed to yield the optimum load impedance required for maximum output power (as described earlier) with the required circuit loaded  $Q$ . If the proper component values and circuit  $Q$  are chosen, losses will be quite low and harmonics kept to acceptable levels.

Describing all the network requirements and design procedures is beyond the scope of this month's column. For those interested in the subject, I particularly recommend references 6 through 8. Many other papers have also been published. Most semiconductor manufacturers can offer applicable application notes.

Sometimes two power transistors are used, particularly when high power is required. These devices can be fed in parallel using a splitter network (fig. 6A) or with hybrid couplers (figs. 6B or 6C).

Push-pull circuitry is often used at lower frequencies because it tends to cancel the second harmonics. Many modern transistors are now offered in matched pairs in a common package, making this technique very practical. Ninety-degree hybrids are also popular, since if one side of the amplifier fails, the output power drops to only about one-half. Another advantage of the 90-degree hybrid is that the amplifier input impedance match is quite good, since any mismatch is diverted to the external loads,  $R1$  or  $R2$ .

### recommended circuitry

The scope and size of this column do not permit me to describe a cookbook of circuits. Many suitable VHF/UHF power amplifier designs have been described both in Amateur and Commercial publications and on suppliers' data sheets. However, I will provide a universal circuit that can be used on the 2 meter, 135 or 70-cm bands (see fig. 7).

Note, in that circuit, that the input and output networks are similar to those just described. The diode bias network described earlier is also shown because it's very inexpensive; but the Byistor or Z0-28 devices (or their equivalents) are highly recommended as a replacement because they will definitely be more stable and reliable. *The variable capacitor and inductor values are only target values and can be varied slightly to obtain the desired performance.*

Since bipolar power transistors have much more gain below the operating frequency, they are often prone to self-oscillate at a lower frequency. This can usually be completely eliminated by the use of both low value and high value bypass capacitors as well as the network shown as L4 and R3. The low value capacitors should have short leads and be self-resonant well above the operating frequency.  $R1$  is not

# SAVE \$10.00\* with home delivery

\*One year newsstand cost \$30.00

Payment enclosed

Bill me later

\$19.95

\$32.95

\$44.95

U. S. prices only

Here's my address label, enter my subscription,

1 Year . . . . . 12 issues . . . . . \$19.95

2 Years . . . . . 24 issues . . . . . \$32.95

3 Years . . . . . 36 issues . . . . . \$44.95

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Check here if this is your renewal (attach label)

## Subscribe to **ham radio** magazine

Please allow 4-6 weeks for delivery of first issues.

**Foreign rates:** Europe, Japan and Africa, \$28.00 for one year by air forwarding service. All other countries \$22.95 for one year by surface mail.

**Please  
enter my  
subscription**



NO POSTAGE  
NECESSARY  
IF MAILED  
IN THE  
UNITED STATES

**BUSINESS REPLY CARD**

First Class    Permit No. 1    Greenville, NH

Postage Will Be Paid By Addressee

**ham  
radio**

Greenville, NH 03048



# JPC/AZDEN®

## 4000 SERIES FM TRANSCEIVERS

### 10 METERS & DOWN

**\$239**

**SPECIAL PRICE**  
90 DAY WARRANTY

**COMMERCIAL-GRADE  
QUALITY AT AMATEUR PRICES**

**EXCLUSIVE 1 YEAR LIMITED WARRANTY! COMPARE!**



PCS-4000  
2-m FM Transceiver

#### THE 4000 SERIES



PCS-4300 70-cm FM Transceiver



PCS-4500 6-m FM Transceiver



PCS-4800 10-m FM Transceiver

- **WIDE FREQUENCY COVERAGE:** PCS-4000 covers 142.000-149.995 MHz in selectable steps of 5 or 10 kHz. PCS-4200 covers 220.000-224.995 MHz in selectable steps of 5 or 20 kHz. PCS-4300 covers 440.000-449.995 MHz in selectable steps of 5 or 25 kHz. PCS-4500 covers 50.000-53.995 MHz in selectable steps of 5 or 10 kHz. PCS-4800 covers 28.000-29.990 MHz in selectable steps of 10 or 20 kHz.

- **CAP/MARS BUILT IN:** PCS-4000 includes coverage of CAP and MARS frequencies.

- **TINY SIZE:** Only 2"H x 5.5"W x 6.8"D. COMPARE!

- **MICROCOMPUTER CONTROL:** At the forefront of technology!

- **UP TO 8 NONSTANDARD SPLITS:** Ultimate versatility. COMPARE!

- **16-CHANNEL MEMORY IN TWO 8-CHANNEL BANKS:** Retains frequency and standard simplex or plus/minus offsets. Standard offsets are 600 kHz for PCS-4000, 1.6 MHz for PCS-4200, 5 MHz for PCS-4300, 1 MHz for PCS-4500, and 100 kHz for PCS-4800.

- **DUAL MEMORY SCAN:** Scan memory banks either separately or together. COMPARE!

- **TWO RANGES OF PROGRAMMABLE BAND SCANNING:** Limits are quickly reset. Scan the two segments either separately or together. COMPARE!

- **FREE AND VACANT SCAN MODES:** Free scanning stops 5 seconds on a busy channel; auto-resume can be overridden if desired. Vacant scanning stops on unoccupied frequencies.

- **DISCRIMINATOR SCAN CENTERING (AZDEN EXCLUSIVE PATENT):** Always stops on frequency.

- **TWO PRIORITY MEMORIES:** Either may be instantly recalled at any time. COMPARE!

- **NICAD MEMORY BACKUP:** Never lose the programmed channels!

- **FREQUENCY REVERSE:** The touch of a single button inverts the transmit and receive frequencies,

no matter what the offset.

- **ILLUMINATED KEYBOARD WITH ACQUISITION TONE:** Unparalleled ease of operation.

- **BRIGHT GREEN LED FREQUENCY DISPLAY:** Easily visible, even in direct sunlight.

- **DIGITAL S/R F METER:** Shows incoming signal strength and relative power output.

- **BUSY-CHANNEL AND TRANSMIT INDICATORS:** Bright LEDs show when a channel is busy and when you are transmitting.

- **FULL 16-KEY TOUCHTONE® PAD:** Keyboard functions as autopatch when transmitting (except in PCS-4800).

- **PL TONE:** Optional PL tone unit allows access to private-line repeaters. Deviation and tone frequency are fully adjustable.

- **TRUE FM:** Not phase modulation. Unsurpassed intelligibility and audio fidelity.

- **HIGH/LOW POWER OUTPUT:** 25 or 5 watts selectable in PCS-4000; 10 or 1 watt selectable in PCS-4200, PCS-4300, PCS-4500, and PCS-4800. Transmitter power is fully adjustable.

- **SUPERIOR RECEIVER:** Sensitivity is 0.2 uV or better for 20-dB quieting. Circuits are designed and manufactured to rigorous specifications for exceptional performance, second to none. COMPARE!

- **REMOTE-CONTROL MICROPHONE:** Memory A-1 call, up/down manual scan, and memory address functions may be performed without touching the front panel! COMPARE!

- **OTHER FEATURES:** Dynamic microphone, rugged built-in speaker, mobile mounting bracket, remote speaker jack, and all cords, plugs, fuses, and hardware are included.

- **ACCESSORIES:** CS-7R 7-amp ac power supply, CS-4.5R 4.5-amp ac power supply, CS-AS remote speaker, and Communications Specialists SS-32 PL tone module.

- **ONE YEAR LIMITED WARRANTY!**

126

EXCLUSIVE DISTRIBUTOR

**AMATEUR-WHOLESALE ELECTRONICS**

8817 S.W. 129th Terrace, Miami, Florida 33176

DEALER INQUIRIES INVITED

**TOLL FREE... 800-327-3102**

Telephone (305) 233-3631

Telex: 80-3356


MANUFACTURER:

**JPC/AZDEN**

**JAPAN PIEZO CO., LTD.**

1-12-17 Kamirenjaku, Mitaka, Tokyo, 181 Japan.

Telex: 781-2822452

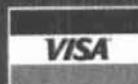

# PACKET RADIO COMES OF AGE

## ANNOUNCING THE FIRST FULLY INTEGRATED

### PACKET RADIO TERMINAL

# THE PACKETERM<sup>®</sup> IPT

Packet radio is a new mode of Amateur communication which is growing more popular every day. It provides armchair, error-free copy for local, national, and world-wide communication. It is also useable with the new generation of amateur satellites.

Networks are growing across the country and in the DX regions through the use of store-and-forward "digipeater" capability built into packet controllers. Enjoy QSOs, called "connects", with other Amateurs across the street or across the country; send messages; swap computer files; access information of general interest; and much more....

### WHY PACKET ??

- \* simultaneous use of a single frequency by multiple stations...without interference. Enjoy rag-chewing or round-tables.
- \* access to computer bulletin boards to read messages, and leave them !
- \* high speed operation...1200 baud
- \* error free transmission of long messages or computer files.
- \* experiment with the newest and fastest growing mode in Amateur Radio.
- \* send messages through SATELLITE to virtually anywhere in the world.
- \* enjoy a whole new world of contest operation, or ...



Packeterm IPT with optional printer  
(sorry, radio not included)

... breath new life into that dusty old 2 meter rig !

## ALL YOU NEED FOR PACKET OPERATION IS... A PACKETERM IPT AND YOUR RIG !

The Packeterm IPT is both a terminal and a full function packet node controller

- \* free your computer from packet duty, or get in on the fun without one.
- \* try portable operation with optional 13.8 volt adaptor

For more information about packet radio and the new PACKETERM IPT,  
or to place your order, contact us at:




**PACKETERM<sup>®</sup>**  
PO BOX 835  
AMHERST, NH 03031  
(603)-673-6630  
monday-friday, 9 am-5 pm EDST



introductory prices:


PACKETERM IPT	\$995
printer	\$349
dc adaptor	\$125

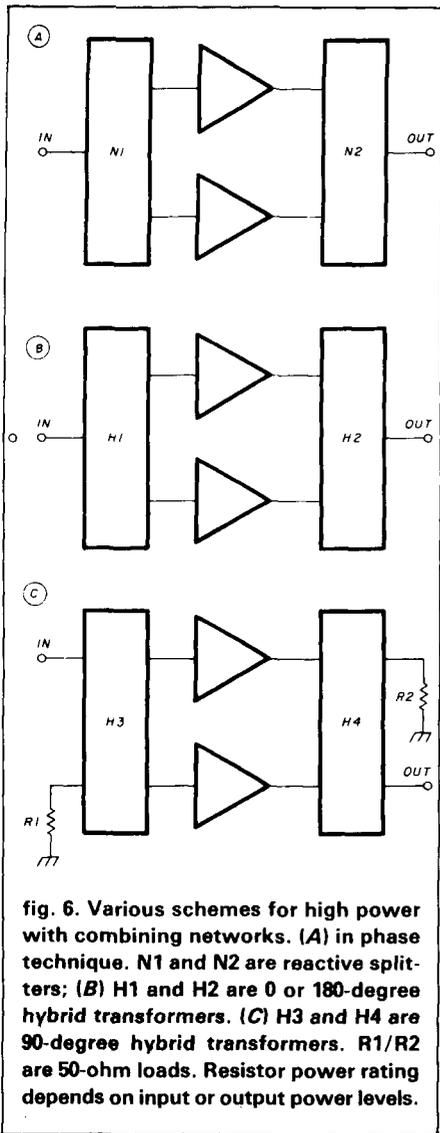

always required, but often helps maintain stability in more stubborn cases. Since the input impedance of the power transistor is low, the value is not too critical.
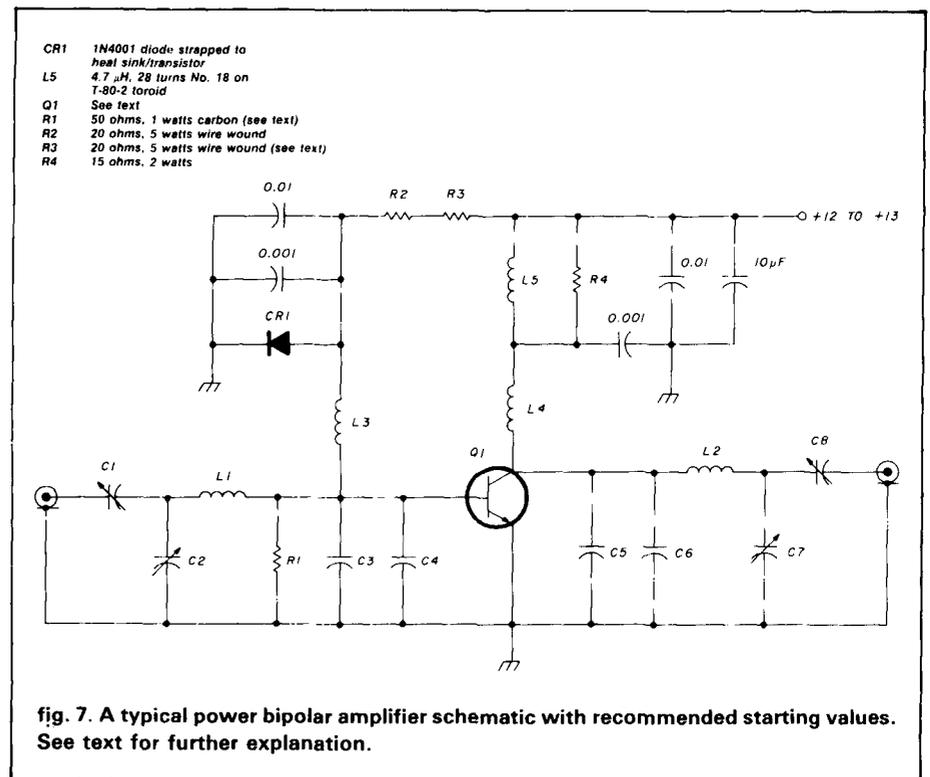
### component selection

The choice of components is very important. All capacitors should have short low-inductance leads and be able to handle the RF current often present when operating at these impedance and power levels. At VHF and low UHF, mica trimmers such as the Arco/Elmenco or equivalent are good for tuning elements. The Unelco type of sandwich micas are suggested for the collector RF choke bypass as well as in the fixed value input and output



part of fig. 7

value	2 meters	135 cm	70 cm	units
C1	8-60	3-35	3-35	pF
C2	3-35	3-35	2-20	pF
C3	150 (Unelco)	100 (Unelco)	33 (Unelco)	pF
C4	150 (Unelco)	100 (Unelco)	22 (Unelco)	pF
C5	not used	100 (Unelco)	33 (Unelco)	pF
C6	not used	50 (Unelco)	33 (Unelco)	pF
C7	8-60	8-60	3-35	pF
C8	3-35	3-35	3-35	pF
L1	2 turns, No. 18, 0.25" ID, 0.25" long	2 turns, No. 18, 0.25" ID, 0.25" long	1.1" x 3/16" copper strap	
L2	2 turns, No. 14, 5/16" ID, 0.25" long	1 turn, No. 16, 0.25" ID,	1.2" x 3/16" copper strap	
L3	0.33 RFC	0.33 RFC	0.1 RFC	microhenry
L4	4 turns, No. 18, 0.25" ID, 0.5" long	3 turns, No. 18, 0.25" ID, 0.38" long	2 turns, No. 18, 0.3" ID, 0.3" long	

matching networks. These capacitors are easy to find at flea markets and are often available from surplus vendors.

At UHF and above, ATC (American Technical Ceramics) or equivalent porcelain chip capacitors are recommended. They have low loss, low inductance (if properly installed) and can handle high RF current without overheating.

Inductors should be large enough to keep the unloaded  $Q$  high.<sup>9</sup> The wire

should also be large diameter, especially on the collector circuit, where, depending on power level, there can be high RF as well as DC amperes of current flowing.

You're probably wondering why I didn't mention microstrip or stripline inductors. These are fine if you're copying a working design, producing many copies of the same amplifier, or are proficient with the use of a Smith chart. However, for the typical one-

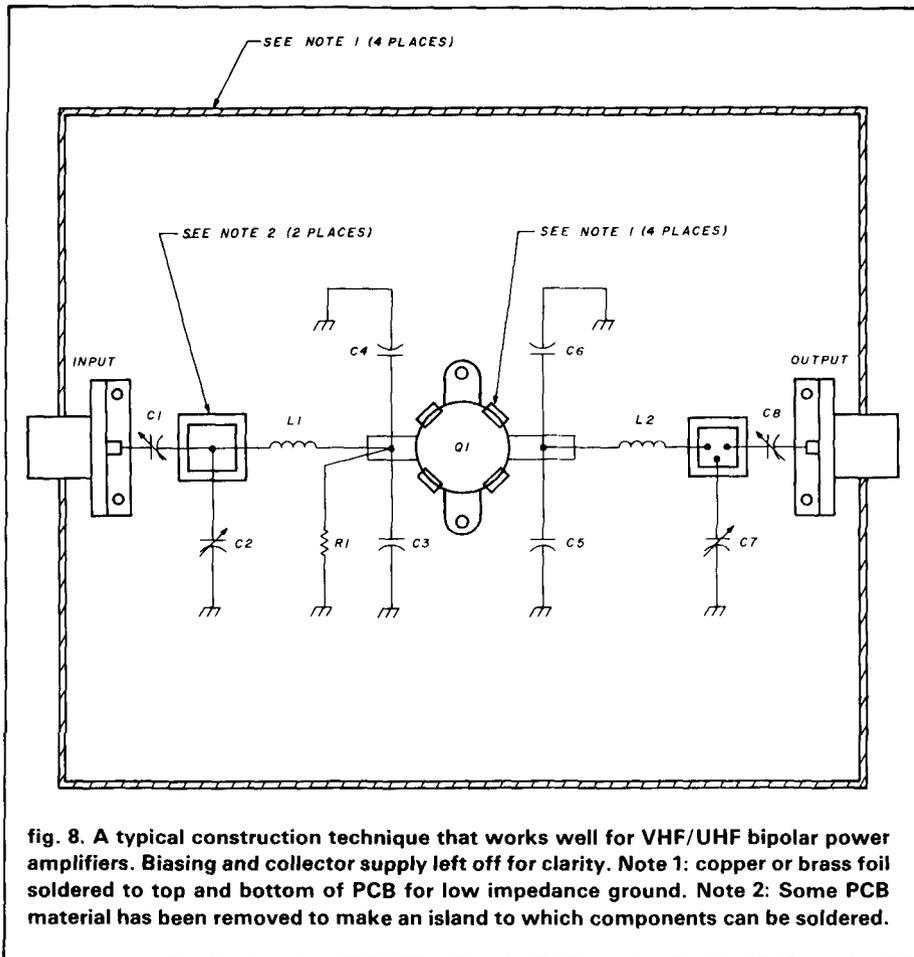


fig. 8. A typical construction technique that works well for VHF/UHF bipolar power amplifiers. Biasing and collector supply left off for clarity. Note 1: copper or brass foil soldered to top and bottom of PCB for low impedance ground. Note 2: Some PCB material has been removed to make an island to which components can be soldered.

shot design that is unproven, the discrete inductor is hard to beat. If you err in the value, just add a turn to or drop a turn from the coil and you're back in business. It isn't easy to cut up, extend, or decrease the length of a microstrip line on a printed circuit board if the tuning is incorrect!

In selecting transistors, choose those that will deliver sufficient power at the frequency of interest at the supply voltage available. As stated earlier, the 12-volt units are usually preferred for availability and price, but 28-volt units with better linearity would be a better choice, especially if you want to stay friendly with your neighborhood Amateurs. Consult manufacturers' data sheets. Don't be tempted to use a transistor at a lower frequency than recommended — it may self-destruct!

There are many power transistor manufacturers such as Acrian,

Amperex, Motorola, RCA, Solid State Scientific, and TRW, to name a few. Order from the many suppliers who offer these devices in small quantities, manufacturers generally have a "minimum order" requirement that can make the per-unit price prohibitive. Many companies sell kits of parts, some even with a PC board. These are highly recommended for the Amateur who doesn't have a large junk box!

### construction techniques

When building power transistor amplifiers, I prefer to build the circuits directly on or above a double-clad PC board type of material similar to the construction technique mentioned in reference 1. The choice of PCB material is not important because it's used only for ease of construction and to keep low impedance grounds.

For best performance, especially on UHF, the edges of the PCB should be

wrapped with a thin copper or brass foil which can then be soldered to both the top and bottom of the board. This insures a good low-impedance ground. Next, drill a hole in the PCB sufficiently large to pass the power transistor package. Likewise, place a similar metal foil around this hole and solder it to the top and bottom of the PCB as shown in fig. 8. This will help keep the emitter (or base, if appropriate) at a low impedance to ground. Gain will not be reduced and the circuit will be more stable.

Then attach the PCB material to an adequately sized heat sink with an appropriate number of sheet metal or machine screws. The input/output connectors can be attached by right angle brackets at the ends of the board. Where appropriate, small squares or islands can be cut with a small sharp knife on the PCB as shown in fig. 8. Variable capacitors and other components can be tack soldered between these islands and grounded for mechanical circuit stability.

### mismatches

Most modern power transistors are quite rugged, especially if they're emitter-ballasted. However, the voltages can soar if the amplifier looks into a high VSWR such as an open circuit. Therefore, always bring drive power up slowly and test for VSWR before running full power. If the VSWR is greater than 2:1, fix the problem before using your amplifier!

### filtering

The harmonic content of a transistor power amplifier is usually quite high. This is why it's important to select the proper circuit operating  $Q$  and low-loss components as just discussed. Fortunately the amount of harmonic output acceptable (usually 40 dB minimum) is easy to obtain. Also your antenna system will often add some margin. If a transistor power amplifier drives a vacuum tube amplifier, the output harmonics will usually be lower due to the extra filtering usually present in tube amplifiers. However, if harmonics are unacceptable (as evidenced by TVI,

etc.), an output low-pass filter may be required.<sup>9</sup>

## heatsinking tips

Several times in this month's column I've stressed heat dissipation as an extremely important parameter when using bipolar power transistors. The thermal resistance or conductivity to the heat sink must be low if long life and reliable operation are to be achieved. All power transistors should be directly attached to a heat sink without an intermediate surface. That is why I recommend the construction techniques above.


Thermal resistance can be kept low by applying a suitable heat sink compound to the transistor base where it mates with the heat sink. Use Dow Corning 340® or an equivalent compound. Mica washers or other objects should be avoided if at all possible.

The size and type of the heat sink is also important. Heat sinks with plenty of radiating fins are highly recommended. It's almost impossible to provide too much heat sink, but remember that the heat must travel away from the device, so the location of the attachment point is most important. Often the sink must be milled slightly to provide room for the nuts on stud packages. Don't remove any more fin area than necessary. (For those interested in choosing the correct heat sink, I strongly recommend that you refer to recent *ham radio* articles on thermal design.<sup>10,11</sup>)


## tuneup and test

At last we get to the bottom line — the final tuneup and operation. A recommended test setup is shown in **fig. 9**.

If the amplifier is operated in linear mode, first set up the  $I_{CQ}$  or collector operating current, as previously discussed. A 100 or 250 milliamper meter is usually sufficient. Temporarily break the collector line, making sure that the biasing circuitry is ahead of the meter. A variable supply is recommended for this step. Increase the supply voltage slowly while monitoring  $I_{CQ}$ . If the recommended current is obtained

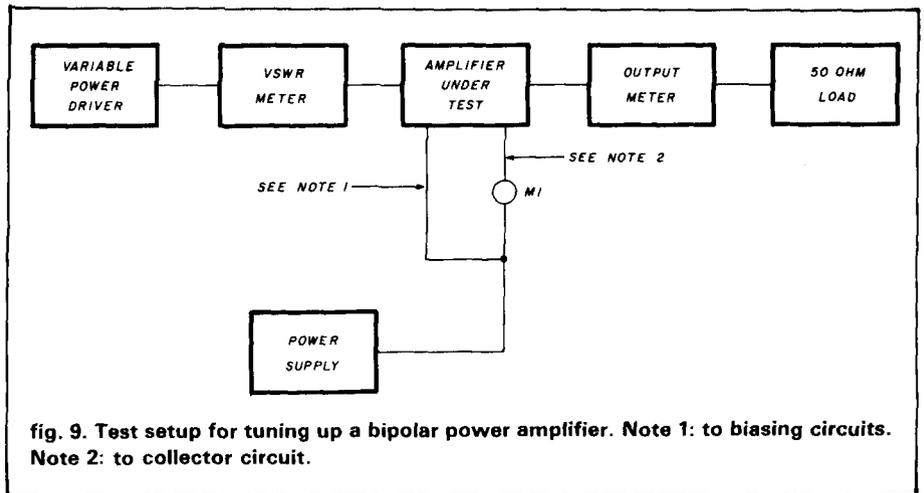

**fig. 9.** Test setup for tuning up a bipolar power amplifier. Note 1: to biasing circuits. Note 2: to collector circuit.

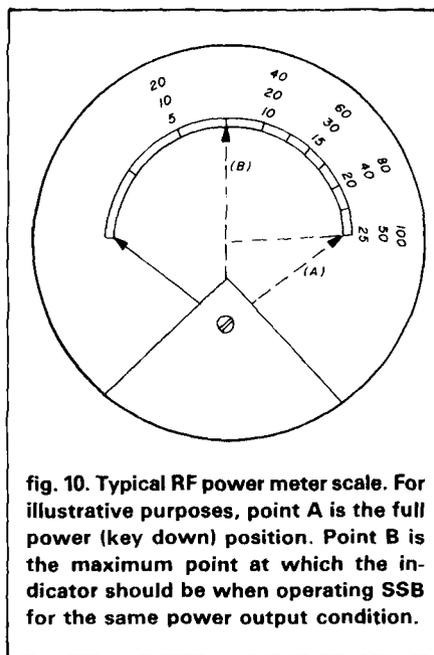

**fig. 10.** Typical RF power meter scale. For illustrative purposes, point A is the full power (key down) position. Point B is the maximum point at which the indicator should be when operating SSB for the same power output condition.

before the final operating voltage is reached, decrease the bias circuit current accordingly. Repeat this test and adjustments until the proper current is reached at the nominal operating voltage. If the transistor is stable and the heat sink adequate, the collector current should remain fairly stable.

Next, short out the meter or put a high current type in its place. Apply a small amount of drive and quickly tune the output network for maximum output power. If none is forthcoming, tune the input network until the device starts to run power and adjust the output for maximum. Keep increasing in-

put power while readjusting both the input and output tuning for maximum output power.

When the final desired or expected power is obtained, check the amplifier input VSWR. If it isn't 1.5:1 or better, adjust the input matching network accordingly. If you can measure collector current at maximum output power, calculate the amplifier's efficiency by dividing the indicated output power by the collector power (collector current times collector voltage). It should be at least 35 to 60 percent, depending on frequency and devices. If it is not, readjust the output tuning slightly to increase efficiency.

The final test is to see whether the amplifier output power is fairly linear. This can best be done by noting the amplifier gain (indicated power output divided by input power) at several power levels. At full power, the gain should be only slightly lower, perhaps 0.5 to 1 dB (80 to 90 percent), below that at lower power levels.

## power meter syndrome

Let me broach one other subject before closing: I call it the "Power Meter Syndrome." Joe Ham tunes up to full power and sees 100 watts indicated on his wattmeter. Then he switches to SSB and proceeds to watch the meter jump around. He's tempted to talk the power up to the same maximum tuneup level on the power meter, thinking that doing so will make him easier to copy at the

other end. Doing this causes splatter galore!

Why? Well, most power meters have some meter damping. What this means is that the indicator is slow to respond. Hence, on a voice peak, the meter will typically indicate only 25 to 30 percent of the peak power. I've illustrated this in **fig. 10**. Also, the maximum output point is probably at compression and therefore the IMD is poor at best. So, if you want to stay friendly with your local competition, keep your level down so that you're running only about 25 to 35 percent of the maximum possible output power as indicated by voice peaks.

### conclusion

The intent of this article was to familiarize you with the bipolar power transistor and its use, rather than to provide a cookbook design approach. For some this will be sufficient. For others it will not be enough. However, with the material presented and the

references provided, you should be able to forge ahead in the direction you choose.

Note: In several previous columns I've mentioned a home computer program called "RF-CAD." It's a very useful tool for designing filters and antennas and for matching, etc. This program is now available for use on the IBM PC or compatible machines. For further details and a list of capabilities, write Gary Field, WA1GRC, 5 Pluff Avenue, North Reading, Massachusetts 01864 (enclose SASE).

### references


1. Joe Reiser, W1JR, "VHF/UHF World: VHF/UHF Exciters," *ham radio*, April, 1984, page 84.
2. Joe Reiser, W1JR, "VHF/UHF World: VHF/UHF High Power Amplifiers, Part 1," *ham radio*, January, 1985, page 97.
3. Joe Reiser, W1JR, "VHF/UHF World: High Power Amplifiers, Part 2," *ham radio*, February, 1985, page 38.
4. Lee B. Max, "The Bystor, a New Device for Linear Amplifier Bias Networks," *CTC Application Note No. 2.08.1D*.
5. Bruce Utter, "20 28, A Bias Device for High Power Amplifiers," *CTC Application Note No. 2.28.2A*.

6. Helge O. Granberg, "A Simplified Approach to VHF Power Amplifier Design," *Motorola Application Note No. AN-791*, 1979.
7. Frank Davis, "Matching Network Designs with Computer Solutions," *Motorola Application Note No. AN-267*, March, 1968.
8. B. Becciolini, "Impedance Matching Networks Applied to RF Power Transistors," *Motorola Application Note No. AN-721*, February, 1974.
9. Joe Reiser, W1JR, "VHF/UHF World: The VHF/UHF Primer: An Introduction to Filters," *ham radio*, August, 1984, page 112.
10. Vaughn D. Martin, "Cooling Semiconductors: Part 1 — Designing and Using Heat Sinks," *ham radio*, July, 1984, page 33.
11. Vaughn D. Martin, "Cooling Semiconductors: Part 2 — Blowers and Fans," *ham radio*, July, 1984, page 33.

### upcoming VHF/UHF events:

- August 3-4: *ARRL UHF Contest*  
 August 12: *Predicted peak of Perseids meteor shower (0130 UTC)*  
 August 20: *EME perigee*  
 September 7-8: *International Region 1 VHF Contest*  
 September 14-15: *ARRL VHF QSO Party*  
 September 16: *EME perigee*  
 September 20-22: *First annual 1296/2304 MHz Conference, Estes Park, Colorado (Contact W0PW).*

ham radio

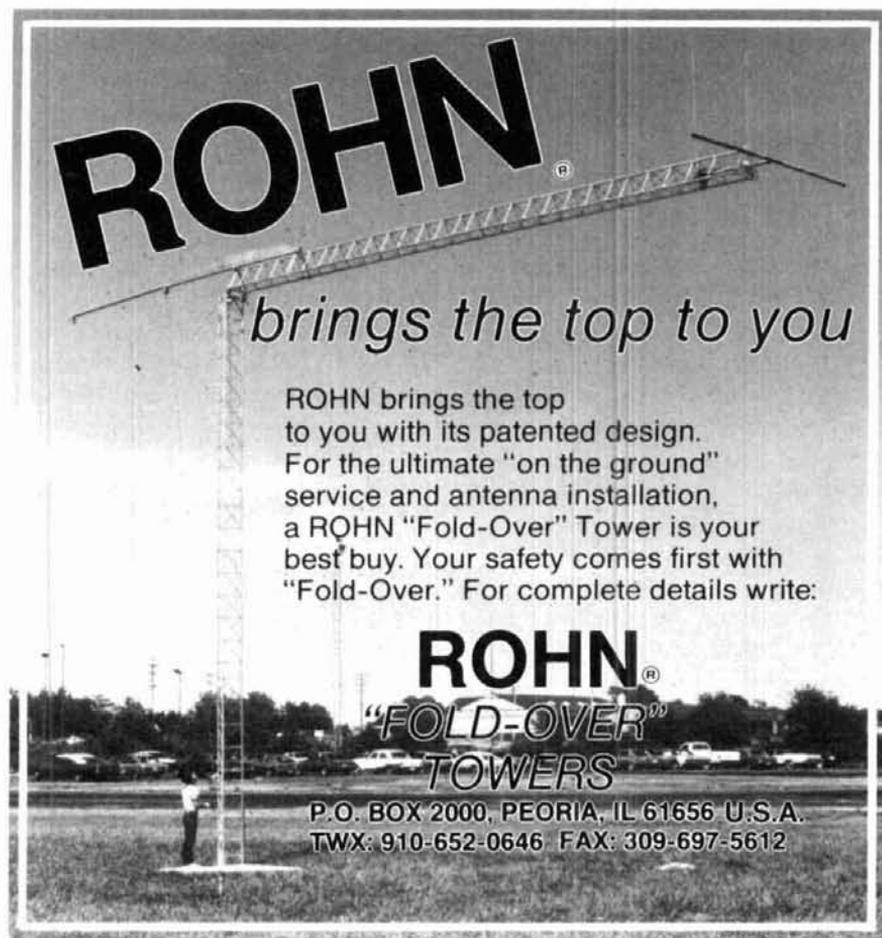

**ROHN**  
*brings the top to you*

ROHN brings the top to you with its patented design. For the ultimate "on the ground" service and antenna installation, a ROHN "Fold-Over" Tower is your best buy. Your safety comes first with "Fold-Over." For complete details write:

**ROHN**  
 "FOLD-OVER"  
 TOWERS

P.O. BOX 2000, PEORIA, IL 61656 U.S.A.  
 TWX: 910-652-0646 FAX: 309-697-5612



**UR CALL UR NAME**  
**BASEBALL CAP**

How about an attractive **BASEBALL** style cap that has name and call on it. It gives a jaunty air when worn at Hamfests and it is a great help for friends who have never met to spot names and calls for easy recognition. Great for birthdays, anniversaries, special days, whatever occasion. Hats come in the following colors: **GOLD, BLUE, RED, KELLY GREEN**. Please send call and name (maximum 6 letters per line).

**UFBC-81** \$6.00

**CRAIG NIACH**  
**I.D. BADGES**

No ham should be without an I.D. badge. It's just the thing for club meetings, conventions, and get-togethers, and you have a wide choice of colors. Have your name and call engraved in either standard or script type on one of these plastic laminated I.D. badges. Available in the following color combinations (badge/lettering): white/red, woodgrain/white, blue/white, white/black, yellow/blue, red/white, green/white, metallic gold/black, metallic silver/black.

**UID** Engraved I.D. Badge \$2.50

Please Enclose \$1.00 to cover shipping and handling

**ham radio** magazine **BOOKSTORE**  
 GREENVILLE, NH 03048



# ICOM

# KENWOOD YAESU



Regular SALE  
 IC-751 9-band Xcvr./1-30 MHz Rcvr. \$1399.00 Call  
 IC-745 9-band Xcvr./1-30 MHz Rcvr. \$ 999.00 Call



IC-271 H 100w 2m FM/SSB/CW Xcvr. \$899 Call  
 IC-271 A 25w 2m FM/SSB/CW Xcvr. \$699.00 Call  
 IC-471 A 10w 430-450 SSB/CW/FM Xcvr \$799.00 Call



IC-02AT Call  
 IC-04AT Call  
 IC-2AT Call  
 IC-3AT Call  
 IC-4AT Call

**IC-R71A  
GENERAL  
COVER RCVR**



Regular SALE  
 TS-930S/AT ..... \$1799.00 Call  
 TS-930A ..... \$1599.00 Call



TS-711A TS-811A ..... Call



TR-2600A Call  
 TH-21A Call  
 TH-21AT Call  
 TH-41A Call  
 TH-41AT Call

**R-2000  
GENERAL  
COVER**



Regular SALE  
 FT-980 ..... \$1659.00 Call  
 FT-DNG ..... Call



FT-726R ..... \$ 899.00 Call



FT-209RH Call  
 FT-709RH Call  
 FT-203RH Call  
 FT-103R Call  
 FT-703R Call

**FRG-8800  
GENERAL  
COVER RCVR**



**SALE!!  
NEW RTTY/CW  
COMPUTER  
INTERFACES**



**THIS MONTH'S  
SPECIAL**

FREE PB-26  
with the purchase of a TR-2600A

FREE PB-21  
with the purchase of a TH-21AT

IC-04AT Yaesu FT-709R  
Call for special price

**MIRAGE  
AMPLIFIER  
SALE!**



**AMERITRON  
AL-80**



## JUN'S

# ELECTRONICS

800-882-1343  
INCLUDES ALASKA  
HAWAII

Calif. Call  
Collect  
for Order

● AMATEUR ● TWO WAY ● MARINE  
● CELLULAR MOBILE PHONE ● SCANNER

- ★ Free U.P.S. Cash Order (Most Item, Most Place)
- ★ Shoppers, call us last, save \$\$
- ★ SE HABLA ESPANOL

(213)390-8003

3919 Sepulveda Blvd.  
Culver City, CA 90230



PROGRAM  
DISK  
NOW  
AVAILABLE

## PACKET RADIO THRU SOFTWARE

AX.25 Protocol By Bob Richardson, W4UCH

You can get on Packet Radio two ways. One is with a sophisticated "black box". The other is by making your computer act like a "black box" by programming it in a high level machine language code. W4UCH has written a machine language program for the Radio Shack TRS-80 Models 1, 3 and 4 computer (Model 4 works with Model 3 disk while in Model 3 mode). This book has twelve chapters plus seven appendices that take you step by step through the process of setting your computer to first convert the digital information into a usable format and then to decode the information.

© 1984 3rd edition

- RE-AX Softbound \$21.95  
 PROGRAM NOW AVAILABLE IN DISK FORM
- RE-MI Model I Disk \$29.00
  - RE-MIII Model III & 4 Disk \$29.00
  - RE-BD SPECIAL BOOK AND DISK \$49.95
- (Specify disc; Mod. I or Mod. III) **SAVE \$2**


Please add \$3.50  
for shipping

ham  
radio  
magazine

## BOOKSTORE

GREENVILLE, NH 03048

(603) 878-1441

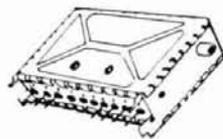

AMNEC EPU 202  
 UHF VARACTOR TUNER  
 REC. CHANNELS: 14 - 83  
 ANTENNA INPUT: 75 Ohm  
 \$12.95 \$11.50 EACH  
 EACH 100 & OVER



24 DB GAIN UHF/VHF/FM  
 ANTENNA/LINE AMPLIFIER  
 AUV-724

75 Ohm in and out ✓ 128  
 \$19.50 EACH 3/\$17.50 EACH

### Accessory Specialties

SHIPPED UPS

P.O. BOX 486 HAWTHORNE, CA 90250

TELEPHONE (213) 324-1973

WE ACCEPT MONEY ORDER, VISA, MASTERCARD

PERSONAL CHECK ORDERS HELD 30 DAYS, NO COD

ADD \$3.50 for Shipping & Handling. CA Residents ADD 6% TAX

# ICOM

IC 745 HF XCVR/Gen Cov. 759 95  
 IC 751 HF XCVR/Gen Cov. 1179.00  
 IC 271A 2m XCVR Special 559.95  
 IC 3200 2m/440 bands 489.95  
 IC 271H 100-watt 2m XCVR 732.95  
 IC 02AT 2m HT, 10 Memories CALL  
 IC 04A1 440 HT/Touctone 299.95  
 M12 12 ch Marine HT 219.95  
 M80 25-watt Marine Scan 387.26  
 M5 all-channel Marine HT 325.95

# KENWOOD

TS-940S HF Transceiver CALL  
 TS-430S HF Transceiver SPECIAL  
 TR-7950 2m mobile, 45W CALL  
 TR-9130 2m All-mode, 25W CALL  
 TR-2600A 2m FM scan HT CALL

# YAESU

FRG 9600 Scanner Intro 549.95  
 FT 757 HF XCVR with mic 699.95  
 FT 980 CAT System 1439.00  
 FRG 8800 SWL Receiver 519.95  
 FT 209RH 2m HT Special 299.95  
 FT 270RH 2m mini 45W 369.95  
 FT 2700RH 25W dual-band 499.95

# SANTEC

ST 142 Handheld 249.95  
 KDK FM 2033 2m 25-watt 259.95

# TEN-TEC

2591 2m Synth Handheld 259.95  
 Century 22 CW XCVR 350.00  
 2510 Model B 410.95  
 CORSAIR Model 560 999.95  
 ARGOSY II 525D Digital 519.95  
 TRITON 425 HF Amp 1.5kW CALL

# Want It? We've Got It!

... at a Discount

## SCANNERS

**REGENCY**  
 MX4000 30-900 MHz 389.00  
 New R1060 10-ch, 6-band 99.95  
 HX2000 HT 120-900 MHz 349.00  
 MX3000 30-ch, 6-band 210.95

**BEARCAT**  
 New 100XL Handheld Call  
 201 16-channel/aircraft 169.95  
 2020 40-ch/aircraft 274.00  
 210XL 195.00  
 300 50-ch scanner/aircraft 341.00

## AMPLIFIERS

**TOKYO HY-POWER**  
 VHF & UHF amps CALL for Quotes  
**DAIWA**  
 LA-2035 2m Amp, 2-30W 68.95  
 LA-2035R 2m Amp/preAmp 74.95

**MIRAGE**  
 B1016 2m Amplifier 10-160 242.95  
 B215 2m Amp 2-150 245.95  
**AMERITRON HF AMPS**  
 AL80 1200 watt 589.95  
 AL1200 1.5 kW Amp 1399.95

**KENWOOD TL922 2kW CALL**  
**AMP SUPPLY**  
 AT 1200A 1200 PEP Tuner 169.95  
 LK 500ZA 2.5 kW hipersil 999.00  
**VOCAM AMPLIFIERS**  
 2 watts-60 watts 2m Amp 107.95  
 2 watts-120 watts 2m Amp 169.95

**TE Systems GaAs FET CALL**  
**ASTRON Power Supply**  
 RS7A 49.95 VS20M 124.95  
 RS50A 189.95 RS50M 209.95

**Compare Our Sample Prices Then Call Toll Free for Orders & Quotes 800-336-4799 (800-572-4201 in VA)**

Hard to get through on the 800 number? Call before 10 a.m. or after 5 p.m. or call one of our regular numbers. If you pay for the call and order, we'll credit your order with \$1.

# ege, inc.

13646 Jefferson Davis Highway  
 Woodbridge, Virginia 22191  
 Information & Service: (703) 643-1063

Store Hours: MTT 10 a-6 p  
 WF: 10 a-8 p, Sat 10 a-4 p

Order Hours: M-F 9 a--7 p, Sat 10 a-4 p  
 Send 3 22¢ stamps for a flyer.  
 Dealer Inquiries Invited



Terms: No personal checks accepted. Prices do not include shipping UPS COD fee \$2.35 per package. Prices are subject to change without notice or obligation. Products are not sold for evaluation. Authorized returns are subject to a 15% restocking and handling fee and credit will be issued to you on your next purchase.

## ANTENNAS

**CUSHCRAFT**  
 A4 4-element 10-15-20m 264.95  
 R3 10-15-20m Vertical 256.95  
 ARX-28 2m Ringo Ranger 34.95

**KLM**  
 KT34A 4-ele 10-15-20m 334.95  
 2m-11X 11-element 2m 59.95

**MOSLEY**  
 CL 33 3-ele Triband Beam 265.95  
 Pro 37 7-ele 10-15-20m 465.95

**HUSTLER**  
 6-BTV 10-80m Vert/30m 128.95  
 MOBILE RESONATORS Reg Super  
 10 and 15 meter 11.95 17.95  
 30 and 40 meters 17.95 25.95

**HY-GAIN**  
 391S TH7DX 10-15-20m 445.00  
 395S Explorer 14 Triband 305.00

**MORE ANTENNAS**  
 AEA Isopoles CALL  
 AVANTI HM 151 36 2m 31.95  
 LARSEN LM-150 5/8 Mag 39.95  
 MINIDUAD HO-1 141.95  
 BUTTERNUT HF6V Vert 109.95

## TOWERS

**UNARCO-ROHN Self-supporting towers:**  
 HBX40 40-foot with Base 198.00  
 HBX48 48-foot with Base 264.00

**Guyed foldover towers:**  
 FK2558 58-foot, 25G 940.00  
 FK4554 54-foot, 45G 1296.00

**Straight Sections:**  
 20G Straight Section 37.95  
 25G Straight Section 48.95

**Tower Packages** CALL  
**TRI-EX & HY-GAIN** CALL  
**Cable by Saxton** CALL  
**Cablewave Hardline** CALL

## ROTATORS

Alliance HD73 98.95  
 Kenpro KR500 Elevation 159.95  
 Hy-Gain Ham IV 229.95  
 Hy-Gain Talltwister TTX 269.95  
 Hy-Gain Heavy-duty 300 530.00

## INTERFACES

**HAL**  
 CWR 6850 Teletreader 746.95  
 CRI 200 RTTY/CW Interface 259.95

**PACKET**  
 AEA PKT1 Packet Controller 459.95  
 Kantronics Packet Controller 339.95

**HARDWARE**  
 MFJ 1224 with MFJ Software 79.95  
 Kantronics interface II 210.95  
 AEA CP-100 interface 284.95  
 AEA CP-1 interface 179.95

**PACKAGES**  
 Microlog AIR-1 Vic-20/C-64 179.95  
 AEA Microamtor Patch 119.95

## SOFTWARE

**Kantronics Hamtext**  
 Vic-20, C-64, Apple CALL

**Kantronics Hamssoft/Amtor**  
 Vic-20, C-64, TRS-80, Atari 69.95

**Microlog AirDisk V20/C64** 39.95  
**AEA Marstext** Vic-20 or C-64 79.95

**Dr. DX by AEA** 95.95  
**Dr. QSO by AEA** 71.95


## ACCESSORIES

**BENCHER PADDLES**  
 Black/Chrome 38.95/48.95

**AEA KEYS**  
 CK-2 Contest Keyer 146.95  
 MM-2 Morsematic Keyer 172.95

**TELEX HEADSETS** CALL  
**MFJ PRODUCTS** CALL  
**B & W PRODUCTS** CALL  
**AMPHENOL** Connectors CALL

# CB-10 FM SPECIAL

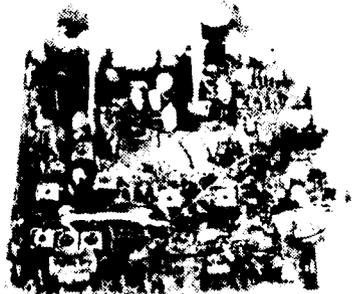

- Hy Gain 40-Channel Board
- 40-Channel Switch
- Volume & Squelch Control
- FM Detector Module
- Full Instructions Included

**\$14.95** Add \$2.00 shipping & handling BOARD ONLY \$6.95

**QRP TRANSCEIVER SET - \$34.95**

**VHF CONVERTER SET - \$24.95**

Add \$2.00 For Shipping & Handling - Send For FREE Brochure

SEND \$2.00 FOR FULL MANUAL WITH CIRCUIT DIAGRAMS

MANY OTHER MODULES AVAILABLE

**MORNING DISTRIBUTING CO.**

P.O. BOX 717, HIALEAH, FLA. 33011  
 (305) 884-8886

# HOBBY KITS®

EXPERIMENT - LEARN ELECTRONICS  
 BUILD AND DESIGN YOUR OWN AM, FM, CW,  
 OR SSB RECEIVERS, TRANSMITTERS AND ETC.  
 WITH OUR MINI-LINEAR CIRCUIT KITS  
 All kits Come Complete With Etched and Drilled Circuit Boards  
 and All Parts Needed To Function As Described

- AFA-1 AUDIO AMP, LM 380 1-2 Watts 4-16 OHM Output \$4.95
- AFP-1 AUDIO PREAMP, Dual Audio Preamp - For Mike Etc \$3.95
- BMD-1 BAL. MIX, LM 1496 Mixer - S B Modulator Tuned Output \$9.95
- DET-1 AM DET, Am Envelope Detector With AGC Output \$3.95
- DET-2 FM DET, LM 3065 FM Detector (455 KHZ or 4-11 MHz) \$7.95
- DET-3 SSB DET, LM 1496 SSB Detector (Needs OSC-1 or OSC-4) \$9.95
- DET-4 DETECTOR CW/SSB using a dual gate FET transistor \$4.95
- IFA-1 IF AMP, CA 3028 30 DB Gain, Optional AGC (455 KHZ or 9-11 MHz) \$6.95
- FLS-9 SSB FILTER 9 MHz 2:1 KHZ BW with USB XAL for OSC-1 \$49.95
- IFA-2 IF AMP, CA 3028 30 DB Gain, 1 100 MHz Optional AGC \$6.95
- MBA-1 FREQ. MULT, Tuned Output Buffer Mult. Amplifier To 250 MHz \$5.95
- OSC-1 CRYSTAL OSC, 100 KHz - 20 MHz Not Tuned \$3.95
- OSC-2 CRYSTAL OSC, Ov. 18-200 MHz Tuned Output \$4.95
- PSV-1 POWER SUPPLY LM 723 With Pass Transistor 3 amps max \$7.95
- PLL-2 TONE DETECTOR LM567 PLL Tone Detector \$5.95
- RF/MIX-1 RF-AMP/MIXER CA 3028 - Tuned RF AMP/Mixer 1-100 MHz \$7.95
- RF/MIX-2 RF-AMP/MIXER 3N204 Tuned RF AMP/Mixer 1 - 250 MHz \$7.95
- VCO-3 VARIABLE HI STAB. OSC, Varactor tuned 400 to 600 KHz output \$7.95
- VCO-4 VARIABLE HI STAB OSC, Varactor tuned 3 to 20 MHz output \$7.95

Add \$2.00 For Shipping & Handling - Send For FREE Brochure

SEND \$2.00 FOR FULL MANUAL WITH CIRCUIT DIAGRAMS AND

TYPICAL RECEIVER AND TRANSMITTER HOOK-UPS

MANY OTHER MODULES AVAILABLE

**MORNING DISTRIBUTING CO.**

P.O. BOX 717, HIALEAH, FLA. 33011

## THINGS TO LOOK FOR (AND LOOK OUT FOR) IN A PHONE PATCH

- A patch should work with any radio. AM, FM, ACSB, relay switched or synthesized.
- Patch performance should not be dependent on the T/R speed of your radio.
- Your patch should sound just like your home phone.
- There should not be any sampling noises to distract you and rob important syllables. The best phone patches do not use the cheap sampling method. (Did you know that the competition uses VOX rather than sampling in their \$1000 commercial model?)
- A patch should disconnect automatically if the number dialed is busy.
- A patch should be flexible. You should be able to use it simplex, repeater aided simplex, or semi-duplex.
- A patch should allow you to manually connect any mobile or HT on your local repeater to the phone system for a fully automatic conversation. Someone may need to report an emergency!
- A patch should not become erratic when the mobile is noisy.
- You should be able to use a power amplifier on your base to extend range.
- You should be able to connect a patch to the MIC and EXT. speaker jack of your radio for a quick and effortless interface.
- You should be able to connect a patch to three points inside your radio (VOL high side, PTT, MIC) so that the patch does not interfere with the use of the radio and the VOL. and SQ. settings do not affect the patch.
- A patch should have MOV lightning protectors.
- Your patch should be made in the USA where consultation and factory service are immediately available.

**ONLY  
PRIVATE PATCH III  
GIVES YOU ALL  
OF THE ABOVE  
BEWARE OF INFERIOR  
IMITATIONS**

**N  
E  
W**

# PRIVATE PATCH III

## SIMPLEX SEMI-DUPLEX INTERCONNECT

**N  
E  
W**



With an amazingly low price, the all new PRIVATE PATCH III is the most powerful personal phone patch system available. You can use it simplex, repeater aided simplex (from your base) or semi-duplex (at the repeater). That's right, you will never have to buy another patch. PRIVATE PATCH III does it all! There are many new and important features which were formerly only available in our top commercial models.

With a flick of the new connect switch you can patch your friends on the repeater into the phone system. One of them may need to report an emergency!

No hassles with busy signals! If you call a number that is busy, just put your MIC down and relax. PRIVATE PATCH III will disconnect automatically.

The new CW ID keeps you completely informed as to patch status. ID occurs when you access and again when you disconnect. ID is also sent after toll call attempts, all automatic disconnects, manual disconnect and when timeout is imminent. And of course your CW ID chip is free.

PRIVATE PATCH III does not interfere with the normal use of your base radio. A new audio pre-amp permits audio take off before the VOL. control. As a result, the VOL. and squelch settings do not affect patch operation. Of course you can also connect PRIVATE PATCH III to the MIC and EXT speaker jacks as before.

A new digit counting system makes the toll restrict positive even in areas where you do not have to dial "1" first. A secret five digit code disables the toll restrict for one toll call. Re-arm is automatic.

Additional new features: MOV lightning protection — Three digit access code (eg. \*93) — Spare relay position on board — Plus former features: 3/6 minute timeout timer — Digital fast VOX (pat. pend.) — 115 VAC supply — Modular Jack and cord plus much more!


Please write or call for our four page brochure to get the complete story.

Options:  
FCC approved coupler  
12 VDC or 230 VAC power

Warranty? Yes, one full year!

### DEALERS

- |   |   |
|---|---|
| <b>AMATEUR ELECTRONIC SUPPLY</b><br>Milwaukee WI, Wickliffe Oh,<br>Orlando FL, Clearwater FL,<br>Las Vegas NV | <b>JUNS ELECTRONICS</b><br>Culver City CA, Reno NV            |
| <b>COLES COMMUNICATIONS</b><br>San Antonio TX   | <b>MIAMI RADIO CENTER CORP.</b><br>Miami FL                   |
| <b>ERICKSON COMMUNICATIONS</b><br>Chicago IL  | <b>MIKES ELECTRONICS</b><br>Ft. Lauderdale, Miami FL          |
| <b>HAM RADIO OUTLET</b><br>Anaheim CA, Burlingame CA,<br>Oakland CA, Phoenix AZ,<br>San Diego CA, Van Nuys CA | <b>N&amp;G DISTRIBUTING CORP.</b><br>Miami FL                 |
| <b>HENRY RADIO</b><br>Los Angeles CA, Anaheim CA,<br>Butler MO  | <b>PACE ENGINEERING</b><br>Tucson AZ                          |
|   | <b>THE HAM STATION</b><br>Evansville IN                       |
|   | <b>CANADA:</b><br><b>DOLLARD ELECTRONICS</b><br>Vancouver, BC |

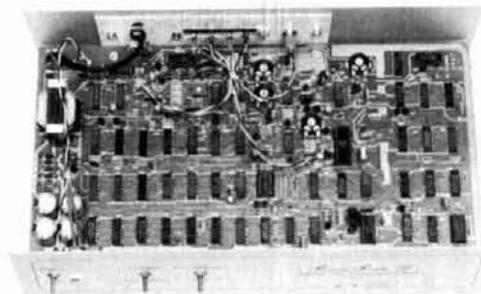

**CONNECT SYSTEMS INCORPORATED** (213) 373-6803 ✓ 131  
23731 Madison St., Torrance, CA 90505

# ATU-1000™

## Advanced Terminal Unit

**NEW!**



**More Hardware Features And Performance Than Any Other Morse, Baudot, ASCII, AMTOR, SITOR, or H.F. Packet Terminal Unit Anywhere At Any Price!**

We recognize that there are few amateurs who can appreciate or afford the outstanding value of the ATU-1000, but those who can are in for some very pleasurable operating. The ATU-1000 is a commercial/military unit with all the performance and flexibility that is attainable from today's technology. Just check out the features below.

- 32 poles, active filtering
- Morse/Baudot/ASCII/AMTOR/SITOR/H.F. Packet
- Set receive filters to one Hz accuracy
- Set receive MARK & SPACE filters independently from 1000 to 3000 Hz
- All shifts, 170 Hz fixed or 0 to 2000 Hz adjustable
- Set AFSK output tones independently from 1000 to 3000 Hz to one Hz
- 5mV to 5V AGC
- Front-panel squelch control
- Built-in 4 digit counter
- CW filter adjustable 700 to 2500 Hz
- D.C. coupled automatic threshold correction
- Twin full-wave detectors
- Built-in TTL/RS-232/and loop keyer I/O
- Discriminator-type tuning indicator
- FSK, AFSK, and scope outputs
- 13 VDC operation, 110 VAC adaptor supplied
- TTL I/O logic inversion for use with virtually any software
- Optional 19 inch rack mount kit


Ask your favorite dealer for a demonstration of the world's finest RTTY/CW advanced terminal unit/computer interface—the AEA model ATU-1000. If you cannot see your dealer, send for our latest specification sheet.

*Prices & Specifications Subject To Change  
Without Notice Or Obligation.*

**Advanced Electronic Applications, Inc.**  
P.O. BOX C-2160 • LYNNWOOD, WA 98036  
(206) 775-7373 • TELEX: 152571 AEA INTL

**AEA**

**Brings you the  
Breakthrough!**

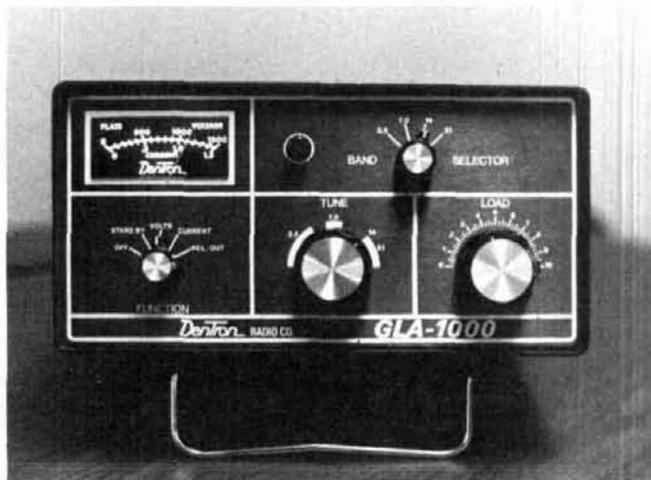

Individual  
cathode bias  
does the trick

## stop blowing finals in the GLA-1000 amplifier

The Dentron GLA-1000 linear amplifier, introduced in 1978, has since become popular with HF operators on both sides of the Atlantic. Measuring only 11 × 5-3/4 × 11 inches (27 × 13.7 × 27 cm), this compact amplifier runs up to 1200 watts PEP input when driven by any of the popular 100-watt SSB transceivers. The amplifier uses four tubes in parallel operated in grounded grid configuration with 1200 volts on the anodes.

Though the tubes are capable of supplying the rated output with ease, problems were encountered often in daily use. The techniques used for solving the problem are applicable to all amplifiers with similar bias arrangements.

### tubes destroyed with high SWR

My GLA-1000 linear amplifier operated well for the first three months until operation was attempted on 15 meters into a 3:1 SWR. The AC fuse blew and examination revealed that all the tubes were ruined. A replacement matched set of tubes was acquired from Dentron and installed, but suffered a similar fate when an accidental mismatch occurred.

In despair, I contacted Dentron for advice. They rec-

ommended updating the GLA-1000 into the latest GLA-1000B using a tuned circuit kit, a new grid bias zener diode, and add-on resistors for the anode parasitic chokes.



The original amplifier section of the unit is shown in skeleton form in fig. 1, which clearly depicts the bias arrangement.

### tuned input kit

The modification kit replaces the fixed filter at the input with a PC board containing five pretuned pi circuits. These reduce the input SWR and improve the power transfer from the transceiver while filtering unwanted harmonics.

The zener diode in the modification kit is a 24-volt 1N3321 that replaces the original 9.1 volt 1N3308. This increases the negative grid bias, which reduces the no-signal anode current to 150 mA and reduces both the overall dissipation and the peak currents under drive conditions.

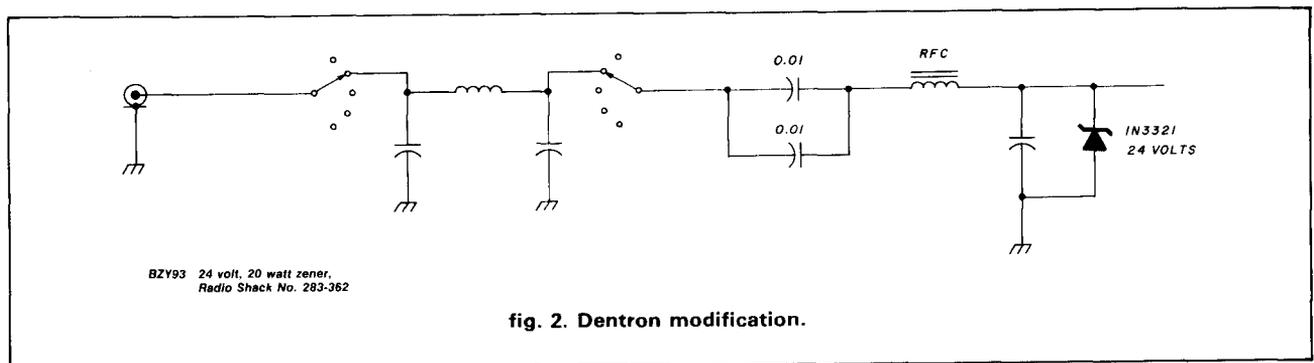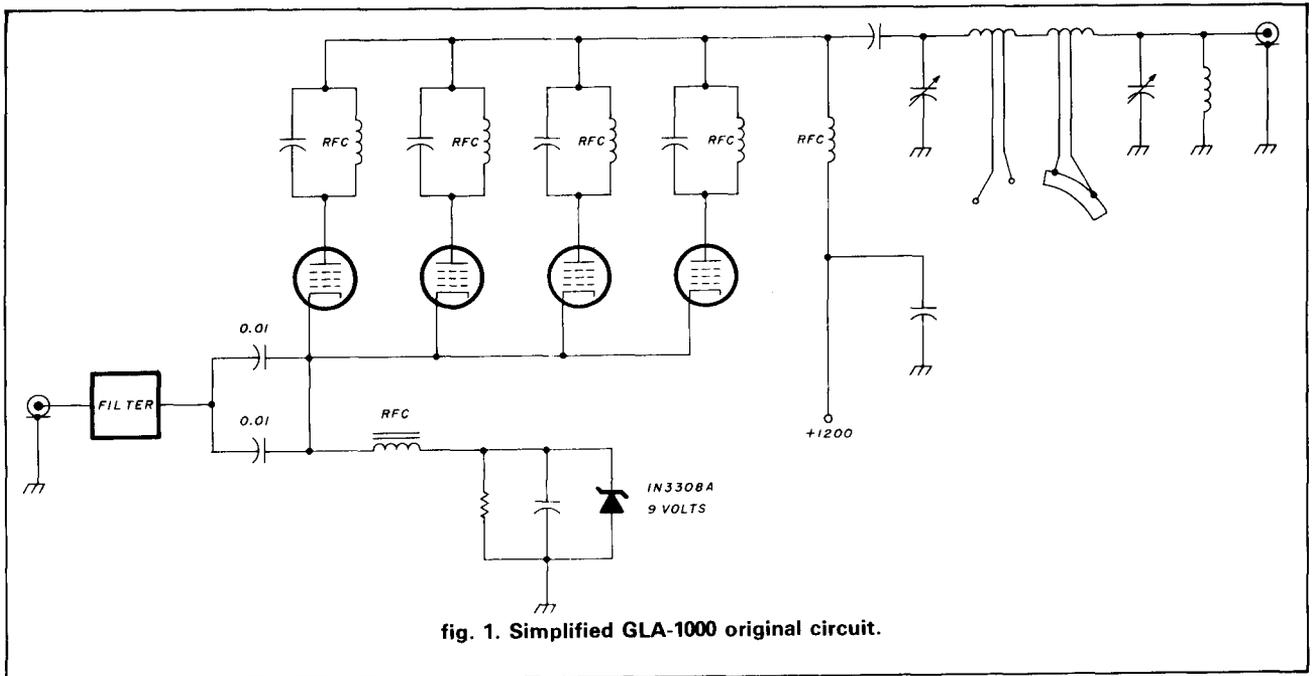By **A. J. Nailer, G4CFY**, 12 Weatherbury Way, Dorchester, Dorset, England DT1 2EF, and **G. J. Morgan, G3ROG**, 1 Saint John's Mead, Saint John's Street, Winchester, Hampshire, England



The four 100-ohm resistors added to the anode parasitic chokes are included to reduce their  $Q$ , which may prevent possible VHF instability.

A simplified diagram of the modified circuit is shown in **fig. 2**.

After modification, the third set of PA tubes lasted twelve months until an open circuit antenna feeder caused their demise together with the new zener diode. The circuit arrangement is far too critical of any mismatch, and instead of providing a fail-safe condition, it always destroys the costliest circuit components.

### reason for sensitivity

Examination of the modified circuit reveals that the pi input circuit would not help power sharing between the tubes but would make the input look close to 50 ohms on all bands. While this is obviously an advan-

tage to owners of all solid-state transceivers, it is of little help to operators of transceivers with tube power amplifier PAs that include their own pi output networks.

The zener diode replacement, obviously intended to control performance, does not accommodate unmatched sets of tubes. This is especially true if one tube is very different from the others. Under such circumstances the bad tube either shuts down by going gassy or shorts. In the shut-down case the remaining tubes would overdissipate and successively fail, just like dominos falling down. This is what appears to have happened the first two times. The third catastrophe would indicate a short circuit tube that blew the zener and left the remaining tube with no negative grid bias.

The bias is developed by drawing the cathode current of all four tubes from the single zener diode. This places the cathodes positive with respect to the grounded grids by the value of the zener voltage.

With the replacement of the Motorola zener diode likely to be expensive, drastic modifications to provide a separate bias supply were considered.

To control tube conditions both dynamically and quiescently, bias has to be supplied to each tube's cathode. This, together with the zener bias, would ensure equal power sharing. The idea was taken from the common practice used with parallel transistor stages, in which balancing resistors are used in the base or emitter circuit to overcome differences in base/emitter voltages and to ensure equal power sharing. **Figures 3 and 4** show typical transistor power-sharing circuits.




Automatic bias is provided simply by adding a resistor in the cathode so that cathode current produces grid bias. The value of resistor has to be chosen with


care so that it does not drop too many volts on current peaks and cause flat topping. Nevertheless, it has to be large enough to cause about 1 volt change of bias for a 50 percent change of cathode current. With a combined current of 150 mA, each tube should be drawing 37.5 mA, about right for most class AB1 tube finals. A 50 percent change would be 18.75 mA, so for 1 volt the automatic bias resistor  $R_X$  would be

$$R_X = \frac{1V}{18.75 \text{ mA}} = 53.33 \text{ ohms,}$$

(a 56 ohm resistor was chosen).

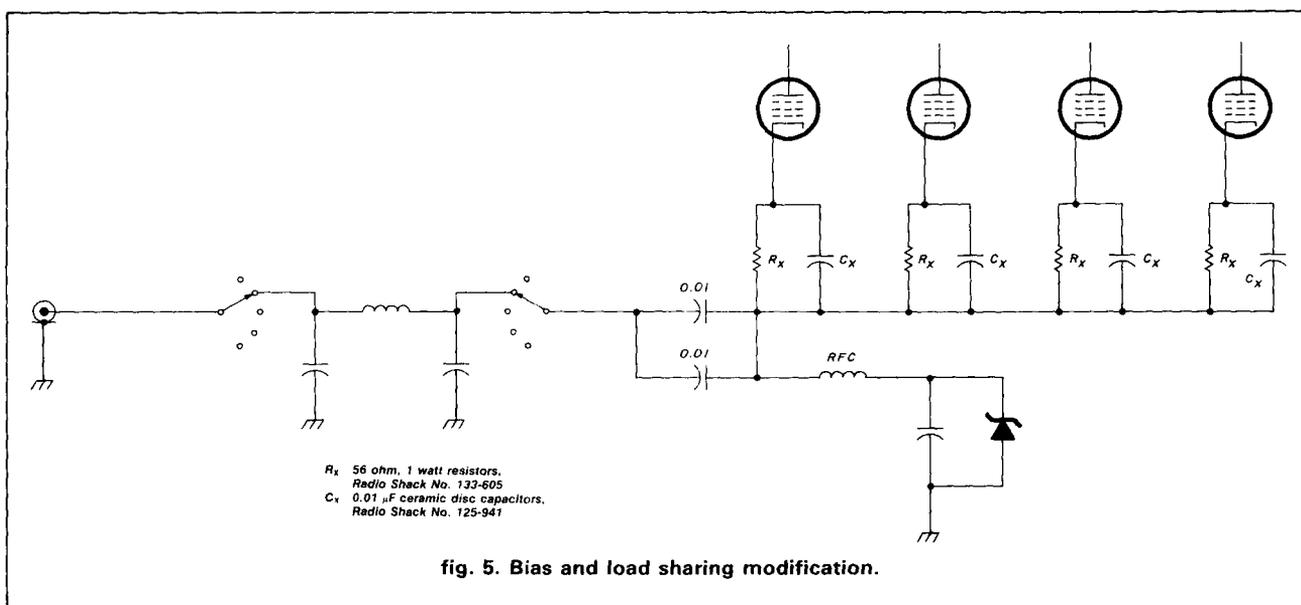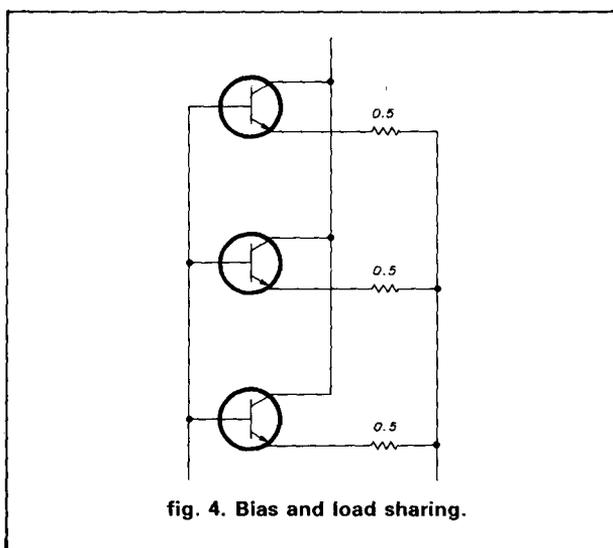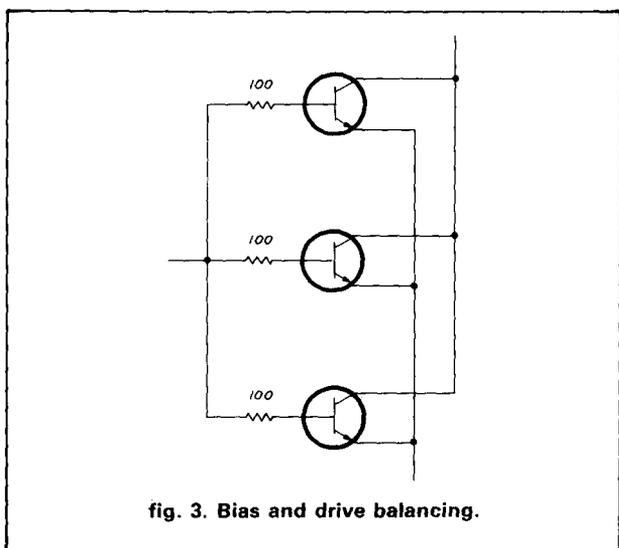However, since the signal is also applied to the cathodes in this configuration, the 56-ohm resistors in series would cause appreciable loss of drive and also mismatch the newly installed pi input circuit. To over-



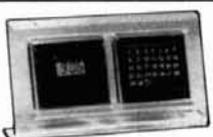

RECEIVE THIS LCD CALENDAR/CLOCK FREE WITH YOUR SUBSCRIPTION

## WHAT'S REALLY HAPPENING IN HOME SATELLITE TV?

# STV THE HOME SATELLITE TELEVISION MAGAZINE™

A monthly of 100-plus pages—has everything you need to know about where to find equipment, how to install it, system performance, legal viewpoints, and industry insights! With your subscription to STV® you will receive a FREE LCD Calendar/Clock.

- Only \$19.95 per year (12 monthly issues)
- \$1.00 for sample copy

IF YOU HAVE A SATELLITE SYSTEM, THEN YOU REALLY NEED ...



# OnSat

The best in satellite programming! Featuring: ★All Scheduled Channels ★Weekly Updated Listings ★Magazine Format ★Complete Movie Listing ★All Sports Specials ★Prime Time Highlights ★Specials Listing and ★Programming Updates!

- Only \$39.00 per year (52 weekly issues)
- 2 Years \$69.00 (104 weekly issues)
- \$1.00 for sample copy

Visa® and MasterCard® accepted (subscription orders only). All prices in US funds. Write for foreign rates.

Send this ad along with your order to:

**STV®/OnSat®**

P.O. Box 2384—Dept. HR • Shelby, NC 28151-2384

**SUBSCRIPTION CALLS ONLY**

**TOLL FREE 1-800-438-2020**

come this, each resistor could be bypassed to RF by a low reactance capacitor. A value was chosen by trying standard values in the formula  $X_c = \frac{1}{2\pi fC}$  where it was found that 0.01  $\mu$ F was 4.55 ohms at 3.5 MHz and 0.57 ohm at 28 MHz.

The new circuit configuration is shown in fig. 5.

### construction details

The tube sockets in the GLA-1000 are mounted on a PC board. A scale drawing of this is shown in fig. 6. The 0.01  $\mu$ F bypass capacitors,  $C_X$ , are attached to the resistors as shown and wired across the breaks marked on the tracks connecting pins 3 of the tubes.

A suitable alternative to the 1N3321 zener is the BZY93 24-volt type. Available at low cost, it has a stud anode instead of cathode. It can be fitted into the hole used by the old diode but must use an insulating kit and solder tag to pick up the positive stud. Use a grounding strap on its wire end.

### performance

It was well over a year since the modification was done. Since that time, the unit has undergone intense activity and repetitive abuse. The absence of TVI complaints suggests that the modification has not degraded signal purity in any way. The peak output power is easily achieved and appears stable under continued full power operation.

The current sharing technique prevents the "domino effect" breakdown under fault conditions. This was convincingly demonstrated when a severe mismatch caused the AC fuse to blow — but nothing else was damaged!

The amplifier was designed to use selected and matched tubes designated D50 by Dentron. Nevertheless the third and fourth sets were standard type 6LQ6 manufactured in the USA. Tube types 6LQ6, 6JE6, or 6MJ6 may be used, although idling currents may differ sufficiently to require adjustment of the bias zener voltage to give between 35 and 40 mA quiescent current. The 6LQ6 tube and the 6MJ6 type, which are capable of higher power at lower frequencies but unsuitable for 10-meter use, are both readily available. Although Japanese tube substitutions were found to be unstable in this design, both before and after modification, they appear to provide higher gain. The American types are the lowest cost and have shown no signs of instability. (Higher power types 6MJ6 have not been tried at any time.)

This modification has been so successful that I've shelved my half-built homebrew 813 linear. Undoubtedly the principles involved can be extended to other linears of similar design and should result in greatly extended tube life.

**ham radio**

# Message Master™

**Real-voice message system  
For any repeater or base**

Now you can communicate vital information even when the station you are calling is not on the air — with Message Master. Message Master is a solid state voice recording system which can record messages just by listening to you speak, store messages in memory, and deliver messages on demand. If you can't be there to deliver your messages let Message Master deliver them for you - any messages in any language and in your own voice!

Message Master connects easily to any radio system for remote access: repeaters, base stations, even transceivers. It can even be connected to an autopatch device to exchange messages between your radio system and the telephone network.

Message Master is a multi-user system with mailbox style personalized message service for a hundred users. With 8 minutes of message storage it can store hundreds of messages simultaneously making it ideal for large, active repeater groups.

Would you like your callsign identifications, tail messages, and bulletin messages sent in real-voice? Message Master can send them too. Record several identification messages and it will even send a different ID each time. Almost like magic, Message Master knows when to send identifications and tail messages so it needs no special control signals from your base or repeater.

Call or write for further information before you make another wasted call.

Commercial users: Ask for a brochure on the Message Master Electronic Dispatcher with group and all call messaging.



- **Create messages just by talking.** Message Master's 'real-voice' technique saves YOUR VOICE in digital memory to deliver messages in your own voice, language and dialect.
- **Mailbox-style operation gives individual message delivery service to 100 system users.**
- **Easily added to any repeater or base station for remote operation with only four connections.**
- **Special features include callsign identifications, tail messages, and bulletin messages.**
- **Digital message storage provides instant playback of stored messages.**
- **Modular memory meets your exact needs from 2 to 8 minutes of total message storage.**

## Serving all your repeater needs

- *Mark 4 Repeaters and Repeater Controllers are THE PERFORMANCE LEADERS with real voice, more autodial numbers, more synthesized voice and more features.*
- *Mark 3 Repeaters offer the winning combination of high performance and high value.*
- *LR-1 Repeaters boast superb RF circuitry at an economical price.*
- *MR-4 Receivers with 7 helical resonators are the only receivers to choose in harsh RF environments.*
- *PA-100 Amplifiers with rugged TMOS power FETs give you a continuous duty high power signal.*

**COMING SOON:** A 4-channel receiver voting system which operates on true signal-to-noise ratio to extend your coverage by linking to remote receivers.



**KENDECOM INC.  
MICRO CONTROL SPECIALTIES**

23 Elm Park  
Groveland, MA 01834  
(617) 372-3442







THE OPRYLAND HOTEL

# SPACE/STTI NASHVILLE SHOW! THE OPRYLAND HOTEL NASHVILLE, TENNESSEE SEPTEMBER 2-3-4, 1985

There is no place on the globe quite like Nashville — The Music Capital of the World! Everybody who goes there loves it and everybody who leaves wants to hurry back!

SPACE and STTI take great pride in bringing by popular demand the '85 Fall edition of Satellite TVRO Industry's largest Seminar/Trade Shows back for the third year to the beautiful, world-renowned Opryland Hotel in Nashville, Tennessee!

Three huge Exhibit Halls will feature 640 booths showing the latest in private terminal satellite television systems! The Exterior Exhibit Area will display over 400 operating antennas! And numerous Meeting Rooms will house the Extensive Seminar Training Programs!

Attendance fee for the entire SPACE/STTI Nashville Show '85 is only \$40. Special fee for spouse is \$5. Children under 18 admitted free. Special discounts for pre-registration and SPACE dealer members.

For Convention Details: Call or write STTI, Box G, Arcadia, Oklahoma 73007. 1-800-654-9276 (in Oklahoma or outside U.S.A., call 405-396-2574).



OPRYLAND'S NEW  
STEAMBOAT,  
"GENERAL JACKSON"



# ALINCO CORPORATION

P.O. Box 70007 • Reno, Nev. 89570  
 44 Glen Carran Circle • Sparks, Nev. 89431  
 Phone (702) 359-1414 • Telex 4993999 EGELECTR  
 International Division of ALINCO Group

## RF POWER AMPS

(All-mode VHF 2m-70cm) With Rx Preamps



ELH 230G\*

- ★ HEAVY-DUTY HEAT SINK
- ★ LOW PASS FILTER INSTALLED
- ★ PROTECTION CIRCUIT BUILT IN
- ★ RELIABLE & RUGGED
- ★ CLEAN RF OUTPUT

Model	ELH 230D*
Frequency Range	144-148 MHz
Modes	FM-SSB-CW
Input Power	1W-3W
Output Power	30W
Power Source	DC 13.8V/45A
RX-Preamp (Approx.)	10 dB
Input & Output Impedance	50-Ohm
Dimensions (in.) (W x H x D)	3.64" x 1.64" x 6.52"
Net Wt. (Approx.)	1.11 Lbs.

\*Note: Photo shows Model ELH 230G (without RX Preamp). Specs are otherwise the same. Other models available for 2M & 70CM.

## DC POWER SUPPLIES

(From 4 to 55 Amperes)

Model	EP-3030*
Input Voltage	Mains: 115V AC (Nom.)
Output Voltage	10-15V DC (Adjustable)
Output Current	25A DC Cont.; 30A DC Max
Ripple Voltage	Under 30mV, P-P (Rated)
Power Consumption	770VA (Rated)
Circuit Protection System	Shut-down type, Auto current limiting
Dimensions (in.) (L x W x H)	13.34" x 9.6" x 6.32"
Weight	18.92 Lbs.



EP 3030\*

- ★ IC SERIES REG.
- ★ AUTOMATIC CURRENT LIMITING
- ★ HIGH STABILITY
- ★ VOLTAGE ADJUSTER ON SOME MODELS
- ★ FULL METERING

\*Note: Many different power supply Models available from 4A to 55A output current.

**"WATCH ALINCO G R O W"**  
 MORE EXCITING EQUIPMENT AND ACCESSORIES ON THE WAY

✓ 136

**quality  
 service  
 price**



**International Crystal Manufacturing Co., Inc.**

10 North Lee, P.O. Box 26330, Oklahoma City, OK 73126-0330 (405) 236-3741

This publication is available in microform from University Microfilms International.



Please send information about these titles:

\_\_\_\_\_

Name \_\_\_\_\_

Company/Institution \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

Phone ( ) \_\_\_\_\_

Call toll-free 800-521-3044. In Michigan, Alaska and Hawaii call collect 313-761-4700. Or mail inquiry to: University Microfilms International, 300 North Zeeb Road, Ann Arbor, MI 48106.

# a pulsed, constant current, NiCad battery charger

Longer life,  
shorter charge time  
— plus automatic  
shutoff

**“Zapping” NiCad batteries** with a burst of high current is an old trick often used to revive seemingly dead cells. Word has it that some RC model airplane enthusiasts extended this idea to the actual charging of batteries, with favorable results; their batteries lasted twice as long and charged more quickly than those who used conventional charging methods. The idea was to charge with a train of pulses instead of a steady current. Apparently, less energy was lost to heat during the charging process, resulting in shorter charging times and increased battery life.

This charger was designed with these goals in mind. Over the two years it's been in use, charging times have been shortened by one-third and new life has been given to a battery pack about to be thrown away.

## principle of operation

The key to pulse charging is to keep the average value of the charging current the same as it would be in conventional schemes, but use a low duty cycle waveform. The plot shown in **fig. 1** is the current waveform used in this charger. For 10 percent of each cycle, current equal to  $I_{MAX}$  charges the battery. For the remaining 90 percent of the cycle, no current flows. This produces a rectangular waveform with a 10 percent duty cycle.

The DC, or average value of this waveform is 10 percent of the pulse amplitude, or

$$I_{DC} = 0.1I_{MAX} \quad (1)$$

As long as normal charging precautions are observed and the DC charge rate is within the capability of the battery, pulse charging will in no way harm the

battery. A pulse width of about 100 microseconds ( $\mu s$ ) is appropriate for this application, which, because of the 10 percent duty cycle, yields a pulse rate of 1 kHz.

## circuit description

The block diagram in **fig. 2** outlines the basic design of the charger. The schematic is shown in **fig. 3**. The charger — designed to handle from one to ten NiCad cells, with an adjustable charge rate of 50 to 450 mA — consists of the following sections:

**Constant-current source.** The charging current is supplied by a constant-current source that can be pulsed at peak currents of up to 5.0 amperes. A constant-current source can be made from a three-terminal voltage regulator and a resistor, as shown in **fig. 4**. In this circuit the current,  $I_{DC}$ , is simply the output voltage of the regulator,  $V_o$ , divided by  $R3$ , or

$$I_C = \frac{V_o}{R3} \quad (2)$$

Unfortunately, this method does not easily lend itself to high frequency switching.

A better approach is shown in **fig. 5A**, in which the regulator is replaced with a zener diode and pass transistor. Here, the current is equal to the zener voltage,  $V_Z$  (less the base-emitter voltage drop of Q1) divided by  $R3$ , or



$$I_C = \frac{(V_Z - 0.6)}{R3} \quad (3)$$

The current can be instantly switched off by grounding the base of Q1. This circuit worked well except at high currents.

To improve its operation at high currents, I added a second transistor as shown in **fig. 5B**.<sup>1</sup> This circuit worked very well. It could supply a constant current into either a short circuit or 10 cells in series and still hold the current to within 1 percent of its setting.

As shown in **fig. 3**, the current is adjusted by  $R3$ .  $R4$  is inserted in series with  $R3$  to limit the current if  $R3$  is set to zero.

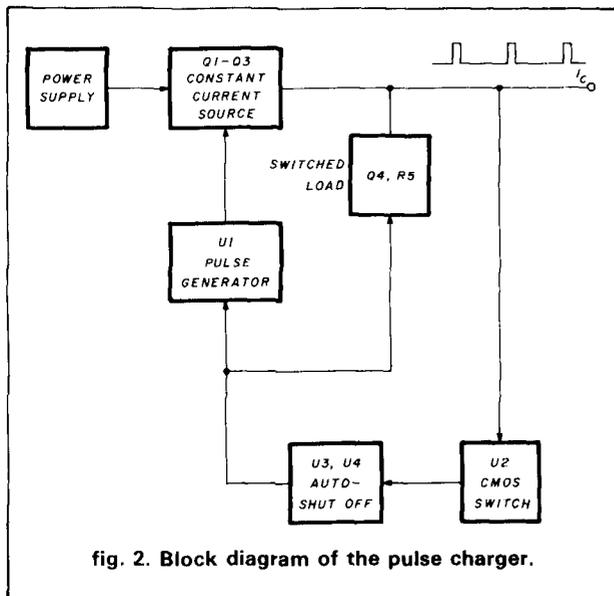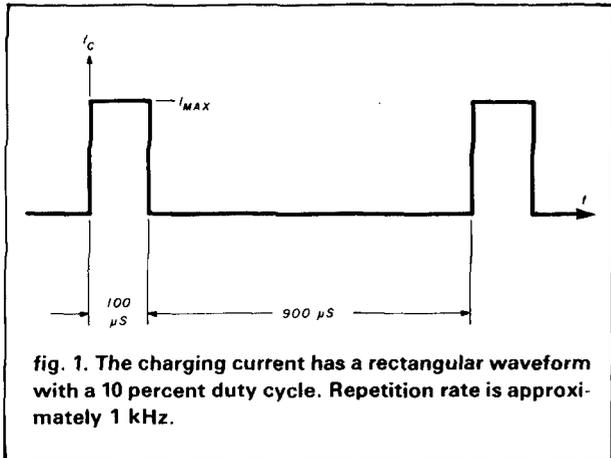By Alan Lefkow, K2MWU, 17 Jacobs Road,  
Thiells, New York 10984



**Power supply.** For the constant current circuit to work properly while charging up to 10 cells in series, the power supply must provide at least 30 VDC. The unregulated power supply shown in **fig. 3** satisfies that requirement if T1's taps are wired for 22.3 VAC, as shown. A separate zener regulated section provides 15 VDC for the control circuitry of the charger.

**Pulse generator.** The pulse waveform is generated by U1. Actually, U1 produces a 90 percent duty cycle waveform instead of 10 percent in order to accommodate the inverting action of Q3. Q3 turns the current source off when the output of U1 is high, and on when it is low. That converts U1's 90 percent duty cycle to a 10 percent duty cycle charging current.

**Automatic shutoff.** Different schemes abound for controlling the charging time, each with their advantages and disadvantages. In the scheme chosen for this charger, charging stops when the battery

reaches a set voltage. However, the battery voltage is not monitored in an ordinary manner.

Because of a battery's internal resistance, the voltage at its terminals during charging is less than its open circuit voltage, and will vary with the charge rate. As soon as a load is put across the battery, the voltage will drop further. In this charger, battery voltage is monitored only during that part of each cycle in which the charge current is off. Furthermore, a small load, R5, is kept across the battery to give a truer indication of the state of charge when the battery is monitored. The load is automatically switched out of the circuit during automatic shutdown.

Automatic shutoff is accomplished by monitoring the battery voltage with comparator U3. R15 and R16 divide down that voltage and U3 compares it with the voltage provided by reference diode CR8. When the voltage at the comparator rises above the reference voltage, Q5 turns on, shorts out C5, and stops U1 from oscillating. That forces the output of U1 high, which holds the constant-current source off.

R13 and R17 add hysteresis to the action of the comparator. With the values given, the battery voltage must drop about 30 percent before charging will switch on again after automatic shutoff. The amount of hysteresis can be changed by raising or lowering the value of R17.

In order for U3 to monitor the battery voltage only during the off portion of a charge cycle, CMOS switch U2 passes the voltage on to the comparator in sync with U1. In this way, when U1 stops oscillating, the comparator will still see the battery's voltage because U2 is kept closed by U1 in the automatic shutoff state.

**Current metering.** The torque on the pointer in a standard D'Arsonval meter movement is directly proportional to the true DC value of any current passing through it. As a result, the DC milliamp meter M1 in **fig. 3** correctly indicates the true charge rate delivered to the battery. Load resistor R5 is wired in the circuit so that the load current delivered to R5 by the battery during the off period of a cycle is taken into consideration by M1. The value of R5 was chosen to add a load of about 25 mA when charging an 11-volt battery pack.

## construction

Perfboard was used for mounting most of the components. The board was connected to the rest of the circuit by an edge connector to make it removable during the design phase of the project, but any convenient construction method can be used because parts layout is not critical. A Radio Shack cabinet (former catalog No. 270-269, **fig. 6**) housed the circuit. M1 is specified as 0-500 mA, in the parts list; a 0-100  $\mu$ A movement was used in the original model by adding a current shunt.

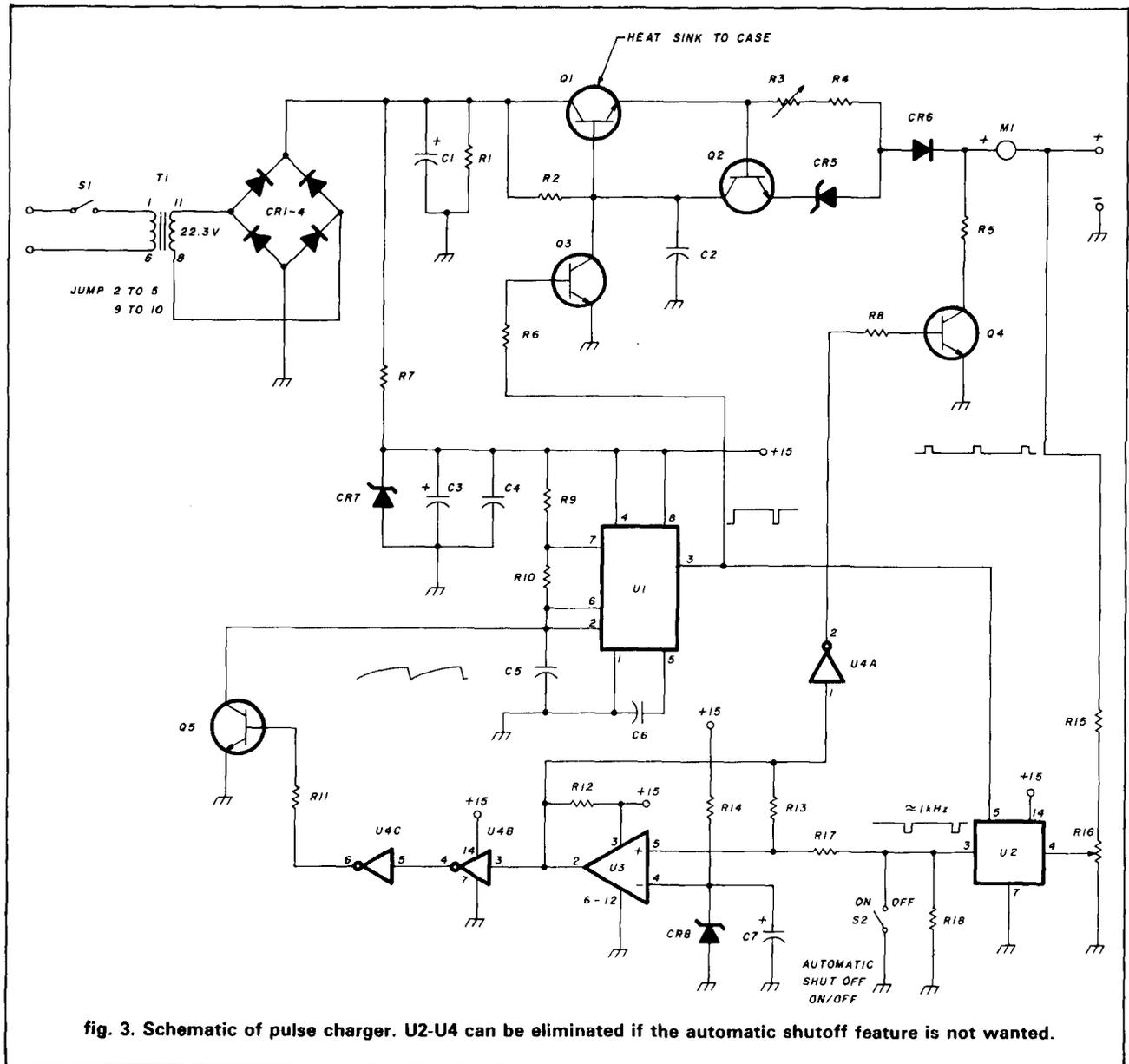


fig. 3. Schematic of pulse charger. U2-U4 can be eliminated if the automatic shutoff feature is not wanted.

Although pass transistor Q1 is heat-sinked to the case, it must be electrically insulated from it. During conduction, the current through Q1 can be as high as 5 amperes and the voltage across it about 15 volts. Instantaneous power is  $5 \times 15 = 75$  watts, but the power which must be dissipated by Q1 is only ten percent of that because of the duty cycle. Using the case as a heat sink works well for this low power level.

The heat dissipated in R3 and R4 is proportional to the square of the RMS voltage across them, divided by their resistance. Because of the ten percent duty cycle, that RMS voltage is approximately one-third of the peak voltage across the resistors, as is the RMS current value through the resistors. With this in mind, the wattage ratings should be 10 watts for R4 and 5 watts for R3. An old loudspeaker level control was

used for R3, but any 70-100 ohm, 5-watt potentiometer will do. Since the charge current is inversely proportional to R3, the higher current settings will bunch up at one end of the shaft rotation. A potentiometer with a non-linear taper can reduce that effect.

Switch S2 disables the automatic shutoff feature. If desired, the entire shutoff feature can be left out by removing U2 through U4 and their related components, as well as R5 and Q4.

### operating the charger

NiCad batteries can be charged at a significantly higher rate than that provided by the average stock charger as long as the battery is not overcharged.<sup>2</sup> Once fully charged, the battery must dissipate any additional charging as heat. At the popular C/10

Parts list figure 3.

item	description
C1	1500 $\mu$ F, 50 volt electrolytic
C2	0.001 $\mu$ F
C3	100 $\mu$ F, 25 volt electrolytic
C4,C6	0.01 $\mu$ F
C5	0.01 $\mu$ F mylar, 10 percent
C7	10 $\mu$ F tantalum
CR1,CR2	6 ampere, 100 volt rectifier bridge
CR3,CR4	1N753 6.2 volt zener diode
CR5	2 ampere, 50 volt rectifier diode
CR6	1N4744, 15 volt zener diode
CR7	1.2 reference diode
CR8	0-500 mA DC ammeter
M1	TIP120 (Radio Shack No. 276-2068)
Q1	TIS97
Q2	2N3904
Q3	2N2222
Q4	2N3704
Q5	2.2 kilohms, 1 watt
R1	2.2 kilohms, 2 watts
R2	70-100 ohms, 5 watt potentiometer (see text)
R3	1.5 ohms, 10 watts
R4	470 ohms, 2 watts
R5	1.5 kilohms
R6	680 ohm, 2 watts
R7	10 kilohms
R8,R11	120 kilohms
R9	22 kilohms
R10,R18	3.3 kilohms
R12	2.2 megohms
R13	15 kilohms
R14	5.6 kilohms
R15	2 kilohms, 10-turn trim potentiometer
R16	51 kilohms
R17	SPST toggle switch
S1,S2	Stancor RT-201 power transformer or equivalent
T1	NE555 timer
U1	CD4016 CMOS switch
U2	LM339 comparator
U3	National CMOS 74C04

All other capacitors are disc ceramic. Except as noted, all resistors are 1/4 watt.

charge rate, where C is the ampere-hour capacity of the battery, NiCad cells can be overcharged continuously without risk of damage from overheating. This assures safety in case the battery is left on "charge" continuously. On the other hand, if the battery is charged at a higher charge rate, say C/3, and goes into overcharge, cell temperature will rise, with possible damage and loss of battery life. However, if care is taken to avoid overcharging, there is no inherent reason why a NiCad cell cannot be charged at the higher rate. The automatic shutoff will prevent just such overcharging from occurring after it is properly set.

To set the automatic shutoff, first remove any diode in series with the HT's charging jack if the battery will remain inside the HT during charging. (If you don't do this, the automatic shutoff feature won't work.) Connect the discharged battery to the charger, turn the charger on, and turn off the automatic shutoff with S2. Set the charge rate to C/3, and add another 5 mA to compensate for changes in the load of R5 as the battery voltage rises. (For a 500 mA hour battery, that would be about 155 mA.) Monitor the battery voltage with a precision voltmeter, preferably a DVM — accuracy is not as important as precision. Check the

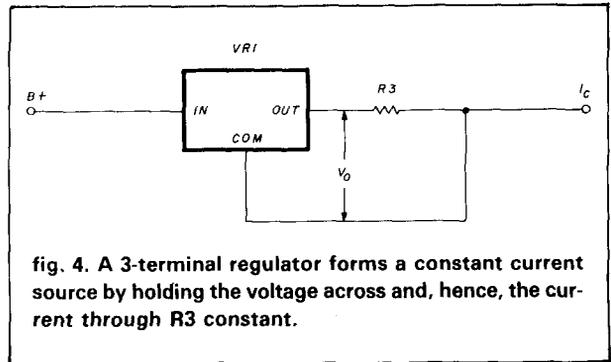


fig. 4. A 3-terminal regulator forms a constant current source by holding the voltage across and, hence, the current through R3 constant.

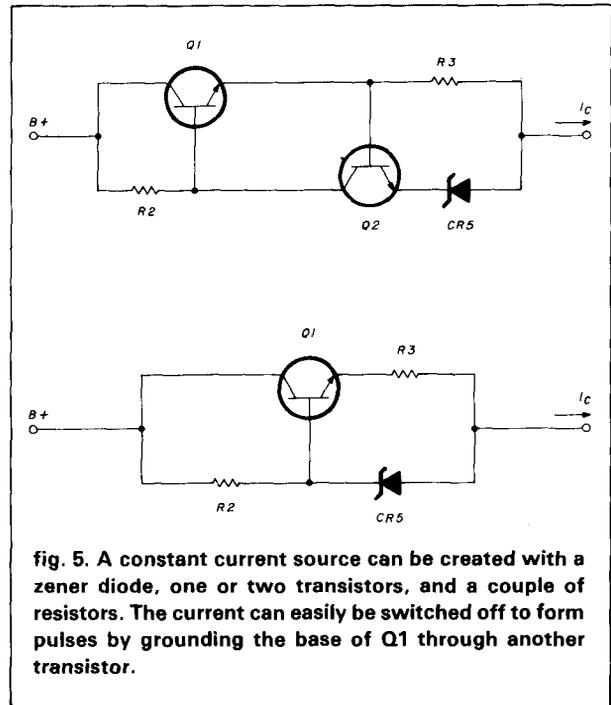


fig. 5. A constant current source can be created with a zener diode, one or two transistors, and a couple of resistors. The current can easily be switched off to form pulses by grounding the base of Q1 through another transistor.

battery frequently as it charges. The battery voltage will rise rapidly initially and gradually thereafter. When the battery nears its fully charged state the voltage will again rise, but more importantly, the battery will start to become warm to the touch. This increase in temperature indicates that the battery is now fully charged. Note the voltage when this occurs; it will probably be the equivalent of 1.45-1.50 volts per cell. Also make a note of how much charging time it took to arrive at this point, starting with a fully discharged battery.

Now turn on the automatic feature, and adjust R16 until the charge current turns off. Reduce the charge rate setting slightly and reset the automatic shutoff by cycling S2 on and off. Raise the charge current back up again and watch the voltmeter to make sure charging shuts off at the voltage just measured. If the shutoff point cannot be set exactly, err on the low side by setting it slightly below the desired voltage.

If the automatic feature is not used, charging can



fig. 6. The charger fits nicely in a standard Radio Shack cabinet. Parts layout is not critical and any convenient construction method can be used.

be controlled by time. An inexpensive mechanical timer can shut off the charger after the proper length of time, as just determined. Remove the "ON" arm of the timer to keep it from again turning on the charger 24 hours later.

#### conclusion

The pulse charger has been a considerable time-saver: it takes only 3-1/2 hours to fully charge a 500-

mA hour battery pack at a 150 mA charge rate; a non-pulsed charger at that same rate took 4-1/2 hours. This represents a time savings of over 30 percent, and increased charging efficiency as well. As a test, the battery was discharged with a load resistor equivalent to a 100 mA load and timed to confirm that it was indeed fully charged by the pulse charger.

The charger was also used to add life to an old, seemingly dead battery pack. The battery was consecutively discharged and charged about four times. From that point on, it lasted another three months.

The pulsed charger should prove to be a worthwhile accessory for anyone who uses NiCad batteries extensively.

#### acknowledgement

Many thanks to Pat Spadafore, KA2MOV, for his invaluable experience and recommendations concerning pulsed charging techniques.

#### references

1. *The Radio Amateur's Handbook*, American Radio Relay League, Newington, Connecticut, 1983, page 4-31.
2. *Nickel-Cadmium Battery Handbook*, 2nd Edition, General Electric Company, 1975.

ham radio

# TOUCH-TONE DECODER SALE!

## SSI-202P CMOS

### WE OVER PURCHASED

Our over supply can be your gain.

We've just got to try and get even so we are going to let our ham friends share in some of these great circuits, for a great price.

#### FEATURES

- Central office quality
- Band-splitting filters included on chip
- Single, low-tolerance, 5-volt supply
- Detects either 12 or 16 standard DTMF digits
- 18-pin DIP package
- Output in either 4-bit hexadecimal code or binary coded 2 of 8. Use 74159 decoder for 1 of 16 output
- Uses inexpensive 3.579545-MHz color-burst crystal for reference (Radio Shack P/N 272-1310 \$1.69)
- Excellent speech immunity

All you need is a color-burst XTAL from Radio Shack & 1 meg resistor to make a C.O. Quality Touch Tone decoder. SSI-202 is a 5V part and unlike the older 201 is TTL compatible and will directly interface to personal computers.

These won't last long and are limited to available supply, so HURRY!!



**\$18** INCLUDING SPECS. & SCHEMATICS  
In Wash. add 7.9% sales tax

**R.M. FULLER CO.**  
902 Industry Dr., Seattle, WA 98188


**1-800-626-6662**

In Wash. Call **(206) 575-8640**



# AMERITRON AL-1200 LINEAR AMPLIFIER

WITH THE NEW EIMAC 3CX1200 CERAMIC TUBE

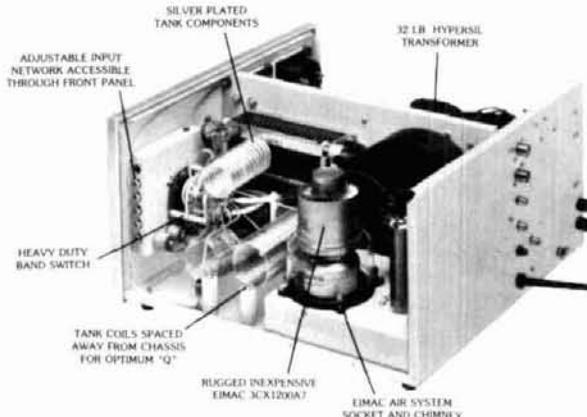

## 1500 WATTS OUTPUT, ALL MODES 160 THROUGH 15 METERS

- Pi-L network with heavy duty components.
- High efficiency bias setting for RTTY/CW.
- ALC compatible with all popular transceivers.
- Peak-reading output meter.

- 32 lb. Peter Dahl hypersil transformer.
- Bridge rectifier supply with computer grade capacitors.
- Inexpensive, instant warm-up tube.
- Full shielding for minimum TVI.

The **Ameritron AL-1200** is designed to give years of trouble-free service at the full legal amateur output power limit. The rugged ce-

ramic/metal Eimac triode is capable of operating continuously at 3000 watts input.

Size 17"W x 10"H x 18-1/2"D Wgt: 77 lbs.

Available at your dealer — Send for a catalog of the complete AMERITRON line.

**AMERITRON, Division of Prime Instruments, Inc.**

9805 Walford Avenue • Cleveland, Ohio 44102 • (216) 651-1740

**Quality Microwave TV Antennas**

Multi-Channel 1.9 to 2.7 GHz  
40dB Gain True Parabolic 20 Inch Dish  
Complete System \$84.95 (Shipping incl.)  
Dealerships, Qty Pricing, Replacement Parts

**Phillips-Tech Electronics**  
P.O. Box 34772 • Phoenix, AZ 85067  
(802) 947-7700 (\$3.00 Credit all phone orders!)  
MasterCard • Visa • CDD's

LIFETIME WARRANTY

✓ 140

AMATEUR RADIO  
SEP TEXAS  
UL E-104  
WD5EQM

\$1295 pr  
H.A.M.-TAGS  
Amateur Radio  
standard for mobiles!

H.A.M.-TAGS Your call on each vehicle. Call at top or bottom of frame, and frame front plate. No-nonsense, full refund, guarantee. \$1.50 shipping (First Class Mail)

B-C 1716 Woodland, Houston, TX 77019 (713) 522-5755

141

NEW

## ARRL TECH-GENERAL LICENSE MANUAL

Written in an easy to read and understand style, this is the guide you need for your Tech/General studying. FCC questions with complete answers ©1985. 1st edition.

□ AR-TG Softbound \$5.00

Please add \$2.50 for shipping and handling

ham radio BOOKSTORE  
Greenville, NH 03048

## DX on 160, 80 and 40 meters with your own **SECRET WEAPON**

Alpha Delta's new DX-A Twin Sloper Antenna combines the tremendous power of the quarter wave sloper with the wide bandwidth of a half wave dipole. Easy to install, simple to tune.

- 160 and 80 m leg approx. 80' long. 40 meter leg 33' long. Installs just like an inverted V. Fed with single 50Ω feedline
- Current lobe up high for maximum radiation. Can be installed between 25 and 40 feet
- Broad band performance. Although bandwidth is determined by your installation, tests have shown 85 kHz on 160 m, 200 kHz on 80 m, and full coverage of 40 m. Tuner usually not required.
- No lossy traps. A single "ISO-RES." isolator/resonator coil is used to tune 80 and 160 meters
- Rated at 1.5 KW output
- Quality hardware and UV protected coil. Stainless steel ensures excellent all weather performance.

**\$4995** ready to install

Available from your local Alpha Delta Dealer or add \$3.00 shipping and handling. (USA only)

**ALPHA DELTA COMMUNICATIONS, INC.**

P.O. Box 571, Centerville, Ohio 45459  
(513) 435-4772 Order line • (513) 376-4180 Tech Info (antennas only)

current solutions to current problems

✓ 143



DX is a snap with my secret weapon!

# Doctor QSO™ Is The Code Buster



## Doctor QSO Relieves All Symptoms Of Morse Code Phobia!



Doctor QSO™ is a plug-in cartridge for the Commodore 64 computer that provides a very realistic simulation of on-the-air two-way Morse Code ragchew contacts (QSOs). AEA, the undisputed leader in Morse training, has introduced Doctor QSO to amateur radio for the purpose of making Morse skill upgrading FUN and EASY. With Doctor QSO you can look forward to practicing your Morse Code skills in a non-confusing manner. Forget about all the drudgery you associated with Morse Code in the past; Doctor QSO ushers in a totally new era in Morse Code learning.

Doctor QSO is based on the same technology that has made the Doctor DX™ contest trainer so famous. The Doctor QSO simulator is so realistic that most skilled operators find it every bit as rewarding as the real thing. You can operate anytime you want; the only extra equipment you need is a Commodore 64 and a TV set.

Doctor QSO also removes the mystery of the CODE BEHIND THE CODE. Many people go so far as to learn the Morse Code characters, only to be frightened of getting on the air the first time because the QSO format is so confusing. With Doctor QSO, you will be a pro before you turn on your first transmitter. The Doctor QSO trainer/simulator is ideal for the aspiring Amateur Radio operator with little or no contact with helpful hams.

With Doctor QSO you will become familiar with all the U.S. call areas and associated call letter prefixes. The standard international QSO format is observed along with all the common amateur radio abbreviations which are explained thoroughly in the operator's manual. All Morse skill levels are addressed by Doctor QSO, from the person who has not yet learned the Code, to the person comfortable with sending and receiving at 40+ WPM.

Who says Morse Code can't be fun? You can even have fun with Doctor QSO before you have learned the Code. To begin with, the operator can view the messages being sent by the computer generated stations in real-time. The operator can also send Morse with the keyboard. In addition, the operator can select simulation of static interference (QRN) and adjacent CW interference (QRM). Normally, the beginner would operate in the novice band where stations will be sending as slow as 3 WPM. Later as the user becomes more skilled, he can move down the band to faster speeds, and he has the choice of using a key or keyer for sending.

If you have tried every other method known to learn the Morse Code and failed, then Doctor QSO has just the prescription for you. Now you can upgrade your Amateur Radio license in record time. Doctor QSO is more than the written word can describe. To fully appreciate all the merits of this trainer, see your dealer for a demonstration or contact AEA for more information.

Prices and specifications subject to change  
without notice or obligation.

 **VHF**  
**COMMUNICATIONS**

915 North Main Street  
Jamestown, New York 14701 (716)664-6345



**Brings you the  
Breakthrough!**

# THE STANDARD OF EXCELLENCE

*The world of CW, RTTY, and new DUAL AMTOR\* is as close as your fingertips with the new brilliantly innovative state-of-the-art microcomputer controlled EXL-5000E.*

**Automatic Sender/Receiver:** Due to the most up to date computer technology, just a console and keyboard can accomplish complete automatic send/receive of Morse Code (CW), Baudot Code (RTTY), ASCII Code (RTTY) and new ARQ/FEC (AMTOR).

**Code:** Morse (CW includes Kana), Baudot (RTTY), ASCII (RTTY), JIS (RTTY), ARQ/FEC (AMTOR).

**Characters:** Alphabet, Figures, Symbols, Special Characters, Kana.  
**Built-in-Monitor:** 5" high resolution, delayed persistence green monitor — provides sharp clear image with no jiggle or jitter even under fluorescent lighting. Also has a provision for composite video signal output.

**Time Clock:** Displays Month, Date, Hour and Minute on the screen.

**Time/Transmission/Receiving Feature:** The built-in timer enables completely automatic TX/RX without operator's attendance.

**Selcal (Selective Calling) System:** With this feature, the unit only receives messages following a preset code. Built-in Demodulator for High Performance: Newly designed high speed RTTY demodulator has receiving capability of as fast as 300 Baud. Three-step shifts select either 170Hz, 425Hz or 850Hz shift with manual fine tune control of space channel for odd shifts. HIGH (Mark Frequency 2125Hz)/LOW (Mark Frequency 1275Hz) tone pair select. Mark only or Space only copy capability for selective fading. ARQ/FEC features incorporated.

**Crystal Controlled AFSK Modulator:** A transceiver without FSK function can transmit in RTTY mode by utilizing the high stability crystal-controlled modulator controlled by the computer.

**Photocoupler CW, FSK Keyer built-in:** Very high voltage, high current photocoupler keyer is provided for CW, FSK keying.

**Convenient ASCII Key Arrangement:** The keyboard layout is ASCII arrangement with function keys. Automatic insertion of LTR/FIG code makes operation a breeze.

**Battery Back-up Memory:** Data in the battery back-up memory, covering 72 characters x 7 channels and 24 characters x 8 channels, is retained even when the external power source is removed. Messages can be recalled from a keyboard instruction and some particular channels can be read out continuously. You can write messages into any channel while receiving.

**Large Capacity Display Memory:** Covers up to 1,280 characters. Screen Format contains 40 characters x 16 lines x 2 pages.

**Screen Display Type-Ahead Buffer Memory:** A 160-character buffer memory is displayed on the lower part of the screen. The characters move to the left erasing one by one as soon as they are transmitted. Messages can be written during the receiving state for transmission with battery back-up memory or SEND function.

**Function Display System:** Each function (mode, channel number, speed, etc.) is displayed on the screen.

**Printer Interface:** Centronics Para Compatible interface enables easy connection of a low-cost dot printer for hard copy.

**Wide Range of Transmitting and Receiving:** Morse Code transmitting speed can be set from the keyboard at any rate between 5-100 WPM (every word per minute). AUTOTRACK on receive. For communication in Baudot and ASCII Codes, rate is variable by a keyboard instruction between 12-300 Baud when using RTTY Modem and between 12-600 Baud when using TTL level. The variable speed feature makes the unit ideal for amateur, business and commercial use.

**Pre-load Function:** The buffer memory can store the messages written from the keyboard instead of sending them immediately. The stored messages can be sent with a keyboard command.

**"RUB-OUT" Function:** You can correct mistakes while writing messages in the buffer memory. Misspellings can also be erased while the information is still in the buffer memory.

**Automatic CR/LF:** While transmitting, CR/LF automatically sent every 64, 72 or 80 characters.

**WORD MODE operation:** Characters can be transmitted by word groupings, not every character, from the buffer memory with keyboard instruction.

**LINE MODE operation:** Characters can be transmitted by line groupings from the buffer memory.

**WORD-WRAP-AROUND operation:** In receive mode, WORD-WRAP-AROUND prevents the last word of the line from splitting in two and makes the screen easily read.

**"ECHO" Function:** With a keyboard instruction, received data can be read and sent out at the same time. This function enables a cassette tape recorder to be used as a back-up memory, and a system can be created just like telex which uses paper tape.

**Cursor Control Function:** Full cursor control (up/down, left/right) is available from the keyboard. Test Message Function: "RY" and "QBF" test messages can be repeated with this function.

**MARK-AND-BREAK (SPACE-AND-BREAK) System:** Either mark or space tone can be used to copy RTTY.

**Variable CW weights:** For CW transmission, weights (ratio of dot to dash) can be changed within the limits of 1:3-1:6.

**Audio Monitor Circuit:** A built-in audio monitor circuit with an automatic transmit/receive switch enables checking of the transmitting and receiving state. In receive mode, it is possible to check the output of the mark filter, the space filter and AGC amplifier prior to the filters.

**CW Practice Function:** The unit reads data from the hand key and displays the characters on the screen. CW keying output circuit works according to the key operation.

**CW Random Generator:** Output of CW random signal can be used as CW reading practice. **Bargraph LED Meter for**

**Tuning:** Tuning of CW and RTTY is very easy with the bargraph LED meter.

In addition, provision has been made for attachment of an oscilloscope to aid tuning.

**Built-in AC/DC:** Power supply is switchable as required; 100-120 VAC; 220-240 VAC/50/60Hz + 13.8VDC.

**Color:** Light grey with dark grey trim — matches most current transceivers.

**Dimensions:** 363(W) x 121(H) x 351(D) mm; Terminal Unit.

**Warranty:** One Year Limited Specifications Subject to Change



*Everything built in — nothing else to buy!*

EXCLUSIVE DISTRIBUTOR: DEALER INQUIRIES INVITED

**AMATEUR-WHOLESALE ELECTRONICS**

8817 S.W. 129th Terrace, Miami, Florida 33176

FOR YOUR NEAREST DEALER OR TO ORDER:

**TOLL FREE . . . 800-327-3102**

Telephone (305) 233-3631

Telex: 80-3356



MANUFACTURER:

**TONO CORPORATION**

98 Motosoja Machi, Maebashi-Shi, 371, Japan

\*Dual Amtor: Commercial quality, the EXL-5000E incorporates two completely separate modems to fully support the amateur Amtor codes and all of the CCIR recommendations 476-2 for commercial requirements.

# 3CX1200A7

## 10 to 80-meter amplifier

New EIMAC tube provides 1500 watts out

For several years, I have used the popular EIMAC 3-1000Z as the main amplifier tube in my station. I enjoy the instant-on characteristics of the tube as well as the well-matched drive requirements for a 100-watt output exciter. Recently EIMAC introduced the 3CX1200A7, the newest addition to its line of metal ceramic external anode triodes. The electrical characteristics of the tube are identical to the 3-1000Z except for the increased plate dissipation (1200 watts) allowed by the external anode.

I decided to modify my 3-1000Z RF deck to accommodate the new tube. The only change necessary was in the tube socket and chimney. (The 3CX1200A7 uses the EIMAC SK-410 or Johnson 248 socket commonly used for the 3-500Z tube. A matching glass chimney — EIMAC SK-436 — is also available). The modification took less than eight hours. This article summarizes the results of the project.

### the amplifier circuit

As indicated above, this amplifier is designed around the new 3CX1200A7 (see **fig. 1**), using a tuned input network ganged to the main bandswitch. The input circuit minimizes distortion products and helps provide a 52-ohm match to the exciter. Maximum SWR presented to the exciter is 1.2:1. Approximately 100 watts is required to drive the amplifier to 1500 watts output. An effective ALC circuit is also included to prevent overdrive by higher power exciters.

Output impedance matching is accomplished with a pi-network designed for a  $Q$  of 12. Toroids are used for compactness for the 80-meter pi coil and the tuned input network coils.

Also included is a grid trip circuit to disengage the amplifier should the grid current exceed 300 milliamperes. This circuit protects the tube in case of excessive drive or an improper load presented to the amplifier.

The amplifier includes an effective dynamic bias circuit. Response time of the circuit is fast enough to cut the amplifier off between syllables on SSB and between dots and dashes on CW. A defeat switch is included on the rear panel of the amplifier. When

engaged, the heat generated by the tube is substantially *reduced* during amplifier operation as feeling the temperature of the air exiting the amplifier cabinet will confirm.

A 100 VDC power supply is included to power the dynamic bias circuit, and a 26 VDC supply is included for panel lights and relay operation. An RF wattmeter is included for tuneup and measurement of amplifier efficiency.

### amplifier control circuitry

The amplifier control circuitry is illustrated in **fig. 2**. 120 VAC enters the RF deck from the power supply. Power is applied to the amplifier by depressing the front panel switch S1. S1A applies 120 VAC to the HV power supply, the time delay relay TD1, the filament transformer, the 100 VDC bias supply and the 26 VDC supply. The blower receives power immediately through S1B. When the power is turned off with S1, the blower (B) keeps running for approximately three minutes to cool the 3CX1200A7. This delay is accomplished through the use of the time delay relay TD1. The control circuitry is quite simple because of the "instant on" characteristics of the 3CX1200A7 tube.

### grid trip protection

A grid trip module has been included in the amplifier design to protect against high levels of grid current which could be dangerous to the 3CX1200A7 tube. High levels of grid current could be caused by excessive drive, improper tuning or lack of a 50-ohm load on the output of the amplifier. In this design, if the grid current exceeds 280 milliamperes, the circuit trips relay RL3 (see **fig. 3**), which breaks the VOX amplifier line to deactivate the amplifier and lights the front panel "grid trip reset" push button (S4). It is necessary to push the reset button to put the amplifier back into operation. Of course, one should determine why the amplifier exceeded 280 mA before proceeding with amplifier operation.

The circuit operates as follows: grid current is drawn through the 10-ohm resistor (R1) as shown in **fig. 1**. The current flowing through the 10-ohm resistor develops a voltage that turns on transistor Q3 in the grid trip circuit when the current reaches 280 mA (or any other value if desired). 280 mA through a 10-ohm

By Jerry Pittenger, K8RA, 2165 Sumac Loop South, Columbus, Ohio 43229

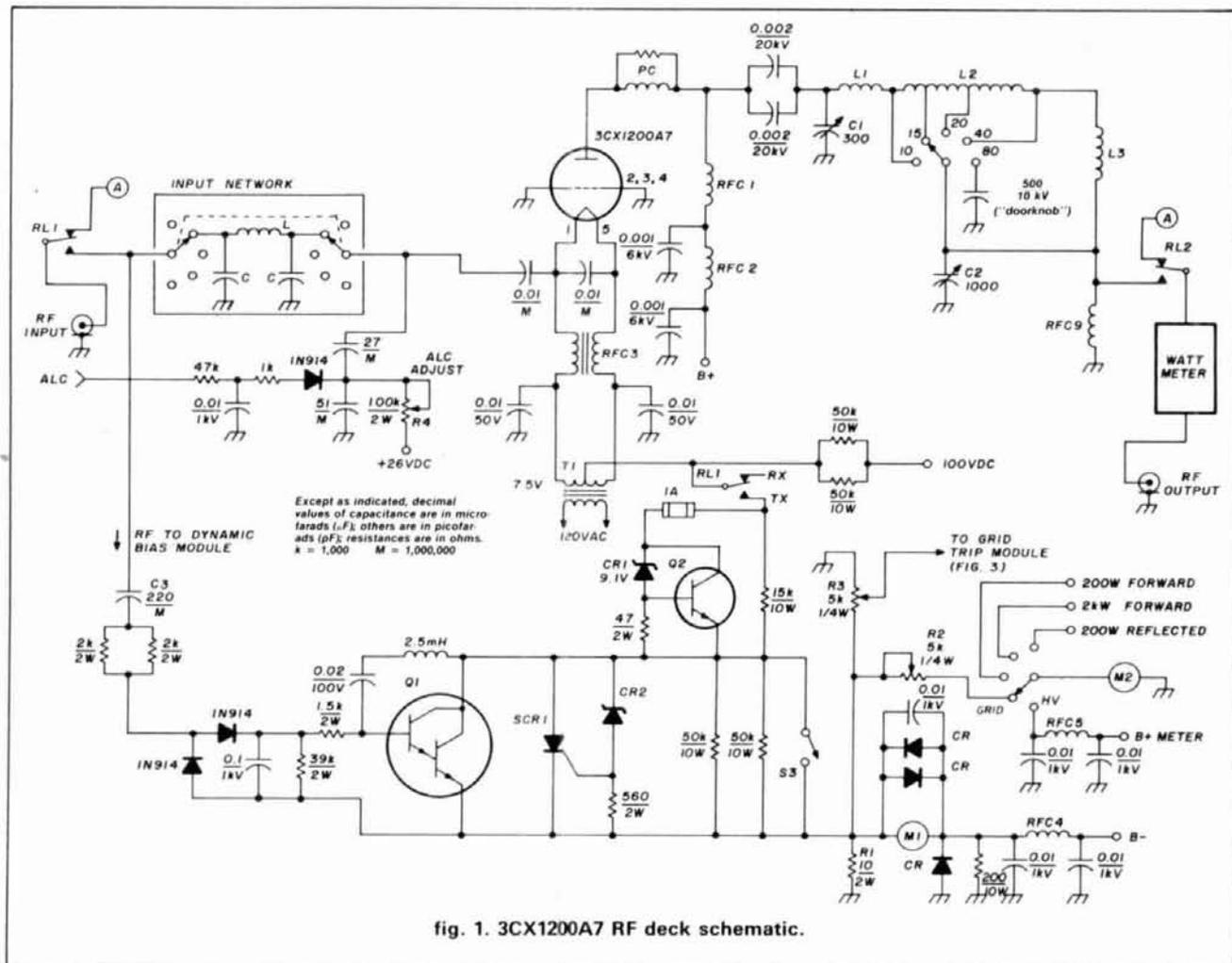


fig. 1. 3CX1200A7 RF deck schematic.



3CX1200A7 amplifier provides full legal output on 10-80 meters.

resistor results in the development of 2.8 volts. Only 0.6 volts is necessary to turn on Q3. Therefore, a 5-kilohm trim pot (R3) has been included as a voltage divider for adjustment.

When Q3 turns on, it serves as a switch providing

a path to ground to actuate relay RL3. A set of the relay contacts physically grounds the relay coil of RL3, taking the current load off Q3. If this feature were not provided, the transistor would start gating the amplifier on and off. It is therefore essential to latch the grid trip relay closed. Another set of contacts on relay RL3 breaks the VOX line, deactivating the amplifier. A third set of contacts applies power to the pilot light on the front panel "grid trip reset" pushbutton (S4) located on the front panel of the amplifier to make the operator aware of what happened. Pushing S4 breaks the path to ground for relay RL3, deactivating the relay and putting the amplifier back into a ready state.

This circuit provides simple and effective protection from costly mistakes during amplifier operation.

### dynamic bias circuit



The amplifier design includes a dynamic bias circuit to bias the 3CX1200A7 tube beyond cut off between speech syllables on SSB or between dots and dashes on CW. This is especially useful when operating in a full break-in mode when the amplifier is placed in ready

### Parts list for 3CX1200A7 amplifier (figs. 1-7).

item	description
<b>B</b>	blower — Dayton 1C180
cabinet	10 x 17 x 14 inch, CTS model MCLS-101714, SPP-1014 side panels CP-1714 chassis panel (CTS IntraFab, 660 Lenfest Road., San Jose, California 65133)
C1	300 pF/10 kV vacuum variable capacitor
C2	1000 pF/3 kV vacuum variable capacitor
C3	1-8 pF miniature air variable capacitor
CR	HEP 170 diode or equivalent
CR1	9.1 volt, 1 watt zener diode (1N4739)
CR2	75 volt, 1 watt zener diode (1N4761)
CR3	100 volt, 1 watt zener diode (1N4764)
CRB1,CRB3	400 volt/4 ampere diode block (RS 276-1173)
CRB2	100 volt/4 ampere diode block (RS 276-1171)
CRB4,CRB5	diode strings, 10 HEP 170 diodes in series, each paralleled by a 470 kilohm resistor and a 0.01/1 kV disk capacitor
L,C	see table 2
L1,L2,L3	see table 1
L4	RF wattmeter pickup coil, 20 turns No. 22 enameled wire on T-50-2 ferrite toroid core
M1	1 ampere plate meter, Triplett 320-G
M2	100 $\mu$ A meter, Triplett 320-G
Q1	MJ1000 NPN Darlington or equivalent
Q2	2N3055 NPN power transistor
Q3	2N3053 NPN transistor
PC	2 turns, 1/2 silver strap, 1-inch diameter 3 x 150-ohm 2-watt resistors
RFC1	90 turns No. 20 enameled wire on 3/4-inch form
RFC2	11 turns No. 14 enameled wire on 1/2-inch diameter air wound
RFC3	30 ampere bifilar filament choke, each coil is 16 turns on 1/2-inch ferrite rod
RFC4,RFC8	10 turns No. 14 enameled wire on 1/4-inch diameter ferrite rods
RFC9	1 mH/800 mA RF choke
RL1,RL3	4PDT Potter & Brumfield KHU17D11, 24VDC coil
RL2	SPDT vacuum relay, 26VDC coil
RL4	2PDT mercury plunger relay, Dayton 6X598-3
RL5	DPDT power relay, Potter & Brumfield PR-11-DY
S1,S2	2PDT push-button switches: ALCO 16TL5-22 ALCO 6T-4 yellow lens (S1) ALCO 6T-2 green lens (S2)
S4	momentary push-button switch, 1 pole/N.C. ALCO 16SL-11 switch ALCO 6S-2 red lens
SCR	2N1596 100 volt/1.6 ampere SCR
T1	filament transformer, 7.5 volt/21 ampere
T2	80 VAC (approx.) transformer, low current
T3	24 VAC/1 ampere transformer (Stancor P8661)
T4	1400 VAC-2 kVA power transformer
TD1	time delay relay, Amperite 115-N-180 (3 minute)
Z1,Z2	MOV transient protectors V130LA10A (RS 276-570)

#### Notes:

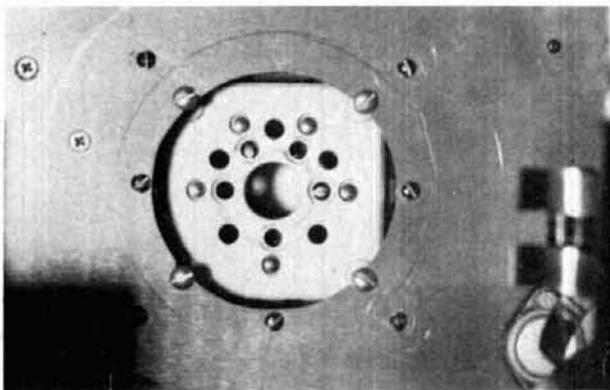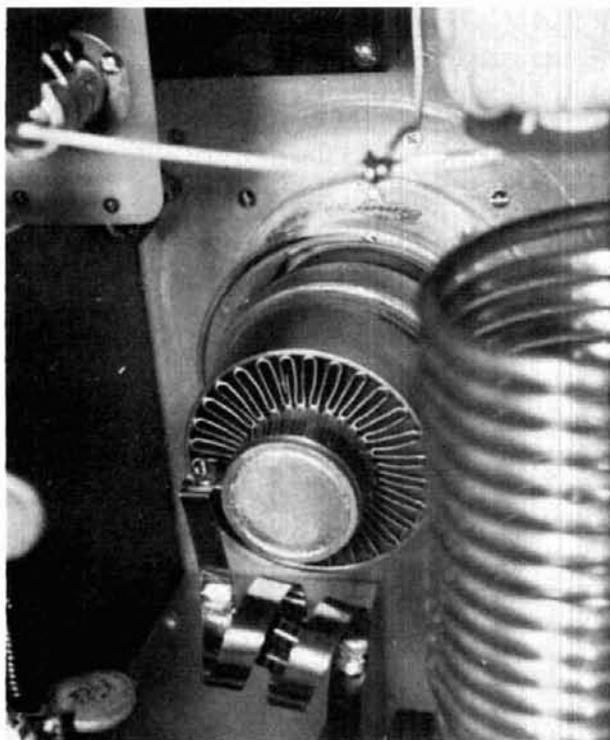1. Only the major items have been indicated in this parts list. See individual schematics to determine complete component complement.
2. The letter M indicated under the component value of capacitors indicates silver mica.



The 3CX1200A7 tube uses the same socket and chimney as the popular 3-500Z.

state at all times. The circuit can save up to 500 watts of power dissipation in the idle state.

Operation of the dynamic bias circuit is quite simple. RF is sampled through the 220 pF mica capacitor, C3. A voltage doubler is formed by the 1N914 diodes, providing a DC voltage to turn on the Darlington transistor Q1. Therefore, Q1 acts as a switch to return the bias voltage to the level determined by the zener diode CR1. The crowbar circuit formed by the SCR and zener diode CR2 is a protection circuit to prevent the amplifier from going into class C operation or the cathode voltage to rise toward the value of the plate voltage when enough drive power is applied should the Darlington transistor Q1 fail to conduct. A full

theoretical treatment of this design is provided in reference 1.

Switch S3 provides a defeat of the dynamic bias circuit to set the operating bias level or defeat the circuit should the circuit fail in an open state. The circuit can be omitted if desired by replacing the bias module with a wire connecting the emitter of Q2 to the B-minus line (see fig. 8).

### meter circuits

Metering is provided for plate current, grid current, high voltage and RF power output. Plate current is monitored at all times. This meter is in series with the B-minus lead. All other metered parameters are selected on a multimeter. The multimeter has a 100 mA



# in stock now

## LUXOR 9550

A high performance 4 GHz, 70 MHz input receiver featuring programmable video and audio, hand held remote, four different audio systems, switchable audio bandwidths, built-in RF modulator, two speed scanning modes and built-in stereo processor.




## Mark 2™

Offers independent channel selection for multiple TV sets from a single antenna, with a selection of up to 24 individual channels from a single satellite. The Mark 2 also features individually programmed audio, automatic fine tuning control, fine tuning storage, special function switches and built-in stereo processor.
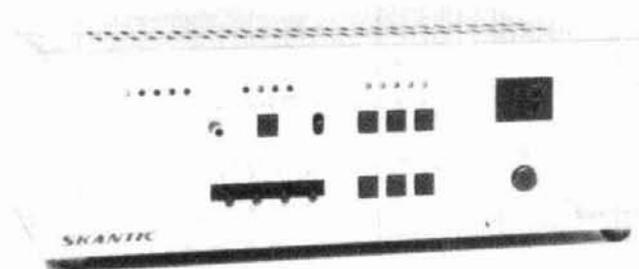
## SKANTIC

Offers versatility and quality performance including fine tuning and video, automatic audio and video digital memory, automatic polarization and four programmable audio modes.



## The Northeast's Leading Distributor



Sales and Marketing Assistance  
Factory Authorized Service  
Professional Training Seminars  
Co-op Advertising Support  
Automated UPS Shipping

Satellite Video  
Services, Inc.  
RR #1, Box 85-S  
Catskill, NY 12414  
**518-678-9581**  
800-528-DISH - National  
800-831-DISH - NY Only

Satellite Video  
Services NH, Inc.  
RFD #2, Harriman Hill Rd.  
Raymond, NH 03077  
**603-895-3182**  
800-448-0012 - National

Satellite Video  
Services PA, Inc.  
317 E. Pleasant Valley Blvd.  
Altoona, PA 16602  
**814-942-5003**  
800-242-3860 - PA Only  
800-367-8899 - National

Satellite Video  
Services WNY, Inc.  
East Avenue Extension  
Hornell NY 14843  
**607-324-3435**  
800-641-0018 - NY Only  
800-831-1134 - National

Uniden M/A Com Norsat Gensat Houston Tracker Winegard Conifer Laux Orbitron Kaul-Tronics



# FALCON COMMUNICATIONS



AFTER A LONG INVESTIGATION AND EVALUATION, EVERETT L. GRACEY, FORMER CO-OWNER OF MIRAGE COMMUNICATIONS, HAS JOINED FORCES WITH FALCON.

### A FEW FEATURES:

- All-mode BIPOLAR Mobile/Base Amplifiers
- All-mode MOSFET Mobile/Base Repeater Amplifiers
- "Real" Repeater Amplifiers (not the add-on type)
- Optional Plug-in Receiver Preamplifiers (not everyone needs a receiver preamplifier)

### ALL-MODE BIPOLAR AMPLIFIERS

Model 5123 (2-Meter Amplifier) .....	List \$235
25 Watts in = 150+ watts out	
10 Watts in = 90 watts out	
Model 5121 (2-Meter HT Amplifier) .....	List \$285
2 Watts in = 150 Watts out	
1 Watt in = 90 Watts out	
Model 5122 (2-Meter Multi-purpose Amplifier) .....	List \$275
10 Watts in = 150+ Watts out	
2 Watts in = 50+ Watts out	
Model 5124 (1 1/2-Meter Amplifier) .....	List \$240
30 Watts in = 120 Watts out	
10 Watts in = 80 Watts out	
Model 5125 (70-Cm Amplifier) .....	List \$305
3 Watts in = 100 Watts out	
1 Watt in = 40 Watts out	

### MOSFET POWER AMPLIFIERS

(Same Ranges as Bipolars) ..... Send for Prices)


### MOSFET REPEATER AMPLIFIERS



Model 4111 (2-Meter Repeater Amplifier) .....	List \$295
20 Watts in = 100 Watts out	
10 Watts in = 90 Watts out	
2 Watts in = 30 Watts out	
Model 4114 (2-Meter Repeater Amplifier) .....	List \$365
2 Watts in = 100 Watts out	
1 Watt in = 80 Watts out	
Model 4112 (1 1/2-Meter Repeater Amplifier) .....	List \$295
25 Watts in = 100 Watts out	
10 Watts in = 70 Watts out	
Model 5142 (70-Cm Repeater Amplifier) .....	List \$375
30 Watts in = 100 Watts out	
10 Watts in = 40 Watts out	

For more information see your local dealer or call factory for details.

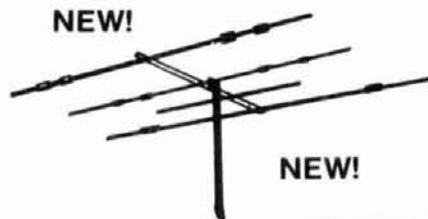Post Office Box 8979  
Newport Beach, CA 92658  
Telephone: (714) 760-3622



NEW!

NEW!

## THE ARRL ANTENNA COMPENDIUM

Because of space limitations in *QST*, we don't have room to run all of the good antenna articles that are submitted. The solution to this problem? **THE ARRL ANTENNA COMPENDIUM!** You'll find 178 pages packed with new material on quads, loops, log periodic arrays, other beam antennas, multiband antennas, verticals, reduced size antennas, plus such interesting topics as: Mr. Smith's "Other" Chart and Broadband Rigs; Available Power, SWR and Loading; Baluns: What They Do and How They Do It; The Horizontal Dipole Over Lossy Ground; and Antenna Polarization. Copyright 1985. Paperbound: \$10.00 in the U.S., \$11.00 elsewhere.

✓ 147

THE AMERICAN RADIO RELAY LEAGUE  
225 MAIN ST.  
NEWINGTON, CT 06111

## DESIGN EVOLUTION IN RF P.A.'s

Now with  
GaAs FET  
Preamp



- Linear (all mode) RF power amp with automatic T/R switching (adjustable delay). Amplifier useable with drive powers as low as 1/2 watt.
- Receive preamp option, featuring GaAs FETS (lowest noise figure, better IMD). Device NF typically .5 dB.
- Thermal shutdown protection incorporated
- Remote control capability built-in
- Rugged components and construction provide for superior product quality and performance
- All models include a complete operating/service manual and carry a factory warranty on all components
- Designed to ICAS ratings, meets FCC part 97 regulations
- Approximate size is 2.8 x 5.8 x 10.5" and weight is 5 lbs.

Specifications/price subject to change

MODEL	FREQUENCY	OUTPUT POWER	INPUT POWER	PREAMP
	(MHz)	(W)	(W)	NF GAIN
0508	50-54	170	1	- -
0508G	50-54	170	1	6 15
0510	50-54	170	10	- -
0510G	50-54	170	10	6 15
1410	144-148	160	10	- -
1410G	144-148	160	10	6 15
1412	144-148	160	30	- -
1412G	144-148	160	30	6 15
2210	220-225	130	10	- -
2210G	220-225	130	10	7 12
2212	220-225	130	30	- -
2212G	220-225	130	30	7 12
4410	420-450	100	10	- -
4410G	420-450	100	10	1.1 12
4412	420-450	100	30	- -
4412G	420-450	100	30	1.1 12

1. Models with G suffix have GaAs FET preamps. Non-G suffix units have no preamp.
2. Covers full amateur band. Specify 10 MHz Bandwidth for 420-450 MHz Amplifier.

★SEND FOR FURTHER INFORMATION★



TE SYSTEMS  
P.O. Box 25845  
Los Angeles, CA 90025  
(213) 478-0591

## ALL BAND TRAP ANTENNAS!

PRE-TUNED-ASSEMBLED ONLY ONE NEAT SMALL ANTENNA FOR ALL BANDS! EXCELLENT FOR APARTMENTS! IMPROVED DESIGN!

FOR ALL MAKES AMATEUR TRANSCEIVERS! GUARANTEED FOR 2000 WATTS SSB INPUT FOR NOVICE AND ALL CLASS AMATEURS!

COMPLETE with 90 ft. RG58U-52 ohm feedline, and PL259 connector, insulators, 30 ft. 300 Ohm test dacron end supports, center connector with built in lightning arrester and static discharge. Low-SWR over all bands - Tuners usually NOT NEEDED! Can be used as inverted V's - slopers - in attics, on building tops or narrow lots. THE ONLY ANTENNA YOU WILL EVER NEED FOR ALL BANDS! NO BALUNS NEEDED!

80-40-20-15-10 - 2 trap - 104 ft. - Model 998D .... \$79.95  
40-20-15-10 - 2 trap - 54 ft. - Model 1001D .... \$78.95  
20-15-10 meter - 2 trap - 26ft. - Model 1007D .... \$77.95

SEND FULL PRICE FOR POSTPAID INSURED. DEL. IN USA. (Canada is \$5.00 extra for postage - clerical - customs etc.) or order using VISA - MASTER CARD - AMER. EXPRESS. Give number and ex. date. Ph 1-308-236-5333 9AM - 6PM week days. We ship in 2-3 days. ALL PRICES MAY INCREASE. SAVE - ORDER NOW! All antennas guaranteed for 1 year. 10 day money back trial if returned in new condition! Made in USA. FREE INFO. AVAILABLE ONLY FROM

WESTERN ELECTRONICS  
Dept. AH-B Kearney, Nebraska, 68847

SAY  
YOU SAW  
IT IN  
ham radio!

# ham radio

## Reader Service

For literature or more information, locate the Reader Service number at the bottom of the ad, circle the appropriate number on this card, affix postage and send to us. We'll hustle your name and address to the companies you're interested in.

101 113 125 137 149 161 173 185 197 209 221 233 245 257 269 281 293 305 317 329 341  
102 114 126 138 150 162 174 186 198 210 222 234 246 258 270 282 294 306 318 330 342  
103 115 127 139 151 163 175 187 199 211 223 235 247 259 271 283 295 307 319 331 343  
104 116 128 140 152 164 176 188 200 212 224 236 248 260 272 284 296 308 320 332 344  
105 117 129 141 153 165 177 189 201 213 225 237 249 261 273 285 297 309 321 333 345  
106 118 130 142 154 166 178 190 202 214 226 238 250 262 274 286 298 310 322 334 346  
107 119 131 143 155 167 179 191 203 215 227 239 251 263 275 287 299 311 323 335 347  
108 120 132 144 156 168 180 192 204 216 228 240 252 264 276 288 300 312 324 336 348  
109 121 133 145 157 169 181 193 205 217 229 241 253 265 277 289 301 313 325 337 349  
110 122 134 146 158 170 182 194 206 218 230 242 254 266 278 290 302 314 326 338 350  
111 123 135 147 159 171 183 195 207 219 231 243 255 267 279 291 303 315 327 339  
112 124 136 148 160 172 184 196 208 220 232 244 256 268 280 292 304 316 328 340

*Limit 15 inquiries per request.*


NAME \_\_\_\_\_ CALL \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

Please use before October 31, 1985

**August 1985**

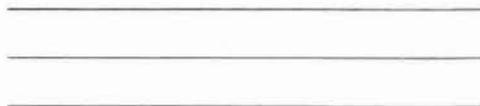

AFFIX POSTAGE  
OR  
POST OFFICE  
WILL NOT  
DELIVER

**ham**  
**radio**  
*magazine*

READER SERVICE CENTER  
P.O. BOX 2558  
WOBURN, MA 01888

ATTN: Reader Service Dept.

ward, and 200 watts reflected. Voltage lines from the wattmeter into the front meter compartment use 0.001 feed-through capacitors to keep RF out. The wattmeter is in the RF line at all times even if the amplifier is not turned on.

Labeling the meters takes a lot of patience but really contributes to the appearance of the amplifier. It is necessary to choose a meter with an analog scale that has the correct number of divisions. However, the meter labeling makes no difference. In a very clean environment, remove the meter scale plate from the meter. Any markings on the meter can be removed with a pencil eraser. (Rub lightly but persistently.) The markings will come off the face plate, leaving a clean surface with an analog scale. The new number and letter markings can now be applied. I use dry transfer lettering to mark the meter scales to the desired values. The dry transfers now available from Radio Shack may be too large for small meters; varied assortments of smaller letters are available from most art supply stores.

### RF relay sequencing

It is important to properly sequence the input RF relay, RL1, and the high power vacuum relay, RL2, to insure that the antenna is always connected to the amplifier before RF drive power is applied. This is accomplished by closing the output relay, RL2, slightly before the input relay RL1.

The timing circuit is shown in **fig. 6**. The 150-ohm resistor and the 100- $\mu$ F capacitor form a time constant that delays closing of the input relay, RL1. The timing can be checked by applying a small voltage across the contacts of both RL1 and RL2 and watching the voltages on the scope as the amplifier is keyed up. The output relay, RL2, should close approximately 25 milliseconds before the input relay, RL1. The timing is adjusted by increasing the value of the 100- $\mu$ F capacitor for longer delay or decreasing the value for shorter delay. The timing constants are totally dependent upon the relays used for RL1 and RL2. Avoid long time delays since a 50-ohm load isn't presented to the exciter when RL1 is open.

### lead filtering

All control and power leads entering or leaving the RF deck are filtered with a pi-section circuit. The coils are made by winding ten turns of No. 16 enamel wire on 1/4-inch diameter ferrite rods. Bypass capacitors are placed to ground at each end of the coil to form a pi-section. Locate each filter as close to the entry or exit point on the panel as possible. The line filters may not be necessary but provide insurance against RF running on leads outside the cabinet.

### tank circuit

The tank circuit uses a pi-network design. The

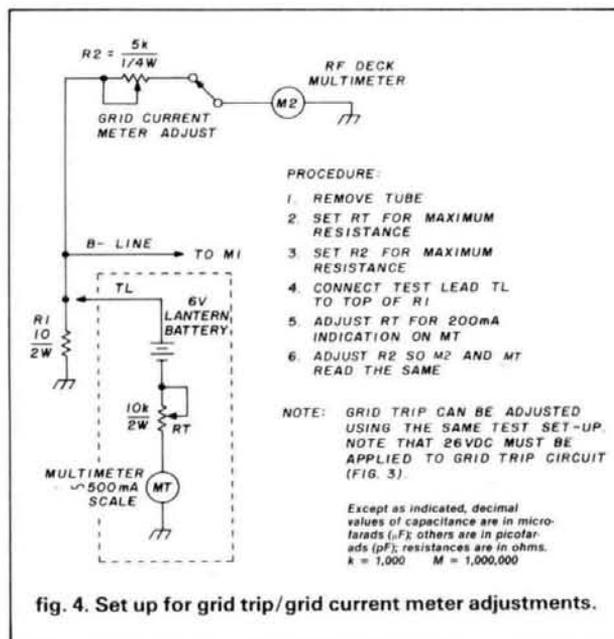


fig. 4. Set up for grid trip/grid current meter adjustments.


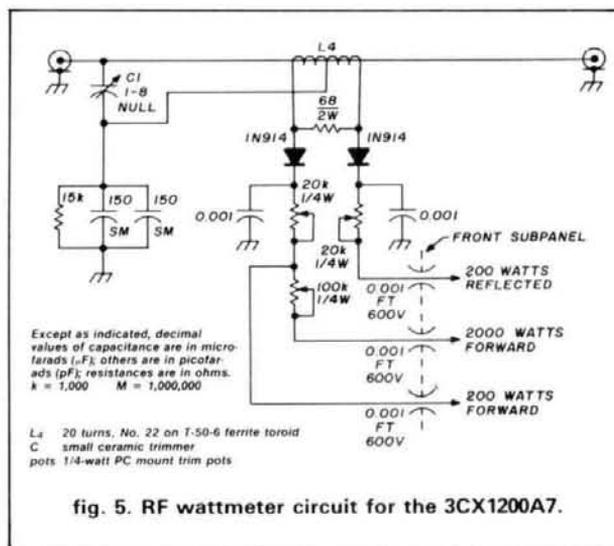


fig. 5. RF wattmeter circuit for the 3CX1200A7.

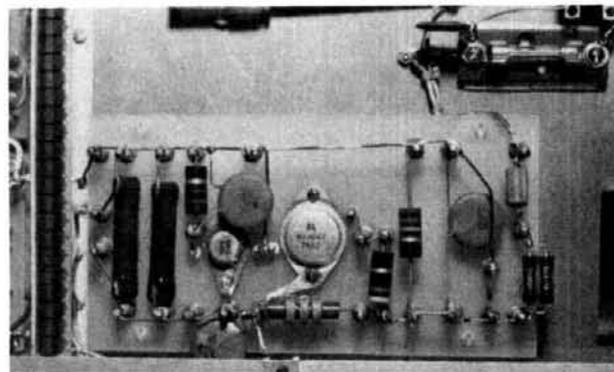

Dynamic bias module.


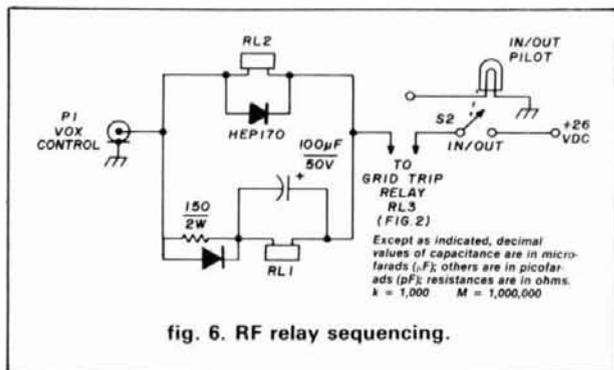


fig. 6. RF relay sequencing.

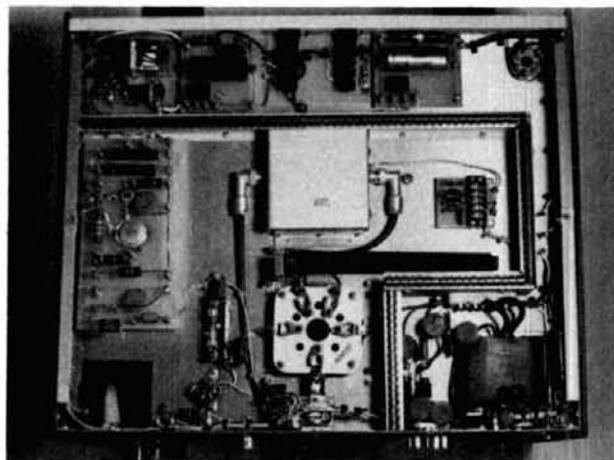

Bottom view of the amplifier illustrates the method used to isolate the RF circuitry from the control and power devices.

design was originally constructed with the 3-1000Z several years ago when the pi-network was the convention. Recent designs recommend a pi-L tank design because of a potential 15 dB improvement in attenuation of the second harmonic. However, the pi-L network needs a double pole band switch to select the inductance on both the pi-coil and the L-coil. Since a single pole switch was already in the amplifier and there was no evidence of TVI, the pi network was not retrofitted with a pi-L design. However, if this amplifier is built from "scratch," it is recommended that a pi-L design be used.

The design parameters for the pi and pi-L circuits are provided in **table 1**. The value for the plate impedance is 2500 ohms.

Vacuum variable capacitors are used for both the tune (C1) and load (C2) controls. Major advantages of vacuum capacitors include compactness, wide capacitance range with a low minimum capacitance necessary for 10 meters and tuning dial resettability. Equivalent air variables can be substituted. However, they are larger and their  $Q$  on 10 and 15 meters is lower.

table 1. Tank circuit design parameters.

pi network:

F(MHz)	C1	C2	L	Q = 12 $R_L = 2500$ ohms
3.5	206	1174	9.95	
7.0	107	608	5.15	
14.0	54	307	2.60	
21.0	36	204	1.74	
28.0	27	153	1.30	

- coil: 4 turns, 1/4-inch tubing, 2-inch diameter
- 13 turns, 1/4-inch tubing, 3-1/4 inch diameter
- taps: 28.0- 3 turns on 2-inch coil
- 21.0- 1 turn on 3-1/4-inch coil
- 14.0- 4 turns on 3-1/4-inch coil
- 7.0-11 turns on 3-1/4-inch coil
- 3.5 MHz toroid tank coil
- 3 × T200-2 cores taped together with fiberglass tape
- 25 turns No. 12 enameled wire

pi-L network:

F(MHz)	C1	C2	L1	L2
3.5	244	1132	10.99	4.45
7.0	113	503	6.03	2.24
14.0	55	245	3.08	1.24
21.0	37	164	2.05	0.83
28.0	26	112	1.48	0.60

Q = 12  
 $R_L = 2500$  ohms

## input network

An input network is included to minimize distortion products and help insure that a 50-ohm load is presented to the exciter. The input network is a pi design with a  $Q = 1$ . **Table 2** summarizes the component values for each pi-section. The capacitors have been selected as standard values. The coils are wound on T50-2 toroid cores. The cores are large enough for the 100 watts drive power without overheating. However, if room permits, use T68-2 or even T75-2 cores to provide an extra safety margin.

The input network is built as a separate module (see input network pictorial) and ganged to the main band-

table 2. Input network design parameters

band	C1(pF)	L(µH)	C2(pF)	No. turns (T50-2)
80	860	2.15	860	23t/No. 20
40	440	1.11	440	17t/No. 20
20	220	0.56	220	12t/No. 18
15	150	0.38	150	9t/No. 14
10	110	0.28	110	8t/No. 14


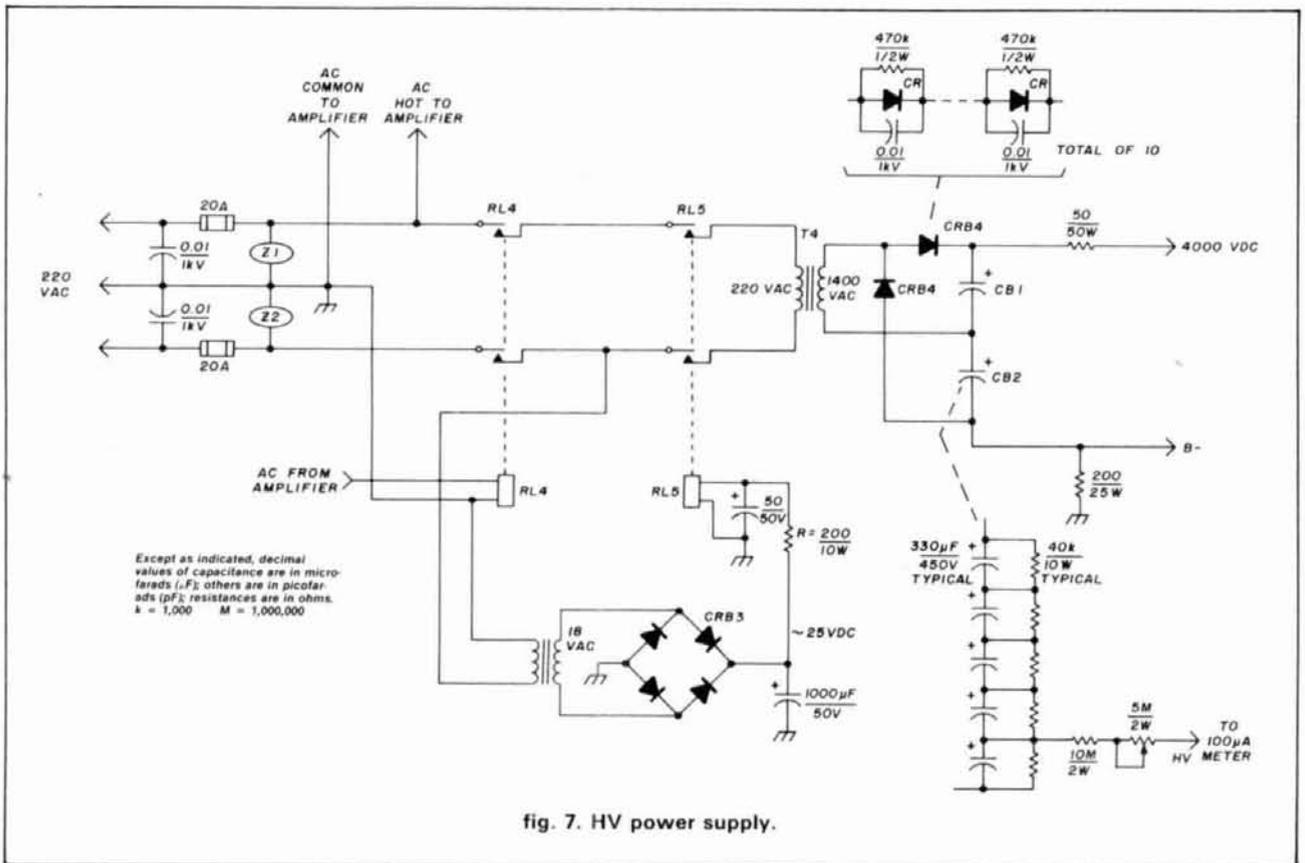


fig. 7. HV power supply.

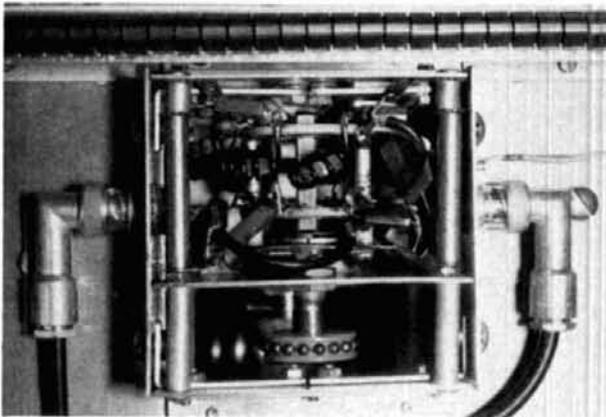

Input network is built as a separate module.

around the base of the tube, through the external anode, and out the top of the amplifier. Refer to the 3CX1200A7 technical data sheet for more information on the cooling at different altitudes.<sup>3</sup>


### HV power supply requirements

A good solid HV power supply is required to get the most out of any amplifier. This amplifier uses a 4000

switch using a small chain sprocket available from reference 2. The unit was fully tested prior to installation into the amplifier.
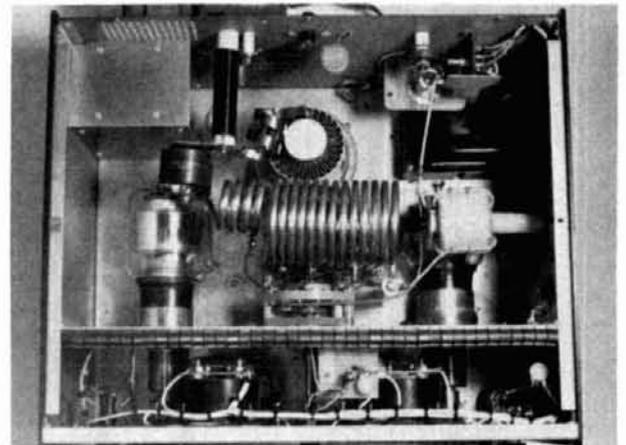
### cooling

Proper cooling is essential for long tube life. The 3CX1200A7 tube socket is mounted approximately 1/2 inch below the chassis. The under chassis is pressurized by a Dayton 1C180 blower mounted on the rear panel. The air flow is ducted by the tube chimney up



Top view of amplifier illustrates small size of 3CX1200A7. Compare it to the vacuum variables in the lower section of the photo.

# the ham notebook

## a \$100 printer for the Commodore 64

The interface and program for converting an ASR-33 teletype machine to an inexpensive printer for the VIC-20 ("VIC-20 Printer," ham notebook, September, 1984, page 88) can be adapted for use with the Commodore 64.

Figure 1A of the original article remains unchanged; in fig. 1B, only the labeling of the user's port is changed. Figure 2 is replaced with a program listing that provides instructions to the Commodore 64.

Like its VIC-20 predecessor, the ASR-33 printer for the Commodore 64 produces typewriter-quality text appropriate for most data listing applications. Because ASR-33's can be found for as little as \$50 to \$75 — and because other parts and materials can be found in junk boxes or very cheaply — the total cost of this project should not exceed \$100.

J.W. Dates, W2QLI

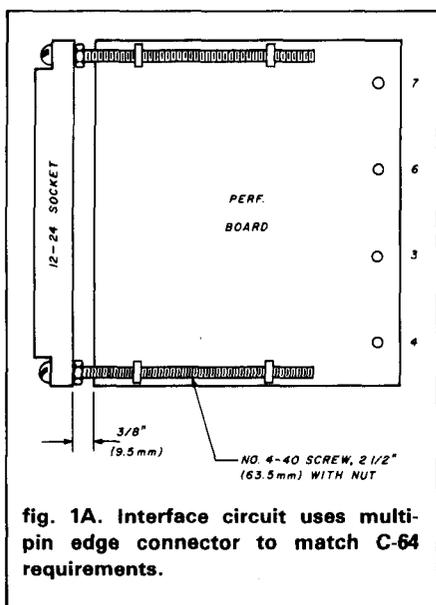


fig. 1A. Interface circuit uses multi-pin edge connector to match C-64 requirements.

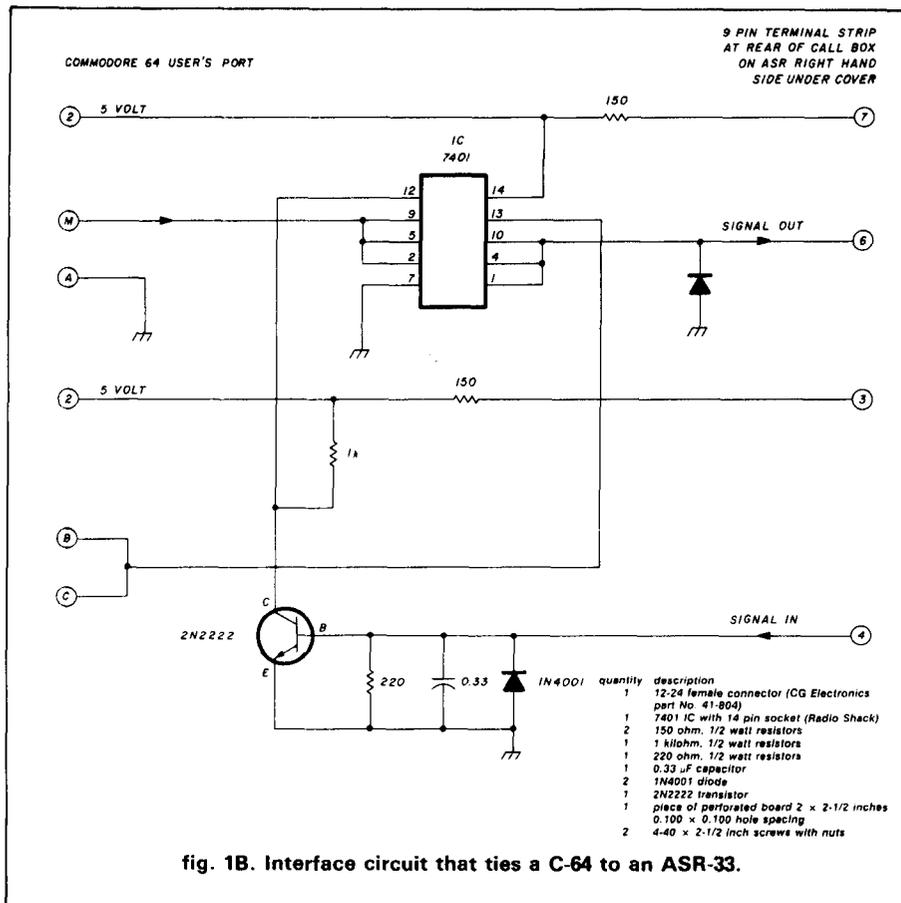


fig. 1B. Interface circuit that ties a C-64 to an ASR-33.



```

10 REM ASR 33 TTY
15 REM FILE#>128 FORCR WITH LF
20 REM 163=2STOP,7 BIT ASCII,110 BAUD
100 OPEN129,2,3,CHR$(163)+CHR$(224)
110 GET#129,A$
200 REM MAIN LOOP
210 GET B$
220 IF B$<>" THEN IF B$=CHR$(13) THEN
PRINT#129,B$;CHR$(0);CHR$(0);GOTO230
225 IF B$<>" THEN PRINT#129,B$;
230 GET#129,C$:IFC$<>" THEN PRINT#129,C$;
240 PRINT B$;C$;
250 SR=ST: IF SR=0 OR SR=8 THEN200
300 REM ERROR REPORTING
310 PRINT "ERROR";
320 IFSR AND 1 THEN PRINT "PARITY"
330 IFSR AND 2 THEN PRINT "FRAME"
340 IF SR AND4 THEN PRINT"REC BUFF FULL
"350 IF SR AND8 THEN PRINT "BREAK"
360 IF(PEEK(673)AND 1)=0 THEN360
370 CLOSE129:END

```

READY.


fig. 2. C-64/ASR-33 program listing.

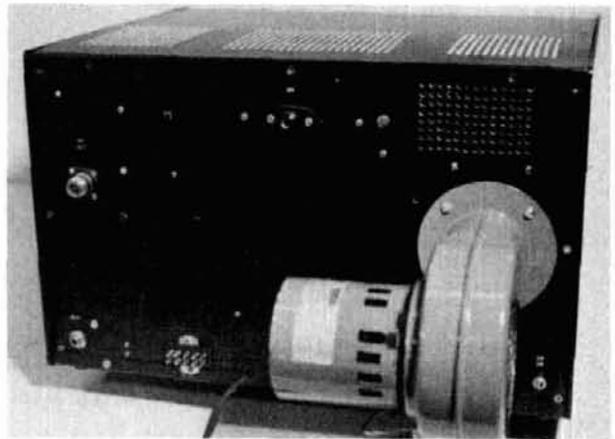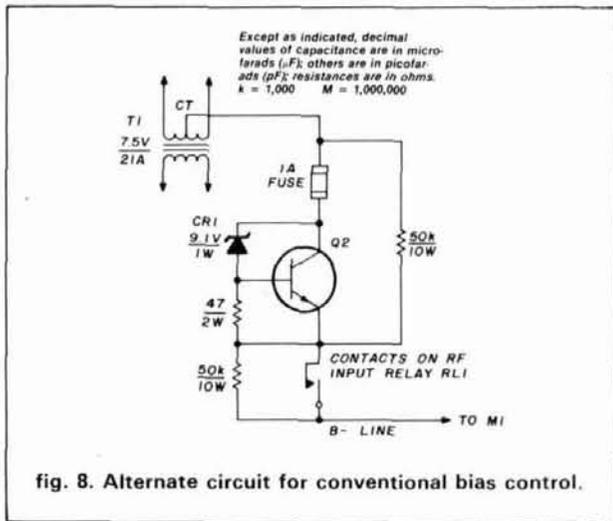

Amplifier rear view. Notice the dynamic bias defeat switch in the lower right corner.

volt power supply. The HV drops to 3600 volts when 800 mA is drawn.

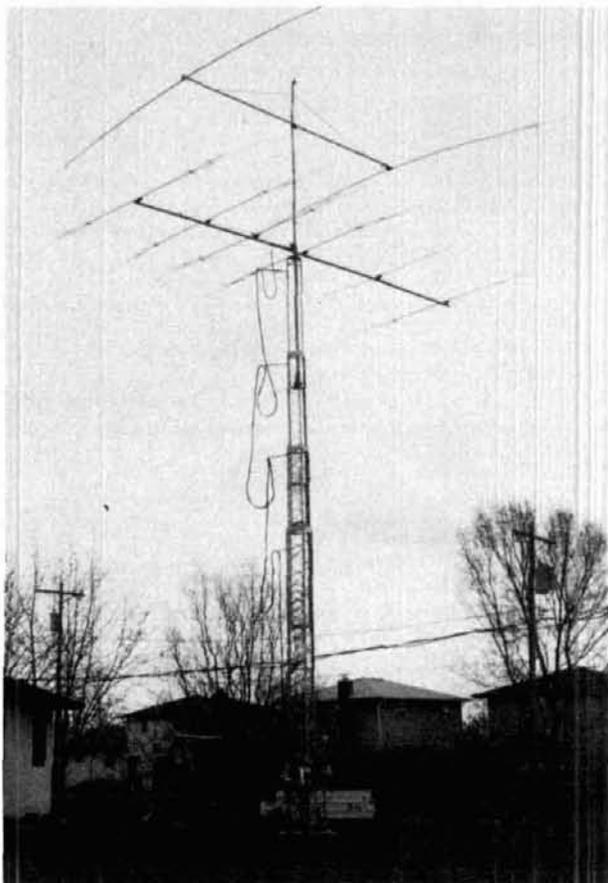The power supply is built as a separate unit that sits behind the operating desk. Its circuit is shown in fig. 7.



Set in 7½ cubic yards of concrete, author's 70-foot Tri-ex 470D tower is completely self-supporting, with fully motorized crank-up, tilt-over capability. Lower antenna is a KLM KT34XA; upper antenna, at 80 feet, is a two-element Cushcraft 40-meter beam. Both were erected by K8RA without assistance.



K8RA's station is largely home-brewed. Shelf holds receiver described in August, 1983, edition of *QST*; construction details will appear in W6SAI's forthcoming revision of *The Radio Handbook*. To the right are two homebrewed keyers and a speaker to match the amplifier. On desk top are a second speaker, a Collins KWM 380 transceiver, a Collins 30L1 linear amplifier, a rotor control and a 2-meter rig. Rack, at right, contains homebrewed equipment exclusively; from top to bottom, the 3CX1200A7 amplifier described in this article, a station monitoring oscilloscope, a station control console, and an antenna tuner with built-in memory. Blank panel marks space for new 8877 linear amplifier currently under construction. (No, Jerry didn't build the clock; it was a \$25 "find" at Dayton. But he did build the 16 × 22-foot solid cedar addition to house his station. Skylights, not pictured here, afford overhead view of antennas.)

## amplifier tuning

Amplifier adjustment is initially done into a 50-ohm dummy load. With filament and operating plate voltage applied, grid and plate current meters should read zero when the amplifier is not keyed up by the exciter. Shorting the VOX in/out line engages the antenna relays which switches the amplifier into the RF line. Static plate current should still be zero if the dynamic bias circuit is used. If the dynamic bias circuit is not

# Join AMSAT...Today

*Amateur Radio Satellite OSCAR 10 provides:*

- A New Worldwide DX Ham Band open 10 hours a day.
- Rag Chew With Rare DX Stations in an uncrowded, gentlemanly fashion.
- Popular Modes In Use: SSB, CW, RTTY, SSTV, Packet
- Full Operating Privileges open to Technician Class licensee or higher.

*Other AMSAT Membership Benefits:*

**ORBIT Magazine Subscription:**  
Dependable technical articles, satellite news, orbital elements, product reviews, DX news, and more.

**Satellite Tracking Software**  
Available for most popular PCs.

QSL Bureau, AMSAT Nets, Area Coordinator Support, Forum Talks

Construction of Future Satellites For Your Enjoyment!

AMSAT Membership is \$24 a year, \$26 outside North America. VISA and MC accepted.

**AMSAT**  
P.O. Box 27  
Washington, DC 20044  
301 589-6062

✓ 151

included or bypassed with the defeat switch, S3, the static plate current should rest at approximately 150 mA. If grid current is observed with the plate or tune capacitors in any position, it is probably a sign of parasitic oscillations and should be corrected.<sup>4</sup>

Drive power can now be slowly increased until the plate current is approximately 250 mA. The Tune and Load controls are adjusted for maximum power output as indicated on the RF power output meter. Excitation is now increased and the plate and load tuning capacitors adjusted until approximately 800 mA plate current with 200 mA grid current is achieved, with maximum output indicated. When the above conditions have been met, the loading should be increased slightly to insure proper linearity. The RF power output should not exceed 1500 watts. Use a scope to monitor signal quality if available. Under SSB speech conditions, peak plate current with no clipping or compression will kick to about 400 mA and grid current to about 100 mA.

## conclusion

The amplifier has been in operation for over six months and has operated flawlessly. As expected, another fine tube by EIMAC.

## references

1. J.A. Bryant, W4UX, "Electronic Bias Switching for RF Power Amplifiers," *QST*, May, 1974, page 36.
2. *Precision Mechanical Components*, Winfred M. Berg, Inc., 499 Ocean Avenue, East Rockaway, New York 11518.
3. *3CX1200A7 Technical Data Sheet*, Varian/EIMAC, 301 Industrial Way, San Carlos, California 94070.
4. William Orr, W6SAI, *Radio Handbook*, 20th Edition, Howard W. Sams, Inc., Indianapolis, Indiana, (See "Low-frequency Parasitic Suppression," page 17.20.) (*The 22nd Edition of Radio Handbook is available from Ham Radio's Bookstore, Greenville, New Hampshire 03048, for \$12.95 plus \$3.50 shipping and handling.*)

ham radio

**BRAND NEW**


## BEAM ANTENNA HANDBOOK

by Bill Orr, W6SAI and Stu Cowan, W2LX

Completely revised and updated. Includes the very latest information on state-of-the-art antenna design. Accurate, computer generated beam dimensions for the 40, 30, 20, 17, 15, 12, 10 and 6 meter bands and VHF bands included. Also covered are: Beam height and optimum apex of radiation, how element types and hardware affect performance, effect of nearby objects on radiation patterns, feedlines, baluns and matching systems and much more. 268 clearly written pages — 204 illustrations  
©1985. 1st edition.

RP-BA Softbound \$9.95

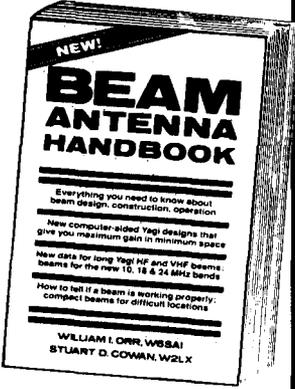Please enclose \$3.50 for shipping and handling.



**ham radio** **BOOKSTORE**  
GREENVILLE, NH 03048 (603) 878-1441

✓ 152

**DO YOU  
KNOW  
WHERE  
TO FIND  
REAL  
BARGAINS**



**on NEW and USED  
ELECTRONIC Equipment?**

**You'll Find Them  
in the Nation's No. 1  
Electronic Shopper Magazine**

# NUTS & VOLTS

**Now in Our 5th Year**

Nuts & Volts is published MONTHLY and features:  
**NEW STATE-OF-THE-ART PRODUCTS •  
SURPLUS EQUIPMENT • USED BARGAINS  
• LOW COST AD RATES • PRIVATE AND  
COMMERCIAL CLASSIFIEDS • NATIONAL  
CIRCULATION • NEW PRODUCT NEWS  
SECTION • AND A FREE CLASSIFIED AD  
WITH YOUR SUBSCRIPTION**

### SUBSCRIPTION RATES

- One Year - 3rd Class Mail ..... \$10.00
- One Year - 1st Class Mail ..... \$15.00
- One Year - Canada & Mexico (in U.S. Funds) .. \$18.00
- Lifetime - 3rd Class Mail (U.S. Only) ..... \$35.00

### ORDER NOW!

SEND:  CHECK  MONEY ORDER  
 VISA  MASTERCARD

TO: **NUTS & VOLTS MAGAZINE  
P.O. BOX 1111-H  
PLACENTIA, CALIFORNIA 92670  
(714) 632-7721**

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_  
Card No. \_\_\_\_\_  
Exp. Date \_\_\_\_\_

**IF YOU'RE INTO ELECTRONICS,  
THIS MAGAZINE WILL SAVE YOU MONEY!**

Dealer Inquiries Invited

✓ 153

# Your Ham Tube Headquarters!

**TUBES BOUGHT, SOLD AND TRADED  
SAVE \$\$\$—HIGH \$\$\$ FOR YOUR TUBES**

**Call Toll Free 800-221-0860**

Tubes		
3-400Z.....	\$85.00	7360.....\$10.00
3-500Z.....	85.00	7735A.....27.50
4-400A.....	80.00	8122.....110.00
4CX250B.....	50.00	8156.....12.50
572B.....	55.00	8643.....82.50
811A.....	12.00	8844.....26.50
813.....	30.00	8873.....175.00
6146B.....	6.50	8874.....195.00
6360.....	4.25	8877.....500.00
6883B.....	6.75	8908.....12.50

### MAJOR BRANDS ON RECEIVER TUBES 75% off list

Semiconductors	
MRF 245/SD1416..	\$30.00 SD1088.....19.95
MRF 454.....	14.95 2N3055.....75¢
MRF 455.....	10.95 2N6084.....12.50

RF Connectors	
PL259.....	10/\$4.95 M358.....2.50 ea.
PL258.....	10/8.95 M359.....1.75 ea.
UG 175/176.....	10/1.60 Type "N" Twist on
UG255/u.....	2.50 ea. (RG8/u).....\$4.75 ea.
UG273/u.....	2.25 ea. Minimum Order \$25.00

Allow \$3.00 min. for UPS charges ✓ 154



**COMMUNICATIONS, Inc.**

2115 Avenue X Brooklyn, NY 11235

SERVING THE INDUSTRY SINCE 1922 Phone (212) 646-6300  
Call CECo For Your CCTV Security And Color Production Requirements.



## Use Your Wireless Control FROM ANY ROOM!

Works with most infrared  
remote control receivers or VCR's.

### XTRALINK™



## SWITCH COMPONENTS REMOTELY

FOR YOUR  
**MRTV™**  
MULTI-ROOM TELEVISION  
SYSTEM



**Wholesale and Retail Sales**

# 800-545-3522

**In Wisconsin 800-362-7212**  
(Authorized Video Link™ Distributor)

**MERRIMAC** SPACE  
**SATELLITE**

327 Palisade St. Merrimac WI 53561 ✓ 155



# ham radio TECHNIQUES

Bill W6SAI

## big signals from the north

Have you heard those outstanding signals from Finland? Every active DXer has heard these block-busters in DX contests. Why? Because our friends up north have no hesitation about erecting *giant* antennas.


Consider the antenna system that Marti, OH2BH, uses. A photo of his "Christmas Tree" systems and rotator are shown in **figs. 1** and **2**. The 140-foot (42 meter) rotatable steel tower was manufactured and installed by OH8QD. It is guyed by nonmetallic Parafil ropes which terminate on slip rings. A heavy duty ART-8000 rotator supports the system.

A brace of six-element KLM beams is mounted on the tower — six over six on 20 meters at the 140-foot (42.6 meter) and 170-foot (51.8 meter) levels. Single six-element beams for 21 and 28 MHz are at the 120-foot (36.5 meter) and 95-foot (29-meter) levels. Antenna switching is accomplished by a set of remotely controlled vacuum relays located at the 105-foot (32-meter) level.

The relay allows a selection of either one or both of the antennas. Three SPST (single pole, single throw) relays are used in **fig. 3**. The relays are shown in the "off" position. Coax line L1 is an electrical 1/4-wavelength of 75-ohm coax and transforms the nominal 50-ohm antenna feedpoint resistance to about 112 ohms. The two 112-ohm ports at relay 2 are put in parallel and become a 56-ohm termination that closely matches the 50-ohm

system design value. The relays are in a weatherproof box mounted halfway between the antennas. Fifty-ohm lines from the box run to each antenna.

A representation of the relay wiring in the box is shown in **fig. 4**, as is the switching table located at the operating position.

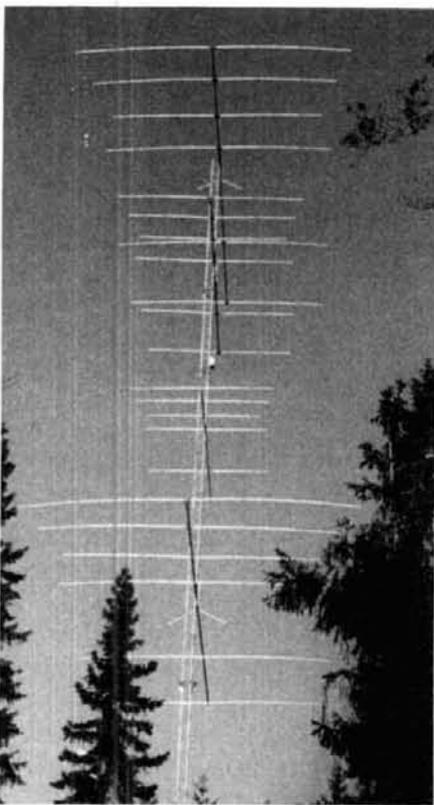

**fig. 1.** The "Christmas tree" antenna at the contest site of Marty, OH2BH. Six-over-six elements on 20 meters, backed up by single six-element beams on 21 and 28 MHz are mounted on the 170-foot high tower. The 20-meter beams can be switched in combinations from the operating position.

To reduce vibration in the antenna system, which could be destructive in harsh winter storms, each element has a 5-foot (1.5 meter) length of rope cemented into the inside of the outer element tips.

Another interesting antenna installation is that of Simon, OH8OS. A close-up view is shown in **fig. 5** and the slip-ring assembly is shown in **fig. 6**. The antenna is composed of eight six-element beams, stacked two-over-two! OH6JW is believed to have a similar setup. The tower sits on a rotator and the guys are attached to slip rings at appropriate levels.

No doubt other big arrays exist. I'd like to receive pictures of them to put in this column!

## how about 160 meters?

Even though there aren't any stacked, rotary arrays on 160 meters that I know of, there are certainly some big signals from well-known DXers on this band. One of the prominent signals on this band (and on others) comes from Jay, AD8C. Jay has a 106-foot (32.3 meter) Rohn tower, guyed at three levels with 1/4-inch (0.6 cm) diameter stranded steel wire. Only the top set of guys is broken by insulators at 25-foot (7.6 meter) intervals. A length of heavy-wall aluminum tubing projects 15 feet (4.5 meters) above the top of the tower. The tower is turned by a W0MLY-modified prop-pitch rotator.

On 160 meters, the tower is shunted with an 82-foot (25 meter) length of electrical conduit as the gamma rod, spaced 1.5 feet (0.45 meter) from the

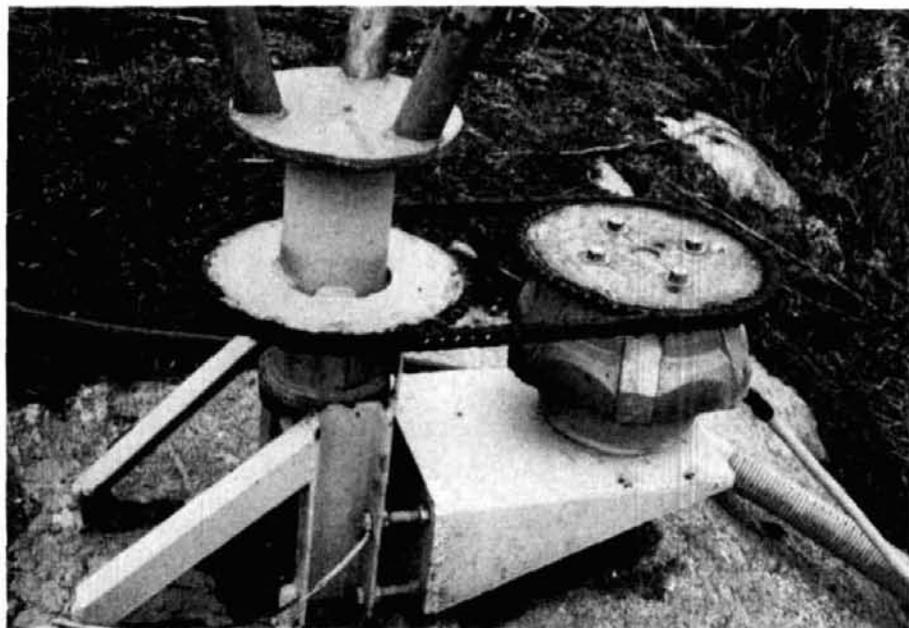


fig. 2. The 170-foot high tower of OH2BH is rotatable. This is view of the base support and the offset rotating mechanism. The tower is guyed by nonmetallic Parafil ropes which terminate on slip rings.

tower. Thirty radials are used, with 15 of them a full quarter-wavelength long. A 5kV, 1000 pF vacuum variable capacitor is used as the gamma capacitor. The 2-to-1 bandwidth of the antenna is about 55 kHz.

As for the other bands, Jay uses five phased slopers on 80 meters, patterned after the 40-meter system described in the ARRL *Antenna Handbook* (1974 edition). It provides about 3 dB forward gain and a front-to-back ratio of about 10 to 15 dB.

The rest of the antennas include: a three-element Yagi for 7 MHz at 107 feet (32.6 meters), a four-element Yagi for 14 MHz at 120 feet (36.5 meters), and four-element Yagis for 15 and 10 meters at 55 and 113 feet (16.7 and 34.4 meters). To complete the "antenna farm," there is an eight-element Yagi for 2 meters at 95 feet (29 meters).

Jay says he is satisfied with the installation that it has withstood severe winter storms, and does a "credible job" in DX pileups, particularly on the lower bands.

One of the outstanding 160-meter signals from Asia comes from Kuni, JA7NI, who lives in a three-story

apartment house. Atop the building Kuni has a 46-foot (14 meter) high heavy wall aluminum mast (fig. 7). The mast is top-loaded by a 76-foot (23 meter) length of wire that slopes downward to a short pole mounted on an adjacent building. The aluminum roof trim of his building is used as a ground connection. The antenna works well; Amateurs in all US districts have been contacted, with many QSOs made along the east coast, including WA2SPL, W1FC, W2FJ, K2EK, KC2SB, W3ESU, and others.

After getting this information, I wrote Joe, WA2SPL, to see what antennas he's used for DX work to Japan. He told me that his first 160-meter antenna was an inverted-vee with the apex at 150 feet (45.7 meters) and the ends at 75 feet (22.8 meters). Joe says that although it was a "pretty good" antenna for transmitting, precipitation static during snow storms made the antenna useless for receiving. He then put up a 1000-foot (348 meter) Beverage antenna for receiving that worked very well. On the common assumption that "if big is good, bigger is better," Joe erected a 1500-foot (457 meter) Beverage wire

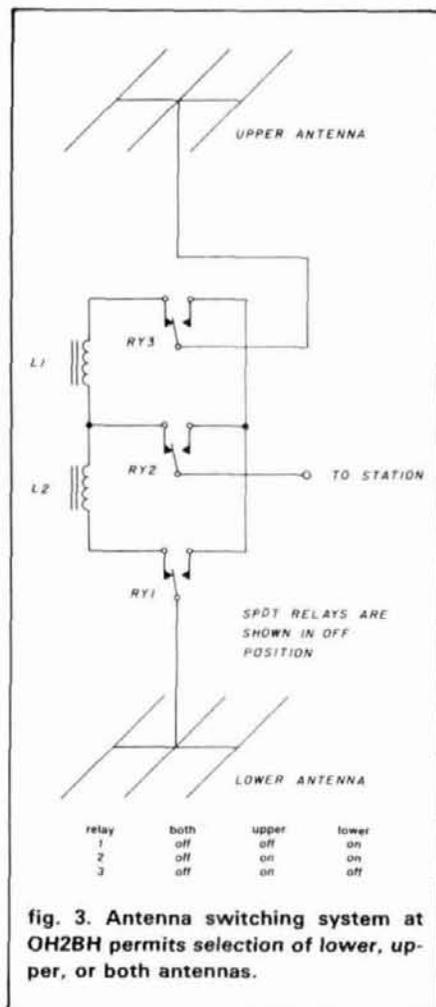


fig. 3. Antenna switching system at OH2BH permits selection of lower, upper, or both antennas.

that proved to be even better than the shorter one.

The next step was to raise the inverted-vee to 200 feet (61 meters), with the ends at 90 feet (27.4 meters). This produced an immediate improvement in his signal — to the point at which he couldn't hear some of the DX that called him! So Joe went back to modifying the Beverage receiving antenna.

It was obvious that more and better Beverages were needed, so Joe put up a 2100-foot (640 meter) wire for Europe, a 1500-foot (457 meter) wire aimed at Japan, a 1000-foot (348 meter) wire for South America, a 1,000-foot wire on the Caribbean and a 3100-foot (944 meter) wire aimed at Australia/New Zealand. (Where do these guys get the space to put up these antennas?)

# NEMAL ELECTRONICS INTL., INC.

SEE US AT DAYTON BOOTH #104

your one stop coax supplier!



## Exclusive SATELLITE CONTROL CABLE

5 TYPES AVAILABLE!

NEW!!! Lowest Loss

AVAILABLE IN  
250-500-1000  
FT. ROLLS  
OR BY  
THE FOOT



TYPE 1 (General Purpose)	TYPE 2 (MTI)	TYPE 3 (Interstat)	TYPE 4	TYPE 5
1 - RG59/U 96% Copper Braid	1 - RG59/U 96% Copper Braid	1 - RG59/U 96% Copper Braid	1 - RG6/U 18 Gauge 96% Copper Shield	1 - RG6/U 18 Gauge 96% Copper Shield
2 @ 17 Gauge				
3 @ 18 Gauge				
3 @ 19 Gauge				
Shielded plus Tinned Copper Drain Wire				
55¢ FT	75¢ FT	95¢ FT	79¢ FT	89¢ FT

Designed for easy one-step installation providing the required cables for most earth station equipment all in a direct burial jacket

Only Nermal offers the quality construction RG59/U copper shielding made to mil spec JAN C 17-12 gauge conductors, tinned copper drain wires, and a true direct burial polyethylene jacket

Call for 1000 FT pricing

### HARDLINE

Two styles, two sizes for all installation needs

- Aluminum Outer Conductor with Polyethylene Jacket
    - 1/2 inch loss .48 dB/100 ft. @ 30 MHz
    - 3.68 dB/100 ft. @ 1000 MHz ..... \$1.25/ft.
    - 7/8 inch loss .28 dB/100 ft. @ 30 MHz
    - 2.54 dB/100 ft. @ 1000 MHz ..... \$3.25/ft.
  - Corrugated Copper Outer Conductor with Polyethylene Jacket
    - 1/2 inch loss .38 dB/100 ft. @ 30 MHz (FLC12-50J) 2.78 dB/100 ft. @ 1000 MHz ..... \$1.59/ft.
    - 7/8 inch loss .13 dB/100 ft. @ 30 MHz (FLC12-78J) 1.3 dB/100 ft. @ 1000 MHz ..... \$3.92/ft.
- COMPARE RG 213 1.25 dB/100 @ 30 MHz  
8.5 dB/100 @ 1000 MHz !

### HARDLINE CONNECTORS

- 1/2 inch aluminum UHF M/F \$19.00 Type N M/F \$22.00
- 7/8 inch aluminum UHF M/F \$49.00 Type N M/F \$49.00
- 1/2 inch copper UHF M/F \$22.00 Type N M/F \$22.00
- 7/8 inch copper UHF M/F \$49.00 Type N M/F \$49.00

#### shipping

Cable — \$6.00 per 100 ft.  
Connectors — \$3.00 per order.  
Orders under \$20 add \$2 additional plus shipping.  
Charge card — orders over \$30 only.  
COD add \$2.00. Florida Residents add 5%.

FACTORY AUTHORIZED DISTRIBUTOR  
AMPHENOL, CABLEWAVE, COLUMBIA, KINGS  
BLONDER-TONGUE, TYTON, B&K

- COAXIAL CABLE
- MULTICONDUCTOR CABLE
- CONNECTORS-ADAPTERS
- HARDLINE
- CABLE TIES
- SMATV PRODUCTS
- COAX-SEAL
- COMPUTER CABLE
- CRIMP TOOLS
- FIELD STRENGTH METER



12240 N.E. 14th Ave.  
No. Miami, FL 33161  
Telephone: (305) 893-3924

IN STOCK  
— OVER 500 ITEMS —  
COMPLETE LINES

✓ 156

## DRAKE R-4/T-4X OWNERS AVOID OBSOLESCENCE

PLUG-IN SOLID STATE TUBES!  
Get state-of-the-art performance.  
Most types available

INSTALL KITS TO UPGRADE PERFORMANCE!

- BASIC Improvement
- Audio Bandpass Filter
- Audio IC Amplifier

TUBES \$23 PPD KITS \$25 PPD

OVERSEAS AIR \$7

SARTORI ASSOCIATES, W5DA  
BOX 832085  
RICHARDSON, TX 75083  
214-494-3093 ✓ 186

### SYNTHESIZED SIGNAL GENERATOR



MADE IN USA

MODEL  
SG-100F  
\$429.95  
delivered

- Covers 100 MHz to 199.999 MHz in 1 kHz steps with thumbwheel dial
- Accuracy +/- 1 part per 10 million at all frequencies
- Internal FM adjustable from 0 to 100 kHz at a 1 kHz rate
- External FM input accepts tones or voice
- Spurs and noise at least 60 dB below carrier
- Output adjustable from 5-500 mV at 50 Ohms
- Operates on 12 Vdc @ 1/2 Amp
- Available for immediate delivery
- \$429.95 delivered
- Add-on accessories available to extend freq range, add infinite resolution, AM, and a precision 120 dB attenuator
- Call or write for details
- Phone in your order for fast COD shipment.

✓ 187

### VANGUARD LABS

196-23 Jamaica Ave., Hollis, NY 11423  
Phone: (718) 468-2720 Mon. thru Thu.

### GROTH-Type COUNTS & DISPLAYS YOUR TURNS

- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

Case: 2x4"; shaft 1/4"x3"

TC2 \$12.50 Model TC2: Skirt 2-1/8"; Knob 1-5/8"

TC3 \$13.50 Model TC3: Skirt 3"; Knob 2-3/8"

Spinner Handle Add \$1.50

Prices include UPS or Parcel Post in US

R. H. BAUMAN SALES

P.O. Box 122, Itasca, Ill. 60143

✓ 157

## CADDELL COIL CORP.

35 Main Street  
Poultney, VT 05764  
802-287-4055

### BALUNS

Get POWER to your antenna! Our Baluns are already wound and ready for installation in your transmatch or you may enclose them in a weatherproof box and connect them directly at the antenna. They are designed for 3-30 MHz operation. (See ARRL Handbook pages 19-9 or 6-20 for construction details.)

100 Watt (4:1, 6:1, 9:1, or 1:1 Impedance - select one)	\$ 8.50
Universal Transmatch 1 KW (4:1 Impedance)	12.50
Universal Transmatch 2 KW (4:1 Impedance)	15.00
Universal Transmatch 1 KW (6:1, 9:1 or 1:1-select one)	14.00
Universal Transmatch 2 KW (6:1, 9:1 or 1:1-select one)	18.50

Please send large SASE for info.


### "HAM HOTLINE" THE PROVEN MONEYMAKER

The "Ham Hotline" is a complete mailing list of novice amateur radio operators and current hams who have renewed, upgraded or modified their FCC licenses. These ham enthusiasts have proven to be excellent prospects for radio equipment, accessories and publications.

The Hotline is **UPDATED EVERY TWO WEEKS** with an average of 8,000 names and addresses each month. And, because we know the Hotline is the most up-to-date amateur radio listing available, we'll guarantee 98% deliverability.

Target your sales efforts to your most likely buyers. Call DCC Data Service today and begin your subscription to the "Ham Hotline" . . . the proven moneymaker.

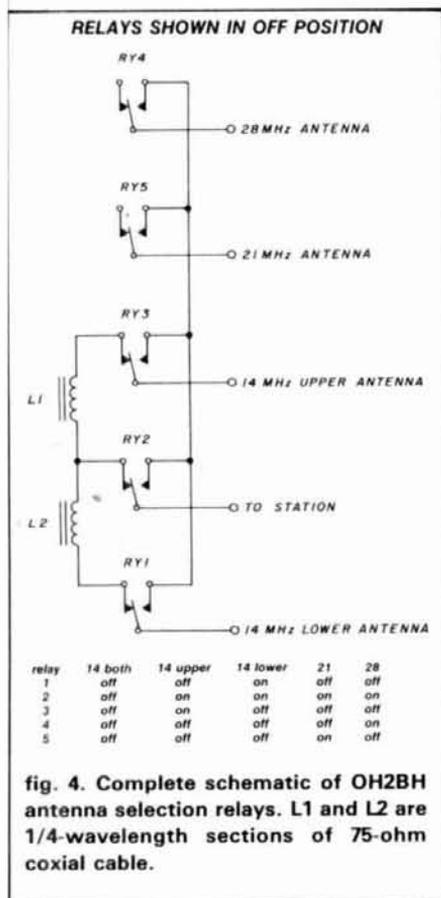DCC Data Service, Inc.  
1990 M Street, N.W. Suite 610  
Washington, D.C. 20036  
(202) 452-1419 ✓ 188




After a few months Joe found out that a Beverage antenna could be too long. He pruned the 3100-foot wire back to 1500 feet (457 meters) and it worked much better.

With each antenna, a 20 dB pre-amplifier was used to bring signals up to good copy. By this time, Joe had 150 countries to his credit on 160 meters!

Even with his success with the Vee and the Beverages, Joe was curious about the luck his DX friends had with vertical antennas on 160 meters. For various reasons, he couldn't shunt-feed his 200-foot tower, so he dropped a rope down on a 45-degree angle to the ground and lowered a wire to ground level from the 130 foot (40 meter) elevation on the rope. He placed 24 quarter-wave radials beneath the vertical antenna.

He soon discovered, by direct comparison, that under no conditions did the vertical perform better than the

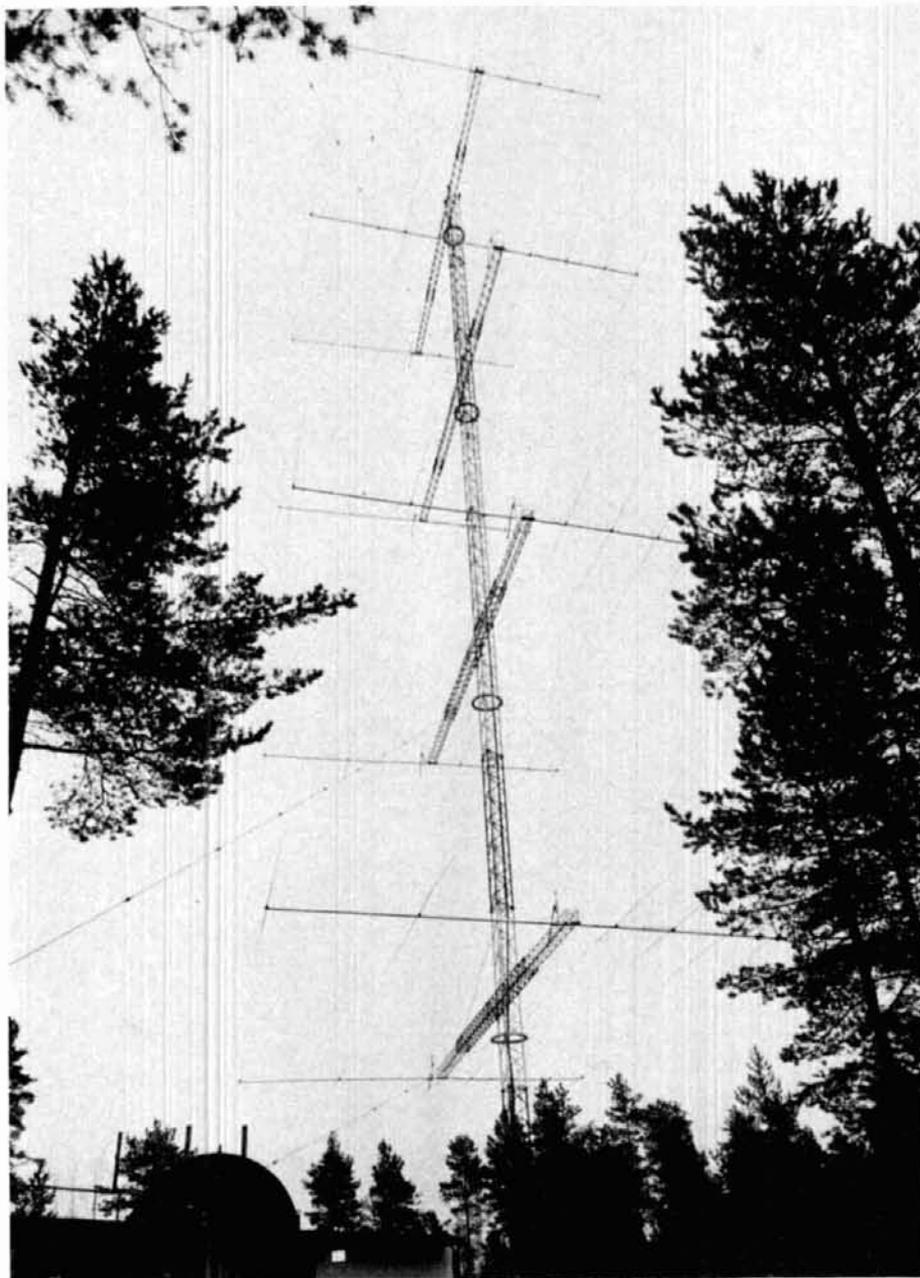

**fig. 5. The monster 20-meter array of Simon, OH8OS. The antenna consists of eight six-element beams, stacked two-over-two. Simon puts through an S-9+ signal on the West Coast of the USA when other Europeans are inaudible. The complete tower is rotatable.**

high Vee antenna. He was sure that the vertical was relatively worthless until he later met Dana, W1CF, and went to Dana's station to work it during a CQ Worldwide DX contest. The station was equipped with two 1200-foot (365 meter) Beverage receiving antennas, plus two Col-Atch-Co 61-foot (18.6 meter) verticals with 80 radials under each one. The contest results were amazing — the W1CF station

ended up with 830 QSOs and a score of 323,000 points!

Now Joe is wondering why his full-size vertical seemed to perform so poorly. Too few radials? Low conductivity ground in the vicinity of the antenna? He may soon have the answer. He's moving to a new location, and by the time you read this, he may have put up his new 160-meter antenna system — four full-size, phased

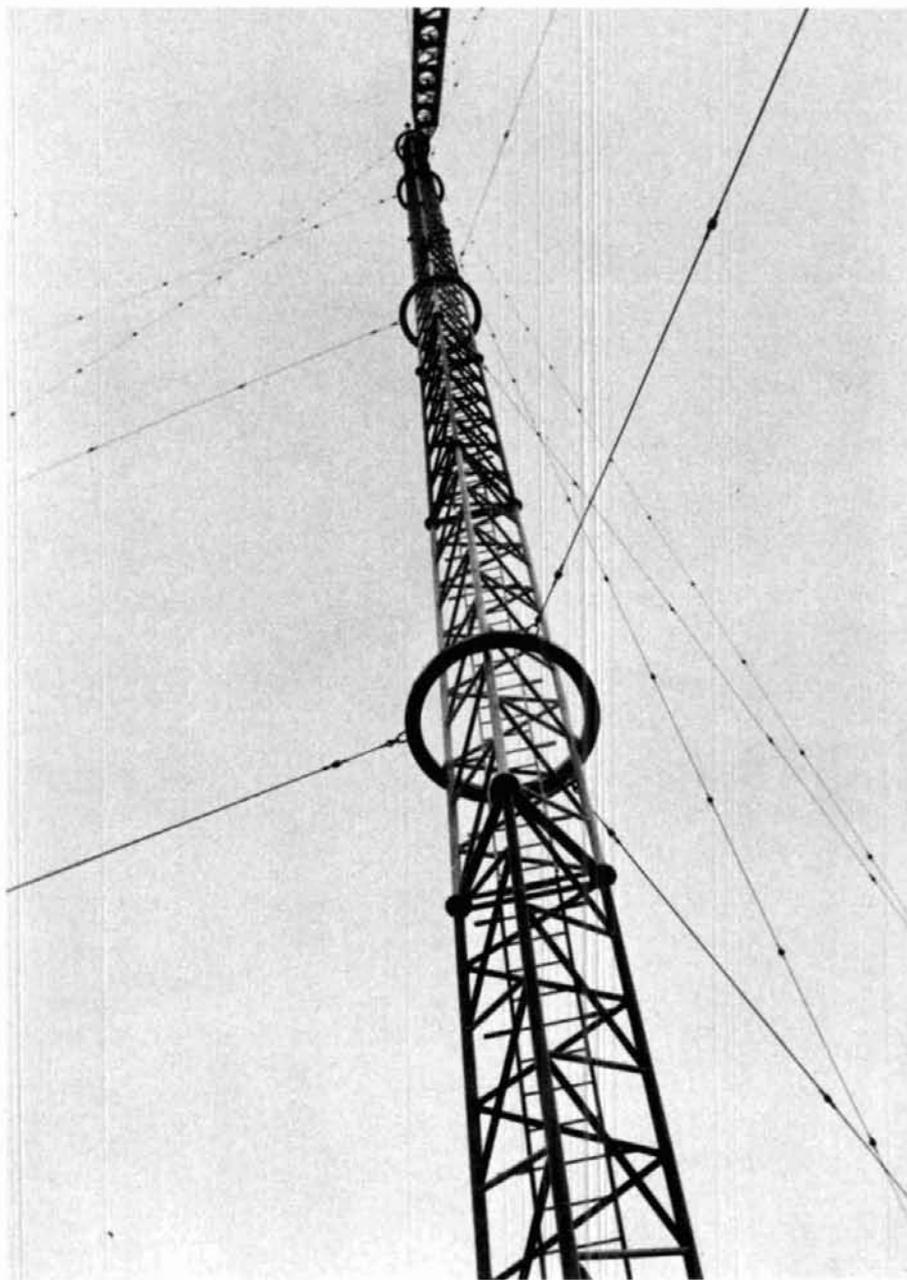


fig. 6. Slip-ring installation on tower of OH8OS. Would you care to climb the ladder to the top array? (Visible at top of picture is the arm of the crane ready to lift the antennas to their final positions on the tower.)

verticals on a mountain in northern Vermont. JA7NI, keep your ears open for this one!

You *can* be a topnotch 160-meter DXer with only a simple antenna. Bob, VE1YX, says, "No super-antenna here! I have a simple, coax-fed dipole, 60 feet high on a hilltop about 450 feet above sea level. So far, 135 countries — the best DX being VK6HD long path at 2100Z."

### long-wave hams in Australia

Sixteen years ago, before WARC 79, the United States considered an Amateur band in the 160-190 kHz region. The idea had merit, but opposition arose because this was the range used by carrier current data transmissions on power lines and also by long-wave European broadcasting stations. Sadly, the idea was dropped before WARC 79 started.

Even so, John (VK3ACA) and Peter (VK3QI) pursued the idea with the Department of Communications in Australia and, after a pause, they were issued experimental licenses for low frequency operation on 196 kHz (153 meters). John received the call sign AX3T35 and Peter became AX3T36. A third Amateur, Dennis (VK3WV), joined them and got the call sign VL3 (fig. 8). The stations all ran about 10 watts input.

Antennas were a problem. AX3T35 used a 30-foot vertical with a huge base loading coil and an extensive grounding system. He estimated his antenna efficiency was about 0.37 per cent. Station VL3Y used a 135-foot wire, which wasn't much better. Even with the poor antennas, the first contact was made in April, 1981. Continued contacts between the three sections showed that the propagation range via ground wave was about 30 miles during daylight, and possibly more during the hours of darkness.

AX3T35 is writing an article, scheduled to appear shortly in the journal of the Wireless Institute of Australia: *Amateur Radio*, about the experience of the only three licensed low-frequency ham stations in the world (Good work, lads — I'll put a shrimp on the barbie for you!)

### an anti-jamming HF loop antenna

People other than Radio Amateurs are interested in efficient and effective HF antennas. Radio Free Europe, in particular, tries in every way to combat the Soviet jamming that plagues their broadcasts. In this regard, they have published information on building a simple and inexpensive directional receiving antenna that can be helpful in reducing jamming interference. Details of this antenna are shown in (fig. 9.)

The antenna consists of a shielded loop made of coax cable (RG-58/U, or RG-59/U, for example). A smaller loop couples the tuned loop to the receiver. To hold the cables in the loop form a wooden support in the shape of a cross is used. The coax is passed

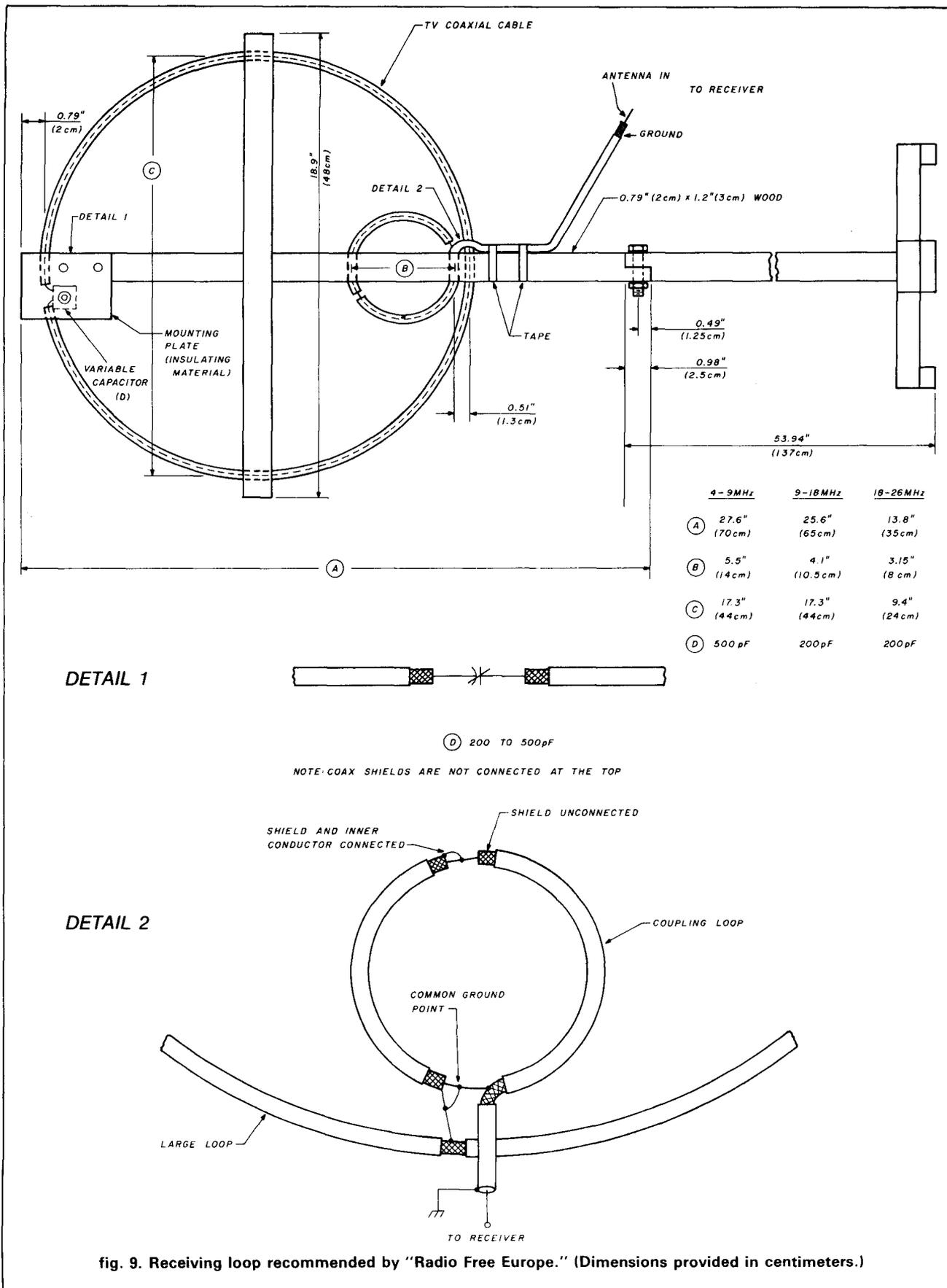


fig. 9. Receiving loop recommended by "Radio Free Europe." (Dimensions provided in centimeters.)

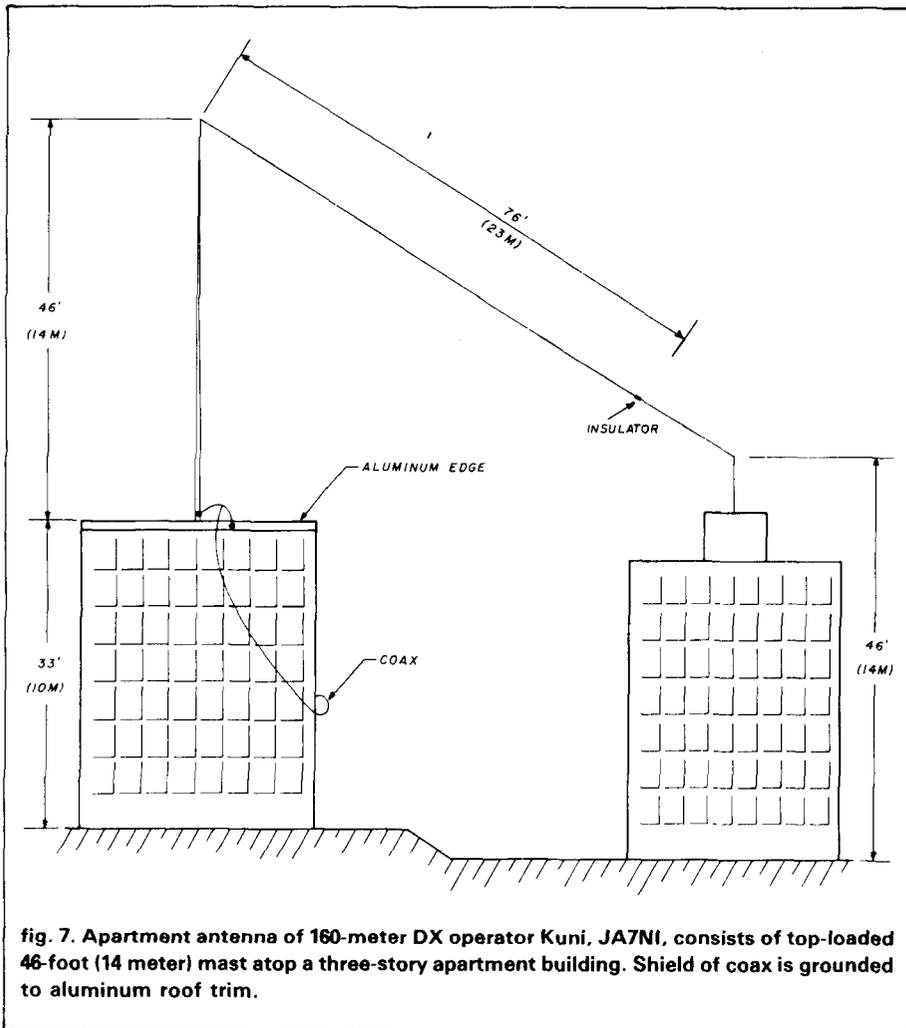


fig. 7. Apartment antenna of 160-meter DX operator Kuni, JA7NI, consists of top-loaded 46-foot (14 meter) mast atop a three-story apartment building. Shield of coax is grounded to aluminum roof trim.

through appropriate holes in the structure. A variable capacitor at the open end of the loop tunes it to the required frequency. The coupling link matches the symmetrical, balanced loop to the unbalanced coax line to the receiver.

The vertical portion of the support structure is hinged to allow tilting the antenna for improvement of the rejection null. The antenna can be rotated horizontally to provide both azimuth and elevation alignment.

To cover the shortwave spectrum from 4 to 26 MHz, three loop sizes are required, as shown in fig. 9.

To use the loop antenna, receiver and antenna are tuned for maximum signal at the desired frequency. The antenna is then rotated and tilted to minimize the interfering signal. A reduction of 30-to-1 in jamming strength is predicted for short wave

listeners, depending upon the location of the jamming station with respect to the desired station.

While Radio Amateurs may not use the loop for reduction of intentional jamming, this design may prove to be of benefit for operation in DX contests where it's helpful to null out loud local competition.

Because of the reduced pickup of the loop compared to a full-size antenna, it may be necessary to add a preamplifier between loop and receiver to bring signals up to full strength.

### the new *Beam Antenna Handbook*

For the past two years I've been absent from the bands, devoting every moment of my spare time to completing, with Stu, W2LX, the extensive revision of the *Beam Antenna Hand-*

Dennis Silett, 40 Mather Rd, Noble Park, Vic  
Melbourne Australia

EXPERIMENTAL STATION

**VL3Y**

crim ~~447~~ / QSO 113735 Date 10-7-83 Time 2140 AEST  
Freq 196 KHz Mode 1K0A0N RST 599  
Rx QRL66 Tx Mod. AT5 Ant 125' wire  
Pwr 17 w. 1/P Qst psc 73 Dennis

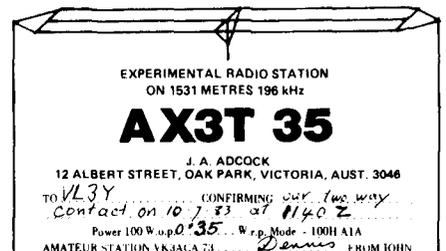


fig. 8. QSL cards of low-frequency experimental Amateur stations in Australia.

book. It was a lengthy job; the old text was ripped apart and new text prepared. New illustrations were added. New, up-to-date antenna dimensions, based upon recent computer studies conducted on Yagi arrays were cataloged. The result, after much hard work, is a completely new edition of *Beam*.\*

The book includes new data on HF Yagi antennas (two to five elements), element spacing, and the effect of element taper. There's new information on erecting beams and general installation data as well. VHF long Yagis are covered, together with complete design tables for the home constructor. Complete English and metric dimensions are given for all antennas.

There's helpful information on feed systems and SWR measurements. A systematic test procedure is provided to help you determine whether your beam is operating properly. The information on checking the accuracy of your SWR meter is worth the price of admission!

Now that the book is ready, perhaps I'll have time to get on the air! Or will another project come along?

\*Available from Ham Radio's Bookstore, Greenville, New Hampshire 03048, \$9.95 plus \$2.50 shipping and handling.


ham radio



# B. G. MICRO

P. O. Box 280298 Dallas, Texas 75228

(214) 271-5546

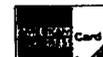

## 74LS

LS00	.20	LS163	.45
LS01	.20	LS164	.65
LS02	.20	LS165	.90
LS03	.20	LS166	.99
LS04	.20	LS169	1.25
LS05	.20	LS174	.45
LS08	.20	LS175	.40
LS09	.20	LS181	1.50
LS10	.20	LS191	.90
LS11	.20	LS192	.80
LS12	.35	LS193	.80
LS13	.40	LS194	.65
LS14	.40	LS195	.60
LS15	.32	LS196	.70
LS20	.20	LS197	.85
LS21	.25	LS221	.65
LS27	.28	LS240	1.00
LS30	.20	LS241	.80
LS32	.25	LS242	1.00
LS33	.40	LS243	1.00
LS37	.33	LS244	1.00
LS38	.30	LS245	1.00
LS42	.40	LS251	.50
LS51	.24	LS253	.50
LS54	.25	LS257	.50
LS55	.24	LS258	.55
LS73	.35	LS259	2.00
LS74	.30	LS260	.50
LS85	.60	LS266	.40
LS86	.25	LS273	1.00
LS90	.50	LS279	.40
LS93	.55	LS280	1.00
LS107	.37	LS283	.50
LS109	.25	LS290	.85
LS112	.30	LS293	.85
LS122	.45	LS298	.75
LS123	.55	LS299	1.60
LS124	2.00	LS323	2.60
LS125	.40	LS348	.75
LS126	.49	LS364	1.10
LS132	.50	LS366	.45
LS133	.35	LS367	.50
LS138	.45	LS368	.40
LS139	.40	LS373	1.00
LS151	.45	LS374	1.00
LS153	.40	LS375	.50
LS154	.99	LS377	1.00
LS155	.50	LS378	.85
LS156	.50	LS390	1.00
LS157	.40	LS393	1.00
LS158	.50	LS399	1.25
LS160	.65	LS670	1.50
LS161	.50	25LS2569	3.00
LS162	.65		

## TTL

7400	.22	7473	.34	74162	.60
7402	.22	7474	.40	74163	.60
7405	.22	7483	.45	74164	.80
7406	.33	7485	.55	74165	.80
7407	.33	7486	.30	74166	1.00
7408	.24	7490	.35	74173	.75
7410	.19	7493	.33	74174	.85
7413	.33	7496	.40	74175	.80
7420	.22	74107	.28	74181	1.50
7425	.25	74109	.45	74185	1.70
7427	.25	74121	.27	74192	.70
7428	.25	74123	.40	74193	.80
7430	.20	74125	.49	74195	.80
7432	.27	74132	.40	74199	1.00
7433	.25	74148	1.00	74221	1.00
7440	.19	74151	.50	74273	1.75
7442	.40	74153	.50	74365	.60
7451	.20	74154	1.19	74366	.60
7453	.22	74157	.50	74367	.60
7454	.22	74160	.80	74390	1.40
7472	.25	74161	.60		

## EPROM

2708 1KX8 450 n.s.	2.20
2758 1KX8 +5V 450 n.s.	2.00
2716 2KX8 450 n.s.	2.75
2716-1 2KX8 350 n.s.	4.50
2732 4KX8 450 n.s.	3.65
2732A	4.00
2732A-35	3.75
2532 4KX8 450 n.s.	3.00
2764-25	3.50
2764-45	3.00
27128-25	5.00
27128-3	4.50
27128-45	3.50

## EPROM SPECIAL

We bought a large quantity of 2708s from a computer manufacturer who redesigned their boards. We removed them from sockets, erased and verified them, and now we offer the savings to you. Complete satisfaction guaranteed.

2708

\$1.49 or 10/\$12.00

## STATIC RAM

2016-2KX8 200 n.s.	2.50
2101-1 - 256X4 500 n.s.	.75
21L02-1 350 n.s.	.65
2102AL-4 L.P. 450 n.s.	.49
2111-1 256X4 500 n.s.	1.50
2114L-3 1KX4 300 n.s.	1.00
2125A-2 1KX1 70 n.s.	2.20
2142-3 1KX4 300 n.s.	1.50
2147 4KX1	3.95
TMS4044 4KX1	1.00
6116P-4-2KX8	2.50
6264-15	7.50

## BAUD RATE GENERATOR

COM8116	6.95
INS8250B	7.95

## DRIVERS & RECEIVERS

75107	.75
75110	.80
75451	.35
75452	.35

## DYNAMIC RAM

2108-4 8KX1	1.50
2118-4 16KX1-5Volt	1.50
4027-4KX1-250 n.s.	.80
4116-16KX1-250 n.s.	.60
4116-16KX1-200 n.s.	.75
4116 16KX1-150 n.s.	1.00
4164- +5v 64K 200 n.s.	1.05
4164 150 n.s.	1.30
TMS4416-16KX4-150 n.s.	3.95
MK4516-15 16KX1-5Volt	1.50
5280N-5 (2107B-4 • TMS4060) 4KX1	8/3.95
41256 150 n.s.	5.00

## SPECIAL

AY3-8910  
W/60 Page Manual  
New Price — \$7.00

58321 Clock-Calendar	2.95
----------------------	------

## 8000

Z8002	20.00	8085	3.00
8035	3.00	8086-2	24.95
8039	3.00	8087-3	129.00
8080A	1.25	8088	9.00

## 8200

8202A	8.00	8254	7.50
D8203-1	29.95	8255-5	4.00
8212	1.50	8257	6.00
8214	2.00	8259A	3.50
8216	1.75	8259C-5	5.00
8228	3.25	8275	14.95
8237-5	5.00	8279-5	5.75
8250B	7.95	8284	3.00
8251	4.20	8287	5.75
8253-5	5.95	8288	7.50

## Z80

Z80 2.5 MHZ CPU	1.25
Z80CTC	.75
Z80DMA-DMA	7.50
Z80PIO	1.25
Z80SIO/O	3.50
Z80A-4MHZ CPU	1.99
Z80A-CTC	1.50
Z80A DART	7.50
Z80A-DMA	9.00
Z80A-PIO	1.99
Z80A SIO/O	4.99
Z80B 6 MHZ CPU	7.00

## F.D. CONTROLLERS

1771 Single Density	12.95
1793 Special	12.50
1797	15.00
2793	20.00
2797	15.00

## CONTROLLER SET

THREE CHIP SET

1797 or 1793, 2143-03, 1691

by W.D.

B.G. SPECIAL

All 3 for only \$20.00

## UART

TR1602B (COM 2017)	1.75
IM6402-(1863)+5v High speed AY5-1013 pin out	2.95
INS 8250B	7.95

## 6800

6800	2.50	6840	10.00
6802	3.50	6845P	4.00
6803	5.00	6845S	7.50
6808EP	3.99	6850	2.60
6810	2.00	68A09EP	4.99
6820	3.25	68A21	3.00
6821	1.50	68B45	10.00

## 6500

6502	2.60	6545	5.00
6522	4.00	6551	5.00
6532	5.70		

## SPECIALS

8155	3.95
9216	4.00
TMS99532	19.95
BR1941L	5.95
LF353	.60
LF356	.60
TL494	2.50
LM555	.30
9401	5.00
DS8835	1.50
MC4024P	2.50
NE592	1.00
MC1350	1.00
LM2917	.50
LM339	.50

## SOCKETS

Low Profile SOLDER TAIL	
6 Pin	14/1.00
8 Pin	13/1.00
14 Pin	10/1.00
16 Pin	8/1.00
18 Pin	8/1.00
20 Pin	7/1.00
22 Pin	7/1.00
24 Pin	6/1.00
28 Pin	6/1.00
40 Pin	5/1.00

BUY \$10  
GET \$1.00 - FREE CHOICE


## 2114 SPECIAL!

COMPUTER MANUFACTURERS EXCESS INVENTORY SALE!  
PRIME! 2114-300 n.s. INCREDIBLE PRICE!  
YOU SAVE!  
65¢  
GUARANTEED

## CRYSTALS

32.768 KHz SPECIAL	.65
262.144	.75
300.000	.75
1.5432 Mhz	.75
1.8432	2.49
2.000000	2.49
2.560	1.49
3.000	1.15
3.120	1.20
3.2	1.49
3.4560	1.49
3.579545	.75
3.6864	1.10
4.000	1.75
4.194304	1.50
4.433618	.75
4444.000	1.25
4.9152	2.49
4.916 Bd. Rate	1.25
5.000000	1.50
5.0688	2.50
5.616	1.59
6.000	2.49
6.176	1.49
7.164112	1.00
7.3728	1.49
8.000	1.49
9.000	1.49
9.90000	1.25
10.69425	2.50
10.8664	1.49
10.920	1.49
11.088	1.59
12.000	2.75
13.440	1.00
14.31818	1.00
15.2	1.10
16.00000	1.50
16.5888	1.49
17.430	2.49
18.000	1.49
18.2259	1.00
18.4320	1.49
20.000	1.50
21.87108	1.00
22.092	1.00
32.000	2.49
40.000	2.00
87.3333	1.00
91.000	1.00
104.8	1.00

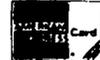TERMS: (Unless specified elsewhere) Add \$1.50 postage, we pay balance. Orders over \$50.00 add 8% for insurance. No C.O.D. Texas Res. add 6-1/8% Tax. 90 Day Money Back Guarantee on all items. All items subject to prior sale. Prices subject to change without notice. Foreign order - US funds only. We cannot ship to Mexico. Countries other than Canada, add \$3.50 shipping and handling.



**Big Computer Mfg. Makes \$900,000 Goof!!**

## COMPUTER/DISK DRIVE SWITCHING POWER SUPPLY

ORIGINALLY DESIGNED TO RUN A Z-80  
BASED SINGLE BOARD COMPUTER  
WITH TWO 5-1/4 IN. DISK DRIVES AND  
CRT MONITOR.


ORIGINAL  
OEM COST  
\$72 EACH!

BRAND NEW: UNUSED!

**\$24<sup>95</sup>** EA

**NEW  
PRICE**

ADD \$1.50 PER UNIT FOR UPS

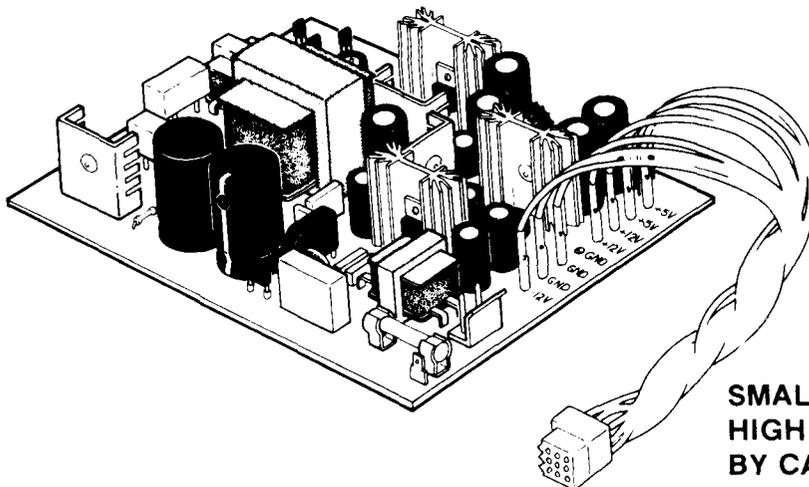

SPECS: + 5VDC 5 AMPS MAX  
#1 + 12 VDC 2.8 AMPS MAX  
#2 + 12 VDC 2.0 AMPS MAX  
- 12 VDC .5 AMPS MAX


INPUT: 115 or 230 VAC 60Hz

CAN EASILY BE MODIFIED TO  
GIVE 24V @ 1.5 AMP

SMALL SIZE: 6-1/8 x 7-3/8 In.  
HIGH EFFICIENCY SWITCHER MFG.  
BY CAL. DC IN USA!

The poor Purchasing Agent bought about 10 times as many of these DC switchers as his company would ever use! We were told that even in 10,000 piece lots they paid over \$72 each for these multi-output switchers. When this large computer manufacturer discontinued their Z-80 Computer, guess what the Big Boss found in the back warehouse; several truckloads of unused \$72.00 power supplies. Fortunately we heard about the deal and made the surplus buy of the decade. Even though we bought a huge quantity, please order early to avoid disappointment. Please do not confuse these high quality American made power supplies with the cheap import units sold by others.

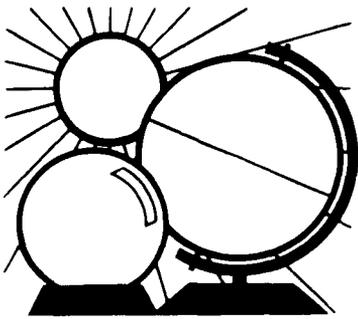TERMS: (Unless specified elsewhere) Add \$1.50 postage, we pay balance, orders over \$50.00 add 85¢ for insurance. No C.O.D. Texas Res. add 6-1/8% Tax. 90 Day Money Back Guarantee on all items. All items subject to prior sale. Prices subject to change without notice. Foreign order - US funds only. We cannot ship to Mexico. Countries other than Canada, add \$3.50 shipping and handling.



# DX FORECASTER

Garth Stonehocker, KØRYW

## signal levels during the summer months

Absorption results in loss of energy from the signal as it collides with ions on its path through the D region, 60-80 miles (100-120 km) above the earth. How much energy is absorbed per transit of the D region depends on the location of the sun, and is a function of cosine X, the zenith angle to the sun. Maximum absorption occurs at the subsolar point, directly under the sun; absorption decreases as the signal path moves away from the subsolar point in any direction.

On any propagation path, absorption increases with the number of crossings of the D region and also varies inversely with frequency. Therefore, in working DX it pays to use the higher frequency bands and obtain consequently greater distances per hop.

In a study of several midlatitude communication links of varied lengths over the years of this 10.7 solar cycle, some general trends were noticed. The ionosphere, a balanced energy system tends to return to a "normal" level of ion density after each new solar perturbation. It is a fact that between sunspot numbers 20 and 120, signal absorption changes only by approximately 8 dB for a one-hop path 2500 km in length. The one-hop path is the easiest in which to see changes. When the signal travels three or more hops, the changes get blurred between the hops. There is more absorption with the larger number of hops, but the effect of absorption per hop is not linearly additive. Each additional hop subtracts less energy from the signal.

Absorption is inversely proportional to frequency when the angle the signal wave makes with the ionospheric layer is constant, as in vertical ionospheric sounding. However, this frequency dependency is hard to assess because as the frequency changes so does the extent of layer penetration, thereby changing the incidence angle somewhat. As a rough estimate, 10 MHz signals tend to incur twice as much signal absorption as 20 MHz signals. However the largest absorption effect occurs between night and day; it is so great it tends to mask out the measurement of the secondary causes. The midlatitude communication link paths showed 10-30 dB of signal loss between night and day in most seasons, with paths near the equator surpassing even these. These different absorption effects add up to give an overall signal loss of 120 dB on the average.

What can DXers do to enhance their effectiveness during summertime operations? Review the chart on the next page for the highest band available to the DX area you wish to contact. Operate on towards evening, taking advantage of its lower absorption, but before the maximum usable frequency drops off very much. Then use the graph provided in the February, 1985, column that shows take-off angle (TOA) vs. ionosphere height. Use the height chart provided, too. The lowest TOA means fewer hops and less absorption of your signal. Make sure your antenna radiates substantial energy at that low TOA in order to give you the best chance of contacting the desired DX station.

Know the current conditions (in terms of signal absorption and variability,

QSB) by listening to radio station WWV on 5, 10, 15 MHz at 18 minutes after the hour. If the solar flux has just increased, absorption will be high. In addition, potential fading conditions (QSB) are associated with an A figure of greater than 15 or a K figure greater than 4. These indicate pronounced signal absorption on the higher latitude paths. These clues can help you be your own forecaster — therefore a better DX operator.

## last-minute forecast

During August noise will be up and signal strength down, however sporadic-E propagation will occur. This just means that we can expect good DX conditions on the higher frequency bands in the third and last weeks of the month while the lower bands are expected to be best the first week of the month. It's always helpful to check WWV broadcasts to confirm these conditions. For the VHF/UHF enthusiast the moon's perigee will occur on the 19th, with a full moon on the 30th. The Perseids meteor shower will occur from the 10th to 14th, with a maximum rate expected on the 11th and 12th, with better than fifty meteors per hour. This is an excellent shower. Meteor shower activity has already been reported as heavier than usual this year.

## band-by-band summary

*Six-meter* paths will open for a half hour to a couple of hours on some days around local noon. Sporadic-E propagation will make this short-skip path possible out to nearly 1200 miles (2000 km) per hop.

*Ten and fifteen meters* will have a few short-skip E<sub>s</sub> openings and some long-skip openings to southern areas of the world during daylight, though only during periods of high solar flux. Some transequatorial (TE) openings associated with mildly disturbed geomagnetic-ionospheric conditions may occur in the evening hours toward the end of the month.

*Twenty, thirty, and forty meters* will have DX from most areas of the world

**WESTERN USA**

GMT	PDT	Directional Indicators							
		N	NE	E	SE	S	SW	W	NW
0000	5:00	20	20	15	15	20	15	15*	20
0100	6:00	20	20	20	15	20	15	15	20
0200	7:00	20	20	20	15	20	15	15	20
0300	8:00	20	20	20	15	20	15	15	20
0400	9:00	20	20	20	20	20	15*	15	20
0500	10:00	20	20	20	20	30	15*	15	20
0600	11:00	20	30	20	20	30	15*	15	20
0700	12:00	20	30	20	20	30	15	15	20
0800	1:00	20	30	20	20	30	15	20	20
0900	2:00	30	30	30*	20	30	15	20	20
1000	3:00	30	30	20	30	30	20	20	30
1100	4:00	30	30	20	20	30	20	20	30
1200	5:00	30	20	20	20	30	20	20	30
1300	6:00	30	20	15	20	30	20	20	30
1400	7:00	30	20	15	20	20	20	20	30
1500	8:00	30	20	15	15	20	20	20	30
1600	9:00	30	20	15	15	20	30	20	30
1700	10:00	20	20	15	15	20	30	30	30
1800	11:00	20	20	15	15	20	30	30	30
1900	12:00	20	20	15	15	20	20	20	20
2000	1:00	20	20	15	15	20	15	20	20
2100	2:00	20	20	15	15	20	15	15	20
2200	3:00	20	20	15	15	20	15	15	20
2300	4:00	20	20	15	15	20	15*	20	20

**AUGUST**

**MID USA**

GMT	MDT	Directional Indicators							
		N	NE	E	SE	S	SW	W	NW
0000	6:00	20	20	20	15	20	15*	15	20
0100	7:00	15	20	20	15	20	15	15	20
0200	8:00	15	20	20	15	20	15	15	20
0300	9:00	20	20	20	20	20	15	15*	20
0400	10:00	20	20	20	20	20	15	15	20
0500	11:00	20	20	30	20	30	15	15	20
0600	12:00	30	30	30	20	30	20	15	20
0700	1:00	30	30	20	20	30	20	20	20
0800	2:00	30	30	30	20	30	20	20	30
0900	3:00	30	30	20	20	30	20	20	30
1000	4:00	30	30	20	20	30	20	20	30
1100	5:00	30	30	20	20	30	20	20	30
1200	6:00	30	20	15	20	30	20	20	30
1300	7:00	30	20	15	20	30	20	20	30
1400	8:00	20	20	15	20	20	20	20	30
1500	9:00	20	20	15	15	20	30	20	30
1600	10:00	20	20	15	15	20	20	20	30
1700	11:00	20	20	15	20	20	30	20	30
1800	12:00	20	20	15	20	20	30	20	20
1900	1:00	20	20	15	15	20	15	20	20
2000	2:00	20	20	15	15	20	15	20	20
2100	3:00	20	20	15	15	20	15	20	20
2200	4:00	20	20	15	15*	20	15	20	20
2300	5:00	20	20	15	15	20	15	20	20

**EASTERN USA**

GMT	EDT	Directional Indicators							
		N	NE	E	SE	S	SW	W	NW
0000	8:00	20	20	20	15	20	15*	15	20
0100	9:00	30	20	20	15	20	15	15	20
0200	10:00	30	20	20	20	20	15	15	20
0300	11:00	30	20	20	20	20	15	15	20
0400	12:00	30	20	30	20	30	20	15	20
0500	1:00	30	20	30	20	30	20	15	20
0600	2:00	30	30	20	20	30	20	15	30
0700	3:00	30	30	20	20	30	20	20	30
0800	4:00	30	30	20	20	30	20	20	30
0900	5:00	30	30	20	30	30	20	20	30
1000	6:00	20	30	15	30	30	20	20	30
1100	7:00	20	30	15	20	30	30	20	30
1200	8:00	20	30	15	20	30	20	20	30
1300	9:00	20	20	15	20	30	20	20	30
1400	10:00	20	20	15	15	20	20	20	30
1500	11:00	20	20	15	15	20	20	30	20
1600	12:00	20	20	15	15	20	15	30	20
1700	1:00	20	20	15	15	20	15	20	20
1800	2:00	20	20	15	15	20	15	20	20
1900	3:00	20	20	15	15	20	15	20	20
2000	4:00	20	20	15	15	20	15	20	20
2100	5:00	20	20	15	15	20	15	20	20
2200	6:00	20	20	15	15	20	15	20	20
2300	7:00	20	20	15	15	20	15	20	20

The italicized numbers signify the bands to try during the transition and early morning hours, while the standard type provides the MUF during "normal" hours.

\*Look at next higher band for possible openings.

ASTRON			
RS7A	45.00	RS35M	138.95
RS12A	62.75	VS35M	156.95
RS20A	79.95	RS50A	179.85
RS20M	96.45	RS50M	203.25
VS20M	114.95	VS50M	223.95
RS36A	123.75	RM50A	206.95

**FOR THE BEST DEAL IN TOWN**  
**CALL THE BEST NUMBER AROUND 1-800-HAM-7373**  
**SPECIALS: Astron Power Supply Sale (see prices at left); Yaesu FT-980 \$1,330, FT-757GX \$745.95; Kenwood TS-430S - Call!, TS-711A - CALL!**

MIRAGE			
A1015 6Mtr 150w Amp/Pa.		CALL	
B23A 2 Mtr HT Amp/Pa.		FOR	
B1016 2 Mtr 100w Amp/Pa.		OUR	
B3016 2Mtr 30 in / 160 out UPS (MIRAGE)		LOW	
C1012 1.3Mtr 120w Amp/Pa.		LOW	
D1010N 430-450MHz. 100w N's		QUOTE	

YAESU			
FT203R NEW 2Mtr HT		CALL	
FT-209HR		FOR	
FT708R 440MHz. HT		OUR	
FT77 Great Mobile Rig		FOR	
FT757GX HF XCVR - A Winner!		OUR	
FT960 CAT System Special		ROCK	
FT726R with 2Mtr. Module		QUOTE	
SU726 Sat. Duplex Module			
432/435 Module - 726R			
50 MHz Module - 726R			
HF726 10 - 12 - 15Mtr Module			

MUTEK LTD.			
Low Noise - High dynamic range front-end boards with: Low loss relay, RF Amp, DBM, 8-pole Xtal filter, and IF Amplifier.			
ICOM IC211/251 Board	135.95		
ICOM IC271A Board	149.95		
GLNA432E mast mount GaAsFet preamp and sequencer	269.95		
SLN1448 RF Switched Preamp, 100w max. input, NF 1dB Gain 15dB typ	74.95		
SLNA50a Same as above for 50MHz	74.95		
SBLA144e Mast-Mounted RF Switched preamp, 250w, max input NF 1dB	159.95		
GFBA144e Mast-Mounted GaAsFet preamp, 1 Kw PEP Max, Includes Lin. amplifier sequencer, interfaces to all rigs!	249.95		

KENPRO			
KR500 Elevation Rotor	169.95		
FM2033 2Mtr 25w FM	279.95		
FM6033/4033/7033	Call!		

SSB ELECTRONICS			
High Performance - Low Noise DBM converters for 30MHz, 144MHz, or 432MHz	109.95		
SSB1206-26/144 GaAsFet converter	149.95		
SSB144-28 10w Transverter Kit with Double Balanced Mixer on Tx/Rx	199.95		
SSB432/435-28 10w Transverter Kit with GaAsFet front-end, DBM's on Tx/Rx	Call!		
LT23a 1296 MHz 10w X-verter, NF 1.8dB	650.00		
GaAsFet front-end, Dual Channel	399.95		
MicroIne13 2.3GHz Linear X-verter	279.95		
LSM24 OSCAR MODE L up-converter	124.95		
DX144 GaAsFet Preamp NF .4dB	124.95		
DX432 GaAsFet Preamp NF .5dB	124.95		
DX1296 GaAsFet Preamp NF .8dB	124.95		
SSB MAST-MOUNTED GaAsFet Preamps:			
MV144S-01 NF .8dB 1Kw PEP Max	275.95		
MV432S-01 NF .7dB 1Kw PEP Max	275.95		

CUE DEE			
The Swedish Boomer "SALE"			
144-15AN 15el 144MHz Yagi w/N conn.	79.95		

**PARABOLIC - UHF UNITS - LABE**

1296/28 dual conversion xverter	385.00		
1296/1296 single tube amp (60w)	279.95		
1296/1296 dual tube amp (120w)	386.95		
1.2 meter dish kit	95.95		
Dish feeds 1296 or 2304	85.95		
2 way ant. combiners 144/432	51.95/49.95		
4 way ant. combiners 144/432	59.95/56.95		

TERMS: Prices do not include shipping except where indicated and are subject to change without notice. At our discretion some COD's may require a deposit. Returns are subject to a 15% restocking charge.  
 \*Continental USA only

HENRY RADIO			
2KD-Classical 2 Kw Amp.	965.00		
2002/2004A KW's	1250.00/1350.00		

**FLASH**  
**NOW UNDER NEW MANAGEMENT!**

Information & Pa. Residents  
**Call (717) 474-9399**

16 S. Mountain Blvd - Rt 309  
 Mountaintop, Pa. 18707

MC/VISA

**HOURS: Monday & Friday 9:00am - 8:00pm**  
**Tues. Wed. Thurs. Sat. - 9:00am - 5:00pm**

during the daytime and into the evening hours almost every day. Forty meters will join this daytime group toward the end of the month because of lower signal absorption (lower lowest usable frequency) during these sunspot minimum years. During unusually high 27-day solar flux days, 40 meters may not be usable; both 40 and 30 meters may not be usable at the predawn hours after the high flux day. The DX on these bands may be either long-skip to 2500 miles (4000 km) or short skip E<sub>s</sub> to 1250 miles (2000 km) per hop. The length of daylight will be decreasing noticeably at the end of the month.

Thirty, forty, eighty, and one-sixty are all good for nighttime DX, even though the background thunderstorm noise may be severe, especially on 80 and 160 meters. Propagation of signals via sporadic-E layer may occur and assist around sunset. This will be the final month of the E<sub>s</sub> season.

ham radio

**MULTI-BAND SLOPERS**  
 ALSO: DIPOLES & LIMITED-SPACE ANTENNAS

Outstanding performance of W8JHN antennas is well known. Now enjoy multi-band BIG-SIGNAL, reports! Automatic bandswitching - Very low SWR - Coax feed - 3kw power - Compact - FULLY ASSEMBLED to your specified center frequency each band - EASY TO TEST! - Very low profile - Complete instructions - Your personal check accepted

4-BAND SLOPER - 160, 80, 40, 30, or 20M	60 ft. long	\$ 48 ppd
3 .. .. 160, 80, 40M	60 ft. ..	\$ 43 ..
2 .. .. 80, 40M	40 ft. ..	\$ 35 ..
3 .. .. NO-TRAP DIPOLE - 160, 80, 40M	113 ft. long	\$ 71 ..
2 .. .. 80, 40M	85 ft. ..	\$ 55 ..

9-BAND SPACE-SAVER DIPOLE - 160 thru 10M\* \$ 81.11 long \$ 85 ppd  
 \* Requires wide-range tuner (80, 40, 20, 15M without tuner)

SEND SASE for complete details of these and other unique antennas

W8JHN ANTENNAS 312-394-3414  
 BOX 393-H MT. PROSPECT, IL 60056

Custom Mailing Lists on Labels!  
**Amateur Radio Operator NAMES**  
 Custom lists compiled to your specifications

- Geographic by ZIP and/or State
- By License Issue or Expiration Date

Self stick 1x3 labels

**Total List 453,000 Price: \$25/Thousand**

**Buckmaster Publishing** ✓ 165  
 Whitehall  
 Mineral, VA 23117 U.S.A. (703) 894-5777

**WARNING**  
**SAVE YOUR LIFE OR AN INJURY**

Base plates, flat roof mounts, hinged bases, hinged sections, etc., are not intended to support the weight of a single man. Accidents have occurred because individuals assume situations are safe when they are not.

Installation and dismantling of towers is dangerous and temporary guys of sufficient strength and size should be used at all times when individuals are climbing towers during all types of installations or dismantlings. Temporary guys should be used on the first 10' or tower during erection or dismantling. Dismantling can even be more dangerous since the condition of the tower, guys, anchors, and/or roof is unknown.

The dismantling of some towers should be done with the use of a crane in order to minimize the possibility of member, guy wire, anchor, or base failures. Used towers in many cases are not as inexpensive as you may think if you are injured or killed.

Get professional, experienced help and read your Rohn catalog or other tower manufacturers' catalogs before erecting or dismantling any tower. A consultation with your local, professional tower erector would be very inexpensive insurance.

**Paid for By the Following:**  
**ROHN**  
 P.O. Box 2000  
 Peoria, IL 61656

**Bind 'em and Find 'em**

Keep those valuable issues of Ham Radio like new. Prevent smears, tears and dog ears. Bind 'em together and enjoy for years to come. You'll be happy you did!

**HAM RADIO BINDERS**

Beautiful buckram bound, rich brown material with gold embossing. These binders will really dress up your collection of Ham Radio. Year stickers included.

HR-BDL **\$6.95 ea.**  
**3 for \$17.95**

Please add \$2.50 for shipping and handling, U.S. only.

**HAM RADIO'S BOOKSTORE**  
 GREENVILLE, NH 03048



HF Equipment	Regular	SALE
IC-735 Xcvr/SW rcvr/mic	849.00	749 <sup>95</sup>
PS-55 Power supply	160.00	144 <sup>95</sup>
AT-120 Automatic antenna tuner	TBA	
FL-32 500 Hz CW filter	59.50	
EX-243 Electronic keyer unit	50.00	
IC-730 8-band 200w PEP xcvr w/mic	829.00	569 <sup>95</sup>
FL-30 SSB filter (passband tuning)	59.50	
FL-44A SSB filter (2nd IF)	159.00	144 <sup>95</sup>
FL-45 500 Hz CW filter	59.50	
EX-195 Marker unit	39.00	
EX-202 LDA interface; 730/2KL/AH-1	27.50	
EX-203 150 Hz CW audio filter	39.00	
EX-205 Transverter switching unit	29.00	
SM-5 8-pin electret desk microphone	39.00	
HM-10 Scanning mobile microphone	39.50	
MB-5 Mobile mount	19.50	
IC-720A 9-band xcvr/1-30 MHz rcvr	1349.00	799 <sup>95</sup>
FL-32 500 Hz CW filter	59.50	
FL-34 5.2 kHz AM filter	49.50	
SM-5 8-pin electret desk microphone	39.00	
MB-5 Mobile mount	19.50	
IC-745 9-band xcvr w/1-30 MHz rcvr	999.00	779 <sup>95</sup>
PS-35 Internal power supply	160.00	144 <sup>95</sup>
EX-241 Marker unit	20.00	
EX-242 FM unit	39.00	
EX-243 Electronic keyer unit	50.00	
FL-45 500 Hz CW filter (1st IF)	59.50	
FL-54 270 Hz CW filter (1st IF)	47.50	
FL-52A 500 Hz CW filter (2nd IF)	96.50	89 <sup>95</sup>
FL-53A 250 Hz CW filter (2nd IF)	96.50	89 <sup>95</sup>
FL-44A SSB filter (2nd IF)	159.00	144 <sup>95</sup>
HM-10 Scanning mobile microphone	39.50	
SM-6 Desk microphone	39.00	
HM-12 Extra hand microphone	39.50	
MB-12 Mobile mount	19.50	



IC-751 9-band xcvr/1-30 MHz rcvr	1399.00	1199
PS-35 Internal power supply	160.00	144 <sup>95</sup>
FL-32 500 Hz CW filter (1st IF)	59.50	
FL-63 250 Hz CW filter (1st IF)	48.50	
FL-52A 500 Hz CW filter (2nd IF)	96.50	89 <sup>95</sup>
FL-53A 250 Hz CW filter (2nd IF)	96.50	89 <sup>95</sup>
FL-33 AM filter	31.50	
FL-70 2.8 KHz wide SSB filter	46.50	
HM-12 Extra hand microphone	39.50	
SM-6 Desk microphone	39.00	
CR-64 High stability reference xtal	56.00	
RC-10 External frequency controller	35.00	
MB-18 Mobile mount	19.50	
Options: 720/730/745/751	Regular	SALE
PS-15 20A external power supply	149.00	134 <sup>95</sup>
EX-144 Adaptor for CF-1/PS-15	6.50	



# ICOM

Options - continued	Regular	SALE
CF-1 Cooling fan for PS-15	45.00	
EX-310 Voice synth for 751, R-71A	39.95	
SP-3 External base station speaker	49.50	
Speaker/Phone patch - specify radio	139.00	129 <sup>95</sup>
BC-10A Memory back-up	8.50	
EX-2 Relay box with marker	34.00	
AT-100 100w 8-band automatic ant tuner	349.00	314 <sup>95</sup>
AT-500 500w 9-band automatic ant tuner	449.00	399 <sup>95</sup>
AH-1 5-band mobile antenna w/tuner	289.00	259 <sup>95</sup>
PS-30 Systems p/s w/cord, 6-pin plug	259.95	234 <sup>95</sup>
OPC Optional cord, specify 2 or 4-pin	5.50	
GC-4 World clock (Closeout!)	99.95	79 <sup>95</sup>

HF linear amplifier	Regular	SALE
IC-2KL w/ps 160-15w solid state amp	1795.00	1299
VHF/UHF base multi-modes	Regular	SALE
IC-551D 80 Watt 6m transceiver	699.00	599 <sup>95</sup>
EX-106 FM option	125.00	112 <sup>95</sup>
BC-10A Memory back-up	8.50	
SM-2 Electret desk microphone	39.00	
IC-271A 25w 2m FM/SSB/CW xcvr	699.00	569 <sup>95</sup>
AG-20 Internal preamplifier*	56.95	
IC-271H 100w 2m FM/SSB/CW xcvr	899.00	759 <sup>95</sup>
AG-25 Mast mounted preamplifier*	84.95	
IC-471A 25w 430-450 SSB/CW/FM xcvr	799.00	699 <sup>95</sup>
AG-1 Mast mounted preamplifier*	89.00	
IC-471H 75w 430-450 SSB/CW/FM xcvr	1099.00	969 <sup>95</sup>
AG-35 Mast mounted preamplifier*	84.95	

**For a Limited time!**  
 With the purchase of IC-271A/H or IC-471A/H get the matching Preamp\* for just \$1.00 extra.

Common accessories for 271A/H and 471A/H	Regular	SALE
PS-25 Internal power supply for (A)	99.00	89 <sup>95</sup>
PS-35 Internal power supply for (H)	160.00	144 <sup>95</sup>
PS-15 External power supply	149.00	134 <sup>95</sup>
CF-1 Cooling fan for PS-15	45.00	
EX-144 Adaptor for PS-15/CF-1	6.50	
SM-6 Desk microphone	39.00	
EX-310 Voice synthesizer	39.95	
TS-32 CommSpec encode/decoder	59.95	
UT-15 Encoder/decoder interface	12.50	
UT-15S UT-15S w/TS-32 installed	79.95	

VHF/UHF mobile multi-modes	Regular	SALE
IC-290H 25w 2m SSB/FM xcvr, TTP mic	549.00	479 <sup>95</sup>
IC-490A 10w 430-440 SSB/FM/CW xcvr	649.00	579 <sup>95</sup>
VHF/UHF/1.2 GHz FM	Regular	SALE
IC-27A Compact 25w 2m FM w/TTP mic	369.00	319 <sup>95</sup>
IC-27H Compact 45w 2m FM w/TTP mic	409.00	359 <sup>95</sup>
IC-37A Compact 25w 220 FM, TTP mic	449.00	299 <sup>95</sup>
IC-47A Compact 25w 440 FM, TTP mic	469.00	419 <sup>95</sup>
UT-16/EX-388 Voice synthesizer	29.95	
IC-3200A 25w 2m/440 FM w/TTP	549.00	489 <sup>95</sup>
UT-23 Voice synthesizer	29.95	
IC-120 1w 1.2 GHz FM transceiver	499.00	449 <sup>95</sup>
ML-12 10w amplifier	339.00	299 <sup>95</sup>

6m portable	Regular	SALE
IC-505 3/10w 6m port. SSB/CW xcvr	449.00	399 <sup>95</sup>
BP-10 Internal Nicad battery pack	79.50	
BP-15 AC charger	12.50	
EX-248 FM unit	49.50	
LC-10 Leather case	34.95	
SP-4 Remote speaker	24.95	



Hand-held Transceivers	Regular	SALE
Deluxe models	Regular	SALE
IC-02AT for 2m	349.00	289 <sup>95</sup>
IC-04AT for 440 MHz	379.00	289 <sup>95</sup>
Standard models	Regular	SALE
IC-2A for 2m	239.50	189 <sup>95</sup>
IC-2AT with TTP	269.50	199 <sup>95</sup>
IC-3AT 220 MHz, TTP	299.95	239 <sup>95</sup>
IC-4AT 440 MHz, TTP	299.95	239 <sup>95</sup>

Accessories for Deluxe models	Regular	SALE
BP-7 425mah/13.2V Nicad Pak - use BC-35	67.50	
BP-8 800mah/8.4V Nicad Pak - use BC-35	62.50	
BC-35 Drop in desk charger for all batteries	69.00	
BC-60 6-position gang charger, all batts	359.95	SALE
BC-16U Wall charger for BP7/BP8	10.00	
LC-11 Vinyl case	17.95	
LC-14 Vinyl case for Dlx using BP-7/8	17.95	
LC-02AT Leather case for Dlx models w/BP-7/8	39.95	

Accessories for both models	Regular	SALE
BP-2 425mah/7.2V Nicad Pak - use BC35	39.50	
BP-3 Extra Std. 250 mah/8.4V Nicad Pak	29.50	
BP-4 Alkaline battery case	12.50	
BP-5 425mah/10.8V Nicad Pak - use BC35	49.50	
CA-2 Telescoping 2m antenna	10.00	
CA-5 5/8-wave telescoping 2m antenna	18.95	
FA-2 Extra 2m flexible antenna	10.00	
CP-1 Cig. lighter plug/cord for BP3 or Dlx	9.50	
DC-1 DC operation pak for standard models	17.50	
LC-2AT Leather case for standard models	34.95	
RB-1 Vinyl waterproof radio bag	30.00	
HH-SS Handheld shoulder strap	14.95	
HM-9 Speaker microphone	34.50	
HS10 Boom microphone/headset	19.50	
HS-10SA Vox unit for HS-10 & Deluxe only	19.50	
HS-10SB PTT unit for HS-10	19.50	
ML-1 2m 2.3w in/10w out amplifier	79.95	SALE
SS-32M CommSpec 32-tone encoder	29.95	

Shortwave receiver	Regular	SALE
R-71A 100 kHz-30 Mhz digital receiver	\$799.00	659 <sup>95</sup>
RC-11 Wireless remote controller	59.95	49 <sup>95</sup>
FL-32 500 Hz CW filter	59.50	
FL-63 250 Hz CW filter (1st IF)	48.50	
FL-44A SSB filter (2nd IF)	159.00	144 <sup>95</sup>
EX-257 FM unit	38.00	
EX-310 Voice synthesizer	39.95	
CR-64 High stability oscillator xtal	56.00	
SP-3 External speaker	49.50	
CK-70 (EX-299) 12V DC option	9.95	
MB-12 Mobile mount	19.50	



**Order Toll Free - Use your Credit Card!**

**HOURS** • Mon. thru Fri. 9-5:30; Sat. 9-3  
 Milwaukee WATS line: 1-800-558-0411 answered evenings until 8:00 pm Monday thru Thursday.  
**Please use WATS lines for Ordering**  
 use Regular lines for other Info and Service dept.

**Order Toll Free: 1-800-558-0411** In Wisconsin (outside Milwaukee Metro Area) 1-800-242-5195

# AMATEUR ELECTRONIC SUPPLY<sup>®</sup> Inc.

4828 W. Fond du Lac Avenue; Milwaukee, WI 53216 - Phone (414) 442-4200

## AES BRANCH STORES

<b>WICKLIFFE, Ohio</b> 44092 28940 Euclid Avenue Phone (216) 585-7388 Ohio WATS 1-800-362-0290 Outside Ohio 1-800-321-3594	<b>ORLANDO, Fla.</b> 32803 621 Commonwealth Ave. Phone (305) 894-3238 Fla. WATS 1-800-432-9424 Outside Florida 1-800-327-1917	<b>CLEARWATER, Fla.</b> 33575 1898 Drew Street Phone (813) 461-4267 No In-State WATS No Nationwide WATS	<b>LAS VEGAS, Nev.</b> 89106 1072 N. Rancho Drive Phone (702) 647-3114 No In-State WATS Outside Nevada 1-800-634-6227	<b>Associate Store</b> <b>CHICAGO, Illinois</b> 60630 ERICKSON COMMUNICATIONS 5456 N. Milwaukee Avenue Phone (312) 631-5181 Outside Illinois 1-800-621-5802
--	---	---	---	--

# TUBES

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
2C39/7289	\$ 34.00	1182/4600A	\$500.00	ML7815AL	\$ 60.00
2E26	7.95	4600A	500.00	7843	107.00
2K28	200.00	4624	310.00	7854	130.00
3-500Z	102.00	4657	84.00	ML7855KAL	125.00
3-1000Z/8164	400.00	4662	100.00	7984	14.95
3B28/866A	9.50	4665	500.00	8072	84.00
3CX400U7/8961	255.00	4687	P.O.R.	8106	5.00
3CX1000A7/8283	526.00	5675	42.00	8117A	225.00
3CX3000F1/8239	567.00	5721	250.00	8121	110.00
3CW30000H7	1700.00	5768	125.00	8122	110.00
3X2500A3	473.00	5819	119.00	8134	470.00
3X3000F1	567.00	5836	232.50	8156	12.00
4-65A/8165	69.00	5837	232.50	8233	60.00
4-125A/4D21	79.00	5861	140.00	8236	35.00
4-250A/5D22	98.00	5867A	185.00	8295/PL172	500.00
4-400A/8438	98.00	5868/AX9902	270.00	8458	35.00
4-400B/7527	110.00	5876/A	42.00	8462	130.00
4-400C/6775	110.00	5881/6L6	8.00	8505A	95.00
4-1000A/8166	444.00	5893	60.00	8533W	136.00
4CX250B/7203	54.00	5894/A	54.00	8560/A	75.00
4CX250FG/8621	75.00	5894B/8737	54.00	8560AS	100.00
4CX250K/8245	125.00	5946	395.00	8608	38.00
4CX250R/7580W	90.00	6083/AZ9909	95.00	8624	100.00
4CX300A/8167	170.00	6146/6146A	8.50	8637	70.00
4CX350A/8321	110.00	6146B/8298	10.50	8643	83.00
4CX350F/8322	115.00	6146W/7212	17.95	8647	168.00
4CX350FJ/8904	140.00	6156	110.00	8683	95.00
4CX600J/8809	835.00	6159	13.85	8877	465.00
4CX1000A/8168	242.50*	6159B	23.50	8908	13.00
4CX1000A/8168	485.00	6161	325.00	8950	13.00
4CX1500B/8660	555.00	6280	42.50	8930	137.00
4CX5000A/8170	1100.00	6291	180.00	6L6 Metal	25.00
4CX10000D/8171	1255.00	6293	24.00	6L6GC	5.03
4CX15000A/8281	1500.00	6326	P.O.R.	6CA7/EL34	5.38
4CW800F	710.00	6360/A	5.75	6CL6	3.50
4D32	240.00	6399	540.00	6DJ8	2.50
4E27A/5-125B	240.00	6550A	10.00	6DQ5	6.58
4PR60A	200.00	6883B/8032A/8552	10.00	6GF5	5.85
4PR60B	345.00	6897	160.00	6GJ5A	6.20
4PR65A/8187	175.00	6907	79.00	6GK6	6.00
4PR1000A/8189	590.00	6922/6DJ8	5.00	6HB5	6.00
4X150A/7034	60.00	6939	22.00	6HF5	8.73
4X150D/7609	95.00	7094	250.00	6JG6A	6.28
4X250B	45.00	7117	38.50	6JM6	6.00
4X250F	45.00	7203	P.O.R.	6JN6	6.00
4X500A	412.00	7211	100.00	6JS6C	7.25
5CX1500A	660.00	7213	300.00*	6KN6	5.05
KT88	27.50	7214	300.00*	6KD6	8.25
416B	45.00	7271	135.00	6LF6	7.00
416C	62.50	7289/2C39	34.00	6LQ6 G.E.	7.00
572B/T160L	49.95	7325	P.O.R.	6LQ6/6MJ6 Sylvania	9.00
592/3-200A3	211.00	7360	13.50	6ME6	8.90
807	8.50	7377	85.00	12AT7	3.50
811A	15.00	7408	2.50	12AX7	3.00
812A	29.00	7609	95.00	12BY7	5.00
813	50.00	7735	36.00	12JB6A	6.50

NOTE \* = USED TUBE

NOTE P.O.R. = PRICE ON REQUEST

"ALL PARTS MAY BE NEW, USED, OR SURPLUS. PARTS MAY BE SUBSTITUTED WITH COMPARABLE PARTS IF WE ARE OUT OF STOCK OF AN ITEM.

NOTICE: ALL PRICES ARE SUBJECT TO CHANGE WITHOUT NOTICE.

For information call: 602-265-0731

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

## MHz electronics

3802 North 27th Ave., Phoenix, AZ 85017

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

# "FILTERS"

## COLLINS Mechanical Filter #526-9724-010 MODEL F455Z32F

455KHZ at 3.2KHz wide. May be other models but equivalent. May be used or new, \$15.99

## ATLAS Crystal Filters

- 5.595-2.7/8/LSB, 5.595-2.7/LSB  
8 pole 2.7KHz wide Upper sideband. Impedance 800ohms 15pf In/800ohms 0pf out. 19.99
- 5.595-2.7/8/U, 5.595-2.7/USB  
8 pole 2.7KHz wide Upper sideband. Impedance 800ohms 15pf In/800ohms 0pf out. 19.99
- 5.595-.500/4, 5.595-.500/4/CW  
4 pole 500 cycles wide CW. Impedance 800ohms 15pf In/800ohms 0pf out. 19.99
- 9.0USB/CW  
6 pole 2.7KHz wide at 6dB. Impedance 680ohms 7pf In/300ohms 8pf out. CW-1599Hz 19.99

## KOKUSAI ELECTRIC CO. Mechanical Filter #MF-455-ZL/ZU-21H

455KHz at Center Frequency of 453.5KC. Carrier Frequency of 455KHz 2.36KC Bandwidth.  
Upper sideband. (ZU) 19.99  
Lower sideband. (ZL) 19.99

\*\*\*\*\*

## CRYSTAL FILTERS

NIKKO	FX-07800C	7.8MHz	\$10.00
TEW	FEC-103-2	10.6935MHZ	10.00
SDK	SCH-113A	11.2735MHZ	10.00
TAMA	TF-31H250	CF 3179.3KHz	19.99
TYCO/CD	001019880	10.7MHz 2pole 15KHz bandwidth	5.00
MOTOROLA	4884863B01	11.7MHz 2pole 15KHz bandwidth	5.00
PTI	5350C	12MHz 2pole 15KHz bandwidth	5.00
PTI	5426C	21.4MHz 2pole 15KHz bandwidth	5.00
PTI	1479	10.7MHz 8pole bandwidth 7.5KHz at 3dB, 5KHz at 6dB	20.00
COMTECH	A10300	45MHz 2pole 15KHz bandwidth	6.00
FRC	ERXF-15700	20.6MHz 36KHz wide	10.00
FILTECH	2131	CF 7.825MHz	10.00

\*\*\*\*\*

## CERAMIC FILTERS

AXEL	4F449	12.6KC Bandpass Filter 3dB bandwidth 1.6KHz from 11.8-13.4KHz	10.00
CLEVITE	TO-01A	455KHz+-2KHz bandwidth 4-7% at 3dB	5.00
	TCF4-12D36A	455KHz+-1KHz bandwidth 6dB min 12KHz, 60dB max 36KHz	10.00
MURATA	BFB455B	455KHz	2.50
	BFB455L	455KHz	3.50
	CFM455E	455KHz +-5.5KHz at 3dB, +-8KHz at 6dB, +-16KHz at 50dB	6.65
	CFM455D	455KHz +-7KHz at 3dB, +-10KHz at 6dB, +-20KHz at 50dB	6.65
	CFR455E	455KHz +-5.5KHz at 3dB, +-8KHz at 6dB, +-16KHz at 60dB	8.00
	CFU455B	455KHz +-2KHz bandwidth +-15KHz at 6dB, +-30KHz at 40dB	2.90
	CFU455C	455KHz +-2KHz bandwidth +-12.5KHz at 6dB, +-24KHz at 40dB	2.90
	CFU455G	455KHz +-1KHz bandwidth +-4.5KHz at 6dB, +-10KHz at 40dB	2.90
	CFU455H	455KHz +-1KHz bandwidth +-3KHz at 6dB, +-9KHz at 40dB	2.90
	CFU455I	455KHz +-1KHz bandwidth +-2KHz at 6dB, +-6KHz at 40dB	2.90
	CFW455D	455KHz +-10KHz at 6dB, +-20KHz at 40dB	2.90
	CFW455H	455KHz +-3KHz at 6dB, +-9KHz at 40dB	2.90
	SFB455D	455KHz	2.50
	SFD455D	455KHz +-2KHz, 3dB bandwidth 4.5KHz +-1KHz	5.00
	SFE10.7MA	10.7MHz 280KHz +-50KHz at 3dB, 650KHz at 20dB	2.50
	SFE10.7MS	10,7MHz 230KHz +-50KHz at 3dB, 570KHz at 20dB	2.50
	SFG10.7MA	10.7MHz	10.00
NIPPON	LF-B4/CFU455I	455KHz +-1KHz	2.90
	LF-B6/CFU455H	455KHz +-1KHz	2.90
	LF-B8	455KHz	2.90
	LF-C18	455KHz	10.00
TOKIN	CF455A/BFU455K	455KHz +-2KHz	5.00
MATSUSHIRA	EFC-L455K	455KHz	7.00

\*\*\*\*\*

## SPECTRA PHYSICS INC. Model 088 HeNe LASER TUBES

POWER OUTPUT 1.6MW. BEAM DIA. .75MM BEAM DIR. 2.7MR SKV STARTING VOLTAGE DC  
68K OHM IWATT BALLAST 1000VDC +-100VDC At 3.7MA \$59.99

## ROTRON MUFFIN FANS Model MARK4/MU2A1

115 VAC 14WATTS 50/60CPS IMPEDENCE PROTECTED-F 88CFM at 50CPS \$ 7.99  
105CFM at 60CPS THESE ARE NEW

# MHz electronics

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

3802 North 27th Ave., Phoenix, AZ 85017

PRICES SUBJECT TO CHANGE WITHOUT NOTICE For information call: 602-265-0731

# RF TRANSISTORS

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
2N1561	\$25.00	2N5920	\$ 70.00	40608 RCA	\$ 2.48	BFY90	\$ 1.50
2N1562	25.00	2N5921	80.00	40673 RCA	2.50	BLW60C5	15.00
2N1692	25.00	2N5922	10.00	40894 RCA	1.00	BLX67	12.25
2N2857	1.55	2N5923	25.00	60247 RCA	25.00	BLX67C3	12.25
2N2857JAN	4.10	2N5941	23.00	61206 RCA	100.00	BLX93C3	22.21
2N2857JANTX	4.50	2N5942	40.00	62800A RCA	60.00	BLY87A	7.50
2N2876	13.50	2N5944	10.35	62803 RCA	100.00	BLY88C3	13.08
2N2947	18.35	2N5945	10.00	430414/3990RCA	50.00	BLY89C	13.00
2N2948	13.00	2N5946	12.00	3457159 RCA	20.00	BLY90	45.00
2N2949	15.50	2N5947	9.20	3729685-2 RCA	75.00	BLY92	13.30
2N3118	5.00	2N6080	6.00	3729701-2 RCA	50.00	BLY94C	45.00
2N3119	4.00	2N6081	7.00	3753883 RCA	50.00	BLY351	10.00
2N3134	1.15	2N6082	9.00	615467-902	25.00	BLY568C/CF	30.00
2N3287	4.90	2N6083	9.50	615467-903	40.00	C2M70-28R	92.70
2N3288	4.40	2N6084	12.00	2SC568	2.50	C25-28	57.00
2N3309	4.85	2N6094	11.00	2SC703	36.00	C4005	2.50
2N3375	17.10	2N6095	12.00	2SC756A	7.50	CD1659	20.00
2N3478	2.13	2N6096	16.10	2SC781	2.80	CD1899	20.00
2N3553	1.55	2N6097	20.70	2SC1018	1.00	CD1920	10.00
2N3553JAN	2.90	2N6105	21.00	2SC1042	24.00	CD2188	18.00
2N3632	15.50	2N6136	21.85	2SC1070	2.50	CD2545	24.00
2N3733	11.00	2N6166	40.24	2SC1216	2.50	CD2664A	16.00
2N3818	5.00	2N6267	142.00	2SC1239	2.50	CD3167	92.70
2N3866	1.30	2N6304	1.50	2SC1251	24.00	CD3353	95.00
2N3866JAN	2.20	2N6368	30.00	2SC1306	2.90	CD3435	26.30
2N3866JANTX	3.80	2N6439	55.31	2SC1307	5.50	CD3900	152.95
2N3866JANTXV	4.70	2N6459	18.00	2SC1424	2.80	CM25-12	20.00
2N3866AJANTXV	5.30	2N6567	10.06	2SC1600	5.00	CM40-12	27.90
2N3924	3.35	2N6603	13.50	2SC1678	2.00	CM40-28	56.90
2N3926	16.10	2N6604	13.50	2SC1729	32.40	CME50-12	30.00
2N3927	17.25	2N6679	44.00	2SC1760	1.50	CTC2001	42.00
2N3948	1.75	2N6680	80.00	2SC1909	4.00	CTC2005	55.00
2N3950	25.00	021-1	15.00	2SC1945	10.00	CTC3005	70.00
2N3959	3.85	01-80703T4	65.00	2SC1946	40.00	CTC3460	20.00
2N4012	11.00	35C05	15.00	2SC1947	10.00	DV2820S	25.00
2N4037	2.00	102-1	28.00	2SC1970	2.50	DXL1003P70	22.00
2N4041	14.00	103-1	28.00	2SC1974	4.00	DXL2001P70	19.00
2N4072	1.80	103-2	28.00	2SC2166	5.50	DXL2002P70	14.00
2N4080	4.53	104P1	18.00	2SC2237	32.00	DXL3501AP100F	47.00
2N4127	21.00	163P1	10.00	2SC2695	47.00	EFJ4015	12.00
2N4416	2.25	181-3	15.00	A2X1698	POR	EFJ4017	24.00
2N4427	1.25	210-2	10.00	A3-12	14.45	EFJ4021	24.00
2N4428	1.85	269-1	18.00	A50-12	24.00	EFJ4026	35.00
2N4430	11.80	281-1	15.00	A209	10.00	EN15745	20.00
2N4927	3.90	282-1	30.00	A283	6.00	FJ9540	16.00
2N4957	3.45	482	7.50	A283B	6.00	FSX52WF	58.00
2N4959	2.30	564-1	25.00	A1610	19.00	G65739	25.00
2N5016	18.40	698-3	15.00	AF102	2.50	G65386	25.00
2N5026	15.00	703-1	15.00	AFY12	2.50	GM0290A	2.50
2N5070	18.40	704	4.00	AR7115	20.00	HEP76	4.95
2N5090	13.80	709-2	11.00	AT41435-5	6.35	HEPS3002	11.40
2N5108	3.45	711	4.00	B2-8Z	10.70	HEPS3003	30.00
2N5109	1.70	733-2	15.00	B3-12	10.85	HEPS3005	10.00
2N5160	3.45	798-2	25.00	B12-12	15.70	HEPS3006	19.90
2N5177	21.62	3421	28.00	BALO204125	152.95	HEPS3007	25.00
2N5179	1.04	3683P1	15.00	BF25-35	56.25	HEPS3010	11.34
2N5216	56.00	3992	25.00	B40-12	19.25	HF8003	10.00
2N5470	75.00	4164P1	15.00	B70-12	55.00	HFET2204	112.00
2N5583	3.45	4243P1	28.00	BF272A	2.50	HP35821	38.00
2N5589	9.77	4340P3	18.00	BFQ85	2.50	HP35826B	32.00
2N5590	10.92	4387P1	27.50	BFR21	2.50	HP35826E	32.00
2N5591	13.80	7104-1	28.00	BFR90	1.00	HP35831E	30.00
2N5596	99.00	7249-2	10.50	BFR91	1.65	HP35832E	50.00
2N5636	12.00	7283-1	37.50	BFR99	2.50	HP35833E	50.00
2N5637	15.50	7536-1	30.00	BFT12	2.50	HP35859E	75.00
2N5641	12.42	7794-1	10.50	BFW16A	2.50	HP35866E	44.00
2N5642	14.03	7795	15.00	BFW17	2.50	HXTR2101	44.00
2N5643	25.50	7795-1	15.00	BFW92	1.50	HXTR3101	7.00
2N5645	13.80	7796-1	24.00	BFX44	2.50	HXTR5101	31.00
2N5646	20.70	7797-1	36.00	BFX48	2.50	HXTR6104	68.00
2N5651	11.05	40081 RCA	5.00	BFX65	2.50	HXTR6105	31.00
2N5691	18.00	40279 RCA	10.00	BFX84	2.50	HXTR6106	33.00
2N5764	27.00	40280 RCA	4.62	BFX85	2.50	J31G	1.00
2N5836	3.45	40281 RCA	10.00	BFX86	2.50	JO2000	10.00
2N5842	8.45	40282 RCA	20.00	BFX89	1.00	JO2001	25.00
2N5847	19.90	40290 RCA	2.80	BFY11	2.50	JO4045	24.00
2N5849	20.00	40292 RCA	13.05	BFY18	2.50	KD5522	25.00
2N5913	3.25	40294 RCA	2.50	BFY19	2.50	KJ5522	25.00
2N5916	36.00	40341 RCA	21.00	BFY39	2.50	M1106	13.75

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

For information call: 602-265-0731

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

**MHz electronics**

3802 North 27th Ave., Phoenix, AZ 85017

## RF TRANSISTORS (CONTINUED)

M1107	\$16.75	MRF458	\$20.70	NEO2160ER	\$100.00	SD1009	\$15.00
M1131	5.15	MRF464	25.30	NEO21350	5.30	SD1009-2	15.00
M1132	7.25	MRF466	18.97	NE13783	61.00	SD1012	10.00
M1134	13.40	MRF472	1.50	NE21889	43.00	SD1012-3	10.00
M9116	29.10	MRF475	3.10	NE57835	5.70	SD1012-5	10.00
M9579	6.00	MRF476	3.16	NE64360ER-A	100.00	SD1013	10.00
M9580	7.95	MRF477	20.00	NE64480 (B)	94.00	SD1013-3	10.00
M9587	7.00	MRF479	8.05	NE73436	2.50	SD1013-7	10.00
M9588	5.20	MRF492	23.00	NE77362ER	100.00	SD1016	15.00
M9622	5.95	MRF502	1.04	NE98260ER	100.00	SD1016-5	15.00
M9623	7.95	MRF503	6.00	PRT8637	25.00	SD1018-4	13.00
M9624	9.95	MRF504	7.00	PT3127A	5.00	SD1018-6	13.00
M9625	15.95	MRF509	5.00	PT3127B	5.00	SD1018-7	13.00
M9630	14.00	MRF511	10.69	PT3127C	20.00	SD1018-15	13.00
M9740	27.90	MRF515	2.00	PT3127D	20.00	SD1020-5	10.00
M9741	27.90	MRF517	2.00	PT3127E	20.00	SD1028	15.00
M9755	16.00	MRF525	3.45	PT3190	20.00	SD1030	12.00
M9780	5.50	MRF559	1.76	PT3194	20.00	SD1030-2	12.00
M9827	11.00	MRF587	11.00	PT3195	20.00	SD1040	5.00
M9848	35.00	MRF605	20.00	PT3537	7.80	SD1040-2	20.00
M9850	13.50	MRF618	25.00	PT4166E	20.00	SD1040-4	10.00
M9851	20.00	MRF626	12.00	PT4176D	25.00	SD1040-6	5.00
M9860	8.25	MRF628	8.65	PT4186B	5.00	SD1043	12.00
M9887	2.80	MRF629	3.45	PT4209	25.00	SD1043-1	10.00
M9908	6.95	MRF641	25.30	PT4209C/5645	25.00	SD1045	3.75
M9965	12.00	MRF644	27.60	PT4556	24.60	SD1049-1	2.00
MM1500	25.00	MRF646	29.90	PT4570	7.50	SD1053	4.00
MM1550	10.00	MRF648	33.35	PT4577	20.00	SD1057	10.00
MM1552	50.00	MRF816	15.00	PT4590	5.00	SD1065	4.75
MM1553	50.00	MRF823	20.00	PT4612	20.00	SD1068	15.00
MM1607	8.45	MRF846	44.85	PT4628	20.00	SD1074-2	18.00
MM1614	10.00	MRF892	35.50	PT4640	20.00	SD1074-4	28.00
MM1810	15.00	MRF894	46.00	PT4642	20.00	SD1074-5	28.00
MM1810	15.00	MRF901 3 Lead	1.00	PT5632	4.70	SD1076	18.50
MM1943	1.80	MRF901 4 Lead	2.00	PT5749	25.00	SD1077	4.00
MM2608	5.00	MRF902/2N6603JAN	15.00	PT6612	25.00	SD1077-4	4.00
MM3375A	17.10	MRF902B	18.40	PT6619	20.00	SD1077-6	4.00
MM4429	10.00	MRF904	2.30	PT6708	25.00	SD1078-6	24.00
MM8000	1.15	MRF905	2.55	PT6709	25.00	SD1080-7	7.50
MM8006	2.30	MRF911	2.50	PT6720	25.00	SD1080-8	6.00
MM8011	25.00	MRF965	2.55	PT8510	15.00	SD1080-9	3.00
MPSU31	1.01	MRF966	3.55	PT8524	25.00	SD1084	8.00
MRA2023-1.5	42.50	MRF1000MA	32.77	PT8609	25.00	SD1087	15.00
MRF134	10.50	MRF1004M	31.05	PT8633	25.00	SD1088	22.00
MRF136	16.00	MRF2001	41.74	PT8639	25.00	SD1088-8	22.00
MRF171	35.00	MRF2005	54.97	PT8659	25.00	SD1089-5	15.00
MRF208	11.50	MRF5176	24.00	PT8679	25.00	SD1090	15.00
MRF212	16.10	MRF8004	2.10	PT8708	20.00	SD1094	15.00
MRF221	10.00	MSC1720-12	225.00	PT8709	20.00	SD1095	15.00
MRF223	13.00	MSC1821-3	125.00	PT8727	29.00	SD1098-1	30.00
MRF224	13.50	MSC1821-10	225.00	PT8731	25.00	SD1100	5.00
MRF227	3.45	MSC2001	30.00	PT8742	19.10	SD1109	18.00
MRF230	2.00	MSC2010	93.00	PT8787	25.00	SD1115-2	7.50
MRF231	10.00	MSC2223-10	245.00	PT8828	25.00	SD1115-3	7.50
MRF232	12.07	MSC2302	POR	PT9700	25.00	SD1115-7	2.10
MRF237	3.15	MSC3000	35.00	PT9702	25.00	SD1116	5.00
MRF238	13.80	MSC3001	38.00	PT9783	16.50	SD1118	22.00
MRF239	17.25	MSC72002	POR	PT9784	32.70	SD1119	5.00
MRF245	35.65	MSC73001	POR	PT9790	56.00	SD1124	50.00
MRF247	31.00	MSC80064	35.00	PT31083	20.00	SD1132-1	15.00
MRF304	36.00	MSC80091	10.00	PT31962	20.00	SD1132-4	12.00
MRF306	50.00	MSC80099	3.00	PTX6680	20.00	SD1133	9.50
MRF313	11.15	MSC80593	POR	RE3754	25.00	SD1133-1	10.00
MRF314	29.21	MSC80758	POR	RE3789	25.00	SD1134-1	2.50
MRF315	28.86	MSC82001	33.00	RF35	16.00	SD1134-4	12.00
MRF316	55.43	MSC82014	33.00	RF85	17.50	SD1134-17	12.00
MRF317	63.94	MSC82020M	130.00	RF110	21.00	SD1135	10.25
MRF412	18.00	MSC82030	33.00	S50-12	23.80	SD1135-3	12.00
MRF420	20.12	MSC83001	40.00	S3006	15.00	SD1136	12.50
MRF421	25.00	MSC83003	82.00	S3007	10.00	SD1136-2	12.50
MRF422	38.00	MSC83005	70.00	S3031	22.00	SD1143-1	10.00
MRF427	17.25	MSC83026	POR	SCA3522	5.00	SD1143-3	17.00
MRF428	63.00	MSC83303	POR	SCA3523	5.00	SD1144	4.00
MRF433	12.07	MSC84900	60.00	SD345	5.00	SD1145-5	15.00
MRF449/A	12.65	MT4150	14.40	SD445	5.00	SD1146	15.00
MRF450/A	14.37	MT5126	25.00	SD1004	15.00	SD1147	15.00
MRF452/A	17.00	MT5596(2N)	99.00	SD1007	15.00	SD1188	10.00
MRF453/A	18.40	MT5768(2N)	95.00	SD1007-2	15.00	SD1189	24.00
MRF454/A	20.12	MT8762	25.00	SD1007-4	15.00	SD1200	1.50
MRF455/A	16.00	NEO2136	2.00	SD1007-5	15.00	SD1201-2	15.00

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."


For information call: 602-265-0731

# MHz electronics


3802 North 27th Ave., Phoenix, AZ 85017

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

## E.F. JOHNSON ROLLER INDUCTORS

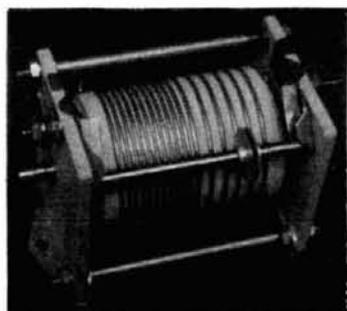


MODEL 229-0201-01  
10UH at 3AMPS MAX. \$36.99

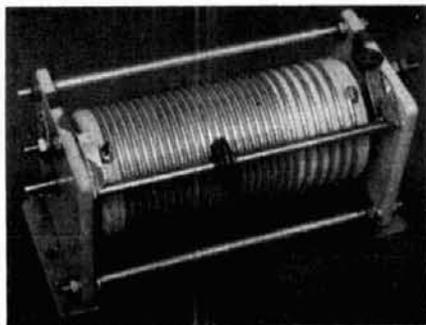

MODEL 229-0202-01  
18UH at 5AMPS MAX. \$44.99

## NI-CAD BATTERY CHARGERS

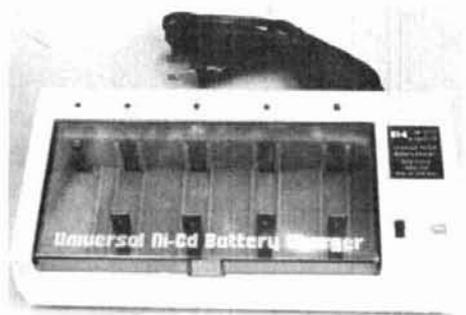

UNIVERSAL CHARGER \$19.99

### UNELCO, SEMCO, ARCO METAL CLAD MICA CAPACITORS

Standard Size				Micro Size		
3.9	14	33	62	175	5	25
4.7	15	34	68	180	5	27
5	18	36	75	200	7	33
5.1	20	38	80	220	8	36
6.8	22	39	82	240	9	51
7	24	40	100	250	12	62
8.2	25	43	110	300	15	
9.1	27	44	120	360	16	
10	27.5	47	123	470	18	
11	28	50	125	500	20	
12	30	51	140	820	22	
13	32	56	150	1000	24	

\*\*\*\*\*NOTE ALL VALUES LISTED IN PICO FARAD\*\*\*\*\*

#### PRICE INFORMATION

1 to 10 \$.90ea. 11 to 51 \$.80ea. 52 to 102 \$.70ea.  
103 and up call



MALLORY CHARGER \$23.99

\*\*\*\*\*

#### GOULD NI-CAD BATTERIES

AA size 1.25v at 500mahr new a \$ 1.99  
D size 1.25v at 4 AMPHR new h 7.49

#### GENERAL ELECTRIC NI-CAD BATTERIES

AA size 1.25v at 500mahr new a 2.99  
195194 3.75v at 100mahr new 1.99  
AA size 3.75v at 100mahr new a 2.99  
AA size pack of 10 12.5v at 450mahr used a 5.99  
Sub C Pack of 10 12.5v at 2.5Amphr new c 9.99

#### UNION CARBIDE NI-CAD BATTERIES

193817 3.75v at 225mahr new a 2.99

#### GLOBE GEL-CELL BATTERIES

2v at 8AMPHR GC280 new g 5.99  
12v at 20AMPHR GC12200 new g 49.99  
12v at 23AMPHR GC12300 new q 54.99

#### EAGLE PICHER GEL-CELL BATTERIES

12v at 1.5AMPHR CF12V1.5 new d 11.99


#### GATES SEALED RECHARGEABLE LEAD ACID BATTERIES AND PACKS

2v at 2.5AMPHR D Cell new b 5.99  
8v at 5AMPHR 4 X Cell used f 14.99  
12v at 2.5AMPHR 6 D Cells new f 24.99  
18v at 2.5AMPHR 9 D Cells new f 29.99

#### GENERAL ELECTRIC SEALED RECHARGEABLE LEAD ACID BATTERIES AND PACKS

6v at 2.5AMPHR 3 D Cells used e 10.00  
12v at 2.5AMPHR 6 D Cells used e 19.99  
12v at 5AMPHR 6 X Cells used e 24.99

\*\*\*\*\*

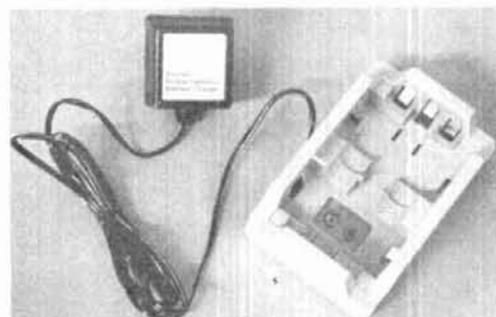

EVEREADY CHARGER \$9.99



**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

For information call: 602-265-0731

# MHz electronics

3802 North 27th Ave., Phoenix, AZ 85017

PRICES SUBJECT TO CHANGE WITHOUT NOTICE

## RF Transistors (continued)


SD1202	\$10.00	SD1304-8	\$ 2.50	SD1451-2	\$15.00	SRF1427	\$50.00	SD1244H12	25.00	SD1410-8	21.00	SD1536-1	41.00	SRF2917	15.00
SD1212-8	4.95	SD1305	3.00	SD1452	30.00	SRF1431	40.00	SD1262	15.00	SD1413-1	18.00	SD1539H	100.00	SRF2918	15.00
SD1212-11	4.95	SD1305F	3.00	SD1452-4	26.00	SRF1834	40.00	SD1263	15.00	SD1416	28.00	SD1542H1	170.00	SRF2919	15.00
SD1212-16	4.95	SD1308	3.00	SD1453H1	20.00	SRF2053-3	60.00	SD1263-1	15.00	SD1422-2	24.00	SD1544	26.00	SRF3071PF	50.00
SD1214-2	5.00	SD1311	1.00	SD1454-1	48.00	SRF2092	50.00	SD1272	10.95	SD1428	24.00	SD1545	33.00	SS4006	25.00
SD1214-11	5.00	SD1311	8.00	SD1477	35.00	SRF2147	22.00	SD1272-1	10.95	SD1428-6084	12.00	SD1546H1	55.00	SS4152	15.00
SD1216	12.00	SD1319	2.50	SD1478	21.00	SRF2225	15.00	SD1272-2	10.95	SD1429-2	15.00	SD1561	79.00	TA7686	15.00
SD1219-4	15.00	SD1345-6	5.00	SD1480	33.00	SRF2264	25.00	SD1272-4	10.95	SD1429-3	14.90	SD1574-1	6.95	TAB559	15.00
SD1219-5	15.00	SD1347-1	1.00	SD1484	1.50	SRF2265	100.00	SD1278	13.75	SD1429-5	15.00	SD1575	6.95	TAB561	15.00
SD1219-8	15.00	SD1365-1	2.50	SD1484-5	1.50	SRF2281	5.00	SD1278-1	13.75	SD1430	12.00	SRF4557	25.00	TAB562	15.00
SD1220	8.00	SD1365-5	2.50	SD1484-6	1.50	SRF2371	15.00	SD1278-5	13.75	SD1430-2	18.00	SRK048	5.00	TAB563	15.00
SD1220-1	4.50	SD1375	7.50	SD1484-7	1.50	SRF2347	50.00	SD1279-1	18.00	SD1434	28.00	SL501-59	15.00	TAB564	15.00
SD1220-9	8.00	SD1375-6	7.50	SD1488	22.85	SRF2356	18.00	SD1279-3	18.00	SD1434-5	28.00	SL501-173	15.00	TAB894	15.00
SD1222-8	16.00	SD1379	15.00	SD1488-1	28.00	SRF2378	18.00	SD1281-2	8.00	SD1434-9	28.00	SM714	5.00	TIS189	3.55
SD1222-11	7.50	SD1380-1	1.00	SD1488-7	27.00	SRF2572	25.00	SD1283	10.00	SD1438	26.00	SRF112	15.00	TP312	2.50
SD1224-10	18.00	SD1380-3	1.00	SD1488-8	28.00	SRF2584	40.00	SD1283-2	10.60	SD1441	56.00	SRF395	50.00	TP1014	5.00
SD1225	18.00	SD1380-7	1.00	SD1499-1	36.00	SRF2597	23.00	SD1283-3	10.00	SD1442	15.00	SRF750	36.00	TP1028	15.00
SD1225-1	15.00	SD1405	21.00	SD1511H3	75.00	SRF2741	40.00	SD1283-4	10.00	SD1444	1.25	SRF769H	20.00	TR3	5.00
SD1229-7	10.95	SD1408	25.00	SD1520-2	18.00	SRF2747	40.00	SD1289-1	15.00	SD1444-8	3.25	SRF887E3	2.50	TXF2201/HP	450.00
SD1229-16	10.95	SD1409	18.00	SD1522-4	33.00	SRF2767H	40.00	SD1290-4	15.00	SD1444-9	1.25	SRF898H	13.00	X222-2	23.00
SD1232	4.00	SD1410	18.00	SD1528-1	24.00	SRF2821	25.00	SD1290-7	15.00	SD1446	4.03	SRF1005	50.00	V4101E	20.00
SD1240-8	15.00	SD1410-3	21.00	SD1528-3	34.00	SRF2822/ZR66403	13.50	SD1300	1.25	SD1450-1	28.00	SRF1018	5.00	V415	5.00
SD1244-1	14.00	SD1410-6	21.00	SD1530-2	38.00	SRF2857	20.00	SD1301-7	3.00	SD1451	15.00	SRF1074	50.00		

## Relays

BNC To Banana Plug Coax Cable RG-58 36 in. or N Coax Cable RG-58 36 in.

• \$7.99 or 2 For \$13.99 or 10 For \$50.00

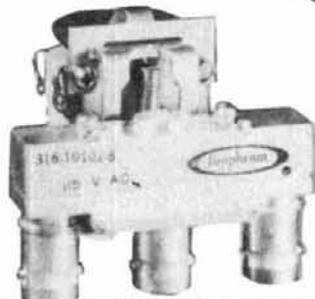• \$8.99 or 2 For \$15.99 or 10 For \$60.00



Amphenol  
Part # 316-10102-8  
115Vac Type BNC DC to 3 GHz.

\$29.99

### COAXIAL RELAY SWITCHES SPDT

FXR  
Part # 300-11182  
120Vac Type BNC DC to 4 GHz.  
FSN 5985-543-1225

\$39.99

FXR  
Part # 300-11173  
120Vac Type BNC Same  
FSN 5985-543-1850

\$39.99

**TERMS:** DOMESTIC: Prepaid, C.O.D. or Credit Card  
FOREIGN: Prepaid only, U.S. Funds, Money Order, or Cashier's Check Only.

**C.O.D.:** Acceptable by telephone or mail. Payment from customer will be CASH ONLY. We are sorry but we cannot accept personal checks for C.O.D.'s. C.O.D.'s are shipped by air only and thru United Parcel Service.

**CONFIRMING ORDERS:** We would prefer that confirming orders not be sent after a telephone order has been placed. If company policy requires a confirming order, please mark "CONFIRMING ORDER" boldly on the order. If problems or duplicate shipments occur due to an order which is not properly marked, the customer will be held responsible for any charges incurred, plus a 15% restocking fee on the returned parts.

**CREDIT CARDS:** We are now accepting MASTERCARD, VISA, AND AMERICAN EXPRESS

**DATA SHEETS:** When we have data sheets in stock on devices we will supply them with the order.

**DEFECTIVE MATERIALS:** All claims for defective materials must be made within 30 days after receipt of the parcel. All claims must include the defective material (for testing purposes), a copy of our invoice, and a return authorization number. The return authorization number can be obtained by calling (602) 265-0731 or sending us a postcard. This must be obtained before shipping the merchandise back to us otherwise the package could be refused and notification will not be considered completed until this number has been assigned. Due to manufacturers warranties we are unable to replace or issue credit on items which have been soldered to or have been altered in any way. All return items must be packed properly, and insured if this is not done so it will void all warranties. We do not assume any responsibility for shipping charges incurred.

**DELIVERY:** Orders are usually shipped the same day they are placed or the next business day, unless we are out of stock on an item. The customer will be notified by post card if we are going to backorder the item. Our normal shipping method is UPS or U.S. Mail depending on size or the weight of the package. Test Equipment is shipped only by air and is freight collect, unless prior arrangements have been made and approved.

**FOREIGN ORDERS:** All foreign orders must be prepaid with Cashier's check, Money Order, or bank wire made out in U.S. Funds only. We are sorry but C.O.D. is not available to foreign countries and letters of credit are unacceptable forms of payment.

**HOURS:** Monday thru Friday 8:30 a.m. to 5:00 p.m. Saturdays 8:30 a.m. to 4:00 p.m.

**INSURANCE:** Please include 25¢ for each additional \$100.00 over \$100.00 UPS only. All insured packages are shipped thru UPS and U.S. Mail. U.S. Mail insurance is calculated at the time of shipment. In the United States insured packages are shipped only by UPS.

**ORDER FORMS:** New order forms are included with each order for your convenience. Additional order forms are available on request.

**PARTS:** We reserve the right to substitute or replace any item with a part of equal or comparable specification.

**POSTAGE:** Minimum shipping and handling in the U.S., Canada, and Mexico is \$3.00 for ground shipments. Foreign countries is \$5.40 or 25% of order whichever is greater. Air rates are available at the time of your order. C.O.D.'s are shipped AIR ONLY.

**PREPAID ORDERS:** Orders must be accompanied by check, bankcard number, or money order.

**PRICES:** Prices are subject to change without notice.

**PURCHASE ORDERS:** We accept purchase orders accompanied by a check. All others must have prior approval by management.

**RESTOCK CHARGES:** If parts are returned to MHz Electronics, Inc. due to customer error, the customer will be held responsible for all fees incurred and will be charged a 15% restocking fee with the remainder in CREDIT ONLY. Return authorization must be obtained within 5 working days of receipt of the parcel, otherwise the order will be considered complete. The following must accompany any return: A copy of our invoice, return authorization number which must be obtained prior to shipping merchandise back and must appear on the outside of the package. Return authorizations can be obtained by calling (602) 265-0731. Return authorizations will not be given out on the 800 number. All items must be properly packed and insured. We will not give any credit on items which are damaged due to improper packing.

**SALES TAX:** ARIZONA residents must add 6% sales tax, unless a signed ARIZONA resale tax card is currently on file with us. All orders placed by persons outside of ARIZONA, but delivered to persons in ARIZONA are subject to the 6% sales tax.

**SHORTAGES OR DAMAGED MERCHANDISE:** All claims for shortages or damages must be made within 5 DAYS of receipt of parcel. Claims must include a copy of our invoice, along with a return authorization number which must appear on the outside of the package. The return authorization number can be obtained by calling (602) 265-0731 or sending us a postcard. Authorizations cannot be given on any damages which may occur in shipment back to us. We do not assume any responsibility for shipping charges incurred. If you have received a damaged package please make sure to contact the carrier so that they can come out and inspect the package before it is shipped back to us. All damaged packages must be returned to us with its original shipping material and contents. Customers who do not notify us within this time period will be held responsible for the entire order as we will consider the order complete.

OUR 800 NUMBER IS STRICTLY FOR ORDERS ONLY (800) 528-0180. INFORMATION CALLS ARE TAKEN ON (602) 265-0731



# MHz

electronics

3802 North 27th Ave., Phoenix, AZ 85017

"All parts may be new or surplus, and parts may be substituted with comparable parts if we are out of stock of an item."

For information call: 602-265-0731

**Toll Free Number**  
**800-528-0180**  
**(For orders only)**

**PRICES SUBJECT TO CHANGE WITHOUT NOTICE**



## NEW products

### 900-MHz scanner converter

Hamtronics, Inc. has announced a new converter for scanner radios to cover the 900-MHz land mobile band. An adaptation of the very popular CVR-806, which covers the 806-896 MHz band, the new 900-MHz converter allows coverage of new services now being assigned or proposed for the 880-960 MHz range, including additional land mobile services, such as police and fire departments, government and non-government fixed stations, industrial, scientific, and medical services, and the proposed 902-928 MHz Amateur band. Also included are proposed new cellular telephone and paging services and existing and new broadcast studio-transmitter links. The price of the CVR-900 is \$88 plus \$3 for shipping and handling. Other converters are available for the 72-76, 135-144, 240-270, 400-420, and 806-896 MHz bands at the same price.

For a complete catalog of Hamtronics' products, send \$1 to Hamtronics, Inc., 65-F Moul Road, Hilton, New York, 14468-9535. (For overseas mailing, please send \$2 or 4 IRCs.)

### UHF cavity amplifiers

Varian/EIMAC has introduced six new UHF cavity power amplifiers designed for FM, CW, pulse, or single-sideband linear service in the 280 to 530 MHz frequency range.

Using the EIMAC 3CX800A7 high- $\mu$  power triode, the cavity amplifiers eliminate equipment design complications and extra power supplies associated with UHF tetrode cavities, yet provide comparable stage gain. Power gain in FM or CW service for all cavities is on the order of 11 dB with efficiency ratings in excess of 55 percent.

In addition to being more efficient, the new cavity amplifiers offer reliability in the targeted bands because of the comparatively simple design.

The cavities provide approximately 450 watts power output in CW and FM service over the following ranges: CV-2401, 390 to 450 MHz; CV-2402, 375 to 420 MHz; CV-2403, 280 to 300 MHz; CV-2404, 470 to 530 MHz; CV-2405, 330 to 370 MHz; and CV-2406, 450 to 470 MHz.

Standard 50-ohm Type N input and output RF connectors are used for all cavities. Silver-plated components are used to ensure the best performance and efficiency.

The cavities are forced-air cooled and de-

signed for mounting to a customer's 19-inch panel. Each has a net weight of about 13 pounds. All are 14 inches wide, 10 inches deep, and range in height from 6.2 to 9.3 inches.

For additional information or literature, contact Varian/EIMAC, 301 Industrial Way, San Carlos, California 94070.

Circle #308 on Reader Service Card.

### packet communicator

Kantronics has announced a new product for Amateurs using computers in the shack: the Kantronics Packet Communicator.

Interest in packet radio has grown in recent years with volunteer Amateur groups doing research and testing of the new mode. With the ARRL adoption of the AX.25 protocol as the Amateur standard, packet radio became a viable form of data exchange. Thousands of Amateurs have proven the new mode reliable using a hardware and software program devised by the Tuscon Area Packet Radio group (TAPR).

To better utilize the new packet technology Kantronics has designed a new hardware format for processing the packet protocol. By using an internal microprocessor to handle the protocol, and integrated circuits for signal processing, the Kantronics Packet Communicator becomes the most compact and inexpensive finished packet unit available today.

Data is transmitted between the Kantronics Packet Communicator and the computer using a Series RS232 or TTL port. Baud rates of 300, 1200, and 9600 can be used. Any terminal or communications software program can be used to set up the computer to communicate with the Packet Communicator. Special Packet Terminal (PAC-Term™) programs for many popular personal computers will be available soon from Kantronics.



System compatibility, the ability to exchange data with existing Packet Terminal Node Controllers, has been achieved with the Kantronics Packet Communicator by using the popular TAPR software.

Almost all of the commands and operation procedures used by the TAPR group are used with the Kantronics Packet Communicator. Both

the ARRL standard AX.25 and Vancouver protocols are incorporated in the unit. The Kantronics Packet Communicator supports baud rates of 300, 400, 600, and 1200, but the unit does not support full duplex operation.

An added feature of the Kantronics Packet Communicator is the ability to select either Bell 103 or 202 tones for 300 baud operation. This will allow the operator to switch to the lower tone set, improving performance at slower speeds on the HF bands. This feature makes the Kantronics Packet Communicator an excellent choice for gateway use on the HF bands. The suggested retail price is \$389.95.

For further information, contact your local Kantronics dealer, or Kantronics, 1202 East 23rd Street, Lawrence, Kansas 66046.

Circle #307 on Reader Service Card.

### headset/boom microphone for TR-720

Communications Specialists has announced the availability of a high quality headset/boom microphone that plugs directly into the TR-720 handheld airband transceiver. The CS-65 HEAD-



SET/MIC was developed to permit improved transmission and reception with the TR-720 in noisy environments. This new accessory is light (12 ounces) and features cushioned, noise-attenuating ear pads that can be adjusted for a comfortable fit. A flexible boom supports and electret noise-cancelling microphone. Supplied with a 5-foot cable to connect to the radio, the unit comes with a push-to-talk switch attached. The CS-65 HEADSET/MIC lists for \$69.95.

For further information, contact Communications Specialists, Inc., 426 West Taft Avenue, Orange, California 92665.

Circle #306 on Reader Service Card.

# TNT RADIO SALES INC.

**1-800-328-0250**

1-612-535-5050

(IN MINNESOTA—COLLECT)

## YOU GET MORE "BANG FOR YOUR BUCK" AT TNT RADIO SALES!

- |              |                |               |             |
|--------------|----------------|---------------|-------------|
| ■ Kenwood    | ■ Mirage       | ■ MFJ         | ■ Welz      |
| ■ Icom       | ■ KLM          | ■ Astron      | ■ Azden     |
| ■ Bencher    | ■ Telex Hygain | ■ Alpha/Delta | ■ Santec    |
| ■ AEA        | ■ Nye Viking   | ■ Bearcat     | ■ KDK       |
| ■ Kantronics | ■ Larsen       | ■ Regency     | ■ Ameritron |

SALES AND SERVICE AT PRICES YOU CAN AFFORD!  
CALL OUR WATS LINE FOR LOW LOW PRICES!

**SPECIAL OF THE MONTH: LARSEN MAG MOUNT 2M  $\frac{5}{8}$  PKG—\$36.95**

VISA/MASTER CARD  
FREE SHIPPING  
ON MOST RIGS FOR CASH!



S.A.S.E. FOR OUR  
"BENCH-TESTED"  
USED EQUIPMENT LISTING

MON-FRI 9 AM - 6 PM CENTRAL TIME  
SATURDAY 9 AM - 5 PM

4124 West Broadway, Robbinsdale, MN 55422 (Mpls./St. Paul)

✓ 167

### TWO NEW ONES FROM ARCSOFT

#### QUICK-N-EASY ELECTRONICS PROJECTS



by Bob Green

Here's a neat book to help while away a rainy afternoon. Contains 40 quick and easy to build projects using commonly found electronic components. Learn-by-doing format is a boon to beginners while advanced builders will enjoy the range of projects included. Projects include: CPO, high VSWR alarm, three battery charger, body bug and sun spotter to

name just a few. Also includes list of mail order and local parts supplier suggestions. 1st edition © 1985 96 pages.

AR-QN Softbound \$7.95

#### EASY-TO-BUILD ELECTRONICS PROJECTS

by Bob Green



40 more electronics projects to work on! Complete plans and schematics and easy-to-locate parts means that you can usually complete these projects in an evening. Projects include: Ad silencer, Mugger bugger, radio-tester, fuse telltale plus 36 more. More practice for the beginner and more fun for the advanced builder. 1st edition © 1985 96 pages

AR-ET Softbound \$7.95

Please enclose \$3.50 to cover shipping and handling

ham  
radio

BOOKSTORE

GREENVILLE, NH 03048

(603) 878-1441

All you need to know about land  
mobile crystals is our phone  
number: 800-526-3935



## BOMAR

CRYSTAL COMPANY

Fast Delivery Elements, icoms,  
Lifetime Guarantee TCXO's, etc.

201 Blackford Avenue, Middlesex, N.J. 08846  
(In N.J. call) 201-356-7787

"We are small enough to care, yet big enough  
to do something about it!"

✓ 168

#### Invitation to Authors

ham radio welcomes manuscripts from readers. If you have an idea for an article you'd like to have considered for publication, send for a free copy of the ham radio Author's Guide. Address your request to ham radio, Greenville, New Hampshire 03048 (SASE appreciated).

# The Problem Solver...

The RF Wattmeter Model 81000-A from Coaxial Dynamics, Inc. does more than provide accurate rf measurements. Testing of transmission lines, antennas, connectors, filters and related components can reveal unknown problems and assure optimum equipment performance.

The 81000-AK Wattkit features this easy-to-read RF Wattmeter (pictured here), with its optional carrying case and an array of elements and accessories. Coaxial Dynamics elements can be purchased separately for use in other manufacturer's Wattmeters. For more information on the 81000-A Wattmeter or any of the complete line of Coaxial Dynamics RF products and OEM components please contact Coaxial Dynamics, Inc.



**COAXIAL DYNAMICS, INC.**

15210 Industrial Parkway, Cleveland, OH 44135 • (216) 267-2233  
Outside Ohio, WATS: (800) Coaxial, Telex: 980-630

169



**the HAM STATION**

220 N. FULTON AVENUE  
P.O. BOX 4405  
EVANSVILLE, INDIANA 47710

LARGE STOCK OF NEW EQUIPMENT  
AT DISCOUNT PRICES

Orders 1-800-523-7731  
Indiana (812) 422-0231  
Info & Service (812) 422-0252

CALL FOR PRICES ON  
EQUIPMENT FOR OSCAR 10

PRICES AND AVAILABILITY SUBJECT TO  
CHANGE. FREIGHT FOB EVANSVILLE.

**AEA**  
ATU-1000-Superb interface \$1100.00  
CP-100-Deluxe interface CALL  
CP-1-interface 189.95  
MP-1-Micropatch 129.95  
DR-DXOR QSO 99.00  
MBA-TOR Software 99.95/79.95  
PKT-1 Packet Controller 459.95  
Isopoles, Hot Rods, Software in Stock

**ALINCO**  
Amplifiers in stock CALL

**ASTRON**  
RS7A 5-7 Amp \$ 49.00  
RS10A 7.5-10 Amp 59.00  
RS12A 9-12 Amp 89.00  
RS20A 16-20 Amp 89.00  
RS20M 16-20 Amp w/meter 109.00  
RS35A 25-35 Amp 135.00  
RS35M 25-35 Amp w/meter 149.00  
RS50A 37-50 Amp 199.00  
RS50M 37-50 Amp w/meter 225.00

**BENCHER**  
BY-1 Black Chrome/By-2 Chrome \$39/49.00  
ZA-1A Balun 19.00



New 561 Corsair List \$1354.00  
Call for Discount Price

**B & W**  
370-15 80-10M Folded Dipole \$145.00  
AT-110 5 Band Trap Dipole 76.00  
AT-55 4 Band Trap Dipole 58.00  
Various Antennas & Coax Switches in Stock

**Butternut**  
HF3B-Butterfly Compact Beam \$179.95  
HF6 80-10M Vertical 119.95  
HF2V 80-40M Vertical 115.00  
TBR-160-S 160M Resonator 49.00

**Cuecraft**  
A4 Tribander \$269.00  
A3 Tribander 215.00  
A147-11 2M 11 EL 49.00  
A449-11 450 MHZ 44.00  
215WB 2M JR Boomer 79.00  
230WB Stacked 215's 219.00  
32-19 Boomer 19 EL 2M 95.00  
AOP-1 OSCAR PKGE 149.00  
Ringo Rangers 2M, 6M, 220, 450 39.95

**DAIWA**  
CN-520 1.8-60 MHZ Mtr \$ 63.00  
CN-620B 1.8-150 MHZ Mtr 110.00  
CN-630 140-450 MHZ Mtr 129.00  
CN-410M 3.5-150 MHZ Mtr 85.00  
CS-201 2 Pos Switch 23.00  
CS-401 4 Pos Switch 63.00

**ENCOMM**  
NEW FM-240 25W FM Xcvr CALL

**HAL**  
Computer interfaces & dedicated Terminals

**HEIL**  
Products in Stock CALL

G-7-144 MHZ Vertical \$119.95  
G-6-144B 2M Vertical 85.95  
G-6-440 MHZ Vertical 109.95  
68TV 80-10M Vertical 129.95  
Mobile HF & VHF Antennas in Stock

**HYGAIN**  
TH7DXS 7EL Tribander \$435.00  
Explorer 14 3EL Tribander 299.95  
QK710 30/40 Mtr Kit 79.00  
Discoverer 2-EL 40 Mtr 319.00  
18HTS 80-10M Vertical 439.00



IC-3200  
Call for Special Price

**HYGAIN**  
18AVT/WBS 80-10M Vertical 109.00  
14AVO/WBS 40-10M Vertical 75.00  
214BS-14EL 2M Beam 55.00  
V2, V3, V4 2M, 220, 440 Verticals CALL  
287 2Mtr Mag Mnt 26.00

**ICOM**  
751 Top of the Line \$1179.00  
735 New Fantastic Xcvr 749.00  
271A/M 2M All Mode CALL  
471A/M 430-450 MHZ All Mode CALL  
27A/M Mtr Mobiles CALL  
37A 220 MHZ Mobile CALL  
47A 440 MHZ Mobiles CALL  
3200 Dual Band 144 & 440 CALL  
02AT/04AT 2 Mtr-440 MHX H.T.'s CALL  
2AT 2 Mtr H.T. 199.95  
3AT/4AT 220/440 MHZ H.T.'s 229.95  
Huge inventory of Accessories & Radios

**KANTRONICS**  
Packet Communicator \$349.95  
UTU Universal Terminal Unit 179.95  
Interface II Deluxe interface 229.95  
Challenger economical interface 89.95  
Software in Stock—CALL

**KLM**  
2M-14C 2M Circular Ant. w/CS-2 \$ 85.00  
2M-22C 2M Circular Ant. w/CS-2 120.00  
435-18C Circular Ant. 85.00  
435-40CX Circular Ant. w/CS-2 149.95  
CS-2 Circularity Switch 55.00  
2M-16L BX 2mtr Yagi 105.00  
432-30L BX Yagi 99.75

**LARSEN**  
NLA-150/220/450 Mag. Mnt \$39.95 ea.  
NLA 2/70 Dual Band Mag. Mnt Ant. 59.95

**MFJ**  
1229 interface/free Software \$159.95  
1224 interface/free Software 85.00  
1228 interface/free Software 59.95  
989 3KW Roller inductor tuner 289.95  
949C 300 W Tuner w/D. Load 135.00  
941D 300 W full feature tuner 89.95  
204 Antenna Bridge 71.95  
422 Keyer/Benchmer Combo 99.95



"New KDK FM-240"  
"Call for Discount Price."

**MIRAGE**  
B1016 10/180W-Preamp \$249.95  
B3016 30/180W-Preamp 204.95  
B23A 230W-Preamp 89.95  
D1010N 10/100W 430-450 MHZ 289.95

**NYE**  
MB-V-A The Ultimate Tuner \$499.95

**SHURE**  
444D Hi-Lo Z Desk Mic \$55.00

**TEN-TEC**  
NEW Corsair—Very Nice CALL  
Century 22 CW Xcvr \$ 349.95  
2510 Satellite Station 409.95  
Titan—Your Last Amplifier 2175.00

**TOKYO HY-POWER**  
HL30V 3/30W Amp \$ 62.95  
HL35V 3/30 Amp w/Gaslet 75.00  
HL180V 3/10-180W Amp 295.95  
HL180V25 25-180W Amp 259.95  
HL20U 430-449 MHZ 3/20W Amp 105.95  
HL120U 430-449 MHZ 10/100W Amp 319.95  
HC-2000 2KW Tuner 295.95  
HC-400L Tuner w/Dual Needle Mtr 175.95  
HRA-2 2Mtr Gaslet Preamp 115.95  
HRA-7 70 CM Gaslet Preamp 119.95

**YAESU**  
FT-980 Deluxe Xcvr \$1425.00  
FT-757 Gen Cov. Xcvr CALL  
FT-757H D. P. S. w/fan 175.00  
FT-747AT Autotuner 235.00  
FT-726R Multi Band Xcvr CALL  
FT-270R 45W 2Mtr 375.00  
FT-2700RH 2Mtr/440MHZ 489.95  
FT-206RH 5W 2Mtr H.T. 299.95  
FRG-8800 HI Communications Rcvr 499.95  
FRG-9800 80-980MHZ Scanning Rcvr CALL  
Large Stock of Accessories

**WELZ**  
Mtra. Antennas, Duplexers in Stock

**ROTATORS**  
Alliance HD-73 \$115.00  
Alliance U-110 49.95  
Telex CO-45 139.95  
Telex Ham 4 239.95  
Telex T2X 289.95  
Ken Pro KR500 155.95



## touchtone decoder kit

Engineering Consulting has announced the model TSD 4-digit sequential touchtone (DTMF) decoder for mobile and base station use. Each board can have a unique 4-digit user-programmable access code. The board will install in most VHF/UHF and HF gear, allowing alarm or mute functions to be implemented. Typical applications include muting the audio circuit until a valid 4-digit code is received. An alarm can be sounded upon receipt of the access code to alert the operator that someone is calling on the channel, without having to listen for your call sign.

The model TSD decoder is easy to install in any 12-volt radio. Speaker audio or low-level audio may be used to listen to the tones. An open collector transistor provides the output control to switch a small relay or alarm device. Either momentary or latching control is provided with jumper selection. Upon receipt of the access code a latch or momentary pulse is provided. Send the code again and the latch will reset. The TSD is available wired and tested from Engineering Consulting for \$59.95.

For further information, contact Engineering Consulting, 583 Candlewood Street, Brea, California 92621.

Circle #305 on Reader Service Card.

## super CW

Super-CW, a CW audio processor from Hildreth Engineering, includes an 8th order Butterworth cascade of staggered pairs to provide excellent skirt rejection without excessive response to impulse noise. The 3-dB passband is from 700 to 800 Hz with a 3 to 30 dB shape factor of less than 3.

More than just a filter, the unit features an S/N BOOST function, which is driven by the pre-filter, to provide a signal-to-noise ratio enhancement of over 10 dB as compared with the linear filter position. It does this for signals that are well below the noise in a typical 3 kHz audio bandwidth. This boost circuitry uses compound-complex filter/limiter/filter elements with added active circuits (patent applied for) that creates S/N enhancement for CW — or any pulse-code-modulation (PCM) signal — analogous with that enjoyed by FM communications systems. A second and very important benefit is ear protection. When in the S/N BOOST position, the sudden onset of strong signals or noise pulses just can't happen. You get a clean, distortion-free signal at a sound pressure level uniquely determined by the AF GAIN control.

A 2-watt power amplifier with a controlled



voltage gain of 25 is included to allow a reduction in receiver RF gain, which reduces the tendency toward non-linear disturbances in your receiver's IF and/or product detector when listening to a weak signal under the condition of strong signal QRM outside of the 700 to 800 Hz passband. The unit receives its input from your receiver's speaker output. Power supply requirements are 12 to 15 VDC at a nominal 350 mA peak. The unit will drive a 4 to 8 ohm speaker.

For more information, contact Hildreth Engineering Corporation, P.O. Box 60003, Sunnyvale, California 94088.

Circle #303 on Reader Service Card.

## filters for TS-940S

Matched sets of filters for the Kenwood TS-940S are available from International Radio, Inc. The SSB-2.1 kHz set consists of one 8.83 MHz, 2.1 kHz drop-in, 8-pole crystal filter and one 2.1 kHz 455 kHz 8-pole crystal filter (wired in). This matched set will provide an overall system selectivity of 2.0 kHz at 6 dB and 2.5 kHz at 60 dB. The shape factor is 1.25.

The CW-400 Hz matched set consists of one drop-in 8.8 MHz 400 Hz 8-pole crystal filter and one drop-in 455 kHz filter, for system selectivity of 400 Hz at 6 dB and 700 Hz or less at 60 dB. The shape factor is 1.75 or less.

Sets are priced at \$139.00 each, or \$260 for both. All crystal filters are guaranteed for two years. Quantity discounts are available.

For further information, contact International Radio Inc., 364 Kilpatrick Avenue, Port St. Lucie, Florida 33452.

Circle #304 on Reader Service Card.

## solar breakthrough

The ENCON Corporation has introduced the first commercially available amorphous (thin film) photovoltaic to the Amateur Radio marketplace. Genesis,™ a state-of-the-art 5-watt PV module, represents a breakthrough in solar cell technology. Typical applications for the new modules, which may be wired together for increased power, include battery maintenance on ham equipment, recreational vehicles, and boats. The modules can produce enough power for telecommunication from QRP stations, security equipment, and some home lighting.

Manufactured by ARCO Solar, the Genesis is designed for easy use. Convenient front mount-

**SPS  
DIST.**

**TI  
FINDER +**



Complete Line of  
Satellite Receiving Systems

**SPS**

San Pierre, IN

(219) 828-7255 — 828-3091

✓ 170

**AUTHORIZED KENWOOD  
I-COM RADIO DEALER**



✓ 171

H. L. HEASTER, INC., 203 Buckhannon Pike, Clarksburg, W. Va. 26301  
Clarksburg Phone (304) 524-5485 or W. Va. Toll-Free 1-800-352-3177  
Harold Heaster, KANOHX, 350 Hickory Hill Place, Ormond Beach, FL 32074  
Florida Phone (904) 673-4066

We sell all brands of amateur radios, amplifiers, antennas, towers, etc.  
Call us for a quotation for your needs. **we guarantee to save you money!**  
Nation wide toll free (answers 24 hrs.) 1-800-824-7888, operator 885 when  
using the nation wide toll free telephone you must leave a message for a  
call back from me. Please allow 3-5 days for a return call. Thank you!

**Electronic Repair Center  
Servicing**

**Amateur Commercial Radio**

The most complete repair facility on  
the East Coast.

Large parts inventory and factory  
authorized warranty service for  
Kenwood, Icom and Yaesu.

**SEND US YOUR PROBLEMS**

Servicing "Hams" for 30 years, no rig  
too old or new for us.

**HAMTRONICS, INC.**

4033 Brownsville Road  
Trevose, Pa. 19047

**215-357-1400**

# High Performance vhf/uhf preamps



Receive Only	Freq. Range (MHz)	N.F. (dB)	Gain (dB)	1 dB Comp. (dBm)	Device Type	Price
P28VD	28-30	< 1.1	15	0	DGFET	\$29.95
P50VD	50-54	< 1.3	15	0	DGFET	\$29.95
P50VDG	50-54	< 0.5	24	+12	GaAsFET	\$79.95
P144VD	144-148	< 1.5	15	0	DGFET	\$29.95
P144VDA	144-148	< 1.0	15	0	DGFET	\$37.95
P144VDG	144-148	< 0.5	24	+12	GaAsFET	\$79.95
P220VD	220-225	< 1.8	15	0	DGFET	\$29.95
P220VDA	220-225	< 1.2	15	0	DGFET	\$37.95
P220VDG	220-225	< 0.5	20	+12	GaAsFET	\$79.95
P432VD	420-450	< 1.8	15	-20	Bipolar	\$32.95
P432VDA	420-450	< 1.1	17	-20	Bipolar	\$49.95
P432VDG	420-450	< 0.5	16	+12	GaAsFET	\$79.95


### Inline (rf switched)

SP28VD	28-30	< 1.2	15	0	DGFET	\$59.95
SP50VD	50-54	< 1.4	15	0	DGFET	\$59.95
SP50VDG	50-54	< 0.55	24	+12	GaAsFET	\$109.95
SP144VD	144-148	< 1.6	15	0	DGFET	\$59.95
SP144VDA	144-148	< 1.1	15	0	DGFET	\$67.95
SP144VDG	144-148	< 0.55	24	+12	GaAsFET	\$109.95
SP220VD	220-225	< 1.9	15	0	DGFET	\$59.95
SP220VDA	220-225	< 1.3	15	0	DGFET	\$67.95
SP220VDG	220-225	< 0.55	20	+12	GaAsFET	\$109.95
SP432VD	420-450	< 1.9	15	-20	Bipolar	\$62.95
SP432VDA	420-450	< 1.2	17	-20	Bipolar	\$79.95
SP432VDG	420-450	< 0.55	16	+12	GaAsFET	\$109.95

Every preamplifier is precision aligned on ARR's Hewlett Packard HP8970A/HP346A state-of-the-art noise figure meter. RX only preamplifiers are for receive applications only. Inline preamplifiers are rf switched (for use with transceivers) and handle 25 watts transmitter power. Mount inline preamplifiers between transceiver and power amplifier for high power applications. Other amateur, commercial and special preamplifiers available in the 1-1000 MHz range. Please include \$2 shipping in U.S. and Canada. Connecticut residents add 7-1/2% sales tax. C.O.D. orders add \$2. Air mail to foreign countries add 10%. Order your ARR Rx only or inline preamplifier today and start hearing like never before!
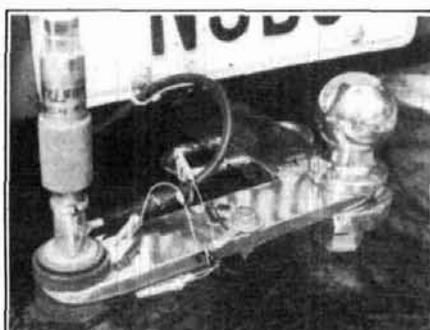
## Advanced Receiver Research

Box 1242 • Burlington, CT 06013 • 203 582-9409



## TENNA HITCH by DC SALES

For Class #1 & #2 hitches  
Adapts your existing car trailer hitch for any HF Antenna No holes in your car

Complete \$29.95

Plus \$5 postage & handling

Contact your favorite dealer or:



DC SALES

1602 Chestnut Ridge Rd.

Kingwood, TX 77339

(713) 358-0051

Dealer inquiries invited

174

## WARC for FT-101/901

### WELCOME TO 12 METERS!

Add all three WARC Bands to your FT-101

- Increases Resale Value of your Rig.
- Installs easily, detailed instructions.
- Includes all crystals, relays, wire, etc.
- Tested, fool-proof design for all but 'ZD

FT-101 3-band WARC Kit.....\$25

FT-901 30M Only WARC Kit.....\$10

Shipping \$3, Air \$5 (US & Canada), \$10 Elsewhere  
Order by mail or phone: VISA/MC or COD Accepted

GO FOX TANGO - TO BE SURE!

## FOX TANGO CORPORATION

Box 15944 H, W. Palm Beach, FL 33416

(305) 683-9587

175

## STATION MANAGER/ADVANCED

A General Purpose Logging Program

Designed for the IBM® PC,® XT,® enhanced PC jr.® Menu driven; prompts for easy use; full color displays; multiple logs (each up to 1,000 entries with user editing), several reporting methods including one by partial callsign.

\$79.00 includes: 90 pg. User's Guide & Diskette (source code included)

\$20.00 — User's Guide only (may be applied to full purchase price)

Ohio residents include sales tax

## OMEGA CONCEPTS

Professional software for the Radio Amateur™

P.O. Box 615  
Troy, OH 45373



T.L. Jones (KB80A)  
Author

176

IBM is a registered trademark of International Business Machine Corp.



## GUS BROWNING, W4BPD's DX'ERS MAGAZINE

For over 17 years, Gus's DX'ERS MAGAZINE has brought thousands of DX'ERS worldwide, timely, pertinent information on when and where to find those elusive DX stations.

Gus's personable, chatty writing style and his years of DX operating experience makes the DX'ERS MAGAZINE a unique publication. One year \$14.00 USA, Canada & Mexico.

Gus also prints high quality QSLs and other related items.

Write today for a free sample of his QSLs and DX'ERS MAGAZINE.

Gus Browning, W4BPD • PO Drawer 405 • Cordova, SC 29039

173

172

Tell 'em you saw it in HAM RADIO!




ing holes and a long lead wire make the Genesis module easy to install and use. Modules bolt directly to almost any secure surface and produce power even in low or diffused light. Power specifications for the Genesis include: voltage at maximum power, 14.5 VDC; current at maximum power, 0.35 amperes; open-circuit voltage, 20.8 VDC; and short-circuit current, 0.435 amperes. Carrying a one-year warranty and retailing for under \$100, its advanced technology provides an affordable solar alternative accessible to everyone.

For more information, contact ENCON Corporation, 27600 Schoolcraft, Livonia, Michigan 48150.

Circle 302 on Reader Service Card.
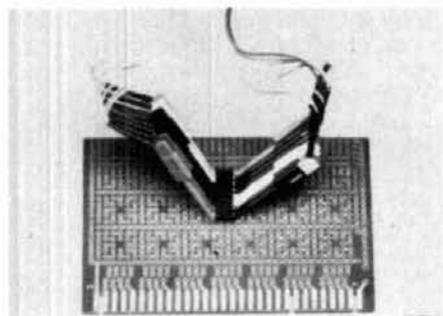
## pico hook adapter with wire/cable plug-on capability

Designed specifically for narrow test contact access, the E-Z HOOK P-25 "pico Hook" adapter features an ultra-thin blade and housing to allow connector stacking and ease of use, while allowing the flexibility of independent wire and cable assembly.



Incorporated into the design is a one-piece, gold-plated beryllium copper conductor and hook for assured signal accuracy, qualified to MIL-G-45204. The P-25 permits connection to 0.025-inch square or 0.030-inch round push-on bumpers and is designed for connection directly to a single leg of a DIP or other components which have a maximum diameter of 0.025 inch.

Lightweight and Finger-eze Hypo Action permit hook-up to delicate wires where weight and leverage may otherwise damage components. The barrier on the tip prevents shorting between DIP legs. A durable plastic body and plunger, and stainless steel compression spring provide approximately eight ounces of contact pressure.

For details, contact E-Z hook, Inc., P. O. Box 450, Arcadia, California 91006-0450.

Circle 301 on Reader Service Card.

# Barry Electronics Corp.

WORLD WIDE AMATEUR RADIO SINCE 1950  
Your one source for all Radio Equipment!

For the best buys in town call:  
212-925-7000  
Los Precios Mas Bajos en  
Nueva York

KITTY SAYS: WE ARE NOW OPEN 7 DAYS A WEEK.  
Saturday & Sunday 10 to 5 P.M.  
Monday-Friday 9 to 6:30 PM Thurs. to 8 PM  
Come to Barry's for the best buys in town.



Barry's is Busting Out All Over with Summer Savings. Izzy, Toni, Kitty WA2BAP, Mark K2CON, Jan KB2RV

CU at FRAB, Swanton, NY Aug 28th  
CU at G2000, NY Aug 29th


## KENWOOD



R-600, R-1000, R-2000, TS-940/S/AT  
TS-430S, TR-3600A, TR-7950,  
TW-4000A, Kenwood Service/Repair,  
TH21/31/41/AT, TM-211A/  
411A & TS-711A/B11A

COMPU-FIRE EXTINGUISHERS  
EXL 5000E KITTY/AMTOR TERMINAL

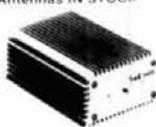VoCom/Mirage/Daiwa Large inventory of  
Tokyo Hy-Power Saxton Wire & Cable  
Amplifiers & Antennas IN STOCK



Computer Interfaces  
stocked: MFJ-1224  
AEA CP-1, PKT-1, DR.DX  
CP-100, ATU, Dr. QSO,  
Morse University

MICROLOG-AIR I, Air Disk,  
SWL, Morse Coach  
KANTRONICS  
UTU, Interface II, Challenger

AEA 144 MHz  
AEA 220 MHz  
AEA 440 MHz  
ANTENNAS

BIRD  
Wattmeters & Elements  
In Stock

## Antennas

A-5  
Cushcraft  
Hustler  
KLM  
METZ  
Mini Products  
Mobility

FT-ONE, FT-980, FT-757GX, FRG-8800  
FT-726R, FRG-9600, FT-270RH, FT-2700RH

YAESU ICOM  
FT-107/703R IC2AT  
FT-2709FH IC202AT  
FT-1903 IC-04AT



FT-ONE, FT-980, FT-757GX, FRG-8800  
FT-726R, FRG-9600, FT-270RH, FT-2700RH

YAESU ICOM  
FT-107/703R IC2AT  
FT-2709FH IC202AT  
FT-1903 IC-04AT

ONV Safety belts-in stock

ICOM  
IC-R71A, IC-751, IC745, IC-27AH, IC-37A, IC-47A,  
IC-1271A, IC-217AH, IC-3200A, IC-471 AH, IC-735

SMART PATCH  
IC-5 Complex Antenna 5/10 SA Win Patch FM  
Transmitter to Your Telephone. Great For  
Telephone Call From Mobile to Base. Simple  
to Use. \$149.95

CELLULAR PHONES  
WELZ  
FLUKE 77 Multimeter

Nye MBVA 3 Kilowatt Tuner

SANTEC  
ST-222/UP  
ST-142/UP  
ST-442/UP  
ST-117

MFJ Models  
422, 949C, 1224 & 941D

MURCH Model  
2000 A  
HAM MasterTapes—  
Beta or VHS Tapes

HEIL EQUIPMENT IN STOCK

DIGITAL FREQUENCY COUNTERS  
Yaesu, Icom, Engineering  
Model TR-1000 0-1 GHz (20MHz)  
0-100 MHz 0-1 GHz (20MHz)

Long range Wireless  
Telephone for export in stock

BENCHER PADDLES,  
BALUNS, AUDIO FILTERS,  
IN STOCK

MIRAGE AMPLIFIERS  
ASTRON POWER SUPPLIES  
Alinco/Falcon Amps

New TEN-TEC  
2591HT, Corsair II, Argosy II, Century 22

Tri-Ex Towers  
By Gain Towers & Antennas, and  
Roteis will be shipped direct to you FREE of  
shipping cost

MAIL ALL ORDERS TO BARRY ELECTRONICS CORP., 512 BROADWAY, NEW YORK CITY, NY 10012.

## New York City's LARGEST STOCKING HAM DEALER COMPLETE REPAIR LAB ON PREMISES

"Aqui Se Habla Espanol!"

BARRY INTERNATIONAL TELEX 12-7670  
MERCHANDISE TAKEN ON CONSIGNMENT  
FOR TOP PRICES

Monday-Friday 9 A.M. to 6:30 P.M. Thursday to 8 P.M.  
Saturday & Sunday 10 A.M. to 5 P.M. (Free Parking)

AUTHORIZED DIST. MCKAY DYMEK FOR  
SHORTWAVE ANTENNAS & RECEIVERS.  
IRTILEX-Spring St Station

Subways: BMT-Prince St Station  
IND-F Train-Buy Station

Bus: Broadway #6 to Spring St.  
Path-9th St/6th Ave. Station.

Commercial Equipment  
Stocked: ICOM, MAXON,  
Midland, Standard, Yaesu,  
Yaesu. We serve  
hobbyists, business  
users, etc. Partials, motors,  
batteries, repeaters.

Local  
Ham Club  
Speaches  
Given

We Stock: AEA, ARRL, Alpha, Ameco, Antenna Specialists, Astatic,  
Astron, B & K, B & W, Bash, Bencher, Bird, Butternut, CDE, CES, Collins,  
Communications Spec. Connectors, Covercraft, Cushcraft,  
Daiwa, Dentron, Digimax, Drake, ETO (Alpha), Eimac, Encom, Heil,  
Sound, Henry, Hustler (Newtronics), Hy-Gain, Icom, KLM, Kantronics,  
Larsen, MCM (Daiwa), MFJ, J.W. Miller, Mini-Products, Mirage,  
Newtronics, Nye Viking, Palomar, RF Products, Radio Amateur Callbook,  
Robot, Rockwell Collins, Saxton, Shure, Telex, Tempo, Ten-Tec,  
Tokyo Ham Radio, Tronity TUBES, W2JAU, Waber, Wilson, Yaesu Ham and  
Commercial Radios, Vocom, Vixtron, Curtis, Tri-Ex, Wacom Duplexers,  
Repeaters, Phelps Dodge, Fanon Intercoms, Scanners, Crystals, Radio  
Publications.

WE NOW STOCK COMMERCIAL COMMUNICATIONS SYSTEMS  
DEALER INQUIRIES INVITED. PHONE IN YOUR ORDER. BE REIMBURSED

COMMERCIAL RADIOS stocked & serviced on premises.  
Amateur Radio Courses Given On Our Premises. Call  
Export Orders Shipped Immediately. TELEX 12-7670

## AR-200 XL MEDIUM DUTY ANTENNA ROTOR

Select a Heading - Antenna  
Turns and Stops Automatically.



## SIDEBAND SQUELCH

- Fits inside most HF-SSB transceivers
- Requires human voice to activate
- Ignores static, noise and heterodynes
- On/off switch only—no adjustments!
- Connects to audio leads and 9-12 VDC
- Fully assembled and tested \$99.95
- Complete with comprehensive manual
- Used worldwide in commercial and military transceivers

CMC COMMUNICATIONS  
5479 Jetport, Tampa, FL 33614 (813) 885-3996

177

## MICROWAVE EQUIPMENT

RMLA - 2.3  
Single Stage, Low Noise  
Gas Fet Amplifier  
\$60.00

Optimum Transistor Noise Figure less than 5 dB,  
Associated Gain Greater Than 15dB at 2.3 GHz.  
Source/Load must be 50 ± 10 ohm Non-Resistive.  
SMA Connectors. Requires ±5VDC Power with  
-5VDC present when +5VDC applied. Power Supply  
and Sequencing is not supplied. Zener Protection.  
Unenclosed on 2" x 2" PC Board

Write for Price/Delivery for any frequency from 1 to 8  
GHz. Also VCO's, Signal Generators, Detectors, At-  
tenuators, Filters, Mixers, and Converters

Price includes Shipping and Insurance when paid by  
check or money order. Charge or C.O.D. orders,  
F.O.B., Brookfield, MO

ROENSCH MICROWAVE  
R.R. 1, Box 156B,  
BROOKFIELD, MISSOURI 64628

178

# MEMO

from the desk of  
THE PUBLISHER

**Skip Tenney, W1NLB**  
The Ham Radio Publishing Group

## IS YOUR HAMSHACK COMPUTERIZED?

The modern home computer, with some priced at less than \$150, is certainly one of the most exciting and challenging new items to be offered to the Radio Amateur in many years. These machines are such a logical extension of our Amateur activities, that it's a wonder that it has taken some of us as long as it has to get involved.

Thousands of hams are using these new machines to do everything from handling their logging and QSLing and as CW, RTTY and ASCII terminals to doing many of their routine station calculations in areas such as antenna and circuit design. Others are now able to do their own propagation forecasting with MUF and greyline programs. It's all mindboggling. We have just begun to see the tip of what is yet to come in the months and years ahead.

Whether you are merely contemplating the purchase of your first computer or you are an experienced user, Ham Radio's Bookstore wants to help you in this important new area. We have selected a number of the more interesting new programs which have been written for Amateur use, along with some excellent books to help you learn more.

Sincerely,

Skip Tenney, W1NLB

# ham radio magazine

# BOOKSTORE



**NOW WITH  
COMPUTER DISKS**

## COMPUTER PROGRAMS FOR THE RADIO AMATEUR

by Wayne Overbeck, N6NB, and Jim Steffen, KC6A

Here's the first source book of computer programs for the Radio Amateur. Besides covering computer basics, this book gives you programs that will help you log, determine sunrise/sunset times, track the Moon's path across the sky, use Greyline propagation and set up record systems for WAS, DXCC and VUCC, or any other award. You can either buy the book alone or you can buy the book with the programs already on disk. Take full advantage of your computer with this well written source book. ©1984, 1st edition, 327 pages.

### Program Listing

**Data Base Mgmt.**  
Logs, Awards Data Base, Gridlocator  
**Latitude/Longitude Programs**  
Data File, Beamheadings, DX Display, Sunrise Ct  
Greyline, DX Checker  
**Contest and Duping**  
Dupechecker, General Contest Logger,  
Field Day Logger, Sweepstakes Logger, Log Pri  
**Antenna Programs**  
Antenna Scaler, Matching Evaluator, Vertical Pat  
Plotter  
**EME**  
EME System Calculator, Sky Locator, Moontrack

- HA-0657 **Softbound \$16.9**
- HA-0657 with program disk **\$29.9**  
specify computer (see list below)
- Program disk alone **\$19.9**

Programs available for: Apple II (DOS and CP/M), IBM (DOS), TRS-80 Model I and Model III and Commodore C-64. Please mark your order with the program disk you want.



By  
**Chip Lohman  
NN4U**

AMATEUR RADIO COMPUTER SOFTWARE

## ANTENNA DESIGN

This self-prompting program covers dipoles, Yagis, long wires, rhombics, quads, loops, verticals and other antennas. You simply enter the frequency you are designing an antenna for, the antenna you want to make, and the computer will give you all the initial design specifications you need. The results can be stored on disk for permanent retention.

- HD-AD (For C-64) **\$9.95**

## CONTEST LOG

This disk contains four different contest programs; ARRL Sweepstakes, Field Day, Universal WW Contest log, plus a dupe checking routine. Each program is designed for real time use. It automatically enters date, time, band and serial number for each contact. A 24-hour clock is displayed at the top of the VDT screen. When the contest is over, the program will print your results listing all duped and scored contacts in serial sequence with all the necessary information as well as completed score at the bottom of the page.

- HD-CL (For C-64) **\$24.95**

## SUPER LOG

Super log gives you all the advantages of a computerized data base without significantly changing the traditional log format. For contesters, Super Log can be configured to either manually or automatically enter serial number as well as time of contact. Make an error and you can easily go back and edit the entry. Super Log also allows you to print out either selected contents or the whole log. Will print QSLs. Easy to modify.

- HD-SL (For C-64) **\$19.95**

## PROPAGATION CHART

Invaluable addition to any Hamshack. The Propagation Chart allows you to determine the maximum usable frequency (MUF) and the optimum frequency (FOT) between your QTH and any spot on the globe. You can get either a screen display, a printed tabular list over several days, or a printed graph of MUF and FOT. You also get automatic beam headings and distance to the DX station. Covers 160-10 meters and the new WARC bands.

- HD-PC (For C-64) **\$16.95**

## STAR 1.0 DESIGN PROGRAM

by Randall Rhea



STAR, S-parameter Two part Analysis Routine, is a professional engineering program designed to help analyze elec-

tronic circuits. It is particularly helpful in frequency domain analysis of RF and microwave circuits. To use STAR, you input circuit information by component; inductors, resistors, capacitors, transformers, transmission lines, two port data and several two port manipulations. STAR will then give you S-parameter data for each requested frequency in tabular or plot form. You can also use STAR to optimize component values for maximum circuit performance. This program is definitely not for electronic beginners. Engineers and serious hams, however, will find STAR to be an invaluable design tool.

- RR-IBM program for IBM **\$99**
- RR-C-64 program for Commodore C-64 **\$99**
- RR-AP program for Apple II **\$89**
- RR-KP program for KayPro **\$89**

## COMPUTERIZED DX EDGE

Generate your own Greyline display.

Xantek has adapted their best selling DX Edge to the computer world and it comes at a very reasonable price. This computerized operating aid brings into your ham shack the ability to know and predict when and where DX is going to appear. When you are using the program, the computer will automatically update the information as the sun progresses across the face of the Earth. To make the computerized DX Edge even easier to use, the display is keyed to the DXCC list and the 40 CQ zones. Disk and documentation are just \$34.95. This is something you've GOT to have! ©1985.

- XN-C64 (For Commodore C-64) **\$34.95**



## RF NOTES

by John Simmons, W6MDI

Here's an easy way to get answers for often asked electronics questions. RF NOTES contains programs written by broadcast engineers that answer: dB conversion, to convert voltage, current or power levels to dB, dBm conversions, converts voltages or power levels to dBm and dBm to voltage or power, VSWR calculations, calculates VSWR and return loss when both reflected and incident powers are known; Filter design, 14 different filter configurations including schematics (6 low pass, 4 high pass, 2 band pass and 2 band elimination circuits); Basic Microstrip and basic strip line design; and resonant circuits, design parallel and series resonant circuits, PI, capacitive impedance divider and inductive impedance divider. This disk is an invaluable reference for all Radio Amateurs.

- E-RF (IBM PC only) \$59.95**

## CONTENDER II LOGGING DATABASE (Commodore C-64)

This Commodore C-64 program will meet just about every logging need you can imagine. It can be used as a contest log, general log or dupe checker and can be used for all band WAS, WAZ or DXCC. The storage disk holds up to 2,000 exchanges and can be edited and updated simply and easily. Each entry contains callsign, signal reports,

automatic or manually entered time and date, band and mode as well as name and QTH. Contender will also print QSL's, mail labels and contest dupe sheets. The Content USA-CA (three disks) is a Worked All County data base that saves time and hassle and a tremendous amount of paperwork.

- CT-C \$34.**

Basic Contender (C-64) 1 disk

- CT-CUSA \$49.**

Contender Plus USA-CA (C-64) 3 disks

## RTTY MAILBOX MSO for Vic 20 and C-64 Computers

Here's a super user friendly software package that turns Commodore home computer into a powerful, easy-to-use message handling system. Messages can be stored, read or deleted by either incoming RTTY signals or by using the computer's keyboard. Each message is listed in a direct by file name, along with date and time of message initiation. The Basic/Assembly language software combines his speed with user friendly features and fully controls your transmitter and receiver with automatic identification, an optional special message and automatic transmission of date and time during MSO use. You can also use this program to operate direct RTTY and 60, 67, 75 or 100 wpm Baudot or 110 baud ASCII. Vic 20 needs 24k of memory use this program.

- VC-CP Use with AEA CP1 interface & equiv. \$79.**
- VC-MF Use with MFJ interface & equiv. \$79.**
- VC-KT Use with Kantronics interface & equiv. \$89.**

## AMPRO SOFTWARE FOR THE IBM PC

Edited by E.B. Rough, KB3GX


Programming by Ron Nord, N3AKP

These four programs have been written with the Active Amateur in mind and are designed to greatly simplify record keeping chores. You simply enter basic QSO data; call, prefix, country, state, or zone, date, RST and mode. The program then adds the contact to the disk data base. You can review your current status of stations worked, confirmed or verified at a glance. You can also print up a "wish list" to give to your friends who are helping you find those missing stations. The DXCC and 5 band DXCC lists are current through January 1, 1985 and can be easily updated should any new countries be added. These programs are a great value at a good price and represent a major time saver.

- AMP-DXCC (IBM PC only) \$29.95**  
DXCC Program
- AMP-5CC (IBM PC only) \$29.95**  
5 Band DXCC Program
- AMP-WAZ (IBM PC only) \$29.95**  
CQ Worked All Zones
- AMP-WAS (IBM PC only) \$29.95**  
ARRL Worked All States



## SATELLITE TELEVISION RECEIVER SEMIKIT

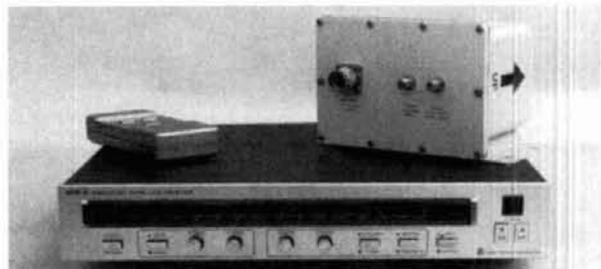

with dual conversion downconverter

### FEATURES:

- Infrared remote control tuning
- AFC, SAW filter
- RF or video output
- Stereo output
- Polorator controls
- LED channel & tuning indicators

Install six factory assembled circuit boards to complete.

<b>SEMIKIT</b>	<b>\$300.00</b>
Completed downconverter add	100.00
Completed receiver and downconverter add	150.00

### JAMES WALTER SATELLITE RECEIVER

2697 Nickel, San Pablo, CA 94806 ✓ 179 Tel. 415-724-0587

## ORR BOOKS



### BEAM ANTENNA HANDBOOK

by Bill Orr, W6SAI and Stu Cowan, W2LX

The Beam Antenna Handbook, first published in 1955, has been completely revised and updated with the latest information on Beam Antenna design. Computer designed Yagis give maximum gain in minimum space. New info on Yagi HF and VHF beams and dimensions on beams for 10, 18 and 24 MHz WARC bands. Everything you need to know about beam design, construction and operation. 204 illustrations. 268 pages. 1st edition. ©1985.

RP-BA Softbound \$9.95

### SIMPLE LOW-COST WIRE ANTENNAS

by Bill Orr, W6SAI

Learn how to build simple, economical wire antennas. Apartment dwellers take note! Fool your landlord and your neighbors with some of the "invisible" antennas found here. Well diagrammed. 192 pages. ©1972. 2nd edition.

RP-WA Softbound \$7.95

### THE RADIO AMATEUR ANTENNA HANDBOOK

by William I. Orr, W6SAI and Stuart Cowan, W2LX

Contains lots of well illustrated construction projects for vertical, long wire, and HF/VHF beam antennas. There is an honest judgment of antenna gain figures, information on the best and worst antenna locations and heights, a long look at the quad vs. the yagi antenna, information on baluns and how to use them, and new information on the popular Sloper and Delta Loop antennas. The text is based on proven data plus practical, on-the-air experience. 190 pages. ©1978. 1st edition.

RP-AH Softbound \$7.95

### ALL ABOUT CUBICAL QUAD ANTENNAS

by Bill Orr, W6SAI — New 3rd Edition

**Includes NEW data for WARC bands**

The cubical quad antenna is considered by many to be the best DX antenna because of its simple, lightweight design and high performance. You'll find quad designs for everything from the single element to the multi-element monster quad. There's a wealth of data on construction, feeding, tuning, and mounting quad antennas. 112 pages. ©1982. 3rd edition.

RP-CQ Softbound \$6.95

Please add \$1.50 for one book, \$2.50 for two or more books to cover shipping and handling.

**Ham Radio's Bookstore** Greenville, NH 03048



The monthly magazine with a natural blending of two popular hobbies — Ham Radio and Computers

- ★ Articles on Ham Radio & Most Personal Computers
- ★ Hardware & Software Reviews
- ★ Various Computer Languages
- ★ Construction Articles
- ★ Much Much More...

*"...received my moneys worth with just one issue..."*

—J. Trenbick

*"...always stop to read CTM, even though most other magazines I receive (and write for) only get cursory examination..."*

—Fred Blechman, K6UGT

U.S.A.....	\$15.00 for 1 year
Mexico, Canada .....	\$25.00
Foreign .....	\$35.00(land) - \$55.00(air)
(U.S. funds only)	
Permanent (U.S. Subscription) .....	\$100.00
Sample Copy .....	\$3.50



Circulation Manager

1704 Sam Drive

Birmingham, Alabama 35235

Phone 205/854-0271

Name \_\_\_\_\_

Call Sign \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_ Phone \_\_\_\_\_

Date \_\_\_\_\_

Signature \_\_\_\_\_

✓ 180

# NCG Co. NEW-TECHNOLOGY HIGH-QUALITY

AFFORDABLE TRANSCEIVERS FOR ALL. WINNERS IN COMPARISON HANDS DOWN!

## 10/160 M HF TRANSCEIVER



## 40-15-6 M NEW TRI-BANDER



## 15 M 15 METER MOBILE



JUST SLIGHTLY AHEAD! WITH THE QUALITY YOU HAVE ALWAYS LOOKED FOR!

4 MEMORYS - 3 WAY AUTO SCAN, DUAL VFO, IF SHIFT, CW-W, 400 Hz. CW-N 200 Hz. ALL 9 BANDS PLUS MARS. BUILT IN AC/DC POWER. SSB. CW OR RTTY. I.F. TUNE 3-STEP TUNING SPEED, 200 WATT PEP, MICROPHONE IMPEDANCE 600-50K OHM HAND MIC. INCLUDED.

40, 15 AND 6 METERS ARE YOUR BASE STATION OR MOBILE WITH AC/DC BUILT IN POWER SUPPLY CW-N 200 Hz OR USB, 2.S0239 ANTENNA CONNECTORS, HAND MIC, BUILT IN TV FILTER LITTLE TO NO TV INTERFERENCE, 20 WATTS PEP, MARS ON 40 AND 6 METERS.

A GREAT QRP RIG WITH THE BIG RIG SIGNAL, 2 WATTS OR 10 WATTS OUT, BUILT IN CW SIDE TONE, DIGITAL DISPLAY, HAND MIC. TOP MOUNTED SPEAKER. MOBILE BRACKET, RIT OR FINE TUNE TX&RX  $\pm 4$ KHz, 21 TO 21.450 MHz SIGNAL TO NOISE MORE THAN 10dB DOWN.

SPECIAL

SPECIAL

SPECIAL

90 DAY WARRANTY ON ALL TRANSCEIVERS - DIRECT FROM NCG OR YOUR DEALER

WE HAVE 1.2 GHz BASE/REPEATER & MOBILE ANTENNAS

1275 N. Grove Street, Anaheim, CA 92806 (714) 630-4541

181

NOTE: PRICES AND SPECIFICATIONS SUBJECT TO CHANGE WITHOUT NOTICE OR OBLIGATION




### TOUCHTONE™ DECODER KIT



MODEL TTK  
\$22.95

- SSI 201 DTMF Receiver
- Receive all 16 DTMF digits
- No additional filtering
- Output BCD or hex format
- Low power (29ma @ 12V)
- Kit includes 3.58Mhz crystal, 22 pin IC socket, resistor, capacitors, data sheet and schematics

### 4 DIGIT SEQUENCE DECODER

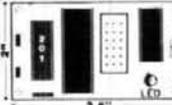

WIRED & TESTED - MODEL TSD  
\$59.95

- Completely wired & tested
- User programmable
- LED status indicator
- Open collector output
- Control relays: mute audio
- Control link on/off
- Custom IC insures high reliability & small size!
- Fits inside most rigs - runs on 12 VDC (35ma)
- Over 1500 different codes!


- Makes excellent private call on busy repeaters!
- Use it to turn on audio or sound an alarm
- Momentary and latching outputs

MasterCard and Visa accepted, or send check/M.O. Cal. address add 6%, price includes shipping USA. Send to:

ENGINEERING CONSULTING  
583 CANDLEWOOD ST., BREA, CA 92621  
TEL: 714-671-2009

### ENGINEERING CONSULTING INTRODUCES
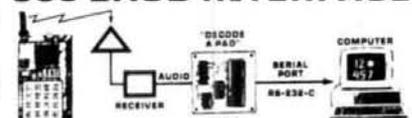
## TOUCHTONE™ DTMF to RS-232-C 300 BAUD INTERFACE



- Use your computer to decode DTMF touchtones.
- Receive all 16 digits as fast as they can be transmitted.
- Easily program your computer in BASIC to decode multi-digit "strings", display digits, sound alarms, observe secret codes, control relays, remote base
- Simple to use, just provide +12 VDC and audio, hook two wires to the RS-232-C serial input on your computer, enter a simple BASIC program and begin to decode.
- Sample BASIC program and instructions included.
- LED indicator

Model DAP-1 "Decode-A-Pad"  
Wired and Tested \$89.95

Includes shipping USA. Cal. addresses add 6%.

VISA and MasterCard accepted, or send check/M.O. to  
ENGINEERING CONSULTING  
583 CANDLEWOOD ST., BREA, CA 92621  
714 / 671-2009

### ENGINEERING CONSULTING INTRODUCES

## 'REMOTE A PAD'™ MODEL RAP-1



2 FOUR DIGIT DTMF DECODERS, PLUS 16 DIGIT KEYPAD CONTROL

TUNE THE WORLD FROM YOUR HANDHELD VHF/UHF RADIO

- Audio tones from any source are converted to solid state switches when control and 16 digit keypad are added to other device
- Some examples you can control include the Pro-Search™ Rotator (rotatable beam remote), ICOM IC-701 or ICOM IC-711 when using the RM-2 controller, ICOM FP-20, 251, Aiden PCS-8000, handhelds such as Yaesu FT-208, FT-708, ICOM IC-207A1 and many more.
- Anything you can do manually with your 16 digit keypad, the RAP-1 will do remotely using audio touch tones from any source!
- Two (four digit) programmable access codes are used to operate relays in other on-off functions.

Model RAP-1  
\$149.95

- LED decoder status indicators and momentary push steady state decoder outputs are provided
- 20 gold pin card edge connector, 16 pin dip socket and ribbon cable are included
- An LM555 low power drain (30ma) 5.5V Zener Decoder
- Four eight wires (4 rows and 4 columns) in parallel with the existing keypad of the radio you wish to control remotely. Connect each wire to a switch, 12 volts D.C. and you are in control!
- The dual 8 digit decoders will turn your links on and off using your programmable access code
- Detailed interface diagrams and instructions included with purchase. Interface cable for Pro-Search™ \$99.95 (shown in ad. 80041)

### ICOM IC-02AT USER'S "AUDIO BLASTER"™ MODULE

- Module installs inside the radio in 10 minutes
- Boosts audio to nearly 1 watt!
- Low power drain (3ma stand by)
- Complete step by step instructions included
- Corrects the LOUD audio problem!
- Drive external speakers to full volume
- Main signals with the navigation!



Model AB-1 \$19.95  
Price includes postage and handling, U.S.A. CA res. add 6%

Send check or money order to  
ENGINEERING CONSULTING  
583 CANDLEWOOD ST., BREA, CA 92621  
(714) 671-2009

## ALL BAND TRAP "SLOPER" ANTENNAS!

FULL COVERAGE! ALL BANDS! AUTOMATIC SELECTION with PROVEN Weatherproof sealed Traps 18 Ga. Copperweld Wire! GROUND MOUNT SLOPERS - No Radials needed! Ground to rod, or house water faucet! Connect Top to Trees, Buildings, Poles, etc at ANY angle from Straightup to 60 degrees for excellent "SLOPER" DX. Antenna Gain or bend it anywhere you need to! 2000 Watt PEP Input, Max. Permanent or portable Use. Installs in 10 minutes. SMALL - NEAT - ALMOST INVISIBLE - No one will know you have a Hi-Power DX Antenna. Ideal for CONDO'S APARTMENTS - RESTRICTED AREAS - Pre-tuned for 2-1 or less SWR over ALL bands (except 80-160-300kc)! No adjustments needed - EVER! 50 ft RG-58U Coax feedline and PL-259 connector - Built in lightning arrester - ready to hookup! FULL INSTRUCTIONS! COMPLETELY ASSEMBLED

SEND FULL PRICE FOR POSTPAID INSURED DEL. IN USA, order using VISA - MASTER CARD AMER. EXP. Ph 1-308-236-5333. We ship in 2-3 days. 1 year guarantee - 10 day money back trial. FREE INFO AVAILABLE ONLY FROM WESTERN ELECTRONICS Dept. AQ-7 Kearney, Nebraska, 68847

No. 1080S	80-40-20-15-10	-1 trap	49 ft.	----	\$49.95
No. 1040S	40-20-15-10	-1 trap	26 ft.	----	\$48.95
No. 1020S	20-15-10	-1 trap	13 ft.	----	\$47.95
No. 1016S	160-80-40-20-15-10	-2 trap	83 ft.	----	\$79.95

# HAM MART

*Ham Radio's guide to help you find your local dealer*

## California

**C & A ROBERTS, INC.**  
18511 HAWTHORN BLVD.  
TORRANCE, CA 90504  
213-370-7451  
24 Hour: 800-421-2258  
Not The Biggest, But The Best —  
Since 1962.

**FONTANA ELECTRONICS**  
8628 SIERRA AVENUE  
FONTANA, CA 92335  
714-822-7710  
714-822-7725  
The Largest Electronics Dealer in San Bernardino County.

**JUN'S ELECTRONICS**  
3919 SEPULVEDA BLVD.  
CULVER CITY, CA 90230  
213-390-8003  
800-882-1343 Trades  
Habla Espanol

## Connecticut

**HATRY ELECTRONICS**  
500 LEDYARD ST. (SOUTH)  
HARTFORD, CT 06114  
203-527-1881  
Call today. Friendly one-stop shopping  
at prices you can afford.

## Delaware

**AMATEUR & ADVANCED COMMUNICATIONS**  
3208 CONCORD PIKE  
WILMINGTON, DE 19803  
(302) 478-2757  
Delaware's Friendliest Ham Store.

**DELAWARE AMATEUR SUPPLY**  
71 MEADOW ROAD  
NEW CASTLE, DE 19720  
302-328-7728  
800-441-7008  
Icom, Ten-Tec, Microlog, Yaesu,  
Kenwood, Santec, KDK, and more.  
One mile off I-95, no sales tax.

## Florida

**AMATEUR ELECTRONIC SUPPLY**  
1898 DREW STREET  
CLEARWATER, FL 33575  
813-461-4267  
Clearwater Branch  
West Coast's only full service  
Amateur Radio Store.  
Hours M-F 9-5:30, Sat. 9-3

**AMATEUR ELECTRONIC SUPPLY**  
621 COMMONWEALTH AVE.  
ORLANDO, FL 32803  
305-894-3238  
Fla. Wats: 1 (800) 432-9424  
Outside Fla: 1 (800) 327-1917  
Hours M-F 9-5:30, Sat. 9-3

**AMATEUR RADIO CENTER, INC.**  
2805 N. E. 2ND AVENUE  
MIAMI, FL 33137  
305-573-8383  
The place for great dependable  
names in Ham Radio.

## Hawaii

**HONOLULU ELECTRONICS**  
819 KEEAUMOKU STREET  
HONOLULU, HI 96814  
(808) 949-5564  
Serving Hawaii & Pacific area for 51  
years. Complete lines of Amateur equip-  
ment, accessories and parts.

## Illinois

**ERICKSON COMMUNICATIONS, INC.**  
5456 N. MILWAUKEE AVE.  
CHICAGO, IL 60630  
312-631-5181  
Hours: 9:30-5:30 Mon, Tu, Wed & Fri;  
9:30-8:00 Thurs; 9:00-3:00 Sat.

## Indiana

**THE HAM STATION**  
808 NORTH MAIN STREET  
EVANSVILLE, IN 47710  
812-422-0231  
Discount prices on Ten-Tec, Cubic,  
Hy-Gain, MFJ, Azden, Kantronics,  
Santec and others.

## Massachusetts

James Millen Components by  
**ANTENNAS ETC.**  
16 HANSOM ROAD  
ANDOVER, MA 01810  
617-475-7831  
Bezels, binding posts, capacitors, con-  
densers, chokes, coils, ceramics, H.V.  
connectors, plate caps, hardware  
knobs, dials, scopes and grid dippers.  
Inquire SASE or visit.

**TEL-COM, INC.**  
675 GREAT ROAD, RTE. 119  
LITTLETON, MA 01460  
617-486-3400  
617-486-3040  
The Ham Store of New England  
You Can Rely On.

## Michigan

**ENCON PHOTOVOLTAICS**  
Complete Photovoltaic Systems  
27600 Schoolcraft Rd.  
Livonia, Michigan 48150  
313-523-1850  
Amateur Radio, Repeaters, Satellite,  
Computer applications.  
Call Paul WD8AHO

## Nevada

**AMATEUR ELECTRONIC SUPPLY**  
1072 N. RANCHO DRIVE  
LAS VEGAS, NV 89106  
702-647-3114  
Dale Porray "Squeak," AD7K  
Outside Nev: 1 (800) 634-6227  
Hours M-F 9-5:30, Sat. 9-3

**JUN'S ELECTRONICS**  
460 E. PLUMB LANE — 107  
RENO, NV 89502  
702-827-5732  
Outside Nev: 1 (800) 648-3962  
Icom — Yaesu Dealer

## NEW YORK

**ADIRONDACK ELECTRONICS, INC.**  
1991 CENTRAL AVENUE  
ALBANY, NY 12205  
518-456-0203  
Amateur Radio for the Northeast since  
1943.

**BARRY ELECTRONICS**  
512 BROADWAY  
NEW YORK, NY 10012  
212-925-7000  
New York City's Largest Full Service  
Ham and Commercial Radio Store.

**VHF COMMUNICATIONS**  
915 NORTH MAIN STREET  
JAMESTOWN, NY 14701  
716-664-6345  
Call after 7 PM and save! Supplying all  
of your Amateur needs. Featuring ICOM  
"The World System." Western New  
York's finest Amateur dealer.

**Dealers:** *YOU SHOULD BE HERE TOO!*  
*Contact Ham Radio now for complete details.*

# Amateur Radio Dealer

## Ohio

**AMATEUR ELECTRONIC SUPPLY**  
28940 EUCLID AVE.  
WICKLIFFE, OH (CLEVELAND AREA)  
44092  
216-585-7388  
Ohio Wats: 1 (800) 362-0290  
Outside Ohio: 1 (800) 321-3594  
Hours M-F 9-5:30, Sat. 9-3

**UNIVERSAL AMATEUR RADIO, INC.**  
1280 AIDA DRIVE  
REYNOLDSBURG (COLUMBUS), OH  
43068  
614-866-4267  
Featuring Kenwood, Yaesu, Icom,  
and other fine gear. Factory author-  
ized sales and service. Shortwave  
specialists. Near I-270 and airport.

## Pennsylvania

**HAMTRONICS,  
DIV. OF TREVISE ELECTRONICS**  
4033 BROWNSVILLE ROAD  
TREVISE, PA 19047  
215-357-1400  
Same Location for 30 Years.

**LaRUE ELECTRONICS**  
1112 GRANDVIEW STREET  
SCRANTON, PENNSYLVANIA 18509  
717-343-2124  
Icom, Bird, Cushcraft, Beckman,  
Larsen, Hustler, Astron, Belden,  
Antenna Specialists, W2AU/W2VS,  
AEA, B&W, Amphenol, Saxton, J.W.  
Miller/Daiwa, Vibroplex.

**THE VHF SHOP**  
16 S. MOUNTAIN BLVD., RTE. 309  
MOUNTAINTOP, PA 18707  
717-474-9399  
Lunar, Microwave Modules, ARCOS,  
Astron, KLM, Tama, Tonna-F9FT,  
UHF Units/Parabolic, Santec, Tokyo  
Hy-Power, Dentron, Mirage,  
Amphenol, Belden

## Texas

**MADISON ELECTRONICS SUPPLY**  
3621 FANNIN  
HOUSTON, TEXAS 77004  
713-520-7300  
1 (800) 231-3057  
Christmas?? Now??

## Wisconsin

**AMATEUR ELECTRONIC SUPPLY**  
4828 W. FOND DU LAC AVE.  
MILWAUKEE, WI 53216  
414-442-4200  
Wisc. Wats: 1 (800) 242-5195  
Outside Wisc: 1 (800) 558-0411  
M-F 9-5:30  
Sat 9-3

## AZOTIC INDUSTRIES

2026 W. BELMONT  
CHICAGO, IL 60618  
312-975-1290

### ELECTRONIC COMPONENTS & SUPPLIES

- RF CONNECTORS
- UG CONNECTORS
- AUDIO CONNECTORS
- LINEAR IC'S
- DIGITAL IC'S
- TRANSFORMERS
- METERS
- COMPUTER CABLES
- DISKETTES
- IDC CONNECTORS
- D-SUBMINIATURE
- TEST EQUIP
- TRANSISTORS
- DIODES
- TRIM CAPS
- RELAYS
- SWITCHES
- TOOLS

WRITE FOR FREE CATALOG  
VISIT OUR RETAIL STORE  
HRS. MON-FRI 10-5 SAT 10-2  
PHONE ORDERS WELCOMED  
312-975-1290

✓ 182

## HAZER YOUR ROHN 25 G Tower

- Antenna and rotator mount on HAZER, complete system trams tower in vehicle upright position.
- Safety lock system on HAZER operates while raising-lowering & normal position. Never can fall.
- Weight transferred directly to tower. Winch cable used only for raising & lowering. Easy to install and use.
- Will support most antenna arrays.
- High quality materials & workmanship.
- Safety - speed - convenience - smooth travel.
- Complete kit for 50' or less tower includes winch, cable, hardware and instructions.

Hazer 2-Heavy duty alum., 12sq ft. load \$297.00 p.pd.  
Hazer 3-Standard alum., 8 sq ft. load 213.00 p.pd.  
Hazer 4-Heavy galv. steel, 16 sq ft. load 278.00 p.pd.  
Ball thrust bearing TB-25 for any of above 42.50 p.pd.

As an alternative, purchase a Martin M-13 or M-18 aluminum tower engineered specifically for the HAZER system.



GLEN MARTIN ENGINEERING INC.  
P.O. Box H 253 Boonville, Mo. 65233  
816-882-2734



✓ 183

## COMMODORE

**- USER WRITTEN SOFTWARE -**  
Supporting COMMODORE computers ONLY  
★ GAMES ★ UTILITIES ★ EDUCATIONAL ★  
**INVENTORY REDUCTION SALE**

\* Please note: You must mention Special Sales Offer #104 in order to get our sale prices.

★★ \* Sale Ends 9-30-85 \* ★★

Software Collections	Reg	Sale
on DISK	10.00	8.00
on TAPE VIC-20 or Commodore 64	10.00	5.00
* Please note we are phasing out our tape stock *		
10 foot shielded Serial Cable	10.00	8.00
15 foot shielded Serial Cable	15.00	12.00

### P.D.L. Program Manual

For COMMODORE 64 or VIC-20 software volumes 1 thru 12 only. \$5 with purchase of 5 or less collections. \$3 with purchase of 5-9 collections. Free with purchase of 10 or more collections. (Limit one free per customer)

### COMAL STARTER PAK Reg \$35

A 4 disk set for the beginner or programmer. Sale \$20.00

### ★ ★ HEAD CLIPS - for your HT ★ ★

Specify Boom Mike or Speaker Mike version only \$15 each

Shipping and Handling Charges

US/Canadian Add \$3. Foreign Orders Add \$5. U.S. Funds Only

CHECK MO's VISA & MC accepted. No COD's or P.O.'s

**FOR A CATALOG** to be sent 1st class mail with listings of all collections, helping hints and 21 free programs, send \$1.00 U.S. / \$2.00 Foreign. Catalog request without payment will be sent bulk mail (3-6 wks. U.S. only)

### 'PUBLIC DOMAIN', INC.

5025 S. Rangeline Rd., W. Milton, OH 45383

10:00 a.m. - 5:00 p.m. EST - Mon. thru Fri.

(513) 698-5638 or (513) 339-1725

✓ 184

# RF TRANSISTORS

FRESH STOCK - NOT SURPLUS  
TESTED - FULLY GUARANTEED

P/N	2-30 MHz 12V (* = 28V)		Match Pr.
	Rating	Each	
MRF406	20W	\$14.50	\$32.00
MRF412,IA	80W	18.00	45.00
MRF421	100W	25.00	56.00
MRF421C	110W	—	60.00
MRF422*	150W	38.00	82.00
MRF426,IA*	25W	18.00	42.00
MRF428**	150W	55.00	125.00
MRF433	12.5W	12.00	30.00
MRF435*	150W	42.00	90.00
MRF449,IA	30W	12.50	30.00
MRF450,IA	50W	14.00	31.00
MRF453,IA	60W	15.00	35.00
MRF454,IA	80W	16.00	36.00
MRF455,IA	60W	12.00	28.00
MRF458	80W	20.00	46.00
MRF460	60W	18.00	42.00
MRF464*	80W	25.00	60.00
MRF466*	40W	18.75	48.00
MRF475	12W	3.00	9.00
MRF476	3W	2.75	8.00
MRF477	40W	11.00	25.00
MRF479	15W	10.00	23.00
MRF485*	15W	6.00	15.00
MRF492	90W	18.00	40.00
SRF2072	75W	15.00	33.00
SRF3662	110W	28.00	60.00
SRF3775	75W	15.50	34.00
SRF3795	85W	16.50	37.00
CD2545	50W	23.00	52.00
SD1076	70W	17.00	40.00
SD1451	50W	15.00	36.00

Selected High Gain Matched Quads Available

### VHF/UHF TRANSISTORS

Rating	MHz	Net Ea.	Match Pr.
MRF212	10W	136-174	\$16.00
MRF221	15W	136-174	10.00
MRF222	25W	136-174	14.00
MRF224	40W	136-174	13.50
MRF231	3.5W	66-88	10.00
MRF234	25W	66-88	15.00
MRF237	4W	136-174	3.00
MRF238	30W	136-174	12.00
MRF239	30W	136-174	15.00
MRF240	40W	136-174	18.00
MRF245	80W	136-174	28.00
MRF247	75W	136-174	27.00
MRF250	50W	27-174	20.00
MRF260	5W	136-174	7.00
MRF261	10W	136-174	9.00
MRF262	15W	136-174	9.00
MRF264	30W	136-174	13.00
MRF607	1.75W	136-174	3.00
MRF641	15W	407-512	22.00
MRF644	25W	407-512	24.00
MRF646	40W	407-512	28.50
MRF648	60W	407-512	33.00
2N3866*	1W	30-200	1.25
2N4427	1W	136-174	1.25
2N5591	25W	136-174	13.50
2N5642*	20W	30-200	13.75
2N5945	4W	407-512	10.00
2N5946	10W	407-512	12.00
2N6080	4W	136-174	6.25
2N6081	15W	136-174	7.50
2N6082	25W	136-174	8.90
2N6083	30W	136-174	9.30
2N6084	40W	136-174	11.75
TMOS FET			
MRF134*	5W	2-200	\$10.50
MRF137*	30W	2-200	22.50
MRF138**	30W	1.5-150	35.00
MRF150**	150W	1.5-150	80.00
MRF172*	80	2-200	65.00

Selected, matched finals for Kenwood, Yaesu, Icom, Atlas, etc. Technical assistance and cross-reference information on CD, PT, RF, SRF, SD P/Ns.


**QUANTITY DISCOUNTS AVAILABLE**  
**WE SHIP SAME DAY C.O.D./VISA/MC**  
INFORMATION AND CALIF. ORDERS: (619) 744-0728  
OUTSIDE CALIF. ORDER DESK: 800-854-1927



## RF PARTS

1320-16 Grand Ave., San Marcos  
California 92069 (619) 744-0728

# flea market

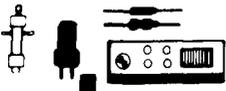

**RATES** Noncommercial ads 10¢ per word; commercial ads 60¢ per word **both payable in advance.** No cash discounts or agency commissions allowed.

**HAMFESTS** Sponsored by non-profit organizations receive one free Flea Market ad (subject to our editing) on a space available basis only. Repeat insertions of hamfest ads pay the non-commercial rate.

**COPY** No special layout or arrangements available. Material should be typewritten or clearly printed (**not** all capitals) and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** cannot check each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue.

**DEADLINE** 15th of second preceding month.

**SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

**CX7 REPAIRS.** 415-549-9210.

**LETTERING** and text for QSL pasteup and label usage. Stamp brings circular. Labelcraft, PO Box 412, W. Sand Lake, NY 12196.

**HOUSE READY FOR HAM.** Beautiful mountain top all brick 4 bedroom, 3 full bath home and radio site on one acre landscaped, private, with huge inground pool. Located 55 miles from Washington, DC and 60 miles from Baltimore, easy commute by Amtrack or van pools. Extremely energy efficient brick home, full basement and other extra rooms, radio room. All cable, poles, antennas, fire alarm system and intercom system stay. Must see to fully appreciate. Call or write to receive free written details of all features, \$250,000. (301) 371-7521. John Murray, Box 290, Jefferson, Maryland 21755.

**PROGRAMMED EPROMS & PROMS:** 82S23123, 82S126/129 fusible link \$6.00 each; 2708, 2716 (+5v), 2732 (+5v) EPROMS \$9.00 each postpaid. Send coding list, hexadecimal format to Douglas Hall, 6434 Melia Street, Springfield, VA 22150.

**CUSTOM MADE** embroidered patches. Any size, shape, colors. Five patch minimum. Free sample, prices and order

ing information. Hein Specialties, Inc., Dept. 301, 4202 N. Drake, Chicago, IL 60618.

**RECLAIM SILVER** from electronics scrap! Write RALTEC, 25884F Highland, Cleveland, OH 44143.

**COMPUTERIZE YOUR IC-720.** Keyboard frequency entry, 64 memories, scanning, (frequency, memory, and mode), many more features. Requires no interface, just cable — directions included. For Commodore 64. Cassette \$14.75, disk \$16.75, ppd. Cables also available. David Oliver, W9ODK, Rt. 2, Box 75A, Shevlin, MN 56676.

**CUSTOM EMBROIDERED** Emblems — Cloisonne' enameled pins, your design, low minimum, excellent quality, free booklet. A.T. Patch Co., Dept. 65, Littleton, NH 03561. (603) 444-3423.

**HAMSWAP Newsletter.** Send us your Free Ad. Include phone. Buy/Sell/Trade. Subscriber equipment discounts. 12 issues \$9.00. HamSwap, PO Box 420171, Sacramento, CA 95842.

**WINDMILL & TOWER:** 1978 Dunlite 2000 watt windmill, 110' Rohn 45G tower with new concrete anchors, 110V - 220 amp battery bank, converter, loading switch. Complete system only. \$4,995.00. (518) 623-9951. Box 196, HCR-01, Warrensburg, NY 12885.

**TRS-80 Model I/III/IV owners.** HF antenna design program calculated dimensions for dipole, Yagi, and quad antennas. \$14.95 (cassette) + \$2.00 s&h to Cynwyn, Dept. H, 4791 Broadway, Suite 2F, New York, NH 10034.

**MILITARY RADIOS:** CPRC-26 Manpack Radio (described in March 1985 Ham Radio). Transceives 46-54 MHz, with battery box, antenna, crystal, handset: \$22.50 apiece, \$42.50/pair, good condition. R-390A Receiver, 5-32 MHz all modes, 4 mechanical filters, meters sealed (government removed, operation unaffected): \$175 complete/checked; spare parts unit (80% complete, missing PTO/IF): \$65. Info SASE. CPRC-26 add \$4/unit shipping. R-390A shipping charges collect. Baytronics, Dept. HR, Box 591, Sandusky, Ohio 44870. 419-627-0460 evenings.

**FOR SALE:** Hallicrafters SX-100 communications receiver. Antique collectors item. Good condition. \$139 or best offer. Gerry Nemetz, W4NEX, 8202 Beechwood Drive, Lynchburg, VA 24502. (804) 239-7789.

**3-500Zs @ \$70.00 each,** new, 50 year collection tubes. Advice requirements, W5QJ, PO Box 13151, El Paso, TX (915) 532-2509.

**MINT ROBOT 400.** First sync modification. Instruction book and original box. 1 ship. \$275 firm. Jim Valentino, KW2W, PO Box 438, Mastic Beach, NY 11951.

**RUBBER STAMPS:** 3 lines \$4.50 PPD. Send check or MO to G. L. Pierce, 5521 Birkdale Way, San Diego, CA 92117. SASE brings information.

**CHASSIS** and cabinet kits. SASE K3IWK.

**IMRA,** International Mission Radio Association, helps missionaries. Equipment loaned. Weekday net, 14.280 MHz, 2-3 PM Eastern. Eight hundred Amateurs in 40 countries. Brother Frey, 1 Pryer Manor Road, Larchmont, NY 10538.

**ELECTRON TUBES:** Receiving, transmitting, microwave . . . all types available. Large stock. Next day delivery, most cases. Daily Electronics, PO Box 5029, Compton, CA 09224 (213) 774-1255.

**RTTY-EXCLUSIVELY** for the Amateur Teleprinter. One year \$7.00. Beginners RTTY Handbook \$8.00 includes journal index. P.O. Box RY, Cardiff, CA 92007.

**HOW TO CONVERT** any cassette tape player to a message sender and automatic IDer for repeater or base station. For complete plans send \$5.00 plus 22¢ stamps to: Jesse Hernandez, Box 322, Memphis, TN 38104 WB5MVP.

**NEEDED:** Schematic and alignment procedure for Swan 700CX Xcvr. Paul Migliore, AK2X, 1102 Drummond Ave., Asbury Park, NJ 07712.

**CABLE TV EQUIPMENT.** Jerrold, Hamlin, Zenith — many others. Factory Units/lowest dealer prices. Complete illustrated catalog \$2.00. Pacific Cable Co., Inc., 7325½ Reseda Blvd., Dept. 1004, Reseda, CA 91335. (818) 716-5914.

**WANTED:** Xtal 6M-FM transceiver (Regency, Genave, commercial, etc.). State asking price, condition, specifications. Barry Ornitz, WA4VZQ, 4740 Edens View Road, Kingsport, TN 37664.

**VIC-20** phone patch. Build your own simplex autopatch for less than \$50 using your own transceiver and VIC-20 or Commodore 64. For full documentation and program cassette tape, send \$20 to: KIE Enterprises, PO Box 72, Running Springs, CA 92382. (714) 867-7120.

**SELL** Cable TV descramblers, converters, remote tuners. Dealers wanted. Part or full time. Work from home. No experience necessary. Full details. P.G. Video Corp., 61 Gatchell St., Dept. HR, Buffalo, NY 14212.

**OLD RADIO** transcription discs wanted. Any size, speed. W7FZ, Box 724 HR, Redmond, WA 98073-0724.

**ANTIQUE RADIOS,** schematics, tubes and literature. Send SASE to VRSHR, 376 Cilley Rd., Manchester, NH 03103 for large list.

**FOR SALE:** Heath HW-101/P.S. \$225, HBO descrambler filter schematic \$2.00. SASE to J.C., PO Box 6349, Evansville, IN 47712.

**SIGNAL GENERATORS:** URM-25D, 10 kHz thru 50 MHz \$245.00; URM-26B, 4 MHz thru 405 MHz \$245.00; HP614A, 900 MHz thru 2100 MHz \$345.00; HP618B, 3.8 GHz thru 7.6 GHz \$375.00; HP608C 10 MHz thru 480 MHz \$345.00; TS-510/U, 10 MHz to 420 MHz \$295.00, all lab calibrated, have good stock so order today. We accept M/C, VISA, or check, FOB Otto. Immediate shipment. Phone Bill Slep 704-524-7519. Slep Electronics Company, Highway 441, Otto, NC 28763.

## Coming Events ACTIVITIES "Places to go..."

**KENTUCKY:** The Central Kentucky ARRL Hamfest, sponsored by the Bluegrass ARS, Sunday, August 11, 8 AM to 5 PM, Scott County HS, Longlick Road and US 25, Georgetown. Tech forums, license exams, awards and exhibits. Air conditioned facilities. Free outdoor flea market space. Tickets \$3.50 advance and \$4.00 at gate. Talk in on 76/16. For information or tickets SASE to Scott Hackney, K1ALE, 629 Craig Lane, Georgetown, KY 40324.

**PENNSYLVANIA:** The Tioga County Amateur Radio Club's 9th annual Hamfest, Sunday, August 18, Island Park, Blossburg, 9 AM to 5 PM. VE's will give walk-in exams. For information write TCARC, PO Box 56, Mansfield, PA 16933. Flea market, dealers, park and pool, snack bar. Admission \$3.00. Spouse and kids free. Talk in on 146-19/79, 146-52/52 and CB. For information: Durwood Learn, WB3DKZ, 11 Bryden Street, Wellsboro, PA 16901. (717) 724-5613.

**TEXAS:** The Austin ARC and the Austin Repeater Association in conjunction with the Texas VHF-FM Society announces the third annual Austin Summerfest, August 2, 3 and 4, Austin Marriott Hotel, I-35 and US 290, Austin. Seminars, QCWA hospitality suite, dealer displays. FCC exams for all classes Saturday. Ladie's programs. Austin's "Aquafest" is this same weekend and will provide additional entertainment. Registration \$5 advance, \$7 at the door. Persons under 18 admitted free. Swapfest tables available starting 6 AM Saturday at \$1 per table, limit two. Talk in on WA5YAN/R 146.34/94. For more information: Austin Summerfest, PO Box 13473, Austin, TX 78711.

**PENNSYLVANIA:** The 48th annual South Hills Brassponders and Modulators Hamfest, August 4, 9 AM to 4 PM, South Campus, Community College of Allegheny County, Pittsburgh. Tickets \$3 each. 2/\$5. Oscar, RTTY and packet radio forums. Flea market. Talk in on 146.13/73 and 146.52 simplex. For more information: Bill Gardiner, 4756 Child Drive, Pittsburgh, PA 15236.

**INDIANA:** The annual Bloomington Hamfest, Sunday, September 1, 147.18/78 repeater site, Vernal Pike off SR 37 bypass. 8 AM to 2 PM. Admission \$2.00. Food concession. No charge for setups, bring your own tables. For more information: Bob Myers, K9KTH, 306 S. Fairview Street, Bloomington, IN 47401. SASE or call (812) 332-1105.

**INDIANA:** The 6th annual Grant County Amateur Radio Club Hamfest, Sunday, August 11, 4H Fairgrounds, Marion. Doors open 8 AM. Refreshments, free parking, license exams. Table reservations \$2/8' table. Donation \$2.00 advance. \$3.00 gate. For more information SASE to WB9EAP, Brooks Clark, 2202 South Boots Street, Marion, IN 46953.

### Foreign Subscription Agents for Ham Radio Magazine

Ham Radio Austria  
Karin Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Ham Radio Belgium  
Sterehouze  
Brusselsesteenweg 416  
B-9219 Gent  
Belgium

Ham Radio Holland  
Postbus 413  
NL-7800 Ar Emmen  
Holland

Ham Radio Europe  
Box 2084  
S-194 02 Upplands Vasby  
Sweden

Ham Radio France  
SM Electronic  
20 bis, Ave des Clairons  
F-89000 Auxerre  
France

Ham Radio Germany  
Karin Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Canada  
Send orders to  
Ham Radio Magazine  
Greenville, NH 03048 USA  
Prices in Canadian funds  
1 yr. \$29.95, 2 yrs. \$53.30  
3 yrs. \$75.40

Ham Radio Italy  
Via Pordenone 17  
I-20132 Milano  
Italy

Ham Radio Switzerland  
Karin Ueber  
Postfach 2454  
D-7850 Loerrach  
West Germany

Ham Radio England  
c/o P.S.G.B.  
Alma House  
Crabtree Road  
Potters Bar  
Herts EN6 3JW  
England

Holland Radio  
143 Greenway  
Greenville, Johannesburg  
Republic of South Africa

**WASHINGTON:** Tacoma Hamfair, sponsored by the Radio Club of Tacoma. August 17 and 18, Pacific Lutheran University, Tacoma. Tech seminars, forums, travels and more. Large flea market. License exams, send 610 to W7BUN. Registration \$5.00. Dinner \$8.00. Flea market table \$15/day; \$20/2 days includes one registration. Register with Grace Tietzel, AD7S, PO Box 45079, Tacoma, WA 98445 or call Eva Anderson, WB7QNS, (206) 564-8347.

**OHIO:** 43rd annual Findlay Hamfest sponsored by the Findlay Radio Club at the Hancock County Fairgrounds. Sunday, September 8, 6:30 AM to 5 PM. Advance tickets \$3.00 by September 1. At the door \$4.00. Tables \$6.00 each. Outdoor flea market spaces \$3.00 each. Talk in on 147.75/15. For more information write Findlay Radio Club, PO Box 587, Findlay, Ohio 45839.

**MISSOURI:** The St. Charles Amateur Radio Club's Hamfest '85, August 25, St. Charles City Hall complex, 200 North 2nd Street, St. Charles. Giant flea market, commercial vendors, XYL programs, FCC exams, food available. All under cover. Parking \$1.00, tickets \$1.00 advance; \$1.50 door. Talk in on 146.07/67 and 146.52. Tickets from WD0CZE, 121 Barkwood Trail, St. Charles, MO 63303.

**CALIFORNIA:** Valley of the Moon Amateur Radio Club's fifth annual "Ham" breakfast and swapmeet, Sunday, August 11, Sonoma Community Center, 276 East Napa Street, Sonoma. 9 AM to 4 PM. Breakfast 9 to 11:30 AM. Sausage, eggs, pancakes, 'laters, o.j. and coffee, all you can eat for \$5.00! Swap tables setup starts 8 AM, spaces \$5.00 each. Better bring your own tables. Open auction at 1 PM. Surrounding points of interest for the whole family. Admission \$1.00. For reservations or more information: Darrel Jones, WD6BOR, 358 Patten St., Sonoma, CA 95476. (707) 996-4494.

**VERMONT:** The annual BARC International Hamfest, August 10 and 11, Old Lantern Campgrounds, Charlotte. \$4.00 both days. Children under 12 free. Outdoor flea market space \$2.00. Indoors \$5.00. RC model airplane show. CAN-AM tug-o-war. Talk in on 34/94, 01/61 and 52. Queries to Roger, WA10ZE; flea market info Bob, W1DQO. Both at Box 312, Burlington, VT 05402.

**ILLINOIS:** The Shawnee Amateur Radio Association is sponsoring SARA Hamfest '85 Sunday, September 8, John A. Logan College Gym, Highway 13 near Cartersville. New equipment and computers, ladies' activities, displays, flea market, crafts. All inside. FCC exams Sunday AM. Lunch available. Admission \$3.00. Talk in on 146.25/85, 146.52 simplex, 3.925 MHz. For information: Shawnee ARA, 502 West Kenicott, Carbondale, IL 62901. (618) 457-7586.

**1985 BLOSSOMLAND BLAST**, Sunday, October 6, 1985. Write "BLAST", PO Box 175, St. Joseph, MI 49085.

**MAINE:** The 1985 Windsor Hamfest, Saturday, September 7, Windsor Fairgrounds. Flea market, programs, speakers, distributors, and the traditional Saturday bean and casserole supper. Gate donation \$1.00. Camping \$3.00 per night; \$5.00/2 nights. Talk in on 146.22/82 repeater. For information: Ron Dishman, N1CMZ, 37 Marlboro Avenue, Augusta, ME 04330. (207) 623-8351.

**NEW JERSEY:** The Ramapod Mountain ARC, WA2SNA, presents its 9th annual flea market, August 17, Oakland American Legion Hall, 65 Oak Street, Oakland, 20 miles from GW bridge. Admission \$1.00. Non-ham family members free. Indoor tables \$6.50. Tailgating \$3.00. Talk in on 147.49/146.49 and 52. For information: Tom Risseeuw, N2AAZ, 63 Page Drive, Oakland, NJ 07436. Tel. 337-8389 after 6 PM.

**WISCONSIN:** Green Bay Mike & Key Club's Summer Swapfest, Saturday, August 17, Ashwaubenon Community Center, Anderson Drive across from Baypark Square Mall. Free admission and parking. Doors open 8 AM. Sellers 7 AM. Buy, sell, trade. Reserved 8' tables \$5.00. Limit 4. SASE with check to Green Bay Mike & Key Club, Bill Johnson, N9CNO, 2177 Orrie Lane, Green Bay, WI 54304. (414) 494-8948.

**MISSOURI:** The Ozarks Amateur Radio Society's 4th annual Congress & Swapfest, Sunday, September 8, City Park, Jct. of US 60 and Highway 37, Monett. Swapfest 11:00 AM. Buffet dinner 1:00 PM. No tickets necessary. All Amateurs and families welcome. Talk in on 146.37/97, 146.52 and 7.250 MHz. For information: Ozarks Amateur Radio Society, Box 327, Aurora, MO 65605. (417) 678-5330.

**GEORGIA:** Augusta Hamfest, September 15. Dealers and tailgaters welcome. Food and drinks available. ARRL/VEC exams 8 AM. Tickets \$1.00. 6/\$5, 13/\$10. Talk in on 34/94. SASE to Bill Hardin, 4430 Forrest Drive, Martinez, GA 30907. (404) 863-4360.

**INDIANA:** The Tippecanoe Amateur Radio Association's 14th annual Hamfest, Sunday, August 18, Tippecanoe County Fairgrounds, Teal Road and 18th Street, Lafayette. Grounds open 7 AM. Tickets \$3.00. Large flea market, dealers, refreshments and fun. Talk in on 13/73 or 52. For tickets or information: Lafayette Hamfest, Route 1, Box 63, West Point, IN 47992.

**ILLINOIS:** Bolingbrook Amateur Radio Society's B.A.R.S. Hamfest '85, Sunday, September 8, Santa Fe Park, 91st and Wolf Road, Willow Springs. Advanced registration \$2.00. \$3.00 at the gate. Talk in on 147.33/93 and 146.52. For information: Ed Weinstein, WD9AYR, 7511 Walnut Ave., Woodridge, IL 60517. (312) 985-0527.

**MICHIGAN:** The Grand Rapids Amateur Radio Association's annual Swap and Shop, Saturday, September 21, Hudsonville Fairgrounds. Dealers, indoor sales area, outdoor trunk swap, concession. Gates open 8 AM. Talk in on 146.16/76. For information: Grand Rapids ARA, PO Box 1248, Grand Rapids, MI 49501.

**PENNSYLVANIA:** The Skyview Radio Society's annual Hamfest, Sunday, September 16, Clu Grounds, Turkey Ridge Rd., New Kensington. Noon to 4 PM. Registration \$2.00. Vendors \$4.00. Talk in on 146.04-64 and 52.

**PENNSYLVANIA:** The Central Pennsylvania Repeater Association's 12th annual Hamfest/Computerfest, August 25, adjacent to Hersheypark, Chocolate Town, USA. Registration \$3.00. Children 12 and under free. Special reduced admission to Hersheypark for registrants and families. Large indoor dealer and flea market. Large outdoor tailgate area. Food and refreshments. Talk in on 145.47 repeater or 146.52 simplex WA3KXG. For information: Paul W. McDonnell, N3BK1, (717) 697-1880, noon to 8 PM.

**PENNSYLVANIA:** The Uniontown Amateur Radio Club (W3PIE) will hold its 36th annual Gabfest, Saturday, September 7, Club grounds, Old Pittsburgh Road, Uniontown. Registration \$3.00 or 2/\$5.00. Free Parking — Free Coffee — Free Swap & Shop with registration. Talk in on 147.645-.045 & 144.57-.17. For information: John Cermak, WB3DOD, U.A.R.C. Gabfest Committee, PO Box 433, Republic, PA 15475. (412) 246-2870.

**VIRGINIA/WEST VIRGINIA:** The Bluefield Hamfest, sponsored by the East River Amateur Radio Club, will be held Sunday, August 25, Brushfork Armory Civic Center, 1 mile north of Bluefield, WV. 9 AM to 3 PM. Admission \$4.00. Children under 12 free. Large indoor flea market, satellite TV and various specialty dealers. Paved parking, food on site, other activities. Walk in license exams 9 AM. Bring copy of license and completed 610 Form. \$4.00 fee. Talk in on 144.89/145.49 and 146.52. For information: Jim Perdue, KC8NG, Rt. 5, Box 457, Bluefield, WV 24701.

**NEW YORK:** The Putnam Emergency Amateur League (PEARL) will have its annual Electronics Extravaganza, August 17, 9 AM to 4 PM, J.F. Kennedy Elementary School, Brewster. Admission \$2.00. Tables \$5.00. Walk in VEC exams. For table reservations and information: R. Dillon, N2EFA, RFD 7, Noel Court, Brewster, NY 10509. Talk in on 144.535/145.135.

**ALABAMA:** The Huntsville Hamfest, Saturday and Sunday, August 17 and 18, Von Braun Civic Center in Huntsville. Free admission. Exhibits, forums, air-conditioned indoor flea market and non ham activities. Walk in FCC exams 9 AM Saturday, August 17. Family tours of the Alabama Space & Rocket Center available. Some camp sites with hookups available, first come, first served. Reserved flea market tables \$5/day. For more information: Huntsville Hamfest, 2804 S. Memorial Parkway, Huntsville, AL 35801.

**PENNSYLVANIA:** The Mid Atlantic Amateur Radio Club's annual Hamfest, Sunday, August 11, 9 AM to 4 PM, rain or shine, Bucks County Drive-In Theater, Rt. 611, Warrington. Admission \$3.00 + \$2.00 for tailgating. Setup starts 8 AM. Bring your own table. Plenty of parking, refreshments. Talk in on WB3JOE/R, 147.66/06 or 146.52. For information: MARC, PO Box 352, Villanova, PA 19085 or call Bob, WA3PZO (215) 449-9727.

**ARKANSAS:** The 16th annual Queen Wilhelmina Hamfest, Queen Wilhelmina State Park, September 7 and 8. This beautiful state park facility on top of Rich Mountain near Mena, offers family fun and relaxation. Free admission, dealer display, Saturday night banquet, \$7.00, camping, tailgating, flea market, miniature golf, wild life zoo, new playground, miniature train ride, ladies' tour. Talk in on 146.19/79. For information: John Harris, KC5XX, 5018 S. 9th, Ft. Smith AR 72903.

**ILLINOIS:** Vermilion County Hamfest, August 25, W9MJL Clubhouse, Harrison Park West, Danville. Donation \$1.50 at gate; \$1.00 advance. Saturday evening steak cookout,

\$5.00/reservations. Talk in on 146.22-82. For information and reservations: Joe Mayer, KB9GS, 613 E. Kelly, Box 356, Westville, IL (217) 267-2946.

## OPERATING EVENTS

### "Things to do..."

**Riding Radio Operators** — Amateur Radio Motorcycle Club Net meets every Thursday night at 0300 UTC at 3888 kHz standard time and 7237.5 kHz daylight saving time. An eastern USA group meets one hour earlier at 3888 kHz year-round. Send business SASE to AG0N, Gary McDuffie, Rt. 1, Box 464, Bayard, NE 69334 and ask for net information.

**September 4:** Howdy Days. Eligibility — all licensed women operators throughout the world. Operations — all bands and modes. No cross band. Station counted only once. Exchange — YLRL member or non YLRL member. Score 2 points for each YLRL member worked and 1 for non YLRL member. All logs must show YLRL membership or not, score and must be received by October 4, 1985. Send to Marty Silver, NY4H, 3118 Eton Road, Raleigh, NC 27608.

**August 18:** The DuPage Amateur Radio Club will operate special event station W9DUP from the War Museum submarine, U.S.S. Silversides, Navy Pier in Chicago. 1300Z August 18 to 0200Z August 19. For a special submarine QSL card, SASE to W9DUP, PO Box 71, Clarendon Hills, IL 60514.

**August 17:** 26th annual New Jersey QSO Party: 2000 UTC Saturday, August 17 to 0700 UTC Sunday, August 18 and from 1300 UTC Sunday, August 18 to 0200 UTC Monday, August 19. Phone and CW are considered same contest but separate bands. Station may be contacted once on each band. Suggest phone activity on even hours; 15 meters on odd hours. Exchange QSO number, RST, and QTH. NJ stations send county for QTH. Send logs and comments to: Englewood Amateur Radio Association, PO Box 528, Englewood, NJ 07631-0528. Include #10 SASE for results.

**PRICE REDUCTION**

**DX EDGE \$16.95**

**GRAYLINE AND LONG PATH PREDICTOR**

**Price Slashed on 2nd OP \$2.95**

**PREFIX CALLS TIME ZONES BEAM HEADINGS REGULAR \$19.90 PLUS SHIPPING**

**JUST \$18.95 plus \$3.50 S&H**

**HAM RADIO'S BOOKSTORE GREENVILLE NH 03048**

You can either buy one or buy both and save.

# THE GUERRI REPORT

Ernie Guerri  
W6 MGI

## surface-mounted components improve circuit designs

The traditional approach to printed circuit board design has been to lay out the board so that component leads go through holes in the board and are soldered to pads on one or both sides of the board. A technique first developed in the mid-1970's, using Surface Mounted Components (SMCs), has finally caught on, and achieves dramatic improvement over standard PCB designs. In the new approach, the PCB is designed for the same functional application, but the components are all mounted directly on the surface of the circuit paths themselves — *no holes!* All of the components are designed with short, flat leads that are flush with the PC path. This technique is particularly useful for RF circuits because lead lengths are dramatically shortened, thereby reducing parasitic inductance and capacitance, and improving EMI/RFI problems. Proper design of the components can maintain the impedance integrity of stripline designs right into the active region of the component. Circuits using this approach at 1200 to 1500 MHz give performance nearly as good as their low frequency counterparts. Let's hope that this attracts some real attention to the development of more equipment for the 1200 MHz Amateur band! Additionally, manufacturing costs are significantly reduced and reliability is improved. Circuit densities can be increased by 30 to 50 percent, resulting in considerable reduction in size, for use in complex equipment. The technique is particularly well suited to full automated production, and high volume producers such as the audio and TV industry are now regularly delivering products incorporating this approach. We should see the first uses

of this improved technique in Amateur equipment in the immediate future.

## computer-aided everything

The flood of information that seems to fill everyone's mailbox these days includes an increasing amount of data promoting the ways in which a computer can make each of our personal endeavors a snap. Productivity is the magic word, but much of what's offered seems to actually add complexity to such nominally simple tasks as home budget management.

This is not the case with computer-aided engineering, design, and manufacturing — CAE, CAD, CAM as they're called. Each of these tasks normally involves thousands of steps, each of which must be executed exactly, in complete compliance with design rules, and in concert with other phases of the process. All must be organized so that the final product is technically and physically correct, and on time. Modern product development cycles are frequently so short that there would be no way to do all the necessary steps by hand.

Take the example of designing a new computer chip. Such a chip may have a complex architecture, and 30 to 40 thousand active elements. By using computer-aided techniques, the design rules for circuit interconnects, layout, propagation delays, etc., can all be simultaneously considered every time a single change is made. A CAE tool called a "silicon compiler" actually contains the design rules for making the IC masks stored in computer memories. As the system architect and design engineer work on the chip's functional characteristics, the silicon compiler automatically includes the necessary semiconductors, routings, chip real-estate and thermal characteristics in the final design. Using these techniques, three employees of a major computer manufacturer were

able to design a 32-bit minicomputer chip set (including nearly 40,000 transistors) in less than a year.

It's been estimated that there are fewer than 5000 integrated circuit designers in the entire world. With the design tools offered by CAE and CAD systems, at least half of all electronic engineers could participate directly in the design of semi-custom ICs.

The prospects for even more dramatic advances in electronics are thus enhanced by the broad participation of another half-million or so engineers whose creativity is now frustrated.

## microwaves cook rocks

The success of commercial mining operations depends on assessing the extent to which rocks bearing sufficient quantities of desired material can be processed. Therefore, the quantity of desired ore per ton of rock is an important measure of the ultimate financial value of the process. Because one of the major problems in ore processing is keeping impurities out of the desired product, complex — and therefore expensive — steps must be taken to resolve these problems.

A new technique developed by a Colorado company may represent a major breakthrough in this field. Recognizing that each element has an atomic structure that can be excited by external energy sources, the company has devised a technique for illuminating rocks containing various elements with microwave energy matched to the resonant frequency of the element. The result is an ability to selectively melt desired material and leave surrounding material and impurities "cool" and undisturbed. Although the energy expenditure/recovery ratio is not obvious, the technique merits watching as yet one more example of RF in the "workhorse" environment.

**ham radio**



## Inter-Ear-Communication-System

A space age system that allows you to send and receive your message through your ear and leave your hands free.

# n-ear-talk

- Replace your HT's awkward speaker-microphone with an n-ear-microphone.
- Discrete HT communications leaves you with both hands free.
- Allows voice communications in noisy environments.
- Our n-ear-talk interfaces with almost all HT's, which have external speaker microphone output jacks.
- Custom hybrid circuit.
- Low power consumption. Transmits at 5mA and less than 10uA when receiving.
- One year warranty.

Dealer inquiries are invited.

### IECS-200




\$99.95 includes IECS-200 control unit, Ear transducer, 9V battery, 6-pin output connector and Instruction sheet. (Add 6% sales tax for California residents.)

Custom made interface cable for TEMPO S-15 and all ICOM HTs are available at \$19.95

FOR ALL PREPAID ORDERS, SHIPPING AND HANDLING CHARGE WILL BE PAID BY N-EAR-TALK. ✓ 189
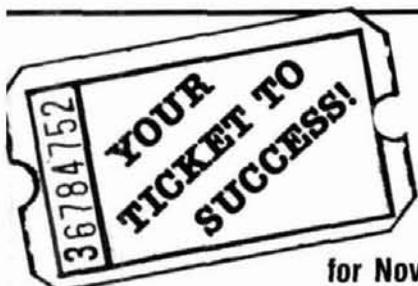
## ACE communications, inc.

22511 Aspan Street • Lake Forest • Calif. 92630-6321  
(714) 581-4900 Telex 29-7385 ACE UR Fax (714) 768-4410



## AMECO STUDY GUIDES

for Novice, General, Advanced and Extra

AMECO study guides are taken from the FCC Amateur Exam syllabus, PR 1035A and have answers keyed to the ARRL's recently released study material. These study guides are compatible with ARRL and all other VEC exams. While nothing can guarantee that you will pass, AMECO study guides will make sure that you are fully prepared and ready-to-go when you sit for the exam.

Each study guide has been written in a clear, precise easy-to-read format. Each question is fully explained. For subjects that need a more complete explanation, AMECO has cross referenced the Novice and General Class study guides with AMECO's AMATEUR RADIO THEORY COURSE, 102-01.

27-01	Novice Class	Softbound	\$2.25
12-01	General Class	Softbound	\$4.95
26-01	Advanced Class	Softbound	\$4.95
17-01	Extra Class	Softbound	\$4.95
23-01	Novice Class Theory Course	Softbound	\$3.75
102-01	Amateur Radio Theory Course	Softbound	\$6.95

Order today! Get yourself ready to upgrade with AMECO Study guides.

Please enclose \$3.50 per order for shipping and handling.

**ham radio** magazine  
GREENVILLE, NH 03048

**BOOKSTORE**  
(603) 878-1441

## MISSOURI RADIO CENTER

### ANTENNA SALE

#### HYGAIN TOWERS

HG37SS	799.00
HG52SS	1195.00
HG54HD	1799.00
HG70HD	2799.00

#### CUSHCRAFT

A3	199.00
A4	275.00
R3	255.00
40-CD2	275.00
AV5	96.00
32-19	89.00
215WB	75.00
ARX2B	35.00
A144-11	46.00
A144-20T	69.00
424B	75.00
AOP-1	137.00

#### KLM

KT34A	329.00
KT34XA	475.00
432-20LBX	64.00
432-30LBX	90.00
435-18C	109.00
435-40C	149.00
2M-13LBA	77.00
2M-14C	85.00
2M-16LBX	89.00
2M-22C	115.00

#### HYGAIN

TH3JR	185.00
TH7	459.00
EX 14	289.00
14AVQ	69.00
18AVT	102.00
V2	44.00
V3	44.00
V4	55.00

#### HUSTLER

25% OFF ALL MOBILE	
6BTV	125.00

#### AEA

144SR	42.00
-------	-------

#### BUTTERNUT

HF6V	110.00
HF2V	110.00
RG213U	\$.26/foot

#### ROTATORS

CD45	139.00
HAM IV	228.00
T2X	275.00
AVANTI 2M	29.95
HI-Q BALUN	9.95

#### KENPRO

KR400	119.00
KR500	149.00
KR600	199.00
KR5400	249.00

2900 N.W. VIVION ROAD  
KANSAS CITY, MISSOURI 64150  
816-741-8118


CALL TOLL FREE  
1-800-821-7323

MASTERCARD VISA & C.O.D.'s WELCOME



# ALL MODE MOBILE TELEPHONE INTERFACE

## Automatic Vox Phone Patch System

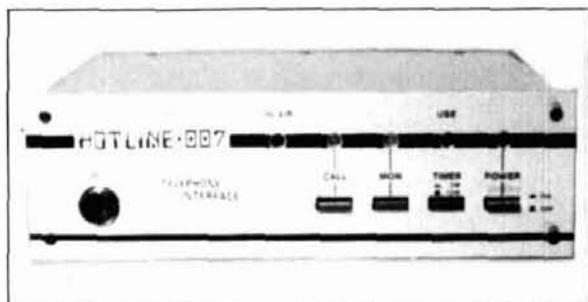

**OPTIONAL:**  
DTMF TELEPHONE  
TYPE SPEAKER/  
MICROPHONE

**HOTLINE-007** is a fully automatic simplex telephone interconnect. Operates through any base transceiver with FM-AM-  
quelled SideBand mode. No modifications to the transceiver, just connect to the external speaker, microphone and phone line.  
VOX operation both transmit and receive. Selectable tone or rotary dialing. Repeater pickup operational also.

- † Programmable access code
- † Adjustable VOX both transceiver and phone line.
- † Will not transmit when frequency is busy, 7 second clear time
- \* Programmable CW ID
- \* Adjustable microphone and line gain
- \* Microphone jack for base operation
- \* 3 or 12 minute timer
- \* Dial restrict switch
- \* Ringback (reverse patch)
- \* Accepts speed dialing
- \* Operates on 115/220 VAC, 12 VDC

NO EXTRAS TO PURCHASE FOR OPERATION, TRANSCIVER AND PHONE LINE CONNECT TIME 30 MINUTES.

N.C.G. CO.



**EXCLUSIVE IMPORT DISTRIBUTOR**

1275 N. Grove Street  
Anaheim, California 92806

NOTE: Prices and specifications subject to change without notice or obligation



## "TUNE IN" THE WORLD OF SPECIALIZED COMMUNICATIONS!

Thousands of "Ham Radio" operators across the country are enjoying "Specialized Communications" modes. Whether it's FSTV, SSTV, FAX, OSCAR, EME, RTTY, PACKET or COMPUTERS, today's Radio Amateur is a highly skilled Communications Specialist!

Providing full, in-depth coverage of these modes is our business and we've been doing it now for over 19 years! And now we're expanding!

Now published "monthly" 10 times per year, **SPEC-COM™** readers are kept up-to-date in a world of fast moving modern technology.

Why not give us a try? Back issue samples are available for just \$2.00 ppd. (Master Article Indexes add \$1.00).

Special Six Month Trial Subscription - \$10.00. U.S./Canada/Mexico Annual Subscription \$20.00. (Foreign Subscriptions slightly higher).

### SPEC-COM™

Amateur Radio Specialized  
Communication Journal  
P.O. Box H  
Lowden, Iowa 52255  
(319) 944-7669 (Membership Services)

Iowa Residents Must  
Add 4% Sales Tax



4% Added To All  
Charge Card Orders

191

### MULTI BAND TRAP ANTENNAS



#### TRAP DIPOLES:

Model	Bands	Traps	Length	Price
D-42	10/15/20/40	2	55	\$59.95
D-52	10/15/20/40/80	2	105	64.95
D-56	10/15/20/40/80	6	99	109.95

#### TRAP VERTICALS - "SLOPERS"™

Model	Bands	Traps	Length	Price
VS-31	10/15/20	1	12	42.95
VS-41	10/15/20/40	1	27	44.95
VS-52	10/15/20/40/80	2	52	59.95
VS-53	10/15/20/40/80	3	49	69.95

\*Can be used without radials. \*Feed line can be biased if desired. \*Permanent or Portable Use

ALL ANTENNAS are Ready to use - Factory assembled - Commercial Quality - Handle full power - Comes complete with Deluxe Traps, Deluxe center connector, 14 ga Stranded CopperWeld ant. wire and End Insulators. Automatic Band Switching - Tuner usually never required - For all transmitters, Receivers & Transceivers - For all class amateurs - One feedline works all bands - Instructions included - 10 day trial!

#### COAX CABLE: (includes PL-259 connector on each end)

Type	Length	With antenna purchase	Separately
RG-58	50	\$8.00	\$11.95
RG-58	90	12.00	16.95

#### DELUXE CENTER CONNECTOR

- NO RUST Brass Terminals
- NO jumper wires used
- NO Soldering
- Built in Lightning Arrestor
- With SO-239 Receptacle
- Handles Full Power
- Completely sealed - weatherproof
- Easy element adjustments
- Commercial quality



**DELUXE ANTENNA TRAPS** Completely sealed & weatherproof. Solid brass terminals. Handles Full power. NO jumpers. NO Soldering. Instructions included.  
For 4 band Dipole Ant. 40/20/15/10 \$36.00/pr  
For 5 band Dipole Ant. 80/40/20/15/10 \$38.00/pr

ORDER DIRECT FROM FACTORY. All orders shipped US Postpaid. VISA/MC give card # Exp. date, Signature.

**SPI-RO MANUFACTURING, INC.**  
Room 103, P.O. Box 1538  
Hendersonville, NC 28793

Dealer Inquiries Invited

192



# The Nicest Things Come In Small Packages.

The SS-32HB is a new hybrid sub-audible encoder plucked from Communications Specialists' Hothouse. It has grown through a cross of the time tested SS-32, the subminiature SS-32M and space age micro circuitry. This programmable 32 tone encoder measures a scant .5 x 1.0 x .15 inches; no small wonder it allows the addition of continuous tone control to a bunch of hand held transceivers that lack space.

Why not snip your problems in the bud, with our fast, one day delivery and attractive one year warranty.

\$29.95 each



**COMMUNICATIONS  
SPECIALISTS**

426 W. Taft Ave., Orange, CA 92665-4296  
Local (714) 998-3021 • FAX (714) 974-3420  
Entire U.S.A. 1-800-854-0547

✓ 193





# Presenting two small cases for a lot of mobile power.

You won't find a 45-watt, 2-meter FM mobile rig that's built smaller than the Yaesu FT-270RH.

Nor will you find a dual-band FM mobile that offers the crossband full-duplex capability found in the 25-watt Yaesu FT-2700RH.

It shouldn't be surprising. We've been coming up with a lot of innovative concepts lately.

The FT-270RH measures just 2 x 6 x 7 inches. Conveniently fitting its high-power punch into many small spaces of your car. Places where other 45-watt mobiles just won't fit.

The FT-2700RH is small too. Smaller than other dual-banders. But with one big difference: a "DUP" button. Push it, and you're operating full duplex, 2 meters on one VFO, 440 MHz on the other. Each at 25 watts. So you can simultaneously

transmit and receive in true telephone style.

Once installed, you'll find the FT-270RH and the FT-2700RH equally simple to operate. Just turn the rig on, dial up a frequency, select offset or duplex split, and you're on the air.

Each rig gives you 10 memories for storing your favorite frequencies. Dual VFO capability. A clean, uncluttered LCD display for easy readout. Push-button jumps through the band in 1 MHz steps. Band scanning with programmable upper and lower limits. And priority channel operation.

You don't even have to take your eyes off the road to determine your operating frequency and memory channel. An optional voice synthesizer announces them both at the push of a button on the microphone. The FT-2700RH announces both your

2-meter and 440 MHz operating frequencies.

Also, tone encode and encode/decode capability is programmable from the front panel, using an optional plug-in board.

So when you need a lot of power in a compact mobile radio, discover Yaesu's FT-270RH and FT-2700RH. There's nothing else like them on the road.

## YAESU

**Yaesu Electronics Corporation**  
6851 Waltham Way, Paramount, CA 90723  
(213) 633-4007

**Yaesu Cincinnati Service Center**  
9070 Gold Park Drive, Hamilton, OH 45011  
(513) 874-3100

Prices and specifications subject to change without notice.

✓ 194



# KENWOOD

...pacesetter in Amateur radio

NEW

## “DX-cellence!”

### TS-940S



The new TS-940S is a serious radio for the serious operator. Superb interference reduction circuits and high dynamic range receiver combine with superior transmitter design to give you no-nonsense, no compromise performance that gets your signals through! The exclusive multi-function LCD sub-display panel graphically illustrates VBT, SSB slope, and other features.

- 100% duty cycle transmitter. Super efficient cooling system using special air ducting works with the internal heavy-duty power supply to allow continuous transmission at full power output for periods exceeding one hour.
- Programmable scanning.
- Semi or full break-in (QSK) CW.

- Low distortion transmitter. Kenwood's unique transmitter design delivers top "quality Kenwood" sound.
- Keyboard entry frequency selection. Operating frequencies may be directly entered into the TS-940S without using the VFO knob.
- Graphic display of operating features. Exclusive multi-function LCD sub-display panel shows CW VBT, SSB slope tuning, as well as frequency, time, and AT-940 antenna tuner status.
- QRM-fighting features. Remove "rotten QRM" with the SSB slope tuning, CW VBT, notch filter, AF tune, and CW pitch controls.
- Built-in FM, plus SSB, CW, AM, FSK.
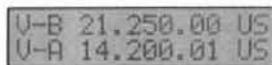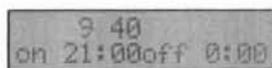
#### Optional accessories:

- AT-940 full range (160-10 m) automatic antenna tuner
- SP-940 external speaker with audio filtering
- YG-455C (500 Hz), YG-455CN-1 (250 Hz), YK-88C-1 (500 Hz) CW filters;
- YK-88A-1 (6 kHz) AM filter
- VS-1 voice synthesizer
- SO-1 temperature compensated crystal oscillator
- MC-42S UP/DOWN hand mic.
- MC-60A, MC-80, MC-85 deluxe base station mics.
- PC-1A phone patch
- TL-922A linear amplifier
- SM-220 station monitor
- BS-8 pan display
- SW-200A and SW-2000 SWR and power meters.



- High stability, dual digital VFOs. An optical encoder and the flywheel VFO knob give the TS-940S a positive tuning "feel".
- 40 memory channels. Mode and frequency may be stored in 4 groups of 10 channels each.
- General coverage receiver. Tunes from 150 kHz to 30 MHz.
- 1 yr. limited warranty. Another Kenwood First.



More TS-940S information is available from authorized Kenwood dealers.

## KENWOOD

TRIO-KENWOOD COMMUNICATIONS  
1111 West Walnut Street  
Compton, California 90220

Complete service manuals are available for all Trio-Kenwood transceivers and most accessories. Specifications and prices are subject to change without notice or obligation.