

# RADIO-TV

## Experimenter

75c

Over 40 Projects, Plus

No. 551 Published by Science and Mechanics Magazine




Latest Directory  
of U.S. and Canadian  
AM-FM-TV STATIONS  
WORLD-WIDE SHORT WAVE



How to Build



Spit-Powered  
Oscillator

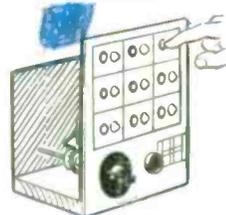

Electronic  
Tic-Tac-Toe

Designer's Chassis

Decade  $\Omega$  Box

P. E. Controls

Signal Tracer

Sun-Cell TRF

Experimenter's  
Test Bench

# BUILD 16 RADIO CIRCUITS AT HOME

only

## with the New Deluxe PROGRESSIVE RADIO "EDU-KIT" \$22.95

### A Practical Home Radio Course

- Now Includes
- ★ TRANSMITTER
  - ★ SIGNAL TRACER
  - ★ SIGNAL INJECTOR
  - ★ CODE OSCILLATOR
  - ★ No Knowledge of Radio Necessary
  - ★ No Additional Parts or Tools Needed
  - ★ Excellent Background for TV
  - ★ School Inquiries Invited
  - ★ Attractively Gift Packed

### WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction practice and servicing.

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with RF and AF amplifiers and oscillators; detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble-shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester & the accompanying instructional material.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for TV.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with a most modern and complete method of radio construction known as "Printed Circuitry." The Signal Tracer alone is worth more than the price of the entire Kit.

### THE KIT FOR EVERYONE

You do not need the slightest background in radio or science. Whether you are interested in Radio & Electronics because you want an interesting hobby, a well paying business or a job with a future, you will find the "Edu-Kit" a worthwhile investment. Many thousands of individuals of all

ages and backgrounds have successfully used the "Edu-Kit" in more than 79 countries of the world. The "Edu-Kit" has been carefully designed, step by step, so that you cannot make a mistake. The "Edu-Kit" allows you to teach yourself at your own rate. No instructor is necessary.

### PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore you construct, learn schematics, study theory, practice trouble-shooting—all in a closely integrated program designed to provide an easily-learned, thorough and interesting background in radio. You begin by assembling the various radio parts into the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set you will enjoy listening to regular broadcast stations, learn theory, practice testing and trouble-shooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a Professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer, and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

### THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, a High Fidelity Guide and a Quiz Book. You receive all parts, tools, instructions, etc. Everything is yours to keep.

### UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER DIRECT FROM AD  
RECEIVE FREE BONUS RESISTOR & CONDENSER KITS WORTH \$7

- Send "Edu-Kit" Postpaid. I enclose full payment of \$22.95.
- Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name .....

Address .....

### PROGRESSIVE "EDU-KITS" INC.

497 Union Ave., Dept. 502NN, Brooklyn 11, N. Y.



Reg. U.S. Pat. Off.

### FREE

- SET OF TOOLS
- SOLDERING IRON
- ELECTRONIC TESTER
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- TESTER INSTRUCTION MANUAL
- HIGH FIDELITY GUIDE • QUIZZES • TELEVISION BOOK • RADIO TROUBLE-SHOOTING BOOK • MEMBERSHIP IN RADIO-TV CLUB • CONSULTATION SERVICE • FCC AMATEUR LICENSE TRAINING • PRINTED CIRCUITRY

### SERVICING LESSONS

You will learn trouble-shooting and servicing in a progressive manner. You will practice repairs on the sets that you construct. You will learn symptoms and causes of troubles in home, portable and car radios. You will learn how to use the professional Signal Tracer, the unique Signal Injector and the Dynamic Radio & Electronics Tester. While you are learning in this practical way, you will be able to do many a repair job for your friends and neighbors, and charge fees which will far exceed the price of the "Edu-Kit." Our Consultation Service will help you with any technical problems you may have.

J. Stataitis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The 'Edu-Kit' paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

### FROM OUR MAIL BAG

Ben Valerio, P. O. Box 21, Magna, Utah: "The Edu-Kits are wonderful. Here I am sending you the questions and also the answers for them. I have been in Radio for the last seven years, but like to work with Radio Kits, and like to build Radio Testing Equipment. I enjoyed every minute I worked with the different kits. The Signal Tracer works fine. Also like to let you know that I feel proud of becoming a member of your Radio-TV Club."

Robert L. Shuff, 1534 Monroe Ave., Huntington, W. Va.: "Thought I would drop you a few lines to say that I received my Edu-Kit, and was really amazed that such a bargain can be had at such a low price. I have already started repairing radios and phonographs. My friends were really surprised to see me get into the swing of it so quickly. The Troubleshooting Tester that comes with the Kit is really useful, and finds the trouble, if there is any to be found."

### PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

# RADIO-TV Experimenter

VOLUME FIVE

## CONTENTS

Troubleshooter's Signal Tracer	21	Earphone Speaker Wrist Radio	92
Experimenter's Chassis	25	Dry Cell Charger	94
Spit-Powered Oscillator	29	Transistorized Megaphone	97
Photo-Electric Controllers	31	Single-Tube Electronic Organ	103
Buying the Right Tape Recorder	34	Testing Vacuum Tubes	107
B-Battery Eliminator for Portables	41	Versatile Oscillator	111
Decade Resistance Box	43	Magnetic Pendulum	114
Code-Practice Buzzer	46	Record Player Dress-up	118
Experimenter's Test Bench	49	Pocket Superhet	119
Thread the Needle!	58	Sun-Powered, Two-Transistor Radio	123
Electronics "Numbers Game"	58	Coil-Winding Machine	126
Instant-Ready Intercom	59	Air-Cloud Hi Fi	134
Test Bell for the Bench	62	Electronic Tic-Tac-Toe	137
Mystery Coil	62	Junior-Size Record Player	140
Crystal Headset	63	Battery Applications	141
Improved Razor-Blade Detector	64	Dry Cell Tester	142
Crystal Microphone	65	True-Fidelity Amplifier	145
Vibrator Repair	68	Portable Hi-Fi Record Player	149
Pepping up Record Players	69	Making Slide Wire Resistors	153
Battery Data	70	Super Widget	155
TV-Set Scope Conversion	71	Caring for Soldering Irons	157
Civil Air Patrol Radio	76	Twin Speakers Improve Fidelity	159
Three Speeds from a Two Speed Phono Motor	80	Tips on Using Small Decals	160
Midget Record Player	81		
Curing Radio Troubles	83		
Experimenter's Power Supply	87		

### SPECIAL SUPPLEMENT

White's Radio Log	161
A History of Broadcasting	190

Cover by Dick Locher

Curt Johnson, Handbook Editor  
Herb Siegel, Handbook Assistant Editor  
Bill Watkins, Assistant Art Director, for Handbooks  
Thomas A. Blanchard, Radio-TV Editor

Published and Copyrighted 1958 by  
**SCIENCE AND MECHANICS PUBLISHING COMPANY**

450 East Ohio Street

Chicago 11, Illinois

The Radio-TV Experimenter contains a selection of the most popular electronics projects and radio and TV maintenance articles that have appeared in *Science and Mechanics Magazine*, plus a number of projects and helpful articles on the same subject, appearing for the first time.

Science and Mechanics Handbook Annual No. 1, 1958—No. 551

### Editorial Board

V. D. ANGERMAN  
Editor and Publisher  
DON DINWIDDIE  
Managing Editor  
ART YOUNGQUIST  
Home Workshop Editor  
RAY WHITMAN  
Feature Editor  
P. D. URBAIN  
Associate Editor  
L. G. ANDERSEN  
Associate Editor  
RAY S. LINDENMEYER  
Technical Editor  
F. M. EISENZOPH  
Art Director  
CHUCK BACHTTEL  
Assistant Art Director

# HOW WOULD YOU LIKE TO BREAK INTO ENGINEERING STARTING NEXT MONTH?

Your start in Engineering could mean higher pay, more interesting work, a real chance for advancement. Here's how to do it—fast!

A career in Engineering may be closer than you think, whatever your age or education or present job.

You know about the tremendous demand for engineers and technicians. But do you know how easy it is to get the training that will qualify you for this vital work, and how quickly you can advance?

## First Step Wins Job Consideration

The moment you enroll for a course in Engineering you're in a position to change your job. I. C. S. Engineering Courses, for example, start you off with Basic Mathematics and Drafting. Most employers are quick to accept men who start technical training.

## Your Advancement Is Rapid

Your interest, your determination, your willingness to spend free hours improving your-

self all work in your favor. But your mastery of engineering subjects is what wins you the biggest boosts.

The I. C. S. method makes it possible for you to learn while you earn, to qualify yourself for upgrading step by step—from Draftsman to Detail Designer to Engineering Technician to full-fledged Engineer. It's a plan fitted to your needs, with personalized instruction and guidance, and, if you like, regular progress reports to your employer.

## Mail Coupon for Free Books

If you are seriously interested in a fresh start in an opportunity-packed field, then mark and mail the coupon today. We'll send you *three* free books—(1) the 36-page career guide "How to Succeed," (2) Opportunity outlooks in your field of interest, (3) sample lesson (Math) demonstrating I. C. S. method.

For Real Job Security—Get an I. C. S. Diploma! I. C. S., Scranton 15, Penna. Accredited Member, National Home Study Council

## INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX 14248M, SCRANTON 15, PENNA.

(Partial list of 257 courses)

Without cost or obligation, send me "HOW TO SUCCEED" and the opportunity booklet about the field BEFORE which I have marked X (plus sample lesson):

### ARCHITECTURE and BUILDING CONSTRUCTION

- Air-Conditioning
- Architecture
- Arch. Drawing and Designing
- Building Contractor
- Building Estimator
- Carpentry and Millwork
- Carpenter Foreman
- Heating
- Interior Decoration
- Painting Contractor
- Plumbing
- Reading Arch. Blueprints

### ART

- Commercial Art
- Magazine & Book Illus.
- Show Card and Sign Lettering
- Sketching and Painting

### AUTOMOTIVE

- Automobiles
- Auto Body Rebuilding and Refinishing
- Auto Engine Tuneup
- Auto Technician

### AVIATION

- Aero-Engineering Technology
- Aircraft & Engine Mechanic

### BUSINESS

- Accounting
- Advertising
- Business Administration
- Business Management
- Cost Accounting
- Creative Salesmanship
- Managing a Small Business
- Professional Secretary
- Public Accounting
- Purchasing Agent
- Salesmanship
- Salesmanship and Management
- Traffic Management

### CHEMICAL

- Analytical Chemistry
- Chemical Engineering
- Chem. Lab. Technician
- Elements of Nuclear Energy
- General Chemistry
- Natural Gas Prod. and Trans.
- Petroleum Prod. and Engr.
- Professional Engineer (Chem)
- Pulp and Paper Making

### CIVIL ENGINEERING

- Civil Engineering
- Construction Engineering
- Highway Engineering
- Professional Engineer (Civil)
- Reading Struc. Blueprints
- Structural Engineering
- Surveying and Mapping

### DRAFTING

- Aircraft Drafting
- Architectural Drafting
- Drafting Machine Design
- Electrical Drafting
- Mechanical Drafting
- Sheet Metal Drafting
- Structural Drafting

### ELECTRICAL

- Electrical Engineering
- Elec. Engr. Technician
- Elec. Light and Power
- Practical Electrician
- Practical Lineman
- Professional Engineer (Elec)

### HIGH SCHOOL

- High School Diploma

- Good English
- High School Mathematics
- Short Story Writing

### LEADERSHIP

- Industrial Foremanship
- Industrial Supervision
- Personnel-Labor Relations
- Supervision

### MECHANICAL and SHOP

- Diesel Engines
- Gas-Elec. Welding
- Industrial Engineering
- Industrial Instrumentation
- Industrial Metallurgy
- Industrial Safety
- Machine Design
- Machine Shop Practice
- Mechanical Engineering
- Professional Engineer (Mech)
- Quality Control
- Reading Shop Blueprints
- Refrigeration and Air Conditioning
- Tool Design
- Tool Making

### RADIO, TELEVISION

- General Electronics Tech.

### INDUSTRIAL ELECTRONICS

- Industrial Electronics
- Practical Radio-TV Engr'g
- Practical Telephony
- Radio-TV Servicing

### RAILROAD

- Car Inspector and Air Brake
- Diesel Electrician
- Diesel Engr. and Fireman
- Diesel Locomotive

### STEAM and DIESEL POWER

- Combustion Engineering
- Power Plant Engineer
- Stationary Diesel Engr.
- Stationary Fireman

### TEXTILE

- Carding and Spinning
- Cotton Manufacture
- Cotton Warming and Weaving
- Loom Fixing Technician
- Textile Designing
- Textile Finishing & Dyeing
- Throwing
- Warming and Weaving
- Worsted Manufacturing

Name \_\_\_\_\_ Age \_\_\_\_\_ Home Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_ Working Hours \_\_\_\_\_ A.M. to P.M.

Occupation \_\_\_\_\_

Canadian residents send coupon to International Correspondence Schools, Canadian, Ltd., Montreal, Canada. . . . Special tuition rates to members of the U. S. Armed Forces.

These men are getting practical training in . . .

# ELECTRICITY

## ELECTRONICS

ON REAL

A.C. and D.C. Motors  
Generators  
Switchboards  
Controllers  
Appliances  
Electronic Units

# TELEVISION

## COLOR-TV

ON REAL

Television  
Receivers  
Including Color TV  
AM and FM Radios  
Auto Radios  
Test Equipment

# Train in Great Shops of COYNE

in Chicago—Prepare for a better job and a real future in **TOP OPPORTUNITY FIELDS**. Train on real full-size equipment at COYNE where thousands of successful men have trained for nearly 60 years—*largest, oldest, best equipped school of its kind*—est. 1899. Trained instructors show you how, then do practical jobs yourself. No previous experience or advanced education needed. Employment Service to Graduates. **START NOW—PAY LATER**—Liberal Finance and Payment Plans. Part-time employment help for students. **GET FREE BOOK**—"Guide to Careers in ELECTRICITY-ELECTRONICS and TELEVISION-RADIO"—no obligation; no salesman will call. Vets and Non-Vets get vital facts now.

Coyne Electrical School 500 So. Paulina Street  
Chartered Not For Profit Chicago 12, Dept. 28-8C



**MAIL COUPON TODAY!**

**COYNE ELECTRICAL SCHOOL**  
500 S. Paulina St., Chicago 12, Ill., Dept. 28-8C

Send **BIG FREE** book and details of your training offer by return mail. I am interested in:

Electricity-Electronics  Television-Radio

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

COYNE offers  
LOW COST

# TELEVISION RADIO - COLOR TV

Training in  
Spare Time **AT HOME**



The future is **YOURS** in **TELEVISION!**

A fabulous field—good pay—fascinating work—a prosperous future in a good job, or independence in your own business!

Coyne brings you **MODERN-QUALITY** Television Home Training; training designed to meet Coyne standards at truly lowest cost—you pay for training only—no costly "put together kits." Not an old Radio Course with Television "tacked on." Here is **MODERN TELEVISION TRAINING** including Radio, UHF and Color TV. No Radio background or previous experience needed. Personal guidance by Coyne Staff. **Practical Job Guides** to show you how to do actual servicing jobs—*make money early in course*. Free Life-time Employment Service to Graduates.

*Send Coupon for Free Book*

and full details, including easy Payment Plan. No obligation, no salesman will call.



**COYNE Television Home Training Division**

500 S. Paulina St., Chicago 12, Ill. Dept. 28-H8

Send Free Book and details on how I can get Coyne Quality Television Home Training at low cost and easy terms.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

# COYNE ELECTRICAL SCHOOL

A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT  
500 S. Paulina Street, Chicago 12, Dept. 28-H8

B. W. COOKE, Jr., President



Coyne—The Institution behind this training... the largest, oldest, best equipped residential school of its kind. Founded 1899.

# BARGAINS

IS THE ONLY BIG TABLOID PUBLICATION in Existence That Tells You WHERE & HOW —EVERY MONTH—



- To Buy Bankrupt, Closeout, Surplus Bargains!
- To Buy Items at Wholesale! • At Below Wholesale!
- To Buy New & Unusual Items!
- To Obtain Information on Rare Money Making Offers!

TOYS, BOOKS, JEWELRY, GREETING CARDS, COSMETICS, HOUSEHOLD MERCHANDISE, APPLIANCES, INDUSTRIAL MATERIALS, MACHINERY, TOOLS, ETC.

Often as Low as 10c-25c on the Retail Dollar!!

ONE issue of this Sensational NEW publication can save you MORE MONEY than the cost of the entire subscription! You can BUY BETTER, CHEAPER, NEWER THINGS EVERY MONTH OF THE YEAR! Today, when your dollar buys so little, you absolutely need every single issue of BARGAINS in order to get the MOST FROM EVERY PENNY YOU SPEND. Each issue carries HUNDREDS of bargain offers . . . many times SO EXTRAORDINARY that it's hard to believe that they're GENUINE! Buying at WHOLESALE, BANKRUPT, SURPLUS, CLOSEOUT PRICES can save you from 40¢ to 80¢ or more on every dollar you spend! THIS MAY BE HARD TO BELIEVE, BUT IT IS THE TRUTH!

**YOU Can Make FANTASTIC PROFITS Buying Up Bargain Merchandise CHEAP and Selling It CHEAP SAVE MONEY ON CHRISTMAS GIFTS—TOO!**

**DON'T Take Our Word For It—Here's What Subscribers Say About "BARGAINS"!**

" . . . Received my 1st issue and may I say IT IS A GREAT MAGAZINE."—M. C., Ark.  
 ". . . I am very pleased with BARGAINS. I have never seen anything like it."—Mrs. D. M., Maine.  
 ". . . Just received my 1st copy of "Bargains" and believe me, it is all that you claimed it to be."—T. A., N. Y.

". . . I was the recipient of my 1st copy a few days ago. I am completely satisfied with the periodical. I also wish to express my appreciation to you for having made the magazine available to me. I shall be pleased to continue my subscription as long as the magazine is available."—W. S., Wash.  
 Every One OF THESE LETTERS ARE IN OUR FILES & WERE NOT SOLICITED IN ANY WAY OR MANNER!

Thousands of Agents, Salesmen, Dealers are subscribers to "BARGAINS." They want to know where to buy BEST in order to sell at low prices for BIG PROFITS. NO REASON why you CAN'T DO THE SAME! Special articles in BARGAINS give you valuable tips on HOW to sell these bargains for BIG PROFITS. And you know, EVERYBODY is looking for bargains these days . . . in fact, this is the only kind of merchandise that is being sold in tremendous volume. Ask any big businessman!

**Unique "Subscribers Shopping Service" Enables You to Buy Big Name Merchandise at TREMENDOUS SAVINGS**

You won't find this feature in ANY OTHER MAGAZINE. ONLY "BARGAINS" has it. For subscribers ONLY, each month it negotiates bargain offers in famous merchandise at LOW WHOLESALE PRICES and then offers them to subscribers AT NO PROFIT! Enables you to buy in small lots—singly or in quantity at the same prices (sometimes even lower) that dealers are paying! This SINGLE FEATURE OF BARGAINS IS WORTH THE LOW SUBSCRIPTION PRICE A DOZEN TIMES OVER. Yes, it's only ONE feature among many to be found! Yes, Just one!

**"Bargains" is the ONLY Publication of Its Kind in Existence!**

Search your newsstand high and low. You won't find another publication like it! BARGAINS is available by subscription ONLY. Read the glowing letters by subscribers who received their 1st copies and WERE AMAZED by this sensational publication! You will be, too!

**SAVE Up to \$1,000—EARN Up to \$3,000!**

We honestly believe that it's possible to SAVE up to \$1000—and EARN up to \$3000, within a year by reading "BARGAINS" EVERY MONTH! WHY NOT PROVE THIS FOR YOURSELF!

Your subscription will automatically include the BIG 1957 CHRISTMAS SPECIAL ISSUE . . . jam full of terrific, eye opening holiday BARGAINS! JUST \$2.00—17¢ per month gives you 12 great money saving issues of Bargains!

**\$2.00 Per Year—12 Big Issues**

(Regular price, \$3.00 per Year)

Special Limited Time Offer to Get 10,000 New Subscribers!

**Your Money Back IN FULL**

**if the First Issue Doesn't Please You!**

LET'S FACE IT . . . Claims, promises are easily made on paper. You may or may not believe all we say here. BUT can you go wrong in subscribing to "Bargains" on this iron-clad MONEY BACK GUARANTEE . . . Your money back IN FULL if the first issue that you receive doesn't please you! Can any offer be more POSITIVE, more FAIR than this POWERFUL guarantee?

Tower Press, Inc., P. O. Box 591, Lynn 872, Mass.

Here's a FEW Samples of the Bargains Usually Found in "BARGAINS"!

- PENCILS, 571/2¢ per Gross!
- 25¢ Rudolph the Reindeer Brooches, 2¢ each!
- Plastic Toy GUNS, 2¢ each!
- \$1. Mufflers, Scarfs, 12 1/2¢ each!
- Double edge razor blades, \$1.50 per 1000!
- LADIES APRONS, 6 1/4¢ each!
- \$2.50 WALLETS, 30¢ each!
- \$1. val. BILLFOLDS, 15¢ each!
- \$1. Kiddies handbags, 3¢ each!
- CIGARETTE HOLDERS, 1¢ each!
- BUTTONS, 144 for 25¢!
- NEW Phono records, 78 & 45 r.p.m. 7¢ each!
- 6¢ Insect Repellent, 5¢ each!
- New 20" T.V. Pic. tubes, \$21.95 each!
- Famous brand \$18.75 perfume, \$1. each!
- 49¢ Xmas window decorations, 10¢ per set!
- \$1-\$3 Hard cover books, 20¢ each!
- \$200.00 Surplus typewriters, \$23.00 each!
- 50¢ Everyday greeting cards, 7¢ per box!
- \$1.95 Men's Silk Ties, 12 1/2¢ each!
- \$1. val. personal cloth name tapes, 40¢ for 72!
- 39¢ Under arm deodorant, 2¢ jar!
- \$1. Automatic card shufflers, 9¢ each!
- NEW HAIRNETS, 1/2¢ each!
- \$15.00 Electric Percolators, \$5.00 each!
- \$1.75 Rudolph Reindeer kiddies toiletry sets, 35¢ each!
- \$5.50 Lucite Hairbrushes, 65¢ each!
- New Bobby Pins, 70¢ per 700 pins!
- \$10. Men's Toiletry Sets, 60¢ each!
- Calendar Wrist Watches, \$5. each!
- Christmas Seals, 25¢ per 1000!
- \$2.98 Horserace game records, 30¢ each!

**• PLUS HUNDREDS OF OTHER SENSATIONAL BUYS!**

(Above list merely illustrates type of bargains usually found in this paper. Lists naturally change from month to month.)

**"Tear out Coupon. Mail NOW—at once!"**

Tower Press, Inc., Box 591, Lynn 872, Mass.

O.K. Here's my \$2.00 for 1 year subscription. Rush me 1st copy! (Canada, foreign, \$3.00).

Name .....

Address .....

City ..... State .....

Remember! Your Money Back IN FULL if the 1st issue you receive doesn't please you!

LET DeVRY TECH PREPARE YOU IN  
SPARE TIME AT HOME AS AN

# ELECTRONICS TECHNICIAN



**NO PREVIOUS TECHNICAL EXPERIENCE  
OR ADVANCED EDUCATION NEEDED!**

Laborers and bookkeepers, store clerks, shop men, farmers, salesmen — men of nearly every calling — have taken the DeVry Tech program and today have good jobs or service shops of their own in Electronics. You don't have to quit your present job. If you are 17 to 55, see how you may get yourself ready for a future in the fast-growing Electronics field.

Whether you prepare at home or in our well-equipped Chicago or Toronto Laboratories, you get sound, basic training in both principles and practice. At home, you use educational movies. You build actual circuits and test equipment. You read simple directions, follow clear illustrations. When you finish, you are prepared to step into a good job in an excitingly different field. You may even start a service shop of your own. Mail coupon for free facts today.

### Live-Wire Employment Service



Puts you in touch with job opportunities—or helps you toward a better position in the plant where you are now employed.

### Draft Age?

We have valuable information for every man of draft age; so if you are subject to military service, be sure to check the coupon.

**SAMPLE BOOKLET FREE!**

We'll give you a free copy of an interesting booklet, "Electronics and YOU." See for yourself how you may take advantage of the opportunities in this fast-growing field.



**AN INDEX  
to a  
BETTER JOB,  
A BRIGHTER  
FUTURE**

Electronics

Radar

Guided  
Missiles

Television

Micro-Waves

Communications

Radio

Industrial  
Electronics

Computers

Automation  
Electronics

Remote Control  
Systems

Broadcasting

Your Own  
Service Shop

**MAIL TODAY FOR FREE FACTS**

"One of North America's Foremost Electronics Training Centers"



Accredited Member  
of National  
Home Study Council

**DeVRY TECHNICAL INSTITUTE**

CHICAGO 41, ILLINOIS

FORMERLY

DeFOREST'S TRAINING, INC.



**DeVry Technical Institute**

4141 Belmont Ave., Chicago 41, Ill., Dept. RTE-0

Please give me your FREE booklet, "Electronics and YOU," and tell me how I may prepare to enter one or more branches of Electronics as listed above.

NAME \_\_\_\_\_ AGE \_\_\_\_\_

STREET \_\_\_\_\_ Please Print \_\_\_\_\_ APT. \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

Check here if subject to military training.

1090 DeVry Tech's Canadian Training Center is located at  
626 Roselawn Avenue, Toronto 12, Ontario

## HERE'S JUST WHAT YOU NEED!

• For Home Electronics • For Home Hi-Fi Assembly • For ALL Hobbyists (Model Railroading, etc.) • For Home Workshop

Here is the first and only kit of its kind—a heavy duty soldering and electrical kit by Ungar—a kit of a hundred uses. It contains the famous Ungar soldering handle (used by large electronics manufacturers everywhere) with interchangeable tips for every type of soldering and plastic welding. This iron will do everything you'd expect from a bulky 100-watt iron only better. Kit contains ten most useful items.

1. Famous Ungar Heavy Duty Handle, feather light, made to give years of service—simply thread in choice of tips. 110-120 AC-DC. 2. Heavy Duty Screw-in Tip for all types of heavy duty soldering. Supplies a searing 825° F. tip temperature in 90 seconds. 3. Precision Soldering Tip. Consists of heating element and 1/8"x1" changeable tiptlet for fine soldering—printed circuits, jewelry repair, plastic welding of model railroad cars, airplanes and boats. Tip temperature 600°F in 60 seconds. 4. Trouble Light. Supplies steady, bright light into hard-to-get-at places. 5. Circuit tester for tracing electrical troubles. Thread globe into handle and connect circuit tester to handle cord. Touch bare wires to terminals and if current is flowing the bulb lights. 6. and 7. Terminal Connectors, perfect for making permanent cord connections. Emery Paper for better soldering surfaces. 8. Rosin Core Solder specified for electronics soldering—no flux required. 9. Insulating Tape. 10. Fully illustrated—easy to read 20-page "How to Do It" booklet.

Ungar Handle and Tips are U/L listed. Yes, all these useful items, beautifully packaged in this handy kit at only \$4.95. This Ungar kit #507 is sold by electronics shops, hardware and hobby stores and Hi-Fi dealers.

UNGAR ELECTRIC TOOLS, INC. 4101 Redwood Avenue Los Angeles 66, Calif.



1.




2.



3.




4.

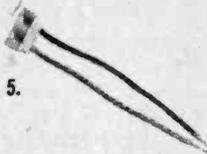

5.



6.

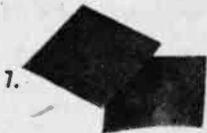

7.



8.



9.



10.

If your dealer is out of stock, send \$4.95 direct to the Ungar Electric Tools, Inc., 4101 Redwood Avenue, Los Angeles 66, Calif. Shipment made within ten days, prepaid.


Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Postage and tax included in above price. Sorry no C.O.D.'s.

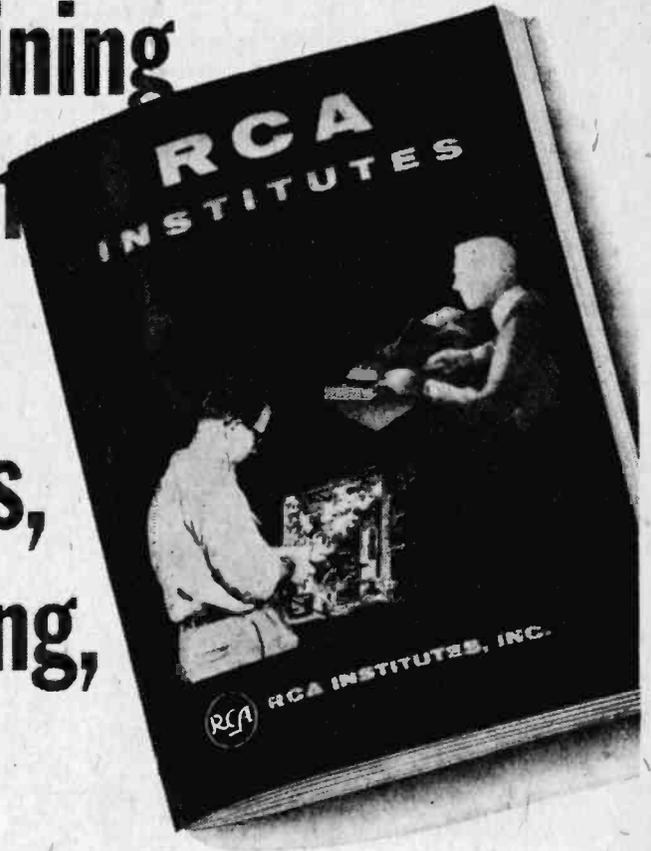**RCA offers you the  
 finest training  
 at home in  
 Radio-TV  
 electronics,  
 TV servicing,  
 Color TV**



**SEND FOR THIS FREE  
 BOOK NOW!**



**RCA INSTITUTES**

A SERVICE OF RADIO CORPORATION OF AMERICA  
 350 WEST FOURTH STREET, NEW YORK 14, N. Y.

In Canada - RCA Victor Company, Ltd.  
 5001 Cote de Liesse Rd., Montreal 9, Que.

RESIDENT SCHOOL courses in New York City offer comprehensive training in Television and Electronics. Day and evening classes start four times each year.  
 Detailed information on request.

**Pay-as-you-learn. You need pay for only one study group at a time. Practical work with very first jesson. All text material and equipment is yours to keep. Courses for the beginner and advanced student.**

RCA Institutes, Inc., Home Study Dept. RTVE-12  
 350 West Fourth Street, New York 14, N. Y.  
 Without obligation, send me FREE 52 page CATALOG on Home Study Courses in Radio, Television and Color TV. No Salesman will call.

Name .....  
 Please Print

Address .....

City ..... Zone ... State .....

KOREAN VETS! Enter discharge date .....  
 To save time, paste coupon on postcard

Abraham Marcus, co-author of famous best-seller "Elements of Radio" makes amazing offer!



**TRY MY TV and RADIO REPAIR COURSE FREE FOR 1 MONTH**

"If you haven't earned at least \$100 in spare time during that period you pay not a cent."

Here it is! The most amazing guarantee ever offered on any radio-TV course anywhere! We'll send you Abraham Marcus' course to use FREE for one full month! If in that time you haven't actually made \$100 fixing radios and TV sets, just return the books to us and pay not a penny!

Why do we make this sensational offer? First, because these books are so easy to use. They are written in the same clear, easy-to-understand language that made the author's "Elements of Radio" a 1,000,000-copy best-seller. Second, because these books set right to the point—tell you what to do in 1-2-3 fashion. For example, once you master the first few chapters of the TV book you are ready for business—ready to do service jobs in the field—jobs that account for over 80% of all service calls.

**DON'T WAIT!** You risk nothing when you send the coupon below. You don't have to keep the books and pay for them unless you actually make extra money fixing radios and TV sets. Even when you decide to keep them, you pay on easy terms. Mail the coupon now.



**WHAT YOU GET IN THESE 3 GIANT VOLUMES**

**ELEMENTS OF TELEVISION SERVICING.** Analyzes and illustrates more TV defects than any other book, and provides complete step-by-step procedure for correcting each. You can actually SEE what to do by looking at the pictures. Reveals for the first time all details, theory and servicing procedures for the RCA 28-tube color television receiver, the CBS-Columbia Model 205 color set, and the Motorola 19-inch color receiver.

**RADIO PROJECTS.** Build your own receivers! Gives you 10 easy-to-follow projects, including crystal detector receiver—diode detector receiver—regenerative receiver—audio-frequency amplifier—tuned radio-frequency tuner—AC-DC superheterodyne receiver—etc.

**RADIO SERVICING Theory and Practice.** Here is everything you need to know about radio repair, replacement, and adjustment. Easy-to-understand, step-by-step self-training handbook shows you how to locate and remedy defects quickly. Covers TRF receivers; superheterodyne receivers, short-wave, portable, automobile receivers, etc. Explains how to use testing instruments, such as meter, vacuum-tube voltmeters, tube checkers, etc., etc.

**MAIL THIS COUPON**

Prentice-Hall, Inc., Dept. 5747-A3  
Englewood Cliffs, New Jersey

Please send me Abraham Marcus' TV & RADIO REPAIR COURSE (3 volumes) for 10 days FREE examination. Within 10 days I will either return it and owe nothing, or send my first payment of \$5.60. Then, after I have used the course for a FULL MONTH, if I am not satisfied I may return it and you will refund my first payment. Or I will keep the course and send you two more payments of \$5.60 a month for two months.

Name .....

Address .....

City ..... Zone ..... State .....

The newest hobby under the sun!

**BUILD THIS SOLAR POWERED RADIO!**


and many other sun-powered electronic, electrical and photometric devices featuring International Rectifier Corporation SUN BATTERIES!

Everyone—from the beginner with a basic understanding of electrical work to the experienced professional engineer—can build this pocket-size portable radio—powered by the sun! No batteries—not even an On-Off switch. All you need is sunshine! The basis for this radio is the International B2M Sun Battery. This unit is a scientific, accurate, precision-made photovoltaic instrument that directly converts light into electrical energy. This radio is just one of many devices you can build powered by solar energy. You have read about this new field of science. Be among the first in this newest hobby. Put the sun to work for you!


THIS NEW BOOK TELLS YOU ALL ABOUT SUN BATTERIES—PHOTOCELLS—AND HOW TO USE THEM. Packed with information and applications, this illustrated book shows wiring, diagrams and plans—every detail necessary to build many interesting devices.

\$150

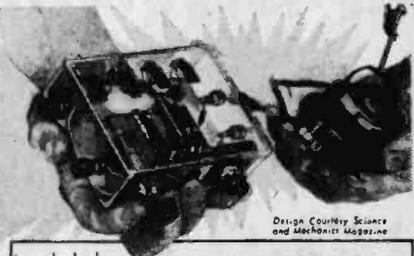THIS IS THE FAMOUS B2M SUN BATTERY YOU'VE READ ABOUT. Widely used in experiments, this unit in bright sunlight (10,000 ft. candles) will deliver 2 milliamperes at 250 millivolts under optimum conditions; will last indefinitely with proper care. A \$2.50 value for only.....\$1.50



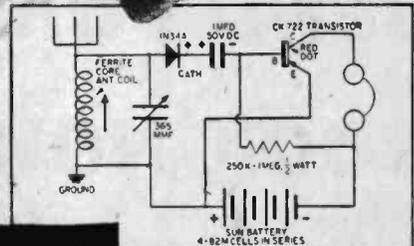Design Courtesy Science and Mechanics Magazine



FREE

Complete plans for building this radio. At your electronic parts distributor.

GET THE B2M SUN BATTERY AND ALL OTHER COMPONENTS REQUIRED AT LEADING ELECTRONIC PARTS DISTRIBUTORS EVERYWHERE. If your favorite distributor doesn't feature the B2M Sun Battery send check or money order to

International Rectifier Corporation  
El Segundo, California

**SPECIAL OFFER, The book and the B2M Sun Battery for only \$2.85 at your distributor**

# Let me send you this amazing - ELECTRONIC KIT!

OWN THIS ELECTRONIC KIT



## ASSURE YOURSELF OF FINANCIAL SECURITY—INDEPENDENCE

Imagine being able to fix anything electrical from the tiniest home electric shaver to large industrial motors! Having a training that makes you command a better job with higher wages or a business of your own. You do not need previous special schooling. Just the ability to read and be mechanically inclined. We furnish you with everything! One of the kits sent to you is our famous ELECTRONIC KIT, an all-purpose trouble detector which shows you where the trouble lies. Training kits whose assembly will give you practical shop training at home during your spare time!

You learn practical electricity by using your hands. Best of all, these kits are yours to keep and use forever!




FRAZER

## REPAIR ELECTRICAL EQUIPMENT!
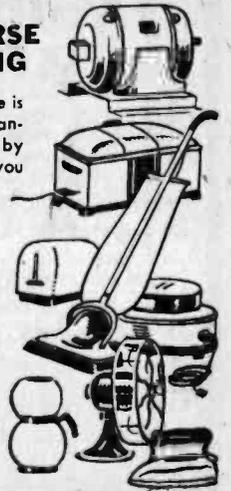
### ILLUSTRATED COURSE SHOWS EVERYTHING

The Christy maintenance and repair course is written in simple, easy-to-understand language. Each section is profusely illustrated by photographs and drawings and shows you what troubles to look for and then how to correct them. In addition, our course shows you how to build power tools at low cost. Also teaches you welding, nickel plating, general repairing (saw filing, bicycle and gas stove repairing, etc.). Should complicated technical problems arise or the need for a special repair part, simply call on us. We offer YOU our FREE Advisory Service for LIFE! We teach you how to solicit business get repeat orders and what to charge. The Christy Course plus our home-shop training kits make a combination that will go a long way toward ASSURING YOUR SUCCESS.



## 3 EASY STEPS TO SUCCESS

- ① WE SEND YOU AN ELECTRIC KIT
- ② WE TEACH YOU ELECTRICAL APPLIANCE REPAIRING
- ③ WE GIVE YOU LIFE-TIME ADVISORY SERVICE

## RUSH THIS COUPON TODAY!

CHRISTY TRADES SCHOOL, Dept. D-311  
4804 N. Kedzie Ave., Chicago 25, Ill.


Please send me your FREE book on Electric Equipment Servicing and instructions for paying later from EARNINGS WHILE LEARNING!

Name.....Age.....

Address.....

City.....Zone.....State.....

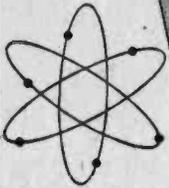**Interesting, Pictorial  
FREE  
BOOKLET**



**to help you decide on  
your career in  
ELECTRONICS  
RADIO-TV  
COMPUTERS**

Here is a graphic story about preparing for your career as an engineer or engineering technician in electronics, radio, television, computers, etc. Booklet tells about:

- Wide variety of job opportunities
- Courses offered, degrees you can earn
- Pictures of the Milwaukee School of Engineering and its facilities
- Recreation and fraternities
- Scholarships; part-time work

—plus other interesting and informative facts to help you make a sound decision on your career. MS-90

**Milwaukee School of Engineering**  
— dedicated to serving young men and industry

**SEND COUPON TODAY!**

**Milwaukee School of Engineering**  
Dept. RTX 58, 1025 N. Milwaukee St., Milwaukee, Wis.

Please send me free new booklet  
"Prepare for Your Career in Engineering"

I'm interested in \_\_\_\_\_  
(name of course)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

I am  I am not eligible for veterans educational benefits. (discharge date)

**CRYSTAL MICROPHONE**

**Built-In Volume Control**

For p.a. systems, radio amateurs, recording enthusiasts. Exceptional frequency characteristics. Response: 50 cps to 10 kc. Output level: -62 db. Case finished in black and satin chrome.



Regular \$18.00 Value

**ONLY \$4.95 EACH**


**POCKET CIRCUIT TESTER**

**Volts • Ohms • Mills**

Big 3-in. meter. Ranges: AC and DC volts: 0-10-50-250-500-2500; DC ma: 0-5-50-500; ohms: 0-10,000-1 meg. Two ranges for db. Size: 4 3/4" x 3 1/4" x 1 1/2". Grey finish. Complete with test leads.

Regular Price: \$14.90

**ONLY \$5.95 EACH**

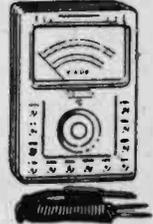

Send check or M.O. for payment in full. Money-back guarantee. Merchandise shipped postpaid.

Calif. customers add 4% sales tax.


**Electronic Equipment Distributors, Inc.**

3686 El Cajon Blvd. • San Diego 4, Calif.

**ETCHES AND SOLDERS-101 USES**

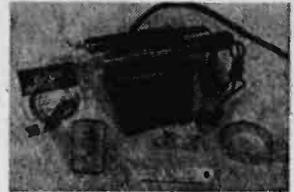**ACTOGRAPH UNIT**

Safe as a pencil, easy to use. This new home model is patterned from our Industrial Unit. With an electric Arc it etches any metal; iron, steel, brass, aluminum, gold, etc. Engrave initials, names, part numbers on tools, jewelry, chassis, toys . . .



Solder the modern way with carbon electrodes, instant intense concentrated heat as soon as tool touches work. No more cold joints. This Actograph unit is a must for the modern work shop. Either tool may be operated directly from car battery. Money back guarantee, order C.O.D. \$19.95. For further information.

**NEWAGE INDUSTRIES, 222 York Road, Jenkintown, Pa.**

**Enjoy Thrilling High-Fidelity  
Super HI-FI FM Record Player**

Build this high-fidelity, frequency modulated phono oscillator and bring your wax-works to life, enjoy all the sound you pay for from your recordings. Full-size pictorial and schematic wiring diagrams, complete materials list, illustrated, step-by-step assembling instructions. Order Craft Print No. 264 now.



**Price \$1.00**

**SCIENCE AND MECHANICS**

450 East Ohio St.

Dept. 5312

Chicago 11, Ill.

Prepare for a Good Paying Job—Or Your Own Business

Learn **PRACTICAL RADIO-TV**  
with **25 BIG KITS**



of equipment I send you while  
you train with me... for valuable  
shop bench experience...



The new Sprayberry Training  
Television receiver, built  
and tested in sections.

I now offer this fine modern  
oscilloscope.

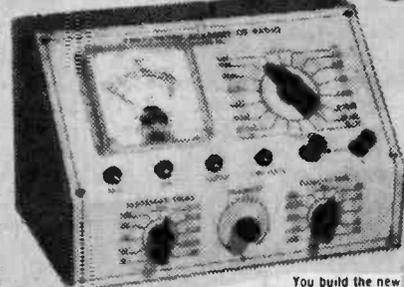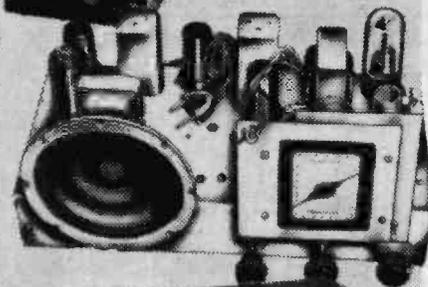You build this powerful 2  
Band superhet radio re-  
ceiver.



You build the new  
Sprayberry Tester 18-range  
Volt-Ohm-Milliammeter readings.

**Average cost per lesson**  
**ONLY \$3.42**

Including Kits and Equipment

**"I Will Train You at Home in  
RADIO-TELEVISION  
on Liberal No Obligation Plan!"**

New Equipment! New Lessons! Enlarged  
Course! The true facts are yours in my  
big new catalog... **YOURS FREE...**  
**JUST MAIL COUPON!**



Frank L. Sprayberry  
EDUCATIONAL DIRECTOR

I can train and prepare you in as little as 10 months to step into the big opportunity Radio-Television service field. Train *without* signing a binding contract... without obligating yourself to pay any regular monthly amounts. You train entirely at home in spare hours... you train as fast or as slowly as you wish. You'll have your choice of **THREE SPRAYBERRY TRAINING PLANS**... planned for both beginners as well as the more experienced man. Get the true facts about the finest most modern Radio-Training available today... just mail the coupon for my big new 56 page fact-filled catalog plus sample lesson—both **FREE**.

**Train the Practical Way—with Actual Radio-Television Equipment**

My students do better because I train both the mind and the hands. Sprayberry Training is offered in 25 individual training units, each includes a practice giving kit of parts and equipment... all yours to keep. You will gain priceless practical experience building the specially engineered Sprayberry Television Training Receiver, Two-Band Radio Set, Signal Generator, Audio Tester and the new Sprayberry 18 range Multi-Tester, plus other test units. You will have a complete set of Radio-TV test equipment to start your own shop. My lessons are regularly revised and every important new development is covered. My students are completely trained Radio-Television Service Technicians.

**NEWEST DEVELOPMENTS**

Your training covers U H F, Color Television, F.M., Oscilloscope Servicing, High Fidelity Sound and Transistors.

**See for Yourself... Make Your Own Decision  
... Mail Coupon Today!**

The coupon below brings you my big new catalog plus an actual sample Sprayberry Lesson. I invite you to read the facts... to see that I actually illustrate every item I include in my training. With the facts in your hands, you will be able to decide. *No salesman will call on you.* The coupon places you under no obligation. Mail it now, today, and get ready for your place in Radio-Television.

**SPRAYBERRY ACADEMY OF RADIO-TELEVISION**

1512 Jarvis Ave., Dept. 212-C, Chicago 26, Illinois

**Mail This Coupon For Free Facts and Sample Lesson**



**SPRAYBERRY ACADEMY OF RADIO-TELEVISION**  
1512 Jarvis Ave., Dept. 212-C, Chicago 26, Illinois

Please rush all information on your **ALL-NEW** Radio-Television Training Plan. I understand this does not obligate me and that *no salesman will call upon me.* Include New Catalog and Sample Lesson **FREE**.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

# Grommes Little Genie HI-FI KITS



**NEW!**

So simple...it's like magic!  
LAYER-BUILT • COLOR-GUIDE

Each Kit complete with all parts and instructions




**NEW**  
**LJ-6K**  
**\$24.95**

**LJ-6K 10 Watt Amplifier (Little Jewel).** Highest value in the low priced field, with built-in pre-amplifier and record compensator on phono channel. Freq. Response:  $\pm 1\text{DB}$  20 to 20,000 CPS at 1 watt. Distortion: 2% harmonic or less at 10 watts. In Charcoal and Brass. Shpg. Wt. 10 lbs. Complete Kit and Instructions.....Net 24.95



**NEW**  
**207A-K**  
**\$44.50**

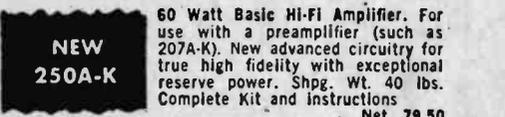**207A-K Hi-Fi Pre-amplifier.** The ideal control unit with self-power feature for use with any basic amplifier. True flexibility with 10 separate controls. Feedback throughout for low distortion and wide frequency response. In charcoal gray and brass. Shpg. Wt. 10 lbs. Complete Kit and Instructions.....Net 44.50



**NEW**  
**250A-K**

**60 Watt Basic Hi-Fi Amplifier.** For use with a pre-amplifier (such as 207A-K). New advanced circuitry for true high fidelity with exceptional reserve power. Shpg. Wt. 40 lbs. Complete Kit and Instructions.....Net 79.50



**61PG-K**

**20 Watt Amplifier.** With built-in pre-amplifier and all controls. Modern flat compact design for tabletop or cabinet installation. Shpg. Wt. 20 lbs. In Charcoal and Brass. Complete Kit with Instructions.....Net 59.50

See your Hi-Fi Dealer or write . . .

**Grommes**—A Division of Precision Electronics, Inc., Dept. EX-12, 9101 King Ave., Franklin Park, Illinois

Send complete Kit details.  Send.....Kit.  
 COD (\$5 enclosed).  Postpaid. (Full payment enclosed. Enclose name of Dealer. (If any.)

Name.....

Address.....


City.....Zone.....State.....

10-day money back guarantee on all Kits

**WALKIE-TALKIE** Transmitter & Receiver Chassis. New. Wired, with Tubes. **\$6.65**

**NEW! Gyro Low-cost**

## RADIO CONTROL RECEIVER

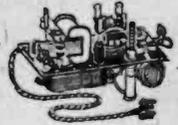

Brand New, Completely Wired & Tested w. Tube, Relay & Installation Kit. Ready-To-Fly, only 3 os. **\$8.61**

Before You Buy—Compare: (27.255 Mc)

**The Most Powerful Hand Held R/C TRANSMITTER** GYRO Model Aq1



• Greatest Power—up to 5 watts input  
• Greatest Distance—Range up to 3 sq. miles  
• Gyro Magic Tuning Indicator—simplest tuning  
• Versatile—operates from 90-180 Volts "B"  
• Complete & Guaranteed with Antenna.  
Ready to operate (less bttry) \$17.95; Complete KIT **\$11.95**

## RADIO CONTROL Headquarters

For model airplanes, boats, cars, etc. **FREE CATALOG "S."** No operator's license required. **FREE—SEND FOR FCC FORM 505** Garage Door Radio Control Transmitting & Receiver Kits Available. **R/C TRANSMITTER & RECEIVER KIT:** 27.74 mc. 5 watt 2-Tube Simple Transm. & 2-Tube Rec incl. Drilled Bases, **\$9.95** Wound Coll. Res., Cond., SIGMA Relay, Instruc. ....

SIGMA 4F RELAY: 8,000 ohm. \$4.25; 6 Reed Relay. .... 14.95  
2-6V Battery Charger Kit \$4.95 ..... wired 6.95  
R/C BOOKS: Model Control \$1; Radio Control \$1; Handbook 2.25  
CRYSTALS: 27.255 Mc. Peterson 29A. .... \$3.95; HOLDER .15  
Flash STROBOSCOPE 110V AC, Range 900-14000 per min. .... 19.85  
factory wired and tested. .... 2.95  
2" METERS, O.J. Ma. \$3.65; 800 MicroA. \$3.95; 3 Ma. .... 2.95

**RELAY CONTROL UNIT** incl. Sensitive 10,000 ohm Sigma Relay (1 1/2 Ma) Thermal Bi-metal Strip. Heating Element, Hi Z Audio Choke, Mini **99c**  
Ainco V Magnet, Neon Lamp, Resistors, Capacitors. .... only  
TUBES: XF01, RK61, 3A4, 3A5, 1A0A, 1A0A, 6X4, Transistor .99  
Mini Storage Cells, 2V 75¢; 1 1/2V Elect. Motor. .... .85  
RELAYS: 10K ohm 2 Ma DC or 110V AC SPDT 95¢; SPST .85  
CHARGER for DRY BATTERIES: Use 2 set of A & B's all season! Charges all batteries; 1 1/2 to 90V up to 8 times 4.95  
DYNAMOTOR 6V/12V—180V/360V @ 100 Ma. .... 2.95  
NEW! Pocket MULTITEST 3000 ohms per volt 11 ranges, checks volts, AC/DC, Milliamps, Resistors, etc. Complete ..... 9.95  
Experimenters' world-famous. .... 4.45  
EARPHONE: Single, Plug-In Ear Type. .... 1.95  
EARPHONES: Standard, Dual 2000 ohm. .... 2.45

**GYRO ELECTRONICS CO.** 328-S Canal St. New York 13, N. Y.



## unlimited opportunity for graduate engineers

Industrial growth . . . automation . . . technical advances create career opportunities for engineers, accountants, management experts. Share rewards awaiting college usa. Important firms visit campus regularly to employ Tri-State College graduates. Start any quarter in the world-famed college. Approved for veterans.

### Bachelor of Science degree in 27 months

Complete Radio Engineering course . . . TV, UHF, FM, Electronics. Also degree courses in Mechanical, Civil, Electrical, Aeronautical and Chemical Engineering. In 26 Months a B.S. in Business Administration (General Business, Accounting, Motor Transport Management majors). Capable students may accelerate. 36-weeks course in Drafting. Intensive program: theoretical fundamentals stressed; comprehensive courses with more professional class work. Small classes; personalized instructions. For earnest, mature students whose time and budget require accelerated course and modest costs. Preparatory courses. Beautiful campus in friendly college town. Well-equipped, new and modernized buildings and laboratories. Enter June, Sept., Jan., March. Write Jean McCarthy, Director of Admissions, for "Your Career in Engineering and Commerce."



## TRI-STATE COLLEGE

3057 College Avenue Angola, Indiana

# INVENTIONS WANTED!

## 140 Wealthy Manufacturers Ready to Pay Top Prices

Do you have an idea for a new product or a way to improve a product already in use—patented or unpatented—you would like to sell for cash or lease on royalty? If so, send your name and address on a post card—NOW—for FREE details explaining how you can turn your "Big Ideas" into big money.

**SCIENCE AND MECHANICS MAGAZINE**  
450 East Ohio Street • Dept. 5513 • Chicago 11, Illinois

# Learn Electronics

## YOUR TICKET TO A BETTER JOB AND HIGHER PAY!

This booklet  
**FREE!**



**More Jobs Than We Can Fill**

Jobs in radio-TV-electronics are going begging. A commercial (not amateur) F.C.C. license is your ticket to higher pay and more interesting employment. We train you quickly - then help you find the job you want!

**Learn by Mail or in Residence**

Grantham School of Electronics specializes in preparing students to pass F.C.C. examinations. Correspondence training is conducted from Washington and Hollywood; resident DAY and EVENING classes are held in both cities. Either way, we train you quickly and well - NO previous training required. Beginners get first class license in 12 weeks.

**Grantham Training Is Complete**

The Grantham course covers all the required subject matter completely. Even though it is planned primarily to lead directly to a first class F.C.C. license, it does this by TEACHING you electronics.

**Our Guarantee**

If you should fail the F.C.C. exam after finishing our course, we guarantee to give you additional training at NO ADDITIONAL COST. Read details in our free Booklet.

**Two Complete Schools**

To better serve our many students throughout the entire country, Grantham School of Electronics maintains two complete schools - one in Hollywood, California and one in Washington D.C. Both schools offer the same rapid courses in F.C.C. license preparation, either home study or resident classes.

*Here's Proof....*

that Grantham Students prepare for FCC examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Wks.
Douglas Moore, 5182 Flambeau Rd., Madison, Wis.	1st	11
Bernard Kirschner, 584 E. 5th, New York, N.Y.	1st	12
Craig Stone, 3838 44th St., NW, Washington, D.C.	1st	22
Albert D. Moolish, Box 138, Elrama, Pa.	1st	12
Don Brocco, Station RDVE, Lander, Wyo.	1st	12
Richard Moolan, 188 Jerome St., Brooklyn, N.Y.	1st	18
Lee Bishop, 37 Calle Concha, Flagstaff, Ariz.	1st	12
Carl Deane, Jr., P.O. Box 487, Jeanerette, La.	1st	11
Jackson York, 1828 N. Quincy St., Arlington, Va.	1st	15

GET YOUR FIRST CLASS COMMERCIAL **F.C.C.**  
**License in 12 Weeks!**

at

### GRANTHAM

School of Electronics



1505 N. Western Ave.  
Hollywood 27, Calif.  
(Phone: HO 2-1411)

821 - 19th Street, N.W.  
Washington 6, D.C.  
(Phone: ST 3-3614)

**MAIL COUPON TO NEAREST OFFICE**

(Mail in envelope or paste on postal card)

### Grantham Schools, Desk M

1505 N. Western Ave. OR 821 - 19th Street, N. W.  
Hollywood 27, Calif. OR Washington 6, D. C.

Please send me your booklet, telling how I can get my commercial FCC license quickly. I understand there is no obligation and no salesman will call.

Name..... Age.....

Address.....

City..... State.....

I am interested in:  Home Study,  Resident Classes

see the amazing new  
EASY-TO-BUILD ELECTRONIC  
**ALLIED knight-kits**



in **ALLIED'S 1958**

**ELECTRONIC SUPPLY CATALOG**

**FREE!**

**BUILD YOUR OWN!  
SAVE MONEY—HAVE FUN**



**HI-FI KITS**



**HOBBY KITS**



**INSTRUMENT KITS**



**HAM KITS**

**404** value-packed pages

**SAVE** on Everything In Electronics

**WORLD'S LARGEST STOCKS**

Everything for Experimenters, Builders, Amateurs, Servicemen, Engineers and Hi-Fi Hobbyists. Get more for your money in Hi-Fi systems and components; build-your-own KNIGHT-KITS; recorders and phono equipment; TV tubes, antennas, accessories; Amateur station equipment; test instruments; industrial electronic equipment—plus the world's largest stocks of parts, tubes, transistors, tools and books. Send today for your **FREE 1958 ALLIED Catalog!**

Everything in Electronics From One Reliable Source  
our 37th year **EASY TERMS AVAILABLE**

**ALLIED RADIO**

send for  
**FREE**  
Catalog

**ALLIED RADIO CORP., Dept. 64-8  
100 N. Western Ave., Chicago 80, Ill.**

Rush **FREE 1958 ALLIED 404-Page Catalog**

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**FARM**

**TELEPHONE CABINETS**



Slightly used crank style CABINETS (once used everywhere) for Home Hobby Shops. Complete with transmitter, receiver, bells, crank and shelf (Less Generator). Has all of the outside parts. Make beautiful, unique Radio Cabinets, Liquor Chests, Spice Cabinets, Flower Planters, etc. Immediate deliveries assured. \$7.00 F.O.B. Chicago.

**TELEPHONES**

and **ALL SUPPLIES**

Room to room, house to garage, private telephone service.  
**HANDSET ORADLE TELEPHONES (2)** Complete outfit with 100' wire, 2 dry cells, instructions, \$14.95.  
**WORM HARVESTER—Dan Mac Magneto**—gathers fish-worms by electricity. Complete with instructions, \$6.50.



**WRITE FOR ILLUSTRATED BULLETIN BB-2**

**MICROPHONE, Dept. BB-2, 1760 W. Lunt Ave. Chicago 26, Ill.**

**Like to Build Models?**

**Try One of These 32**

**Projects**

If you would like to build a model 1909 Stanley Steamer, a radio-controlled Model Chevrolet, a steam-powered Mississippi River boat, an 1834 Hansom Cab, an Oscillating Steam Engine, a Model Colt .44 Pistol, model circus equipment, model airplanes, a 4-cylinder racing engine—in all 32 outstanding projects, get a copy of our 160-page, "Model Craft Handbook," that is jammed with model plans and ideas. You'll get the thrill of a lifetime! Every model is authentic to the smallest detail. Hundreds of photographs and diagrams show exactly H.O.W. to proceed. Bills of materials simplify the laying out of the work. Our easy-to-follow instructions explain every detail. Send 50¢ for Vol. 8, "Model Craft Handbook." Satisfaction guaranteed. Catalog of 151 "Do-It-Yourself" Plans, 10¢.

**SCIENCE AND MECHANICS**

450 East Ohio St., Dept. 5314  
Chicago 11, Ill.



# TRANSISTORIZED POCKET FM RADIO AND TUNER KIT



Fun for the youngster or the veteran in the electronics field . . . A 3-way transistorized pocket FM radio and tuner which tunes the complete FM band from 88 to 108.6 megacycles plus aircraft band from 109 to 145 megacycles. This fantastic set can be used in your car, home, or pocket, and needs no antenna or ground wires. Completely non-directional, this compact FM radio and tuner will play where all other radios have failed. Set has been demonstrated under an X-ray beam and near other electrical devices without any static or distortion. Featuring a two-stage circuit, this FM radio and tuner will produce music of top quality from stations located many miles from the receiver. Kit comes complete with easy-to-build instructions.


**Kit, Complete, \$13.95 postpaid.**

**Special Hi-Fi Earpiece with earmold, cord, and plug, \$8.50 postpaid.**
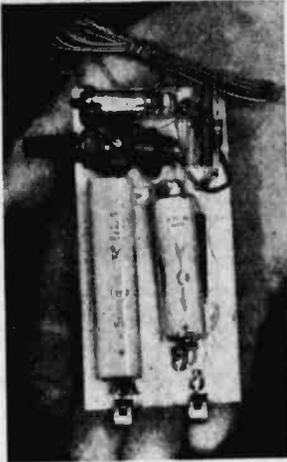
## TWO-STAGE TRANSISTOR AMPLIFIER OR PRE-AMP KIT



You can build a powerful two-stage amplifier or pre-amp which can be used as a phonograph amplifier or amplifier for a crystal set, and as a pre-amp for crystal or magnetic pick-ups. Kit comes complete with two transistors, volume control with switch, attractive plastic case with a snap bottom, and is powered with a single penlight cell with an output of nearly  $\frac{1}{2}$  of a watt. Complete with easy-to-follow instructions. \$5.95 postpaid.



**ALL WAVE KIT**

## IT'S HERE—REAL SATELLITE RADIO

• Tunes all short wave bands plus Broadcast Bands. Complete Kit with Transistor, High Frequency Tube—And double head set:

(limit 3 to a customer) **\$995** postpaid

## UNBELIEVABLE—BUT TRUE! FM RADIO TUNER

(World's Smallest)  
Free With Each Tuner

A plan of a two-stage transistor amplifier that works well with the famous (EKERADIO) FM Tuner. (Each Tuner has been Air Tested before being shipped.)



**\$995**

- Installs Easily • Fits Any Radio
- Gives Beautiful FM Fidelity

Does the work of regular 8-tube tuner . . . easily installs in car or home radio. Tunes complete FM band from 88 to 108 mgs. and 109 to 145 mgs. on aircraft FM band. Tuner includes complete wired chassis, switch, tuning knob and diagram.

**EKERADIO ELECTRONIC DEVELOPMENTS**  
Dept. E • 650 North Fair Oaks Avenue • Pasadena, California

## INVALUABLE FOR BEGINNERS!

Let Us Demonstrate FREE How Quickly  
You Can Master Fundamentals of

# RADIO, TELEVISION, ELECTRONICS, HI-FI

An ideal way for you to get started in a big-pay career or develop a profitable hobby is offered in this remarkable new book. Makes understanding marvels of radio, TV, and Hi-Fi so simple. Used by scores of schools and colleges to unveil mysteries of rapidly growing use of electronics. One reading gives you complete background essential to determine choice of profession. Packed with recent inventions, newest uses. A gold-mine of up-to-the-minute information for servicemen, technicians, hobbyists, students. 288 photos, charts, diagrams.

### FREE 5 DAY EXAMINATION

Fill out and mail coupon. Pay nothing now. Pay nothing to postman on delivery. Simply pay bill after 5 days, or return book.

**AMERICAN TECHNICAL SOCIETY**  
Dept. DC-1, 848 E. 58th St., Chicago 37, Ill.

**AMERICAN TECHNICAL SOCIETY, Dept. DC-1**  
848 E. 58th St., Chicago 37, Ill.

Please send me "Radio-Television and Basic Electronics" for 5 days FREE EXAMINATION. If I keep the book after 5 days, you may bill me for \$4.95, plus shipping costs.

PRINT NAME .....

ADDRESS .....

CITY ..... ZONE ..... STATE .....

Check here if enclosing \$4.95 with coupon; we pay shipping charges. Money back guarantee.

## 186 Do It Yourself Plans ILLUSTRATED CATALOG 10¢

NOW YOU CAN get simple, easy-to-understand plans for building boats, electrical equipment, models of gas and steam engines, famous firearms, antique automobiles, toys, games, cabin trailers, many other projects. In all, 186 useful things you can build. It's easy! It's fun! And you can save money! Do It Yourself! Send 10c now. Science and Mechanics Magazine, 6616 Dunham Bldg., Chicago 11, Ill.



## Electronics School

Midwest's First & Foremost  
(Our 27th Year)

### 10-MONTH RESIDENT SHORT-COURSE

Special 5 in 1 training embraces Electronics, Radio, TV, Communications, and Color TV. Prepares for FCC License. Vet Approved. Free placement. Thousands grads coast-to-coast. Also home study. Send coupon for free information.

**UNIVERSAL TV SCHOOL** 804-K Grand, Kansas City 6, Mo.

Name ..... Age .....

Address .....

City ..... State .....

Veterans give discharge date .....

### SCIENCE OF MODERN ELECTRONICS MADE EASY

#### CONTENTS INCLUDE:

Recent Developments in Electronics, Electrical Measuring Instruments, Oscillatory Circuits, Electron Tubes, Power Supplies, Amplifiers and Amplification, Tape Recorders, Acoustics, Microphones, Transmitting and Receiving Antennas, AM and FM Receivers, High Fidelity Systems, Transistors, Television.

**ONLY \$4.95** if you keep it

**WELD** **BRAZE**  
**SOLDER** **CUT**

**NOW ANYONE CAN  
WELD FOR PLEASURE  
OR PROFIT**

Do your own on-the-spot soldering, brazing, cutting, etc. Make your own beautiful wrought iron furniture and knick-knacks for the home, garden, garage or farm. Repair all metal equipment—bodies, fenders, etc. with this compact, handy portable welder. Easily operated from properly wired 110V AC or DC lines, complete as illustrated with twin carbon arc torch and operating instructions. Order today on ten-day money back guarantee or send for FREE illustrated literature. Literature on larger equipment on request.

**FOUR-WAY WELDER CO., Dept. F82-N**  
1810 S. Federal Street • Chicago 16, Ill.



**4 WAY**  
ONLY  
**\$14.75**  
f.o.b. factory

**WELDER**

Complete with  
Twin Carbon Arc  
Torch and accessories... to handle all metal-craft work.

## THE BIGGEST 25¢ BARGAIN IN THE ELECTRONICS INDUSTRY

Yes, just 25¢ will bring you the next 12 issues of our monthly bargain-packed bulletin, featuring: Motors, Meters, Relays, Timers, Blowers, Pumps, and thousands of outstanding electronic devices. Just a quarter starts you on the bandwagon of values.

**HERBACH & RADEMAN, INC.**

1204 Arch Street, Dept. TV-1, Philadelphia 7, Penna.

*for the best in electronics—receivers,  
transmitters, meters, multitestors, trans-  
formers, relays, sun batteries, wireless  
headsets, the cream of domestic and  
foreign surplus at lowest prices ever!—  
send for our new, free, bargain-rich  
flyer!—you'll be glad you did!*

**ARROW SALES, INC.**

Box 3007-SM

North Hollywood, Calif.



**UPRIGHT BRASS  
TELEPHONE FOR LAMPS!**

Mouthpiece and receiver bakelite.

**ORIGINAL OAK WOOD**

**Antique TELEPHONES!**

Write for free list of telephones.

All shipments F.O.B. Simpson, Pa.

**TELEPHONE ENGINEERING CO.**

Dept. RT

Simpson, Pa.



New Isotronic Training Method!

## LEARN TV REPAIR IN ONE SHORT WEEK

Now, after 5 years research—a dynamic TV training technique that makes others obsolete! If you've waited for a chance to have your own prosperous business, here's an opportunity to make up to \$150 weekly—almost immediately!

**NO EXPENSIVE TRAINING—NO LONG STUDY!**

You want to get started servicing TV sets—not building them! So, why pay up to \$250 for high-priced lessons and equipment... study long months? Our revolutionary ISOTRONIC method qualifies you to handle any make TV set right away! All the complicated technical theory is already taken care of by our Scientists! This new technique—hailed the most practical in the field—was developed by two of the industry's most respected scientists, in cooperation with every major American TV manufacturer!

**PUT YOUR "KNOW HOW" TO WORK FOR PROFIT!**

In addition to the most streamlined training program of its type, you also benefit from a complete Business Plan that explains fully how to start, conduct, and expand your own TV Service business. Written by expert business consultants. Packed solid with practical know-how instead of theory! Yes, a complete "Business Package" designed to quickly bring you the good things in life that come with your own successful business.

**FREE LESSON PROVES ISOTRONIC METHOD WORKS!**

For conclusive proof, send now for full details and **FREE SAMPLE LESSON**. Apply it to your own ailing set or a friend's—repair it without a single tool or testing device—convince yourself that the amazing Isotronic method can put you in a profitable TV business of your own, in one short week!

Write today—free lesson supply limited! (No obligation, no salesman will call.)  
ELECTRONIC ENGINEERING CO., Dept 8-571  
1038 So. La Brea, Los Angeles 19, California

**FREE!**  
Sample  
Lesson

## How to Build Your Own Photo Equipment

It's Easy! It's Fun! And you can save lots of money, too! Our 160-page "Photo Craftsman" Handbook explains H-O-W to build 90 different pieces of photographic Equipment. Hundreds of photos, drawings, diagrams, tables, bills of materials and step-by-step instructions make it as easy as ABC to build precision photo equipment. Send 50¢ for this big handbook of plans now!

**90 "Do It Yourself"**

**Plans 50¢**



### How to Build—

- Photo Enlarger
- Home Movie Titler
- LowCost Speedlight
- Boom Light
- Copying Stand
- Tray Raker
- LowCost Flashgun
- Rotary Washer
- Processing Tanks
- Flash Synchronizer
- Film Viewer
- Electronic Timer
- and 78 other useful projects.

**SCIENCE AND MECHANICS MAGAZINE**

5516 Dunham Building - - Chicago 11, Illinois

## FREE LAFAYETTE CATALOG

JUST OFF THE PRESS!  
NEW 180 PAGE ELECTRONIC CATALOG FEATURING  
THE BEST BUYS IN THE BUSINESS

Packed with the largest selection of Electronic, Radio and T.V. Parts and equipment, PA, HI-FI systems, tubes, antennas, Transistor Kits, parts and components, Test Equipment, new build your own kits, tools, books, Microscope, drafting equipment, Binoculars, Telescopes, All Radio, TV and Ham supplies—ALL AT GREAT SAVINGS! —For the economy minded serviceman, dealer, engineer and technician. **CHUCK FULL OF BUYS! SEND FOR YOUR FREE COPY TO-DAY.**

**LAFAYETTE RADIO**

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**Lafayette Radio** P. O. BOX 511  
JAMAICA 31 N. Y.

# Complete Training FOR BETTER RADIO-TV SERVICE JOBS



Let these two great Ghirardi training books teach you to handle all types of AM, FM and TV service jobs by approved professional methods—and watch your efficiency and earnings soar!

Each book is a complete service training guide. Each contains the complete data on modern methods and equipment—Not a re-hash of old, out-of-date material. Each is co-authored by A. A. Ghirardi whose famous RADIO PHYSICS COURSE and MODERN RADIO SERVICE were, for 20 years, more widely used for military, school and home study training than any other books of their type!

## THE NEW Ghirardi RADIO-TV SERVICE LIBRARY

Almost 1600 pages and over 800 clear illustrations show step-by-step how to handle every phase of troubleshooting and servicing.

### 1—Radio and Television Receiver TROUBLESHOOTING AND REPAIR

A complete guide to profitable professional methods. For the beginner, it is a comprehensive training course. For the experienced serviceman, it is a quick way to "brush up" on specific jobs to develop improved techniques or to find fast answers to puzzling service problems. Includes invaluable "step-by-step" service charts. 820 pages, 417 illus., price \$7.50 separately.

### 2—Radio and Television Receiver CIRCUITRY AND OPERATION

This 669-page volume is the ideal guide for servicemen who realize it pays to know what really makes modern radio-TV receivers "tick" and why. Gives a complete understanding of basic circuits and circuit variations; how to recognize them at a glance; how to eliminate guesswork and useless testing in servicing them. 417 illus. Price separately \$8.75.

**Special low price . . . you save \$1.25**

If broken into lesson form and sent to you as a "course," you'd regard these two great books as a bargain at \$50 or more! Under this new offer, you save \$1.25 on the price of the two books—and have the privilege of paying in easy installments while you use them! No lessons to wait for. You learn fast—and right!

### STUDY 10 DAYS FREE!

Dept. MM-O, RINEHART & CO., Inc.  
232 Madison Ave., New York 16, N. Y.

Send books below for 10-day FREE EXAMINATION. In 10 days I will either remit price indicated (plus postage) or return books postpaid and owe you nothing.

Radio & TV Receiver TROUBLESHOOTING & REPAIR (Price \$7.50 separately)

Radio & TV CIRCUITRY & OPERATION (Price \$8.75)

Check here for **MONEY-SAVING COMBINATION OFFER**  
Save \$1.25. Send both of above big books at special price of only \$13.00 for the two. (Regular price \$14.25 . . . you save \$1.25.) Payable at rate of \$4 plus postage after 10 days if you decide to keep books and \$3 a month for 3 months until the total of \$13.00 has been paid.

Name \_\_\_\_\_

Address \_\_\_\_\_

City, Zone, State \_\_\_\_\_

Outside U.S.A.—\$2.00 for TROUBLESHOOTING & REPAIR; \$7.25 for CIRCUITRY & OPERATION; \$14.00 for both. Cash only, but money refunded if you return books in 10 days.

# SHOOT TV TROUBLE FAST

## With H. G. Cisin's Copyrighted RAPID "TV TROUBLE SHOOTING METHOD"

Without experience or knowledge, this guaranteed new method of servicing TV sets enables you to **DIAGNOSE** TV troubles as rapidly as an expert. **NO THEORY—NO MATH**—you can locate all faults in record-breaking time regardless of make or model. "TV TROUBLE SHOOTING METHOD" is the most valuable aid to TV servicing ever written. Be a TV Trouble Diagnostician. Increase your present earnings. Open your own Profitable Business or get a high-paying skilled job.

It's all in this book . . .

**Nothing more to Pay—Nothing else to Buy**

Alphabetically listed are 85 picture troubles, over 58 raster and 17 sound troubles. By this unique copyrighted method you know **EXACTLY WHERE** the trouble is; plus step-by-step instructions, including 89 **RAPID CHECKS**, help to find faulty part. **IS IMPORTANT PRELIMINARY CHECKS NEED NO INSTRUMENTS!** Of the 89 Rapid Checks, **OVER 85 ALSO REQUIRE NO INSTRUMENTS!** Rapid checks include emergency checks for distorted pictures, defective tubes including PIX tube, plus 57 others. **ALL EXPLAINED IN SIMPLE LANGUAGE. PERFORMED WITHOUT INSTRUMENTS. MANY CHECKS USE THE PICTURE TUBE AS A GUIDE.** H. G. Cisin, the author, is the inventor of the AC/DC midgrid radio. He licenses RCA, AT&T, etc. He has also trained thousands of technicians now owning their own prosperous TV service organizations or holding highly paid TV positions. His years of experience are embodied in this remarkable new book.

Guaranteed Money Back in 5 Days if Not Satisfied!

**ABSOLUTELY FREE** with each order: Your choice of Cisin's newest books: **BASIC ELECTRICITY—Vol. 1 or TV-RADIO TUBE SUBSTITUTION GUIDE.** These sell for 50¢ ea. **ACT NOW—get 2 books postpaid at cost of only one!**

**\$1** Post-paid

### RUSH COUPON NOW!

M. G. CISIN, Consulting Engineer—Dept. SM17  
Amagansett, N. Y.  
Enclosed find \$1. Rush Trouble Shooting Method and free book marked above (if not marked Basic Elec. will be sent).

Name .....  
Address .....  
City ..... Zone ..... State .....

NOW!

# FIX TV FAST!

No Experience Necessary—  
New Book Gives You Easy,  
Step-by-Step Instructions

All New! 2nd  
Revised Edition  
**TRANSISTORS  
COLOR**  
UHF and LATEST  
TV CIRCUITS

Get this brand-new, complete handbook for sure-fire how-to-do-it knowledge of TV repair, installation, maintenance and troubleshooting. You'll be amazed how easy it is to fix your own TV set with the help of this manual. And you'll find it equally as easy to make spare-time money fixing TV sets for your neighbors and friends. Perhaps you will want to get a service shop job . . . even start your own full-time business.

USE IT 10 DAYS FREE! Coupon below brings you TELEVISION SERVICING on FREE trial for 10 days, without cost or obligation. Mail it NOW.

You don't need mathematical training to follow the simple, crystal-clear instructions in this book. All possible defects are classified for ready reference, thoroughly analyzed to show what is wrong and why . . . and what to do to correct the fault. You get step-by-step procedures for audio IF alignment, aligning RF amplifiers, mixers, oscillators, etc. . . . how to use the basic tools of the trade . . . how to adjust the ion trap . . . how to install sets and antennas, etc., etc. Contains complete, up-to-date information on color, UHF, transistors.

Mr. C. W. Morris of Charleston, W. Va., says: "TELEVISION SERVICING is worth many times its cost. I have paid as much as \$200.00 for courses that haven't given me the clear understanding this book has."

Prentice-Hall, Inc., Dept. 5747-A,  
Englewood Cliffs, New Jersey

Send me TELEVISION SERVICING for 10 days FREE TRIAL. Within 10 days I will either return it and owe nothing—or keep it and send \$1.95 down (plus postage) and \$2 monthly for 2 months.

Name .....  
Address .....  
City ..... Zone ..... State .....


SAVE! Send \$5.95 with this coupon and we'll pay postage & packing.

## WRIST RADIO—\$3.95



No need to search around to find ALL the parts to build the Wrist Radio described in last issue of Radio-TV Experimenter. We'll supply \$4 grade metal transistor, micro-glass diode, plastic case, bakelite chassis plate, tuning coil & knob, both ceramic capacitors, battery clips, hardware and wire—everything for \$3.95 postpaid. Set uses only 15¢ 1 1/2 v. hearing aid battery, sold by hearing aid dealers in your town. Set works with regular magnetic earphones or we'll furnish a real miniature hearing aid phone for \$3.75. Do not confuse with cheap imported phones which rarely work.

## PEE-WEE RADIO \$3.95

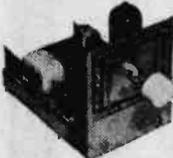

This set has pulled in stations 1500 miles away. It can be converted into a novel radio broadcaster, too, as described in last issue of Radio-TV Experimenter. All parts furnished so that radio can be changed from radio to broadcaster or vice versa.

You get components for both projects for just \$3.95. Set uses standard or miniature phone available at \$3.75. Hearing aid battery available from local hearing aid dealers at same price we would charge.

WE PAY POSTAGE ON ALL ORDERS. SEND CHECK OR MONEY-ORDER. DO NOT RISK CASH. SORRY, NO C.O.D. WITHOUT \$1 deposit. FOREIGN ORDERS SHIPPED 1st CLASS MAIL POST-PAYED ANYWHERE AT SAME PRICE, but C.O.D.'s can not be filled outside U.S.A.

### ELECTRO-MITE

REG. U. S. PAT. OFF.

SPRINGDALE 636-X CONN.


## Develop 380,000 Volts

### With This Van de Graaff Generator

Every electrical experimenter will want to build an operating model of the full-size electrostatic generator that aided in the development of the atomic bomb. This model will perform a variety of fascinating experiments and develop up to 380,000 volts. Complete bill of materials and step-by-step construction details make it easy to build the Generator. Two large illustrated plans, size 22x34 inches. Order Craft Print No. 197—Price \$1.50. Also, "Souped-Up" Tesla Coil. Craft Print No. 191—Price \$1.00. Both plans, \$2.00.
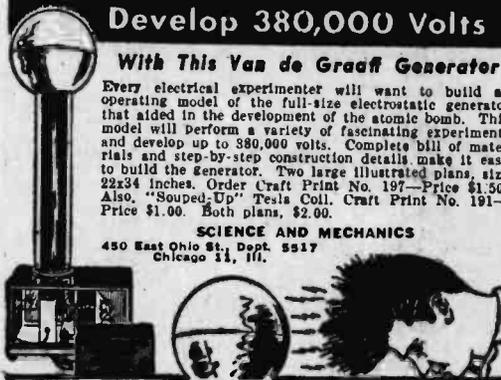
### SCIENCE AND MECHANICS

450 East Ohio St., Dept. 5517  
Chicago 11, Ill.



## Want a Trailer?

### BUILD IT YOURSELF

Ideal for week-ends, fishing or vacation trips. Compact, roomy, comfortable; sleeps two people. Designed for all modern conveniences—sink, water tank and pump, stove, kitchen table, cupboard, clothes closet, drawer chest, storage space, electric lights, ventilator, etc. Sturdy, simple construction. Overall body length, 12 ft. 6 in., weight 1,100 lbs. Our master plan gives bill of materials, explains every construction detail. Satisfaction guaranteed. Order Craft Print No. 50 now!

PLANS  
\$1.00

### SCIENCE AND MECHANICS MAGAZINE

450 E. Ohio St., Dept. 5518  
Chicago 11, Ill.



# Learn Code

prepare yourself for your big opportunity

THE *Candler* WAY IS THE *Champion* WAY!



THE SHORT CUT TO CODE SPEED

Picture yourself at your own transmitter . . . sending out radio code, messages that will be received around the globe. Yes, operators are waiting to communicate with you today, tonight or any time. The knowledge of the world . . . intimate friendships you will gain . . . may help you in your business, may be a stepping stone to success.

Wouldn't you like to be the invaluable link with the outside world in time of disaster? Or to serve in a national or local emergency? Be ready for service when the opportunity arises! Learn telegraphy now—the Candler way.

For 46 years the CANDLER SYSTEM has trained beginners for all telegraphing requirements, all operator licenses, highest ratings, and FCC specifications, both amateur and commercial. The record of famous amateurs and expert operators who learned the Candler way is proof of what the Candler System offers you. Send for details today!

## BEGINNERS CODE COURSE

Especially designed for the beginner. Teaches the basic principles of code operation scientifically.

Here's your chance to learn quickly and easily . . . to get maximum speed and proficiency in code . . . right in your own home. You can save time and money learning the fundamentals of code sending and receiving and the principles of fast, efficient operating with the world-famous CANDLER SYSTEM.

**CANDLER SYSTEM** Dept. 18, P. O. Box 928 Denver 1, Colorado

## ENGINEERING Home Study Courses

COURSES written by world authorities in all branches of engineering. Step-by-step instructions using methods proved successful by thousands of our graduates. One hour each day in your spare time will start you off to higher pay, security, prestige. Check the course you are interested in and we will send you a complete outline of the course with a booklet describing the Institute and our advanced methods of teaching. Send to: Canadian Institute of Science and Technology Ltd., 679 Century Bldg., 412, 5th St. N.W. Wash., D.C.

- Civil Eng.
- Surveying
- Architecture
- Forestry
- Mining
- Structural
- Mechanical Eng.
- Industrial Eng. & Management
- Refrigeration
- Heating
- Drafting
- Plastics
- Electrical Eng.
- Radio
- Electronics
- Television
- Aeronautical Eng.
- Aircraft Engineer
- Navigation
- General
- Education
- Chemical
- Mathematics
- Journalism
- Accounting



## FREE GIANT 1958 B-A ANNUAL CATALOG



- 172 KING-SIZED PAGES
- EVERYTHING IN RADIO TV AND ELECTRONICS
- 100'S OF NEW ITEMS LISTED HERE FOR 1st TIME
- 21 PAGES OF BARGAINS NOT IN ANY OTHER CATALOG

### BURSTEIN-APPLEBEE CO.

Dept. 5M 1012 McGee St., Kansas City 6, Mo.  
 Send Free 1958 B-A Catalog No. 581.

Name.....  
 Address.....  
 City.....State.....

SEND FOR IT TODAY

NAME.....  
 ADDRESS.....  
 CITY..... STATE.....

Course Interested In.....  
 Canadians: Send to Canadian Institute of Science & Technology Limited, 679 Garden Bldg., 263 Adelaide St. West, Toronto, Ontario.

Get into

# TELEVISION

## RADIO-ELECTRONICS



LEARN ALL 8 PHASES  
BY SHOP METHOD

1. Television . . . including Color TV
2. Radio . . . AM, FM
3. Industrial Electronics
4. Communications

OF THE INDUSTRY  
HOME TRAINING

5. Sound Recording & Hi-Fidelity
6. Automation
7. FCC License Preparation
8. Radar & Micro Waves

Let National Schools of Los Angeles, a Practical Resident Technical School for over 50 years, train you at home by Shop Method for unlimited opportunities in All phases of TV, Electronics, Radio.

You got 19 big kits  
of equipment!

### YOU GET EVERYTHING YOU NEED

Clear, profusely illustrated lessons, shop-tested manuals, modern circuit diagrams, practical job projects—all the valuable equipment shown above—many other materials and services—consultation privilege with our qualified staff, and Graduate Employment Service. **EVERYTHING YOU NEED** for outstanding success in Electronics.

**INDUSTRY NEEDS YOU. NATIONAL SCHOOLS WILL TRAIN YOU. SEND FOR FACTS TODAY NO OBLIGATION.**

**YOU LEARN BY SHOP METHOD . . .** you do servicing, circuit analysis, and do over 100 down-to-earth experiments. You build a Superhet Receiver and a modern TV Receiver, from the ground up, including a new, big screen picture tube. You also receive a professional, factory-made **MULTI-TESTER**. All of this standard equipment is yours to keep . . . at just one low tuition.

### GOOD JOBS . . . MORE MONEY SECURITY . . . ALL CAN BE YOURS

YOU are needed in the great modern Television-Electronics industry. Trained technicians are in growing demand, at excellent pay, in sales and service, manufacturing, broadcasting, telecasting, communications, research, and many other important branches of the field. National Schools Master Shop-Method Training, with newly added lessons and equipment prepares you in your spare time right in your own home for these fascinating opportunities. **OUR OUTSTANDING METHOD IS PROVED BY THE SUCCESS OF GRADUATES ALL OVER THE WORLD!**

### YOUR TRAINING IS ALL INCLUSIVE

We prepare you for a long list of job opportunities. Thousands of TV and Radio receivers are being sold every day—more than ever before. And, now, Color TV is here. Applications of Electronics in industry—**AUTOMATION**—are growing in tremendous strides. The whole field is alive—opening up new, important jobs rapidly. National Schools complete training program qualifies you in all phases of the industry.

### YOU EARN WHILE YOU LEARN

Many students pay for their entire training—and more—with spare time earning. We'll show you how you can, too! Early in your course you receive material that shows you how to earn extra money servicing TV and Radio receivers, appliances, etc., for friends and acquaintances.

### RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment—professionally installed—finest most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school . . . and part time job while you learn. Check box in coupon for full information.

Approved for  
GI Training



## NATIONAL SCHOOLS

LOS ANGELES 37, CALIF.

FREE!  
VALUABLE BOOK  
& SAMPLE LESSON  
—Just Send  
Coupon!



### NATIONAL SCHOOLS

TECHNICAL TRADE TRAINING SINCE 1905  
LOS ANGELES 37, CALIFORNIA

#### GET FAST SERVICE—MAIL NOW TO

NATIONAL SCHOOLS, DEPT. RKM-15  
4000 S. FIGUEROA ST.  
LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_


CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

Check if interested ONLY in Resident School training at Los Angeles.  
VETERANS: Give date of Discharge \_\_\_\_\_



## Signal Tracing Troubleshooter

By W. F. GEPHART

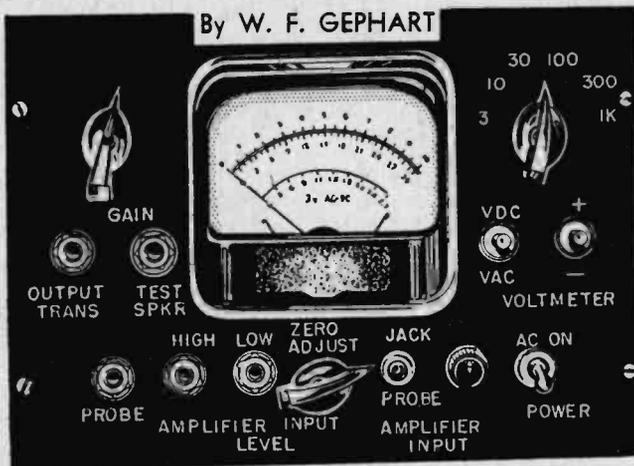

ONE of the handiest tools for servicing work and design testing is the signal tracer, which permits a check of the signal at all points from the antenna (or input) to the output of radios (or amplifiers). Used in combination with a voltmeter and test speaker, virtually all trouble-shooting can be done not only easily but in a minimum of time. The unit shown in Fig. 1 combines the three needs for this type of troubleshooting, allowing an audible check of the signal at any point in the circuit, a voltage measurement at any point, and a speaker test. It also functions as a utility amplifier, an extra vacuum-tube voltmeter, and a utility speaker.

The VTVM, a simple bridge circuit using a dual

Troubleshooter and probe unit (speaker is mounted in top of cabinet). Drawing (left, below) gives front panel designations of switches and jack inputs.

triode (V1 in Figs. 4 and 5), has a high input impedance (12 megohms) and can be used in grid circuits without loading. A meter rectifier permits measurements of audio frequency or ac voltages, making AF voltage gain measurements possible during tracing, and a polarity switch permits measurement of both positive and negative dc voltages without reversing test leads.

The signal tracing section is a high-gain amplifier fed through a crystal detector, permitting the signal to be checked in either RF, IF or AF sections. The detector is mounted in the probe unit, minimizing loading in RF stages. The probe unit also contains a switch which transfers the probe tip from the amplifier to the

voltmeter to permit voltage measurements at signal check points without changing leads, plugs, or reaching to the unit itself to throw a switch.


For utility service, inputs may be fed into the amplifier at either of two gain levels, and the output transformer secondary and built-in speaker voice coil are each available on jacks on the front panel, for testing other speakers, and for using the built-in speaker as a test speaker.

Both the VTVM and signal tracing amplifier are powered by a transformer-type power supply which isolates the unit from the power lines.


Figure 2 shows the probe unit details. The probe housing is a small chili powder can with a screw top. The probe tip is mounted on a small



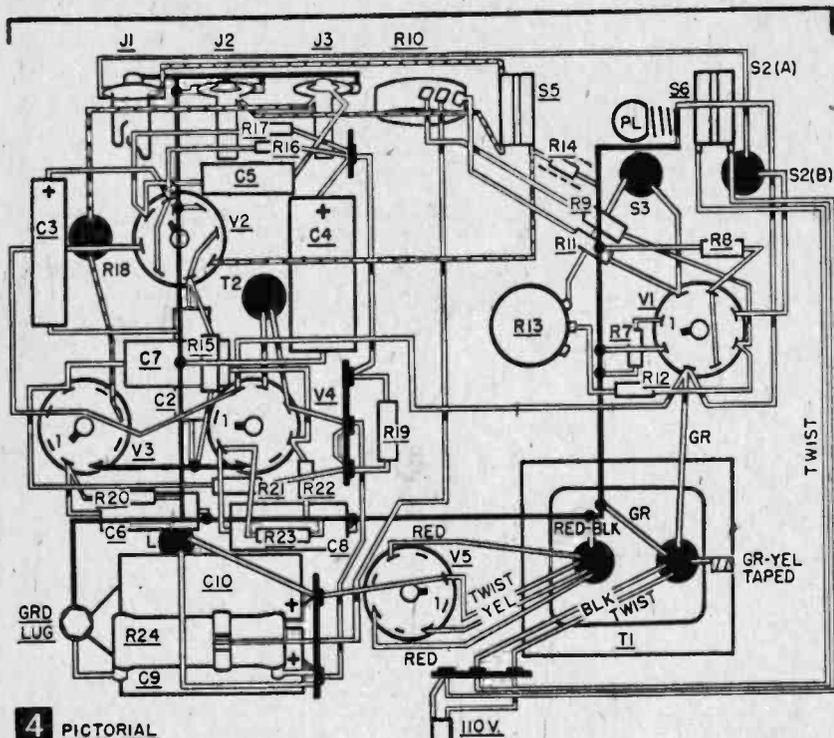NOMENCLATURE NOT UNDERLINED INDICATES LEAD TERMINATION  
 ===== INDICATES SHIELDED LEAD  
 HEAVY BLACK LINE INDICATES COMMON GROUND BUSS



4 PICTORIAL

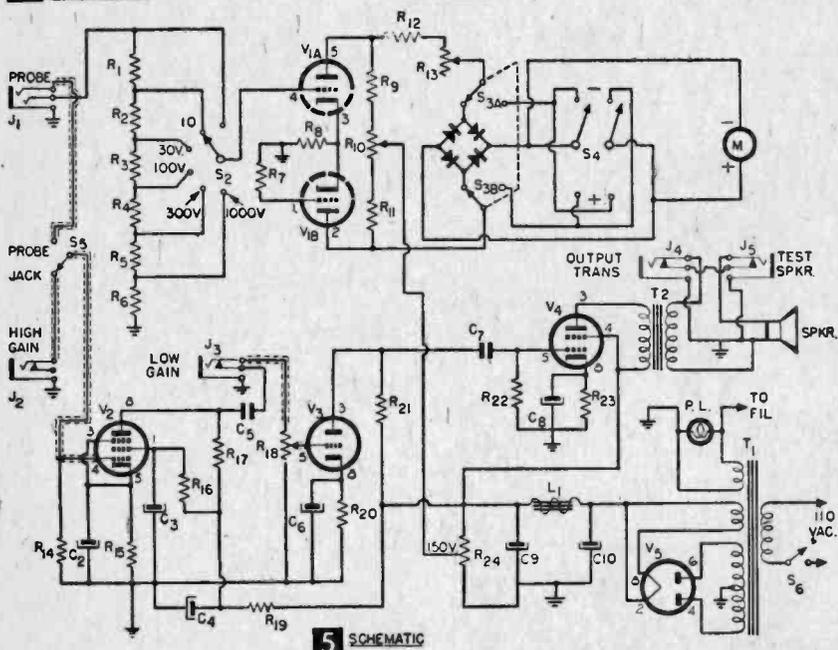

5 SCHEMATIC

cord through the hole in the top of the can, screwing the top in place. The micro-switch should be wired as shown in Fig. 2 so that pressing the button transfers the probe tip to the voltmeter.


Figure 3 gives the chassis layout for the entire unit, Fig. 5 the schematic wiring diagram, and Figs. 4, 6 and 7 the pictorial wiring diagrams. To minimize hum in the amplifier, the power supply is placed as far from the amplifier input as possible, and certain grid leads should be shielded as shown. The voltmeter multiplying resistors (R1 through R6) should be of 1% tolerance, but the specifications on the other parts are not too critical.

The chassis is secured to the front panel by the bottom row of jacks and switches, fastened up from the bottom of the panel enough to clear the lip of the cabinet, which then requires a small "leg" at the back of the chassis for support (see Figs. 6 and 7). The speaker is mounted in the top of the cabinet and is connected to the chassis by a four-conductor cord and plug arrangement, permitting easy removal of



positioning and tightening the micro-switch, and then fasten the terminal strip in place with a small bolt. Check to be sure that no bare sections of wire are shorting out, and thread the

the chassis when removal is necessary.

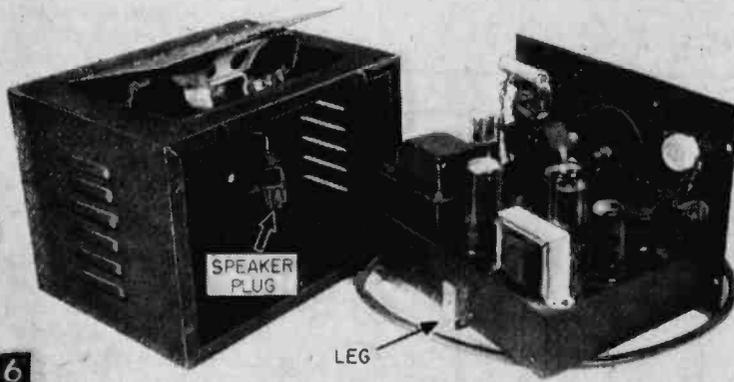To calibrate the voltmeter, turn the unit on, allow several minutes warmup time, and set the pointer of the meter to Zero, using R10. Put the



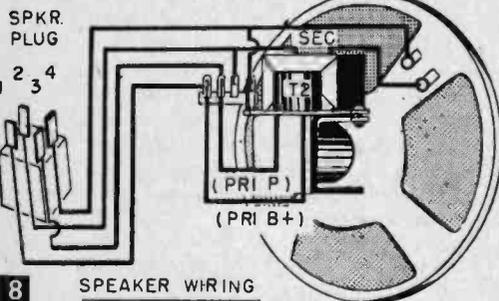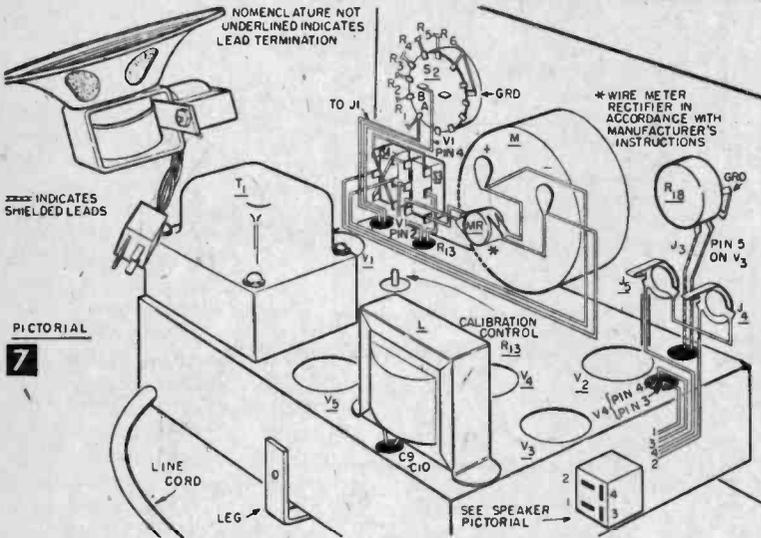Troubleshooting unit out of cabinet showing "leg" on chassis and speaker connecting cord and plug.



reading (10v., as set by the Range Switch) equal to the test voltage. Thus, R13 should be adjusted to have the meter read .6 (on a 0-1 meter scale), 6.0 (on a 0-10 scale), or 60 (on a 0-100 scale).

One calibration will do for all dc and ac scales except the 0-3 v. ac scale. Due to the loading of the meter rectifier, a special scale, established by a series of checks with varying ac voltages between 0 and 3 v., will have to be made for this range.

To use the unit as a Signal Tracer, set S5 on "Probe," plug the probe lead into the proper jack, and clip the ground lead of the probe to the ground of the unit being checked. Touch the point of the probe to the various check points, and adjust the Gain control (R18) for the desired signal level. To read voltage at any point, press the button on the probe, making sure that the Range Switch and the Polarity Switch (S4) are set properly.


To use the unit as a Test Amplifier, set S5 to "Jack," and feed the signal into the amplifier through the High Gain jack (J2) or Low Gain jack (J3), depending on the gain you require for your test.

To test a questionable speaker, feed a signal into the amplifier as you would to test amplification, and plug the questionable speaker into the "Output Transformer" jack (J4) on the front panel of the unit.

To use the built-in speaker as a Test Speaker, plug the desired output signal into the "Test Speaker" jack (J5). In this use (and in the questionable speaker test using the "Output Transformer" jack, J4), the output of the amplifier and the built-in speaker voice coil both have an impedance of 3.2 ohms.

To use the voltmeter separately, the probe can be used (with the button pressed), or a separate set of test leads can be made, terminating in a three-conductor plug (using Ring and Sleeve only), to be plugged into the "Probe" jack on the front panel.

probe cord in the "Probe" jack, set the Range Switch (S2) to "10" v., and connect 6 v. dc across the probe terminals. (It is most important that this test voltage be known to be accurate; an automobile battery source is suggested). With the voltage across the probe terminals, adjust the calibration control (R13) for the proper reading. Since the meter will probably be calibrated 0-10 or 0-100, a new scale should be made for the meter face and the "proper reading" mentioned above will be the percentage of the full scale

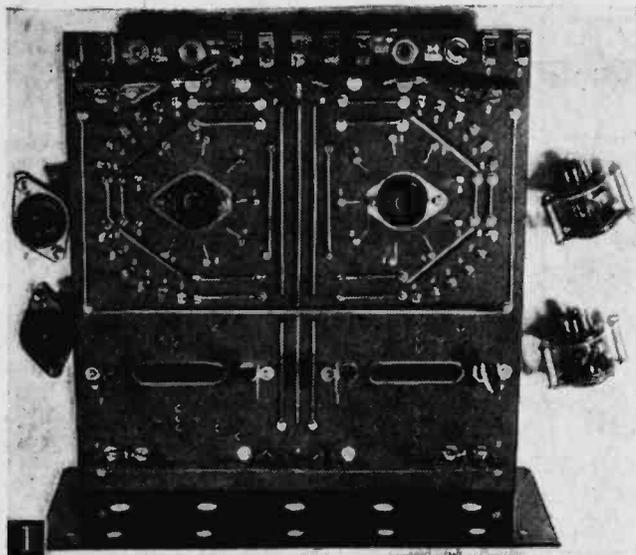

Top view of designer's chassis ready for use. Tube socket adapters are on either side of chassis.

## Designer's Experimental Chassis

**I**n experimental circuit design work, a chassis on which parts can be readily changed and substituted for one another, where any type tube can be used, and where a minimum of wiring is required, is a real boon to designers, saving them both time and temper. Without such a chassis, experimental results are often disappointing due to haywire test rigs. This experimenter's chassis will give "permanent construction" results while still retaining the advantages and simplicity of haywire rigs.

Test circuits for up to two tubes are provided on this chassis, plus a number of features that reduce wiring problems. By the use of socket adapters, any tube (up to nine-pin base) can be used, and there is space on the chassis for small transformers, relays, and other circuit components. All connections (except input, power and output) are soldered, yet components can be changed without disturbing other components connected to the same terminals.

Input, power and output connections are at the back of the chassis; two filament inputs are provided, but if tubes with the same voltage are being used, a switch parallels the filament leads to the tubes so that only one power lead need be connected. Similarly, two plate voltage inputs

are provided; these can be tapped on exposed bus wires at any point down the center of the chassis, but, if only a single plate voltage is used, a switch parallels these leads. The input and output connections are both clip and jack type, and each also appears on two two-terminal tie points (input shown as "W" and output as "Y" on Fig. 3). This makes input and output available both near the tubes and also near the transformer mounting space. Wiring for these units is shown in Figure 4.


A ground (B-minus) clip at the back of the chassis connects to an exposed bus wire that runs down the center of the chassis, across the front, and part way down each side, permitting connection to ground virtually anywhere on the chassis. Each tube socket has nine exposed sections of bus wire—one for each pin—for connections. In addition, six of the tube pins also have lug connections around the opposite side of the other tube, parallel-connected with the basic tube socket bus wires. This arrangement provides convenient connection from pins of one tube to those of the other without running a lead across the chassis. (The parallel connections are made permanently under the chassis.) Each tube pin is numbered with decal letters, both at the tube location and at the paralleling lugs on the other side of the chassis. Also located around each tube socket are seven pieces of isolated bus wire to serve as tie-points or multiplying connections.

At the front of the chassis are two open spaces with a series of mounting holes for various-sized transformers and other, similar electronic parts. On the outer side of these spaces are the two-terminal tie points that parallel the input and output, and on the inner side are two other two-terminal tie points for miscellaneous transformer connections.

A steel panel with five  $\frac{3}{8}$ -in. holes and five  $\frac{1}{2}$ -in. holes for mounting potentiometers, switches, etc., serves as the front of the chassis. Just behind this panel are two five-terminal tie points (one on each side, "V" and "Z" in Fig. 3), and one six-terminal tie point ("X") in the center. These are for connections to panel-mounted components and are parallel-connected to similar tie points at the back of the chassis near the tube sockets. The bus wires are held in place by screws and are raised about  $\frac{1}{4}$ -in. above the surface to permit leads from capacitors, resistors, and other circuit components to be slipped under them before "tacking" with solder.

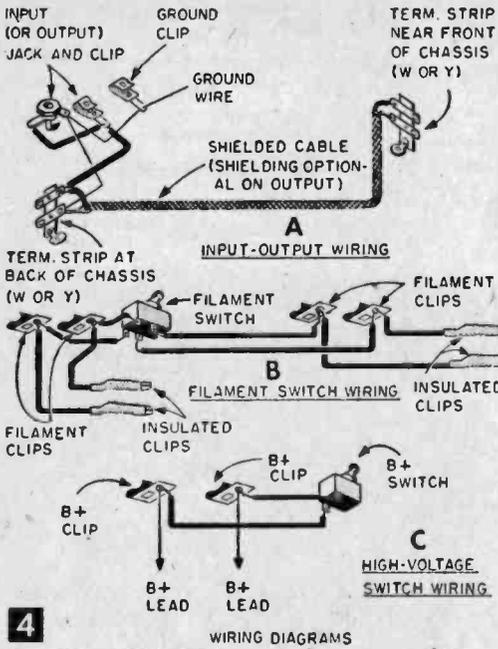Any tube can be used on the chassis by building tube socket adapters as shown in Figure 6.





MATERIALS LIST—DESIGNER'S CHASSIS

No. Req'd	Description
9	medium Fahnestock clips
1	SPST toggle switch
1	DPST toggle switch
2	open-circuit phone jacks
4	five-terminal tie strips
6	two-terminal tie strips
2	six-terminal tie strips
1/2 gross	3/8" #4 rh woodscrews
24	small soldering lugs
24	3/4" 4-36 machine screws and nuts
2	nine contact octal socket with adapter plate (Amphenol 78RS9)
1	1/8 x 11 x 11" tempered hardboard
1	1/4 x 11 x 11" plywood
2	1/2 x 1 1/4 x 10" pine (side pieces)
1	1/2 x 1 1/4 x 11" pine (front panel backing)
1	steel plate, approx. 5" x 12"
4	insulated alligator clips
	#18 bare tinned copper wire
	#16 bare tinned copper wire
	test lead wire
	For each tube socket adapter assembly:
1	nine-prong octal plug with adapter plate (Amphenol 86CP9)
2	1 1/4" x 6-32 machine screws and nuts
2	1 1/4" metal spacers
4	#6 flat washers
2	lock washers
1	tube socket*

chassis, rather than trying to make a series of bends.


Run the B-plus wire next, using the same type of wire, again making connections under the chassis. Next place the miscellaneous bus wires, each with a screw at both ends, using bare #18 tinned copper wire for this purpose. Where space is available, a washer at each screw, under the wire, helps hold the wire slightly above the chassis.

The tube socket bus wires are bare #18, soldered to the socket, run up through the hole by the socket, and then to a screw. The 1/2-in. length between the hole and the screw provides room for connections.

When all surface wiring is done, place the multiplying tube pin soldering lugs, using 4-36 machine screws and nuts. Then screw the various tie points to the top, and complete under-chassis wiring.

Wire the tube pin multiplying screws first, by paralleling the appropriate numbered lugs on each side to each other, and then multiply-

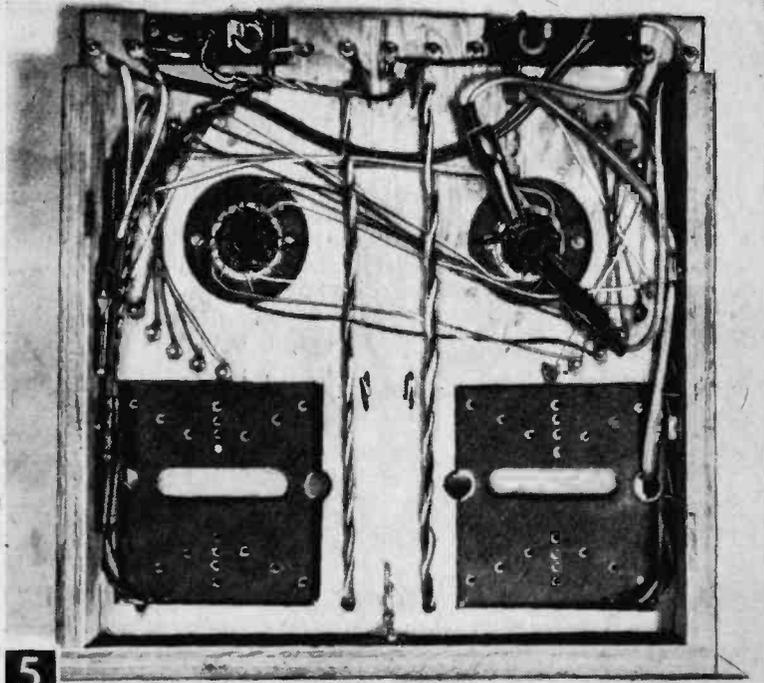\* For four-pin to octal, standard sizes, use Amphenol Type RS. For seven-pin miniature, use Amphenol 78A7P with adapter plate, and for nine-pin miniature, use Amphenol 78A9P and adapter plate.





Bottom view of chassis showing permanent, underchassis tie-point connections. Note filament clips in place on right-hand tube socket.

ing one set of such connections to the properly-numbered pin of the tube socket on the other side of the chassis.

The final wiring to be done under the chassis is the input, output, filament switch and B-plus switch. The lead length of the under-chassis filament leads (made of test lead wire) should be long enough to permit the insulated clips to be clipped to any tube socket pin. Two small nails on the inside of each plywood side piece hold the leads in place when they are not being used. In Fig. 5, one set of leads is connected to tube pins, the others are clipped to the nails.

The steel panel is screwed to the front support piece. A bolt goes through the support and is connected to the ground lead, enabling the steel panel to act as a shield from body capacity.

In using the chassis for circuit design work, the proper tube adapters are plugged in and the filament leads connected to the proper pins under the chassis. Then transformers and other "mountable" components are bolted to the chassis, and panel items are fastened to the panel. Wiring is done by slipping component leads under a bus wire, in a lug, or in a terminal tie point, and tacking them in place with solder. In a few cases, short leads of jumper wire may be required, but the multiplying characteristics of the various tie points and tube socket lugs usually makes this unnecessary.—W. F. GEPHART.

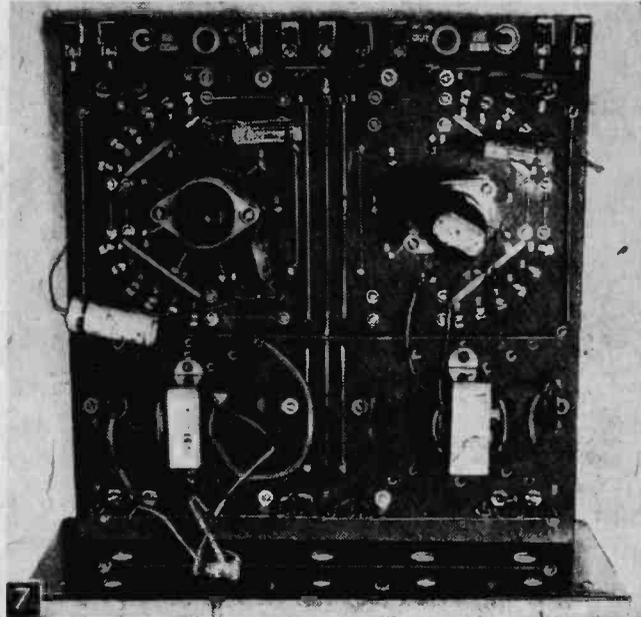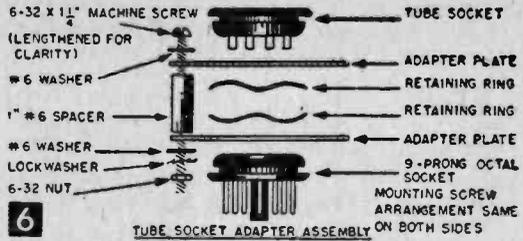

Designer's chassis in use, two-tube amplifier under test.

### Insulated-Wire Tester


• Convert your Christmas tree lamp tester for insulated-wire testing. Solder an insulated wire lead directly to toothed electrode so temporary connections can be made to insulated wires in radio and electrical test work. Sharp teeth on the tester cut through the insulation and contact



the wire without damaging the insulation. Connect 2 of these testers to an ac voltmeter for electrical work, or, to a volt-ohm-milliammeter for radio service work and experimental work. Testers have fiber handles which make them safe for use on high voltages.—ARTHUR TRAUFFER.
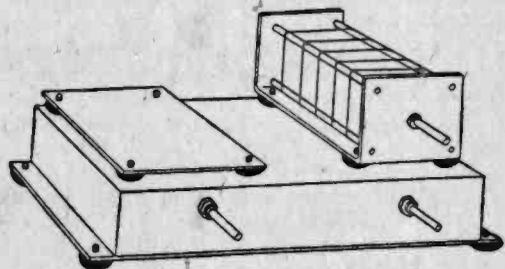
### Vacuum Cups as Cushions

• Radio amateurs and experimenters find that vacuum cups with a machine-screw molded in and a thumb-nut attached, make good rubber cushions and shock absorbers on a receiver or transmitter chassis. Sketch shows a gang-condenser held and cushioned on chassis, a sub-as-




sembly panel cushioned and held to chassis, and chassis itself cushioned from operating table. In latter case, cups also keep chassis from sliding and scratching furniture. Cups are sold in most supply stores.—ARTHUR TRAUFFER.



# Spit-Powered Oscillator

A Scotsman's Delight

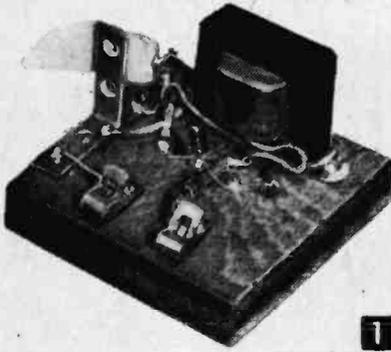

1



By C. F. ROCKEY

**A** YE, LADDIE, if you've got a bit of the Scots in you—or even if you haven't—you'll ken this thrifty little oscillator. Its source of power is tap water—or spit—and it's just the thing for code practice, for circuit continuity testing, for capacitor checking, and for use as a signal source when adjusting hi-fi or public address amplifiers.

To build it, first saw, sand smooth and shellac a 3/4-in. piece of soft pine or plywood to a 4 x 4 in. block. This is your oscillator's chassis. Next, physically modify the driver transformer by bending the bottom fastening lugs away from the core and removing the mounting frame, finding the dividing point between the "E" and the "I" sections of the core (see Fig. 3) and—carefully—prying up and removing the "I" section. Set the "I" section aside, re-insert the modified core in the transformer's frame and bend the fastening lugs in place.

We used a Thordarson 14-D-93 interstage audio coupling transformer (4:1) that we had on hand, but this type has been discontinued by the manufacturer. Its closest present Thordarson equivalent is the 20-A-16 interstage transformer. This—or any similar transformer made by any other manufacturer—will work just as well in the oscillator's ultra-simple circuit.


When transformer is modified, mount it and all other circuit components except the angle brackets on the wood-block chassis (see Fig. 4), with 1/2-in. #6 r.h. wood screws. Before mounting the two angle brackets, clean their facing surfaces carefully with sandpaper or steel wool. Mount them with faces about 1/8 in. apart.


Make all connections to the transistor connecting lugs before mounting the transistor to avoid

A quick dip of the blotting paper, place it between the brackets, and you've set the set to buzzing, ready to key off for code practice.


any possibility of damaging the transistor with soldering heat. When all wiring is complete (see Fig. 2) and checked, put the transistor into the circuit by clamping its leads under the appropriate soldering lugs and screwing them tight. (The transistor lead adjacent to the red dot is the Collector, the center lead is the Base, the remaining lead is the Emitter.)

**Spit Power.** Strictly speaking, the source of power for this oscillator is not spit or water. Water is simply the electrolyte of a simple voltage generating cell whose plates are the dissimilar metal faces of the iron and brass brackets. Immerse a piece of blotting paper (about 1/2 x 1 1/2 in.) in tap water, or moisten the paper with saliva, insert it between the bracket faces and you will have a source of power for your oscillator. What you're doing, is duplicating one of the first steps taken by Alessandro Volta (1755-1837) in developing the world's first battery (or *pila*, as Volta called it). Volta found that if two dissimilar metal plates (he used copper and zinc) were separated by moist paper, a current would

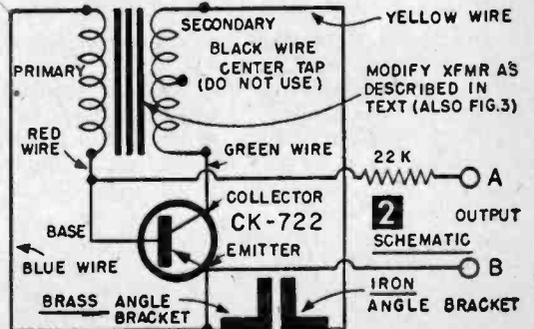


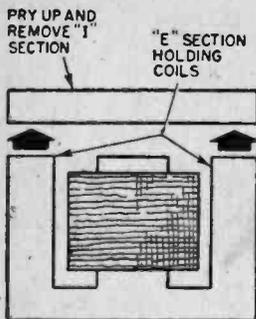

**3** MODIFICATION OF TRANSFORMER

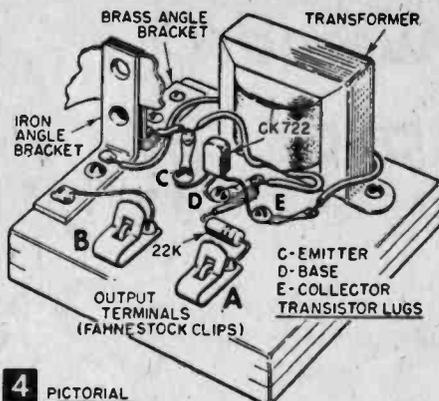

**4** PICTORIAL

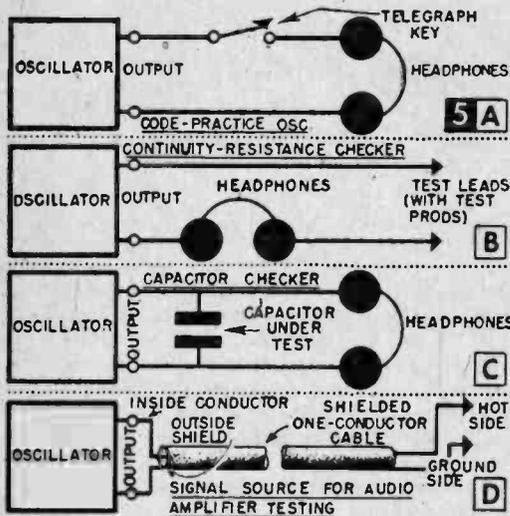

used.) Also, if you have used a transformer other than those specified in the Materials List, see if reversing its primary connections helps the tone.

With the unit operating, it can be used as a code-practice oscillator (see Fig. 5A); as a continuity-resistance checker to locate open circuits (Fig. 5B)—in circuits up to 10-megohms resistance if you use sensitive phones; as a capacitor checker (Fig. 5C); and as a signal source for audio amplifier testing (Fig. 5D). If too much hum is present for best audio amplifier testing, put the oscillator in a grounded coffee can and bring the shielded cable out through a hole in the can's top cover.

In capacitor testing, a good paper or mica capacitor in the capacity range of .001 mfd to .1 mfd will slightly weaken the signal and noticeably change its frequency. An open capacitor will have no effect on the signal, a shorted capacitor will kill it. (It is not recommended that you test electrolytic capacitors with the oscillator.)

#### MATERIALS LIST—SCOTSMAN'S DELIGHT

No. Req'd	Description
1 pc	3/4x4x4" pine or plywood
9	#6x1/2" r.h. wood screws
1	brass angle bracket, 1 1/2" arms
1	iron angle bracket, 1 1/2" arms
2	Fahnestock clips
1	CK722 Raytheon transistor
1	Thordarson 20-A-16 transformer (or Stancor A-53 or Triad A-31X)
1	22,000 ohm, 1/2 watt resistor
1 pr	2000-4000 ohm headphones (Trimm "Featherweight" standard or "Professional"—Allied cat. no's. 59J000, 59J020, or 59J021)
1 pc	blotting paper

flow between them when their outer surfaces were connected together.

Ordinary tap water usually contains enough impurities to act as an electrolyte; saliva, too. But if you don't get oscillation with either used as an electrolyte, do as Volta did, use a dilute salt solution, 1/2 teaspoonful of table salt in a small glass of water.

To test the unit for oscillation, connect a high-impedance (2000 to 4000 ohms) pair of earphones across the output terminals and listen for a clear, smooth tone of about 500-1500 c.p.s. If you

don't hear such a tone, check the wiring and transistor connections for correctness and if these are as they should be insert a 1 1/2v. dry cell temporarily across the brackets (plus side of cell to the brass bracket). This will give you a check on the transistor's condition. If it's good, oscillation will certainly occur. If not, substitute a new transistor in the circuit. (CK722's have proved unusually reliable in this simple circuit, but any other good PNP transistor may also be


#### Heavy Current Relay



• This little relay will handle as much as two amps. without trouble. Remove stationary contact of an electric bell or buzzer and turn it around. When current flows through coil, armature is pulled in and it makes contact with stationary member.—R.F.Y.
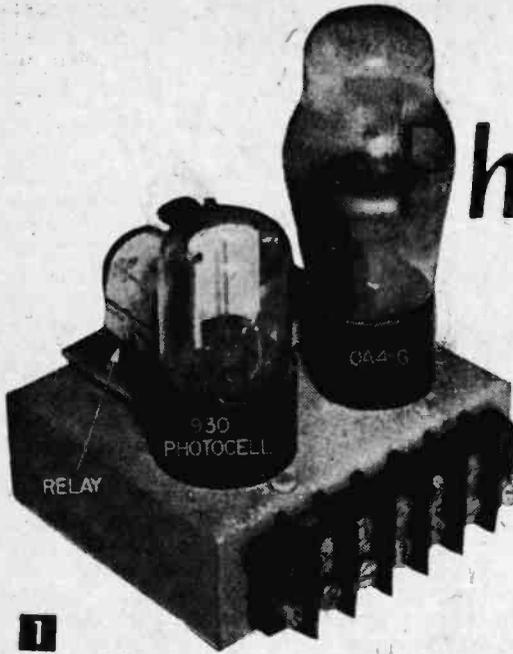
#### Better Soldering

• When using non-corrosive soldering paste flux for radio work, first warm the joint slightly with the soldering iron, then apply the paste with a piece of wire. The small amount of flux which melts on the joint is entirely adequate. Excessive flux spreads to adjacent insulation, causing leakage.



# Photo-Electric Controls

Depending upon the circuit employed, motors, lights, alarms, etc. can be photo-electric controlled by as little as a lead pencil intercepting the beam of light.

**W**HETHER assembled merely for entertainment or put to serious use, the photo-electric control, or "Electric Eye," has an element of mystery about it for spectators. Yet the principles by which these controls operate are the very same principles applicable to simple triode tubes.

A triode has three elements: cathode, grid and plate. Electrons flow through the triode—as they flow in all tubes—from cathode to plate, since the cathode is at a negative potential with respect to the plate. The grid acts as a valve, situated between cathode and plate, controlling this electron flow. (In England, radio tubes are called valves.)


When the grid is connected to a voltage with the same sign (polarity) as the cathode, electron flow from cathode to plate is impeded since like charges repel and both the cathode and the grid (which is closer, physically, to the cathode than the plate) have like charges. The reverse holds true, of course, when the grid is connected to a potential with the sign opposite to that of the cathode; electron flow through the tube is increased. Thus, varying the sign (or the size) of the potential (charge) on the grid of a tube varies the electron flow (current) through it from cathode to plate.


In photo-electric control circuits, a photo-electric cell is used to vary the charge on the grid of a tube and a relay is connected into the plate circuit. When electron flow through the tube becomes sufficient to energize the relay's magnetic coil, it closes its switch contacts and thereby performs the desired work—operating motors, lights, etc. The photocell controls the grid; the grid, the plate; the plate, the relay.

The 930 photocell employed in the unit shown in Fig. 1 is its prime mover, its master control. When light strikes the 930, the relay energizes because the potential on the grid of the OA4-G has been changed (see Fig. 2) to permit greater electron flow to the OA4-G's plate and, thus, through the relay's coil. The same unit can be wired to de-energize an energized relay (see Fig. 4), still using the photocell as prime mover. In the de-energizing circuit, the photocell changes the potential on the grid of the OA4-G so that it will act as a shut-off valve, interrupting the flow of current from cathode to plate and thus through the coil of the relay.

The controls shown in Figs. 2 and 4 employ the most economical and least complicated of possible circuits. The triode OA4-G cold cathode used is a gas-filled, glow discharge tube. When it is conducting, it glows a deep purple. The unit can be used as shown in Fig. 1 for experimental or educational purposes, or it can be enclosed in a metal or wood cabinet, with a small opening opposite the photocell, to perform more serious tasks.

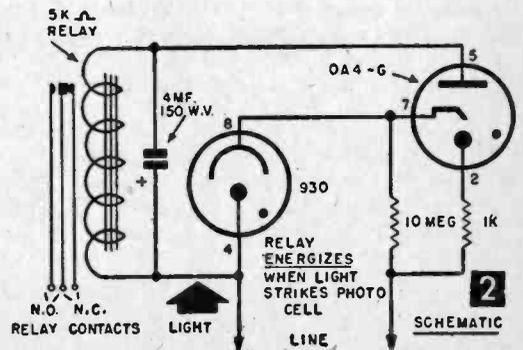Construct the 1¼x3x3½ in. chassis from a piece of sheet steel or aluminum measuring 5½x6 in. Scribe the piece 1¼ in. on all sides, cut out the



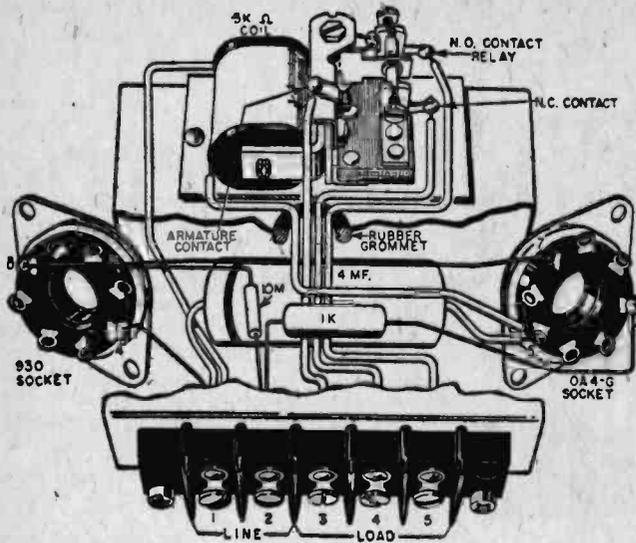

**3** PICTORIAL RELAY ENERGIZES WHEN LIGHT STRIKES PHOTO CELL

corners, and bend the panel to shape in a vise. Cut two 1 in. or  $1\frac{1}{8}$  in. holes on the top of the chassis for mounting the two octal tube sockets, and drill a  $\frac{1}{2}$  in. hole between the socket openings for a  $\frac{1}{2}$ -in. rubber grommet. There is ample room on the chassis top, so location is not critical. The relay coil and contact leads are passed through the rubber grommet. Finally, two  $\frac{1}{8}$  in. holes—spaced as needed—are drilled on the top of the chassis for mounting a 5000 ohm, S.P.D.T. relay. Location of these holes will depend upon the make of relay employed.

To make the control completely flexible, power line input and relay switch contacts terminate on a Cinch-Jones barrier strip mounted on the front apron of the chassis. Provide the apron with a  $\frac{1}{4}$  x 3 in. slot directly behind the upper row of terminal screws, remove these screws and solder the leads into the threaded bushings. Your electronic parts dealer may be able to supply a terminal strip with soldering lugs, but we prefer the arrangement shown in Fig. 1.

Depending upon whether you want to energize a relay, or de-energize it, wire as shown in Figs. 2 and 3 or 4 and 5. While many relays are small enough for such under-chassis mounting, top-chassis mounting is advised. This allows the experimenter to adjust the relay's contacts and armature tension, and also to see it in action. Note that only pins 4 and 8 of the 930 photocell and pins 2, 5 and 7 of the OA4-G are used. Other pins on their tube bases are dummies. Therefore, any blank lugs on their tube sockets may be used as solder tie-points for securing component leads. The electrolytic capacitor, for instance, may be secured to blank socket lugs to insure rigidity.

Make soldered connections to the photocell socket as clean as possible. Leakage across pins

4 and 8 can cause either circuit to operate erratically. In fact, touching these pins with the fingers will cause the circuit to operate. A dirty socket should be cleaned with denatured alcohol after soldered connections have been made.

Since each control uses identical components, no harm will be done if you later wish to rewire your original circuit. In fact, either circuit can do identical jobs because the relay is a S.P.D.T. type. However, the right circuit for a particular job is the circuit that keeps the relay de-energized except when the photocell is to be influenced by the presence or absence of light as called for by the job.


Figures 2 and 3 show the 930 photocell wired to produce a positive potential on the OA4-G's "grid" (starter anode) when the 930 is made conductive by, say, a fire, daybreak, or a beam of artificial light. This hook-up can be used to turn on yard lights, operate motor driven garage doors, etc. At all other times, the control rides on the power line and draws almost zero current. There is no heat or wear on the components, and years of troublefree service are assured.

Figures 4 and 5 show the 930 photocell wired to produce a negative potential on the OA4-G's starter. As long as a beam of light plays on the photocell's light sensitive cathode, the starter grid of the OA4-G has more negative voltage on it because of the photocell, than positive bias (fixed d-c potential) arriving via the 10 megohm resistor. The OA4-G tube, therefore, does not conduct. Breaking the beam focused on the 930, however, stops the flow of electrons through it, making the positive voltage through the 10 megohm resistor the master. The OA4-G instantly fires (conducts), the relay pulls in and, say, the burglar alarm sounds.

Only the experimenter who builds and experiments with these circuits will be able to appreciate their possibilities. The operation of either arrangement is virtually foolproof except for minor relay adjustments. The original control employed a Sigma Type 4-F relay with an 8K (8000) ohm coil. Sigma relays are slightly more expensive than other makes because they provide

#### MATERIALS LIST—PHOTO-ELECTRIC CONTROLS

No.	Description
1 pc	$5\frac{1}{2}$ x 6" light steel or aluminum
2	molded or wafer octal tube sockets
1	930 photocell
1	OA4-G cold cathode triode
1	Cinch-Jones barrier terminal strip #5-141
1	5K (5000) ohm relay (Potter-Brumfield LS-5 or LM-5, or equivalent)
1	1K (1000) ohm, 1 watt resistor
1	10M (10 megohm) $\frac{1}{2}$ watt resistor

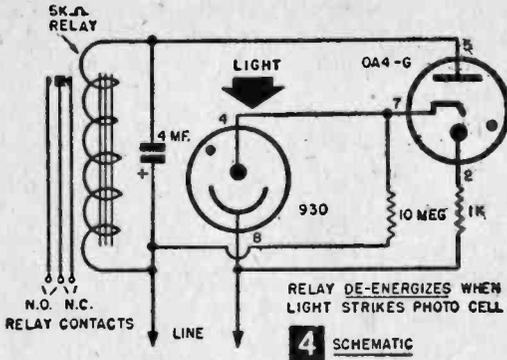


the circuits, though it may be necessary to make minor spacing adjustments of contacts and to reduce the armature tension of the fixed coil spring, for optimum relay sensitivity.

Potter & Brumfield relays are provided with silver contacts which will handle loads up to 5 amps. at 110 v. (550 watts). The Sigma relay contacts are rated at 2 amps. (220 watts). Where greater loads are involved, an auxiliary magnetic contactor or mercury plunger type relay must be used, and the photo-control relay contacts operate the coil of this power relay. A heavy motor or load is handled by the power relay's silver contacts or mercury solenoid displacement. Power relays are made in a variety of sizes and types, including "lock-in" relays which, when momentarily energized, lock and continue to sound alarms, etc. until manually released.

A typical use of the circuit shown in Figs. 2 and 3 might be to run a motor. A 110-125 v. source is connected to terminals #1 and #2 of the terminal strip and one wire of the motor is also connected to terminal #1. A jumper lead is connected across terminals #2 and #3 and the remaining motor wire is connected to terminal #5.

Light (a flashlight, for instance) activating the photocell causes the relay armature (terminal #3) to close the relay's normally open contact (terminal #5) and the motor runs. To reverse this action, move the motor lead on terminal #5 to terminal #4. Now the motor will continue to run until light strikes photocell. The combination of circuits and double throw relay contacts makes possible a great variety of electrical functions—starting one device and stopping another by employing both the normally open (NO) and normally closed (NC) relay contacts.—T. A. B.

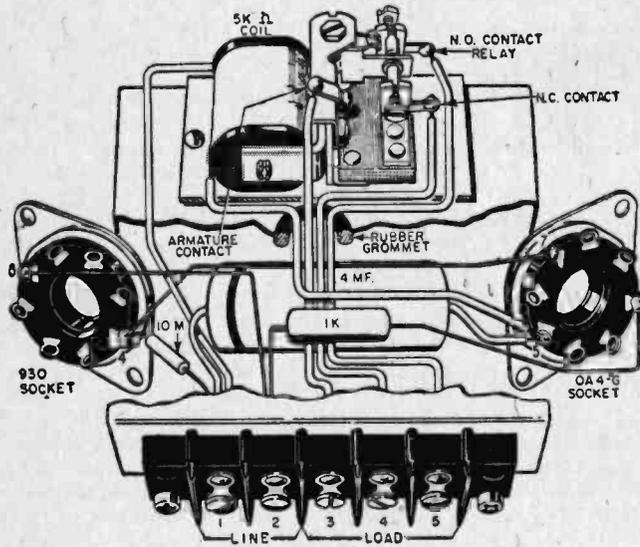


**5** PICTORIAL RELAY DE-ENERGIZES WHEN LIGHT STRIKES PHOTO CELL

precision adjustment of contacts and of armature tension. However, the inexpensive 5K relays made by Potter & Brumfield work quite well in

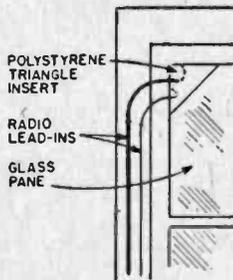
**Plastic Lead-in Window Insert**

• Most radio amateurs know that clear polystyrene window panes are available to replace glass panes so lead-in can be brought in without drilling glass, but fitting in a triangular corner saves the cost of a whole pane.


Remove the glass pane and cut off the corner, not more than 4 in. along either side. For about 20c you can get enough 3/32 in. polystyrene plastic sheet to fill in the corner. Drill through the plastic corner for lead-ins.—ARTHUR TRAUFFER.



**Handy Reel For Solder**

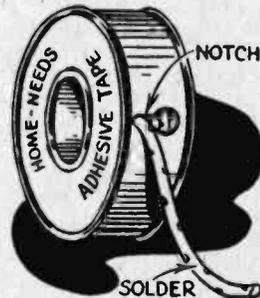

• Small household packages of solder that are not regularly supplied on a reel can be transferred onto a handy dispenser and holder by coiling them on a used adhesive tape reel as shown in the drawing. This does away with much of the direct contact with the solder and any escaped flux. Cut a hole at the side of the can for uncoiling the solder. A wedge-shaped notch at the side of the hole will lock the solder from receding back into the can.

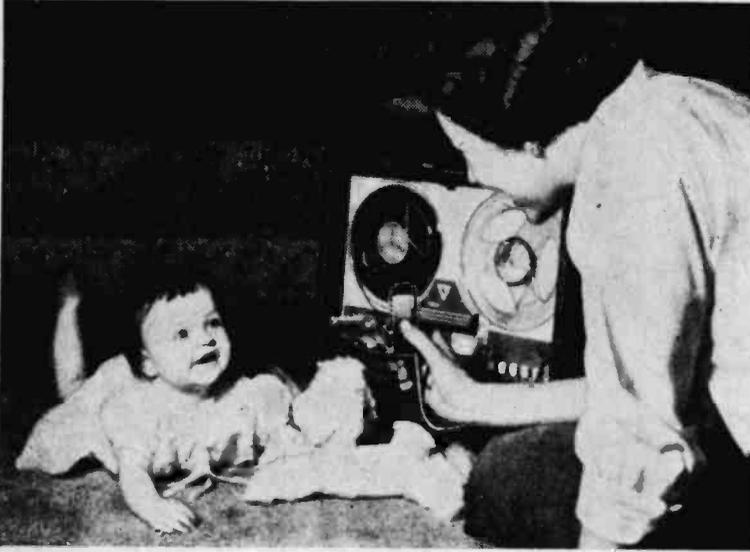

That first "muh-muh" will be just as valuable to you in years to come as the "mi-mi-mi" of a world-famous mezzo-soprano—probably more valuable. But you can capture them both for posterity with a tape recorder. Recorder shown here is a Bell and Howell TDC Stereotone.

your investigation is with the mechanical features of the various makes and models; then go on to check the electronic features.

### MECHANICAL FEATURES

**Motors.** The number of motors is often directly responsible for the quality of the recording. A constant tape speed is required for high fidelity. When this speed varies—even slightly—flutter and wow show up. Flutter is an unsteadiness of sound, volume, and pitch, caused by rapid variations in the tape

speed, usually noticeable in the higher frequency ranges. Wow is a wavering of sound similar to that produced by a disc record rotating at an uneven speed.

Flutter and wow are reduced by having separate motors (three are best) for (1) the capstan (it pulls tape at a constant linear speed), (2) the supply (feeding) reel, and (3) the take-up reel. Separate motors also minimize tape spill (tape that continues to unwind after the capstan has stopped) and tape breakage due to jerkiness.

**Fast Forward and Fast Rewind.** Sometimes you will need to get from one part of your tape to another. That's where the fast forward and fast rewind controls come in. It's a good idea to pick a machine with a forward and rewind ratio of 10 to 1 or greater.

**The Selection Locator** control quickly locates programs on your tape. (Also called index counters and program indicators). While this control is not essential on home machines, some recordists find it convenient.

## How to Get the *Right* Tape Recorder

By MILT GRASSELL and DON HUNTER

**F**IRST words of an infant-size Junior Miss, Elvis Presley, trial summations, hen-house tunes—even TV pictures—can be captured with a tape recorder, the *right* tape recorder. To get that right recorder you have to know, before stepping up to the counter: 1) what type of material you're going to want to tape; and 2) what equipment is equal to the task.

Tape recording has become one of the hot divisions in the home appliance field. One reason is that prices are down. True, some custom-made sets cost more than \$20,000; and professional sets range from about \$300 to \$3600 in price. But for \$75 to \$300 or so you can get excellent home units. (And, after you've paid for the recorder, additional costs for tapes—tapes that can be erased and re-recorded more than 3,000 times—are minor.) A recorder that cost about \$150 ten years ago, sells for around \$90 today—and it's a better machine today than it was 10 years ago, simpler and more economical to operate.

The latest recorders are also more versatile than models were back in the 40's. Business firms, for instance, protect their property with tapes of stern, commanding voices calling for police and telling burglars the jig is up. And hen house custodians find that taped music not only pleases Pertelote, it coaxes greater egg production from her. So what qualities should you look for in order to get the right recorder for your purposes? Well, the best place to start

**TABLE A**

Recording time for 7-inch (1200-foot) reel on full- and half-track tape recorders

	Full Track Machine	Half Track Machine
At 17½ ips	2 hrs	4 hrs (2 hrs in each direction)
At 3¾ ips	1 hr	2 hrs (1 hr in each direction)
At 7½ ips	½ hr	1 hr (½ hr in each direction)
At 15 ips	¼ hr	½ hr (¼ hr in each direction)

If you're shopping for a tape recorder and have \$1500-plus, you can get Bell and Howell's Series 866 radio-phonograph-recorder combination shown at right. If you don't happen to have that much at the moment, units such as Webster Electric's Ekotape Model 240 (inset), are available for under \$200.

Two of the least desired types of locators are (1) lines marked under the reels indicating elapsed time and (2) dial-type pointers indicating remaining time. Neither is very accurate.

An odometer-type counter gives a much more accurate tape location if it is synchronized with some point on the tape each time.

**Maximum Reel Size** partly determines the kind of material you can record. You can't cram a 14-in. reel on a recorder designed for a five-in. reel (except on some machines where adapters are available at extra cost). Be sure you get a recorder that will take large reels if you plan to make long recordings. For most home or amateur uses a seven-in. reel is the most convenient. Professional machines will take 10-inchers.

**Tape Speed** more than anything else determines how much it will cost you to use your



recorder. The faster the tape is used, the more you will spend unless you re-use your tapes. Table A lists the recording time for a seven-inch (1200-ft. reel) of tape on a full- and half-track machine:

Tape speed is also important for fidelity. Table A shows that you get more playing time for your money by using slower tape speeds. But at slower speeds fidelity suffers.

Recorders operating at  $3\frac{3}{4}$  ips (inches per second) are usually adequate to cover the principal frequencies of the human voice. Hi-fi aficionados will want to record at higher speeds ( $7\frac{1}{2}$  ips and 15 ips) since recordings at these speeds will reproduce the tonal qualities of such instruments as violins, French horns, and pipe organs more faithfully.

**Controls.** There are two basic types of controls, mechanical and electrical. The elec-

TABLE B Recorder Features to Check With the Salesman

ELECTRONIC SPECIFICATIONS	This is GOOD	This is BETTER
1. Frequency response	80-8,000 cps $\pm$ 3 db	70-10,000 cps $\pm$ 3 db
2. Tape speed equalization	At higher tape speed only	At higher and lower speeds.
3. Level indicator	Neon bulbs	Magic eye or V.U. meter
4. Inputs	Microphone and radio	Microphone and radio with mixing
5. Heads and amplifiers	Two heads and single amplifier	Three heads and separate amplifiers for record and playback
6. Speaker system	1 good 6" speaker plus ext. speaker jack	8 or 10" speaker, multiple speakers, plus ext. speaker jack
7. Tone controls	Treble only	Bass and treble
8. Extras		Provision to use as a P.A. system. Remote control provision. Built-in radio
MECHANICAL SPECIFICATIONS		
1. Wow and flutter	0.3% at $7\frac{1}{2}$ ips	Less than 0.2%
2. Number of motors	One or two	Three, or synchronous capstan drive motor
3. Tape speeds	$7\frac{1}{2}$ ips, $3\frac{3}{4}$ ips	15, $7\frac{1}{2}$ and $3\frac{3}{4}$ ips
4. Fast forward and reverse	Should have both	Should have both but fast
5. Positive motor action	Mechanical braking	Won't spill or break tape when switched fast
6. Foolproof controls	Record interlock	Record interlock
7. Weight for portables	Less than 30 lbs.	Less than 25 lbs.

This information was developed from the manufacturers' literature and trade sources. (SCIENCE AND MECHANICS does not undertake to guarantee accuracy.)

### ELECTRONIC FEATURES(\*)

Manufacturer and Model	Price	*Frequency Response at 7½ lps	*Tape Speed Equalization	*Recording Level Indicator	*Inputs	*Heads and Amplifier	*Speaker System
Knight 98RZ940 Allied Radio Corp. 100 N. Western Ave. Chicago 80, Ill.	\$84.50	65-8,000 ±3 db	7½ only	Neon lamp	Mike Radio-phon	1 head 1 amplifier	5x7"
Pentron RWN The Pentron Corp. 777 S. Tripp Ave. Chicago 24, Ill.	\$139.50	50-9,000	7½ only	Neon lamp	Mike Radio-phon	2 heads 1 amplifier	4x6"
Bell RT88 Bell Sound Systems Columbus 7, Ohio	\$139.95	50-10,000	7½ and 3¾	Neon lamp	Mike Radio-phon	1 head 1 amplifier	6x9"
Mitchell 2525 Esco Electronics, Inc. 901 West Huron Chicago, Ill.	\$139.95	65-10,000	7½ only	Neon lamp	Mike Radio-phon	1 head 1 amplifier	Two 4" speakers
Ampro 745 Ampro Corp. 2835 N. Western Ave. Chicago 18, Ill.	\$159.50	60-11,000	7½ only	Magic eye	Mike Radio-phon	2 heads 1 amplifier	Two 5x7" woofers 3" tweeter
Masco 500 Mark Simpson Mfg. Co. 32-28 49th Street Long Island City 3, N.Y.	\$168.50	50-12,000 ±3 db	7½ only	2 neon lamps	Mike Radio-phon	1 head 1 amplifier	5x7"
VM 710 VM Corp. Benton Harbor, Michigan	\$189.00	40-14,000 ±5 db	7½ only	2 neon lamps	Mike Radio-phon	2 heads 1 amplifier	6x9" woofer 4" tweeter
Webster Electric W240 (Ekotape) Webster-Electric Co. Racine, Wisconsin	\$189.50	50-7,000	7½ only	Neon lamp	Mike Radio-phon	1 head 1 amplifier	8"
Wilcox-Gay 651 Wilcox-Gay Corp. Charlotte, Michigan	\$189.95	65-10,000 ±3 db	7½ only	2 neon lamps	Mike Radio-phon	1 head 1 amplifier	6x9" 4" 3" tweeter
RCA TTR3 RCA Victor Div. Camden, New Jersey	\$199.95	50-8,000	7½ only	2 neon lamps	Mike Radio-phon	1 head 1 amplifier	8½" two 3½"
Webcor 2711 Webster-Chicago Corp. 5810 Bloomingdale Ave. Chicago 39, Ill.	\$199.95	50-10,000 ±3 db	7½ and 3¾	Magic eye	Mike Radio-phon	2 heads 1 amplifier	8"
Revere T700D Revere Camera Co. 230 East 21st St. Chicago 16, Ill.	\$225.00	40-14,000 ±3 db	7½ and 3¾	2 neon lamps	Mike Radio-phon	1 head 1 amplifier	6x9"
Bell & Howell 300M 7100 McCormick Road Chicago 46, Ill.	\$299.95	50-15,000 ±2 db	7½ only	2 neon lamps	Mike Radio-phon	2 heads 1 amplifier	Two 8" woofers Two electro- static tweeters
Dukane 11A200 DuKane Corp. St. Charles, Ill.	\$395.00	50-10,000 ±1½ db	7½ and 3¾	Magic eye	2 mikes Radio-phon	2 heads 1 amplifier	6x9"
Ampex 801 with 820 Ampex Electric Corp. 934 Charter St. Redwood City, Calif.	\$714.50	40-15,000 ±4 db	7½ only	V.U. meter	Mike: line	3 heads 2 amplifiers	8" speaker, acoustic enclosure

## MECHANICAL FEATURES(\*\*)

*Tone Controls	*Watts Output	**Wow and Flutter at 7½ lps	**Number of Motors	**Tape Speed In lps	**Fast Wind and Rewind	**Positive Tape Braking	**Foolproof Controls	**Carrying Weight	Other Features
Treble loss	—	0.5%	one	7½ 3¾	yes	yes (mechanical)	yes (keyboard)	24 lbs.	—
Treble loss	4 watts	0.8% (flutter only)	one	7½ 3¾	yes	yes (mechanical)	yes (gearshift)	23 lbs.	P.A.
Treble loss	3½ watts	—	three	7½ 3¾	yes	yes (electrical)	yes (keyboard)	27 lbs.	P.A.
Treble loss	2 watts	0.3%	one	7½ 3¾	yes	yes (mechanical)	yes (rotary switch)	22½ lbs.	Tape storage space
Treble loss	5 watts	0.5%	one	7½ 3¾	yes	yes (mechanical)	yes (switch)	25 lbs.	Editing conveniences
Treble loss	5 watts	0.3%	one	7½ 3¾	yes	yes (mechanical)	yes (gear shift)	23 lbs.	P.A., Monitoring facility
Feedback Treble and bass boost	5 watts	0.5%	one	7½ 3¾	yes	yes (mechanical)	yes (keyboard)	30 lbs.	Tape timer, Auto shut-off, Patch cord, Pause control
Treble loss	2½ watts	0.3%	one	7½ 3¾	yes	yes (mechanical)	yes (rotary switches)	29 lbs.	P.A.
Treble loss	7 watts	0.35%	one	7½ 3¾	yes	yes (mechanical)	yes (keyboard)	35 lbs.	Tape index, Can mix mike and radio, P. A., Remote control
Treble loss plus music/ vocal switch	2½ watts	0.3%	one	7½ 3¾	yes	yes (mechanical)	yes (push-button)	38 lbs.	Remote control, Odometer, Patch cord
Treble loss	8 watts (peak)	0.4%	two (4 coil)	7½ 3¾	yes	yes (mechanical)	yes (rotary switch)	45 lbs.	Auto reel reverse, P.A., Reel turn counter, Auto shut-off
Treble and bass	5½ watts	0.3%	one	7½ 3¾	yes	yes (mechanical)	yes (keyboard)	30 lbs.	P.A., Odometer, Remote control provision
Treble loss	10 watts	0.2%	three	7½ 3¾	yes	yes (electrical)	yes (push button)	42 lbs.	Drop-in tape threading, P. A., Odometer, Auto tape shut-off
Treble loss	7½ watts	0.3%	one	7½ 3¾	yes	yes (mechanical)	yes (push buttons and switch)	45 lbs.	P.A., Odometer, Tape splicer
Bass/treble on amplifier	10 watts	0.25%	one	7½ only, others on order	yes	yes (mechanical)	yes (two switches)	56 lbs. in two cases	P.A., Two channel mixer, Drop-in tapethreading

TABLE C

Check for These Tape Recorder Features When Shopping (listed in order of importance).

**ELECTRONIC****MECHANICAL**

1. **Frequency Response.** The highest and lowest sound frequencies that can be recorded and played back; also includes the db variation within this range.
  2. **Equalization for Different Tape Speeds.** An adjustment which makes the recorder give its best performance at each tape speed.
  3. **Level Indicator.** This may be one or two neon bulbs, a magic eye, or volume indicating meter.
  4. **Inputs.** There should be at least two. One for microphone, one for radio. On better machines there are provisions that permit mixing the two and simultaneous recording of both.
  5. **Separate Heads And Amplifiers.** Lower-priced machines use a single amplifier switching from record to playback. More expensive machines use separate amplifiers for each. This usually permits better equalization. Less expensive machines usually use the same head for recording and playback. More expensive machines use a separate head for each (each head can be designed for best performance).
  6. **Speaker System.** All recorders should provide a jack to permit a use of an external high fidelity speaker. High fidelity (particularly bass) is difficult to obtain with a small tape recorder cabinet. One good speaker is enough, the larger the better. Multiple speakers—as used in tape recorders—usually do not aid fidelity; they may help disperse sound more uniformly.
  7. **Tone Controls.** Required on playback only. Separate bass and treble controls are helpful. Better machine will have bass and treble boost as well as bass and treble drop.
  8. **Extras.** Inputs for public address systems, remote control switches, mikes, etc., are helpful.
1. **Wow And Flutter.** Listening for wow and flutter is a way of telling how good the motor and bearings are. If they're poorly made and aligned, recordings of sustained tones (voice, organ, or piano) will have an extraneous tremolo.
  2. **Number Of Motors.** Two or three are preferable. One or two well-made motors give improved wow and flutter performance over three poorly-made motors.
  3. **Tape Speeds Available.** A home machine should be able to play back and record at least  $7\frac{1}{2}$  ips and  $3\frac{3}{4}$  ips. A professional machine should be able to run at 15 ips and  $7\frac{1}{2}$  ips at least. Most pre-recorded tapes on the market are recorded at  $7\frac{1}{2}$  ips, with some at  $3\frac{3}{4}$  ips.
  4. **Fast Forward And Fast Rewind.** These controls save considerable time when changing reels and locating sections within a reel.
  5. **Positive Switching Operation.** When switching between forward and fast forward, forward and rewind, etc., no setting of the function switching should permit the tape to spill or to break.
  6. **Ease of Switching.** Switching controls should be grouped in one section of the recorder. Push button or piano-key switching is most desirable. All recorders should have some type of interlock to permit recording only when an extra switch is thrown. This prevents most erasing of tapes accidentally.
  7. **Weight And Portability.** Twenty to 30 lbs. is a good portable weight for the average home type recorder. If you want to do a great deal of interviewing, a smaller machine would be better. There is some sacrifice of fidelity in the very smallest machines under 10 lbs.

trical types actuate a solenoid; the mechanical types work by pressure. Electrical controls are more expensive, but are easier to adjust. On a very light portable model, mechanical controls would be most practical since their components weigh less.

Piano-style keys, knobs, levers, and push-buttons operate the various makes. Some recording specialists prefer either the piano keys or push-buttons.

Controls to look for are record/playback; volume; fast forward/fast reverse; and record-level indicator. One necessary control is an interlock to prevent accidental erasure. On a well-designed recorder an interlock's actuating handle will be so distinctively designed that it cannot be mistaken for any other control.

**Weight.** Many of the portables used in homes, schools, and churches weigh from 15 to 30 lbs. and are no larger than a typewriter. If you're going to use it for field work, carrying it from place to place frequently, better buy one of the lightweight models that weigh 25 lbs. or less.

Remember though, to some degree, there is a correlation between weight of the recorder and quality of recordings. Weight in the right places reduces distortion from waver and uneven speed.

**Style and Finish.** Keep in mind that while at-

tractive furniture-style cabinets make recorders handsome additions to your furnishings, they up purchase price a good deal. With a luggage-type portable case you can tape and play back just as fine recordings as you can with a walnut-cabinet model.


**ELECTRONIC FEATURES**

**Overall Frequency Response** refers to the frequency of sound waves a recorder can record and play back. It is expressed in cycles-per-second (*cps*). You can only make good recordings within the overall frequency response limits of your machine.

The average adult male's voice has a 100-to-5,000 *cps* range. The human ear, roughly speaking, can hear sounds from 20 to 18,000 *cps*. Many persons, however, cannot hear this well.

Manufacturer's specifications give the *low and the high frequency* limits of their recorders. In general, low-priced recorders suitable for taping such material as music, bird calls, and sound effects have overall frequency response ranges of about 80 to 8,000 *cps*. Higher-priced machines for the same material will bracket 30 to 15,000 *cps*. For recording speech, a range of 150 to 4,000 *cps* is adequate.

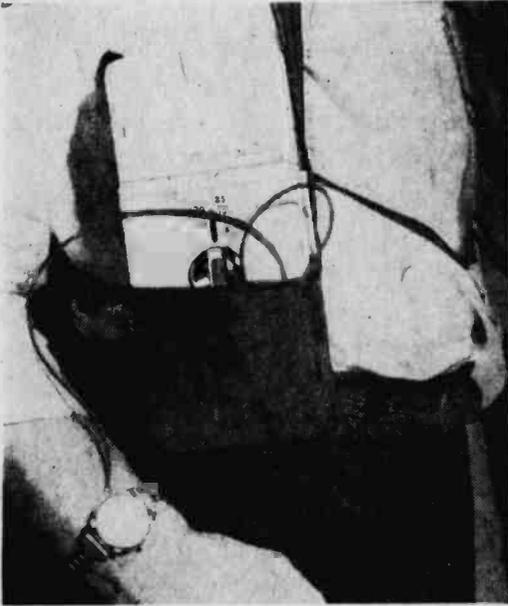**Frequency Response Deviation** refers to a ratio



Carried in a shoulder-holster, this three-lb. Midgetape, manufactured by Mohawk Business Machines Corp., is used by law enforcement agencies, salesmen and many others. Amplifier Corporation of America has an 11¼ lb. recorder which is built into a brief case and is widely used by salesmen.

of loudness which is pegged in terms of the loudness of individual sound tones. A mathematical term known as a decibel (db) stands for the ratio between a common point of loudness or reference volume level (usually at 400 or 1000 cps) and the volume level at another frequency. The faithfulness with which a recorder picks up and records every sound within its frequency response range at the same relative degree of loudness as the original sound determines the closeness of the finished recording to the real thing. That is, a recorder should, ideally, give a "flat" response over its entire frequency range. But this ideal is found only in the most expensive commercial equipment; most equipment will deviate to some extent.

So you will want to remember two things when considering the sound fidelity of a tape recorder: first, the highest and lowest frequencies it will reproduce, and second, how flat its response is between these frequency limits. If audio signals of exactly the same amplitude were fed into the recorder at each in-between frequency, would they be recorded at the same volume? If not, how much would they be above and below an arbitrary reference point?

A perfectly flat system would have no difference, that is, it would have a ratio of 0 db. A tape recorder, with specifications such as 30 cps to 13,000 cps,  $\pm 1$  db at 15 ips, for instance, would be a very fine unit.

Machines with larger deviations, however, are satisfactory for much work: A machine with an overall frequency response of 40 cps to 10,000

cps  $\pm 2$  db at 7½ ips would still make excellent recordings of well played music; 50 cps to 7,000 cps  $\pm 4$  db at 3¾ ips—recordings acceptable for many listeners; 80 cps to 5,000 cps  $\pm 5$  db at 1⅞ ips—many listeners would: 1) object to the wide variations in intensity in normal speech; 2) notice the slight differences of intensity between differently pitched passages in music; and 3) find the sound generally irritating.

**Dynamic Range** is a highly important tape recorder feature for it limits how low a sound and how high a sound can be recorded. If the recording amplifiers have considerable hum and noise in them they will mask over low sounds. A recorder which has a poor dynamic range will not be able to capture the *pianissimo* passages in music, for example. The dynamic range, or signal to noise ratio, is usually expressed in number of db's. The better class of home recorder will have a dynamic range of 40 db or better. Some professional recorders have dynamic ranges of better than 60 db. (Symphonic music will often have dynamic ranges of 60 to 70 db.)

**Equalization Correction.** The slower the tape speed, the more closely wave lengths are crowded on the tape. Sounds of higher frequencies, having the shortest wave lengths, suffer most. A good recorder circuit should build up the higher frequencies to overcome this loss of correct pitch caused by low tape speed. The process of doing this is called *equalization*.

When tape speed is doubled (from 3¾ to 7½ ips for example), the loss occurs an octave higher, and the equalization should be changed to build up the new high limit.

**Recording-Level Indicator.** A distortion level of less than three percent is hard to detect. Many table model radios have distortion as high as 10 percent. Recording at too high a volume level: 1) makes it difficult to erase the tape; 2) introduces distortion; 3) magnetizes the recording head; and 4) reduces the natural dynamic volume range. For all of these reasons you'll want a good recording-level meter on the tape recorder you buy.

A single neon or a magic-eye bulb is the simplest effective type of level indicator. A set of dual bulbs (one that flickers continuously and another that flickers when the level is too high) is more satisfactory than the single bulb. A magic eye indicator is better than the neon bulb type. And a volume-unit indicating meter is best.

**Inputs.** Some of the more professional style recorders have remote control plugs. If you expect to use your machine in theaters or in the field you may want to look for a model equipped with them. Most of the less expensive recorders will handle one microphone (high impedance) and/or one input such as radio or phonograph.

With a more versatile recorder circuit you can mix in a microphone and a phonograph at the same time on separate controls. And the more expensive recorders have inputs such as



Home uses for a recorder are almost unlimited. Narration for home movies, for instance, can be recorded (and synchronized with projector by bar-markings on tape); or dramatic readings, complete with sound effects, can be transcribed. Above, a fire is being simulated with cellophane held near the microphone. The sound of human footsteps in snow are made by squeezing a box of cornstarch; horsesteps on a dirt road, by manipulating two coconut half-shells in a pan filled with sand (for a gravel road, add small pebbles to sand); thunder, by rattling sheetmetal; walking through underbrush, by twisting broomstraws; etc.

line plugs for bringing in sound from a telephone remote line, radio, phonograph, P. A. system, or other source.

#### Separate Recording and Playback Amplifiers.

Some machines with separate record and playback heads also have separate recording and playback amplifiers. With these, the tape can be monitored or listened to as it is being recorded and you can make a continuous check on the recording process, rather than waiting until the recording is finished.

**Heads and Head Alignment Adjustments.** Dual heads are a compromise if you want your recorder to have maximum usefulness. Most lower- and medium-priced machines have two separate magnetic heads, one for erasing, the other for both recording and playback. For maximum utility, you may want a recorder with three separate heads, one for erasing, one for recording, and one for playback.

For highest fidelity you should choose a machine with adjustable heads so that you can align the heads with the tape. The recording or playback head must always be perpendicular to the tape's direction for good recording.

**Editing Ease.** On most of the non-professional tape recorders the erasing and combination record-playback heads are shielded with cover plates. These covers look nice but they make editing difficult. So do reels that will not move when the tape is not in "run" position. It is best to remove the cover plates when extensive split-word editing is done.

When marking tape for editing, we prefer to move the tape manually (by turning the take-up and feed reels by hand) with the sound on. On many of the moderate-priced models this cannot be done. You have to run the machine with the motor going full speed, then control tape position by adjusting push buttons and knobs. This makes it hard to find words.

**Full vs. Half Sound Tracks.** The signal, or strength of magnetization, is stronger on full-track machines. Less area on the tape is used on half-track recordings.

All home recorders are likely to be half-track. On these machines about half the tape width is used to record in one direction, the other half in the opposite direction. That's how you get twice the recording time on a reel of tape on a half-track machine as you do on a full-track recorder. And that's why you spend less for tape with a half-track outfit. But when you cut portions out while editing the track on one half of a tape, you're also cutting out some of the programs on the other half.

**Speakers.** Low- and medium-priced tape recorders generally have built-in speakers; this is a good feature for portable machines. You should have at least one good six- to eight-inch speaker; a bigger one is better yet.

Most of the better recording units have a jack for plugging in a larger external speaker or for feeding a hi-fi amplifier.

**Tone Controls.** On most recorders these controls for decreasing or boosting the intensity of the low, middle and/or high tones operate only during playback. On a few they function during both recording and playback.

A single tone control usually does only one thing—eliminates the high frequencies. This makes a muffled reproduction. If a machine has both treble and bass boost and droop controls, you can usually add bass tones and retain the highs, or reduce the bass without producing shrill high frequencies.

**Public Address Operation.** Any recorder which has switching controls for connecting the microphone directly through the amplifier to the speaker can be used as a public address system.

**Batteries.** Most portable, battery operated machines require a "B" battery and several flashlight type dry cells for filament and motor operation. Other portable machines use a rechargeable wet battery. Spring-wound models for recording in remote areas are available.

Wherever you want to record, keep in mind what *kind* of material you're going to want to get. If it's to be Junior at home reciting Tennyson, the church choir live or symphony concerts off the radio, then \$100 to \$200 should get what you want.

If you want to concentrate on voice tapes at work or at school you can buy recorders for \$90 to \$160. But if you're most interested in taping music and doing the job with excellent fidelity, then you'd better be prepared to spend \$300 to \$350 or more.

# B-Battery Eliminator for Portable Radios

**P**ERSONAL portable battery-operated sets are very convenient gadgets when they are working. Usually when these sets conk out, it's because the A or B batteries have gone dead. Many of today's compact portables use easily-obtained ordinary flashlight cells for A-power. However, the B battery is a specialty item many appliance stores may have to order for you.

When used indoors, it is foolish to waste expensive packaged power when the portable, even if it is not designed for power line operation, can be made to operate off the 115-125 volt ac-dc power line, thus saving the B battery for use only when the set is outdoors. This safe, compact B Battery Eliminator (Figs. 3, 4 and 5) costs less to build than the battery it replaces which retails for about \$2.50 plus local taxes. You can change over from battery to eliminator use, incidentally, in just about one minute's time!

When your radio is operated with this battery eliminator, you'll notice, first of all, a great improvement in tone quality. That's because most small portables are limited to 67½ volts plate supply, but this eliminator delivers 90 volts dc from the power line. Most portable sets are actually designed for best operation at 90 volts, but battery space limits operation to 67½.

Ordinarily, a portable radio operates without benefit of a ground. However, when operated with the eliminator, a ground is automatically established through the power line. Reversing the line cord plug in the outlet will show you which position does the best job of stepping up the volume and range of the receiver.

Because the size and shape of B batteries vary, we chose a set employing a minimum of space for the B battery. The reader can always use a larger plastic box to contain the eliminator if his set is not as crowded as our receiver. To house the eliminator, we secured a re-use type, hinged, 1 x 1¾ x 4¾ in. plastic box (originally containing a boy's bow tie). The eliminator itself was 1 in. shorter than the B battery it replaced.


You'll need just five electronic components to make the eliminator: a half-wave selenium rectifier, two electrolytic capacitors and two resistors. Mount these on a strip of ¼ x 1½ x 3⅞ in. Bakelite as shown in Fig. 2, drill-



Look Ma, no B-battery! Eliminator shown in Fig. 3 saves on costly B-batteries.
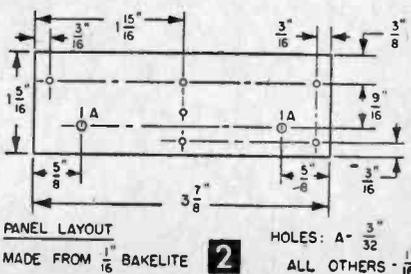
### MATERIALS LIST—B-BATTERY ELIMINATOR


- 1 hinged plastic box (see text)
- 1 6 ft. line cord and plug
- 1 pc ¼" Bakelite or fiber; 3⅞ x 1½"
- 2 20 mf., 150 w.v. electrolytic capacitors (Cornell-Dubilier # Br-2015)
- 1 40 or 50 MA selenium rectifier (Radio Receptor #8J1 or Sarkes-Tarzian #50)
- 1 3300 ohm, 1-watt IRC type BTA-1 resistor
- 1 33 ohm, 1-watt IRC type BTA-1 resistor
- 1 pr United-Carr battery snap connectors
- 2 3/48 fh machine screws and nuts




ing or punching the mounting holes as indicated. With the strip completed, place it inside the plastic box and mark, on the plastic, the locations of the two holes marked "A". Drill ⅜ holes at these points through the plastic, and countersink them on the underside with a ⅜ twist drill.

Next, file a groove or slot in one end with a 3-cornered file, ⅜ wide. In the opposite end of the box, file two grooves with a ⅜ dia. rat-tail file. These filed slots accommodate the line cord and the B minus and B plus leads.

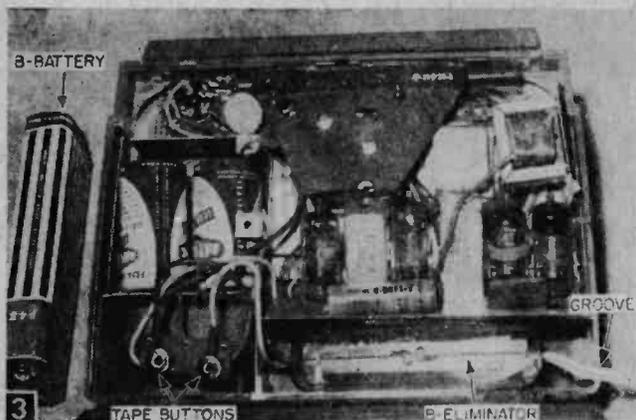
Because of the limited space available, we used a novel method of obtaining tie point lugs for soldering-in components. The two




How Eliminator fits space occupied by B-battery with a full inch to spare. To prevent shorting, apply strip of adhesive tape over exposed connector buttons. (A) shows closeup view of eliminator in its plastic box. Slots filed in case provide clearance for line and leads. (B) shows bottom view of eliminator. Pigtail leads of capacitors form direct wiring and tie point lugs. Two fh screws secure the components rigidly inside the plastic box.

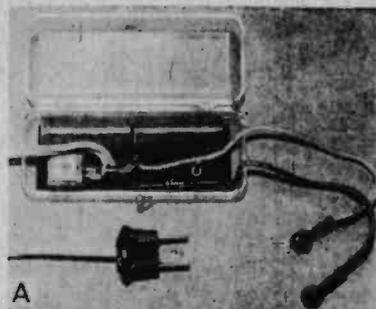

A

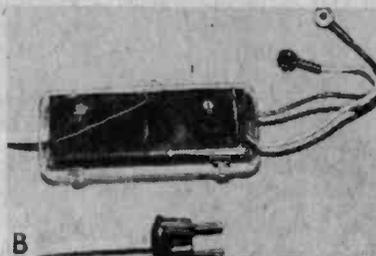


B

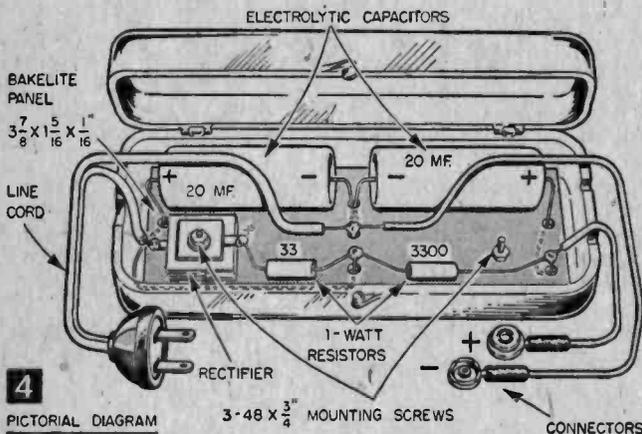

4

PICTORIAL DIAGRAM

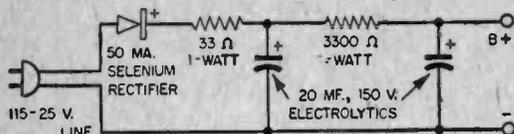

5

SCHEMATIC DIAGRAM

20 mf., 150 v.v. electrolytic capacitors were arranged so both negatives were to the center of the Bakelite strip. The pigtail leads were then laced through the  $\frac{1}{16}$  holes (Fig. 4) as shown in the pictorial. With all but  $\frac{1}{2}$  in. of each lead clipped off, the wires were formed into small loops with flatnose pliers. These loops made perfect soldering lugs for attaching resistors and flexible wire leads.

Dotted lines in Fig. 4 show how all cross-over leads are on the underside of the Bakelite strip, completely insulated from components. The B-battery snap connectors may be salvaged from a dead cell, or purchased new where you buy the main components. However, if you buy a strip type connector observe that its leads will be col-

ored the reverse of the actual polarity required. Thus, black or yellow lead will be *plus*, and red lead *minus*. Snaps are wired as in Fig. 4 regardless of lead color.

With wiring completed, place Bakelite strip in plastic box, install a 3-48 flathead machine screw,  $\frac{3}{4}$  or 1 in. long, up through the selenium rectifier and secure with a nut. Insert and secure another 3-48 screw, about  $\frac{1}{4}$  in. long, in the remaining hole. Finally, slip the fixture cord and B-leads into their respective grooves and shut the box cover.

Attach the B-lead snaps to their mates in the set. Apply a strip of adhesive tape over the snap heads to eliminate any possibility of a short circuit. Do not plug-in the B-Battery Eliminator until snaps have been connected (you might get a shock).

File a not-too-deep groove in the side of the radio cabinet cover (Fig. 3) to clear the line cord. Cover will help grip wire when it has been closed.

Why didn't we design this unit so as to also furnish A power? First, the flashlight batteries which furnish A power are cheap and readily available. Secondly, it would be necessary to re-wire most sets from a parallel to series filament string and add circuit filters. In addition, a voltage dropping resistor generating a great deal of heat would be involved. Finally, the extra components would require too much space.

This little B-battery eliminating power supply in its present form uses very little power, and does not generate heat. It should be disconnected from the power line when the set volume control is turned off. The builder can, however, insert a feed-through Bakelite switch (25¢ in dime stores) in the line cord.—T. A. BLANCHARD.

# Decade Resistance Box

By HAROLD P. STRAND



Decade resistance box in use in radio servicing job. Various values of resistance are being applied across terminals where a defective resistor was formerly soldered, and which is now unidentifiable due to extreme heating.

Ten ohms to ten megohms instantly available for test or experimental work with this handy, portable unit

PROVIDING 51 different standard 1-watt resistors for instant circuit insertion by means of three 17-point rotary switches and plug-in leads, this decade resistance box is ideal for substitution use in the case of defective or suspect resistors in existing circuits, or as a test selection of values for new circuits. Its application in radio and television service work is obvious, and for experimental work—especially with transistor circuits where the amount of resistance used is often critical—its use is almost a necessity.

The 51 resistors in the unit described in this article range from 10 to 470 ohms, 560 to 12,000 ohms, and from 15,000 ohms to 10 megohms; all of 10% tolerance. Resistors of other values can be used to make up a different set of ranges if desired, and 5% or 1% tolerance resistors can be used where greater accuracy is demanded (and cost is no concern), but the values indicated here will usually be found to encompass all those needed for ordinary servicing or experimenting.

The red plug-in jack on the top panel of the Bakelite case housing the unit is common; the other three jacks (A, B, C in Fig. 2) tap off from the individual switches. With the leads plugged in the common and A, you can use all the resistors in the first group (10 to 470 ohms); changing the second lead to the B jack, you get the second group, 560 to 12,000 ohms; to the C jack, 15,000 ohms to 10 megohms.

Dial plates numbered from 1 to 17 are provided at each switch and a chart cemented to the bottom of the case identifies each resistor value. (The bottom is the only location on the case where a space large enough for the chart is

available. If desired, a second chart can be typed up and placed in a transparent plastic envelope for more convenient use at the bench.)

Resistor leads are formed around two nails driven in a piece of wood, thus assuring uniform looped ends and length (see Fig. 3A). Place the nails (6d finish) 1 in. apart on the board and then cut off their heads. Indicate center spacing of the resistor bodies with pencil marks on the board. After bending the leads, cut them off to leave short loops suitable for placing in the switch terminals

at one end, for fitting around the bare wire circular common terminal at the other. (Ohmite or Allen Bradley 1-watt resistors should be used because of their comparatively short length. Some other makes are much longer and their use may result in a fitting problem within the case.)

Pass the looped ends of the resistors through the switch terminal holes from the back side so that the loops at the other ends will be turned out. Press them down tightly with pliers and

## DECADE RESISTANCE BOX CHART

(A)		(B)		(C)	
1	10	1	560	1	15K
2	12	2	680	2	22K
3	15	3	820	3	33K
4	18	4	1000	4	47K
5	22	5	1200	5	68K
6	27	6	1500	6	100K
7	33	7	1800	7	150K
8	47	8	2200	8	220K
9	56	9	2700	9	330K
10	68	10	3300	10	470K
11	82	11	3900	11	680K
12	100	12	4700	12	1.0M
13	150	13	5600	13	1.5M
14	220	14	6800	14	2.2M
15	270	15	8200	15	3.3M
16	330	16	10K	16	4.7M
17	470	17	12K	17	10M

K = 1000 ohms

M = megohms



DECADE RESISTANCE BOX—MATERIALS LIST



- 1 Bakelite case  $2\frac{1}{4} \times 5\frac{1}{4} \times 6\frac{3}{4}$  (MS 218)
- 4' #18 test lead wire
- 3 17-position switches (Mallory 31117J)
- 2 banana plugs (MS 209-black)
- 3 dial plates (Mallory #467, marked 1-17)
- 2 insulated alligator test clips (black)
- 3 binding posts (Superior DF30BC-black)
- 1 binding post (Superior DF30RC-red)
- 1-watt carbon resistor, 10% tolerance, Ohmite or Allen Bradley—

One of each of the following

10 ohms	560 ohms	15,000 ohms
12 ohms	680 ohms	22,000 ohms
15 ohms	820 ohms	33,000 ohms
18 ohms	1000 ohms	47,000 ohms
22 ohms	1200 ohms	68,000 ohms
27 ohms	1500 ohms	100,000 ohms
33 ohms	1800 ohms	150,000 ohms
47 ohms	2200 ohms	220,000 ohms
56 ohms	2700 ohms	330,000 ohms
68 ohms	3300 ohms	470,000 ohms
82 ohms	3900 ohms	680,000 ohms
100 ohms	4700 ohms	1.0 megohm
150 ohms	5600 ohms	1.5 megohms
220 ohms	6800 ohms	2.2 megohms
270 ohms	8200 ohms	3.3 megohms
330 ohms	10,000 ohms	4.7 megohms
470 ohms	12,000 ohms	10 megohms

All of the above material can be obtained from Lafayette Radio, 165-08 Liberty Avenue, Jamaica 33, N. Y. or in New England from their branch at 110 Federal Street, Boston, Mass.

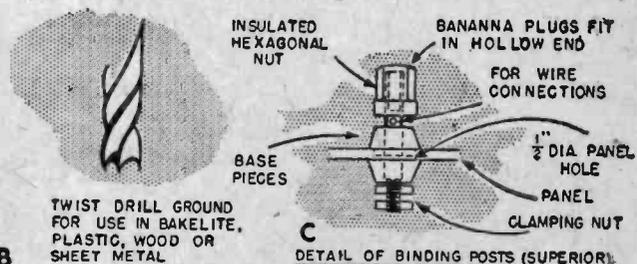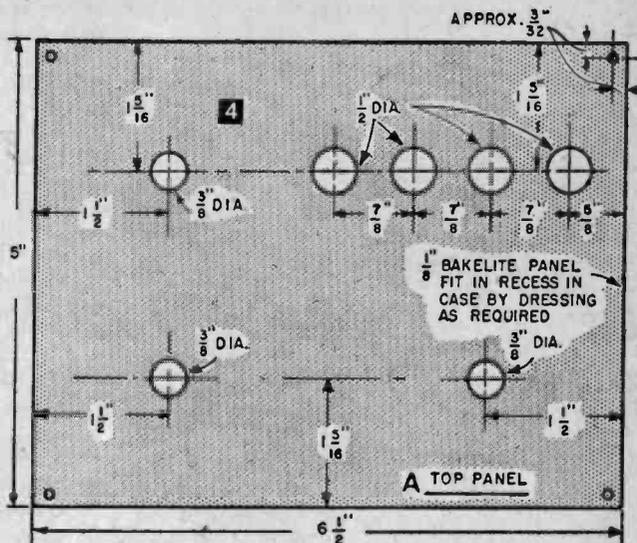- 1 piece Bakelite  $\frac{1}{8} \times 5 \times 6\frac{1}{2}$ "
- 2' of #16 plastic insulated stranded hook-up wire; 15" of bare #14 copper wire; four 4-40 machine screws  $\frac{3}{8}$ " long, binder head plated screws preferred




for 4-40 machine screws; the four Superior combination binding posts require  $\frac{1}{2}$ -in. dia. holes; the switches,  $\frac{3}{8}$ -in. dia. holes. Holes should be made with a twist drill ground as shown in Fig. 4B; regular ground twist drills have a tendency to tear such Bakelite.

Switches come equipped with a round plate having a pin that may be used as a stop. Since all 17 switch contacts are needed for this unit, discard this stop. Cut off the shaft at the first


marked point and install, using a washer on each side of the panel, applying cement (such as coil dope) to the lower washer to keep the switch from turning and to keep the dial plate, top washer and nut clamp assembly tight. Then install knobs.

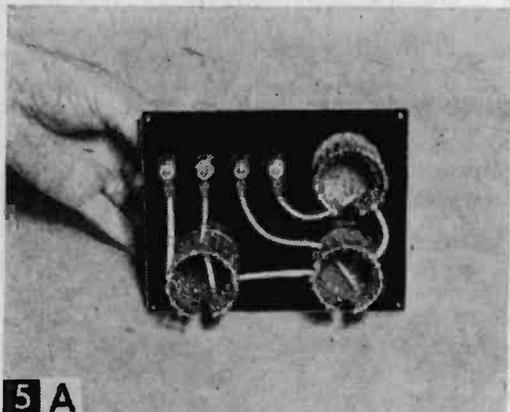The next step is fitting wire rings to the looped ends of the resistor leads and bending them over tightly with pliers (Fig. 3C). Form the rings from bare copper wire (about #14




5 A

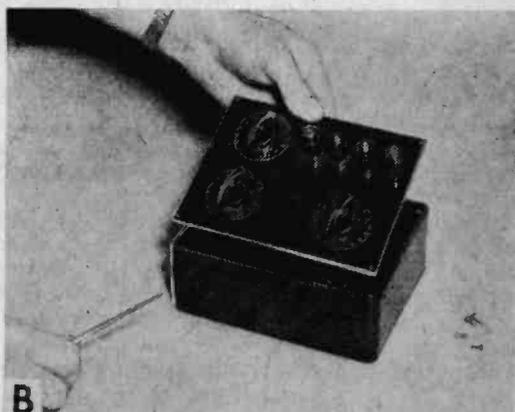Back of the completely wired unit is shown in A. Use #16 insulated wire from the binding posts and also between the ring terminals.



5 B

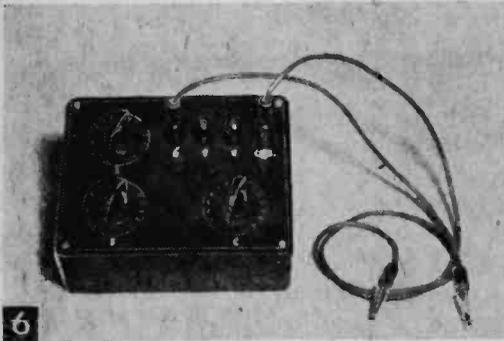Attach the completed panel to the Bakelite meter case, using 4-40 screws at the four corner holes (B). It fits flush in recess of case.





Completed job shows the lettering that was put on with decals sold for the purpose. After decals have thoroughly dried, apply a thin coat of clear plastic with a small brush to make them permanent. Banana plugs and clips soldered to short flexible leads make connections quick and easy.

gage), leaving open ends at the wide-spaced switch contacts. Then connect flexible insulated leads from ring to ring to join them as a common terminal for all resistors and run a lead from one

of the rings to the red binding post. Use #16 wire (negligible resistance itself) for these connections (see Fig. 3D). Finally, run a length of #16 wire from each black binding post to the arm contact of the switch it is controlled by (see Fig. 5A).

Banana plugs and alligator clips soldered to short lengths of rubber-insulated, extra-flexible, #18 test lead wire make convenient connections between the binding post jacks and the points on the circuit under test. Switches are marked A, B and C, and the binding posts to which each switch is connected are similarly marked for quick identification. You can do this with a fine brush and white paint or use decals as supplied by electronic stores for such work.

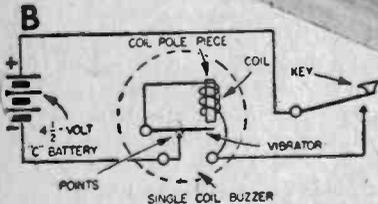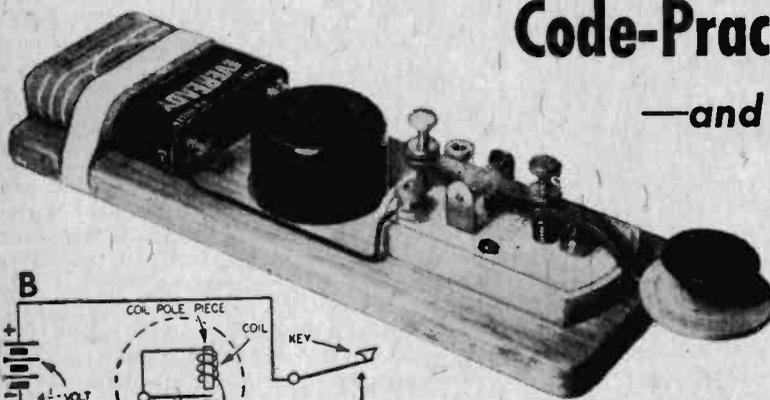The decade resistance box can also be used with the leads plugged into either A and B jacks or B and C, putting the banks of resistors in the two groups used in series for special test cases. Where standard RETMA values only are of interest, however, the leads are used with one in the common and the other shifted to either A, B or C post jack.



## Code-Practice Buzzer


—and How to Use It


By ARTHUR TRAUFFER

Here, fastened to a  $\frac{1}{2} \times 3 \times 9$  in. wood base, is a simple code-practice set. The key is at the right, the buzzer is in the center, the "C" battery is on the left. Inset shows schematic representation of same apparatus.

**M**EET the Buzzer, an electromagnetic vibrator used for signaling purposes. Figure 1B gives a typical schematic for a single-coil buzzer. Figure 2 shows the physical make-up of a single-coil, low voltage, high-frequency buzzer. Note in Fig. 2 that the point on the buzzer's vibrator and the point on the left-hand battery terminal touch, thus closing the circuit through the coil (see Fig. 1B). When a source of voltage is connected across the terminals, current will flow through the coil, setting up a strong magnetic field in the pole piece which then pulls the vibrator toward it, thus separating the points. When the points separate, current flow is interrupted, the vibrator returns to its original position, the points again close, and current again begins to flow through the coil and the cycle is repeated. That, in essence, is how

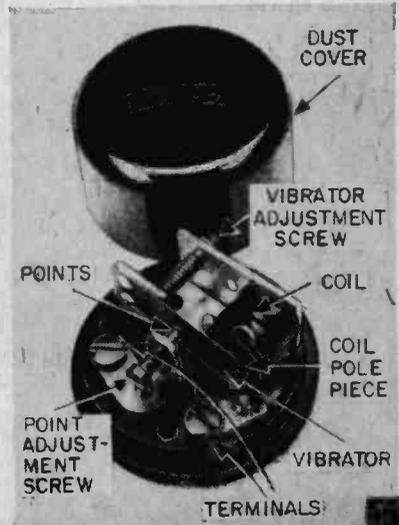
Low-voltage, high-frequency, single-coil code-practice buzzer with dust cover removed to reveal its components. Designed for students of the radio code, this is a Johnson Speed-X Model 114-400.



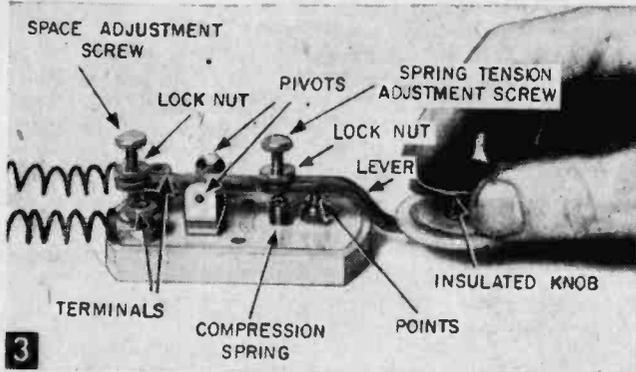

3

Above, A code-practice key for the beginner (Johnson Speed-X Model 114-300). Knob has been converted to Navy type by drilling hole in plastic poker chip and fastening it between standard knob and lever. Navy type knob serves as finger rest and reduces fatigue when key is used for long period of time. Below, With this set-up, you can practice code to your heart's content without disturbing other members of the family. The buzzer is muffled by wrapping it in cotton and sealing it in a half-pint Mason jar. You hear the buzzer in the phones.

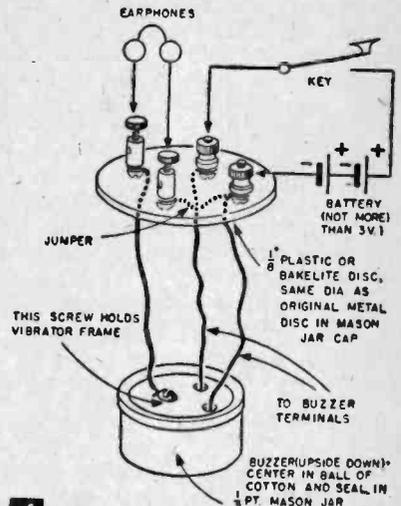

4 ASSEMBLY AND WIRING FOR QUIET CODE-PRACTICE



5

a buzzer is made to operate.

The side-to-side movement of the vibrator is so rapid that it gives forth a high-pitched whine. The frequency of this tone, of course, depends upon the number of times the vibrator moves per second. Note in Fig. 2 that there are two adjustment screws, one for the vibrator and one for the points. When these screws are properly adjusted, the buzzer will give a clear high-pitched tone, free from sputtering and raspiness.

A Radio and Telegraph Key is simply a hand-operated switch used to interrupt the flow of current in a radio or telegraph transmitter and thus send a message from one location to another (either through the air or along wires). The message is transmitted by means of the radio and telegraph codes.

The three types of keys most commonly used are: 1) a vertically operated lever, (Fig. 3) on which the dots and dashes of a code are formed by downward thrusts; 2) a semi-automatic, side-to-side operated key (called a "bug") on which dashes are formed by pressing the lever to one side, while the dots are automatically formed by a weight vibrating on a spring when the lever is

pressed to the other side; 3) a double-action key (called a "side-swiper"), which is similar physically to the vertically operated lever except that it has a blade that moves from side-to-side to form dots and dashes. The double-action key is similar to the semi-automatic key in operation except that its double-action is much simpler and does not form the dots automatically.

A key, a buzzer and a source of voltage connected as in Fig. 1 will give you a simple and compact code-practice set. In Fig. 1, the base is a 1/2x3x9 in. piece of wood. The buzzer and key are mounted on the base with rh wood screws, and the 4 1/2 v. "C" battery that serves as the source of voltage is taped to the base. Instead of a "C" battery you can use two #2 flashlight cells of 1 1/2 v. each, connected in series to provide 3 v. Leads are soldered directly to the cells, and the cells are held together with adhesive tape. You can also use two #6 dry cells (1 1/2 v. each, connected in series), but these are too large to mount on the base shown in Fig. 1. It's better not to use a 2.5 v. or a 6.3 v. a-c filament transformer for powering a buzzer, because of the interference caused in nearby radios and TV sets. And potentials higher than 4 1/2 v. are not recommended for code-practice buzzers, either, because with them you may have excessive sparking and pitting of the points.

Wire your code practice set with bell wire obtained at the dime store. It isn't necessary to drill holes through the wood base to reach the terminals in the buzzer; simply file notches in its bottom rim and pass the wires through the notches. When mounting the buzzer and key on the wood base, do not draw-up the screws too tightly or you may crack their Bakelite bases.

With a Quiet Code-Practice Set, you can practice the code all you want, any time you want, without disturbing other members of the family. To make a quiet set, put the buzzer in the center of a ball of cotton and seal it in a half-pint Mason

jar (Figs. 4 and 5). This will muffle the buzzer's sound, but when you wire in a pair of phones, you'll hear the buzzer in them. Soft, flexible, insulated wire leads should be used to connect the buzzer to the four binding posts on the plastic or Bakelite disc. Stiff wires will permit mechanical vibrations from the buzzer to travel up them and use the plastic disc as a sounding board. The center screw on the bottom of the buzzer holds the bracket to which the vibrator is fastened, so you can make one of your phone terminal connections to it (Fig. 4).

Be sure to place the buzzer in the center of the ball of cotton, because if it should touch one side of the jar, mechanical vibrations will use the jar as a sounding board. And don't pack the cotton too tight or vibrations will pass through the cotton and use the jar as a sounding board. If some do, in spite of precautions, stand the jar on a rubber pad or some other soft material.

If volume in the earphones is too high, you can reduce it by connecting a .001 mfd. capacitor in series with one of the phone leads. The value of the condenser will determine the strength of the signal in the phones, so if with a .001 mfd. capacitor you still get too loud a signal, use 500 mmfd. or 250 mmfd. instead. Once the value of the capacitor has been determined, connect it in place of the jumper between the disc's battery and phone terminals as shown in Fig. 4.

Incidentally, the FM fan who has a set without a tuning indicator can use a buzzer muffled in a jar



of cotton as a tuning aid. Tape two #2 flashlight cells to the jar containing the buzzer, fasten one lead from this battery securely to one buzzer terminal on the plastic disc on the jar and fasten the other lead to the other terminal with an alligator clip so that you can disconnect the buzzer when desired. Now, place this unit close to an FM receiver (on top of the set is a good place) so as to cause AM interference with the FM signal being tuned in. Since the function of the FM circuit is to reject AM and to detect FM, adjust the tuning knob of the receiver for the weakest buzzer signal and you will have the FM station "right on the nose." In FM receivers, stations come in at three closely-spaced points on the dial, the center point being the loudest and the correct point. Buzzer volume will weaken at these three points, and will be weakest at the center point.

**Amplifying a Buzzer.** Instead of quieting the buzzer, you may want to greatly increase its volume so that dots and dashes can be clearly heard by a number of code-practice students anywhere in a room. One way to do this is to place your code-practice set close to the loop antenna on the rear of an AM radio with the buzzer near the center of the loop. The loop will pick up the R.F. energy generated by the buzzer's sparking points and the radio will detect, amplify, and reproduce this R.F. in the usual manner. To pick up the buzzer signal, tune the radio to a quiet place between two stations; volume can be controlled, of course, with the radio's volume-control.

For a code-practice buzzer "amplifier" that will tremendously "amplify" the buzzer's signals without the use of vacuum tubes, see Figs. 6 and 7. The chassis of this unit is made up of two pieces of 7x11 in. 5-ply plywood screw-fastened together and braced with 3x3 in. iron angles (Fig. 7). The front panel of the chassis is 1/2-in. plywood; the base, 1-in. Buzzer and key are mounted on the base with wood screws. Two S.P.D.T. knife switches are mounted side-by-side for volume selection. (If you have a D.P.D.T. switch on hand, you can convert it into two S.P.D.T. switches by sawing through the center of the insulated strip that joins the two blades.)

Use a 5 in. or larger PM speaker with as large a magnet as possible. The larger the speaker, the higher the volume. Cut the proper size hole into the front panel for the speaker, and mount it behind window screening for protection. Two #6 dry cells are connected in series to provide a long-lasting, 3-v. power source.


With the two S.P.D.T. switches, you have a choice of three different buzzer volumes. Referring to Fig. 6, for buzzer only, speaker silent: throw blade 1 to contact B; leave blade 2 open. For medium speaker volume: throw blade 1 to contact A; leave blade 2 open. This puts the speaker voice-coil in series with the battery. Speaker volume is louder than that of the buzzer alone. For loud speaker volume: throw blade 1 to contact B and blade 2 to contact C. This puts the speaker voice-coil across the buzzer's coil.

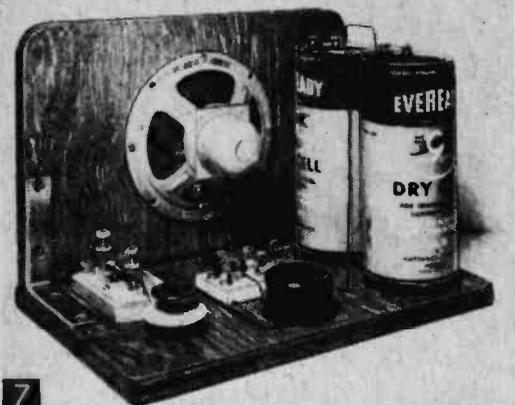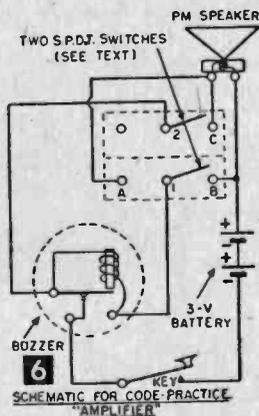

This buzzer "amplifier" is ideal for use wherever a large number of persons assemble to learn the code. No vacuum tubes are used, yet speaker volume is more than enough to fill a large hall.

# Experimenter's Test Bench

By W. F. Gephart

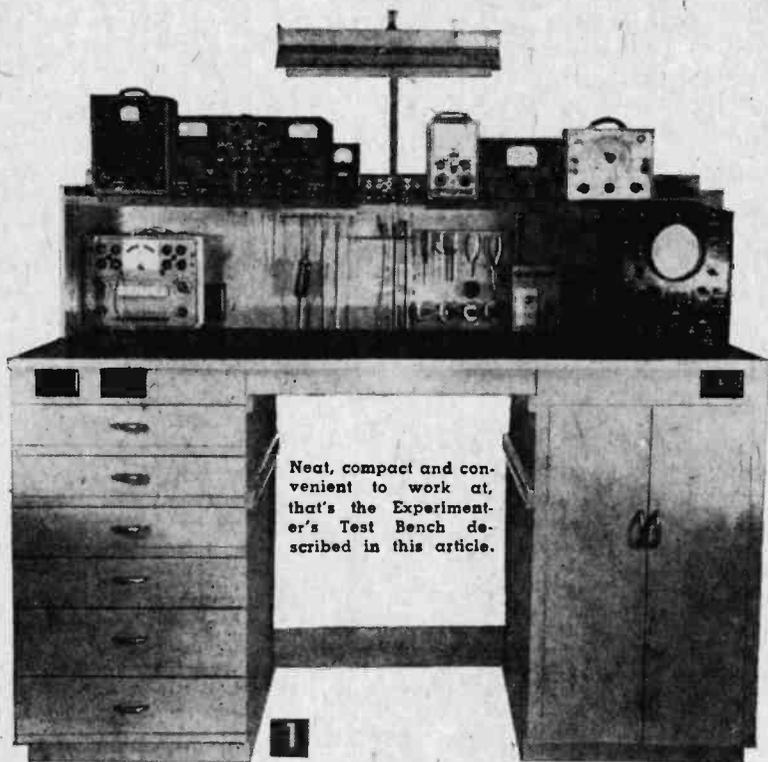

Neat, compact and convenient to work at, that's the Experimenter's Test Bench described in this article.



**R**ADIO-TV experimental work—and servicing work—can be done most easily and efficiently where there is, adequate work space, accessible test equipment and tools, good lighting, and quickly located parts and supplies. A well-designed test bench, such as that shown in Fig. 1, meets each and every one of these requirements and makes even the tough jobs a pleasure.

The bench itself is constructed of fir plywood and can be built without power tools, although if you can borrow or rent an electric hand saw such a tool will simplify the initial cutting steps. The bench includes a number of optional features which can either be included in the original construction or added later. The work area top is replaceable tempered hardboard which, when it has withstood a maximum of abuse (and its maximum is plenty), can be readily replaced. Electrical outlets are numerous and convenient, and test equipment is located—for the most part—outside of the work area, yet is also conveniently at hand. Finally, there is adequate and convenient storage space for tools and parts.

**Begin construction** by cutting the 4 x 8 ft. plywood and hardboard panels (see Materials

List, last page of this article) as shown in Figs. 2 through 8, the lengths of 1-in. stock as shown in Fig. 9. In making these cuts, arrange a guide board as shown in Fig. 10 to insure straight cuts. Clamp the guide board to the panel being cut so that when the edge of the electric hand saw runs along it, the blade will cut along the previously-marked line on the stock. In the cutting plans Figs. 2 through 7, the small black triangles indicate the side of the line along which the saw blade should run to secure the exact desired dimension, making allowance for the kerf of the saw. In cutting the 1-in. stock, use the regular rip guide with the saw. (Lines marked "xxx" and "x" on the cutting plans indicate points where the end of the cut is made with a hand saw.) In some instances, slight additional cutting will be required to fit as assembly proceeds. (These cuts can be made later with a hand saw if an electric saw is rented for initial cutting.)

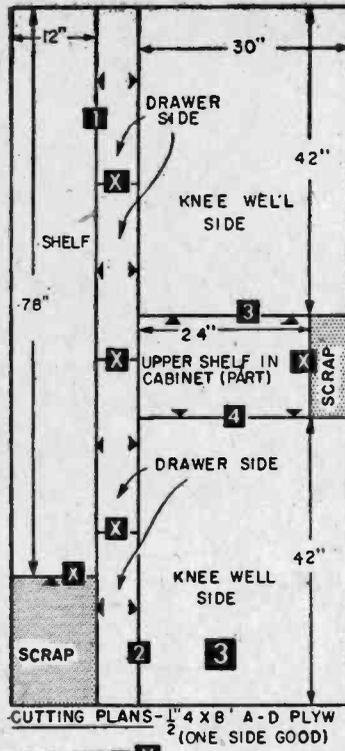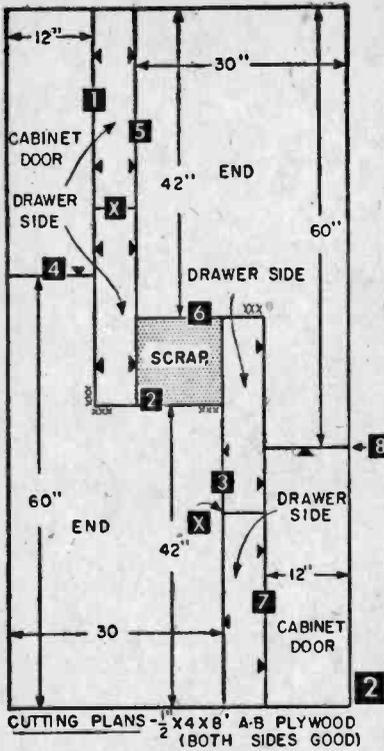
After the material is cut, fasten the side-top braces, drawer slides, and shelf supports, to the sides of the cabinets. Figure 11 illustrates how an actual drawer side, plus a scrap of hardboard, is used for spacing drawer slides. The side-top brace is nailed and glued in place and the first



After the internal members are in place, assemble the cabinets by fastening tops to sides. Cut a piece  $\frac{1}{2}$  x 12 in. out of each top to allow for the part of the side that projects above the top (see arrows in Fig. 15) and completely assemble both cabinets, including facings (as in Fig. 15) before assembling units as a bench.

To assemble as a bench, place both cabinet units face down on the floor, parallel to each other and 30 in. apart, with the bottoms even. Then glue and nail the backboard (Fig. 14) in place, following this with the back bottom brace. As the nailing is done, check alignment with a carpenter's square, and while the assembled unit is in this position, cut holes for the electrical outlets in the backboard. Next, raise the unit to its upright position and secure the shelf in place by screwing the shelf brackets to the backboard (27 in. in from each side), the shelf to them, finishing by nailing in from the ends and backboard. At this stage the unit will look as shown in Fig. 16.

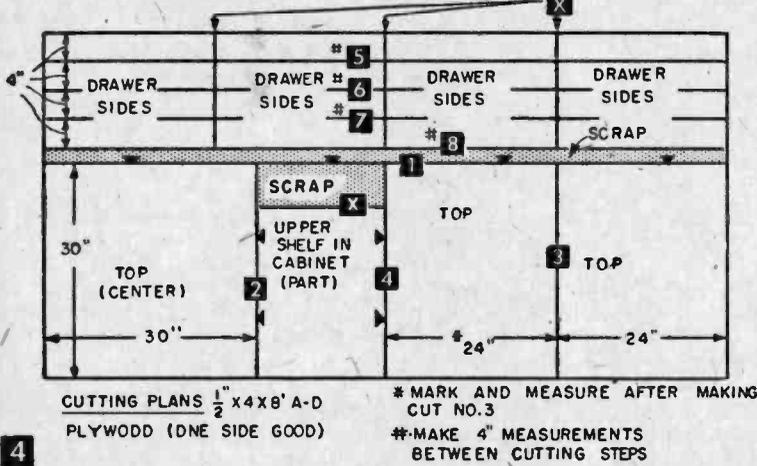Now assemble the drawers as shown in Fig. 17. If power equipment is available, the hardboard bottoms can be grooved into the sides, front and back for



4 drawer slide is then spaced as shown in Fig. 11, the strip of hardboard being a measurement of "slack," to allow the drawer to fit loosely. After the first slide is nailed and glued in place, the remaining slides are positioned in the same manner, working from top to bottom. Before the bottom slide is fastened in place, mark the bottom of it and make a cut-out for the "kick-space" at the bottom of the cabinet side.

Figures 12, 13 and 14 give overall dimensions of the two cabinets and bench assembly. (Some of the dimensions may vary slightly in actual construction, depending on fit.) In all cases, all joints and supports (drawer, shelf, etc.) are glued, using resin-type glue, as well as nailed.

support; if not, glue and nail  $\frac{3}{8}$ -in. sq. strips along the inside bottom of the front, sides and back to support the hardboard bottom. In all cases, small 1-in. metal angles should be fastened between the inside of the fronts and sides to take the strain off the nails when opening or closing the drawers.

Partitioning plans for the drawers are shown in Fig. 18. It is suggested that the top drawer be used for tools; the exact partitioning for it will depend upon your needs. The second, third and fourth drawers (A in Fig. 18) are designed for storage of small parts such as resistors, capacitors, switches, jacks, etc., and the 36-unit partitions shown are recommended. Resistors

and capacitors are grouped in each compartment (such as 1-1000 ohms, 1000-5000 ohms, etc.), and other parts, such as toggle switches, jacks, potentiometers, etc., each have their own compartments. One-hundred-and-eight compartments are available in the three drawers.

The center-to-center dimensions shown in Fig. 18 may vary slightly, depending on the exact size of the inside of the finished drawer. The exact spacing can be computed by the formulas given; the 1/4-in. plywood sections are notched as shown in Fig. 18C. In assembling the partitions, the cross partitions should be on top and all partitions nailed into from the side and back of the drawers. (It is also a good idea to glue and nail them to the top of the drawer.)


The fifth drawer (B in Fig. 18) is for storage of transformers, relays, meters, etc. The compartments are larger, but construction principles are the same as for the other drawers.

The bottom drawer (Fig. 19) is for tube storage and has a special false bottom to hold non-miniature tubes not in cartons. Built as in Fig. 19, the drawer has maximum capacity, although some users might like more space at the front

of the drawer for other tubes. Figure 20 shows a view of the partitions in one of the small drawers; Fig. 21, the interior of the tube drawer, stocked with tubes.

Additional shelves (requiring additional lumber) but adjustable shelves using metal mountings should not be used, since the shelves provide bracing for the overall unit.

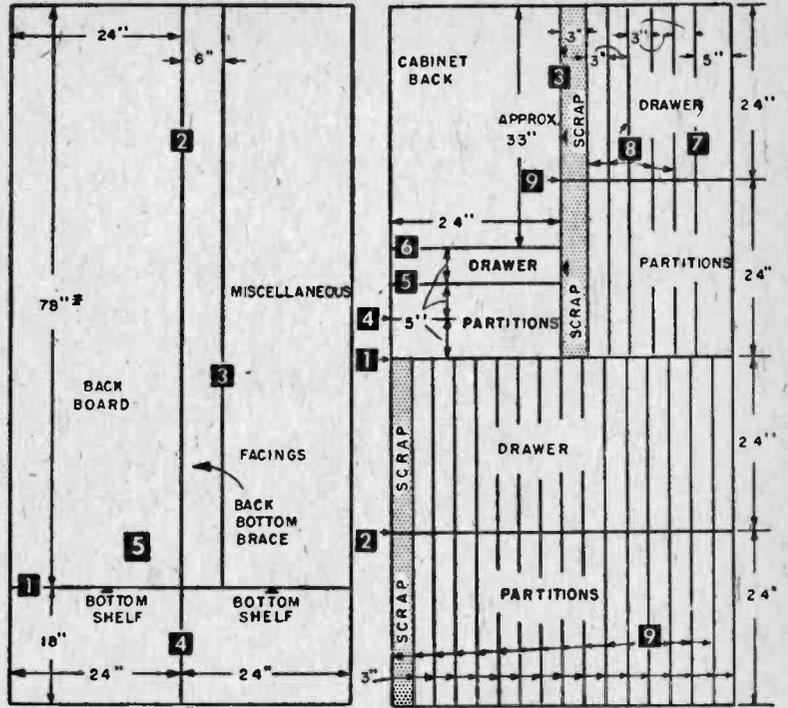The center section is designed so that it can be removed and set at a lower level when working with a large chassis. To assemble the center section, first take one of the center section frame pieces (see Fig. 9) and using it as a guide set the top supports of the center section down




CUTTING PLANS - 1/2" X 4 X 8' A-D PLYWOOD (ONE SIDE GOOD)

CUTTING PLANS - 1/4" X 4 X 8' A-D PLYWOOD (ONE SIDE GOOD)

\* EXACT LENGTH REQUIRED, ON OTHER PIECES, SAW KERF UNIMPORTANT

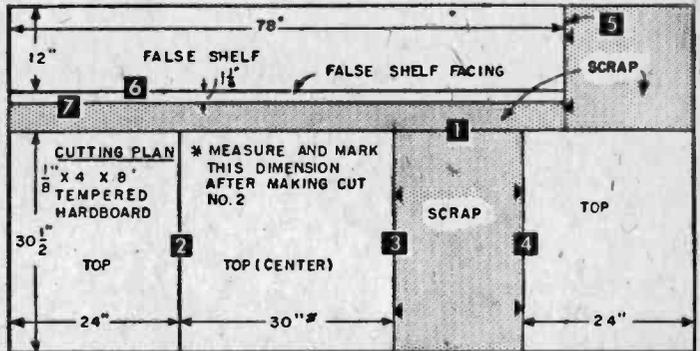
ON CUTS NUMBERS 4 THRU 7, SET GAGE TO 5" AND REPEAT CUTS ON CUTS NUMBERS 8 AND 9, SET GAGE TO 3" AND REPEAT CUTS



enough to make the top of the frame piece flush with the top of the cabinet (see Fig. 22). Glue and screw the supports to the sides of the cabinets, making sure that the screws do not go through the side of the left cabinet to interfere with the sliding drawers.

After the supports are in place, assemble the center section by nailing the four frame pieces together and nailing the top to them. The width of the section should be approximately 30 in., but cut to fit the opening between the cabinets. The depth should be 30 in. if the test lead storage plan (discussed under *Electrical Work*, below) is not to be used, 29 in. if it is to be used.

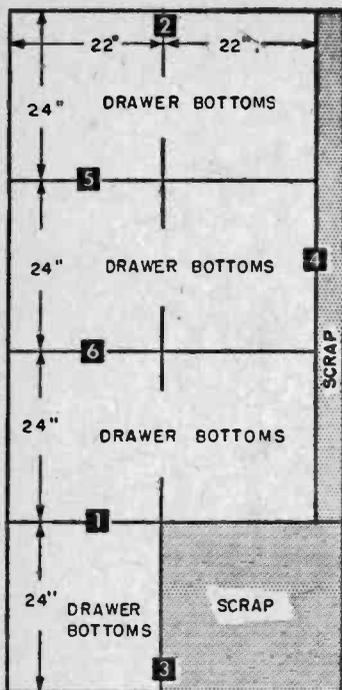
A small barrel bolt (as shown in Fig. 22) holds



**CUTTING PLAN** 1 1/8" X 4 X 8' PLAIN HARDBOARD

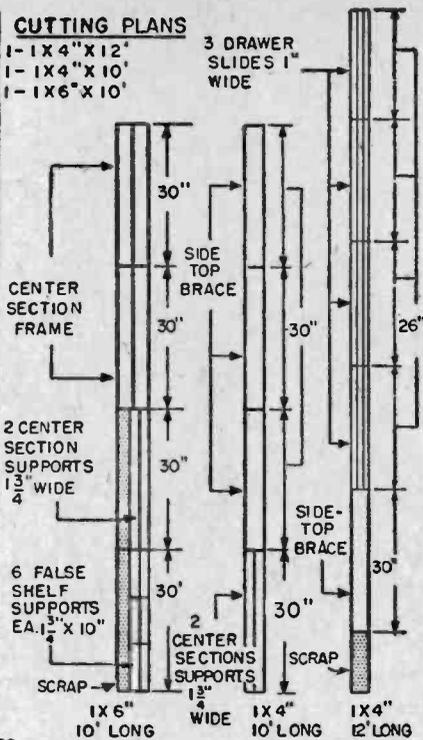**CUTTING PLANS**

- 1- 1X4" X 12'
- 1- 1X4" X 10'
- 1- 1X6" X 10'




**9**

fastened to the cabinets and center section with asphalt roofing cement, their back edges secured with a few small nails. Sides and front edges are further held in place with aluminum edging which overlaps the tops and is screwed to the front of the bench.


A vise (not shown in the photographs), may be mounted on either corner of the bench, depending upon the individual's preference, clearance around the bench, and the location of test equipment on the bench top.

If a Test Lead Concentrator (discussed under *Electrical Work*, below) is to be used, build a false shelf over the regular shelf by gluing a number of scrap pieces of 1/2-in. plywood to the top of the regular shelf, allowing space between them along the entire length of the shelf, and

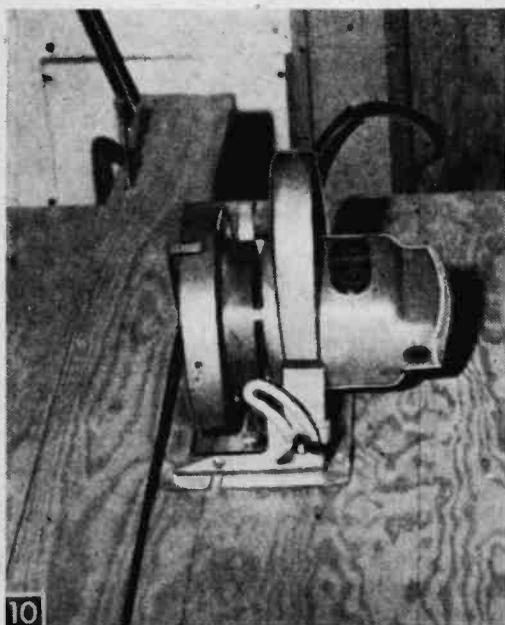**8** ALL DIMENSIONS APPROXIMATE CUT TO FIT DRAWERS



**10**

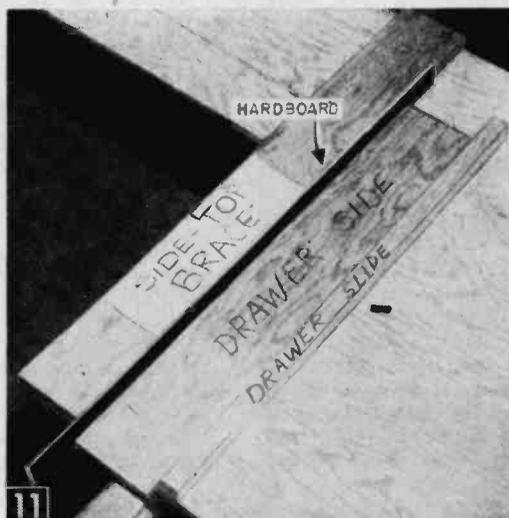

**11**


Piece of scrap hardboard spaces drawer slide.

Cutting guide board is clamped to panel with saw blade in place along marked cutting line.

the center section in place. A second one can be mounted on the bottom support if desired.

The hardboard tops of the cabinets and that of the center section may have to be planed or sanded slightly to assure an exact fit. They are

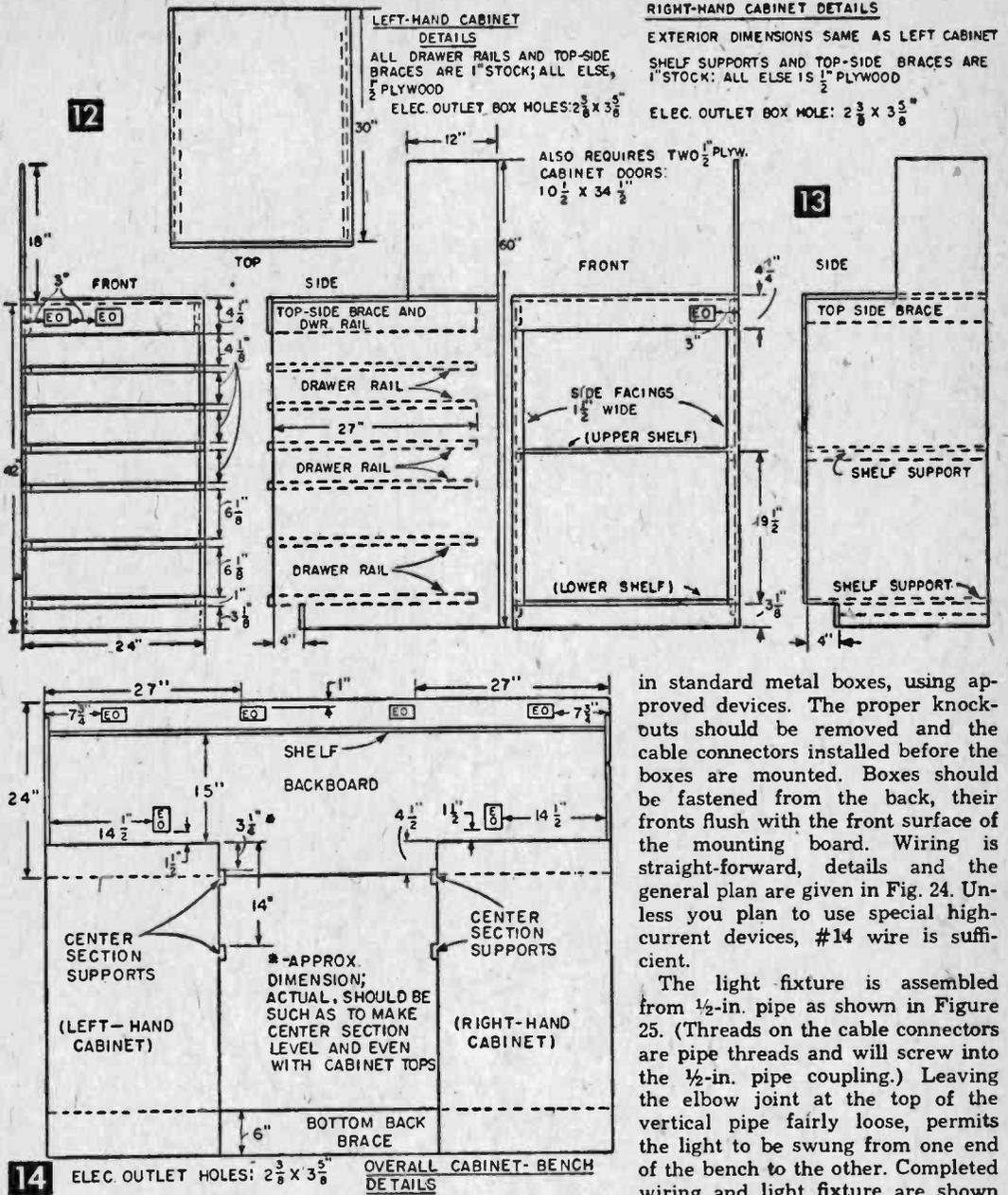at various front-to-back intervals. Then fasten a scrap piece of hardboard 1 1/8 in. wide to the front of the regular shelf, with 1/2-in. holes in it, spaced at regular intervals (between the blocks), and lay the hardboard false shelf on top of the



blocks. The exact length of the hardboard strips, and the cut-out in the center of the false shelf (for leads to the Concentrator) will depend on the size of the Concentrator panel (see below).

**Electrical Work.** Use flexible metal conduit (such as "BX" cable) for all wiring. In many localities local ordinances require it; furthermore, such wiring, with the metal covering grounded, prevents the formation of stray ac fields which often cause problems in delicate testing or experimentation.



To meet local requirements, as well as the Underwriter's Code, all power outlets should be

in standard metal boxes, using approved devices. The proper knock-outs should be removed and the cable connectors installed before the boxes are mounted. Boxes should be fastened from the back, their fronts flush with the front surface of the mounting board. Wiring is straight-forward, details and the general plan are given in Fig. 24. Unless you plan to use special high-current devices, #14 wire is sufficient.



The light fixture is assembled from  $\frac{1}{2}$ -in. pipe as shown in Figure 25. (Threads on the cable connectors are pipe threads and will screw into the  $\frac{1}{2}$ -in. pipe coupling.) Leaving the elbow joint at the top of the vertical pipe fairly loose, permits the light to be swung from one end of the bench to the other. Completed wiring and light fixture are shown in the rear view of the backboard in Fig. 26.

You can use either a fluorescent or an incandescent fixture, but normally, fluorescent fixtures are not recommended, since even the best of them sometimes emanate rf interference. A yard light fixture-reflector (see Fig. 27) provides a simple incandescent light.

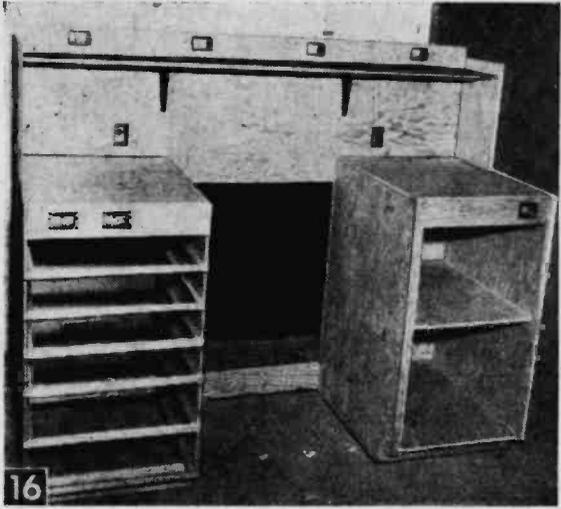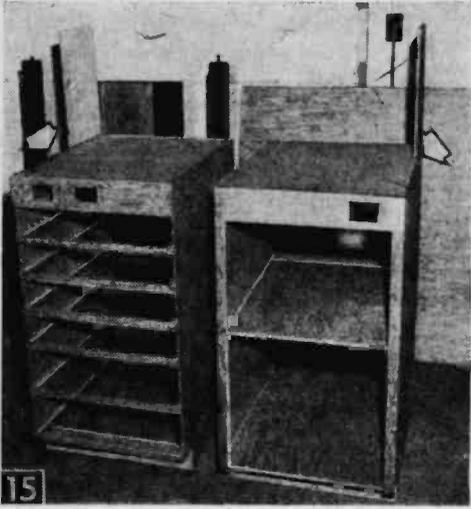**Test Lead Concentrator.** Whenever several pieces of test equipment are used, a number of different leads are required; if the equipment is spread across a shelf, long leads are sometimes needed. Thus, in many tests, when several instruments are used, the bench becomes literally





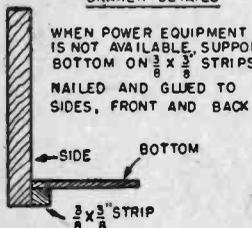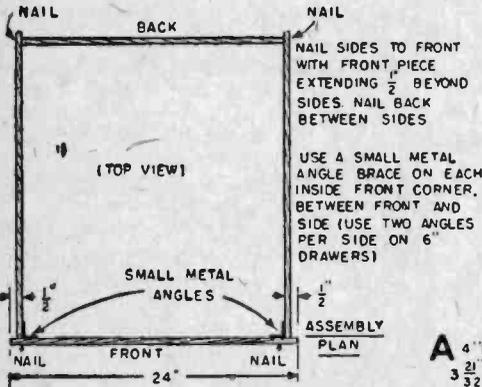Completed cabinet assemblies with facings in place and holes cut for electrical outlets. Arrows point to offset cuts in cabinet tops (Fig. 15). Cabinet-bench assembly before wiring and top installation (Fig. 15).



**17** IF DADO HEAD AND POWER EQUIPMENT IS AVAILABLE, CUT A SLOT  $\frac{3}{8}$ " WIDE AND  $\frac{3}{16}$ " DEEP ALONG SIDES, FRONT AND BACK AS SHOWN

**DRAWER PARTITIONING**

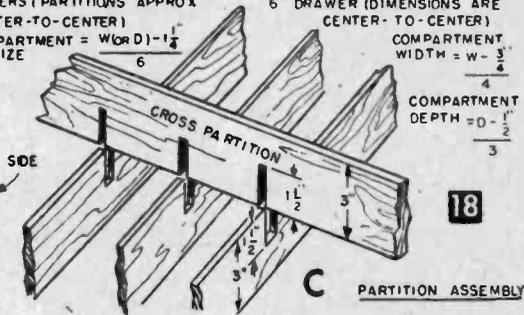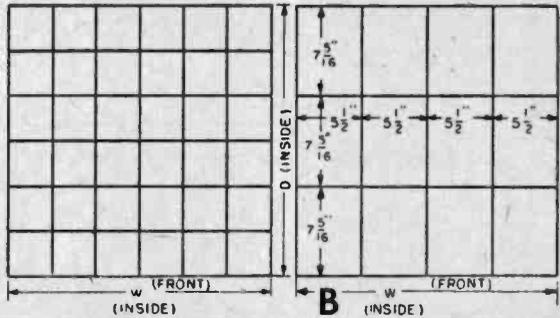



festooned with test leads.

A Test Lead Concentrator provides a central point, at the center of the bench, where the terminals of most test equipment is available. It also provides for standard type leads for all equipment, and gives you the option of connecting all equipment to a common ground, with a single lead to the unit under test. The size and number of jacks for such a unit will depend on the equipment you have, but extra jacks should be built in to allow for growth.

The leads for the units to be used with the Concentrator connect to the test equipment at

the usual jacks or terminals (thus avoiding any alteration of the equipment), go through a hole in the shelf facing (see Fig. 23) under the false shelf, and connect to the back of the Concentrator. In most cases, all except the ground lead should be shielded wire. Figure 28 shows the relation of two units (a VOM and a VTVM) to the Concentrator. Note that the VOM leads are not shielded.

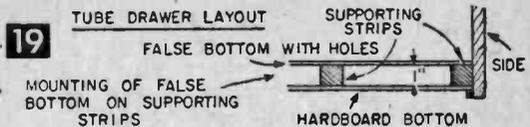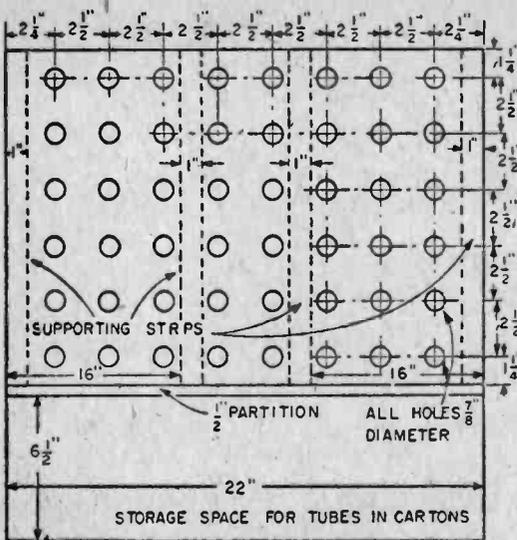At the Concentrator itself, a wire is run across the front of the panel along the bottom and connected to a central—common ground—jack (see Fig. 28). If several test instruments are being






used, and their ground is common, the individual negative terminals of the instruments (appearing on the Concentrator) are jumpered to this bottom wire and a single lead run to the equipment under test from the "Common Ground" jack. (If shelf space is at a premium, a raised shelf can be built over the Concentrator panel, and another piece of test equipment mounted on it.)


Three types of test leads are required for use with the Concentrator; a shielded lead, a regular lead (each full length), and a short, jumper lead (see Fig. 29). The shielded lead has a shielded phono plug on one end and a standard test prod (red) on the other (you'll need at least two of these). The standard lead, with a pin plug on one end and a standard test prod on the other, are used for VOM leads and ground leads (you should have a minimum of two black leads, and one red lead of this type). In both of these types of leads, the test prods used have screw-on alligator clips. The short, jumper lead has a black pin plug on one end and on the other an alligator clip for connection to the common ground wire (you'll need at least two). The shielded and regular leads should be 2 ft. long; jumper leads about 4 in. long.

**Fused Outlet.** Quite often during experimental work, fusing of the primary circuit is desired—or necessary—to protect the equipment. Since ordinary line fuses have too high capacity to offer much protection other than on a dead short, a Fused Outlet, which provides variable fusing, should be installed on your bench.




Figure 30 shows the schematic of such a unit  
Small parts drawer, 4-in. partitions.

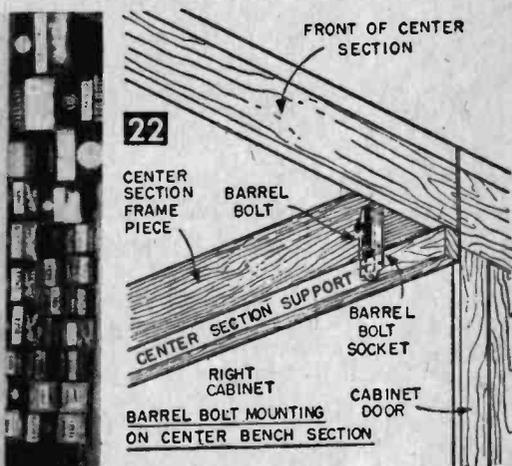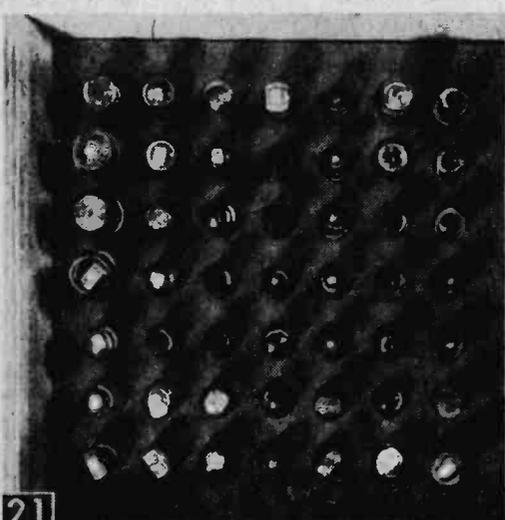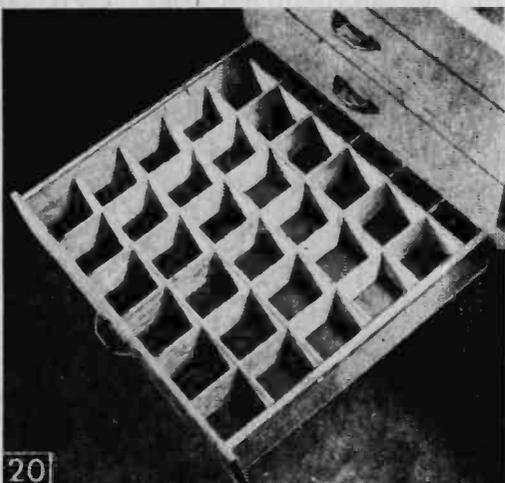


Top view of inside of tube drawer.

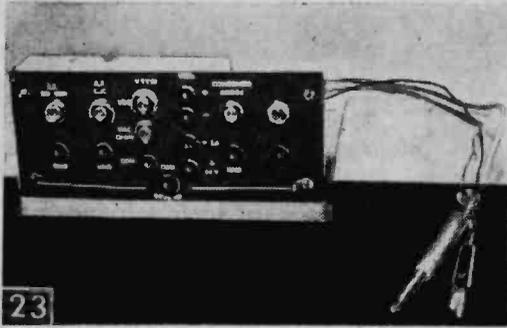

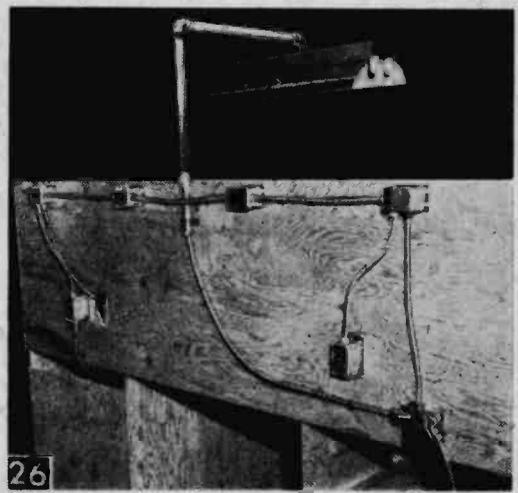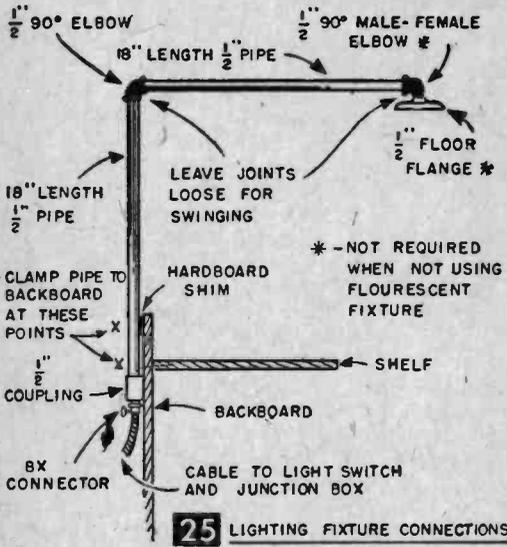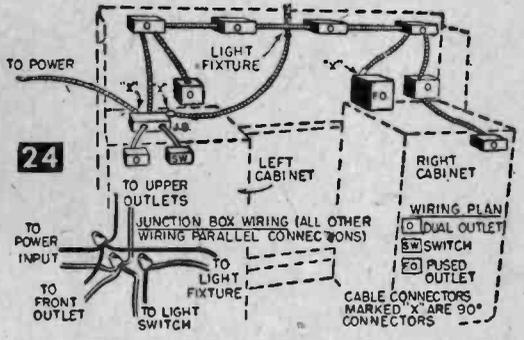
Leads for Test Lead Concentrator go through hole in front strip and run between scrap blocks to back of Concentrator.



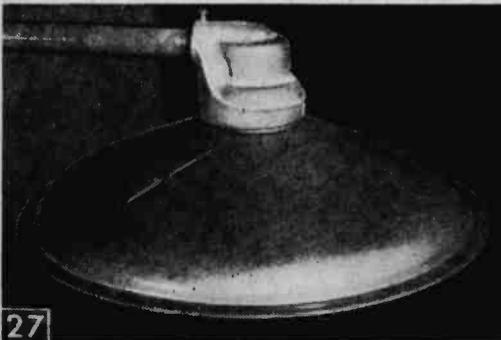Rear of backboard, showing wiring and light fixture details.



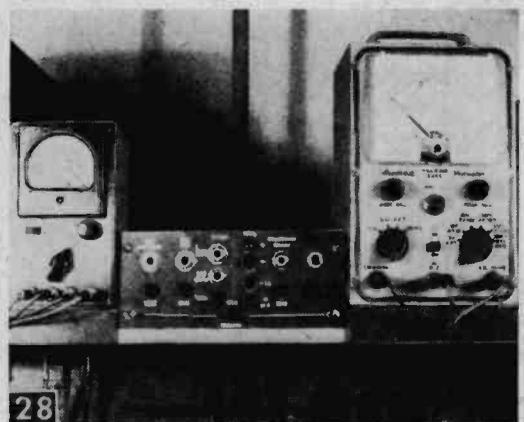
Mounting details of yard light incandescent fixture.



Test Lead Concentrator with leads for VOM and VTVM connected (above).




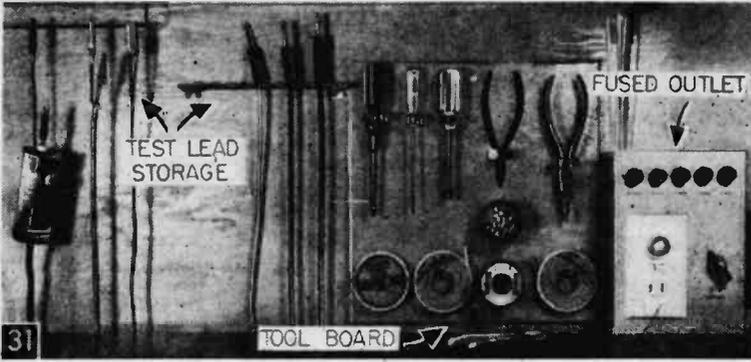Test leads for Concentrator unit: shielded lead (left); jumper lead (center); regular lead (right).



Backboard below shelf with leads, tools, and fused outlet installed.

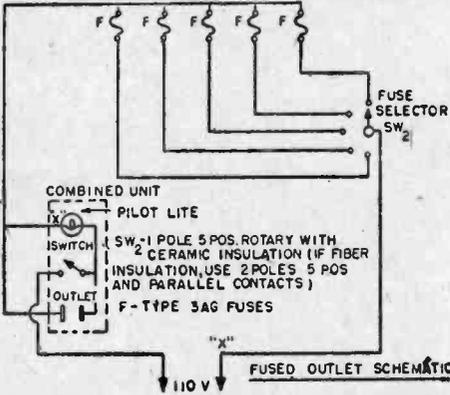ity of any fuse will be reduced by about 50 ma. While a pilot light does make it apparent when the fuse is blown, it does not permit extremely low-current fusing. If extremely low-current fusing is desired, the "X" side of the pilot light should be connected to power lead "X" rather



30

built with five fuses. By increasing the size of the switch and adding fuse holders, even greater selection would be available. The unit is designed to use 3AG fuses; these are available in sizes from 10 ma. to 8 amps.

If a pilot light (a handy reminder that the circuit is "on") is wired through the fuse, the capac-

than as shown in Fig. 30.

Enclose the unit in a metal box (to meet code and Underwriter requirements) as in Fig. 31.

**Test Lead Storage.** Figure 31 also shows a simple means of storing test leads. The center section of the bench is cut 1 in. short (29 in. instead of 30 in.), leaving a 1-in. gap at the back. You can then screw a simple wire hanger (made from coat hanger wire) to the backboard or underside of the shelf, and use this for leads terminating in a clip. Or you can notch a piece of hardboard from the front to take shield leads and mount this on the backboard.

**Tool Board.** While most tools are stored in the top drawer, the most commonly used ones can be kept handy on top of the bench. Figure 31 shows a simple tool board for such items, tools held in place with small spring utility clips, solder, soldering paste and hook-up wire held in place with long finishing nails. To mark the location of each tool, paint a black outline of the tool (as in case of diagonal cutters in Fig. 31) on the board at the appropriate place.


MATERIALS LIST—EXPERIMENTER'S TEST BENCH

No.	Description
1	1/2" x 4 x 8' A-B fir plywood (both sides good)
3	1/2" x 4 x 8' A-D fir plywood
1	1/2" x 4 x 8' A-D fir plywood
1	1/2" x 4 x 8' tempered hardboard
1	1/8" x 4 x 8' hardboard
1	1 x 4" x 12' #1 yellow pine
1	1 x 4" x 10' #1 yellow pine
1	1 x 6" x 10' #1 yellow pine
9	flush outlet boxes w/o clamps
1	surface utility box
19	#14 armored cable clamps for 1/2" knock-outs
4	#14 90° armored cable clamps for 1/2" knock-outs
1	switch
1	switch cover plate
8	dual outlets
8	dual outlet cover plates
1	blank cover for surface box
25'	2 conductor #14 armored cable (plus length req'd to reach power source)
12'	aluminum bench edging
4	1" butt hinges
8	drawer handles
2	cupboard catches
16	1 x 1" angle braces
1	small barrel bolt
2	10 x 12" shelf brackets
	Misc. nails, screws, glue, etc.
2	18" lengths 1/2" steel pipe
1	1/2" pipe coupling
1	female-female 90° 1/2" pipe elbow
1	female-male 90° 1/2" pipe elbow*
1	1/2" floor flange*
2	steel 1/2" pipe clamps
1	fixture (12" yard light or 2 tube 24" fluorescent)

\*Not required with yard light fixture

No.	Description	
<b>FUSED OUTLET</b>		
5	fuse holders for 3AG fuses	
1	1 pole, 5 pos. rotary switch	
1	interchangeable pilot light unit	
1	interchangeable switch unit	
1	interchangeable outlet unit	
1	3 opening cover plate	
1	knob	
1	aluminum box, 4 x 6 x 8" desired fuses	
<b>TEST LEAD CONCENTRATOR</b>		
6	open circuit jacks	
2	phone tip jacks (red)	
8	phone tip jacks (black)	
25'	single-conductor rubber-insulated, shield wire	
	For each shielded lead:	
1	shielded phone plug	
24"	single-conductor shielded wire	
1	test prod (red) with attachable alligator clip	
	For each regular lead:	
1	phone tip plug (black or red)	
24"	test lead wire (black or red)	
1	test prod (red or black) with attachable clip	
	For each common-to-ground jumper:	
1	tip plug (black)	
4"	test lead wire (black)	
1	alligator clip	
<b>TOOLS REQUIRED TO BUILD</b>		
Minimum:	hand drill w/drills	Additional Desired:
handsaw	2 2" C-clamps	electric handsaw
keyhole saw	hammer	electric drill
coping saw	screwdriver	screwdriver attachment for drill
hacksaw	6" square	jigsaw attachment for drill
plane	6" rule	24" carpenter's square

# THREAD THE NEEDLE!

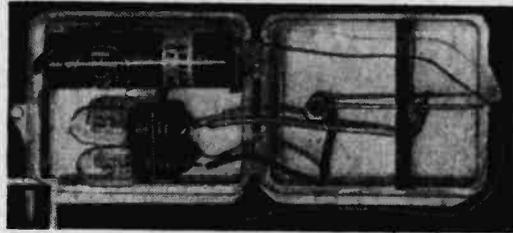

A steady hand, a little skill, and a lot of patience are all that is needed to thread the needle. Plastic case is opened when game is in play, closed for pocket storage.

**S**IMPLE enough for a two year-old to enjoy, and difficult enough to liven up any adult party, this economical little game can be constructed in 20 minutes or less. Circuit and material for *Thread the Needle* are given in Fig. 2. The object of the game is to thread the needle without letting the "thread" (No. 28 wire) touch the needle. If the needle is touched by the thread, the circuit of lamp B is completed to the battery and lamp B lights up indicating failure. If you successfully thread the needle, however, lamp A lights up. You'll find that most people will fail several times before succeeding.

CASE 1X15 X 2 1/8"

\*41  
PANEL  
LAMPS

(RCA  
V5034)  
PEN-  
LITE  
CELL

MACHINE  
SCREW  
NEEDLE

ENCLOSE IN  
PLASTIC CASE  
(LAFAYETTE MS-156)

\*28 WIRE THREAD  
**2** SCHEMATIC

Solder connections directly to the lamp bulbs, battery and needle, fastening the lamp bulbs and battery to the plastic case with Duco cement. Stick the needle through a piece of cardboard or balsa wood and cement this to one side of the case. Use Duco to hold the needle point in place. Drill the hole for the machine screw contact which mounts under the needle eye before you fasten the needle.


Use stranded wire for connections if available. It will allow you to close the case more easily when the game is not being used. You may wish to coat the bulb connected to the needle with fingernail polish or thinned red lacquer to make the game more interesting for youngsters, and you can dress the game up by painting the case if you wish.—FORREST H. FRANTZ, SR.

## Electronics "Numbers Game" by JOHN A. COMSTOCK

**H**OW familiar are you with the many numbers most frequently used in radio and electronics? This simple quiz—containing numbers commonly used in electronics—should give you the answer to that question. For the answers to the numbers questions themselves, see page 160.

- 1) Which of the following is a transistor?
  - a. 1N543
  - b. 0R2
  - c. CK705
  - d. 21AP4
- 2) Which of the following is a vacuum tube commonly used in television?
  - a. 6E5
  - b. 1X2
  - c. 0Y4
  - d. 1V
- 3) In TV, the ratio of picture width to picture height is:
  - a. 6:4
  - b. 3:6
  - c. 4:3
  - d. 2:1
- 4) The common tape recorded speeds in inches-per-second are:
  - a. 3 1/3" and 78"
  - b. 3 3/4" and 7 1/2"
  - c. 16 2/3" and 45"
  - d. 33 1/3" and 45"
- 5) The common commercial power line frequency in the United States is:
  - a. 60 c.p.s.
  - b. 110 c.p.s.
  - c. .06 kilocycles
  - d. 30 c.p.s.
- 6) What is represented by the following number designations?
  - a. 2 through 12
  - b. 13 through 83
- 7) What grade of solder is most often used in electronics work?
  - a. 40
  - b. 70
  - c. 30
  - d. 80
- 8) The field repetition rate in television is:
  - a. 30
  - b. 60
  - c. 20
  - d. 40
- 9) How many watts equal one horsepower?
  - a. 600
  - b. 1,000
  - c. 746
  - d. 95
- 10) What do the following numbers represent?
  - a. 16 2/3 rpm
  - b. 45 rpm
  - c. 33 1/3 rpm
  - d. 78 rpm
- 11) A black and white television channel is how wide?
  - a. 4.5 Megacycles
  - b. 3 Megacycles
  - c. 6 Megacycles
  - d. 12 Megacycles
- 12) How wide is a color television channel?
  - a. 3 Megacycles
  - b. 6 Megacycles
  - c. 10 Megacycles
  - d. 7 Megacycles

(Answers on page 160)

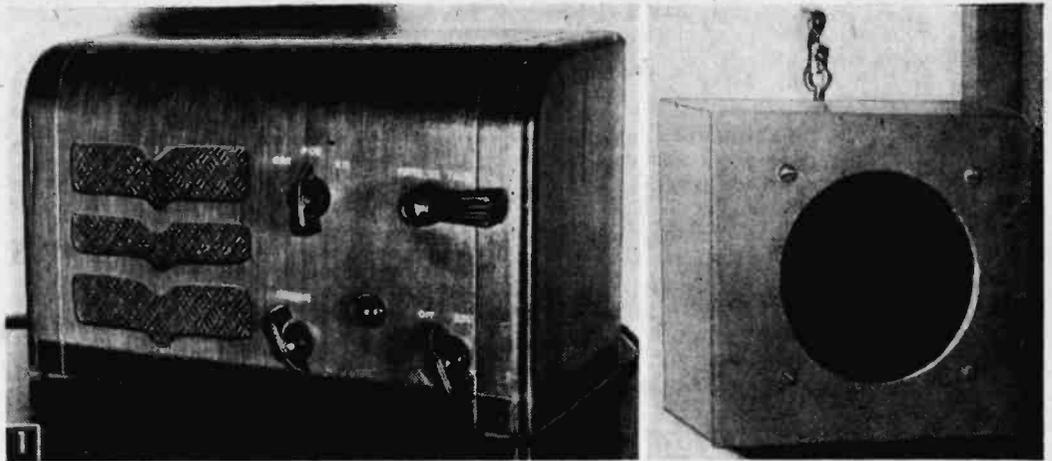

Master station (left) and substation (right) of Instant-Ready Intercom. Master station shown can select from three substation locations.

# Instant-Ready INTERCOM

By W. F. GEPHART

IN MOST home installations, intercom usage is relatively infrequent and it seems a waste of power to keep the intercom on at all times. Yet very few intercom users will tolerate the long warm-up wait required for On-Off operation of most a-c operated units. One solution, of course, is to use a battery-powered intercom; but batteries require regular replacement and—in cases of infrequent usage—they deteriorate from age as fast as they do from current drain. So here's a unit (Fig. 1) that is a-c powered, yet instantly ready for use.


This unit can be used with multiple master stations and an unlimited number of substations and the volume is sufficient for home use and other relatively quiet locations. No provision is made for talking to more than one substation at a time, however, since the output is not adequate for multiple speaker operation. Normally kept Off, the unit is ready for use approximately 2 seconds

after the current has been turned on.

The master station, Fig. 2 (or stations, Fig. 3) is a simple, two-stage audio amplifier, using battery-type tubes (see Materials list) powered by a selenium rectifier circuit supplying both plate and filament voltages. By running the output tube (V<sub>2</sub>, Fig. 2) at maximum ratings, the unit has an output of close to ½ watt. (Since all of this output is usually needed—and is never objectionable—a 1 megohm fixed resistance can be substituted for potentiometer R<sub>3</sub> in Fig. 2. If you make this change, connect the grid of V<sub>2</sub> between C<sub>2</sub> and the fixed resistance.)

The Talk-Listen Switch (SW1) and the Selector Switch (SW2) are conventional types, except that the Talk-Listen Switch should be spring-loaded to hold in the Listen position (see Fig. 6). The number of poles required for the Selector Switch depends upon the number of stations you want in your installation.

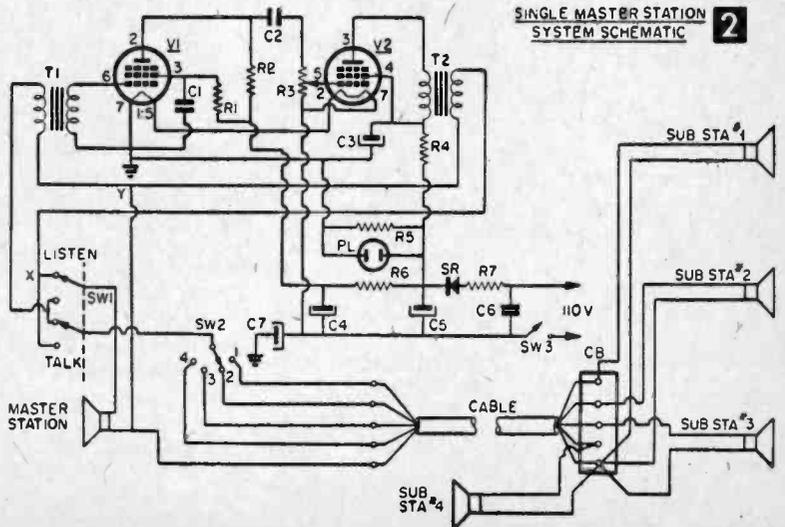When multiple master stations are used (Fig. 3), the basic amplifier and power supply circuit



SINGLE MASTER STATION SYSTEM SCHEMATIC 2


shown in Fig. 2 is used for each master station. The switching circuits and interconnections are slightly different, however, as shown in the example in Fig. 3. A three-pole, double-throw switch (SW3A) is used as an On-Off switch instead of a SPST switch. Switch 3A acts as a power switch, and switches the station to be talked from from substation use to master station use when the power is turned On. In Fig. 3 the master unit on the left is On and the switching circuit connections are the same as those shown in Figure 2. The master unit on the right of Figure 3 is Off—that is, it is connected as a substation unit. If more than one master station is turned on at the same time, there will be a feedback squawk, but no damage will be done to any circuit component.

For single master station unit construction, wire as shown in Figs. 2 and 5; chassis layout is shown in Fig. 4. No particular care need be taken in assembling the master station units, except that the selenium rectifier and other a-

#### MATERIALS LIST—INSTANT-READY INTERCOM

Chassis	2 x 5 x 7" (Bud CB 629)
R1	—1 meg. 1/2 watt
R2	—27 meg. 1/2 watt
R3	—1 meg potentiometer (or fixed resistance; see text)
R4	—2400 ohm, 1 watt
R5	—5000 ohm, 10 watt, wire-wound
R6	—200 ohm, 2 watt, wire-wound
R7	—27 ohm, 1/2 watt
C1	—02 mf, 200 v.
C2	—01 mf, 200 v.
C3	—30 mf, 200 v.
C4, C5	—50 mf, 200 v.
C6	—01 mf, 600 v.
C7	—25 mf, 25 v.
T1	—intercom input transformer (Stancor A-4744)
T2	—8000 ohm to speaker, output transformer (Stancor A-3329)
SW1	—4PDT spring return switch (Centralab 1451)
SW2	—rotary switch (Mallory type 3200J—spring load, see text)
SW3	—SPST toggle or rotary
SW3A	—3PDT switch (rotary: Centralab 1450, Mallory 3242J) (toggle: Cutler-Hammer 7613-K2 or 7612-K2)

Speakers	
V1	—1U4 tube
V2	—3Q5 tube
SR	—75 ma selenium rectifier
PL	—neon pilot assembly (Drake 105)
CB	—connector block (see text: Jones type 140 or 141)
Master Cabinet	5 1/4 x 6 1/8 x 10 3/16" (available from Allied Radio, catalog #98930)
Substation Cabinet	4 x 7 x 7" (ICA 3988)

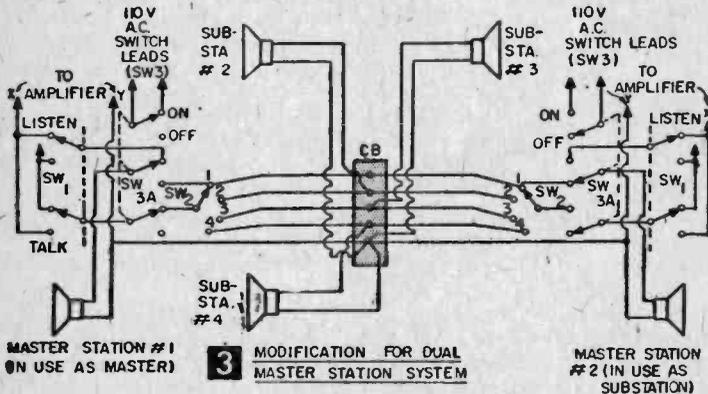


components and leads should be grouped together and isolated as much as possible from the audio frequency wiring and components. This will reduce the possibility of a-c hum. If multiple master units are used, and a rotary switch with widely-spaced wafers is available for SW3A, hum can be reduced even further, but even with the switch specified and rather haphazard wiring, the unit has less a-c hum than conventional a-c models.

Be sure to keep all leads in the primary of the input transformer (T1) and the secondary of the output transformer (T2) isolated from power (a-c or d-c) leads or grounds. This is particularly important if multiple master station units are used, since such audio frequency leads are common between units and direct connection is made to the a-c line in the power supply.

To dress them up, master units can be built into small radio cabinets (Figure 1); they can also be built into home-made boxes, however. The same is true of the substations which can be installed in a commercially available box (see Materials List), or in a 3 x 5-in. box made of 1/4-in. plywood and Masonite. If a substation is to be located on a porch or other outdoor location, it should be shielded from the weather by being placed on the porch ceiling or under an eave. If a weatherproof speaker is not used, the speaker should be mounted face downward to reduce the chance of rubbing in the case of the cone warping due to dampness.

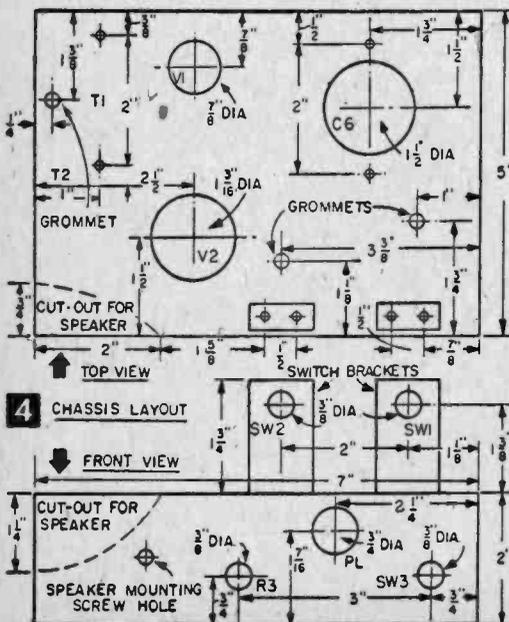In some cases it might be desirable to have one or more master stations "portable," that is, capable of being used at more than one location. By using plugs and jacks on the intercom cable,





# TEST BELL


## For the Bench

By

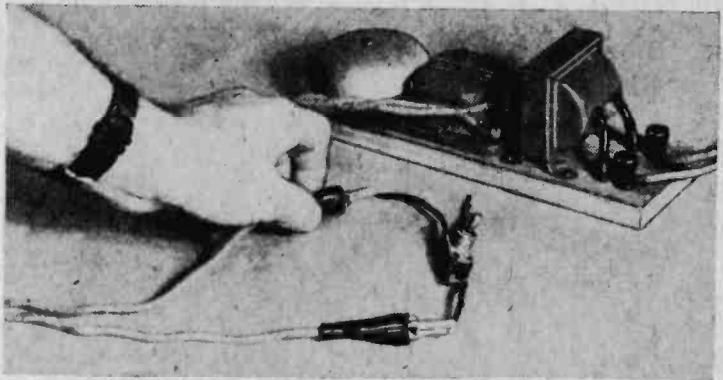
H. P. STRAND

EVERY electrical repair bench should have a test bell for testing continuity of low resistance circuits. Such a bell unit is illustrated in Fig. 1 and the drawings; here a common door bell and a bell transformer have been mounted neatly on a wooden base board. Leads which are completely equipped with alligator clips and insulators are connected in series with the bell and transformer to use as test leads, and insulated binding posts are provided for attachment of the 115 volt line. This piece takes but little room on the bench and is always handy when wanted.


As an example of the usefulness of this tester, an S.P.D.T. toggle switch is being tested in Fig. 1, to determine the common lead, which is not marked. The bell will usually ring through a resistance up to about 20 ohms, depending on the individual bell and voltage of transformer. It is thus possible to use it for testing continuity of coils of low resistance, where it is necessary to pick out the start and finish, in cases where more than one coil or winding is incorporated in the coil unit. In fact, there are countless uses for a handy bell of this sort to the home mechanic.



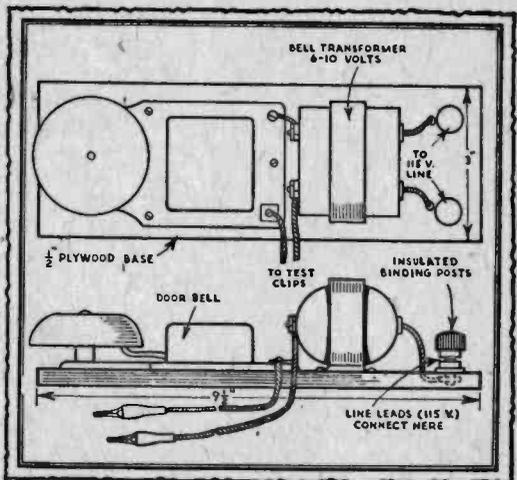This handy door-bell and transformer unit is used for a variety of low resistance testing. In photo above it is used to find the common terminal of an S.P.D.T. switch. Drawing below shows how hookup is made.



## Mystery Coil

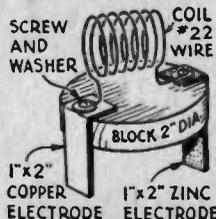

A EUROPEAN electrical experimenter, de la Rive, performed this interesting experiment many years ago. What the device amounts to is a floating cell carrying a coil. The cell generates a current which flows through the coil, the current in turn setting up a magnetic field about the coil. If an ordinary horseshoe or bar magnet is brought near the floating coil, either the coil will be attracted or repelled by it.

Such equipment may be kept on hand for demonstration purposes over a long period if the floating cell is removed from the acidulated water after use and rinsed off with clean water. The cell proper is a circular piece or plug of wood soaked in molten paraffin and carrying two electrodes and the coil of No. 22 copper wire.

The 1 x 2 in. electrodes are fastened to the sides of the plug by means of a small wood screw used also to hold the ends of the copper helix. One electrode is cut from sheet zinc and the other is cut from sheet copper. The solution for the cell is made up of 1 qt. water to 1/2 oz. of sulphuric acid. Between demonstrations of the device, keep the solution in a stoppered glass bottle.— R. F. YATES.

# Crystal Headset



**N**OW you can put together a crystal headset for the price you would ordinarily pay for a cheap pair of magnetic earphones! This crystal headset has much to recommend it. Its sensitivity, frequency range, and clarity of reproduction are superior to magnetic type earphones. Also, it weighs less than two ounces, is easy to assemble, and its "stethoscope" style (Fig. 1) eliminates headband pressure.

The high impedance and high sensitivity of this crystal headset make it ideal for use with crystal radios, but with proper connections it can be used in any earphone application. Parts for making this headset will cost about \$3.25.



Take a 24 in. length of fence wire and make a  $1\frac{1}{2}$ -turn loop in the center by winding the wire around a  $\frac{3}{4}$  in. wood dowel. Form the V with curved sides as

in Fig. 2 and then clip off the ends of the wires so the V measures about 7 in. from the bottom of the loop to the ends of the wires. Space between the two free ends of the V should be about  $6\frac{1}{2}$  in.

Next hammer the two ends of the V flat (Fig. 3) and drill and countersink holes in them, so the earpieces can be held to the ends of the V by their own screws. You may find slight variations in the earpiece measurements and the lengths of the rear screws. If screw isn't long enough to do a good job, file back of plastic disc flat to compensate for short screw (Fig. 3 inset) or use slightly longer screws of the same diameter and threads. But be sure ends of screws don't extend into the earpieces far enough to touch delicate crystal elements inside. These screws and plastic discs on the backs of the earpieces permit easy replacement of worn connecting cords. Be sure cord connecting clips are in their proper places when you put parts together again.


**Wiring.** Leave a little slack in the connecting cords where they enter the earpieces, and then tape the cords to the V using a bit of Scotch transparent tape every inch or so. Connect the two earpieces in parallel just below the loop in the V. Since the cords supplied with the earpieces are short, the writer spliced on a 4-foot length of hearing-aid cord while connecting the earpieces in parallel.

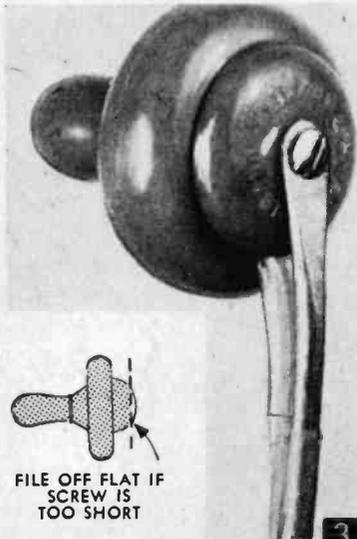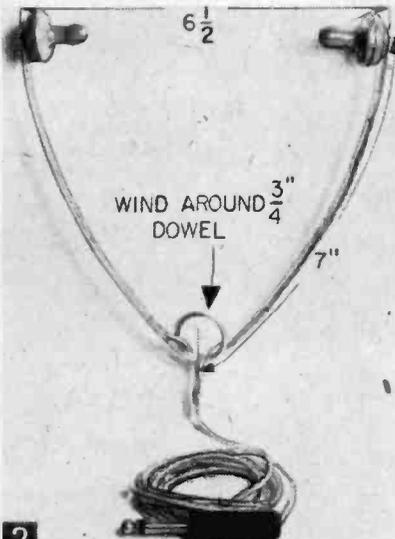Before soldering and taping the splices, be sure the two earpieces are connected in phase, that is, the diaphragm of each earpiece should move in and out together. You can determine this by tracing the cords leads, or by reversing



2

3

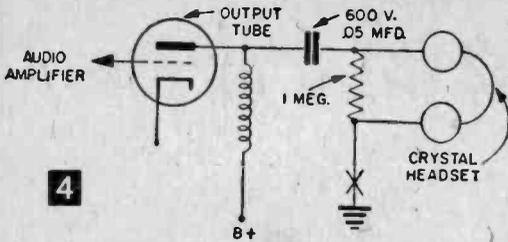

4

**MATERIALS LIST—CRYSTAL HEADSET**

- 24" length of 3/32" dia. galvanized iron electric-fence wire
- Two crystal earpieces (Lafayette Radio MS-111. \$1.49 each net)
- Small roll 1/2 to 1" wide Scotch transparent tape
- Two phone cord tips, and/or one standard or midget phone plug
- Optional: 48" length of plastic-covered hearing-aid cord

the connections to one earpiece to see when the reproduction sounds the most natural. A pair of phone cord tips or a midget phone plug soldered to the free ends of the cord will complete the headset.


For best results, bend the V so the earpieces are at the correct angle to pipe the sound directly into the ear passages. Bass response is best when the ear inserts fit into the ear passages firmly making a good acoustical seal. Remember that crystal phones should not be subjected to dc voltages, or to temperatures over 130°F.

When using this crystal headset with a crystal radio, connect them as you would an ordinary pair of magnetic earphones. Figure 4 shows how these crystal earphones can be connected to

output stage of a vacuum tube, .05 mfd. blocking capacitor, high-grade unit. The 1 megohm resistor and the earphones protects the earphone in case of blocking capacitor. The 600-volt, .05 mfd. blocking capacitor is a high-grade unit. The 1 megohm resistor and the earphones protects the earphone in case of blocking capacitor. **ART TRAUFFER.**

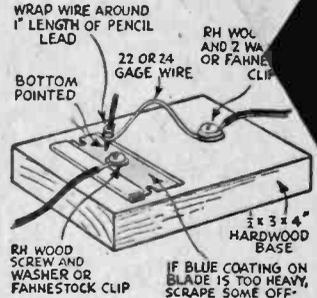**Improved Razor-Blade Detector**

• Here is a more rugged version of the familiar fox-hole, razor-blade "crystal" detector. The original was a piece of pencil lead bridged across the edges of two razor-blades and sometimes used by G.I.'s in fox-



holes to pick up local broadcasting stations. This was fairly sensitive, but it was very difficult to hold an adjustment, as the least vibration or jar caused the lead to rock and roll on the blade edges, resulting in erratic and noisy reception. For the arrangement shown, blue steel single edge or double edge blades (such as Pal razors) seem to be the most sensitive, but many other blades also have sensitive spots on them. Use with a conventional circuit and a good antenna and ground.—**ARTHUR TRAUFFER.**

**No Wiring Kinks in Super-Het Kit**



IN ONE evening an amateur can assemble the 6-transistor super-het kit sold by Lafayette Radio, Dept. HPS, 165-08 Liberty Ave., Jamaica 33, N. Y., under their number KT 119. Lining up is simplified by IF transformers which are pre-set at 455 kc. and require little adjustment. Adjusting the tuning capacitor trimmers and the oscillator coil may be done by ear or with a signal generator.

Powered by a 9-v. battery, the set has a built-in speaker for portability but it will operate a separate 8-in. speaker with room-wide volume. The kit costs \$33.50, the cowhide case \$2.95 extra.

Nine-volt battery gives room-wide volume.



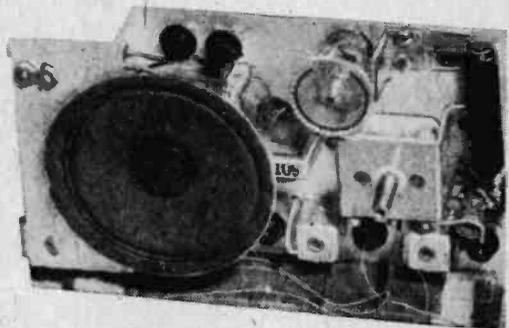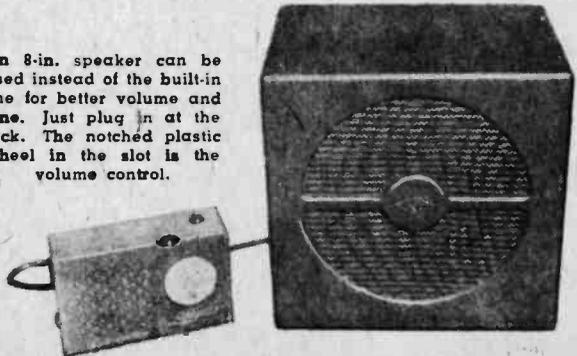An 8-in. speaker can be used instead of the built-in one for better volume and tone. Just plug in at the jack. The notched plastic wheel in the slot is the volume control.



Here the wired chassis is ready for installation in the case. A flat ferrite core antenna is shown fitted in a plastic holder at the bottom.

# Crystal Microphone

By ARTHUR TRAUFFER




A simple, high-impedance mike—for ham rig use or with tape or disc recorder—that will cost you less than \$3 to build

**T**HIS simple little crystal "mike" will give good service with your ham rig, P.A. system, tape or disc recorder, or wherever an expensive microphone is not required. It is, of course, not the most rugged mike you can buy, but you can't expect everything of a project that should cost you less than \$3 to build.

Figure 3 shows you what goes into this project. Note that the rubber foot pedal base is hollow inside making for easy assembly and wiring. It also won't scratch polished furniture surfaces, and the soft rubber cushions the mike against thumps and bumps. A short length of metal spring protects the cable from continual bending where it enters the base.


The small crystal earphone used for the mike unit has high sensitivity and fidelity considering the low price (about \$1.49 net). This is not too surprising, since any transducer that gives good results as an earphone will also give good results as a microphone.

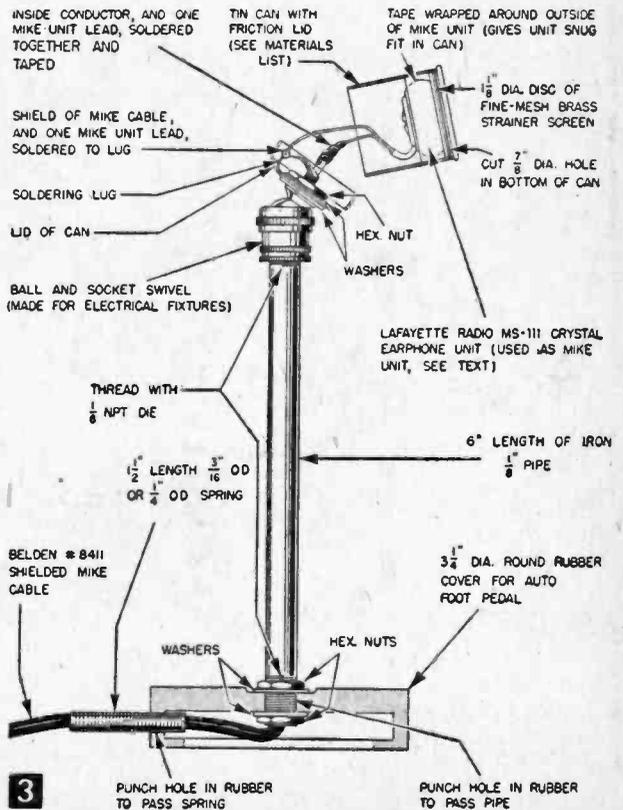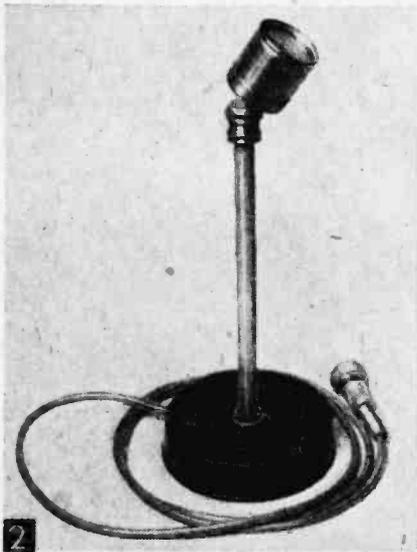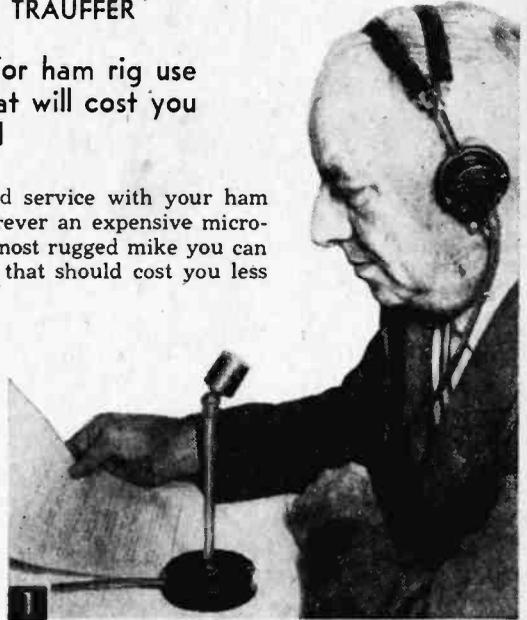In building this mike, start by enlarging the opening in the crystal earphone, to give it greater efficiency as a mike unit. Pry off the front cover of the earphone unit with a knife blade or single-edge razor blade, but be careful not to touch the thin diaphragm covering the crystal unit as it is easily damaged (Fig. 4). Now twist the ear-plug off the cover, and enlarge the opening





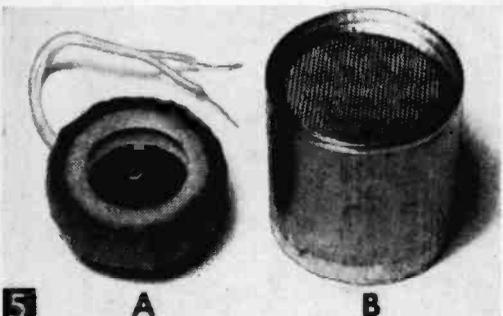(A) Crystal earphone unit as it comes from dealer—  
(B) After front cover has been removed and opening enlarged with rat-tail file. Cover rim is then snapped back on, without injury to diaphragm.



Note how strainer screen has been cemented to inside edges of hole cut in bottom of can (B). Mike unit is then taped (A) for a snug fit.

in the cover to a diameter of about  $\frac{5}{8}$  inch, using a rat-tail file. Then snap cover rim back on the earphone again.


For the mike housing, I used a No. 1-size "Smooth-On" Iron Cement can; these are about  $1\frac{3}{8}$  inches in diameter and have a nice-looking friction lid. The can was cut off to a length of about  $1\frac{1}{2}$  inches using a fine-tooth thin-blade hacksaw. The rough edge was then smoothed with emery paper.

A hole was chopped out of the bottom center of the can and carefully enlarged to a diameter of about  $\frac{7}{8}$  inch, using a rat-tail file. The rough edge was smoothed, using a knife blade and emery paper wrapped around a wood dowel.

A  $1\frac{1}{2}$  inch diameter disc was cut from fine-mesh brass strainer screen and cemented to the inside bottom of the



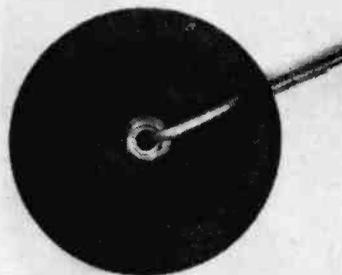Large soldering lug is clamped under hex nut holding can lid to top end of swivel. Shield of cable is unwoven and twisted together to form wire (A).



Bottom view of mike base showing how cable passes through protecting spring and up into stand tube.

#### MATERIALS LIST—CRYSTAL MICROPHONE

No.	Description
1	tin can $1\frac{3}{8}$ " dia., with friction lid (The #1-size "Smooth-On" Iron Cement can is ideal)
1	$1\frac{1}{2}$ x $1\frac{1}{2}$ " square of fine-mesh brass strainer screen
1	ball-&-socket swivel (made for electrical fixtures) with $\frac{1}{8}$ NPT threads on both ends
1	6" length of $\frac{1}{8}$ iron pipe with $\frac{1}{8}$ NPT threads on both ends
1	round rubber cover for automobile foot pedal ( $3\frac{1}{4}$ " dia. and $\frac{3}{4}$ " high). (Western Auto Stores, 25¢ pair)
1	$1\frac{1}{2}$ " length of $\frac{3}{16}$ or $\frac{1}{4}$ " OD steel spring (a piece of dime store kitchen-window-curtain spring was used here)
1	Amphenol 75-MC1F female microphone cable connector
4	$\frac{5}{8}$ " dia. plated brass washers with $\frac{3}{8}$ " holes
3	brass hexagon locknuts with $\frac{1}{8}$ NPT threads
1	soldering lug with $\frac{3}{8}$ " hole
1	small crystal earphone unit, used as mike unit (Lafayette Radio, Dept. 106, 165-08 Liberty Ave., Jamaica 33, N. Y., Catalog MS-111, \$1.49 net. Or Radio Shack Corp., Dept. M106, 167 Washington St., Boston 8, Mass., Catalog R-9021)
	Length of Belden No. 8411 shielded microphone cable

can with Duco cement (Fig. 5). The earphone cord was clipped off leaving about  $2\frac{1}{2}$  inches on the unit, and  $\frac{3}{8}$ -inch wide tape was wrapped around the outside of the unit (Fig. 5), so that it would make a snug fit.

Figures 3 and 6 show how the can lid is joined to the top of the ball-and-socket swivel using a  $\frac{1}{8}$  NPT brass hex nut with a large soldering lug between the nut and the inside of the lid. Drill (or drill and file) a  $\frac{3}{8}$ -inch diameter hole in the center of the can lid to pass the male threads on the top of the ball-and-socket swivel. Scrape off the coating around the hole on the inside of the can lid so the soldering lug makes good contact.

Using a  $\frac{1}{8}$ -pipe (NPT) die, put a few threads on one end of a 6 inch length of  $\frac{1}{8}$ -pipe, and twist the end of the pipe into the female threads on the bottom of the ball-and-socket swivel. The other end of the pipe is threaded for a length of about  $\frac{5}{8}$  inch. Punch a hole in the center of a  $3\frac{1}{4}$  inches diameter round rubber automobile foot pedal cover; and enlarge the hole to  $\frac{3}{8}$ -inch diameter using a rat-tail file.

Fasten the  $\frac{1}{8}$ -pipe upright to the rubber base using two large washers and two brass  $\frac{1}{8}$  NPT hex nuts (Figs. 3 and 7). Punch a hole of the required size in one side of the rubber base, and insert a  $1\frac{1}{2}$ -inch length of  $\frac{3}{16}$  or  $\frac{1}{4}$ -inch

OD steel spring into the hole (Fig. 7). The microphone is now ready to be wired up and the can closed.

Pass one end of a length of Belden #8411 mike cable through the steel spring and up into the  $\frac{1}{2}$ -pipe upright and through the swivel (Figs. 3 and 6). Strip the outside plastic insulation off the end of the cable for a length of about 1 inch. Using a fairly large size sewing needle, unweave the shielding covering on the cable for a length of about  $\frac{3}{4}$  inch, by picking one strand at a time; then twist the loosened strands together to form one twisted wire (A in Fig. 6).

Remove the insulation on the center conductor of the cable for a length of about  $\frac{1}{4}$  inch. Now solder the cable shield and one mike unit lead to the soldering lug. Solder and tape the remaining mike unit lead to the center conductor of the cable, as in Fig. 3.

Now close the can, making sure that the bottom of the can makes good electrical contact with the friction lid so the can acts as an efficient shield for the mike unit to prevent hum pickup. Connect an Amphenol 75-MC1F cable connector to the free end of the cable. Remove cable-protecting spring from 75-MC1F. Strip outside in-

sulation from end of cable and prepare shielding conductor as explained above. Strip insulation from end of inside conductor. Solder shield to inside end of spring. Push spring and cable into 75-MC1F, letting inside conductor pass through eye in center of 75-MC1F to hold spring securely. This takes some practice.

**Uses for Crystal Mike.** Since the crystal earphone unit used here has very high impedance, you can connect this mike directly into the input grid circuit of an amplifier without using an impedance-matching transformer. Of course, any other good small crystal earphone unit or crystal mike unit can be used instead of the one we used. You could also use a small high-impedance magnetic earphone or mike unit, but if you use a low-impedance magnetic or dynamic unit you will have to use an impedance-matching transformer for best results.


If desired, all the metal parts except the screen can be given a coat of enamel of the desired color. Or if you prefer a nice chrome job, you can buy  $\frac{1}{2}$ -pipe and ball-and-socket swivels already chrome-plated. Then you only need to take the can and screen to a plating shop for chrome plating!

## Auto Radio Vibrator Tester

**V**IBRATORS are found in almost all auto radios; they convert the low voltage d-c current supplied by the auto's battery to alternating current (a-c) which is then put through a step-up transformer to supply the high voltage which is then rectified for the d-c plate voltage of the radio's vacuum tubes. When your auto radio behaves in an erratic manner, or fails to work at all, a defective vibrator is the usual cause of the trouble.

The vibrator is enclosed in an aluminum can; it has either three or four pins on the bottom which press into a socket (like a vacuum tube). To remove the vibrator, remove the back cover of the radio and pull out this aluminum can. The vibrator has different-sized base pins, so that it can only be replaced in one way—the correct way.

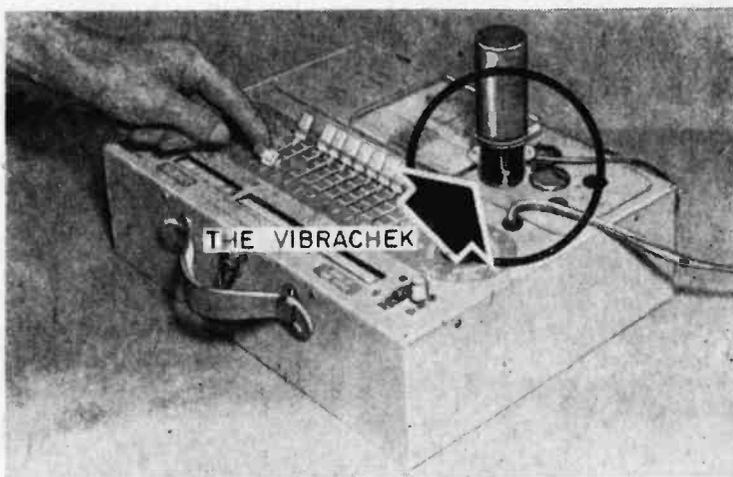Until recently, the usual way to determine whether a vibrator was good or defective was to substitute a new vibrator for the old. But now, a vibrator tester is on the market, sold by Lafayette Radio for \$2.95, called the *Vibrachek*. It has base pins which fit in the octal sockets of



tube testers and it comes in two models, the V-3 for 12 v. 3-prong vibrators, the V-4 for 6 v. and 12 v. 4-prong vibrators.

If the vibrator under test is good, two small lamps on the side of the *Vibrachek* will light with approximately equal brilliance and will flicker at about the same rates. A defective vibrator will cause one lamp to light much brighter than the other in some cases, in others only one lamp will light, in still others neither lamp will light.—H. P. S.

# Quick-Repair of Your Car Radio's

## VIBRATOR

**T**HE number one cause of car radio troubles is the failure of the vibrator in the radio's power pack. The vibrator converts the low d-c voltage supplied by the car's storage battery into square-wave d-c pulses which can be fed into the primary of a step-up power transformer, rectified in the secondary circuit and used as B+ in the car's radio.

So great a troublemaker is the vibrator, that recently two leading car radio manufacturers introduced sets which eliminate the need for a vibrator. Unfortunately, only a handful of these new, vibrator-less sets are in use. The great majority of car radios, meanwhile, must continue to rely on vibrators—and vibrators are not overly reliable.


A vibrator consists of an electromagnetic coil and a two-contact reed (or armature) which vibrates between two stationary contacts (Figs. 1 and 2). Power from the battery is delivered to the vibrator alternately through the upper and lower halves of the primary of the step-up transformer in the power pack. When you turn on your car radio, the vibrator's electromagnetic coil is energized and the reed is pulled toward stationary contact B. The instant the reed contact touches stationary contact B, the electromagnetic coil is short-circuited and thus

With contacts renewed, replace the sponge rubber cup and tape in place. Aluminum foil shielding completes the job.



Vibrators list-price in electronics catalogs starting at \$2.50 and ranging upward to over \$9. With an auto ignition point file, you can renew a vibrator's contacts and save that hefty replacement cost.

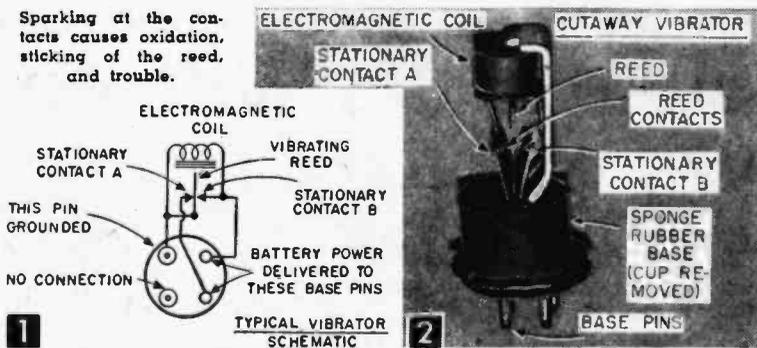Sparking at the contacts causes oxidation, sticking of the reed, and trouble.



1

2



3

de-energized. The reed flies back, its inertia carrying its other contact to stationary contact A, the electromagnetic coil again is energized, the reed is pulled again toward stationary contact B and the cycle repeats itself again and again.

Vibrating at 115 cps through its neutral position, the reed reverses the d-c delivered to the power transformer 57½ times per second. These pulses, fed into the alternate ends of primary of the transformer in the power pack, are stepped-up and rectified to provide the B voltage for the car radio.

Trouble arises—and it often does—when the reed contacts oxidize at one or both of the stationary contacts. Then the reed sticks, fails to vibrate. A stuck vibrator means no reception. It can generally be detected by the absence of the soft

hum you usually hear when you turn your car radio on. (If the contacts have oxidized only on the A side, however, you may still hear some hum, even though the vibrator reed, and consequently the radio, is inoperative.)

To remedy stuck vibrator contact points, first remove the vibrator from the radio. This used to require removal of the entire set from behind the dash, but in recent years sets have been built so that removal of one or two screws securing the cover plate gives access to the chassis.


On a typical car radio chassis you'll see two aluminum cans. One of them—the smaller—is an electrolytic filter capacitor. The other, larger can contains the vibrator. It's provided with a pin base, and pulls out just like a tube.

With tin snips or sharp diagonal wire cutters, separate the rolled aluminum can from the Bakelite pin base. Underneath this shield can is a molded sponge rubber cup which acts as a noise

silencer. The vibrator itself is mounted on a sponge base, further to reduce noise.

Remove the cup and gently draw back the reed and insert a thin auto ignition point file between its contact and stationary contact A. Draw the file back and forth until the contacts are bright. Repeat this same operation with the other pair of contacts. The gap between each pair of contacts should be just wide enough to pass a strip of paper the thickness of the cover of this magazine.

Now replace the sponge rubber cup over the vibrator and make it secure with strips of adhesive or masking tape as in Fig. 3. Operating the vibrator without the shield ordinarily does not introduce interference into the set, but to play it safe, wrap the vibrator neatly in aluminum foil. Make sure that the foil makes positive contact with the chassis when the vibrator is replaced and doesn't short out any pins.—T. A. B.

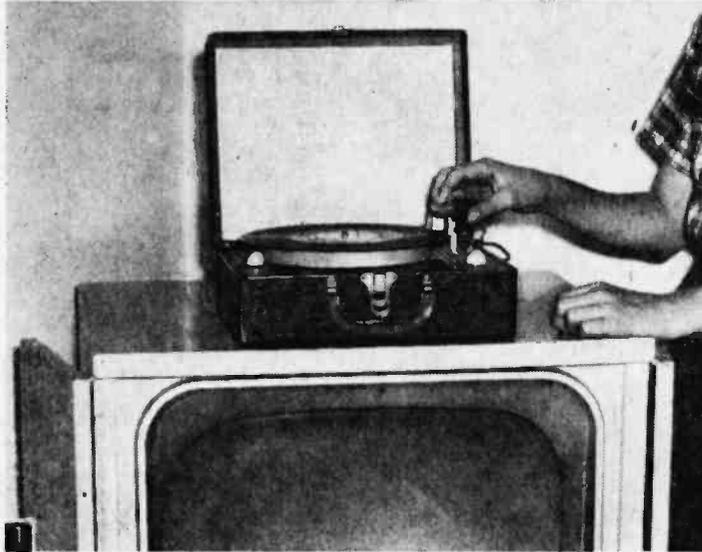


A simple circuit alteration converts any portable record player into a quality sound system that can employ your TV or radio console speaker to emphasize those otherwise lost bass tones.

player's circuit to afford full-range sound reproduction by employing the large speaker and baffle arrangements of console TV or radio receivers in conjunction with the player's speaker. By using a simple cable and jack arrangement, the speaker of the portable record player will function as *tweeter* for high frequency response and the console speaker will function as *woofer* for low frequency response.

The pictorial wiring plan (Fig. 2) shows how this dual speaker system functions. To make the change, drill a 3/8-in. hole on the motorboard of the record player and fit it with a midget phono jack. Then, solder two leads to the voice coil lugs of the record player speaker terminating them on
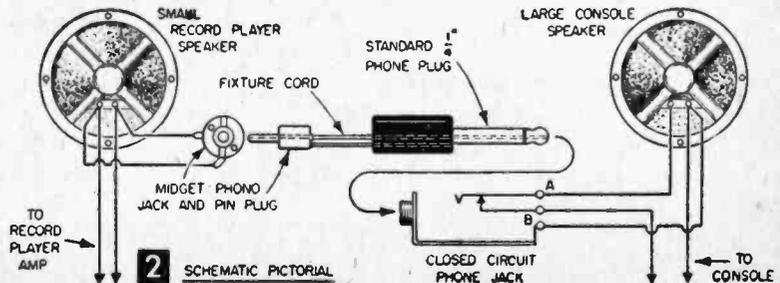
## Making Small Record Players Sound Like Thoroughbreds

THE quality of audio reproduction in most portable record players is limited because of the small 4 and 5 in. PM speakers which they usually employ due to space limitations within their carrying cases. It is, however, a simple operation to modify a record




Record player and console speakers are operated in parallel by plug-in cable. Removal of plug from telephone jack automatically restores console speaker to normal operation.

the jack lugs, and connect a length of plastic covered "zip" fixture cord to the pin and shell of a midget pin plug which matches the phono jack. The other end of the fixture cord is connected to a standard 1/4-in. telephone plug.

Now, enlarge one of the screw holes in an ordinary steel or brass 1/2x2x2-in. angle bracket to 3/8 in. and screw-fasten this bracket to the back of the console set at a 45° angle as shown in Fig. 3. Next, mount a Mallory #2A closed circuit jack in the 3/8-in. bracket hole. Mounting the telephone jack on the angle bracket allows for easy access to it without moving the console set away from the wall. Moreover, the set is in no way defaced, and can be instantly restored to normal operation by pulling the large telephone plug out of the jack.

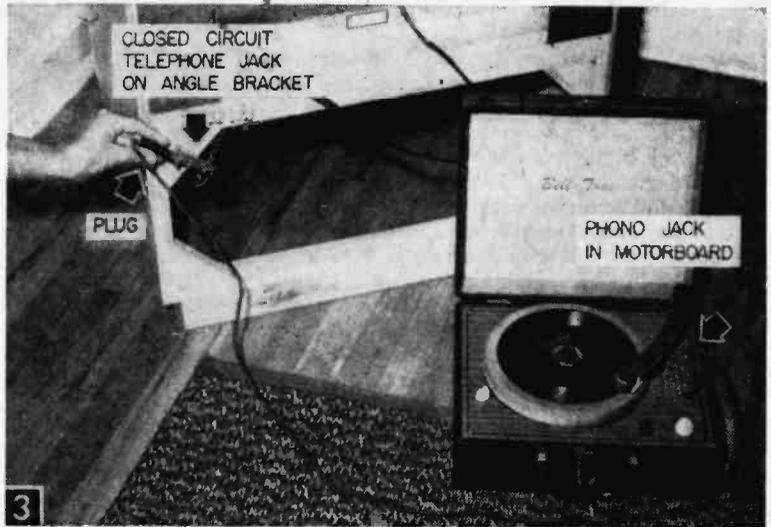Disconnect one of the console speaker wires and attach to jack lug A, Fig. 2, and run a length




of hook-up wire from the vacated speaker lug to jack lug B. Finally, run a length of hook-up wire from the speaker lug, which still has its original wire connected to it, to the frame lug of the closed circuit jack.

To use the player alone, put on a record and warm up the amplifier. Insert the midget phono pin plug in the motorboard jack and insert the telephone plug into the jack mounted on the rear of the console. It is not necessary to turn on the radio or TV set; inserting the telephone plug into the closed circuit jack has automatically disconnected the console speaker from the set so that it will be driven by the record player amplifier. If you enjoy ball games, fights, etc., but are annoyed by never-ending commercials, turn on the TV set, put a long-playing record on the phonograph, and enjoy the game with music and sans commercials.—T. A. B.


MATERIALS LIST—PHONO ADAPTOR

No.	Description
1	midget phono jack
1	midget pin plug
1	standard telephone jack (Mallory #2A)
1	standard telephone plug (ICA #29 or Mallory #75)
1	length two-conductor plastic "zip" fixture cord
1	1/2 x 2 x 2" brass or steel angle bracket


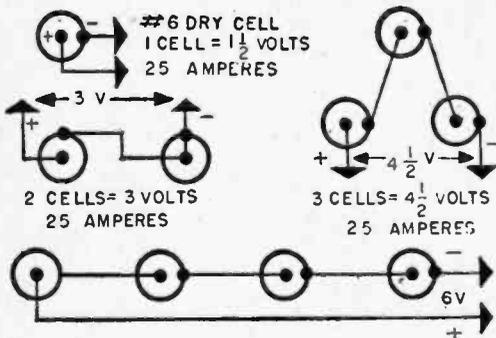
SINGLE CELLS OR BATTERIES CAN BE CONNECTED TO INCREASE VOLTAGE OR CURRENT



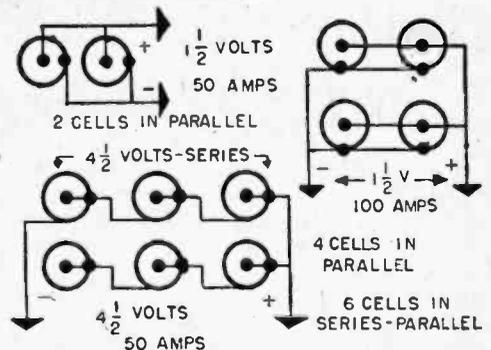SERIES CONNECTIONS OF SINGLE DRY CELLS  
VOLTAGE OF 1 CELL X NUMBER OF CELLS = VOLTAGE OF GROUP. CURRENT REMAINS AMPERAGE OF 1 CELL.



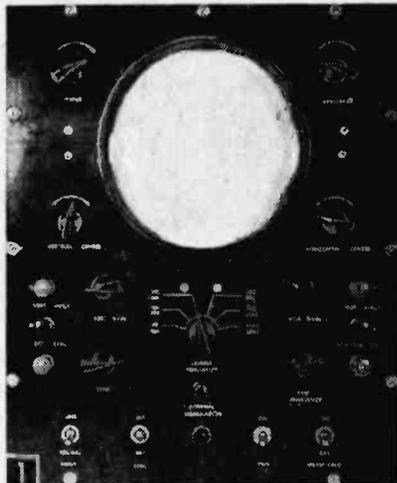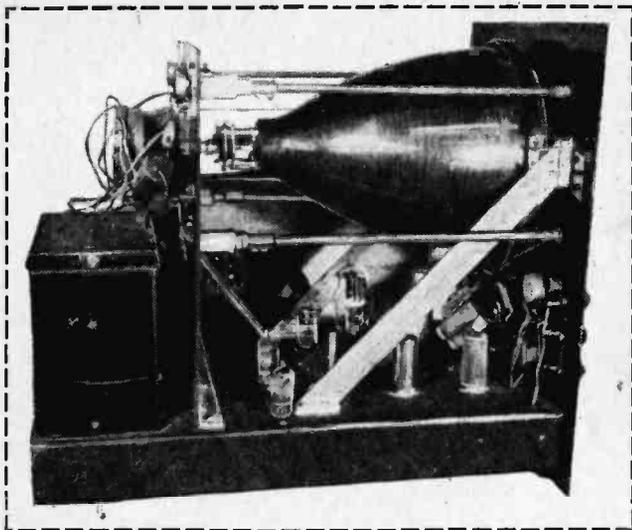SERIES-PARALLEL CONNECTIONS  
VOLTAGE OF 1 CELL X NUMBER IN SERIES = VOLTAGE OF GROUP  
CURRENT OF 1 CELL X NUMBER IN PARALLEL = AMPERAGE OF GROUP



Front-panel and side-chassis views of 7-in. conversion (see Fig. 3). Note that power supply is placed at rear of chassis.

# LARGE SCREEN SCOPES FROM DISCARDED TV SETS

By W. F. GEPHART

**S**TANDING IDLE in the back rooms of many TV-radio service shops, in dealer's trade-in warehouses, and in many attics and garages are hundreds of small-screen television sets that today are considered worthless. Most of these sets, however, can be converted to experimenter's oscilloscopes. The parts can be salvaged and placed on a new chassis and panel, or the existing chassis and cabinet can be adapted as-is.

Such a conversion consists of re-building some of the major circuits in the set, but usually the majority of the parts required are in the set as it stands. Since an oscilloscope consists of two high-gain amplifiers, a cathode ray tube with its associated controls, two power supplies, and a sweep circuit (see block diagram, Fig. 2), a TV set which has electrostatic deflection and focus (such as one with a 7EP4, 7GP4, 7JP4, 10GP4 or 10HP4 picture tube) can usually be used with the CR tube and associated controls and the high-voltage supply just as they appear in the set. In many sets the low-voltage supply is more than adequate (both current and voltage-wise) for oscilloscope use, leaving only the two amplifier circuits and sweep circuit to be designed and built.


In TV sets using tubes with magnetic deflection and focus, conversion problems are slightly greater and the focus usually has to be a mechanical control on the back of the unit, near the neck of the tube.

For most uses, the vertical amplifier in the scope should be more sensitive than the horizontal, since the latter is usually required only to amplify the sweep circuit pulses enough to cover the tube face. The

gain of the horizontal amplifier should be fairly high, however, to permit the use of external sweeping voltage when required. In both cases, the amplifiers should be push-pull output, to give equal deflection on either side of the center of the tube face.

The gain of the amplifiers will depend upon the type of picture tube in the TV set. Most 7-in. and 10-in. electrostatic deflection picture tubes have a deflection sensitivity of 75 to 250 *v.* per in. (the exact figure for individual tubes is given in tube manuals). This means, for example, that a difference of 150 *v.* between opposite deflection plates of the tube will move the electron beam 1 in. off center. If the polarity is reversed, the beam will move 1 in. off center in the other direction. An alternating voltage of 150 *v.*, then, will swing the beam 2 in.—1 in. on each side of center. Therefore, the voltage (*AF* or *RF*) required to "sweep" the tube face from side-to-side (or top-to-bottom) will equal the tube's deflection *v./in.* times the *radius* of the tube face. Thus, a 7-in. tube with a 150 *v./in.* deflection would require an amplifier with about 525 *v.* ( $150 \times 3\frac{1}{4}$ ), while a 10-in. tube with the same rating would require about 750 *v.* ( $150 \times 5$ ).

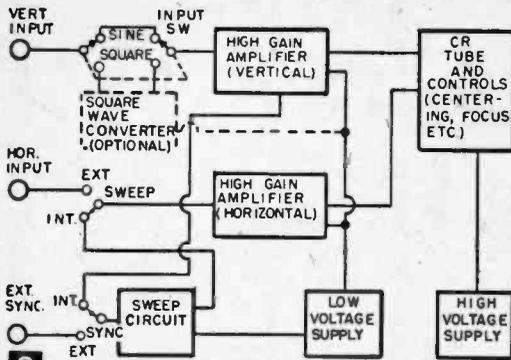Don't let these high output voltages alarm you. Virtually no power is required, and voltage am-



**2** BLOCK DIAGRAM OF OSCILLOSCOPE


plifier stages can easily furnish these voltages.

In magnetic deflection tubes, the deflection/in. data is not available, and must be determined experimentally. To do this, set up the picture tube, with proper anode and filament voltages, so that a spot appears on the face of the screen. Then apply experimental voltages to the vertical and horizontal deflection yokes to see what voltage is required to move the spot 1 in.

In determining amplifier gain, it must be decided what over-all sensitivity is required. Usually .1 v. per in. (meaning that .1 v. input to the

amplifier will cause the CR tube beam to move 1 in.) is the minimum input sensitivity acceptable; .05 v./in. is better. If the tube has a deflection rating of 150 v./in., and the over-all sensitivity is to be 0.5 v./in., the amplifier must amplify .05 v. up to 150 v., or it must have a voltage gain of 3000. Since one stage cannot very well have such high gain and high-voltage output, two or more stages will be needed, but neither stage gain need be too high, since the total gain is the product of the individual stage gains. To get a gain of 3000, for example, one stage could have a gain of 50, another stage a gain of 60, the total being 50 x 60, or 3000.

Amplifier design data is available in many tube manuals, and from this data circuits can be designed around tubes and parts in the TV set. Select a pair of tubes from the set (preferably high-gain triodes or remote cut-off pentodes) and, using the resistance-coupled amplifier data, select the values giving the highest gain. Note the bias on the tubes under the recommended conditions, and divide the output voltage desired (total deflection voltage required to cover the tube) by the voltage gain of the circuit, making sure that the input voltage required (to get the desired output voltage) does not exceed the tube's bias. If it does, other tubes of higher gain

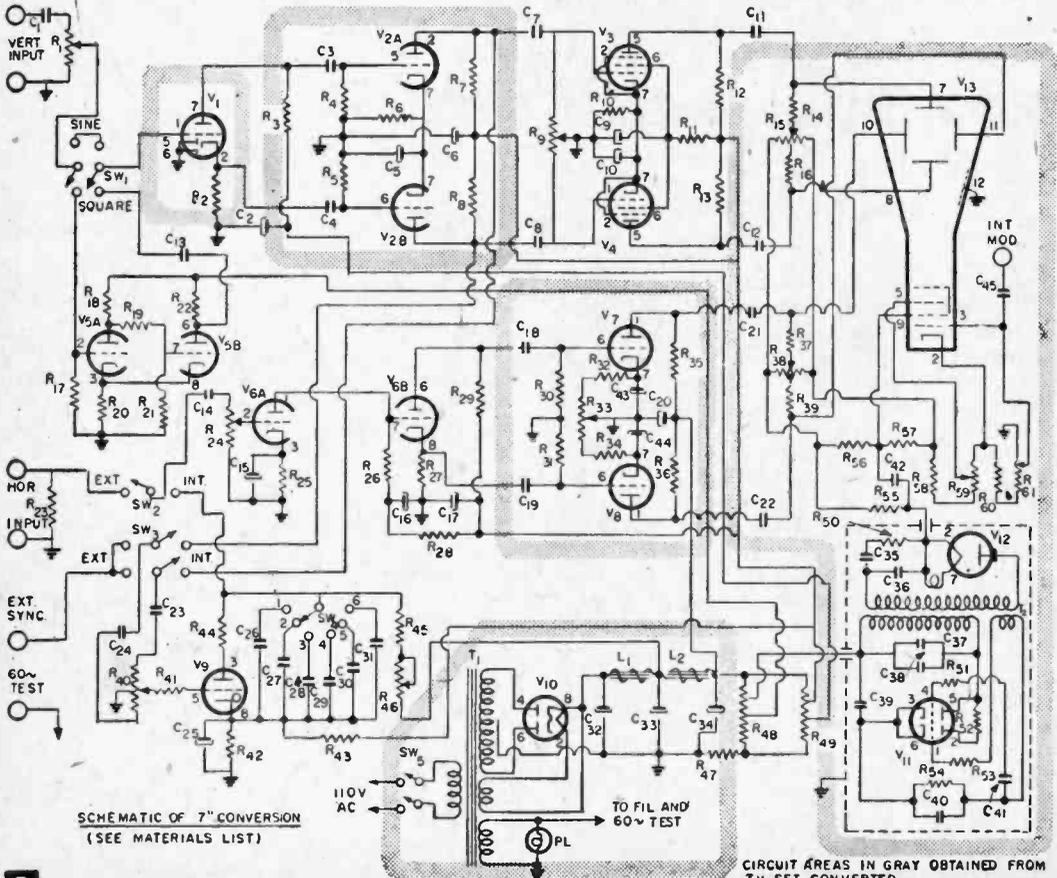

SCHEMATIC OF 7" CONVERSION (SEE MATERIALS LIST)

CIRCUIT AREAS IN GRAY OBTAINED FROM TV SET CONVERTED

MATERIALS LIST—SCOPE CONVERSION (FIG. 3)

Desig.	Description	Desig.	Description
R1	4 meg pot ("Vert. Gain")	C2, C6, C9, C16, C17,	8 mf., 450 v.
R2, R3	20K, 1 watt	C20, C32, C33, C34	.25 mf., 400 v.
R4, R5, R26, R41, R50	.1 meg., 1/2 watt	C3, C4, C7, C8, C14	
R6	120 ohm, 1 watt	C5, C10, C15, C25,	
R7, R8, R12, R13	51K, 1 watt	C43, C44	10-mf., 25 v.
R9	.1 meg pot ("Vert. Bal")	C11, C12, C21, C22	.005 mf., 6000 v.
R-10	690 ohm, 1 watt	C13, C18, C19	.1 mf., 400 v.
R11, R20, R27, R29	47K, 1 watt	C23, C24	.02 mf., 400 v.
R14, R16, R37, R39, R56,		C26	.2 mf., 400 v.
R57, R60	2.2 meg., 1 watt	C27	.04 mf., 400 v.
R15, R38	5 meg. C.T. pot. ("Vert." & "Hor" Centering)	C28	.01 mf., 400 v.
R17	.5 meg., 1/2 watt	C29	.0025 mf., 400 v.
R18	68K, 1 watt	C30	600 mmf., 400 v.
R19	.24 meg., 1/2 watt	C31	125 mmf., 400 v.
R21	92K, 1 watt	C35, C36	500 mmf., 6000 v.
R22, R28	22K, 1 watt	C37	750 mmf., 600 v.
R23	5 meg., 1/2 watt	C38	350-1100 mmf. trimmer
R24	2 meg pot ("Hor Gain")	C39	.01 mf., 400 v.
R25	2500 ohm, 1 watt	C40	.0015 mf. 400 v.
R30, R31	.33 meg., 1/2 watt	C41	360 mmf., 600 v.
R32, R34, R42	2K, 1 watt	C42	.001 mf., 6000 v.
R33	5K pot ("Hor Bal")	C45	.05 mf., 200 v.
R35, R36	.2 meg., 1/2 watt	T1	350-0-350 v. @ 150 ma., 6.3 v. @ 5 amps., 5 v. @ 2 amps.
R40	.2 meg C.T. pot ("Sync")	L1, L2	8 Henry, 150 ma. choke
R44	500 ohm, 1 watt	V1	6AT6
R45	1 meg., 1/2 watt	V2	6I6
R46	5 meg pot. ("Fine Frequency")	V3, V4	6AK6
R47	15K, 25 watt W.W.	V5	12AT7
R48, R49	25K, 25 watt W.W. adj	V6	12AU7
R51, R53	68 ohm, 1/2 watt	V7, V8	6AB4
R52	100 ohm, 1/2 watt	V9	884
R54	75K, 1/2 watt	V10	5V4G
R55, R58	1 meg., 1 watt	V11	6SN7
R59	5 meg pot ("Focus")	V12	183G
R61	.25 meg pot ("Intensity")	V13	7JP4
SW1	DPDT toggle ("Input")	PL	6.3 volt pilot light
SW2	SPDT toggle ("Sweep")		
SW3	DPDT toggle ("Sync")		
SW4	1 pole, 6 pos rotary ("Coarse Frequency")		
SWS	DPST toggle ("Power")		
C1	.5 mf., 600 v.		

Note: Small 7" or 10" screen TV sets can usually be obtained at low cost from any local TV-radio repair shop or TV dealer. Sets with 10" screens can also be obtained from the Video Electric Company, 79 Clinton Place, Newark, N. J., if none are available to you locally.


must be selected.

Next select another pair of tubes from the TV set, and select data from the charts that will furnish an output voltage sufficient to fully drive the stage planned above. Determine the voltage gain of this stage from the charts, and, multiplying by the voltage gain in the first stage designed, see if sufficient over-all gain has been developed. If not, continue with another stage.

The phase inverter, which has no gain, should be at a low level so that full advantage of push-pull operation can be utilized in the high gain stages.

Here's how these calculations would be made:

Using a 7EP4 CR tube, which requires 100 v./in. deflection, and desiring an input sensitivity of .05 v./in., total voltage gain required is 2000. The resistance-coupled amplifier design charts show that a 6AU6 (with proper resistances, etc.) will give a voltage gain of 230 with a grid bias of 2.1 v. Dividing this gain of 230 into 375 v. (the required output voltage for full deflection), gives a required input voltage of about 1.7 v. This input voltage is within the bias of the tube. To drive this, 1.7 v. is needed; the tube data charts show that a 12AU7 (with proper resistance, etc.) will give a voltage gain of 12, which, with an input of about .14 volt, will give the required output. The total gain of these two stages is 12x230 = 2760, which is in excess of requirements, and—assuming no losses—would mean that an input voltage of .132 volts would give full-tube deflection (or the equivalent of about .038 v./in. input). Since this input sensitivity is greater than required, a no-gain phase inverter can be put in front of these stages and the unit will still have the desired over-all gain.

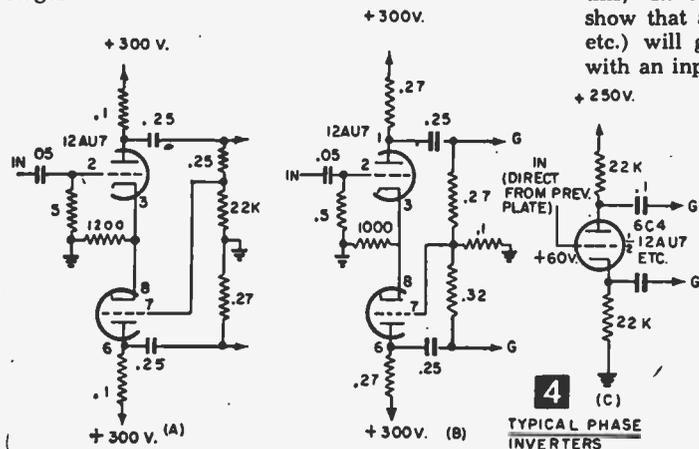

4 TYPICAL PHASE INVERTERS


The horizontal amplifier is designed in the same way, again using tubes from the TV set whenever possible. Usually an input sensitivity of .5 v./in. is sufficient for this purpose. Since power supplies in TV sets are usually ample to power all of these amplifiers, the remaining step is to design a sweep circuit for your scope.

There are two general types of sweep circuits used in commercial oscilloscopes: 1) the gas-discharge tube type, and 2) the multivibrator type. The gas-discharge tube is the simplest type, but it has limitations of maximum sweep frequency (usually 30,000 to 35,000 c.p.s.).

When the sweep frequency of a scope is equal to the frequency of the vertical input signal, one complete cycle will appear on the screen. When the input frequency is twice the sweep frequency, two cycles will appear, and so on. When the input frequency is more than 10 times the sweep frequency, the pattern becomes difficult to read, particularly when using a small CR tube. For example, with a 7 in. tube when there are 10 complete cycles on the screen, each cycle is less than 3/4 in. wide.

The maximum sweep frequency required would then depend upon the normal use of the scope. In TV work, where very high frequencies are encountered, a high sweep frequency would be required and a multivibrator sweep circuit would be necessary. In audio and low frequency RF work, a lower sweep frequency could be used and a gas-discharge sweep circuit would be adequate.

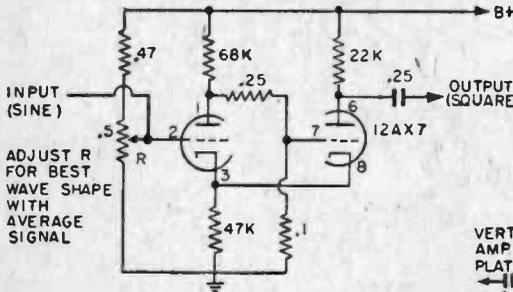
Very low sweep frequencies (such as 20 or 30 c.p.s.) are not feasible with a TV tube oscilloscope. The persistency of the coating on TV



**7** SQUARE WAVE CONVERTER

tubes is less than that on conventional CR tubes, and the trace (which is white, incidentally, not green) will disappear at low frequencies.

To lock in the pattern, a part of the vertical input signal is fed into the sweep circuit as a synchronizing voltage. This is taken from the vertical amplifier, but it should be a very low voltage to prevent distortion. The exact point for tapping to secure this voltage, and the dropping resistances to be placed in the line, can be determined by trial and error, using the lowest voltage that will lock the pattern in.

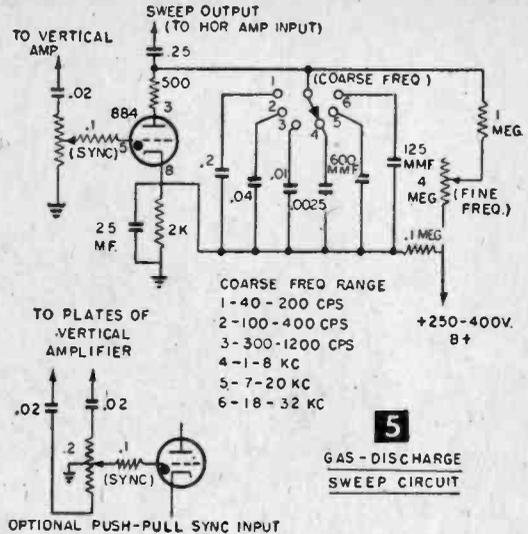


**5** GAS-DISCHARGE SWEEP CIRCUIT

Figure 3 shows the complete schematic of a 7-in. oscilloscope made from a discarded TV set. The majority of the components outlined in grey were secured from the TV set itself. Figure 4 shows three typical phase inverters; Figs. 5 and 6, the two types of sweep circuits.

Basically, these are the major circuits required for an oscilloscope, but another useful circuit is that shown in Fig. 7. Distortion is more evident in square waves than in sine waves, and many scope users prefer to convert sine waves to square waves for scope viewing. Figure 7 shows a simple square-wave converter that can be built into the scope if desired, preferably in the vertical input section (as shown in Fig. 2).

When making your conversion, remember:

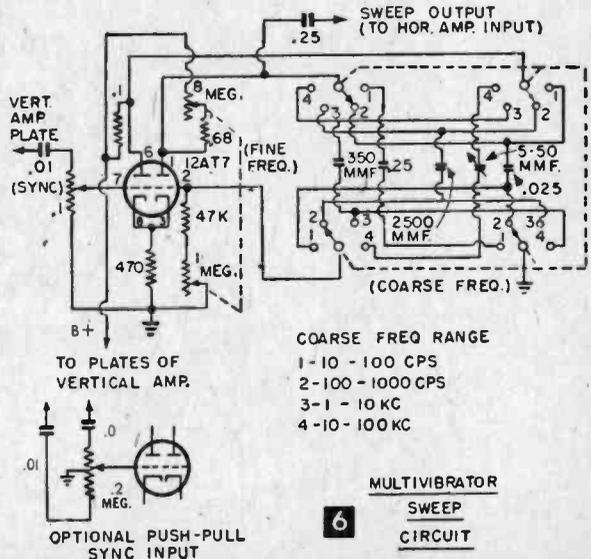1) Most TV set high-voltage supplies consist of an RF oscillator whose output is fed into an air-core transformer, and then to a high-voltage rectifier.




**6** MULTIVIBRATOR SWEEP CIRCUIT

This circuitry should be well-shielded, both from the standpoint of RF shielding, and high-voltage protection. Usually the high-voltage supply, complete in its shielding, can be transferred from the TV set.

2) Electrostatic deflection picture tubes are easily affected by stray ac fields (this will show up as a thick or wavy line trace instead of a sharp line), and good ac shielding should be used throughout your scope. If the power transformer is not shielded, place a steel shield plate (or the chassis) between it and the CR tube. In some cases, a steel shield may also be required around the neck of the CR tube.

3) Certain picture tube controls (such as centering, brightness, etc.) have extremely high voltage on the controls; they should always be used with an insulated shaft. Also, whenever possible, all controls and components carrying these high voltages should be isolated from other controls or components.

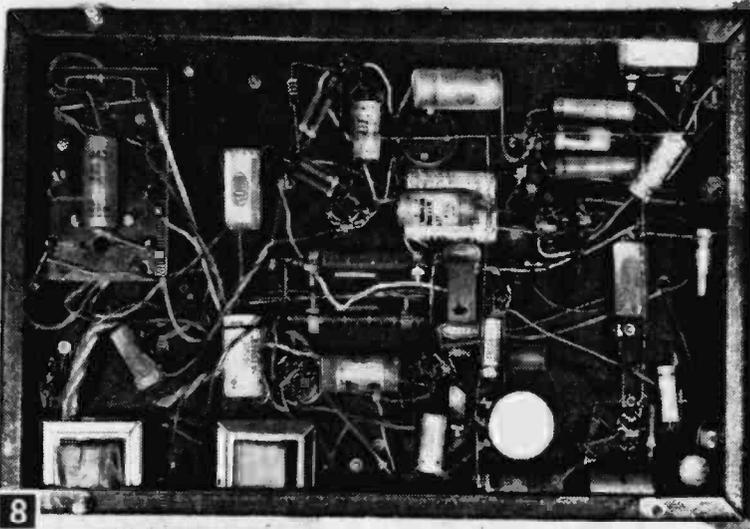4) If at all possible, when the scope is built on a new chassis, the picture tube mountings from the TV set should be used. CR tubes are somewhat delicate, and extremely dangerous if they shatter. Care should be exercised when mounting the tube to be sure that no strain is placed upon it.




Under-chassis view of 7-in. conversion. Scope was built on new chassis, using some new components, many from TV set converted (see Fig. 3).

5) If the set is to be completely re-built on a new chassis, a long, narrow chassis is preferable, with the horizontal amplifier down one side, the vertical down the other (both inputs at the front), and the other circuits in the middle. In such cases, both the high and low voltage power supplies should be at the back of the chassis, as far from the input as possible.


Figures 1 and 8 show views of a re-built TV tube to oscilloscope conversion. Note that the power supplies are at the back of the inner-panel (which has a steel shielding plate on the front of it), and that the amplifiers are built down the side of the chassis.
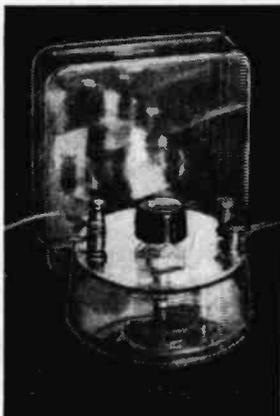
### Kitchenware for UHF Experimentation

• Plastic food containers make good looking low-loss chassis and cabinets for various ultra-high-frequency assemblies. Many of these containers are made of Styron, a member of the polystyrene family and a very good insulator. Containers are cheaper than sheet polystyrene, and come already formed. Photo shows 2 styles which are especially handy. The round one is an experimental FM crystal set using a germanium diode, which slope-detects close-by FM stations.—A. T.



### Solderless Tube Sockets

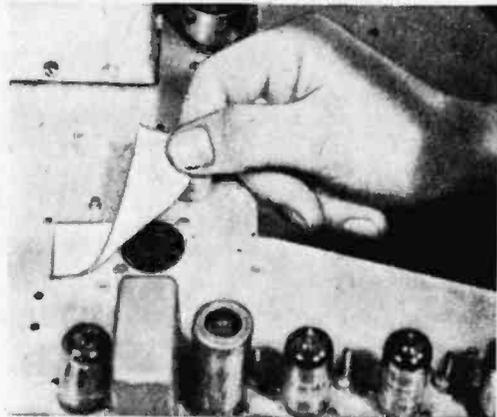

• When soldering on top side of radio or TV chassis, dropping solder in an open tube socket can cause trouble. Eliminate this possibility by placing a strip of wide adhesive tape over the open socket.—H. LEEPER.



CAP Cadets receive communications training with real equipment whenever possible. These Blue Island, Illinois cadets are shown at the control console of "Big Mo" (Yellow Fox 75), a 400-watt semi-trailer mounted mobile unit maintained by the Illinois Wing, during a recent practice alert.

## Civil Air Patrol Radio

The world's largest privately  
owned shortwave network

By CORKLEIGH E. WHITE

**Time:** Late August, 1955. **Place:** East Stroudsburg, Pennsylvania—Torrents of rain brought by Hurricane Diane have turned normally peaceful Broadhead Creek into a raging flood; all of the usual approaches to East Stroudsburg are washed out. Only one slim link with the outside world remains—the damaged remnant of a steel railway bridge.



An excellent example of CAP ability to adapt material at hand for maximum versatility is this combination ambulance-radio station-equipment trailer maintained by the O'Hare CAP Squadron for emergency use in the Chicago area.

fore the Japanese attack at Pearl Harbor, the Civil Air Patrol has grown until today it has more than 91,000 volunteer members. Its founders were civilian pilots who wanted to do their part toward making America strong, but who—for physical or other reasons—were unable to join the armed services. Today, some 51,000 of CAP's members are cadets—young men or women 14 years of age or older who are engaged in an intensive aviation education program.

IT IS a very slim link, indeed. Most of the bridge's foundations have disappeared and the remaining structure has been pounded and tortured until only one twisted girder is left in place.

Within the town and throughout the surrounding farmland, hundreds of homes have been washed out. Streets are flooded, commerce is at a standstill, thousands of persons are in need of food, warm blankets, dry clothing and medical supplies.

But how are rescuers to know exactly what is needed—and where? It is imperative that some means of communication with East Stroudsburg authorities be established, and the call goes out for volunteers.

First to respond is Warrant Officer Philip Hardaker, a member of the Civil Air Patrol's Stroudsburg Squadron. Clutching his small VHF transceiver tightly in one hand, Hardaker inches painfully across the single remaining girder of the railway bridge.

He reaches the far side just in time. Only minutes after he has crossed, the girder gives way and topples into the river below.

For the next 72 hours, Hardaker's small VHF transceiver keeps East Stroudsburg in contact with CAP stations across the river and with CAP aircraft circling overhead. His messages enable armed services helicopters to pinpoint the location of marooned families and to drop supplies to them. His work is credited by rescue officials as being responsible for saving many, many lives. (The exact number of persons who perished in the great flood of 1955 is unknown, but it is a fact that more than 80 bodies were found in the Stroudsburg-East Stroudsburg area alone after the flood waters had subsided.)

Hundreds of stories like Hardaker's are on file at Civil Air Patrol's National Headquarters in Washington, D. C. What, then, is this CAP radio system? How is it staffed, equipped and organized? Who does the maintenance? And who pays the bills?

Before attempting to answer these questions, let's take a look at the Civil Air Patrol organization as a whole and see what makes it tick. Founded on December 1, 1941, just six days be-

Described by officials of the United States Air Force's Air Rescue Service as its "right arm," CAP members use their own private planes and liaison planes donated by the Air Force, Army and Navy to fly each year more than 60% of the total search hours flown by all agencies on aerial searches within the continental limits of the United States. Some 6000 of these light planes, together with more than 11,700 fixed, mobile and airborne radio stations, can be mustered in an emergency.

They can be put to work in a surprisingly short time, too. Just recently, for example, a flying farmer en route from Springfield, Illinois, to Danville in the eastern part of the state, was reported overdue by the Civil Aeronautics Administration. Although the report came in during the small hours of the morning, 20 aircraft and as many radio stations were in service by dawn. They found their target in less than three hours and many of the search participants were back working at their regular jobs by noon of the same day.

A routine mission, but it speaks well for the thousands of hours CAP units spend annually in training to maintain their proficiency.

What kind of pay do Civil Air Patrol members receive for their services? The answer: nothing whatsoever. They even buy their own uniforms, the U. S. Air Force uniform with distinctive CAP insignia. Adult members pay an annual membership assessment for the privilege of promoting aviation. Although the Air Force does pay for fuel and lubricants used by CAP members on Air Force-requested missions, the only real compensation most members get is the satisfaction of a job well done.

Organized into eight regions covering the 52 wings (48 states plus the territories of Hawaii and Alaska, the Commonwealth of Puerto Rico and the District of Columbia), CAP members are further subdivided into some 2500 groups and squadrons. Each of these units is authorized to use two medium-frequency, fixed radio stations and as many mobile and airborne stations as necessary. Flexibility, mobility and reliability, the keystones of the net, enable CAP to blanket the United States with dependable communica-



## CAP WING

## WING CALL

## FIXED

## MOBILE

## AIRCRAFT

Alabama	KIG-442	Golden Rod	Hot Rod	Ram Rod
Alaska	KWA-677	Sourdough	Mulluk	Aurora
Arizona	KOF-424	Thunderbird	Geronimo	Tomahawk
Arkansas	KKI-719	Dogwood	Razorback	Diamond
California	KME-284	White Bear	Black Bear	Brawn Bear
Colorado	KAF-357	Pikes Peak	Red River	Blue River
Connecticut	KCC-590	Nutmeg	Rambler	Racket
Delaware	KGC-462	Gabby	Vagabond	Barfly
District of Columbia	KGC-463	Aero	Aerodyne	Aeronaut
Florida	KIG-444	Sparrow	Crane	Eagle
Georgia	KIG-443	Red Star	White Star	Blue Star
Hawaii	KUA-341	Firebrand	Mobile	Hiboy
Idaho	KOB-425	Magpie	Rabbit	Hornet
Illinois	KSC-952	Red Fox	Yellow Fox	Blue Fox
Indiana	KSC-953	Red Fire	Blue Fire	Green Fire
Iowa	KAF-358	Corn State	Bulldog	Cyclone
Kansas	KAF-359	Jayhawk Post	Jayhawk Bug	Jayhawk Bat
Kentucky	KIG-445	Middleground	Whirlaway	Jet Pilot
Louisiana	KKI-720	Magnolia	Muskrat	Pelican
Maine	KCC-591	Pinetree	Pinekarr	Pineayr
Massachusetts	KCC-592	Freedom	Pilgrim	Clipper
Maryland	KGC-464	Plant	Tug	Jet
Michigan	KQD-405	Red Robin	White Robin	Blue Robin
Minnesota	KAF-360	Starfish	Dog Fish	Cat Fish
Mississippi	KKI-721	Mockingbird	Jay Bird	Snow Bird
Missouri	KAF-361	Blue Bird	Red Bird	Black Bird
Montana	KOF-426	Father	Mother	Angel
New Jersey	KEC-994	Zigzag	Domino	Aircan
Nebraska	KAF-362	Wigwam	Buffalo	Meadowlark
Nevada	KOD-427	North Wind	Yellow Jacket	Red Spider
New Hampshire	KCC-593	Profile	Bobcat	Saucer
New Mexico	KKI-722	Pueblo	Zuni	Navajo
New York	KEC-995	Empire	Tomcat	Wildcat
North Carolina	KIG-446	Red Dog	Blue Dog	Mad Dog
North Dakota	KAF-363	Black Foot	Sioux	Mohawk
Ohio	KQD-406	Black Hawk	Gray Hawk	White Hawk
Oklahoma	KKI-723	Sooner	Oilwell	Gaswell
Oregon	KOF-428	Beaver Fox	Beaver Muskrat	Beaver Bird
Pennsylvania	KGC-465	Keystone	Rolling Stone	Flight Stone
Rhode Island	KCC-594	Rhody	Little Rhody	Air Rhody
Puerto Rico	WWA-353	Pineapple	Sugar	Hurricane
South Carolina	KIG-447	Kiddy Car	Side Car	Box Car
South Dakota	KAF-364	Dakota	Mandan	Cheyenne
Tennessee	KIG-448	Blue Chip	Red Chip	Gold Chip
Texas	KKI-724	Eagle Nest	Gold Eagle	Blue Eagle
Utah	KOF-429	Uncle Willie	Uncle Mike	Uncle Able
Vermont	KCC-595	Pico	Marble	Mansfield
Virginia	KIG-449	Blue Flite	Green Flite	Red Flite
Washington	KOF-430	Fir	Maple	Ash
West Virginia	KQD-407	Lowland	Overland	Highland
Wisconsin	KSC-954	Badger	Scooter	Buzzard
Wyoming	KOF-431	King	Queen	Jack

CAP planes must fly low and slow over rugged, often dangerous terrain to locate victims of air crashes and other disasters. When the "target" has been found, a message flashed over the CAP radio net will bring a radio-equipped mobile support unit to the scene in a hurry.

tions support for Civil Air Patrol's aerial activities.

Most CAP radio equipment is furnished by the members themselves. A small proportion comes from military surplus stocks. Transmitters range in power from portable units of less than one watt output to husky 400-watt control stations.

Some equipment is hand-tailored for CAP use by talented members. One excellent example of such handmade equipment is the tiny ½ watt, dry-cell powered VHF transceiver built by Major Leo Streff of Paxton, Illinois, the Illinois Wing's Director of Mobile Communications. Designed for use in light planes not equipped with electrical systems suitable for powering radio equipment, Streff's unit has given consistently good results at ranges up to 50 miles from altitudes of 2000 feet.

Quality standards for CAP radio stations are high. All transmitters must be crystal-controlled and capable of operating within .01% of frequency. Monitor stations in each region make frequent checks to insure that all equipment is remaining within tolerance



Light, compact equipment is extremely important to the Civil Air Patrol. Here, Major Leo Streff, Director of Mobile Communications for the Illinois Wing, is shown demonstrating the tiny  $\frac{1}{2}$  watt transmitter he designed for use in CAP's light planes to his wife, Captain Evelyn Streff, Illinois' Director of Communications Training.

and that operators are confining their transmissions to official CAP business.

Although operating on military frequencies loaned to its civilian auxiliary by the U. S. Air Force, control of the member-owned stations remains under the jurisdiction of the civilian unit commanders. Six high frequencies and one very high frequency are presently in use, with another very high frequency to be added shortly.

The high frequency wave lengths are used primarily for intra-state traffic over distances of 200 or 300 miles between fixed and mobile stations. Because of its line-of-sight characteristics, VHF is reserved primarily for ground-air, cadet training and local communications, although many operators have erected elaborate towers and antennas to extend the advantages of clear, static-free VHF operation over considerable distances.

"Tactical" call signs are used by all CAP stations. Many of them are derived from state or regional nicknames, or from major industries. "Badger" and "Corn State," for example, appropriately describe Wisconsin and Iowa base stations. The Wing carrying this patriotic practice to the furthest extent is probably Oklahoma, where base stations, mobiles and aircraft are known respectively as "Sooners," "Oilwells," and "Gaswells." In states where it is permitted, many CAP members who have equipped their automobiles with mobile radios use abbreviations of their CAP call signs on their license plates.

Civil Air Patrol radio operators are volunteers, as are all CAP members. Many are housewives, an occupation that presents special advantages because the ladies are usually able to monitor their assigned frequencies during the day, when most male operators must be out earning a living.

One of these valuable ladies is Captain Evelyn Streff, operator of the Illinois Wing's primary control station, "Red Fox 8," and Director of Communications Training for the wing. A CAP member since 1951, Evelyn handles as many as

20 separate pieces of traffic every day between the 459 licensed CAP stations under her jurisdiction. In addition, she makes daily traffic checks with the Great Lakes Region's control station at Detroit, and occasional contacts with passing Air Force aircraft. In spite of the demands on her time made by three very active children and an electronics technician husband, she usually manages to keep her station in operation from 6:30 in the morning until 7 or 7:30 at night. In emergencies she has been known to operate the clock around.

How does she find the time?

"It's not always easy," Evelyn says. "But if you feel that the job you're doing is important enough, you'll find that you can make the time somehow."

Illinois, like most states, conducts a daily half-hour net for all stations who are able to check in during the daylight hours. Many operators, of course, are not ordinarily available during the day and must pass traffic before going to work in the morning or after returning home in the evening. Indeed, some regularly check in with the mobile stations in their cars on the way to and from work.

Among the most unusual CAP stations are those operated by Indians of the Navajo Reservation in Arizona. Since 1951, when a squadron was first established on the reservation, "the wind that speaks" has many times summoned the life-saving assistance of planes of the Arizona Wing. Today, there are three CAP squadrons on the reservation, and 32 landing strips have been built.

Is the network growing?

"Yes, indeed," says Captain John W. Scott, USAF, Director of Communications at CAP's National Headquarters. "The network has grown steadily, both in numbers and in quality. In 1955 alone, we added over 700 stations."

And what does the U. S. Air Force say about the CAP radio net?

In a message lauding CAP on its 15th Anniversary, General Nathan F. Twining, then USAF Chief of Staff, said:

"Well trained and well organized, the Civil Air Patrol provides immediate aid and assistance to the private citizen and to the nation in time of emergency . . . a radio network of thousands of CAP stations which stand ready for duty . . . has earned our deep respect for its work in flood and hurricane disaster . . ."

And now, how about you? Got a quiet evening coming up soon? Drag the old short-wave receiver down off the shelf, hook up an antenna and start tuning the dial.

You'll recognize CAP frequencies by the tactical call signs they use. You may even think you've accidentally stumbled into a zoo if you happen to tune in when the Badgers, the Black Hawks and the Red Dogs are all on the air at the same time. But whatever you hear, you'll know that the volunteer radiomen and women of the Civil Air Patrol are on the job, ready and willing to do their part when disaster strikes.

# How to Get Three Speeds from a Two Speed PHONO MOTOR

By ARTHUR TRAUFFER

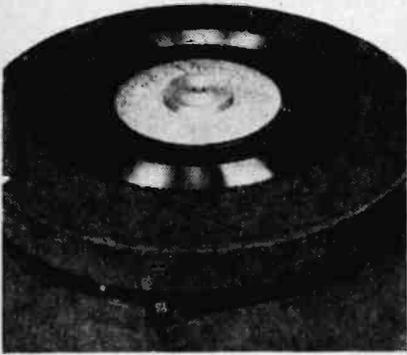


Fig. 1. The centering disc for Victor 45 rpm records. The writer turned his disc from cold-rolled steel.

**I**F YOU own a General Industries Model-DR dual-speed (78 and 33 rpm) phono motor which plays both standard discs and Columbia LP's, you can, by a simple operation, convert it to play in addition the new 45 rpm RCA-Victor discs. An inspection of the motor (Dwg. 1) reveals that the 78 rpm part of the motor shaft is a removable aluminum collar held by a spline type set-screw. When set-screw is loosened and collar removed you will find the motor shaft measures about .3115 in. and gives turntable a speed of about 58 rpm. Pack cotton around motor shaft to keep metal shavings out of motor bearings, and while motor is running, file shaft down to about .263 in. or just enough to give exactly 45 rpm. (Dwg. 2). Now the table speed can be shifted from 45 to 33 rpm instead of from 78 to 33 as formerly and the aluminum collar can be put back


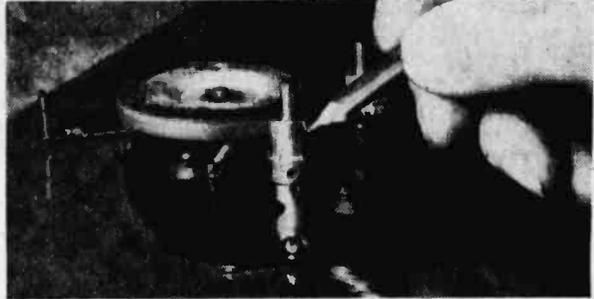


Fig. 2. The works of the General Industries Model-DR dual-speed phono motor. Pencil points to the 78 rpm diameter on removable aluminum collar over motor shaft.

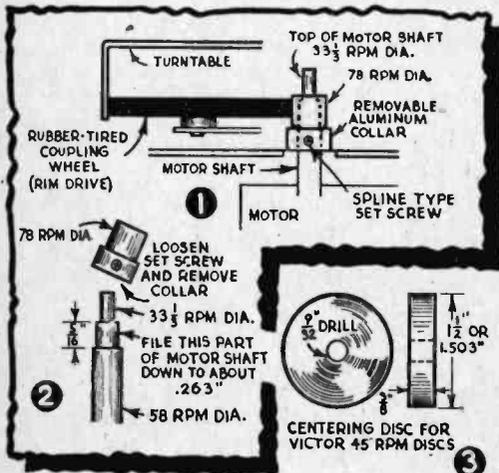

Fig. 3. The 78 rpm aluminum collar has been removed by loosening spline set-screw. Pencil points to part of motor shaft that has been filed down to .263 in. or just enough to give exactly 45 rpm. Aluminum collar can be put back for 78 rpm.



on the motor shaft to play 78 rpm discs.

Use a new or clean file to file shaft to 45 rpm. The motor shaft turns in a counter clockwise direction; move the file against the direction of turn. Take a little at a time off the shaft and test for speed each time to prevent obtaining a turntable speed below 45 rpm. Turn centering disc on a lathe from cold-rolled steel, fiber, plastic, or even hardwood (Dwg. 3).




## Removing Enamel Wire Insulation

• To remove enamel insulation on magnet and hook-up wire quickly and cleanly, wrap a piece of sandpaper around the wire and give a twisting, rotary motion.—E. L. BURNER.




quality and maximum record life use a long-play, sapphire-tipped needle, size .001, in the pickup for LP's and 45's. Ordinary 78 rpm records play best with a .003 osmium or sapphire-tipped needle.

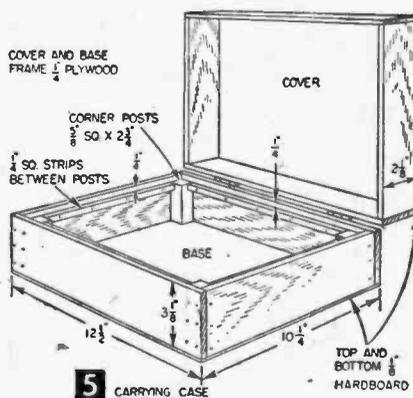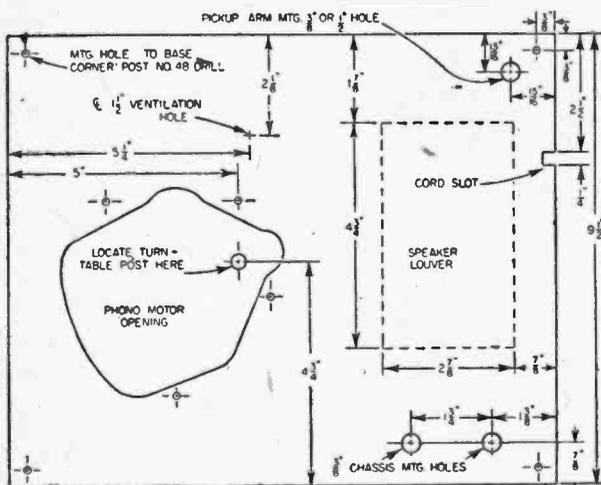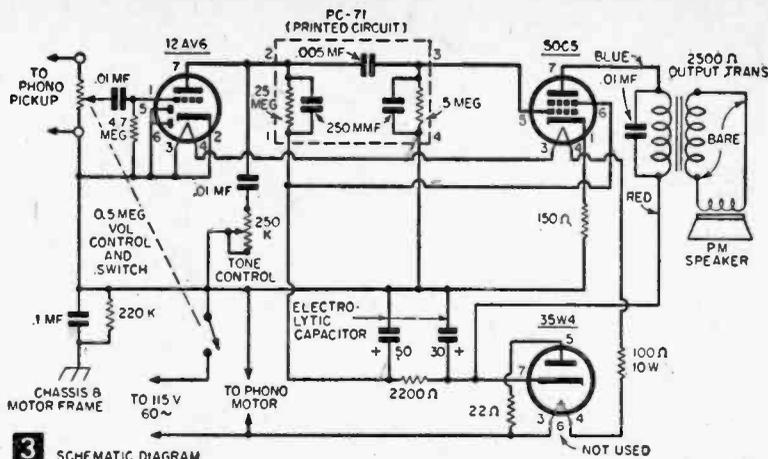Since swivel mounting bushings on pickup arms vary,  $\frac{3}{8}$ -in. or  $\frac{1}{2}$ -in. is indicated in Fig. 4 as hole size for the pickup arm. The speaker louver may be slotted, drilled or cut out and fitted with metallic grille cloth.



#### MATERIALS LIST MIDGET RECORD PLAYER

Amt.	Description
1	$3\frac{1}{2} \times 4\frac{1}{2}$ " metal chassis
3	7-pin miniature wafer or molded sockets
1	2500 ohm output transformer (50L6 type)
1	4" round or 4 x 6" oval PM Speaker
1	6' line cord and plug
3	.01 mf., 200 w.v. plastic tubular capacitors
1	.1 mf., 200 w.v. plastic tubular capacitor
1	30-50 mf. dual electrolytic capacitor
1	Centralab PC-71 couplate (or Erie equiv.)
1	4.7 meg., $\frac{1}{2}$ -watt resistor
1	222,000 ohm $\frac{1}{2}$ -watt resistor (220K)
1	2200 ohm 1-watt resistor
1	22 ohm 1-watt resistor
1	100 ohm 10-watt wire-wound resistor (ICA type AB)
1	0.5 meg. midget volume control-switch, plus push-on or set-screw knob
1	250,000 ohm midget tone control (250K), plus push-on or set-screw knob
1	$\frac{1}{4} \times 9\frac{1}{2} \times 11\frac{7}{8}$ " hardboard
2	$\frac{1}{8} \times 10\frac{1}{2} \times 12\frac{1}{2}$ " hardboard
	89" of $\frac{1}{4} \times \frac{3}{8}$ " plywood
	11" of $\frac{3}{8}$ " sq. softwood
1	Astatic #510-LT-4AG, or Shure #92U all-speed pickup arm
1	General Instrument 3-speed motor with 8-in. turntable
	Miscellaneous hardware

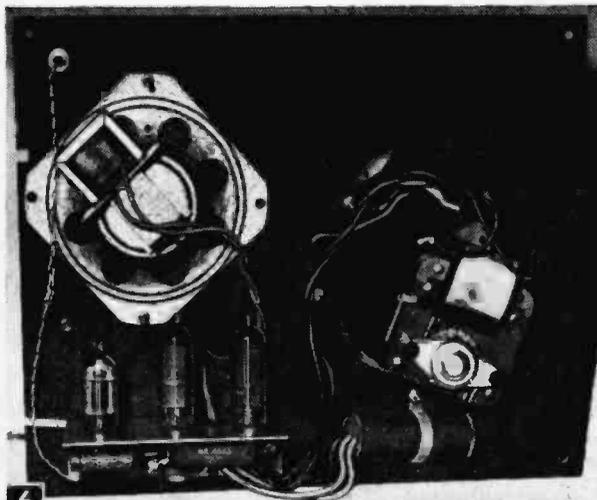

Bottom view of completely assembled motor board with amplifier, pickup arm, speaker and three-speed motor in place.

With wiring completed and all component parts in place on the motor board, test the record player by supporting the motor board on four 1x1-in. wood posts, 3-in. long, and playing a record. If there is hum from the amplifier, run a wire from the grounding lug on the motor frame to the amplifier chassis. If, with the volume control fully advanced, there is a tendency to howl, ground the bushing of the pickup arm.

Construction of the carrying case is detailed in Fig. 5. Brads are used for assembly and plas-

tic, leather-grained fabric is glued to the outside of the case. Hardware (latch, hinges and handle) is inexpensive and available at hardware stores or luggage shops. Use "slip-pin" hinges (the kind you find on typewriter and tape recorder cases) so that the cover can be removed when 12-in. LP's are played.

Four #8, 1½-in. binding-head screws secure the completely assembled motor board (Fig. 6) to the base of the carrying case, screwing into the corner posts.

## Repair Simple Radio Troubles

Resurrect that old radio in attic or basement, or rejuvenate the set you're now using



Explore many other possible sources of trouble before you investigate the wiring under the chassis.

**T**HERE are still far too few radio servicemen available to handle all the work they are called upon to do. Most radio owners yell for help the first time any little thing goes wrong, and if the neighborhood service man cannot come at once, the householder is deprived of the use of his radio, perhaps for days.

A surprisingly large percentage of these jobs involve simple troubles that can readily be repaired by the home craftsman.

By making these minor repairs yourself you can insure uninterrupted use of your radio—and the work itself is fascinating.

These instructions can profitably serve as a guide for checking a great many of the simple and obvious troubles which can occur in radio sets and can be repaired with ordinary shop tools. Once you have checked a receiver for these simple defects and have proved to yourself that some

more serious trouble exists, you can justifiably take your receiver to a radio serviceman for repairs.

### Examine Line Cord

People have called radio servicemen to their homes an astonishingly large number of times simply because the line cord plug came out of the wall outlet. Therefore, direct your attention to this plug first. Be sure it fits snugly in the outlet. Examine its wire connections at the terminal screws. Make sure that power does exist at the wall outlet, by plugging a floor or table lamp into that outlet.

Breaks in the line cord itself are also frequent. These can usually be detected by bending the entire length of the cord through your fingers. If the insulation on the cord is damaged in any way, the entire cord should be replaced. Once insulation begins wearing, it will deteriorate rapidly along the entire length, and taping of damaged portions is not advisable. The chassis must be removed from the cabinet in order to replace the cord, and the connections at the receiver end of the cord must be soldered. This is a simple job for anyone who knows how to use a soldering iron.

### Plug Position Is Critical

With the receiver turned on and tuned to a station, try reversing the position of the plug in the wall outlet. There are a great many receiver-home situations in which the position of the plug is critical. If better reception is obtained in one position, mark both the plug and the outlet with crayon or other means to designate that position.

Defective tubes are undoubtedly the most common causes of troubles in radio receivers.

Fortunately, it is often possible to spot the bad tube by inspection or sense of touch. You can buy a new tube just as readily as could a radio serviceman, and can make the replacement with considerable financial saving to yourself and considerable saving of a trained radio man's time.

First of all, turn on the set and wait about one minute for tubes to warm up. Now inspect each tube in turn to see if a characteristic red glow of the filament is present. For metal tubes, for glass tubes which are hidden by other parts, and for glass tubes constructed in such a way that the filament cannot be seen, allow the set to warm up for about five minutes and then feel each tube in turn. Touch metal tubes lightly and carefully the first time, because some of them can get hot enough to give a painful burn. If one or two tubes in the receiver have no filament glow and remain cold, it is very likely that these tubes are defective.

In universal a.c.-d.c. receivers, the filaments of all the tubes are usually connected in series, like a string of Christmas tree lamps, so failure of one tube will cause them all to be cold. There is no convenient way to determine which tube is bad without instruments, so all of the tubes will have to be tested.

### Have Tubes Tested

Testing of all tubes is a routine part of every radio service job. You are therefore fully justified in removing all the tubes from your set and taking them to a shop for testing. When tubes are brought to the shop loose (not in the set), they can be checked in a few minutes. A charge of five cents per tube for testing is fully justified, but most shops will test tubes free.

When removing tubes from a receiver for testing, be sure that you will be able to replace the tubes in the correct sockets. The safest plan involves making a rough layout of the top of the chassis, showing the position of every tube socket and type number of the tube which belongs in

each socket. This is desirable even though the sockets themselves are marked, because it is not uncommon to find discrepancies between tube and socket numbers. Sometimes a diagram of this type is attached to the inside of the receiver cabinet by the manufacturer.

Tubes can usually be removed without trouble by pulling firmly upward while rocking gently from side to side. Top cap connections and metal shields should of course be removed before taking out the tube. Note on your diagram the tubes which have shields, because it is extremely important that the shields be put back on the tubes requiring them. Also, if there is any possibility that leads to top caps of tubes can become interchanged, identify these leads also on your diagram.

If the receiver trouble is noise or intermittent failure, you may be able to locate the cause before removing the tubes by tapping each tube in turn with your finger while the receiver is in operation. If the noise increases or if a change in receiver operation is noted when a particular tube is tapped, a new tube should be secured.

In general, tubes which differ only in the last letters of the type numbers are interchangeable. These last letters merely indicate some of the mechanical characteristics of the tubes:

- M—Metal envelope and octal base
- G—Glass envelope and octal base
- GT—Short glass envelope and octal base
- L—Used with letters G, M or T to indicate a locking base (lokta) tube

Thus, the 6A8 metal tube is ordinarily interchangeable with 6A8G and 6A8GT glass tubes. When metal tubes are not available for your use, glass equivalents are ordinarily given automatically by radio stores. It is usually necessary to use a shield with a glass equivalent; these cost about a dime each, and come with a special base strip which automatically grounds the shield to pin No. 1 on the tube base. Usually, however, exact replacement types will be available.



PILOT LAMP IDENTIFICATION CHART

Type No.	Bead Color	Bulb and Base	Volts	Amp.	Type No.	Bead Color	Bulb and Base	Volts	Amp.
40	Brown	Tubular Screw	6-8	.15	50	White	Small Globular Screw	6-8	.20
41	White	Tubular Screw	2.5	.50	51	White	Small Globular Bayonet	6-8	.20
42	Green	Tubular Screw	3.2	.50	55	White	Large Globular Bayonet	6-8	.40
43	White	Tubular Bayonet	2.5	.50	292	White	Tubular Screw	2.9	.17
44	Blue	Tubular Bayonet	6-8	.25	292A	White	Tubular Bayonet	2.9	.17
45	Green	Tubular Bayonet	3.2	.50					
46	Blue	Tubular Screw	6-8	.25					
47	Brown	Tubular Bayonet	6-8	.15					
48	Pink	Tubular Screw	2.0	.06					
49	Pink	Tubular Bayonet	2.0	.06					
49A	White	Tubular Bayonet	2.1	.12					

Type 40A is exactly the same as Type 47. Type 49A may not be obtainable, but can be replaced with Type 49.

Types 43, 44 and 46 are used in tuning meters, where replacement with the correct type is particularly important. Be sure the right type is chosen.

Since tube types are constantly being modified and improved, and new types are constantly being added to the list of those available, for older radios especially there are quite a few cases in which other tube types will give equally satisfactory results. A list of these interchangeable tubes accompanies this article.

**Pilot Lamp Replacements**

Pilot lamps ordinarily serve the dual purpose of illuminating the tuning dial and indicating when the receiver is turned on. In larger receivers additional lamps are used for other indicating functions. Burned-out pilot lamps are readily replaced.

In most cases it will be entirely sufficient to remove the defective lamp and take it to the radio shop or hardware store, asking for a duplicate lamp. If you order by mail, however, and if there are no legible markings on the old lamp, you can determine the type number of any pilot lamp for ordering purposes with the aid of the accompanying pilot lamp chart.

If a pilot lamp burns out frequently, use a lamp having a higher voltage-rating. The light will be dimmer but probably still adequate.

Pilot lamps in universal receivers should be replaced as soon as possible because they are often connected in parallel with a portion of the voltage-dropping resistor or a portion of the rectifier tube filament. Failure of the pilot lamp sends excessive current through the other path, and this may cause failure of the resistor or rectifier tube.

**Hunt for Loose Connections**

It is not unusual for a radio serviceman to charge as much as five dollars for resoldering a single loose connection, because it takes a corresponding amount of his time to locate that connection before he can repair it. Here are suggestions for finding this particular trouble yourself.

Starting on top of the chassis, wiggle each exposed lead vigorously with your fingers or a stick of wood. Tap each part and terminal with the stick of wood. Check the antenna system in the same manner, paying particular attention to indoor antennas which run around the room and may make intermittent contact with metal objects in the room. Wiggle all plugs accessible from the outside of the receiver. All this is done, of course, while the receiver is turned on.

If noise occurs or there is a change in receiver operation when a particular part, terminal or wire is moved, concentrate on that location until you find the exact defect. Remember that vibrations can be transmitted through large parts and through the chassis, so the first point at which you produce noise may not be the defect. The trouble can easily be traced, however, by tapping more carefully so as to disturb as few other parts as possible.

If no defect is found outside the chassis, turn off the receiver and remove the chassis from its

cabinet. Now, with the chassis upside down, and with the loudspeaker connected, turn on the receiver and proceed to tap or otherwise move each part, terminal and wire under the chassis.

*Caution:* When working with a universal receiver, there will sometimes be one line cord plug position in which the chassis of the receiver is hot with respect to ground. The use of a wood stick for tapping purposes is particularly advisable here unless you have some means for determining which plug position connects the chassis to the grounded side of the power line.

Sometimes a trouble will develop only after a receiver has been in operation for ten or fifteen minutes. Here the bad connection will be caused by heat given off during operation of the set. With the chassis removed from the cabinet, free circulation of air will prevent parts from reaching normal operating temperatures and the set will work satisfactorily. The trouble can be "forced" in these cases by directing an electric heater at the underside of the chassis. Once heat has caused the trouble to develop, you can hunt for the bad connection as just described.

**Replace Noisy Controls**

If operation of the volume control, tone control or any other continuously variable control causes loud crackling noises in the loudspeaker,

**RADIO TUBE INTERCHANGEABILITY CHART**

Note: When a tube is made with several different envelopes all using the same base, it is listed only once in this chart. Therefore, disregard suffix letters like G, GT, GT/G, etc., when looking up tubes unless the same type of tube is listed with different suffixes.

Type No.	Interchangeable with	Type No.	Interchangeable with
1V	6Z3	25X6	25Z6
2A3H	2A3	25Z6	25X6
2X2	2Y2, 879	37	76
2Y2	2X2, 879	40	O1A
5E1	1A1	40Z5	45Z5/40Z5
5T4	5U4	43MG	25A6GT/G
5U4	5T4	44	39/44
5W4	5Y3G, 5Z4	45A	45
5Y3G	5W4, 5Z4	56A/56AS	76
5Z3	83V	57A/57AS	77
5Z4	5Y3G, 5W4	58A/58AS	78
6AB6G	6N6G	64	36
6AF6G	6AD6G	65	39/44
6B6G	6Q7G	67	37
6C5	6J5	68	38
6C6	77	76	37
6D6	78	77	6C6
6G5	6U5/6G5	78	6D6
6J5	6C5	83V	5Z3
6N5	6AB5/6N5	84	6Z4
6Q6	6T7	84MG	84/6Z4
6T5	6U5/6G5	86	76
6T7	6Q6	117L7	117M7
6U5	6U5/6G5	117M7	117L7
6U5	6Z3	150	50
6X5	6W5	171/171A	71A
1A4	1A4T	182A	71A
1A4P	1A4T	182B	483
1B4	1B4T	183	483
1B4P	1B4T	551	35/51
1D5G	1E5G	585	50
1D5GP	1E5G	586	50
1D5GT	1E5G	879	2X2
1F7G	1F7GH	951	1B4T
1F7GV	1F7GH	1232	7G7/1232
6Z3	1V	1852	6AC7/1852
6Z4	84	1853	6AE7/1853
12B7	14A7/12B7	PZ	47
14Z3	12Z3	PZH	2A5

that control is defective and should be replaced. It is not ordinarily practical to repair these controls. Get new ones.

Before removing the old control, draw a picture diagram showing all connections to the terminals of the control, so that you cannot possibly make any mistakes when connecting the new control. Remember that a little care taken while troubleshooting can save you much time and effort—and needless expense.

When ordering a new control, it is essential to give as much as possible of the following information:

1. The make of the receiver. This is usually printed on the front panel.
2. The model number of the receiver. This will be found printed on the rear of the chassis or on a label attached to the inside of the cabinet. It is best to copy all numbers which you find, exactly as they appear on the set. Admittedly, there will be times when no numbers whatsoever can be found.
3. Name of defective part, such as volume control, tone control, etc.
4. Electrical value of part, if known.
5. Manufacturer's part number, if known.
6. A list of all tubes used in the receiver. (This is particularly important if you are unable to find the model number.)

Practically all receivers bear a notation to the effect that the set was manufactured under an RCA license. This definitely does not mean that you have an RCA set unless confirmed by other markings.

Noisy switches can oftentimes be repaired by taking them apart and cleaning the contacts with carbon tetrachloride or other cleaning fluid, then bending the movable contact arm to provide increased contact pressure. Careful inspection will usually reveal how to correct the trouble.

### Loudspeaker Troubles

The various possible troubles which can occur in loudspeakers will usually reveal themselves by their own peculiar sounds or by complete absence of sound. The output transformer, which is usually mounted on the loudspeaker, is perhaps the commonest trouble in this category. An open primary wire is the usual defect, and blocks all signals. You can therefore suspect the output transformer when no program sounds are heard but there is the normal faint hum coming from the loudspeaker. Preliminary confirmation of the trouble can be made by removing and replacing a tube while the receiver is in operation; this should produce a click or thud in the loudspeaker if the output transformer is good, but no sound if the primary is open. Try this test for several tubes, one at a time, but not on the rectifier tube. Of course, continuity of the output transformer primary winding can be checked as a positive test if you have an ohmmeter.

The chief problem in replacing an output transformer is securing the correct new part. An exact duplicate part can sometimes be secured

by giving all the data specified for ordering volume controls, but radio men today usually prefer to secure a universal output transformer, designed to fit in a large number of sets. About all you need to give when ordering a universal output is the type number of the tube in the output stage of the receiver (if this stage has two identical tubes, be sure to indicate it). A universal unit will have a number of taps on the secondary winding, and instructions for making correct connections will invariably accompany the transformer. In the absence of instructions, however, simply connect the voice coil leads to the two terminals which give maximum volume and fidelity. The voltage at these leads is very low, so you can hold the leads in your hands while hunting for the best terminals.

A rattling sound which is particularly noticeable on low or bass notes can be caused by looseness of the cone around its outer edges. This trouble is cured simply by regluing the cone to the frame of the loudspeaker with loudspeaker cone cement or household glue.

### Simple Noise Test


Another cause for raspiness is an off-center voice coil, which rubs against the metal pole pieces of the loudspeaker. In most loudspeakers the voice coil can be recentered by loosening the adjusting screws (there may be only a single screw at the center of the cone, or there may be three screws anchoring the spider outside the cone), and placing quarter-inch strips of a calling card between the voice coil and the center pole and tightening the screws again. Four strips spaced equally around the coil are usually sufficient. Use the thickest card which will go into the space without forcing.

Loose spider screws can themselves cause rattling sounds. Dirt in the space surrounding the voice coil can cause raspiness.

To determine whether noise is originating inside or outside your receiver, turn on the receiver, make sure the noise condition exists, then short together the antenna and the ground terminals with a screwdriver. If this clears up the noise, you know that the trouble is either due to an antenna system defect or is due to noise interference being picked up by the antenna system. If shorting has no effect on the noise, you know that the trouble is either in the receiver or is due to noise signals coming in over the power line, trouble not easily removed.

A humming sound heard at all times, even when the loudspeaker is disconnected, can usually be traced to vibrating laminations in the power transformer of an a.c. receiver. First try tightening the mounting bolts of the transformer. If this does not reduce the hum sufficiently, drive a few triangular glazier's brads between the laminations, or simply drive in enough ordinary nails or brads to stop the vibration. This will not affect the performance of the transformer.

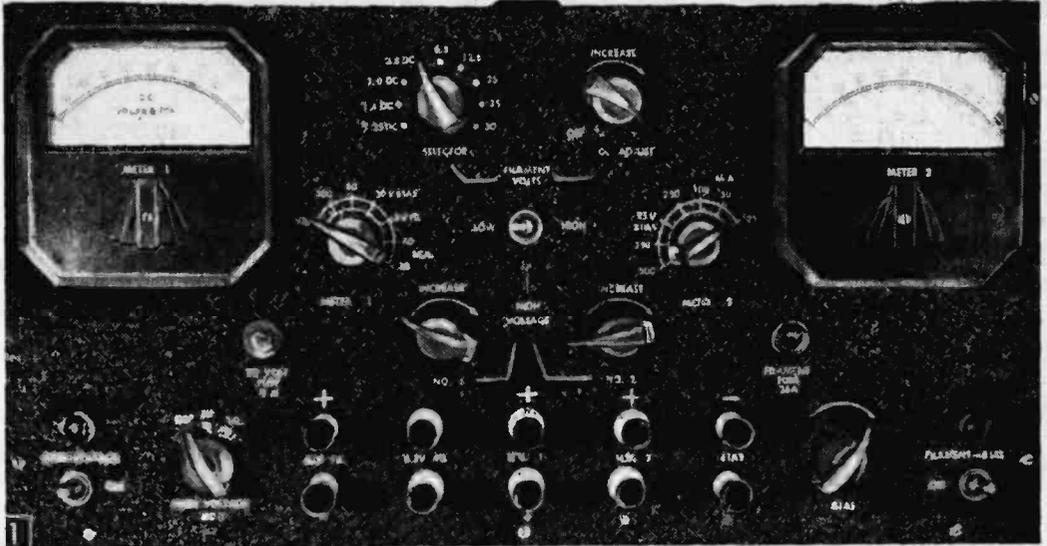In servicing your receiver at home, make haste slowly and *think* before you tinker.




Put it on the panel, connect it to a power source and you're through forever wasting time and losing temper jerry-rigging dropping resistors to get the test voltage you want.

# EXPERIMENTER'S Power Supply

By W. F. GEPHART

**A** VERSATILE, variable voltage, utility power supply is an essential piece of equipment for every electronic experimenter's test panel. The unit shown in Fig. 1 provides a wide variety of controlled voltages and it can be constructed of ordinary components, many of which can be found in the shop junk box, or at surplus stores. It is versatile in that any one of a number of different tube types can be used in the unit without the necessity of re-wiring, and, in many cases, a sub-par tube will work quite satisfactorily in it. This power supply provides the following voltages:

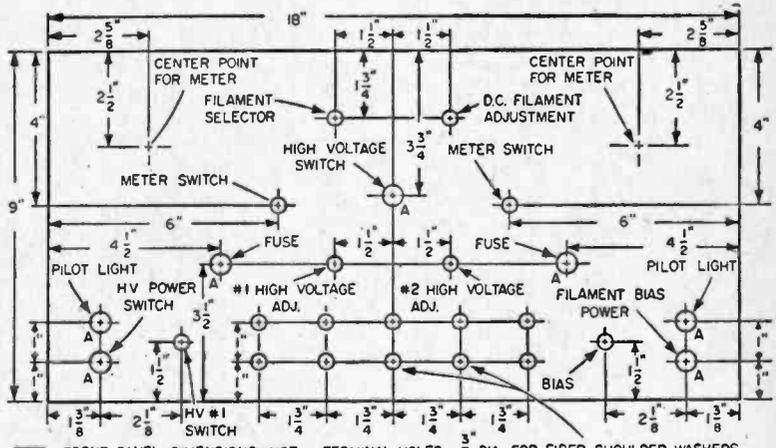
- 1) high voltage, variable between 100 and 450 v. d-c, at up to 200 ma.
- 2) medium voltage, variable between 40 and 450 v. d-c, at up to 100 ma.
- 3) d-c filament voltages, continuously variable from 1 to 3 v., at up to .2 amp.
- 4) a-c filament voltages of 6.3, 12.6, 25, 35 and 50 v., at up to 2 amps.
- 5) d-c bias voltage, variable from 0 to 25 v., at up to 30 ma.



**2** FRONT PANEL DIMENSIONS - USE 9X18X12" CABINET (ICA # 3B31) TERMINAL HOLES,  $\frac{3}{8}$ " DIA. FOR FIBER SHOULDER WASHERS HOLES MARKED "A"  $\frac{1}{2}$ " ALL OTHERS  $\frac{3}{8}$ "

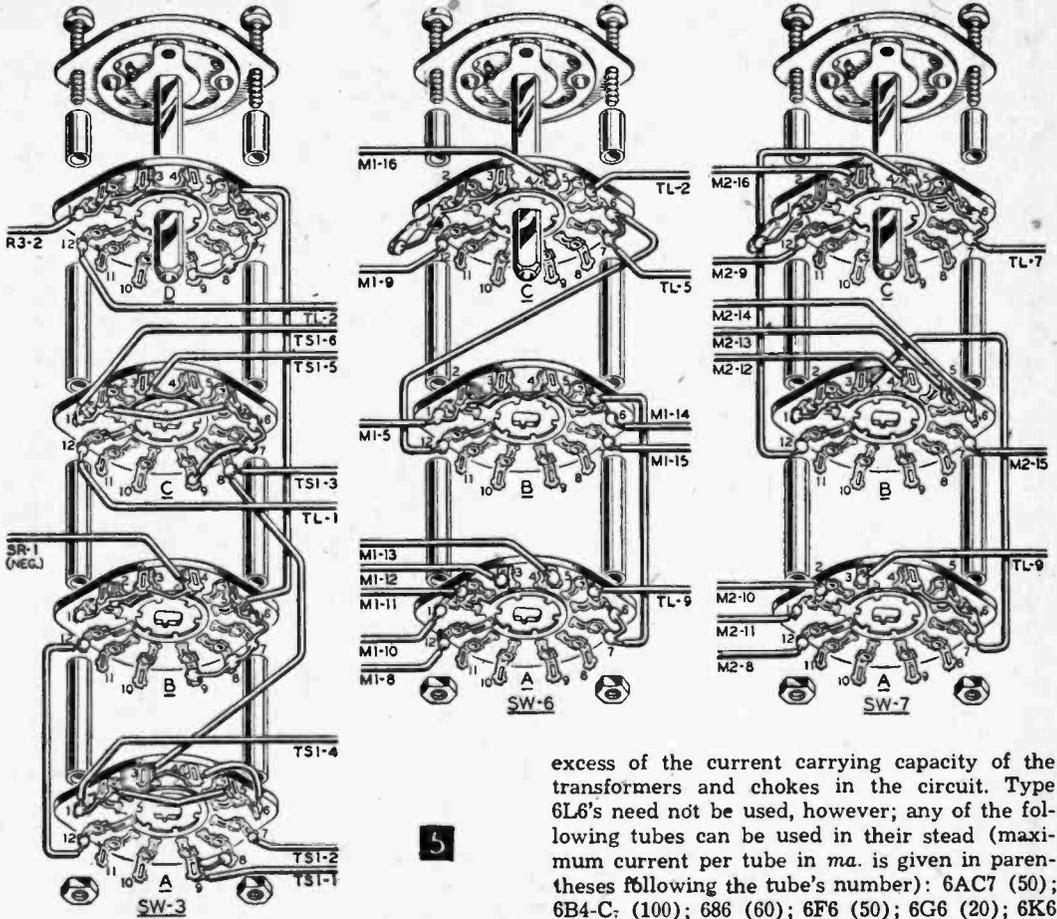6) separate 6.3 v. a-c filament voltage, at 2 amp. The high and the medium voltages can be used simultaneously, so long as the total current drawn from both does not exceed 200 ma., and, at the same time, either the variable a-c or d-c filament supply can be used with the bias supply, as long as the total current from these latter sources does not exceed 2 amps. The separate 6.3 v. a-c filament supply can be used at all times in conjunction with the other voltages. Thus the unit can furnish two high d-c voltages for plate applications, continuously variable, an a-c or d-c filament voltage, and d-c bias—all si-





**SWITCH WIRING**

characteristics of the tube, the amount of bias, and the cathode resistance. The lower the cathode resistance, the higher the ratio.

Bias for control, however, is secured from the cathode resistance, and a certain amount of current always flows through this resistance. The resistance cannot be too low, since this would cause excessive current flow and necessitate a high wattage cathode resistance. A higher resistance than that indicated could be used for R4 or R7, but it should always have at least a 2-watt capacity.

Using 6L6 tubes for V2 through V5 and 70,000 ohm potentiometers for R4 and R7 as specified in the Materials List, the minimum voltage obtainable with a choke input filter and no load, is about 90 v.

For one of the two separate variable control systems, three control tubes (V2, V3 and V4) are wired in parallel, thus providing sufficient current capacity. Type 6L6 tubes were used since we had an adequate supply of this type, removed from public address service because of noise, hum, etc., on hand. At 100 ma. per tube, this section then has a capacity of 300 ma., well in



excess of the current carrying capacity of the transformers and chokes in the circuit. Type 6L6's need not be used, however; any of the following tubes can be used in their stead (maximum current per tube in ma. is given in parentheses following the tube's number): 6AC7 (50); 6B4-C: (100); 686 (60); 6F6 (50); 6G6 (20); 6K6 (40); 6L6 (100); 6V6 (60); 6W6 (50); 6Y6 (70).

On the other variable control system, the filter section output is connected to the single control tube (V5, Fig. 2) through control switch S5 which provides a high or low range (the low range being secured through dropping resistor R6), and an Off position. In the Off position of S5, the current being drawn through the multi-tube control system can be measured on meter M2, the voltage simultaneously on meter M1.

The filament-bias supply consists of three separate transformers with outputs wired in varying series arrangements through the filament selector switch S3. For d-c output, these voltages are fed through S3 into a selenium rectifier circuit with a rheostat-controlled output to compensate for the varying load which might be drawn from the supply (one or more tubes in either series or parallel) causing different voltage drops within the filtering system.

The bias supply is varied by changing the input into the rectifier-filter system so as to present a more constant loading to the external circuit under test. A dual section filter is used, with high impedance chokes. Load resistor R5 can be omitted from the circuit if an external resistance is always used in the circuit under test. R5 can

6 ORIENTATION OF UNDER-CHASSIS

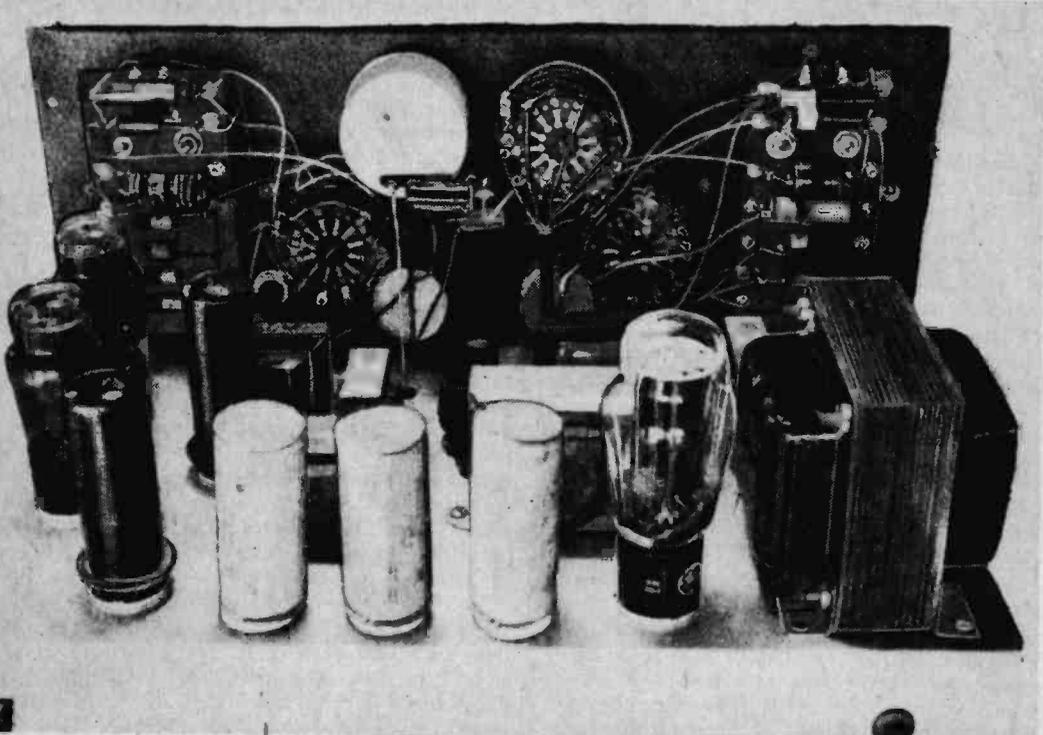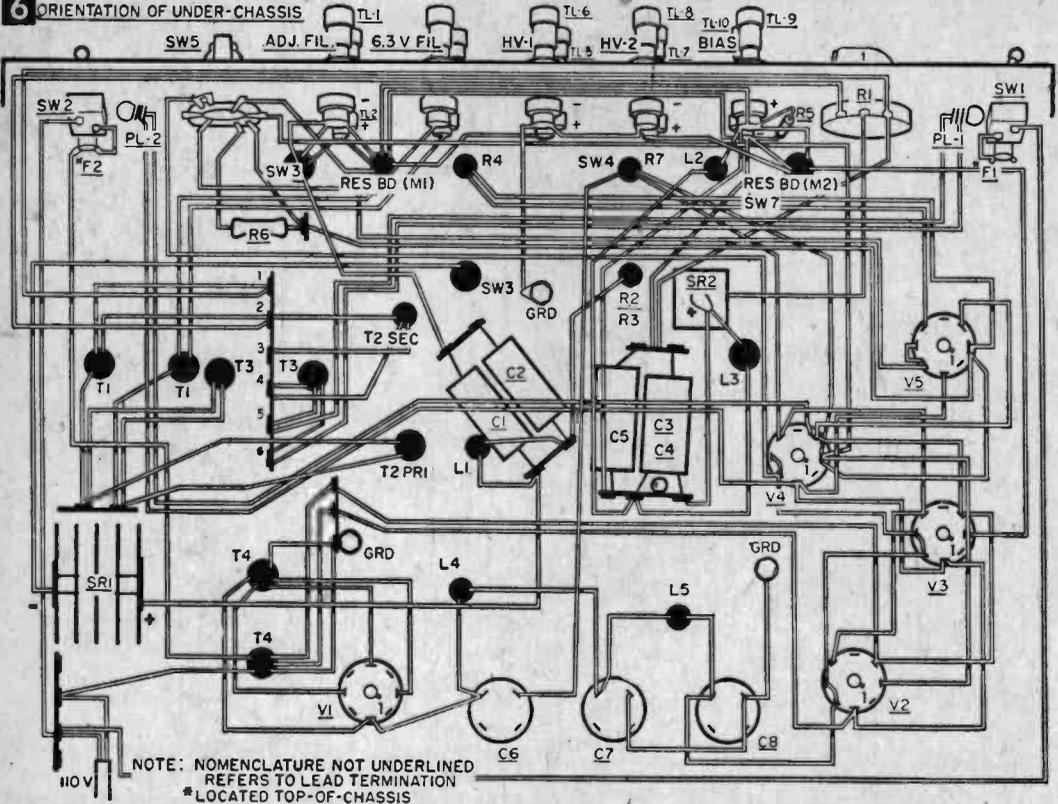

View of rear of completed unit.

MATERIALS LIST—EXPERIMENTER'S POWER SUPPLY

- |  |  |
|--|--|
| R1—2500 ohm, 4 watt potentiometer      | L2, L3—20 Hy at 15 ma. (Stancor C-1515)  |
| R2—20 ohm, 25 watt, wire wound         | L4, L5—2 Hy at 250 ma. (Stancor C-2991)  |
| R3—60 ohm, 100 watt rheostat           | S1, S2, S4—SPST toggle switches  |
| R4, R7—70K 4 watt potentiometer        | S3—4 pole, 9 position rotary switches (Mallory 1341L)                                |
| R5—5 megohm, 1/2 watt                  | S5—2 pole, 3 position rotary switch (Mallory 3223J)                                  |
| R6—2500 ohm, 5 watt wire wound         | S6, S7—3 pole, 7 position rotary switches (Mallory 1331L)                            |
| R8—12,000 ohm, 1 watt, 1%              | V1—5U4G  |
| R9—60,000 ohm, 1 watt, 1%              | V2, V3, V4, V5—6L6 (see text)  |
| R10—120,000 ohm, 1 watt, 1%            | PL1, PL2—6.3 v. pilot lights   |
| R11—1200 ohm, 1 watt, 1%               | F1—1/4 amp. Littelfuse   |
| R12—1.45 ohm, 1%                       | F2—2 amp. Littelfuse   |
| R13—3.20 ohm, 1%                       | SR1—200 ma. selenium rectifier   |
| R14—6,000 ohm, 1 watt, 1%              | SR2—20 ma. selenium rectifier  |
| R15—50,000 ohm, 1 watt, 1%             | M1, M2—5 ma. meter (see text)  |
| R16—100,000 ohm, 1 watt, 1%            | T1—Sec: 6.3 v. at 2 A; 25 v. at 1 amp.   |
| R17—275 ohm, 1%                        | T2—Sec: 18 v., tapped at 6 v. and 12 v. ("Tri-Volt" Bell transformer)                |
| R18—.72 ohm, 1%                        | T3—Sec: 6.3 v. at 1.2 amp. (Merit P-3074)  |
| R19—1.71 ohm, 1%                       | T4—Sec: 400-0-400 v. at 200 ma., 5 v. at 1 amp., 6.3 v. at 5 amp. (Thordarson 24R07) |
| R20—4.36 ohm, 1%                       | Chassis and Cabinet (see text)   |
| R21—5,000 ohm, 1 watt, 1%              | Knobs, binding posts, pilot light holders, etc.                                      |
| C1, C2—50 mf., 50 v., electrolytic     |  |
| C3, C4—15 mf., 30 v., electrolytic     |  |
| C5—30 mf., 30 v., electrolytic         |  |
| C6, C7, C8—8 mf., 500 v., electrolytic |  |
| L1—2 Hy at 200 ma. (Stancor C-2325)    |  |

also be reduced to a value as low as .5 megohm (which will cause a higher "bleeder" current, thus reducing the capacity of the supply) if it is felt that little, if any current will be drawn from the bias supply.

The values for resistors R8 through R21 will depend upon the internal resistance of the meters M1 and M2 which you use. The values given in the Materials List for R8 through R21 were calculated for the meters that we used. Formulas for determining these values are:

$R = \frac{1000 \times E}{I}$ , where R is the size of the unknown series resistor in ohms, E is the upper limit of the desired voltage range, and I is the full scale deflection (in ma.) of the meter; and

$R = \frac{i \times r}{I}$ , where R is the size of the unknown shunt resistor in ohms, i is the full scale deflection (in ma.) of the meter, r is the resistance of the meter, and I is the upper limit of the desired current range (in ma.).

**Construction.** The circuit components required for this power supply are inexpensive and readily available; parts mentioned by manufacturer's name and model numbers in the Materials List are ideally suited for use with the unit, but substitutions of equivalent parts and values can and should be made at will to keep the unit's cost as low as possible. For example, a single 100-ohm, 25-watt rheostat would be the ideal component to use for d-c filament control, but we had R2 and R3 on hand and they work quite satisfactorily. Filament transformer T1 is a surplus item, but any 25 v. transformer could have been used, and the second 6.3 volt supply furnished either by paralleling T3 or providing an additional 6.3 volt transformer, depending on current needs. The 5 ma. meters used were also on hand, but 1 ma. meters would have been better suited to the applications. Since the 5 ma. meters draw appreciable current, the bias scales were cali-

brated to read what the voltage will be with the meters out of the circuit, since it was contemplated that no current would be drawn from the bias supply and that the meters would be used for other purposes during tests.

Parts placement on the chassis is of little importance except that heavy components should be placed near the edge of the chassis for better support. The shunts for the meters are mounted on a plastic plate which is then mounted on the meter terminals. This saves space, wiring, and

simplifies meter removal if such removal should prove necessary.


The chassis and panel layout are planned together and, whenever possible, parts on the chassis should be placed reasonably close to related controls on the panel. We used a 3 x 11 x 17-in. chassis in a 9 x 12 x 18-in. cabinet, but you may want to use units of slightly different size depending upon what you have available in your parts box.

Panel arrangements are often overlooked when designing equipment. Symmetrical arrangements (Fig. 2) not only look well, but when well-planned are also logical; that is, controls related to each other (or to meters, jacks, etc.) are placed together. Controls which are used the most should have the greatest clearance for fingers, and all controls should be located reasonably clear of the high voltage terminals. With large posts mounted, wire according to the schematic and pictorial wiring diagrams (Figs. 3, 4, 5 and 6) and your unit's ready for use.


The use of decal letters, dials and symbols (as in Fig. 1) not only improve the appearance of the panel, but also make the usage simpler and more efficient.

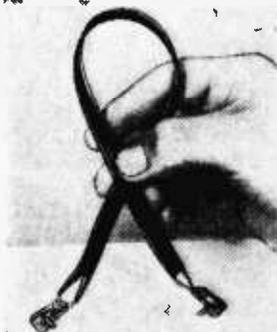**Use TV Lead-in for Radio Lead-in**

• Odd pieces of twin TV lead-in or transmission lines may be used as shown in photo at right for window lead-in cables for radios. Attach a couple of clips such as used on dry batteries to the two ends of wire of the twin line to complete the job.—H. L.



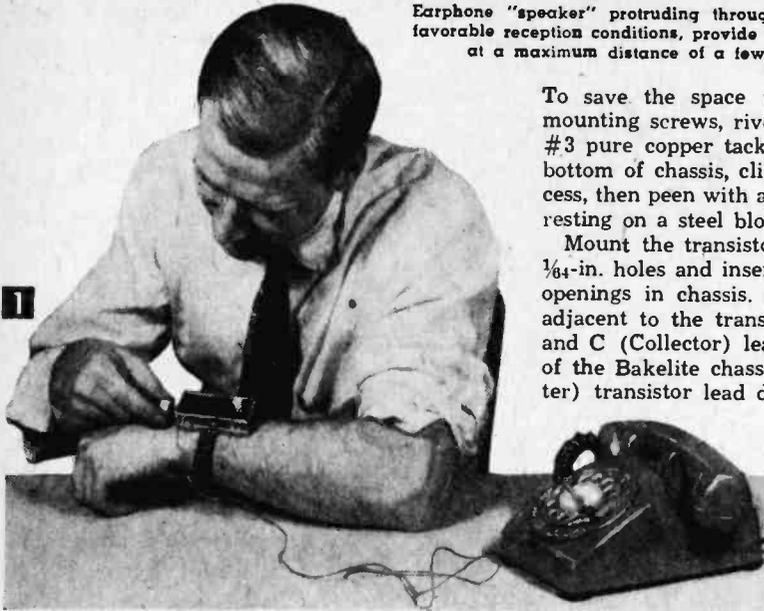Earphone "speaker" protruding through plastic case will, under favorable reception conditions, provide enough volume for listening at a maximum distance of a few feet, as shown here.



To save the space taken up by conventional mounting screws, rivet clips to the chassis with #3 pure copper tacks. Insert the tack through bottom of chassis, clip off all but  $\frac{1}{16}$  of the excess, then peen with a small hammer with chassis resting on a steel block or anvil-vice.

Mount the transistor, Fig. 2, by drilling three  $\frac{1}{64}$ -in. holes and inserting the leads through the openings in chassis. Drill two additional holes adjacent to the transistor and thread B (base) and C (Collector) leads of transistor to topside of the Bakelite chassis plate. Run the E (emitter) transistor lead directly to the plus battery clip and solder (Fig. 2). Make small loops with tweezers in the transistor B and C pigtail leads; these loops form tiny lugs to which the diode is soldered to B and one of the earphone leads to C.

When soldering the transistor and diode, be sure to push a wad of wet cleansing tissue against the soldering iron so heat from the soldering iron is not transmitted into these delicate parts.


Down to an absolute minimum, the cabinet dimensions for this set are a minute  $1\frac{1}{4} \times 3$  inches


# Transistor Wrist Radio Uses Earphone "Speaker"

**I**N ORDER to make this little wrist radio easy-to-construct, no printed circuits, special jeweler-made parts or other gimmicks are used. A hearing aid phone installed in the case serves as a speaker of limited range (see Fig. 1). In localities where reception is weak, the removable hearing aid phone may be taken out of the set and used as an earphone. The set dimensions for this self-contained, transistor radio are the absolute minimum for a tuneable set which uses parts available from any radio supply house.

The radio case is a transparent  $\frac{3}{4} \times 1\frac{1}{4} \times 3$  in. plastic trinket box. Cut a  $1\frac{1}{8} \times 2\frac{7}{8}$  in. plastic chassis from thin Bakelite or fiber to make a snug fit inside the case. This plastic plate provides a rigid mounting for the transistor and battery clips and allows you to complete all wiring before mounting the finished radio in the case.

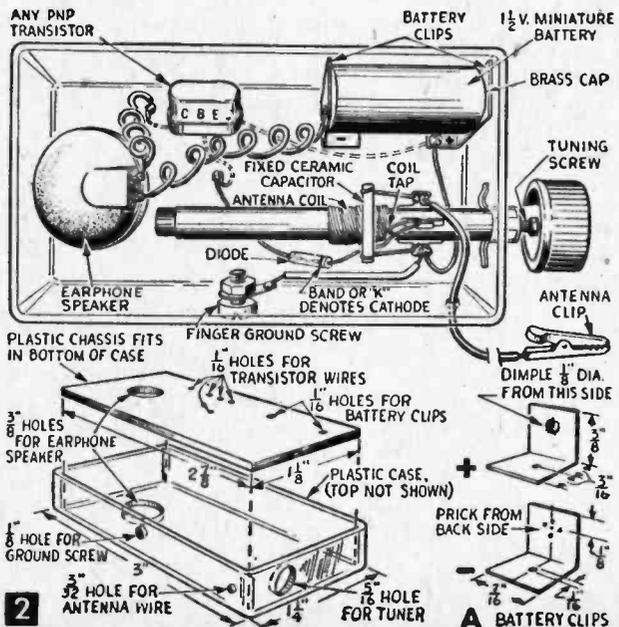Form the battery clips from small tin strips bent to L-shape as in Fig. 2A.



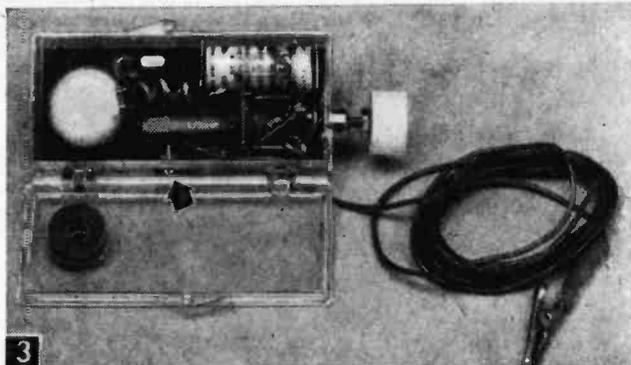

3 Touching head of machine screw (see arrow) greatly increases the volume of this miniature set.

The tuner is a ferrite slug-tuned loop antenna coil, such as is used for regular superhet radios. Unsolder the outside coil lead from its terminal lug and unwind the coil until 21-inches of wire have been removed. At this point, carefully scrape away the cotton insulation, form a tiny loop or twist for the tap, then rewind the wire and resolder to the lug. The small loop is the tap point for connecting the cathode (or banded) end of the diode detector. Some loops are now provided with a blank lug. This lug may be used to terminate the tap lead, thus insuring a rigid terminal point.

A fixed ceramic capacitor connected across the loop determines the set's tuning range. To tune from 1500 to about 880 kc., use a 100 mmf. capacitor. Use a 270 mmf. capacitor to tune from 880 to 550 kc. Attach capacitor to coil before mounting coil in plastic case, as it might be burned by iron working in close quarters. Also connect the antenna and ground leads to the coil lugs at this time.


Note that the tuning coil is mounted in the end of the plastic box (Fig. 3). A snap-mount clip on the end of the coil causes the coil to lock in place when pushed into the 1/16-in. hole drilled in the end of the case. Always push from the end of the coil and never apply pressure to the coil lugs as they will break off.

A standard miniature magnetic earphone (crystal types won't work) is inserted through a 3/8-in. hole drilled through both the Bakelite chassis and plastic case. (You can set aside the plug-in cord provided with the earset for future use.) Make the connection to the earphone "speaker" with small escutcheon pins or brads (your local hardware store has them). If pins are too long, clip off excess metal with wire cutters. Do not solder leads to pins while in phone.

To make the larger holes in the case, for the earphone and tuning coil, first drill small holes through the plastic; then enlarge these with a burring reamer. These inexpensive hand reamers are one of the few tools which will drill a smooth, even hole in plastic, to the exact size required. The 1/8 through 1/2-in. size, available from hardware stores, is ideal for radio work.

MATERIALS LIST—TRANSISTOR WRIST RADIO

Amt.	Description
1	plastic box, 3/4 x 1 1/4 x 3 in.
1	Bakelite chassis plate, 1/16 in. thick x 1 1/8 x 2 7/8 in.
1	Ferrite adjustable screw antenna coil (Tuner Ferri-Loopstick 51C036)
1	100 mmf. ceramic capacitor (to tune 1500 to 880 kc.)
	OR
1	270 mmf. ceramic capacitor (to tune 880 to 550 kc.)
1	Diode detector (any germanium general purpose type)
1	Transistor (any PNP inexpensive type)
1	Magnetic type earphone (1500 to 10,000 ohms. Do not confuse with crystal phones of similar appearance)
	Miscellaneous hardware—see text

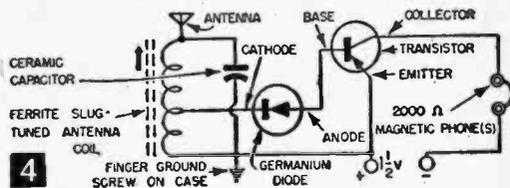

4

Drill a 1/16-in. hole through the side of the plastic case for the flexible antenna lead. Attach a small battery clip to the antenna wire for signal pickup. When using the radio, you can attach this clip to the finger stop of your dial phone (Fig. 1) or any metal part of a rural phone will do, too. If the direct connection with a phone overloads the set and makes for very broad tuning, attach the clip to a pie tin or piece of aluminum cooking foil and set the phone on the metal plate. A water pipe, lamp fixture or the like may also make a good antenna.

In some localities, if the signal is weak, you can increase it 100% by using the human body as a counterpoise antenna (ground). Note that a binding head machine screw (see arrow in Fig. 3) has been attached to the side of the case. A lead connects from this screw to the ground-side lug of the tuning coil. Touching this screw with your thumb or finger will make the volume zoom. You'll find, in fact, that the pressure applied to the screw will vary the volume. So relaxing the tension of your touch will retard the volume without turning dials.

To secure the earphone in the case without damaging it, while still allowing it to be easily removed, we merely cemented a sponge rubber grommet inside the cover of the plastic case (Fig. 3). Of course, a piece of thick felt will also serve as a suitable retainer.

This radio operates on a single 1 1/2 volt transistor hearing aid battery costing about 15¢. Any cell measuring 7/16 in. diameter and 1 1/8 in. long will do. Typical batteries available from any local hearing aid dealer are Eveready #E340E, Zenith N, and Ray-O-Vac #716. No switch is provided . . . nor needed. A strip of adhesive or Scotch cellophane tape is wound around the cell and joined with a tab. To remove the cell, merely pull on the tape tab, and battery comes out easily.—THOMAS A. BLANCHARD.

# Battery Charger

## for Photo-Flash and Flashlight Cells

**P**HOTOGRAPHERS who use flash bulbs will find they can prolong the life of battery cells by giving them a boost with this charger after about every 30 to 40 shots. Also of value to those who use flashlights constantly, this charger can accommodate three sizes of cells—singly or in combination. Naturally, a single cell is recharged more quickly, or in about one to three minutes, while with three cells in the clips it may take about three times as long.

To build, first fit milliammeter and wire-wound potentiometer, used as a variable resistance, to the front panel of a gray-finished utility cabinet (Figs. 2 and 3). Some meters use small screws and nuts around the front rim but the one illustrated has a U supporting clip with insulating washers that fit over meter terminals for clamping. File a section out of the lower rim of the cabinet (Fig. 2) for potentiometer clearance. Next, attach the filament transformer to the cabinet bottom with screws and nuts and bring the line cord in through a rubber grommet. Insert the S. P. switch and fix it with the locknut (Fig. 3). Attach rubber feet to the underside of the cabinet with 4-40 screws and nuts.


Make a terminal board from  $\frac{3}{16}$ -in. clear plastic or Bakelite and also cell terminals of brass or phosphor bronze strips and clips (Fig. 4) which attach to the board with 4-40 x  $\frac{3}{16}$ -in. screws in



FILE TO CLEAR  
POTENTIOMETER

Variable resistor has been mounted to the front cover and meter is being installed. Note curve filed in case for clearance.

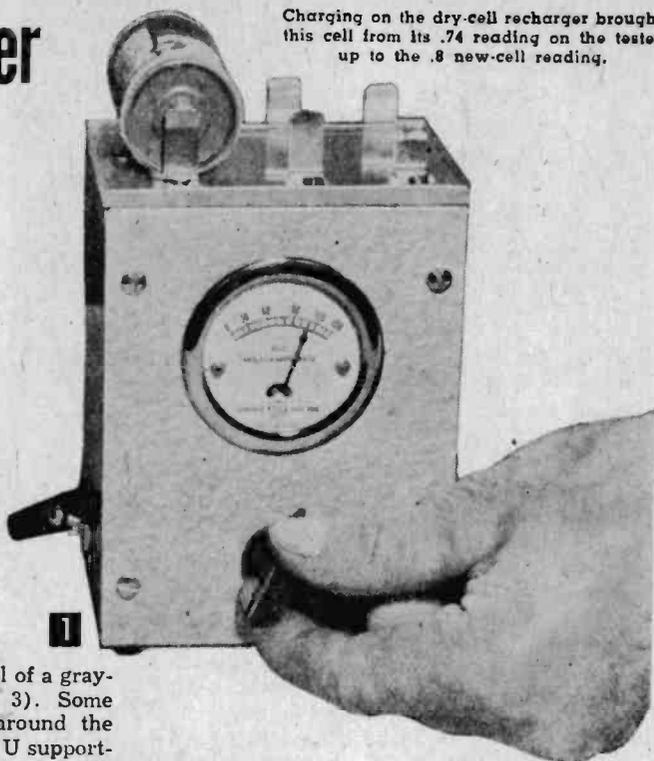
Charging on the dry-cell recharger brought this cell from its .74 reading on the tester up to the .8 new-cell reading.



tapped holes. These short screws will not go entirely through the plastic to ground to the metal box. Attach a plastic-insulated stranded #24 gage wire lead at an end screw at each strip assembly, then drill holes to pass the wires into the cabinet (Fig. 3).

The two yellow terminals usually found on rectifiers are for a-c or input connections from the transformer secondary, the red one is the positive d-c terminal and the two bridged together with a soldered jumper is the negative d-c terminal (Figs. 5 and 6). Solder the wires to the resistance control, leaving one blank, then mount the rectifier to the right side of the cabinet with a 4-40 center screw and nut. Solder all connections except those at the meter. If meter terminals are not marked plus and minus, it may be necessary to interchange them later if the meter reads down scale. Drill 24 holes in the back cover of cabinet for ventilation (Fig. 7). Attach covers with screws supplied.

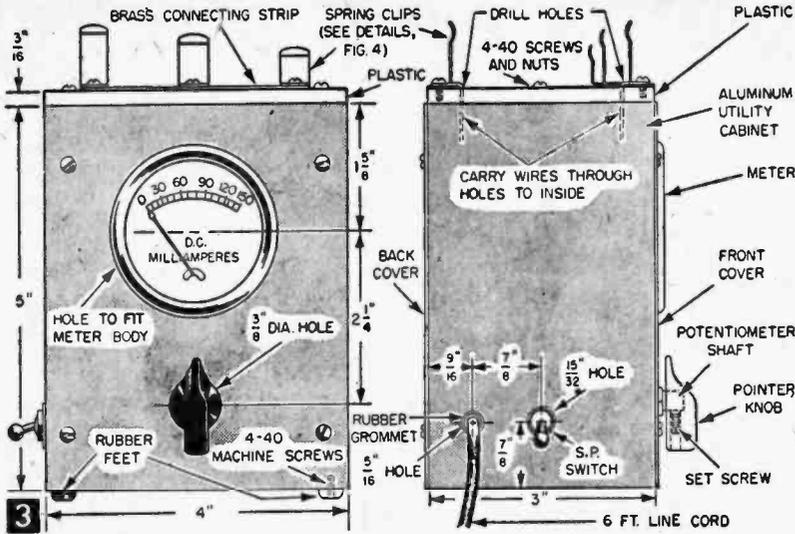After all connections are made, plug in the unit and check for d-c polarity at the cell terminals. A voltmeter with marked plus and minus terminals can be used or two leads equipped with spring clips can be attached to the clips and their ends then placed in strong salt water. Bubbles will appear around the negative lead which should go to the back strip. The other lead goes to the





handbook on pages 142-144. With this tester, a good or new cell will register about .8 on the meter. The cell we tested showed .74 (Fig. 8A). After being charged for two minutes at 120 ma. the reading was .8 (Fig. 8B). Along with two others similarly recharged, this cell has since been used intermittently for about three months and is still going strong with periodic recharging.

To illustrate that voltage is increased, we charged a cell showing but 1.27 on a


positive strip at the front. Mark the strips for quick identification. Always place cells in the clips with the positive terminals toward the front.

Although a recharged cell need not be tested after charging, you can use a low-reading d-c voltmeter, having a fairly high resistance, to test it. Or, you can use the tester described in this

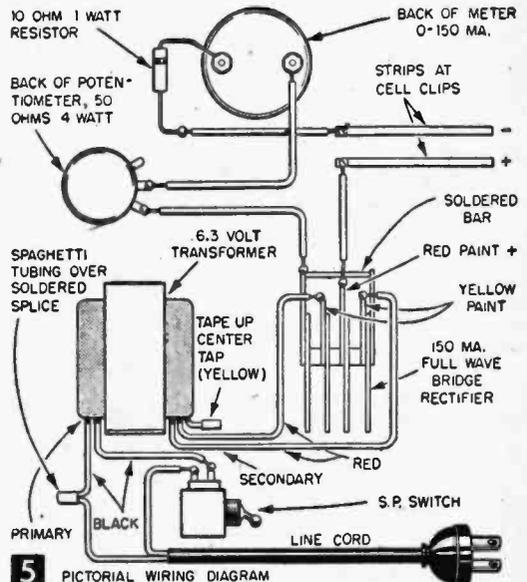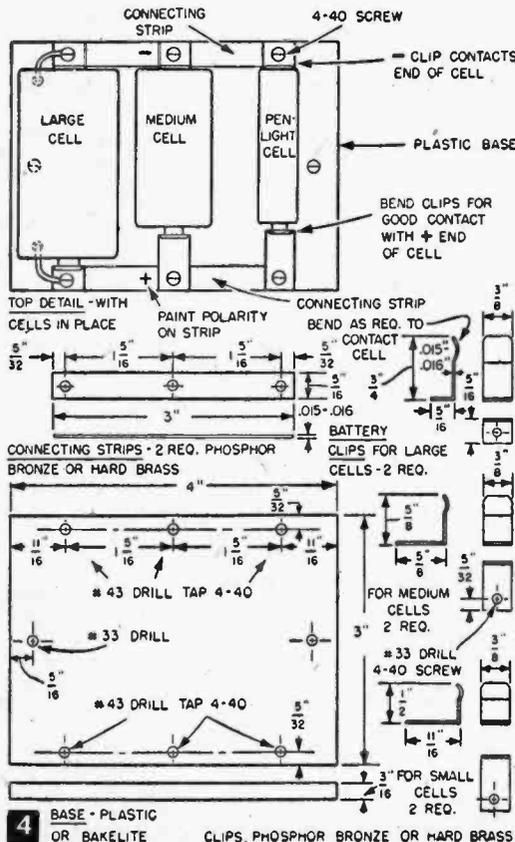
voltmeter (Fig. 9A) for five minutes at 120 ma. A second meter reading showed 1.40 (Fig. 9B). Another short boost brought the voltage up to 1.45 (Fig. 9C). While low cells can often be boosted, the voltage usually drops quickly and they are good only for emergency use. Best results are obtained by recharging for a minute



5 PICTORIAL WIRING DIAGRAM

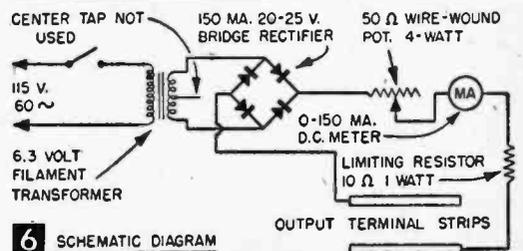

6 SCHEMATIC DIAGRAM

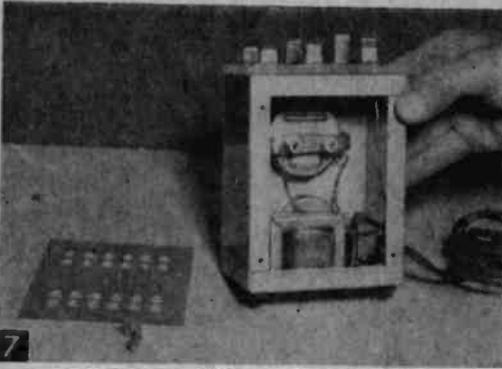

7 Wiring is complete and ventilated back is about to be installed.



8 A



B

The first tester reading on the cell being recharged in Fig. 1 was .74, above, left. Right, after the recharging, the reading jumped to .8; normal for a new cell.

#### MATERIALS LIST—DRY CELL CHARGER

Amt	Description
1	aluminum utility cabinet, hammertone gray finish, ICA 29811 5 x 4 x 3" with removable front and back covers
1	round panel meter, 0-150 d-c milliamperes Shurite #5308
1	50 ohm, 4 watt wire-wound potentiometer IRC Type WPK-50 or Clarostat 3 watt Type 58-50
1	filament transformer, 117v 60 cy. primary, 6.3v at 1.2 amp. secondary. Stancor P-6134, Merit P-3074 or any similar types, such as Triad F-14X.
1	S.P.S.T. toggle switch 3 amp. 125v
1	rubber grommet for $\frac{1}{16}$ " hole
6 ft	flat rubber line cord #18 conductors
1	attachment plug cap
4	rubber mounting feet or knobs $\frac{3}{8}$ " O.D. Use type designed for machine screws, such as Allied Radio 44N763
1	pointer type knob for $\frac{1}{4}$ " shaft
1	10 ohm 1 watt carbon resistor
	Above obtainable from electronic supply houses or Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y., or Allied Radio, 100 N. Western Ave., Chicago 80, Ill.
1	Sarkes Tarzian full-wave bridge type selenium rectifier, 4-1" x 1" plates. 150 ma. D.C. 25v rating. Model 154B. (Local supply house or Durrell Distributors, 222 Mystic Ave., Medford, Mass., \$1.95 P.P.)
1	piece clear plastic or Bakelite $\frac{1}{4}$ " x 4 x 3" (scrap from old electrical apparatus or from Forest Products Co., Inc., 131 Portland St., Cambridge, Mass. \$0.75 P.P. paid in U.S.)
1	piece hard brass or phosphor bronze about .015-.017 x $\frac{3}{16}$ x approx. 12". For strips and cell contact clips (metal supply houses or shops using such material). Misc. screws, nuts, hook-up wire, etc.


or less at 75 (size C cells)-100 (D cells) ma. and for penlight cells, one to three minutes at 30-40 ma. after each prolonged cell use. This usually can be repeated several times before chemical decomposition causes cells to become useless.

Good battery cells register about 1.5 to 1.55 on a voltmeter of high resistance, such as 20,000 per volt multimeter. When voltage reads 1.4 or so, charge to bring back to normal. If a flashlight is involved, boost cells when the light is not as bright as it should be. If recharging does not appreciably brighten the light, the cells probably should be discarded.

In general, the charging time and current rate will depend on cell size and condition, smaller cells requiring a lower charging rate and shorter time. If there is noticeable warmth during charging, reduce rate and/or time, as internal heating is harmful to the cell.—HAROLD P. STRAND.



9 A

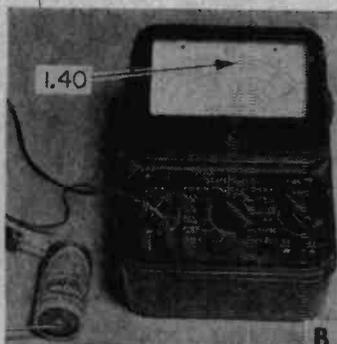

B



C

Cell first recorded 1.27, was recharged, then showed 1.4. After a second recharging period, the reading was 1.45. Usually, when a cell takes this much recharging, it will not hold the charge for very long.

# Transistorized Electronic Megaphone

Highly portable, self-contained P.A. with a 500-ft. plus range


By HAROLD P. STRAND




Weighing only four and one-half lbs., this self-powered, electronic megaphone is ideal for sportsmen or civic leaders. Under favorable conditions, it will "broadcast" up to 600 feet.

amplification. Transistors employed in an amplifier circuit allow the use of small, light batteries contained in an attached housing back of the horn (Fig. 2). It has a volume control, although raising or lowering the voice level usually serves to control the output volume. A push-button switch on the pistol grip handle is controlled by the forefinger. Holding the switch closed turns the power on from the 22½ volt battery and the 3 volt bias battery. Releasing the switch eliminates power drain when megaphone is not in use.

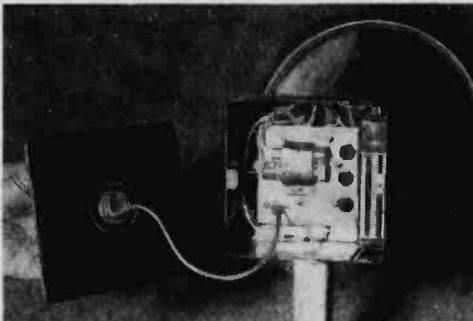Since the in-use maximum current drain at the loudest volume level is about 40-50 milliamperes from the 22½ volt battery, and about 2.5 from the 3 volt battery (used as



2 A

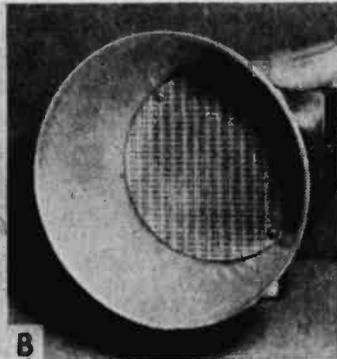


B

Fig. 2A (Left) Cover removed to show housing components (detailed in Figs. 3 and 4). Note small microphone mounted in cover plate at left, with its leads plugged into amplifier chassis. Fig. 2B (Right) Front of megaphone, showing how grille cloth mounted over wooden ring holding speaker presents neatly finished appearance.

**W**HETHER you skipper your own cabin cruiser, or are active in local civic groups which hold or sponsor 'sports events, public meetings or rallies, you'll find this highly portable, self-contained "public address" system mighty handy for long distance hollering. Come to think of it, this megaphone might be just what your wife would like to have for summoning the children for supper. It will "broadcast" intelligible speech from 500 to 600 feet, depending on weather conditions.

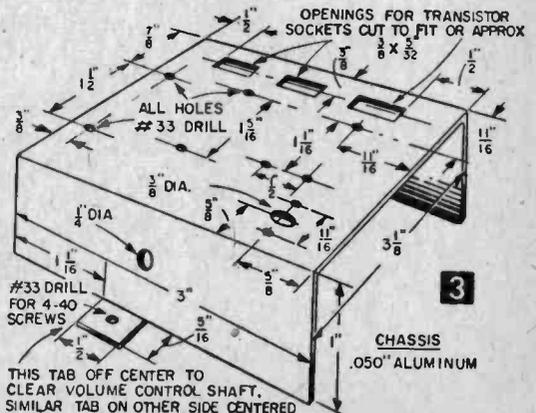This unit is designed for medium level voice



3

MATERIALS LIST—ELECTRONIC MEGAPHONE

Electronic parts listed below were supplied by Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y.

- 1 6" P.M. speaker. 2.15 oz., magnet. Oxford 6EVS 3.2 ohm voice coil or Utah equivalent, with 4-6 watts rating
- 1 Shure microphone, MC-11 controlled reluctance type, 1" diameter
- 3 transistor sockets MS-275
- 3 G. E. 2N44 transistors
- 1 RCA type phono jack and plug
- 10" shielded cable, small diameter (about 1/8" O.D.)
- 1 10,000 ohm miniature volume control VC-34
- 1 Burgess XX15 B battery, 22 1/2 volt
- 2 Burgess #Z nightlight cells
- 1 three-prong plug to fit XX15 battery
- 1 AR-109 driver transformer
- 1 AR-138 output transformer
- 1 Argonne 8 mfd 15 volt capacitor, 15v
- 1 47 ohm 1/2 watt resistor
- 1 22,000 ohm 1/2 watt resistor
- 1 1200 ohm 1/2 watt resistor
- 1 #6 solder lug or more if needed for ground conn. (see below)
- 1 Bakelite terminal strip 7 terminals, two grounded, Jones 55-C
- 2 Bakelite terminal strips 2 terminals, one grounded, Jones 51-A (Note: You can use 5 terminals on first and 1 terminal on second strip mentioned above, all lugs to be insulated and use solder lugs under chassis screws for ground connections)
- 1 miniature knob for 1/8" shaft MS-185
- 1 piece plastic grille cloth about 7 x 7"
- 1 D.P.S.T. push leaf switch, Switchcraft 1004 or Mallory 1014
- 1 speaker cone made of half-hard .032 sheet alum., riveted or with lock seam, front end rolled bead, 12 3/4" long, 9 1/2" O.D. large end, 4" O.D. small end. Robert Towne, 49 Abbott Avenue, Everett, Mass., will make them for our readers for \$7.25 P.P. in U.S., express or money order


**BAKELITE**—supplied by Forest Products Co., 131 Portland Street, Cambridge, Mass., for \$3.00 P.P. in U.S., express or money order.

- 1 pc black paper base 1/4 x 5 x 5". Cut and dress to tightly fit inside housing
- 1 pc black paper base 1/8 x 5 x 5". Cut and dress to fit on outside front of housing
- 2 pcs linen base natural finish 1/8 x 5 x 2 1/4" (handle sides)
- 1 pc paper base natural finish tubing 1 1/2" O.D., 1/16" wall, 1 7/8" long (mouthpiece)

**MISCELLANEOUS METAL AND WOOD STOCK** (Try local metal-working and cabinet shops)



- 1 pc aluminum about .050 x 3 x 5 3/4" (chassis)
- 1 pc aluminum half-hard alloy or material that can be bent but has reasonable rigidity, 1/8" x 1 3/16" x about 11 3/4" (handle frame)
- 1 pc aluminum half-hard alloy about .040-.045 x 3 1/8 x 18 1/2" (housing) can also use soft sheet steel about .034"
- 1 pc aluminum half-hard alloy 1/2 x 1/8 x 5 5/8" x about 17". Bend to form speaker U bracket support
- 1 pc hard brass or phosphor bronze about .010 x 2 3/8 x 7/8" (clip for bias battery)
- 1 pc dry maple or birch 3/4 x 4 1/2 x 4 1/2". Turn to tapered disc to fit tightly in small end of cone
- 1 pc hardwood plywood such as birch 1/4 x 7 x 7". Cut-out ring to hold speaker in cone

Misc. hook-up wire, screws, nuts, paint. Pliobond cement, etc. Note—Pure aluminum bends too easily for our purpose. What is commonly called half-hard can be formed or bent but is strong and rigid. Some trade numbers are 3003H14 half-hard, 11M14 half-hard and 5052H34 quarter-hard. Any similar type could be used where a test shows it workable for bending but as rigid as soft steel. Lightness of aluminum makes it ideal for keeping megaphone light. Usually supply houses do not sell small quantities so it has to be picked up in shops using this stock.

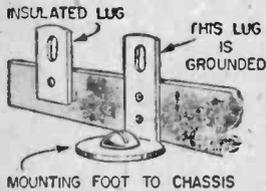

Terminal strips 55-C and 51-A have grounded lugs as shown above for connection of leads going to ground. If strips with all lugs insulated are used, simply use solder lugs under chassis screws for ground connections, as at AR-109 transformer feet.

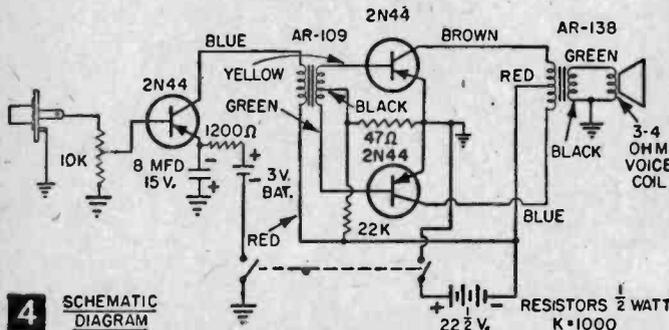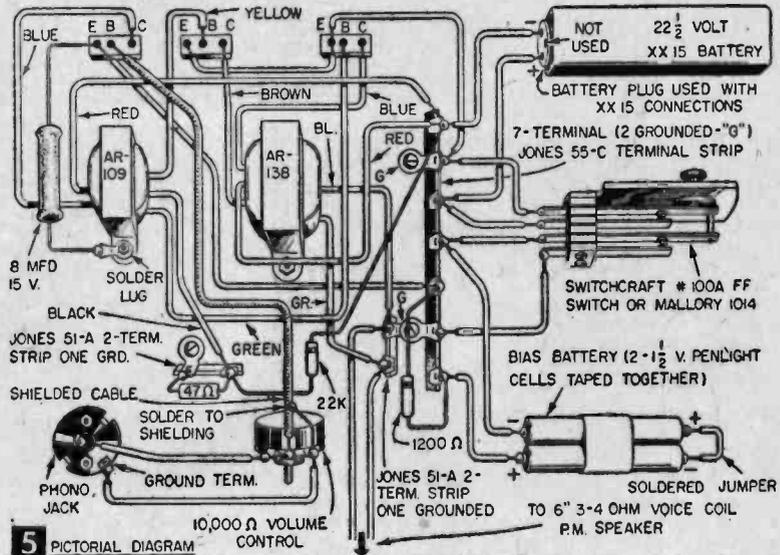bias in the emitter of the driver stage), battery life should be quite high. The Shure controlled-reluctance type microphone has an output level of -71 db below



one volt per microbar, and an impedance of 1000 ohms. It is only one inch in diameter. It is mounted in a Bakelite tube, which also serves as the mouthpiece (Fig. 2). The 6 in. permanent magnet type speaker with its 2.15 ounce Alnico magnet is fixed part way down in the cone as in Fig. 2. The three G.E. 2N44 transistors in a push-pull circuit which power






Forming the amplifier's sheet metal housing, using the rounded edge of a piece of angle iron held in the vise.

Edges of shaped housing are brought together and riveted to an aluminum plate.

rivets, and head the rivets over on the inside in countersunk holes so that the rivets will come flush.

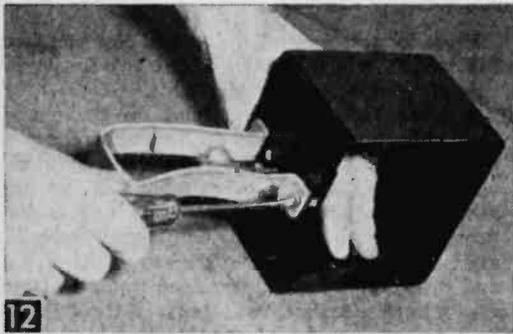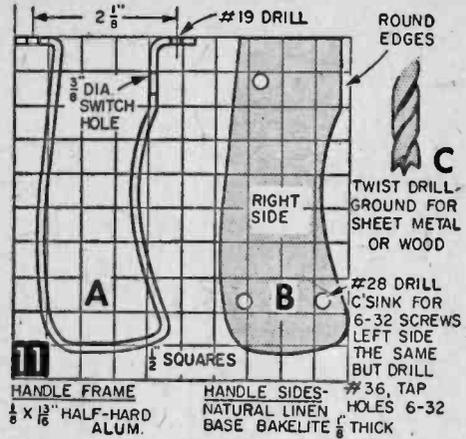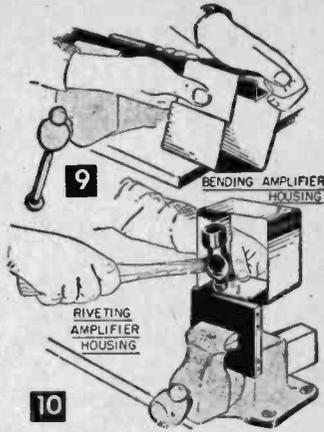To form the frame for the pistol grip handle



12 After fastening switch through its hole in handle with locknuts, attach handle frame to amplifier housing. Note that housing has been finished with primer, then black enamel lightly rubbed with steel wool.

which is of aluminum stock about 3/32 to 1/8 in. thick and soft enough to be bent, lay out the pattern (Fig. 11A) on paper with 1/2 in. squares. Then, carefully bend the aluminum stock to its proper shape over various forming pieces held in the vise.

Install the switch in its hole with locknuts and attach the handle frame to the housing, using two 8-32 machine screws in holes drilled and tapped into the housing and inside plate (Fig. 12).



Because the aluminum cone could be difficult for an amateur to make we recommend you purchase one as indicated in the materials list, or have your local tinsmith make one up for you (Fig. 1). These commercial ones have a neat rolled bead at the front end which helps to stiffen the cone.


To assemble the speaker, you'll need a hardwood disc which fits tightly in the 4 in. end of the cone (Fig. 14). Turn this from maple in any woodturning lathe, giving it a taper to properly fit and come flush with the end. Insert it from the large end of the cone, tapping it down into place. Fasten it with four 3/8 or 1/2 in. #7 flat-head brass wood screws, inserted through the aluminum and into the wood disc in holes spaced and drilled equally around the circumference.

Pliobond cement on the disc edges will further insure its remaining in place.

Figure 14 shows how a piece of 1/4 in. thick black Bakelite, which was carefully cut and fitted to the inside dimensions of the housing as in Fig. 8E, is attached to the maple disc in the end of the cone, using four 3/4 in. #9 roundhead wood screws. Holes for these screws must also be drilled in the maple block so you won't split the wood. Next fit the Bakelite panel into the amplifier housing until it is flush with the edge, and use 4-40 machine screws in drilled and tapped holes to secure it.

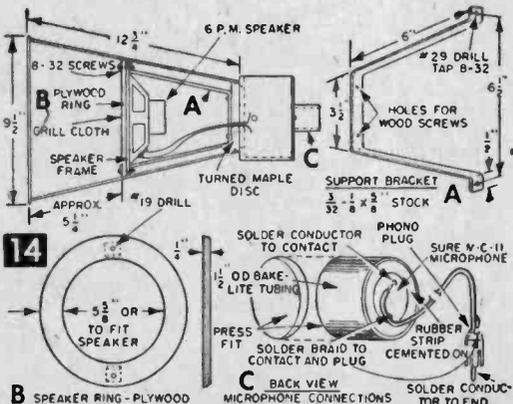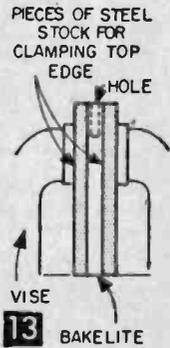Make sure when doing this fitting the switch button is on side of housing nearest speaker cone, and tabs on housing are on the end of housing away from cone. When drilling and tapping Bakelite in its edge, by the way, clamp the Bakelite in a vise so the tap will not tend to split the material, since it splits rather easily in end grain. You can drill the required holes in the metal with



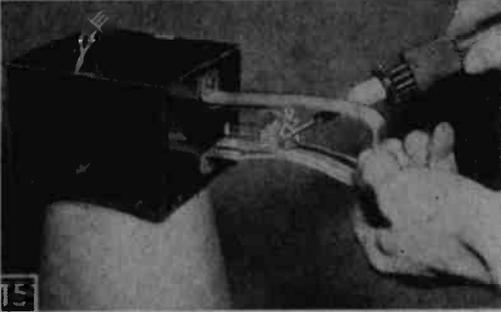

Soldering connections to switch terminals in handle of megaphone—see Fig. 5.

Bakelite in place, but only allow drill enough of a depression in the Bakelite to mark where to drill for tapping. Use a #33 drill through the metal and then change to a #43 drill for making the holes in the piece of Bakelite. Then use a 4-40 tap in each drilled hole.

Before fitting the amplifier to the Bakelite piece you have already attached to the cone, first drill a #29 drill hole through the Bakelite and also the wood disc in the cone just off the center (Fig. 8E), for the speaker wires. Pass the speaker leads through this hole and then fit the amplifier chassis against the Bakelite piece and secure it (Figs. 2A and 3), making sure the control knob shaft is allowed to project through the hole for it drilled in the side of the housing. The chassis should also be so located in the housing so that the 22½ volt XX15 battery will fit between the chassis and the housing (Fig. 2A) when wedged with a folded piece of cardboard.

The switch contact wires are brought through their hole (Fig. 8C) in bottom of the case, and connected as shown in Fig. 5 and Fig. 15. Solder a plug to the two leads that go to the battery and make a knot in one of them which will easily identify the plus lead for you. Examination of the way the three-prong plug fits in the battery quickly shows which terminal of the plug is plus.

**Mounting the Speaker.**


Figure 14 shows how the speaker is held part way down in the cone by mounting it to a support that is bent up from any light metal, as in Fig. 14A. Since the size of the cone and the speaker size may vary a little, the exact length of the bracket is not given.

But it should be such that the screws used to secure the speaker ring (Fig. 14) will pull the ring down tightly in the taper of the cone, coming to rest with the speaker against the support at two of its mounting holes, Fig. 16 shows the bracket support attached to the wood disc at the base of the cone. Note that the leads have already been soldered to the speaker terminals.




Note speaker supporting U-bracket attached to wood disc at far end of horn. Speaker will mount against this bracket and grille cloth-covered wood ring at left will cover front of speaker. Note connected speaker leads going back through wood disc to amplifier.

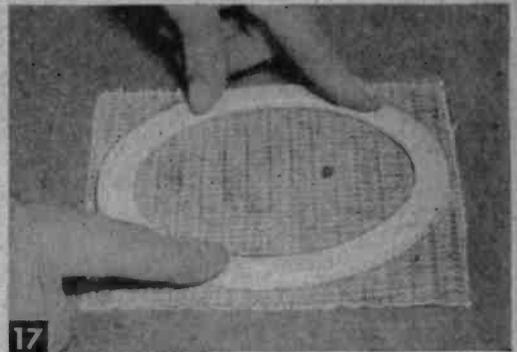
After jigsawing out the plywood ring which fits over the front of the speaker (Fig. 14), cement plastic grille cloth to the ring with Pliobond cement (Fig. 17). After this dries, trim off cloth around the ring with scissors. Make two holes in the ring for the two 8-32 machine screws that turn into the ends of the speaker support in tapped holes.



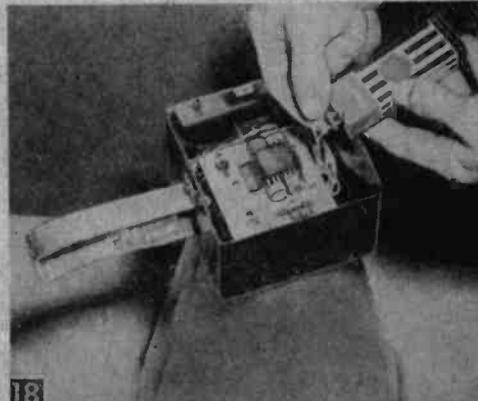Pressing plywood ring, coated with Pliobond cement down firmly onto square of grille cloth.



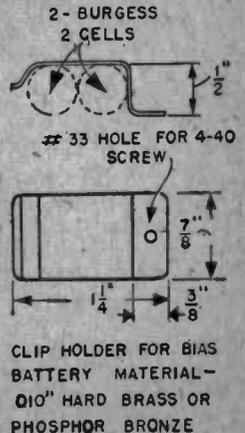Installing 22½ volt B-battery in amplifier housing. See Fig. 2A for battery position in housing.




You can now connect the 22½ volt battery and place it between the chassis and the housing (Fig. 18) using folded cardboard to wedge it tightly in place. You can also place the transistors in their sockets now.

**Mounting the Mike.** The microphone mounts in a rubber strip which in turn is cemented into a 1½ in. diameter Bakelite tubing mouthpiece (Fig. 2A, 14A and C, and 19). The mouthpiece then fits tightly in a hole made in the front Bakelite housing cover, using a fly cutter in the drill press. Before installing mike in the mouthpiece tube, connect a 6 in. length of shielded flexible wire to the terminals and a phonoplug to the other end (Fig. 2A and 14C). Make up the strip into which the mike will mount from the type of sponge rubber used to seal car trunks and doors; it is sold in auto supply stores. This rubber should be about ¼ in. thick, ½ in. wide and long enough to be formed around the mike and have its ends meet. Apply Pliobond cement to outside edge of mike and one surface of the rubber. Then, after a few seconds wrap the piece around the mike, tie with string and let dry for about an hour. Then untie string, apply cement to outside surface of rubber, and press the assembly of mike and rubber in mouthpiece tube until about flush with the end (Fig. 20).

Attach the 3-volt bias battery, consisting of two penlight cells in series, to the chassis under a spring clip bent up from thin hard brass or phosphor bronze (Fig. 18A). The leads were soldered to the battery terminals (Fig. 5). To enclose the megaphone handle, make up Bakelite sides as shown in Fig. 11C, and attach to handle frame with screws and Pliobond cement.

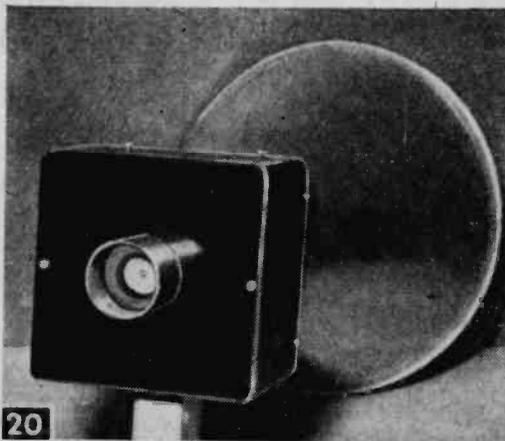**Using the Megaphone.** If you test the megaphone indoors in a small room, you may find a whistle will develop when you press the push-button and try to talk. This is because sound bounces from walls and enters the microphone to



20 Mouthpiece with mike and its rubber ring inserted, mounted to Bakelite panel.

set up a series of oscillations—a common occurrence where a high-gain amplifier, a mike and a speaker are in close proximity to each other. When used outdoors or in large areas, however, this sound has less chance to rebound and there should be little tendency to whistle.


You can use the volume control setting to keep the gain down enough to eliminate whistle when testing indoors. Or, if you want to cut down any tendencies to whistle, line the space inside the cone back of the speaker, and the interior of the box housing the amplifier, with felt. Also cement a piece of felt to the inside surface of the cover. I used a standard dress goods or fabric store type of felt and Permatite Liquid Adhesive R-6229 (from Sears).

For longer battery life, you can place a second XX15 battery in the housing and connect it in parallel with the other one. Simply splice on two leads from the original two battery wires and connect a plug to them, making connections so that the batteries will be plus to plus and minus to minus or parallel. You'll get the same 22½ volts but double the current capacity. The second battery can be taped in place where convenient in the roomy housing.

When using the megaphone, talk close to the mike, even placing the lips directly up to the mouthpiece. This will give maximum volume and also help to prevent stray sounds from entering to cause undesirable oscillations. Avoid taking deep breaths through the mouth while it is close to the mike but rather breathe through the nose. With a little practice, you'll be able to transmit intelligible speech under good atmospheric conditions for distances of 500 to 600 feet, depending on the direction and force of the wind.
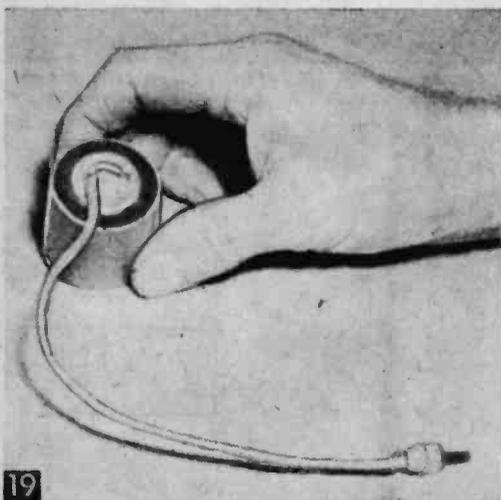
### Draftsman's Tape Holds Tight

• Draftsman's tape makes an excellent "third hand" to hold electronic components together during assembly or soldering. Due to its high insulation, the tape can be left on permanently, or can be peeled off easily.—J. A. McROBERTS.



19 Microphone mounted in insulating rubber ring, which in turn is fitted into Bakelite tubing mouthpiece.

# Fun with a One-Tube ELECTRONIC ORGAN

**T**HIS novel electronic organ employs a simple tuned oscillator circuit, much like that employed in elaborate electronic instruments. However, where the real organ uses many individual oscillators as well as mechanical devices for its effects, the little organ described here limits its scope to a simple one-tube circuit. Yet with its simplicity and limitations, this organ produces musical effects ranging from tuba-to fife-like tones. In the middle ranges, it sounds much like any reed type organ. The organ keyboard consists of 20 chromatic notes. These may be played in a choice of four ranges from treble to bass. The tap-switch on the keyboard functions much like the "stops" on a conventional organ.

The heart of the instrument is the oscillator. A small metal chassis  $3\frac{3}{4}$  in. long,  $3\frac{1}{4}$  in. wide, and  $1\frac{1}{2}$  in. high is made to general design shown in illustrations. However, oscillator can be wired up on a wooden base, if desired. Our pictorial wiring plans show oscillator details so that assembly may be left to individual choice. The oscillator employs a type 117L7/M7GT tube. This tube is really two tubes in one glass envelope: a power pentode and a half-wave rectifier. And since it has a 117-volt filament, no resistor or transformer is needed to lower "heater" voltage. The 117L7/M7GT contributes much to the circuit's simplicity.


A 6-post terminal strip on front of chassis provides means for connecting PM speaker, keyboard, and range control. Since the oscillator is a complete assembly in itself, overall construc-



Completed electronic organ consists of: left, 20-key console with control providing 4 tone ranges; center, 5 in. PM speaker; and right, 1-tube oscillator.

It plays tunes with tone effects ranging from a reed organ to a bass tuba

By THOMAS A. BLANCHARD

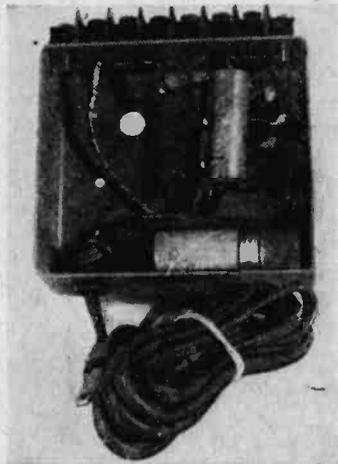



Bottom view of oscillator-amplifier which is heart of organ. Lower right, 20 mf. condenser; center, .05 mf. condenser, with tube socket below it. Tube and input transformer are located on top of chassis.

tion of organ is greatly simplified. After obtaining components given in materials list, wire according to picture plan.

With the oscillator completed, test it by connecting a .00035 mfd. fixed mica condenser across terminals #1 and 2. Then attach a 470,000 ohm,  $\frac{1}{2}$  watt resistor across terminals #3 and 4. Finally attach a PM speaker (through a matching PM output transformer) to terminals #5 and 6. Plug cord into power line and allow oscillator to warm up. After warming up, oscillator should produce a high whistle. If not, check wiring carefully. If everything is in order, reverse primary connections of 3:1 ratio audio input transformer. This will place primary and secondary polarity in proper relation and unit will then oscillate.

Now if the 470,000 ohm resistor is replaced with a somewhat higher value, a different tone will be heard.

Therefore, since each change in grid return resistance produces a different tone, a string of resistors, each with a "tuned" value, will reproduce all tones in the musical scale. The keyboard, therefore, is actually nothing but a series of switches—each black and white key closing the circuit along a series resistance network, and causing a different resistance to be placed between grid and ground of oscillator tube.

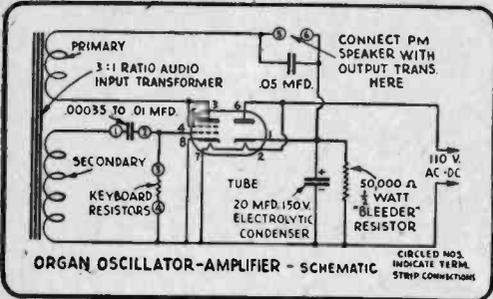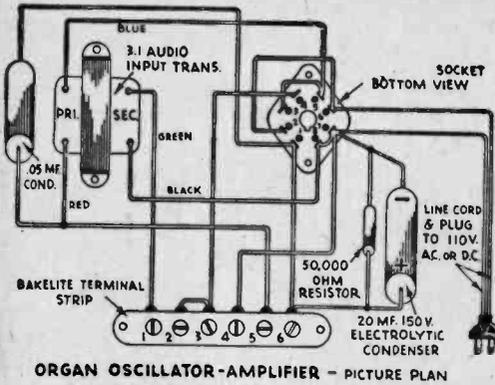

To save time, you can use well-seasoned white pine Xylophone keyboard (see drawings) in place of piano-type keyboard. Use only dry material unless you want organ to be out of tune or worse! Arrange 20 nickled or brass thumbtacks in the manner shown. Under each tack secure resistor leads. It is very important that all connections are solid! Inspect tacks to be sure they are not tarnish-proofed with clear lacquer. If so, soak them in acetone to remove this film. Be certain that keyboard resistors are exactly the values given in Table A, and that no open or poor connections exist anywhere between R1 and R20.

With Xylophone keyboard finished, solder length of wire to free end of R20. Connect this lead to terminal #3 on oscillator. Run another length of flexible insulated wire from terminal #4 to a radio test probe. With the .00035 mfd. condenser still across terminals #1 and #2, you are ready to go. Touch each tack head with the probe tip and you get an electronically-produced note corresponding to those given on the keyboard diagram. Now shut off oscillator and change .00035 mfd. condenser to a larger value: .0006, .001 or .01 mfd. The .01 mfd. will produce very low tones; .0006 and .001 mid-ranges.

Now with a working knowledge of the gadget, you can build up a regular type keyboard, if you wish, entirely from scratch, or get a head-start by purchasing a 20-note toy piano for about \$3.00. In the latter case, remove bells or chimes and revise key actions into individual switches in the following manner. There is usually enough room inside the average toy piano to include

oscillator and a small PM speaker, making the organ completely self contained. You'll find that key actions in most toy pianos, as well as real instruments, work on knife-edge pivot system (see "exploded" plan of keyboard). Base of keyboard consists of two pieces of well-seasoned 1/4 in. plywood.

Each of these pieces measures 12 in. long by 4 3/4 in. wide. Take one panel and rip-saw into two pieces making cut 2 3/4 in. from the edge to give you one panel 2 3/4 x 12 in. and another 2 x 12 in. With brads and glue, attach 2 3/4 x 12 in. panel to 12 x 4 3/4 in. sub-base. The knife-edge pivot strip is placed against edge of 2 3/4 in. panel, and sandwiched-in by the remaining strip of 12 x 12 in. plywood which is also glued and nailed to sub-base.


The knife-edge strip is a 12 in. length of 3/8 in. steel band such as is used to secure shipping containers. If you can't secure one, use a 12 in. hacksaw blade or have a tinsmith cut a strip of 20-gage sheet metal to 12 x 3/8 in. Next cut out keys to dimensions on a jig saw. Use as narrow a saw blade as possible to slot each key on the

TABLE A—ONE-TUBE ELECTRONIC ORGAN


No.	Req'd.	Description
2	68,000 ohm, resistors *	(R1, R2)
3	56,000 ohm, resistors	(R3, R4, R5)
1	68,000 ohm, resistor	(R6)
1	47,000 ohm, resistor	(R7)
4	39,000 ohm, resistors	(R8, R9, R10, R11)
3	33,000 ohm, resistors	(R12, R13, R14)
3	27,000 ohm, resistors	(R15, R16, R17)
2	22,000 ohm, resistors	(R18, R19)
1	470,000 ohm, resistor	(R20)
1	six-post terminal strip	
1	.0003 mfd mica capacitor	
1	.00005 mfd mica capacitor	
1	.0006 mfd mica capacitor	
1	.001 mfd mica capacitor	
1	.01 mfd mica capacitor	
1	5 position tap switch	
1	pointer knob	
1	.05 mfd 400 volt capacitor	
1	3:1 audio input transformer	(Stancor A-53)
1	tube socket (octal)	
1	117L7/M7GT tube	
1	47,000 ohm, 1/2 watt resistor	
1	20 mfd, 150 volt, electrolytic capacitor	
1	output transformer	(Stancor A-3328)
1	5" PM speaker	
1	line cord and plug	

\* Keyboard resistors R1 through R20 should be standard values, 1/2 watt size and 5% (gold band) or 10% (silver band) accuracy.

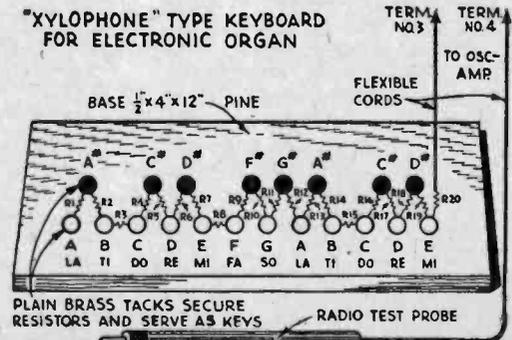
"XYLOPHONE" TYPE KEYBOARD FOR ELECTRONIC ORGAN



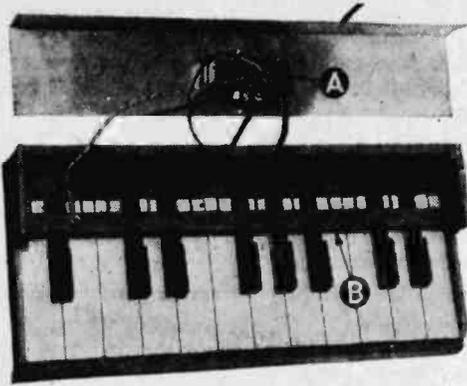PLAIN BRASS TACKS SECURE RESISTORS AND SERVE AS KEYS RADIO TEST PROBE



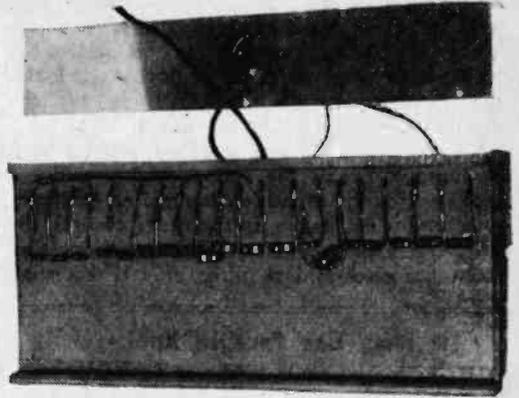
Console with aluminum cover removed. Note condensers and tone switch (A); position of contact bar (B). Keys slip under safety pin springs. Depressing key causes pin to raise and contact bar.



Bottom of keyboard showing resistors R1 to R20 soldered to projecting ends of safety-pin springs.


underside to a depth of  $\frac{1}{16}$  in. Now arrange keys on base according to positions shown in photos. You'll find the individually-notched keys will ride on the steel edge in teeter-board fashion.

With all keys in place, draw a line across rear of base  $\frac{1}{16}$  in. in from edge. At center of each key position, make a centermark on parallel guide line. Do this manually as plotting off fixed spaces will possibly result in key-springs falling in the wrong position. Obtain two cards of #2 safety pins (20 pins) and with diagonal wire-cutting pliers, clip off clasp from each. Now, at each of the 20 marks along previously plotted parallel line, drill a hole (slightly smaller than safety pin) through keyboard base. Now push

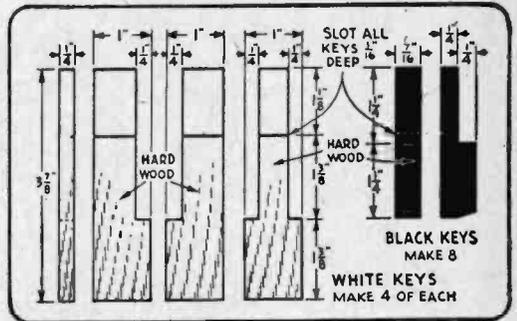


key. Now turn keyboard over and wire in the 20 resistors as shown. Projecting portions of springs serve soldering lugs.

Finish the console with front, side and rear panels tacked and glued as shown. Now cut a strip of wood 12 in. long,  $\frac{3}{4}$  in. high, and  $\frac{3}{8}$  in. thick for the contact bar. To the  $\frac{3}{8}$  in. side fasten a strip of brass, aluminum, or timplat with several brads. At a point where it won't interfere with the key action, solder length of insulated wire, or mount a soldering lug as shown. Set this bar, metal-faced side down, into the console. Position it as close to springs as possible, but without actually touching them. Now fasten

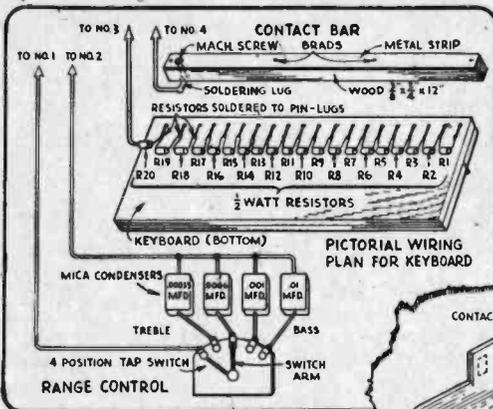

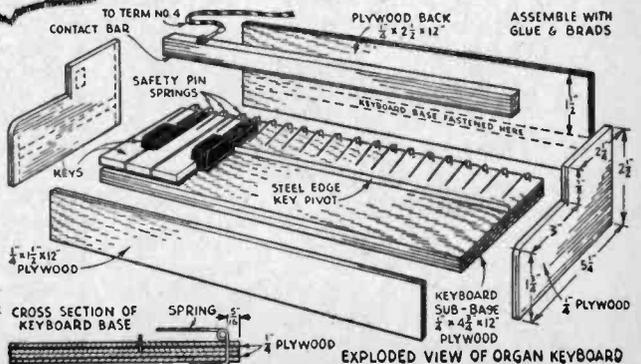a spring through each hole. Bend projecting portion of pin on underside of base down (see cross-section view in plans). With all safety pin springs in place, raise each one up and slide proper key in place. When key is depressed, it will now spring back. Align and adjust each spring so that it falls in center of respective



bar securely at each end of console with small wood screws. As each key is pressed, lever action causes individual spring to raise and contact the bar. This closes circuit and sounds that particular note. Springs may be individually adjusted by careful bending with flatnose pliers.

A metal cover consisting of a piece of light aluminum conceals the actions and provides a mounting for the 4-position tap switch and mica capacitors which make up the range control. By notching end panels of console, cover front slips into these slots and requires only three small


screws across rear top edge to secure it.

Since this organ employs but a single oscillator, it is necessary to strike only one key at a time. The natural limitations of the circuit do not permit the playing of chords, but this is, at worst, only a slight shortcoming.

However, a little practice with the device will result in rapid fingering that is not possible with any instrument other than those of electronic nature. The novel effects gained by virtue of the electronic circuitry of this instrument greatly offset its shortcomings.
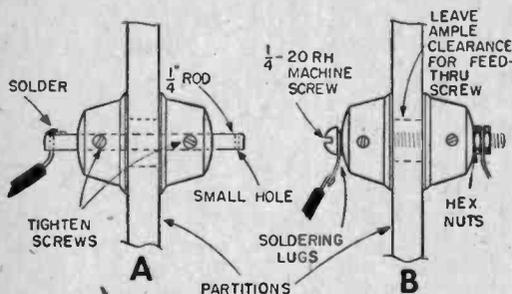
### New Use for Old Knobs

• Use discarded radio knobs as feed-thru insulators in radio and electrical work. To mount them, remove set-screws and run a  $\frac{1}{4}$ -in. drill all the way through the knobs. Pass a  $\frac{1}{4}$ -in. brass or copper rod through the knobs and partition; press both knobs firmly against partition and tighten set-screws (see A). Solder the wires into small holes drilled through the ends of the rod. In an alternate method (B), use a  $\frac{1}{4}$ -20 rh




brass machine screw, washers, hexagon nuts and soldering lugs instead of the smooth rod. A  $\frac{1}{4}$ -in. dia. threaded rod can be used in place of the machine screw, with a pair of hexagon nuts on both ends.—ARTHUR TRAUFFER.

### Connecting and Mounting Flashlight Cells

• To make connections to flashlight cells and hold batteries securely, remove paper wrapper around battery; mount battery on block of wood with conduit bracket and a couple of rh wood screws. Bend large soldering lug at an angle and mount

#### CONDUIT BRACKET

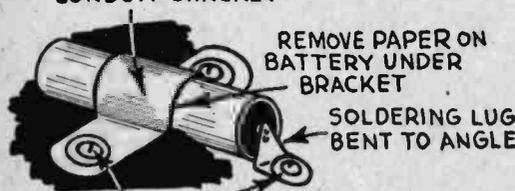

in front of battery so it contacts center electrode. Use one of conduit bracket mounting screws, and screw holding soldering lug, for binding

posts when making connections to battery. Place washer under each of these screws. Two batteries can be mounted in line for a series connection, if desired.—ARTHUR TRAUFFER.

### Auto Antenna Bayonet Connector


• When your auto radio begins to give intermittent reception, check the lead-in to antenna connection. If road vibration has caused the antenna to shake free of contact with the lead-in



bayonet tip, slip a short length of compression spring over the tip. Allow spring to extend beyond tip enough to make constant contact with the antenna when plugged in its socket.—K. H.
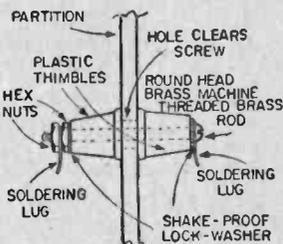
### Thimble-Size Insulators

• Plastic thimbles sold at notions counters or variety stores (especially those made of polystyrene) can be used to make neat-looking, low-loss feed-thru insulators. Drill a hole through metal



panel, cabinet or partition which will give ample clearance for brass screw or rod, to avoid shorts or losses, and assemble with thimbles and nuts as shown in drawing. Since heat will melt or soften the plastic thimbles, make solder connections to solder lugs before bolting onto thimbles.



# Testing TV and Radio Tubes

By  
L. G. SANDS

**D**EFFECTIVE tubes cause more than 90% of radio and television set troubles. Burned-out tubes cause a set to quit working; weak tubes cause poor performance (and under some conditions can stop the set from working). Yet the average person does nothing about having his radio or TV set's tubes tested until the set quits completely—and then is surprised when the serviceman says that several tubes should be replaced.

The electron tube is a reliable device. The jet bomber and the guided missile—to name only two of many similarly indebted mechanisms—depend upon it, so it has to be reliable. Even so, a vacuum tube has a limited life, limited, because of the physical limitations of its individual components.

The typical tube contains a *heater* which is surrounded by another element known as a *cathode*. (Some tubes have a single element which combines the functions of both heater and cathode.) When an electric current flows through the heater, it heats the cathode and the cathode emits electrons. These electrons flow to a metal cylinder known as the *plate*, attracted by the positive charge on the plate. To reach the plate (in every type of tube except diodes which have only plate and cathode elements), the electrons flow through a spiral wire assembly known as a *grid*; some tubes have more than one grid. Grids affect the flow of electrons because of changes on them, allowing either more or fewer electrons to reach the plate. All of these elements are enclosed in a vacuum inside a glass envelope (sometimes a metal envelope is used instead of glass).

A tube will fail to operate entirely if the heater

TV dealers will usually test tubes free. Most stores are equipped with a high-grade general purpose tube tester, similar to the large one in use by the dealer at left. Some dealers also have grid circuit testers (like the small one in the lid of the large tester) for checking critical tubes for grid emission.

burns out. It will fail to operate properly when the cathode becomes worn out and fails to emit enough electrons. And sometimes structural defects inside the tube may cause one of the grids to come in contact with another grid, the plate or the cathode, causing a short circuit and rendering the tube inoperative. If the glass envelope breaks, the tube will also fail to operate.

A perfect vacuum is never achieved in the process of making tubes and some gas will always remain inside the tube. A gassy tube is one in which an excessive amount of gas remains; such a tube is often indicated by a blue or purple glow inside the envelope. Finally, a very prevalent

defect which causes erratic operation of television sets and distortion in hi-fi systems is one called *grid emission*, a condition in which the grid or grids emit electrons as well as the cathode.

Several million tubes are replaced each year because some type of testing apparatus indicated that they were defective. The apparatus may be the radio or television set in which the tubes were in use or it may be an instrument known as a tube tester. Except for obvious structural breakage such as broken envelopes or shorted base pins, you cannot determine just by looking at a tube whether it is good or bad. You cannot, of course, see inside metal tubes, and usually you

---

## TABLE A—Tube Tester Kits

- 1) SECO GCT-5 KITESTER has all the parts required to assemble and wire your own Grid Circuit Tester. Otherwise, identical to the SECO GCT-5. Available through electronics parts distributors. Price: \$19.95
  - 2) HEATHKIT TC-2 tests most tube types for emission and shorts. Has illuminated roll chart listing tube test information. Provided ready to assemble and wire. Heath Company, Benton Harbor, Mich. Price: \$29.50
  - 3) KNIGHT TUBE TESTER KIT checks for emission and shorts. Provided with roll chart. Ready to assemble and wire. Allied Radio Corp., 100 N. Western Ave., Chicago. Price: \$29.75
  - 4) PRECISE 111K tests for transconductance and emission. This is more elaborate tester for checking both tubes and transistors. Sold through electronics parts distributors. Price: \$79.95
-



The professional service technician usually checks tubes by substituting new tubes for those he knows from experience to require most frequent replacement. He also tests certain tubes for grid emission with the grid circuit tester. Grid emission is a very frequent cause of TV ailments and is not readily detected with general-purpose tube testers.

cannot see inside glass-envelope tubes because of the silver or dark coating on the inside surface of the glass. (Incidentally, blackening or discoloration of the glass envelope does not necessarily indicate that there is anything wrong with a tube.)

Ordinary tubes have a rated life of 1000 hours. Many last much longer, some quit after a few minutes or a few hours of use. To insure your getting maximum performance out of your TV, radio or hi-fi set, its tubes should be tested at frequent intervals. You may tolerate and be unaware of substandard performance because tube deterioration may have been very gradual: when new tubes are installed, you may be surprised by the marked improvement. By waiting until your set quits completely, you are not getting all the performance that is built into it.

**Getting Tubes Tested.** The easiest and perhaps the best way to test tubes is to call a reliable radio or TV service shop and have a trained technician check the set and the tubes in your home. Sometimes the technician will bring along a large, bulky tube tester and check each tube individually. This takes time, however, and requires muscle, so the typical technician today carries spare tubes and a *grid circuit tester* which fits inside his tube caddy. If a set has quit entirely, he usually knows from past experience with the same type of set which tube has blown. Once that tube has been replaced, he observes the performance of the set and by substituting other new tubes for old ones and noting any improvement in set performance, determines which—if any—other tubes should be replaced.

The serviceman will next check certain tubes for *grid emission* and *inter-element* leakage with his grid circuit tester, usually finding two or three that may still perform satisfactorily but which—according to his grid circuit tester—have slight grid emission and thus can cause erratic

performance after extended operation. Tubes with excessive grid emission, of course, won't work at all in some applications.

**Checking Your Own.** Instead of calling a technician to test tubes and check your set in your home, you can take the tubes to a service shop or TV store to have them checked. Testing them is easy. The hard part is getting them out of your set initially, and then replacing them in the correct sockets.

In the case of a TV set, first remove the back cover. Usually there is a printed diagram glued or stapled inside of the cabinet that indicates the type number and location of each tube.

To play it safe, number the tubes on this diagram and attach pieces of adhesive tape marked with matching numbers to each tube in the set. (Take the tape off when you replace tubes since some of them get very hot.)

Some tubes may be enclosed inside metal shields. These shields must be removed when the tubes are to be tested, and reinstalled when the tubes are replaced. And don't overlook tubes located inside a protective metal housing on the chassis of your set when you're pulling tubes for testing.

When the back cover of the set is removed, the power cord is also disconnected, or a safety switch is actuated so that the set cannot be

---

### TABLE B—Typical Tube Testers

- 1) A.B.C. TESTER has three sockets for testing filaments of most tube types used in television sets, including picture tubes. If the indicator does not light, the tube is defective. If the lamp does light, however, the tube may or may not be good; further tests with a more complex tester should be made. Although this tester does not check anything but filaments, it can be a handy time saver for the do-it-yourself man. Omega Electronics, 670 N. Michigan Ave., Chicago. Geiger Engineering Corp., 3738 W. Lawrence Ave., Chicago 25. Price: \$3.95
  - 2) SUPERIOR TC-55, a low-priced, general-purpose tube tester for the experimenter with a modest budget. Tests most commonly used tube types. Moss Electronic Distributing Co., 3849 10th Ave., New York 34, N. Y. Price: \$26.95
  - 3) SECO GCT-5, a special type of tube tester for checking for grid emission and inter-element leakage. Finds grid defects usually missed by general-purpose tube testers. This type of tester is used in addition to a general-purpose tube tester and often by professionals to supplement tube-substitution test methods. Sold through most electronics parts distributors. Price: \$29.95
  - 4) TRIPLETT 3412-A, a general purpose tube tester which checks all modern tubes for shorts and emission. Sold through radio parts stores. Price: \$77.91
  - 5) HICKOK 539A, a professional lab tube tester for the expert. More critical than most lower priced tube testers. Sold through electronics parts distributors. Price: \$287.00
-



Many super markets, service stations, druggists and hardware stores have installed serve-yourself tube testers.

turned on. Service technicians sometimes use cheater cords to permit operation of the set with the back cover removed. Don't try it! The safety features built into your set are there for the purpose of protecting you from a dangerous shock.

Neither should you attempt to take out the picture tube for testing. You can easily break the glass and suffer serious injury. If you have doubts about the condition of the picture tube, call in a service technician. But remember, lack of a picture or a poor picture does not necessarily mean that the picture tube is defective.

Most electronics dealers and electronic service shops will test tubes without charge. Most will not try to sell you tubes unless you need them. If you should install new tubes, however, and then reinstall some of the old ones in their place and find that the set works just as well, don't jump to the conclusion that you have been gyped. In some TV set circuits even very weak tubes will work. In some other circuits, on the other hand, you may have to try two or more new tubes to find one which will operate satisfactorily.

Super markets, gas stations, hardware stores and drug stores are among the enterprising business firms which have installed serve-yourself

tube testers. These testers are usually loaned by the wholesaler; the dealer provides floor space and receives a commission on the tubes he sells. Detailed instructions for use are posted at or adjacent to the tester.

**Tube Testers for the Home Workshop.** If you are sufficiently interested in electronics, you will want to buy the necessary equipment for tube testing at home (see Table A and Table B). Tube testers are advertised for sale for as little as \$1.97, but a really critical tube tester sells for as much as \$695. There should be a difference—there is.

So-called tube testers selling for under \$5 test only for open filaments. (An ohmmeter, though not so convenient to use, will make the same test.) Although an open tube filament is the most frequent cause of total failure of a radio or TV set, it is far from being the biggest cause of defective tubes.

In most table model radios (and in many late model television sets), the tubes are connected in series, in Christmas-tree light fashion. If one tube burns out, all or several other tubes will also fail to light, and in such a case an inexpensive tester can locate the one offending tube. But, in

**TABLE D—Testing Tubes at Home Without a Tester**

- 1) Obtain a supply of pre-tested spare tubes, at least one of each type (preferably more) used in the set.
- 2) Assuming set does not work satisfactorily, turn the set on for 10 minutes to let it warm up.
- 3) Turn set off and remove back cover.
- 4) Feel each tube to see if it is warm. (Careful—some tubes get very hot.) If one tube is cold and the others are warm, replace this tube with a new one. (A cold tube may be burned out. In some sets the tubes are connected in series in Christmas-tree light fashion and all or several tubes may be cold even if only one is burned out.)
- 5) Replace back cover and try set. If it does not work, substitute a new tube for an old tube, one at a time, trying set each time. If a new tube does not do the trick, put the old tube back before replacing the next one.
- 6) Once the set is working, replace each tube, one at a time, to note any improvement in performance. Don't forget that the set must be turned off every time a tube is removed or installed.
- 7) Leave new tubes in place whenever an improvement in performance is noted, even if slight. The overall improvement in performance when several tubes are replaced can be appreciable.
- 8) If a Grid Circuit Tester is available, test applicable types of tubes (see Table C) for grid emission. Some tubes which work OK now but fail to pass the grid test may cause serious, hard-to-find trouble after extended operation as tube gets hotter.
- 9) Throw away weak or defective tubes so that they won't be used again.

**TABLE C—TUBE TYPES WHICH SHOULD BE CHECKED FOR GRID EMISSION**

(as well as for shorts and electrical merit)			
3AV6	6AB4	6BC8	6U8
3BA6	6AG5	6DB6	6X8
3BC5	6AH6	6BE6	12AT7
3BE6	6AK5	6BH6	12AU6
3CB6	6AK6	6BH8	12AU7
3CF6	6AM8	6BJ6	12AU7A
3CS6	6AN8	6BK7A	12AV7
4BC8	6AR5	6BK7GT	12AX7
4BQ7A	6AS6	6BQ7AT	12AY7
4BZ7	6AS8	6BX7GT	12AZ7
5AM8	6AU6	6BY6	12BA6
5AN8	6AU8	6BZ6	12BA7
5AS8	6AW8	6BZ7	12BD6
5BK7A	6BA6	6CF6	12BE6
5J6	6BA7	6CG7	12BH7
5U8	6BA8	6CL6	12BH7A
	6BC5	6J6	12BZ7

general, such a tester is not much better than no tester at all.

A kit of parts for building a tube tester that will check the electrical performance of a tube can be purchased for about \$30. Ready-made tube testers can be bought for a similar price. A more adequate tester, however, costs about \$70 in kit form and over \$100 assembled.

The cheaper testers are seldom as critical as the more expensive testers and may pass tubes as OK when they should be rejected. Some testers measure what is known as *emission*, or current flow through a tube; others—like the Hickok—measure transconductance; and some use plate conductance or some other term or form of measurement for indicating the degree of *merit* of a tube. (Transconductance is a technical term denoting the change in current in one tube element as caused by a change in voltage at another element.

The conventional tube tester has a meter scale with numbers, plus a red and green section to indicate *Good* or *Bad*. Also, most testers are equipped to test for *shorts*. Nearly all are rela-

merit test button and note the meter reading. If it is in the green, reduce the filament voltage to the next lowest value (for example, for a 6.3-volt tube, set filament at 5 volts). If the meter reading now drops into the red zone, this may mean that the tube is nearing the end of its useful life and should be replaced.

Having passed the short and merit tests, most tube types should next be checked for grid emission in a grid circuit tester. This is the acid test for miniature tubes. At one shop it was noted that 90% of the tubes which failed to pass the grid emission test, checked OK on a conventional, general-purpose tube tester. So, is it important to check for grid emission? TV technicians seem to think it is since by doing so they have been able to reduce callbacks drastically.

Poor picture contrast; grainy picture; twisting, pulling and bending; jitter and bounce; buzz and poor fringe area reception are among the hard-to-find troubles caused by grid emission. If a grid circuit tester is not available to you at home, take the tubes to a shop that does have one or substitute new tubes for old ones, one at a time, until the trouble clears up.

When no tube tester is available, tubes can be checked at home by the substitution method, installing one new tube at a time in the place of an old one and observing the picture or sound for change in performance (see Table D).

**About Buying Tubes.** A new tube is not necessarily a good tube. There are duds in any batch of new tubes. Sometimes, several tubes in a single batch may be below standard. Tube manufacturers turn out over 100,000,000 radio and television receiver tubes each year. Tube prices are low and demand is great. In spite of stringent quality control methods, some bad tubes get by.

To play it safe, buy tubes of a known brand, RCA, Philco, Sylvania, Tung-Sol, General Electric, etc. Buy from a reputable dealer and beware of phoney bargains. Most retail dealers will sell tubes only at the suggested list price, and small-town wholesalers often refuse to sell to anyone but legitimate dealers. (The wholesale price is about half of the suggested list price.)

Bargain tubes are often packaged in plain white cartons or with an unknown label. They may be rejects, seconds or just plain used tubes. Or they may be perfectly good surplus tubes. You have no certain way of knowing. Tube manufacturers use cartons bearing their own label or a private brand for tubes intended for the replacement market. When you buy new tubes have them tested then and there to make sure they are OK.

A new tube may not operate properly after a short period of use because it may have developed excessive grid emission which went undetected by a conventional, general-purpose tube tester. Or it may quit functioning due to some other cause after a few hours of use. If a tube gets through the first 200 hours of its life, however, it generally lasts a long time. Most new tubes will give long and satisfactory service.



A radio and television tube filament checker such as the one shown above will test TV picture tubes as well as ordinary vacuum tubes.


tively easy to operate if instructions are carefully followed.

Most tube testers do not check for grid emission, but a check of this condition is critical usually only with miniature tubes (see Table C). The professionals use a special tester for this test in addition to a general-purpose tube tester. Grid circuit testers such as the Seco GCT-5 are available ready-made for about \$30, or for \$20 in kit form.

To test tubes yourself, test first for shorts. If the short indicator lamp flickers or glows, do NOT press the *merit* test button or the meter of the tester may be damaged. Tap the tube while testing for shorts to detect intermittent shorts.

If the tube passes the *short* test, then press the

# Versatile Oscillator

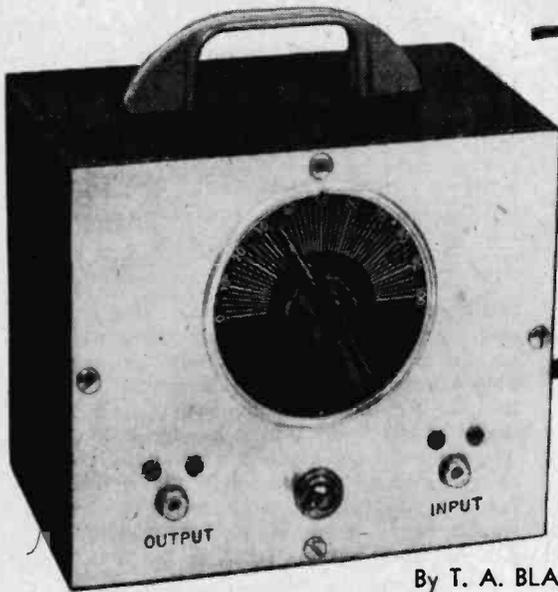


By T. A. BLANCHARD

This compact oscillator plays records by wireless and generates signals for aligning superhet receivers

**T**HIS compact oscillator performs double duty as an efficient wireless record player and signal generator. Employing a miniature 35W4 rectifier and a miniature 12BA6 pentode in a grid-modulated Hartley-type oscillator circuit, the trim assembly shown in Fig. 1 measures only 6 x 5 x 4 inches. A signal generator is a most useful tool when aligning a superheterodyne type receiver that is "out of whack."

The oscillator is built into a standard metal radio utility box (sold by all radio parts suppliers). These boxes are available in a variety of sizes—in black wrinkle steel or hammertone aluminum, which is a bit more expensive than steel. A plastic drawer pull from the dime store provides a neat carrying handle. To get started building the oscillator cut the chassis from 16 or 18-gage aluminum and cut the necessary component mounting holes as shown in Fig. 3. Bend down a  $\frac{7}{16}$  in., 90° fold along the front edge of the chassis for attaching to the front panel of the cabinet. The same screws which secure the chassis to cabinet also fasten the *input* and *output* jacks to the front panel. Instead of using two of the single round phono jacks, a double rectangular phono jack strip was cut in half. If you use the round single jacks, however, separate mounting holes and screws will be required. When purchasing the jacks, order a pair

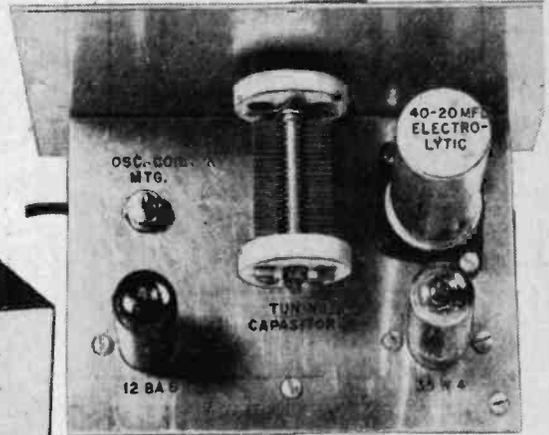

**2** Fig. 2. Chassis provides ample room for using standard-size single-gang capacitor instead of the miniature type shown above. (With standard size, insulate rotor plates from chassis.)

Fig. 1. Trim oscillator is both wireless broadcaster and test instrument for aligning.

of phono tip plugs at the same time to match the jacks. One phono plug connects to the phono pickup at the oscillator. The other tip is used for a shielded or unshielded output wire from the oscillator for testing and

aligning. Arrange the components on chassis as shown in Fig. 2 and pictorial wiring plan (Fig. 5). A can-type dual-electrolytic capacitor with a 40 and 20 mfd., 150 w. v. rating mounts over the  $1\frac{1}{8}$ -in. dia. hole. The electrolytic capacitor should be of the *insulated* type. This unit resembles any other can-type electrolytic capacitor, except that it includes a black paper tube which insulates the can, plus a Bakelite mounting plate instead of the usual metal plate. Fig. 2 shows the capacitor with paper tube removed. The tube is not essential, but the Bakelite mounting plate is required to insure a shockless isolated ground circuit.

The oscillator coil is a regular Hartley tapped type, the same kind used in small portable superheterodyne receivers. Two suitable types are indicated in the Materials List. Sometimes the Hartley coil is cataloged simply as 6SA7 or 12SA7 type. Oscillator coils are built with either a metal bracket for mounting with screws and nuts or a snap-in fastener. After mounting tube sockets and a 2-lug terminal strip, you may begin wiring the oscillator following the pictorial wiring plan. (Fig. 5).

When using the oscillator as a home broadcaster, the maximum capacity of the tuning capacitor need not be over 250 mmf. This will tune from about 1700 kc. to 1000 kc. approxi-





or tape the output wire to the radio's loop for adequate capacitance pick-up. No actual connection need be made to the loop.

Tune both the oscillator and radio dial at 1700 kc. Now adjust the small trimmer capacitor below the oscillator section small plates of tuning capacitor with plastic blade screwdriver until

oscillator signal is loudest. Finally, tune oscillator and radio to 1500 kc. and adjust the small trimmer below the R.F. section large plates of tuning capacitor for maximum volume with the plastic blade screwdriver. With these adjustments for peaking performance, your receiver alignment is finished!

## Magnetic PENDULUM

**H**ERE'S a natural for electrical experimenters and physics students—a pendulum kept in motion indefinitely by two electro-magnets, which are of the same polarity and thus repel each other (Fig. 1).

One magnet, fixed on the lower end of the pendulum arm swings toward another magnet attached to the backboard. Just before the swinging magnet actually touches the fixed magnet, a switch actuated by the motion of the arm makes contact. This energizes the two magnets and the repulsion effect takes place. The arm swings away and then returns again only to be repelled. This pendulum action will take place indefinitely at a rate of about 70 strokes per minute.


Before anyone hollers perpetual motion, however, let's note that there is a power source which is needed to energize the magnet's polarity, and parts do wear out eventually and have to be replaced.

Note the neon lamp which has been added on top of the unit. This flashes at each swing of the arm. For those who insist on a practical use for such an experimental gadget, it could conceivably be rigged up as a movable display.

The S.P.D.T.-type Microswitch used in this unit has one normally-open contact and one normally-closed contact. The magnets are connected in a circuit to the common terminal and the normally-open one so that, as the pendulum arm swings against the switch operating lever, the contacts close and the desired action takes place. The normally-closed contact is connected in a circuit with a neon lamp, so that the bulb will blink at each swing of the pendulum.

Power for operating the unit is taken from a regular 115 volt ac house line. The selenium rectifier stack in this circuit provides half-wave pulsating dc current as required by the magnets.

**Constructing the Base.** Figure 2 shows you the dimensions of the  $\frac{3}{8}$  in. thick birch base pieces and backboard. Note in Fig. 2 the  $\frac{1}{4}$  in. wide framing strip glued and bradded at the back of the backboard panel to form a shallow box-like section. Attach this frame to the top base piece with glue and two screws. Then glue and clamp bottom base piece to top base piece. Countersink all brads and screws and fill holes with

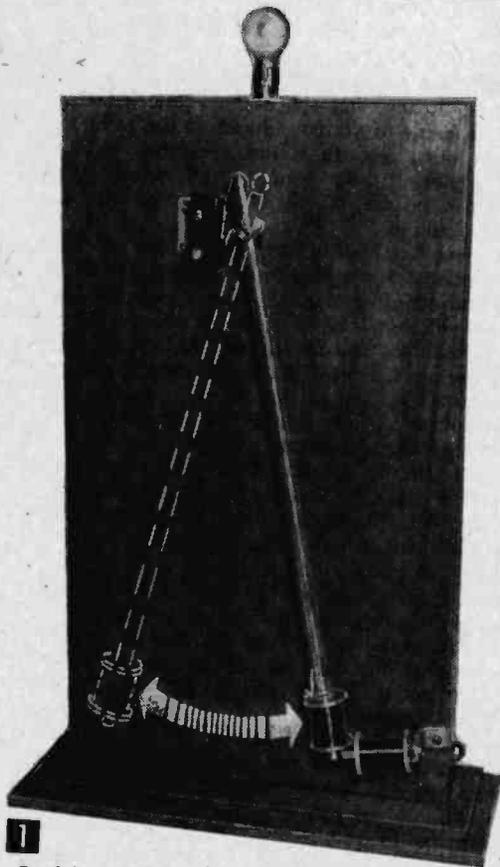


**1** Pendulum at the extreme right position of its swing. Dotted lines indicate extreme left position and travel of pendulum.

Plastic Wood. Then, with sandpaper, dress all mating edges off flush and round corners slightly. Finish with a generous, brushed-on coat of walnut oil stain (allow it to dry 5 to 8 minutes before wiping off all stain remaining on surface). About 4 to 6 hours later, apply several thin coats of white shellac diluted with about 20% alcohol or shellac solvent, lightly rubbing down each coat with fine steel wool after shellac hardens. Finish with paste wax polished briskly with a cloth.

(If wood is not of very close grain, apply some paste wood filler mixed with walnut stain, before applying the shellac. Apply with a piece of bur-lap, allow to dry a few minutes and then wipe off across the grain. Allow an hour to dry before applying shellac.)

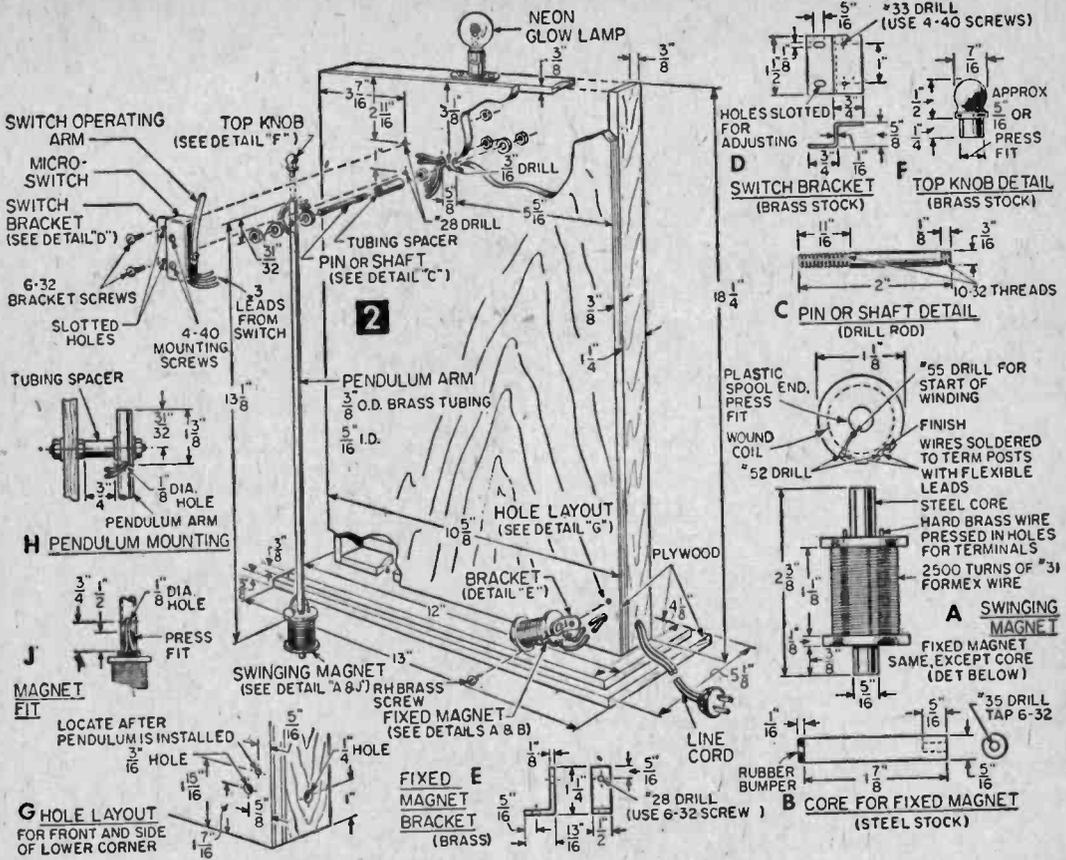**Making the Pendulum Arm (Fig. 2).** First,



MATERIALS LIST—MAGNETIC PENDULUM


No.	Description	Use
1 pc	birch plywood $\frac{3}{8}$ x $10\frac{5}{8}$ x $18\frac{1}{4}$ "	
1 pc	birch plywood $\frac{3}{8}$ x $5\frac{1}{8}$ x $13$ "	
1 pc	birch plywood $\frac{3}{8}$ x $4\frac{1}{8}$ x $12$ "	
2 pcs	birch plywood $\frac{3}{8}$ x $1\frac{1}{4}$ x $18\frac{1}{4}$ "	
2 pcs	birch plywood $\frac{3}{8}$ x $1\frac{1}{4}$ x $9\frac{7}{8}$ "	
1 pc	brass tubing $\frac{3}{8}$ " O.D. $\frac{1}{16}$ " I.D. $13\frac{1}{8}$ " long	(pendulum arm)
1 pc	soft steel or iron rod $\frac{3}{16}$ " dia. $2\frac{3}{8}$ " long	(magnet core)
1 pc	soft steel or iron rod $\frac{3}{16}$ " dia. $1\frac{1}{8}$ " long	(magnet core)
4 pcs	plastic or Bakelite $\frac{1}{8}$ x about $1\frac{1}{2}$ x $1\frac{1}{2}$ "	(make round spool ends)
1 pc	brass $\frac{1}{8}$ x $\frac{1}{2}$ x $2\frac{1}{8}$ "	(fixed magnet bracket)
1 pc	brass rod $\frac{1}{2}$ " dia. about 1" long	(turn to make knob on top of arm)
1 pc	steel drill rod or other smooth steel $\frac{3}{16}$ " dia. 2" long	(pendulum arm support and bearing)
1 pc	brass tubing $\frac{1}{4}$ " dia. $\frac{3}{4}$ " long with $\frac{3}{16}$ " I.D.	(spacer for arm)
3	10-32 nuts and washers (brass)	
1 pc	brass $\frac{1}{16}$ x $1\frac{1}{2}$ x $2\frac{1}{8}$ "	(switch bracket)
2	4-40 rh machine screws 1" long	(switch mounting)
2	4-40 nuts	
2	6-32 rh or buttonhead screws $\frac{3}{8}$ " long	(bracket mounting)
2	6-32 nuts and washers	
1	Microswitch #BZ-2RL S.P.D.T. with operating lever	
1	bayonet-type socket with mounting flange double contact candelabra type	
1	NE-32 1 watt double contact G-10 neon glow lamp	
1	5000 ohm 1-watt resistor	
1	Federal miniature rectifier, type 1028-A 250 ma. or any similar, half-wave 130 v. input type	
1	4-terminal chassis solder terminal strip	
1	1-terminal chassis solder terminal strip	
7 ft	#18 flat rubber lamp cord	
1	attachment plug cap	

About  $\frac{1}{4}$  lb of #31 Formex or Formvar Heavy magnet wire  
 3 ft of #28 extra flexible insulated wire or other small lead wire  
 About 6 ft #24-26 flexible, insulated wire for backside circuit hookup  
 Misc. stain, shellac, screws, etc.


Note: If you can't find brass tubing and steel rods at local hardware store or metal suppliers, try Charles A. Cole, 1355 Church St., Ventura, Calif.

obtain a  $13\frac{1}{8}$  in. long piece of brass tubing ( $\frac{3}{8}$  in. O.D.,  $\frac{1}{16}$  in. I.D.), stocked by some hardware stores and most metals suppliers. Dress the ends off smoothly to make this tubing  $13\frac{1}{8}$  in. long when finished. Turn the brass knob which fits on top of the pendulum arm in a lathe and have it a press fit for the end of the tubing (Fig. 2F). This knob actuates the switch lever.


At the lower end of the arm, ream out the inside diameter of the tubing, if necessary, to get a press fit for the end of the steel magnet core that will be attached to the arm (Fig. 2J). Drill two holes in the tubing for the entrance and the exit of the lead wires that go to the magnet (Figs. 2H and J). Also, drill a  $\frac{3}{16}$ -in. hole,  $\frac{31}{32}$  in. from the top of the pendulum arm, for the drill rod steel shaft or pin on which the arm will swing (Fig. 3). Have this hole a close but free fit for the shaft so the arm swings freely but without side motion or excessive looseness. The shaft is cut and threaded from drill rod as shown in Fig. 2C. Threading can be done by holding rod for shaft in lathe chuck and using tailstock to hold threading die squarely to the work. Then slowly turn

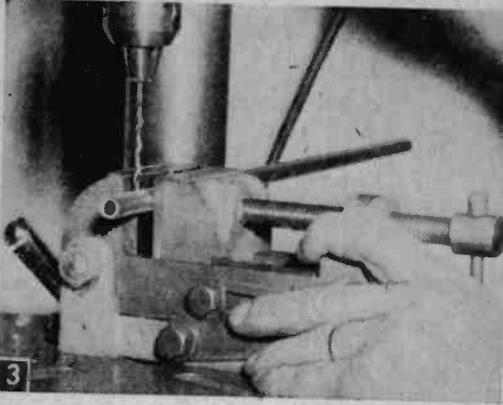

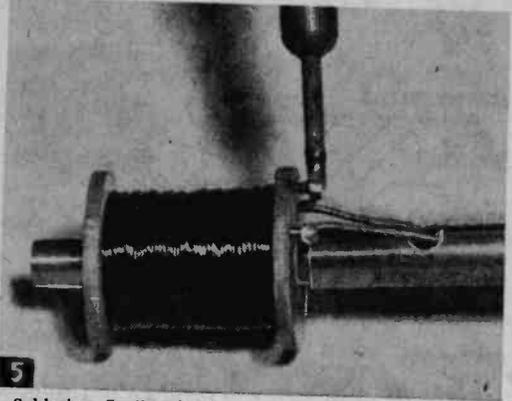3  
Drilling  $\frac{3}{16}$  in. diameter hole in pendulum tubing, for steel shaft which will support pendulum arm. Make sure hole is drilled at perfect right angle and exactly in center of tubing, by locking tubing between the V's of the vise. For a smoother hole you might use slightly undersize drill and then ream to size.



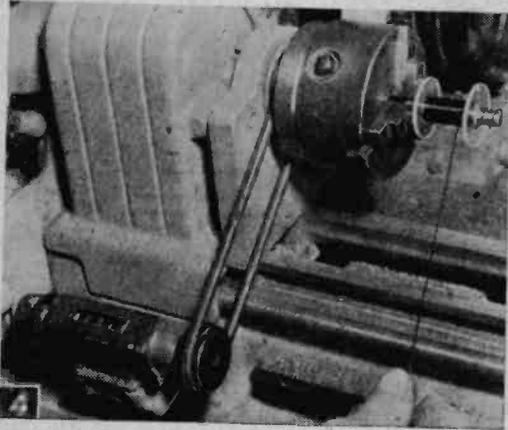5  
Soldering flexible leads to terminal pins, after movable magnet's core has been pressed into pendulum tubing. Avoid too much heat on pins or they may loosen in plastic.



4  
Magnets can be wound on the lathe, using a temporary turn counter rigged up like this with a rubber vacuum cleaner belt, and 1:1 ratio pulleys. Wind turns as evenly as possible, so surface of finished coil will be comparatively level.

die stock by hand and take up advance with tailstock screw.

**Making the Magnets.** Figures 2A and B show how the cores for both the *pendulum* and *fixed* magnets are made. To drill and tap the hole in the end of the *fixed* magnet's core (B in Fig. 2), secure the end of this core in the lathe chuck, and then use a center drill first, followed by a #35 drill. For accurate tapping, allow the tailstock center to enter the hole in the end of the tap wrench to thus keep the tap in line. Then slowly work the tap in by hand, taking up the advance with the tailstock screw. Apply some oil and be very careful not to break off the tap, working it back and forth a bit as the cutting of the threads advances.


Make four spool ends from  $\frac{3}{32}$  or  $\frac{1}{8}$  in. thick plastic (Fig. 2A). You can either turn these in the lathe after cutting them out roughly round

on a jigsaw, or, with care, make them round to a marked line on a sanding disc. The center holes in the spool ends must be a press fit on the steel cores. Press the plastic ends on the steel cores so that they will be  $1\frac{1}{8}$  in. apart between the inside surfaces, to give you the correct amount of winding space. One end of the core should project  $\frac{3}{8}$  in. beyond the spool end in each case. Wrap a layer of paper masking tape around core area between the spools, to act as insulation between the core and the coil that is to be wound on.


Drill a hole with a #55 drill through the spool end, at the side that will represent the back end of the spool, and make this hole come through close to the taped core for the start end of the winding (Fig. 2A). Drill a second hole close to the outer edge of the plastic for the finish end. To make sure spool ends stay in place, apply a little Pliobond cement at the inside junction of the taped core and the ends, and allow this to dry.

Figure 4 illustrates how magnets can be wound on a lathe at slow speed (100-200 rpm) with a turn counter belted to the lathe spindle to count the required turns. You can rig such a counter system by bolting or clamping a counter to the lathe bed, then fitting a 1-in. diameter pulley to the counter shaft and a second 1-in. diameter pulley over the lathe spindle, where it is locked in place by screwing on the chuck.

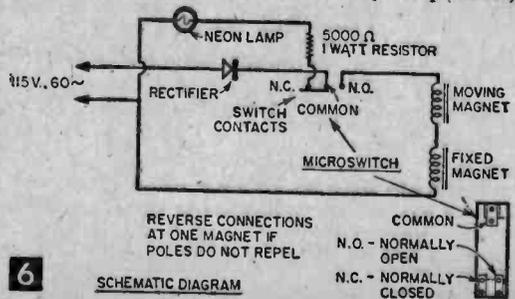
After winding on 2500 turns of #31 Formvar or Formex magnet wire, as evenly as possible,



6

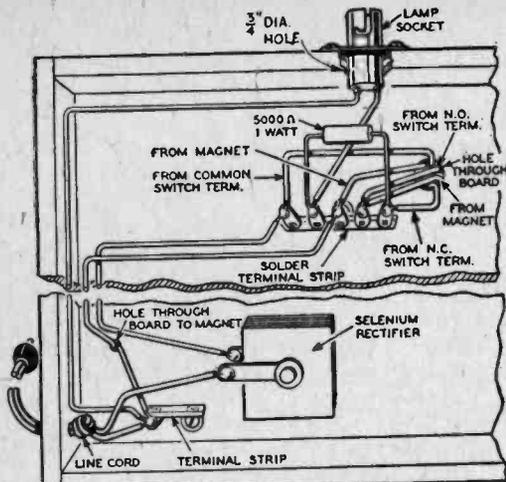

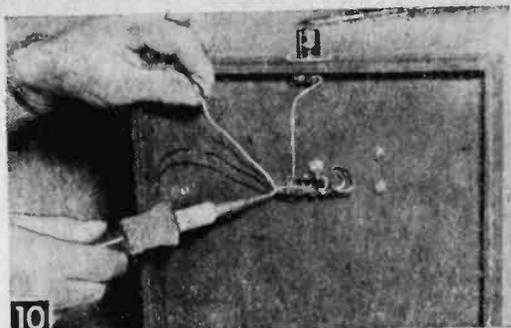**7** PICTORIAL WIRING DIAGRAM (AS VIEWED FROM BACK)



Soldering connections at terminal strip on back.

arrangement indicated in Figs. 6 and 7, and the installation of components shown in Figs. 8 through 10. Note in Figs. 2 and 9 how the fixed magnet is secured with a 1/2-in. #7 roundhead brass screw and washer through its supporting bracket.

You can vary the position of the fixed magnet by swinging the bracket mount so that when the arm is held up to allow the two magnet cores to touch, they will meet without striking the spool ends. Then tighten the screw down. Cut a 1/16 in. thick rubber piece to 5/16 in. diameter circular shape. Cement this to the end of the fixed magnet core (Fig. 2B) with Pliobond cement, to act as a bumper in case the swinging magnet should touch the fixed magnet's core.


Mount the indicating neon lamp on top of the backboard in a flange-type bayonet socket (Fig. 7), fixed in a 3/4 in. diameter hole bored in the top surface. Attach the switch to a brass bracket (Fig. 2D) which has slotted holes, so that switch position can be adjusted as required. The switch position is critical since it has to energize the magnets at the precise moment that the swinging magnet pole almost touches the fixed one. The two magnets are so connected that like poles are produced in the two, so that there is repulsion action. In making the connections, try the operation with the power on and see if the swinging magnet is repelled or attracted. If the two attract, simply reverse the leads to one magnet.

A final touch is to make up and attach a backboard of 1/8-in. Masonite, to cover the wiring and enclose the live connections.


**To Operate the Pendulum**, make sure unit is on a level surface, then plug in the cord and swing the arm by hand until the two magnets touch. After that they will continue operation.

The switch position may need adjusting at first, to find the point for the best action. With the swinging magnet held up to the first one by hand, you should feel the repulsion when it is about 1/2 in. away from the pole of the fixed one. Apply a drop of light oil to the pendulum shaft occasionally to assure free motion.

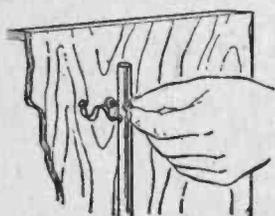If run without stopping, the operation of this pendulum will be limited only by the life of the switch (capable of millions of operations before failure), and the number of times the coiled leads can be flexed without breaking.



**8** ATTACHING PENDULUM

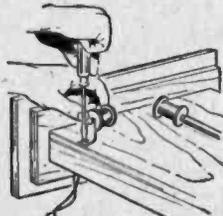

**9** ATTACHING FIXED MAGNET

bring the finish end out the hole provided in the spool end (Fig. 2A). Wind both coils exactly alike. Since the two coils are to be connected in series, there will be a total of 5000 turns in the circuit.

When winding is complete, there should be a margin of about 1/8 in. remaining on the spool ends beyond the coil. Drill two #52 holes in this space (Fig. 2A), but avoid touching the winding with the drill. Next, tightly press into these holes two pieces of 1/4 in. long brass or copper wire; these will act as terminal posts or pins to which the flexible lead wires will be soldered. Clean the ends of the magnet wire and wrap them around these terminal posts. (To clean off Formex insulation, hold a match under the end of the wire a few seconds, then clean with fine sandpaper.)

With the magnet core pressed into the end of the brass pendulum tube, carry two pieces of #28 flexible insulated lead wire down through the tube, and solder them to the terminal pins (Fig. 5). (Very small, extra flexible wire must be used here, so that it can be coiled up at the top end before it enters a hole in the backboard, and still have good flexibility as the pendulum swings.)

Figure 2 shows the holes you will need to drill in the backboard and details D and E in Fig. 2 show the brackets you will need for the switch and the fixed magnet. Attach the pendulum arm to the board as in Fig. 2H. Follow the wiring

# Dress Up that Low Price RECORD PLAYER

By ARTHUR TRAUFFER

**L**OW-PRICE record players are often sold minus everything but the bare essentials, as was the case with the one shown in Fig. 1. But suppose we see what we can add to this player which will improve it. First, let's purchase a chrome drawer handle (for about 25c) and mount it on the front of the player cabinet (Fig. 2).

The flocked finish on most low-price turntables is pretty hard and doesn't wear too long, so let's cut a heavy brown felt disc the same diameter as the turntable, cut a  $\frac{3}{16}$  in. diameter hole in the exact center of the felt disc, apply a thin coat of LePages' glue (thinned with a little hot water) to the turntable top, and press the felt disc on evenly. This felt covering is easier on your records and also helps to reduce rumble.

For an arm rest and lock (Figs. 2, 3, and 6), which is handy when player is being carried, cut and drill a simple plastic strip as shown. Give the top of the strip a slight clockwise twist

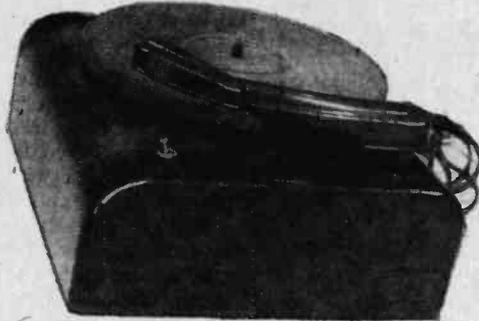


Fig. 1. BEFORE—record player as it came from the dealer.



Fig. 2. AFTER—all dolled up! Note chrome handle, layer of felt on hard turntable, arm rest and lock, and brackets for reeling up line cord and pickup cable.

so that it will line up with the side of the curved pickup arm. Remove crystal from the arm temporarily so that you can drill a  $\frac{5}{32}$  in. hole through side of arm for a 6-32 rh (round-head) brass machine screw about  $\frac{1}{2}$  in. long, a hexagon nut and a thumb nut (Fig. 4). Attach plastic arm rest to side of cabinet with two 6-32 rh brass machine screws about  $\frac{3}{4}$  in. long, positioning the arm rest so that screw on arm slips into slot freely.

If player is to be carried about, you'll want to have line and pickup cords neatly coiled and out of the way. To do this, mount two simple S-shaped brackets on back of player cabinet (Fig. 5). Bend the two brackets from 2 x 2 x  $\frac{1}{2}$ -x  $\frac{1}{16}$  in. brass angle brackets (the dime store has them). Mount brackets about  $7\frac{1}{2}$  in. apart with four  $\frac{3}{4}$  in. long 6-32 rh brass machine screws.



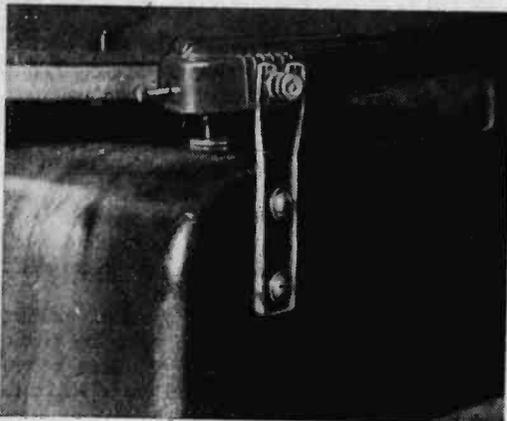


Fig. 6. Closeup of plastic arm rest and lock.

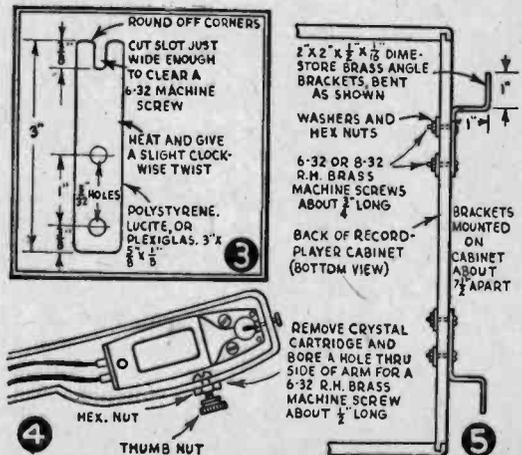

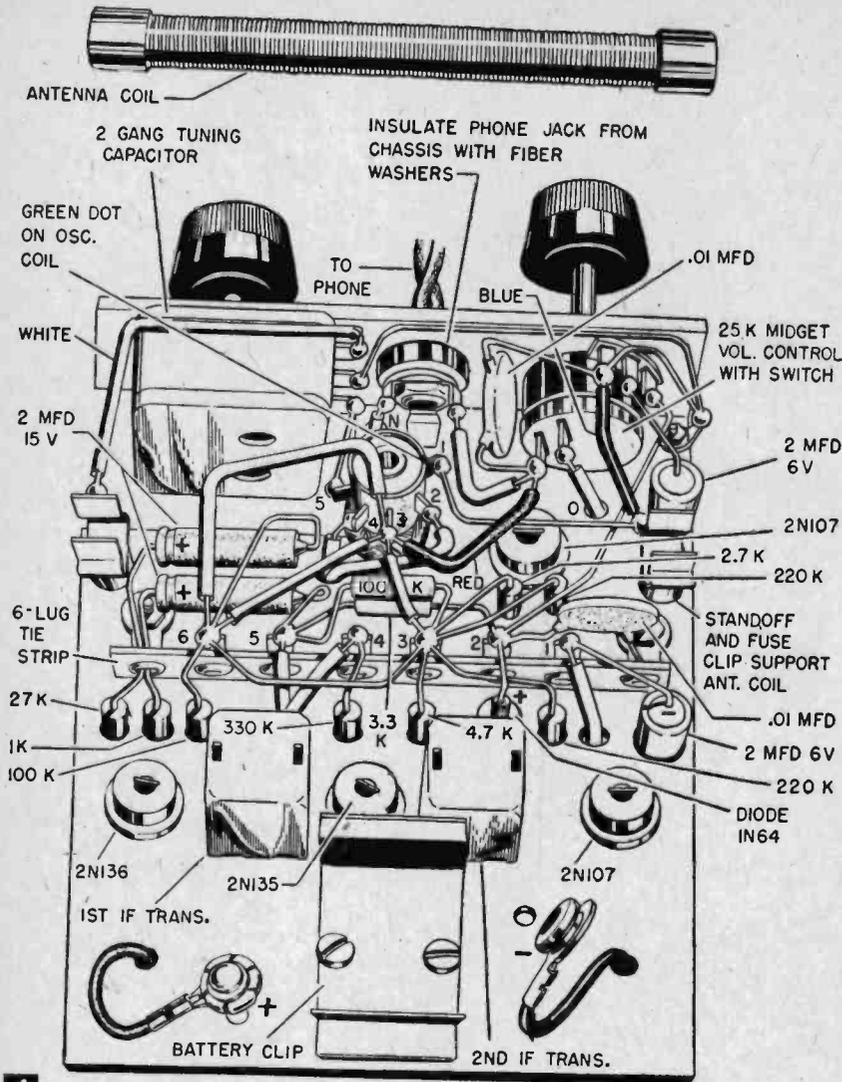



**4** PICTORIAL WIRING DIAGRAM (TOP VIEW)

The set's pee-wee dimensions are made possible through use of a sub-miniature two-gang, plastic encased tuning capacitor, volume control, phone jack, and I.F. transformers. These parts are readily available from the source given in the Materials List. When completed, this tubeless transistorized superhet will be no larger in size than two packages of king-size cigarettes.

The set is assembled on a simple, L-shaped chassis made from a piece of #14 gage aluminum measuring 3-5/16 x 5 in. Drill holes as indicated in Fig. 3 and bend up the end 90° as indicated by dotted lines. Then mount components as shown in Figs. 4, 5 and 6. The I.F. transformers are secured to the chassis by bending the end can lugs over the chassis after properly positioning each unit over the 1/2 x 1/2 in. chassis holes. Note that these ground lugs are not numbered in Fig. 5. Note also that the insulated lugs #4 on these transformers

have no connecting leads since the connection is already made by an internal capacitor.

The tiny Bakelite transistor sockets are secured to the chassis by spring locking rings. Use a screwdriver blade to press and lock the ring to the socket body. The oscillator coil mounts firmly to the chassis without the use of brackets or screws. Simply insert a rubber grommet into the 1/4-in. chassis hole, moisten the Bakelite coil tube with your lips, and press into the grommet hole.

Small components such as resistors, the diode detector, and electrolytic capacitors are neatly and firmly anchored by means of a six-lug tie-strip with separate grounding lugs at each end (see Fig. 6). Note that positive and negative positions are indicated for electrolytic capacitors and diode detector. Capacitors

however, may indicate the positive side with either a dot or a band at one end of the unit. Components are positioned in the row of holes running parallel with the tie-strip, allowing pigtail leads on the top of chassis to terminate on the appropriate strip lug while the pigtail lead on the opposite end of the component terminates on its respective transistor socket lug on the underside of the chassis.

Chassis holes B, G, N and K in Fig. 5 allow passage of hookup leads from the top to the underside of the chassis. Practically all circuit connections can be made with the component pigtail leads. Since most of these leads are quite short, only the longer leads and those passing from one side of the chassis require insulation. Spaghetti radio tubing may be used for insulating purposes, or insulated vinyl hookup wire may be employed

as in the case of battery connector leads.

Mounting of the ferrite rod antenna coil is done last. To support the ferrite rod, mount two Littelfuse clips on 1/2-in. by 3/8-in. dia. spacers using 3/4 in. 4-40 machine screws to secure to chassis. All other screw-fastened components use 1/4-in. by 4-40 machine screws and nuts.

To insulate the miniature phone jack from the chassis, place a fiber washer on each side of the 3/8-in. mounting hole, with jack centered in the opening. A miniature matching phone jack is used to attach the earphone cord. Because the conducting material in the cord is tinsel, it will not solder to the phone plug lugs directly. In removing insulation from the tinsel cord do not "skin" it off with a knife or wire stripper, but apply the tip of a soldering iron to it and melt away about 1/4 in. and with a single strand of wire, such as found in fixture cord, bind the exposed tinsel much as you would tie a fishing fly. Then solder the cord tips to the phone plug lugs. Before screwing down the plug cap, cut out a small piece of cardboard and place it between the lugs to prevent the lugs from shorting against the plug cap as the cap is screwed down.


Wire as shown in the schematic, Fig. 2. With wiring completed, install the transistors in their respective sockets, secure the RCA #VS-300 miniature 9-v. battery in the aluminum clip and attach snap connectors. To roughly align the set, provide an external antenna connection as previously described, turn on set with volume control at maximum and tune set until a station is heard. A good quality hearing aid type phone—one with a resistance of 2,000 to 10,000 ohms should be used with this unit. Do not expect results with imported crystal phones or "dynamic" phones from the Orient. Fine, British-made magnetic phones

cost only a few cents more than the others; many U. S. made hearing aids are equipped with these British earphones.

With a screwdriver blade, fashioned by filing flat the end of a plastic crochet needle, turn the slug screw in the oscillator coil in until signal is loudest, or about 4 1/2 turns from the slug's flush position. Note that on the back of the tuning capacitor there are two screws marked "Ant." and "Osc." These are the trimmer adjustments. Turn the screw marked "Ant." until the movable half-moon plate is 3/4-meshed with the stationary plate. Next turn the "Osc." screw until its rotor plate meshes halfway with the stator plate.

The oscillator coil screw may be again turned a trifle left or right until peak signal strength is obtained. Set should now tune in numerous stations and, if of sufficient signal strength, they will come in without the external antenna pick-up.

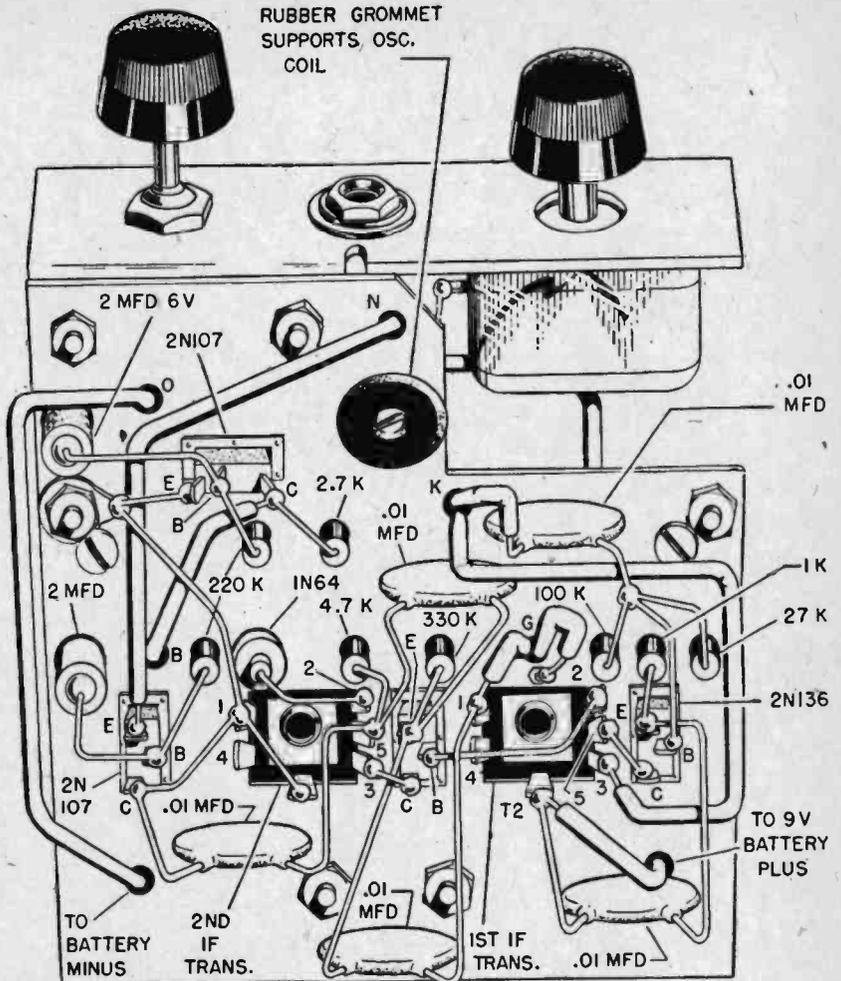This set can be housed in a variety of cabinets, but a leather instrument case such as that shown in Fig. 1A makes a neat arrangement. It is very





5 PICTORIAL WIRING DIAGRAM (BOTTOM VIEW)

MATERIALS LIST—POCKET PORTABLE

No.	DESCRIPTION	No.	DESCRIPTION
1	pc. #14 gauge aluminum 3 1/4"x5"	4	transistor sockets
1	3-gang miniature superhet tuning capacitor.	2	snap type battery connectors
	211 mmf. "Ant.": 101 mmf. "Osc."	2	soldering Lugs, #6
2	2 mfd., 6v. electrolytic capacitors	2	screws 4-40x3/4" w/nuts
2	2 mfd., 15 v. electrolytic capacitors	4	screws 4-40x1/4" w/nuts
6	disc-type ceramic capacitors, .01 mfd.	1	6-lug tie-strip
1	disc-type ceramic capacitors, .005 mfd.	1	sub-miniature phone jack and plug set with insulating fiber washers
1	germanium diode detector, 1N64 or 1N48	1	9 v. miniature transistor radio battery (RCA #VS-300)
1	GE type 2N136 transistor (Osc.-Mixer) (Converter)	1	battery mounting clip
1	GE type 2N135 transistor (I.F. Amp.)	1	1st I.F. transformer for transistor (Lafayette MS-268 or Automatic BS-725)
1	GE type 2N107 transistor (Audio Amp.) (Driver)	1	2nd I.F. transformer for transistor (Lafayette MS-269 or Automatic BS-726)
1	GE type 2N107 transistor (Power Amp.)	1	ferrite rod antenna coil (L <sub>1</sub> ) 1/4"x3 1/2" (Lafayette MS-272)
1	25K ohm, sub-miniature potentiometer w/switch	1	miniature oscillator coil (L <sub>2</sub> ) for transistor Service (Lafayette MS-265)
2	220K ohm, 1/2-watt composition resistors	1	magnetic type hearing aid phone (2000 ohms or higher)
1	4.7K ohm, 1/2-watt composition resistors		
1	2.7K ohm, 1/2-watt composition resistors		
2	100K ohm, 1/2-watt composition resistors		
1	1K ohm, 1/2-watt composition resistors		
1	330 ohm, 1/2-watt composition resistors		
1	3.3K ohm, 1/2-watt composition resistors		
1	27K ohm, 1/2-watt composition resistors		
1	1/16" dia., knurled pointer knob for 1/4" shaft		
1	1/16" dia., plain knob for 1/8" shaft		
1	rubber grommet for 1/4" hole		
1	battery clip		
2	Littelfuse clips: 2 1/4"x1/2" spacers		

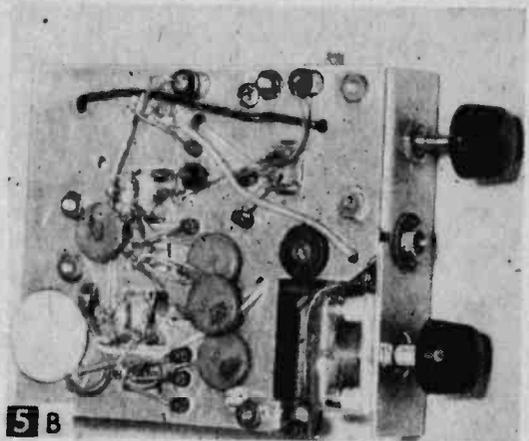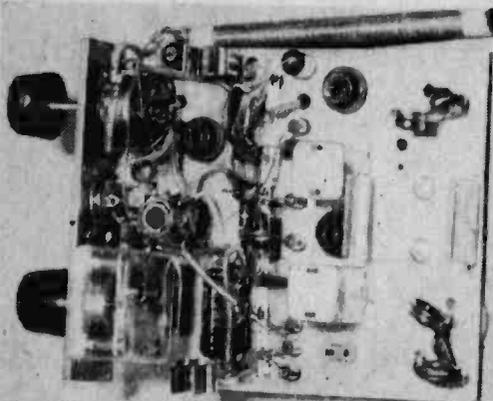
All components listed are available either singly or in complete kit form from Lafayette Radio Div., R-W-T, Inc., 165-08 Liberty Avenue, Jamaica 33, L.I., N.Y.



5 A

5 B

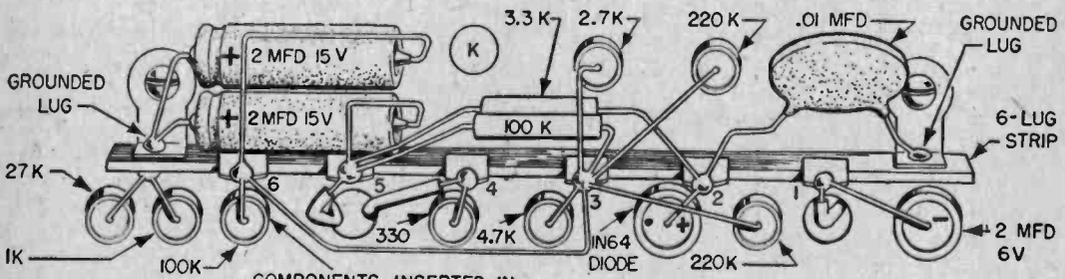Left, top of chassis with battery removed, as well as one transistor to reveal miniature 3-pin socket. Note rigid mounting for components provided by 6-lug tie-strip. Right, underside of chassis. Except for long leads which are covered with plastic spaghetti insulation, short wires and disc capacitor leads are bare since shorts are unlikely.




6 CLOSE-UP DETAILS OF TIE-STRIP CHASSIS HOLES  
LOOKING DOWN ON CHASSIS

stock leather and bindings along with simple instructions for making a case to suit your needs. If you are not too concerned with compactness, the sensitivity of the set can be increased by using a larger ferrite antenna coil and mounting it as far away from the set chassis as possible. Both the standard and miniature "loops" have the same red, white and blue color-coding.—T.A.B.

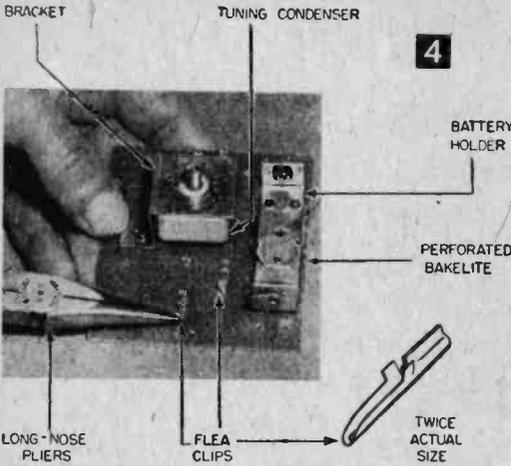important that such a case have inside dimensions sufficient to accept the chassis; to avoid damage to components, inside measurements must be 1 3/16 x 3 1/2 x 4 in. If a commercially made case isn't readily available, handcraft and hobby shops








Terminals and tie points are provided with flea clips that press into the holes. Use diagonal pliers to cut off the projecting ends of the clips on the other side, leaving about 1/2 in., then slightly spread the remaining ends so clips will stay in place. Insert, close-up of flea clip.

Drill the holes in the 1/4 x 3/8 x 3/8 in. plastic case carefully, since this material cracks quite easily (Fig. 3). For the larger holes, use a smaller drill and hand ream to size. There are two holes in each of three sides, four in the bottom and one in the cover to clear the condenser shaft. Cement 1/16 in. thick washers to the bottom of the box over the holes used to secure Bakelite board to box, to act as spacers, and screw board in place with 4-40 machine screws.

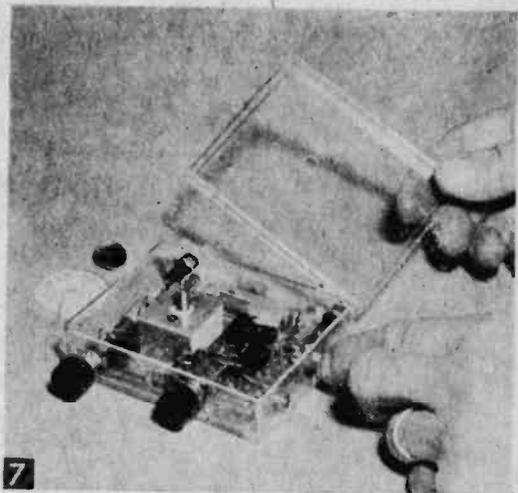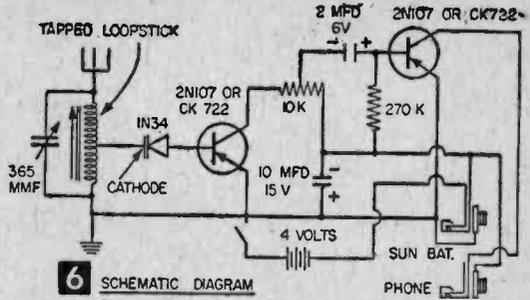
With all components in place as shown in Fig. 5, start the wiring (Fig. 6), using any small



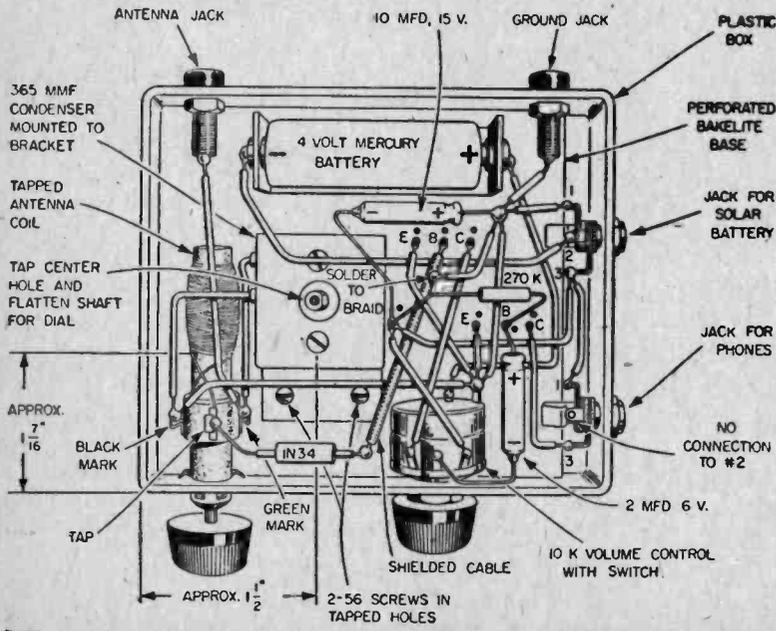To remove cover, first separate one hinge by pulling lightly, then tip cover so that a twist will unlock the other hinge. To replace cover, place it in the position shown above so the hinge pin enters at this side. The other hinge is then pressed together.



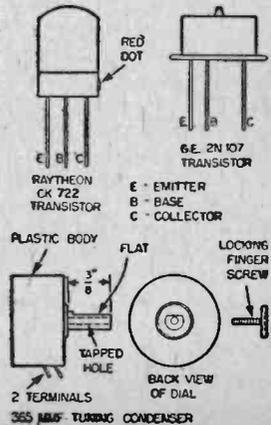plastic-covered hook-up wire such as #24 or 26 gage. Solder all connections carefully. At the transistor terminal clips, connect and solder the other leads first to protect the transistors from receiving too much heat.



5 PICTORIAL DIAGRAM


• LOCATE FLEA CLIP TERMINALS APPROXIMATELY AS SHOWN

Use long-nose pliers to absorb the heat while holding each transistor lead for soldering.

With wiring complete, install condenser dial, the shaft having been cut off to about  $\frac{3}{8}$  in. (Fig. 5). The dial fits on the end in a flattened recess, with a center screw retainer to hold it tightly fixed, which is installed last after cover is closed. Place the battery in its holder, spreading holder if necessary, and taking care to get the plus and minus ends to correspond with the polarity shown in Fig. 5.

A short length of antenna wire and a ground connection may be necessary in some areas; however, good reception is possible in many cases by simply clipping the antenna lead to the finger stop of a dial telephone and using no ground, or to the wire frame of a large lamp shade. Or you can wrap several turns of insulated wire around several slats of a metal venetian blind and these slats picking up radio energy will deliver it to the receiver inductively.

To assemble the solar battery, attach the cells to the sides of the  $1 \times 2\frac{1}{2} \times 3\frac{1}{2}$  in. plastic box with 4-40 screws and nuts in drilled holes (as in Fig. 8). Mount a strip of the perforated Bakelite, such as was used in the radio, in the center to take the flea clips for lead connections. Connect all cells in series, that is, connect the red wire from one cell to the black of the next at a soldered connection and carry this to all cells, using a short jumper at the end of the two rows to join them as shown. This will leave one black (negative) and one red (positive) left over to connect at terminals to the leads with a plug in the end. It is very important to observe the polarity of the leads between cells, at the battery output terminals, and also at the plug connections so that the battery will be correctly connected. The positive lead is soldered to the positive plug terminal which is grounded to the body of the plug, the negative

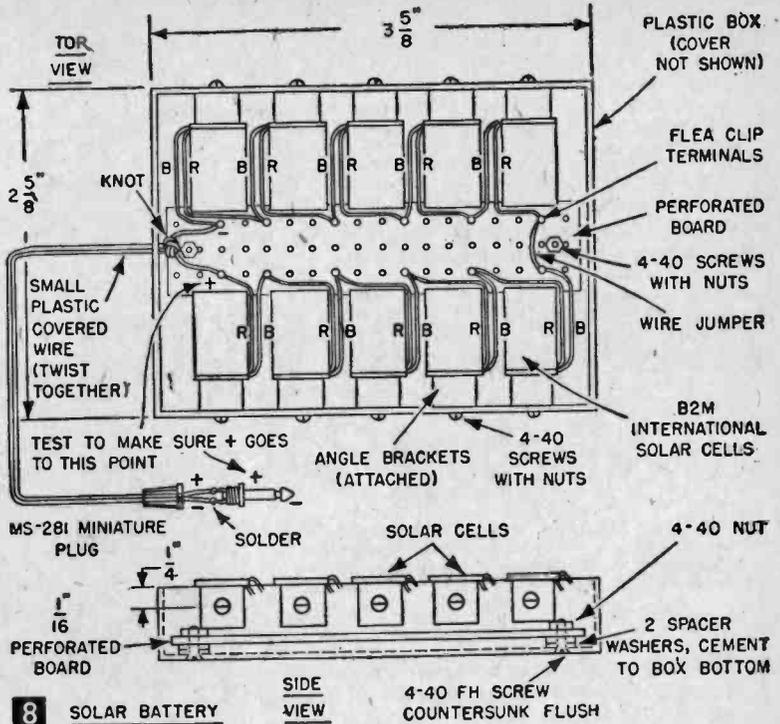

8 SOLAR BATTERY

MATERIALS LIST—SOLAR OR DRY CELL RADIO

All material available from Lafayette Radio, 165-08 Liberty Ave., Jamaica 33, N. Y., or 110 Federal Street, Boston, Mass.

Amt.	Description	Lafayette Cat. (1957)
1	plastic case $1\frac{1}{4} \times 3\frac{1}{8} \times 3\frac{1}{8}$ "	MS-298
1	tuning condenser 365 mmf	MS-274
1	tuning dial	KN-25
1	condenser mounting bracket	MS-310
1	transistor tapped Vari-Loop antenna coil	MS-299
1	10,000 ohm miniature volume control with switch	VC-28
2	miniature knobs for $\frac{1}{8}$ " shaft	MS-185
2	sub-miniature jacks	MS-282
2	sub-miniature plugs	MS-281
2	insulated tip jacks	MS-213 or PJ-23
2	phone tip plugs	MS-212 or PJ-11
1	Mallory mercury 4 volt battery	TR-133R
1	battery holder	MS-139 for Z cell
1 pc	perforated Bakelite sheet $\frac{1}{16} \times 3\frac{1}{16} \times 6\frac{7}{8}$ "	MS-305
2	transistors, G.E. 2N107 or Raytheon CK722	
1 pkg	flea terminal clips (12)	MS-263
1	2 mfd 6 volt Argonne condenser	
1	10 mfd 15 volt Argonne condenser	
1	270,000 ohm $\frac{1}{2}$ watt resistor	
1	1N34 diode (or 1N34A, 1N48, 1N64)	
2	Mueller test clips #45 for antenna and ground connections	
12 ft	plastic insulated stranded wire #22 to 24 gage (for antenna and ground lead)	
3 in.	shielded cable, Belden 8885	
3 ft	hook-up wire, plastic-covered, #24 gage or smaller, solid or stranded	
	2-56 or 4-40 machine screws (from hardware stores) and $\frac{1}{16}$ " thick washers	
1	2000 ohm headphone (Cannon AM-15-2, about \$2.08), or hearing-aid-type earpiece with less volume and tonal quality (Cat. #MS-260, \$3.95)	
	Solar Battery	
1	plastic case $1 \times 2\frac{1}{2} \times 3\frac{1}{2}$ "	MS-159
10	International Rectifier Corp. B2M solar cells (\$1.47 ea., including wire leads and mounting brackets)	
1 pc	perforated Bakelite sheet about $\frac{1}{16} \times 3\frac{1}{2} \times 1\frac{1}{16}$ ", cutting from radio piece	
1 pkg	flea clips (12)	MS-263
3 ft	small gage plastic-covered wire for solar battery leads. Can use hearing aid cord (not tinsel type), or other stranded wire of about 26 gage	

to the terminal which is insulated to form the tip connection or negative side. If the leads are twisted together to form a cable, it may be hard to trace individual wires. In this case, use an ohmmeter or other indicating device to trace the wires at both ends to get the connections correct, or use a voltmeter with the battery in the sun to check for correct polarity. The radio will not work on reversed polarity of either the dry or solar battery and may be damaged.

This solar battery is useful for powering any one- or two-transistor radio or other equipment having very light current requirements. Our radio uses around .45 milliamperes, which allows a voltage of about 2.7 volts, and which is sufficient to run the set very well. With twice as many cells connected in series-parallel, you get twice the output current, but it is probably better to employ larger cells in a straight series circuit for such cases.


# Electrical Coil-winding Machine

By HAROLD P. STRAND  
Craft Print Project No. 265

**U**NLESS you have a metal-turning lathe, or some similar machine capable of holding and turning a coil-winding form at a slow speed, winding a coil having hundreds of turns on it can be quite a chore. To answer the need for such a machine for those of you interested in making home-built electronic devices requiring coils for special size transformers, solenoids, etc., the electric-motor driven winder shown in Fig. 1 has been developed.

The winder is powered with a used Hoover vacuum-cleaner motor purchased at a repair shop for \$5. It is of the ac-dc or universal type which is subject to speed control with a variable resistance or reactor and is of a large heavy-duty type. The machine's foot controlled reactor (Fig. 1) has an infinite number of speed control steps; it will not heat up in use, wasting power; and has no wiping contacts usually employed with a resistance control.

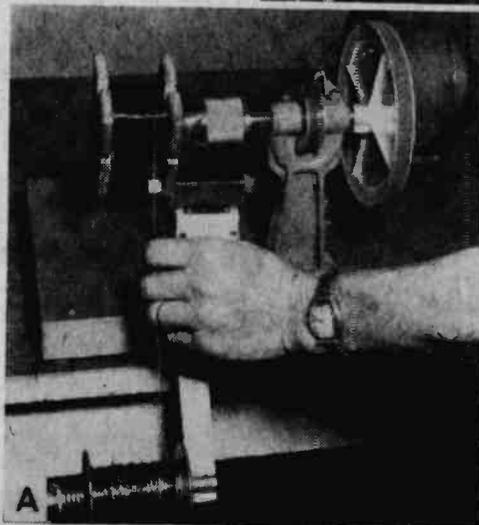When purchasing the vacuum-cleaner motor, turn it on and observe the commutator. There should not be appreciable arcing at the brushes which could indicate a short in the armature winding. Failure to run at its customary high speed is another indication of defective armature windings. However, worn carbon brushes could also produce these effects, so check the length of the brushes—



Variable speed, foot-control switch regulates speed of motor when winding coil. Photo A shows how magnet wire is hand guided from spool to coil windings.

they should be at least  $\frac{3}{16}$  in. long. Also check the armature-shaft bearings for wear. Remove the motor from the cleaner and attempt to move the fan and shaft from side to side. Any side movement indicates worn bearings. A little end play, in and out movement of the shaft, is permissible, however. Select a motor having a  $\frac{3}{8}$  in. dia. shaft on it.



2



3

Left. Cleaning disassembled motor with rag moistened in kerosene. Right. Clean commutator with fine sandpaper to inspect it for grooves or ridges.



4



A 150-watt lamp is connected in series with motor to reduce its speed when test running.

After purchasing a motor in the best possible condition, take it apart and clean with kerosene or carbon-tet. First remove the brush holders and brushes from their supports on the insulated ring. Then remove the two screws at the ring of the outside bearing cap, disassemble the motor as in Fig. 2. When cleaning, do not immerse the wound parts in cleaning fluid, merely wipe them off with a cloth dampened with the cleaning fluid or brush off the dirt if it is dry and loose. Clean the armature commutator with fine sandpaper as in Fig. 3. If ridges or grooves appear on the commutator after cleaning, have it turned down in a lathe and lightly sand smooth. Then clean out any deposits between the segments, which might cause shorts, by scraping with a thin but sharp tool. A quick test for shorts or grounded wiring in the armature can be made by having it tested on a growler at your local automotive generator repair shop. If it is found that new armature-shaft bearings are needed, they can best be installed at a vacuum-cleaner repair shop while you have the motor apart. At this time also saw off the 3/8 in. armature shaft so that it will project only 1 in. beyond the outside edge of the bearing when as-


MATERIALS LIST—COIL-WINDER	
No.	Main Motor Unit Description
1	used universal motor from a (Hoover) vacuum cleaner, having a 3/8" dia. shaft, vertical mounted with toggle switch on base
1	1 1/2" dia. V-pulley for small belt with 1/2" dia. hole (Sears Roebuck)
1	bushing to reduce 1/2" pulley to 3/8" shaft (1/2 O.D. x 3/8 I.D. x 1" long). (Boston Gear Works, 14 Hayward Street, Dept. SM, Quincy 71, Mass. or local distributor)
1	6" dia. pulley for small belt with 1/2" dia. hole (Sears-Roebuck)
1	polishing stand with 1/2" shaft (Sears Roebuck)
1	1/2" chuck to fit shaft (Sears Roebuck)
1	small V-belt, 3/8 x 24" (Sears Roebuck)
1	Bakelite surface type toggle switch with slotted base Leviton #1210 (electrical supply store)
10-14 ft	round rubber, light duty vacuum cleaner cord (vac. cleaner shop)
1	attachment plug cap (electrical supply store)
1 pc	2 1/2 x 2 1/2 x 3/16" angle iron 3/4" long (scrap piece from a metal-working shop)
1	rubber vacuum cleaner belt, 4 3/8"—4 5/8" dia. when laid in a circle (vac. cleaner shop)
1 pc	aluminum or hot rolled soft steel 1/16 x 2 3/8 x about 4 1/2" (scrap) (bend to make counter support)
1	Revolution Veeder-Root counter with reset knob or key, 4 or 5 figure columns with right hand column indicating direct single turns. Purchase from large hardware and machinery supply concerns or write to Veeder-Root Inc., Ninth Floor, 27 Sargeant Ave., Hartford, Conn., for nearest distributor or try surplus concerns
2 pcs	fir plywood 3/4 x 10 x 17" (base)
1 pc	cold rolled steel 1/16 x 10 x 17" (sheet metal shop)
1 pc	Bakelite or brass 1 1/2 dia. x about 1 1/2" long (turn to make counter pulley), or purchase 2 Cat. #PVL 1.5 pulleys from Boston Gear Works. For sprocket drive, order two K2520 sprockets and 19" of 1/4" pitch chain
4	3/4" dia. rubber headed tacks for base feet
1 pc	cold rolled steel 1/8 x 1 x 9" (spool holder)
1 pc	cold rolled steel 1/8 dia. x 5 5/8" long or make it longer if larger than 3 1/4" spools are to be used (spool holder)
3	brass washers about 1" diameter, 1/8" thick to fit over 1/2" shaft (spool holder)
1	coil spring to fit over 1/2" shaft, 1" long, about .075" piano wire (spool holder)
1	cotter pin 1/8" dia., 1" long (spool holder)
2	soft iron rh rivets 1/8 x 3/8" (spool holder)
	miscellaneous screws, nuts, washers, paint, etc.

sembled. Be sure to apply a drop or two of light machine oil on the bearings when assembling the motor and install new brushes if the old ones are worn down to under 7/16 in. in length. Since these motors operate in a clockwise direction, when facing the shaft, change the direction of rotation by interchanging the two brush leads. Later, after testing the motor, adjust the insulated brush ring so that the brushes will be located at a point



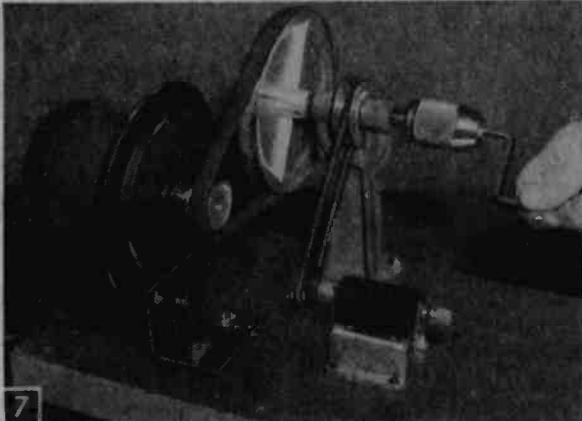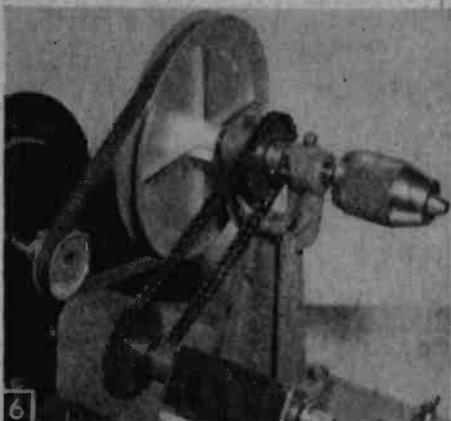

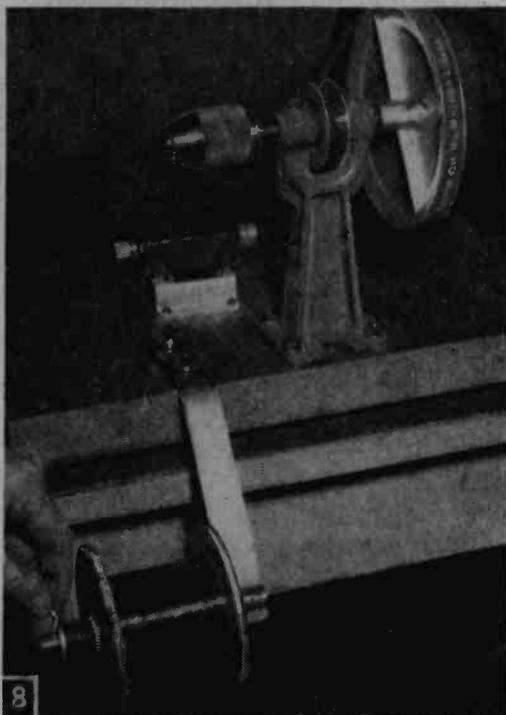Left, Alternate drive design using chain and sprocket assures positive accuracy in counting number of turns. Right, Making accuracy check of counter by turning polishing head shaft by hand a counted number of times.



A cotterpin retains spool and spring which applies braking action on spool to prevent spinning.

threaded shaft and slip the vacuum cleaner belt on the small pulley. Reassemble the shaft and place a 6 in. dia. V-belt pulley on the end of the shaft having the left-hand threads. Bolt the motor to the base first. Then, with the V-belt on the motor and polishing head pulleys pulled taut and in line with each other, mark the base for the polishing head mounting bolts, drill and fasten the head to the base. Locate and mount the counter on the base in the same way.

To check the counter drive for accuracy, mount a hand-tight drill chuck on the polishing-head spindle and grip a piece of wire bent to the shape


of a handle in the chuck jaws as in Fig. 7. Then mark the chuck or 6 in. pulley with a spot of paint or crayon so that the number of revolutions can be counted as the crank is turned. Set the counter at zero, turn the crank exactly 10 times and note the number of turns registered on the counter. If there is much of a difference in pulley diameters it will show up on the counter as over or under 10 turns. If the error in pulley diameter is only very slight, the counter will probably register accurately over so few turns. However, since even a slight error will be cumulative, it is well to try a hundred or more turns of the crank if 10 turns show up accurate. If the figures on the counter are less than the number turned by hand, it indicates the pulley on the counter is larger than the pulley on the polishing head. If the figures are more than the number turned by hand, the pulley on the counter is smaller than the polishing head pulley. You can reduce the diameter of either pulley by putting it in a lathe, if you have one or can secure the use of one, and turning the bottom of the pulley groove down. It is also possible to place a turn of narrow friction tape at the bottom of the pulley grooves to make the size correction.

After testing the counter and making the corrections if needed, make the holder for the magnet-wire spool as detailed in Fig. 5D. Fasten the holder to the base with two bolts and using nuts as in Fig. 8. If various width spools of wire are to be used, make the bar longer and drill several holes spaced to suit the spools. Allow space for the washers and spring compressed enough to supply some braking action on the spool so that when the winding is stopped, the spool will not spin around and tangle the wire.
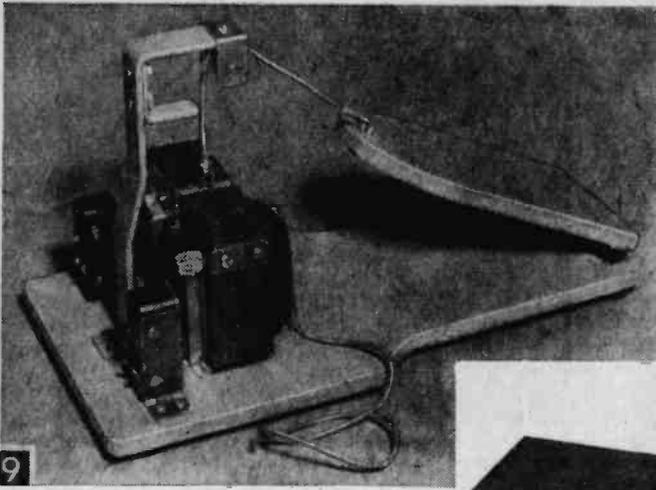
## Making Variable Speed Foot Control Switch

After completing the coil-winding machine itself, your next step is to make the variable


Left, completed foot switch showing pedal in up position, core in down position. Below, when foot pedal is depressed, core is lifted to up position.



speed, foot-control switch (Fig. 1). The variable speed foot-control switch consists of a coil and a stack of steel E-shaped laminations arranged so that the laminations can be raised and lowered in the coil (Figs. 9 and 10). The position of the laminations in the coil varies the reactance, which in turn causes a variation in the motor speed as required for winding various types of coils.

When the core is fully in the coil (Fig. 9), the reactance will be maximum and the power to the motor will be choked off to bring it to a virtual stop. On this position, the foot pedal is at its upper position and a switch arranged to be operated by the downward motion of the core will open the line to fully cut off power to the motor.

As the foot pedal is depressed (Fig. 10), the core is raised out of the coil giving a very smooth increase in motor speed until the pedal is nearly down to the base at which point the core is practically out of the coil and the motor is then running only on the impedance of the winding or nearly full speed. With further pressure on the pedal, a second switch is operated automatically to short out the coil and the motor then is direct-

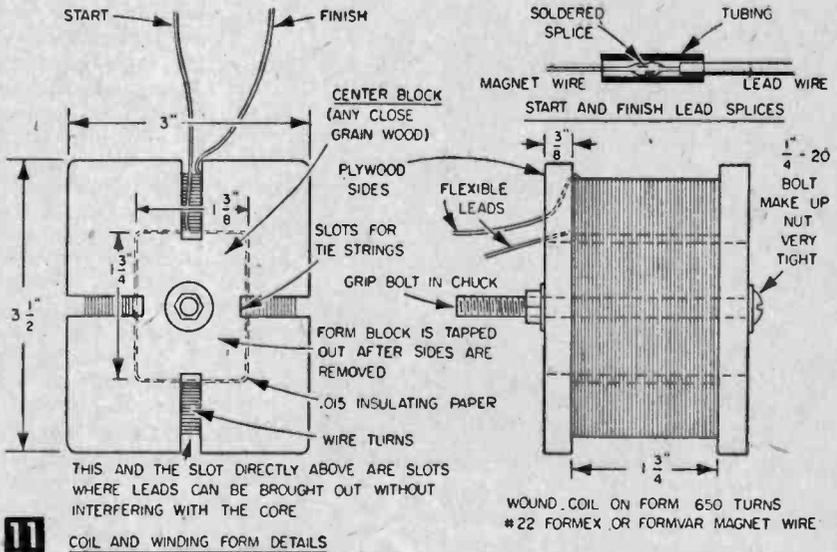

11

COIL AND WINDING FORM DETAILS

ly on the line at full speed.


Start construction with the laminated core. Obtain an old radio power transformer which has laminations of approximately the size shown in Fig. 12. Disassemble the transformer and pile up a stack of the E-shaped laminations 1 1/8 in. high. Clamp, drill and flush rivet the stack together to form a solid block as in Fig. 12.

The coil can be wound on the completed winding machine by using a temporary adjustable resistance, such as a rheostat or slide wire (Fig. 13),




series connected in the motor circuit as a test for speed control at this time. In our case it was found that about  $1\frac{1}{8}$  in. of laminations brought the motor practically to a stop which is correct. Take care not to damage the wire insulation in this test. Now, tape the coil with varnished cambric tape or cotton tape shellacked after taping, pulling it tightly and cutting the strings as they are approached. Bind the end of the cambric tape with some cellophane tape. If the coil seemed a little thick for a good fit with the core, reinsert the slightly dressed down center block and clamp it in a vise as in Fig. 16 to compress it somewhat.


Next, make up the brass core guides (Fig. 12), that provide a wearing surface for the moving core and keep it in a vertical position. Bend the "U" sections of the guides to fit tightly over the coil sides. Before soldering vertical guide pieces to main sections, place main portions on coil and test for clearance by inserting the core into the coil (Fig. 17). Bend the vertical guides to the shape of a 90° angle, and holding them in place on each side of the core so that the core will slide freely, mark their position on the main portions of the core guides. Remove the core and guides from the coil and

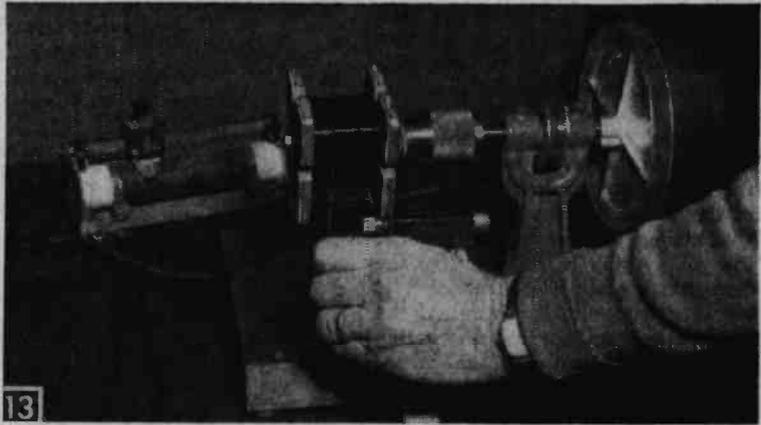

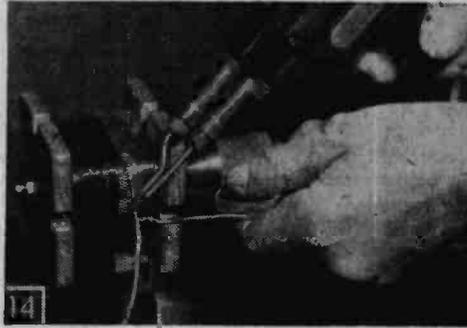
13 Winding machine is hooked up with variable resistance unit (shown in left background) to reduce speed of motor for winding reactor coil.




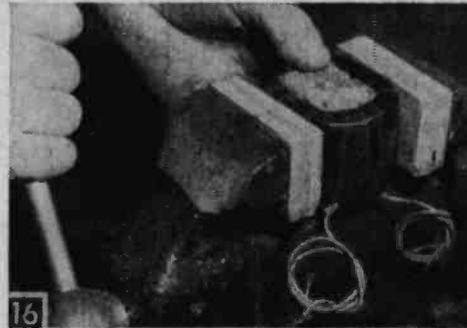14 Left, at 650th turn solder a lead on end of coil wire, insulate the splice with a piece of spaghetti tubing and carry lead out slot at narrow side of form. Right, bind the coil together before removing it from the form.




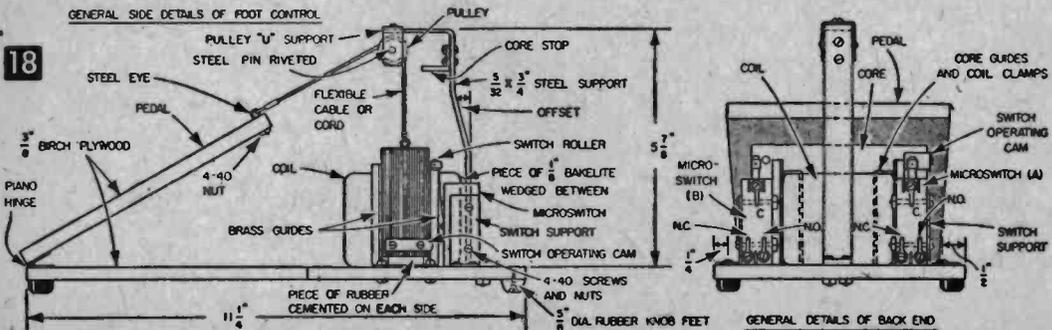16 Left, if the coil is too thick for a proper fit with the core, compress it in a vise. Right, testing core to see that it slides freely up and down in coil.



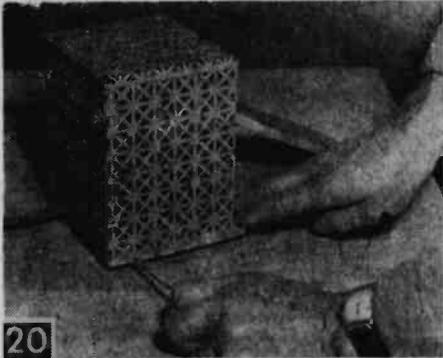

20

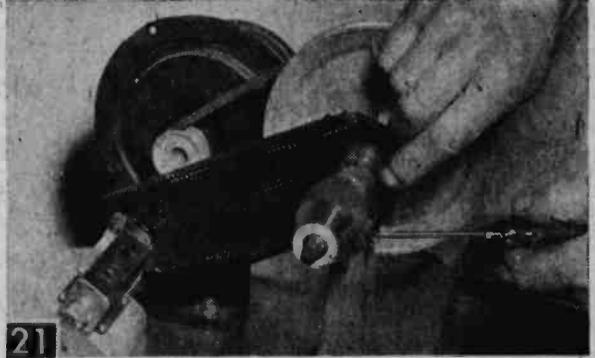

21

Left, fastening perforated metal enclosure to base with wood screws. Right, covering chain drive with guard.

solder the vertical guides to the core guides as in Fig. 12. With a sharp chisel, remove any excess solder that might interfere.

Make the base and pedal for the foot control as in Fig. 12 and fasten together with a piece of piano hinge. Bend up the bracket support core stop and switch supports from cold-rolled strip stock and drill needed holes. Turn the pulley (Fig. 12) from brass stock and make and fasten the pulley bearing bracket to the top of the bracket support with a 6-32 machine screw. If you do not have a metal turning lathe with which to make the pulley, substitute aluminum or hard maple for brass and turn the pulley on a wood-turning lathe. Assemble the pulley to the bracket with a 1/8 in. dia. steel pin riveted over lightly at each end.

Next, fasten the coil to the base with the core guides, bolting them in place. Fasten an 8 in. length of flexible wire cable, 1/8 in. dia. to the wire loop on the top of the core, feed the cable through the pulley on the bracket support and locate the support so that the core is directly below the pulley as in Fig. 18. Offset the bracket support by bending as in Fig. 18 if needed to align the pulley. Drill the end of the foot pedal and fasten an eyebolt to it for the other end of the cable. The length of the cable should be such that the core will be almost raised out of the coil when the pedal is fully down as in Fig. 10.


Fasten the core stop to the bracket support and cement pieces of rubber directly below each end of the core to serve as bumpers for the core.

Bolt two Microswitches to the switch supports and then fasten the supports to the base so that the rollers on the switches will bear lightly against the core but with actuating contacts not operated. To actuate the switches, make the operating cams (Fig. 12) and fasten to the core with 4-40 screws as in Fig. 12. Microswitch A, Fig. 18 cuts off the line current when the pedal is in the up position and core fully down. Microswitch B, Fig. 18 shorts out the coil when the core is in the up position so that the motor operates at top speed directly from the line.

Hook up the foot control switch to the coil-winder motor as shown in Fig. 19. Since the foot switch will be on the floor under the bench or table, make the cord extending from the foot switch to the motor switch about 5 ft. long. Bring this cord into the motor switch box through a notch provided in the base of the Bakelite switch that was substituted for the original motor switch.

To prevent the foot-switch mechanism from becoming damaged and yet provide ventilation make an enclosure of perforated sheet metal as in Fig. 20. Fasten the joining corners with rivets or sheet-metal screws and attach the lower edges to the base with #2 x 3/8 in. rh screws as in Fig. 20. Also make a perforated-metal guard (Fig. 21) if you are using a chain drive on the winding machine. Attach four rubber-knob feet to the bottom of the base to prevent slippage.

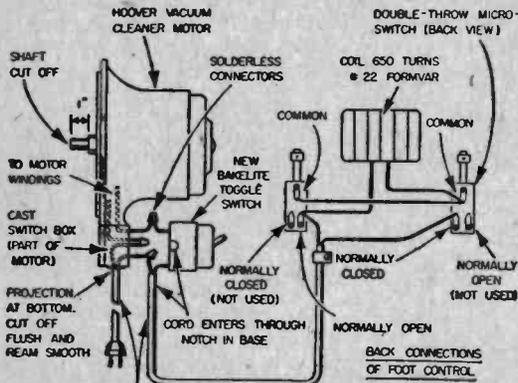When winding coils with this machine be sure that the center bolt extending through the coil form is securely tightened so there is no chance of the form slipping on the bolt. Also securely tighten the chuck holding the bolt to prevent slippage at that point. Otherwise, the number of turns indicated on the counter will be in error.



19 WIRING DIAGRAM

● Craft Print No. 265, in enlarged size for building the Electrical Coil-Winding Machine is available at \$1. SPECIAL QUANTITY DISCOUNT! If you order two or more craft prints (this or any other print), you may deduct 25¢ from the regular price of each print. Hence, for two prints, deduct 50¢; three prints, deduct 75¢; etc. Order by print number, enclosing remittance (no C.O.D.'s or stamps) from Craft Print Dept. 5511, SCIENCE AND MECHANICS, 450 East Ohio Street, Chicago 11, Illinois. Now available, our new illustrated catalog of "126 Do It Yourself Plans," 10¢. Please allow four weeks for delivery.

# Ionized Air Cloud for Super Hi Fi



By JERRY SKELLY

**T**AKE your pick with the Ionovac, a sound-reproducing cell the size of a peanut shell. With it you can tune in superb hi-fi, clean hypodermic needles, age wine, and weld metal. Or other versions of the same type of cell might even be used to kill living tissue.

A tiny cloud of ionized air, glowing a jewel-like violet reproduces and modulates the sound in this small quartz cell. High-frequency electricity, modulated according to the sounds or signals fed into the Ionovac's circuit, ionizes the cloud, making it expand and contract to mechanically push sound waves out of the cell's open end.

With the Ionovac, for the first time, ultrasonic ranges can be dialed at will instead of laboriously preset. Since no moving diaphragms or cones are used in the wasp-waisted unit, it is freed of the bonds these moving parts put on frequency response. And so not only does it reproduce audible sounds impeccably, but its notably smooth high re-

As the heart of a radio hi-fi tweeter sound reproducer, Ionovac ion cell (indicated by pencil) is mounted in a simple cast-and-sheet-metal shielding case (right). High-voltage, high frequency electricity, jiggered by electrical sound impulses from radio circuit or phono pickup, bombards air in Ionovac ion chamber, ionizing it and making it glow violet. Uncovered end of cell opens directly into the air (right and left) at base of the tweeter horn which is about 6 in. long, and 8 in. high at the bell. Upper and lower holes in bell lip take screws for cabinet mounting.




In this hi-fi addict's Sherlock Holmesian closeup nothing goes unnoticed. Small point at top is one golden ionizing electrode lead. Small wire loop around quartz chamber's wasp waist is second ionizing electrode. Air cloud is ionized in long hollow end which narrows at waist to aperture the diameter of an automatic-pencil lead. Cloud is similar electrically to earth's ionosphere.

sponse reaches well into the ultrasonic range.

The first job for the Ionovac, built by DuKane Corp., St. Charles, Ill., will be as a new type of tweeter, or high frequency speaker, in radios and high fidelity phonograph systems (as a 50-cycle woofer, for example, its horn would have to be 28 ft. long). Hi-fi enthusiasts will cheer its wide response and its freedom from the sharp hills and valleys customary with cone and compression type tweeters (see Fig. 3).

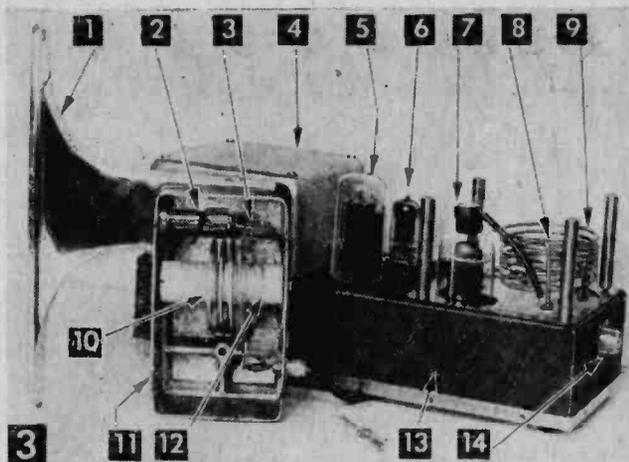Later, industry likely will be lining up to hire the sound cell. Since the Ionovac is an aperiodic device, that is, one which has no resonances and need not be used in a tuned condition



Full Ionovac layout for hi-fi tweeter assembly includes: (1) horn (2) ionizing cell (3) spring contact bracket (4) power transformer (5) rectifier tube (6) modulator tube (7) 6146 oscillator tube 20 mc (8) inner tank coil (9) outer tank coil (10) primary coil of step-up RF transformer (11) Ionovac shield can (12) secondary coil of step-up RF transformer (13) [whole unit] Ionovac power supply and oscillator (14) coaxial cable connector. Oscillator, acting as small-scale broadcasting station, sends modulated, high-frequency power to ion cell to reproduce sound impulses fed into it.

it will have many applications as a transducer to convert supersonic electrical energy into supersonic sound.

Already the little quartz cell is being considered for service in cleaning parts and garments of dust, shavings and soil. It may also be used in the supersonic aging of wines and liquors, the welding and soldering of hard-to-join metals; and the dispersion of smoke and other particles in the air.

Royal Dutch Airlines is now making totally blind touch-down landings with the Ionovac, using it to supplement aircraft radar at altitudes below 250 ft. where radar begins to lose accuracy.

Medical experiments are now being conducted to determine the usefulness of the Ionovac in the supersonic treatments of the symptoms of arthritis and bursitis. Other experimental studies are attempting to discover the effects of silent supersonic sound, radiated from the Ionovac, on various human and animal tissues. Already researchers suspect such a unit may have the

useful, if also frightening, power to control our voluntary muscles. And both frightening and encouraging are the potentialities of larger ionized-air units for breaking down living cells. DuKane is planning ultrasonic-proof labs with built-in employee protection for testing larger ionization units.

The immediate forerunner of the Ionovac was the Ionophone, invented by Siegfried Klein in Paris about six years ago. While the Ionovac's basic operating principle is the same as the Ionophone's, the DuKane unit has better materials, a higher exciting frequency, and a six-fold increase in the sound power level.

Even before the Ionophone, there were many devices aimed at reproducing sound by using modulated expanding air. Thomas Edison worked on equipment aimed at doing the job with heated air.

Between 1928 and 1931 there were at least five U.S. patents issued to inventors, including Lee DeForrest,


for ionic speakers. Many of these were highly ingenious but in general they flunked acceptance because they didn't effectively radiate their sound waves in space and could not compete in efficiency with the moving-coil loud speaker, then coming into its heyday.

With the Post-World-War II increase of interest in high fidelity sound reproduction came a new demand for the distortion-free reproduction of treble sounds. Concerns for efficiency became secondary. Full frequency range in a single speaker was not necessarily required, and the moving-coil speakers' uneven high response began to strike listeners as more objectionable.

Against this background Klein developed his

**IONOVAC FACTS**

Response	3500 cps to 40,000 cps $\pm$ 5 db
Input voltage for full output	.64 V/16 ohms—94 db. (average output from 3500-40,000+)
Input impedance	16 ohms
Level control	16 ohms T or L pad for balancing
Crossover point	3500 cps w/12 db per octave slope
Polar pattern	160° dispersion
Overall dim of unit	7 1/2" deep, 9 1/4" high, 4" wide
Osc. freq.	20 Mc.
Tubes	1-5U4GA/GB, 1-12AU7, 1-6146
Overall dim of osc.-power supply	5" wide, 12 3/4" long, 5 1/2" high
Power consumption	78 watts
Line voltage	115 V A.C., 60 cy. (105 or 125 volts w/taps)
Price	\$135 to \$150 (for transducer, horn, oscillator—marketed by Electro-Voice Corp., Buchanan, Mich.)

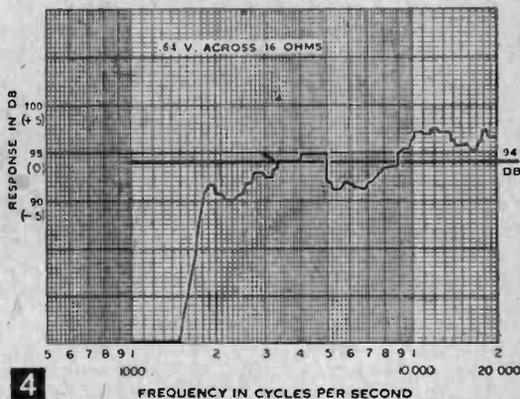

**4** In this sample response curve for Ionovac hi-fi system, note relative freedom from very sharp hills and valleys customary with mechanically actuated cone-type speakers. Besides radio-phonograph applications, ionized-air system can be used as a variable generator of both audible and ultrasonic sound waves of 1000 to 1 million cycles.


**Ionophone.** Its main contribution in the history of ionic speakers was to locate the ion chamber at the throat of an efficient horn. Yet there were still problems of corona noise, low output, and interference with nearby TV and radio equipment.

After getting sole North American manufacturing licensing for the Ionophone in December, 1955, DuKane began its work of refining Klein's Ionophone and hired Klein himself to help with the job. Also racing to do the same perfecting work were the European licensees including Plessey, Ltd., in England; Audax in France; Telefunken, in Germany, and A.E.G. in Sweden. Although DuKane was the first to develop a workable unit, its findings will be shared with other firms through a pool agreement.

**In operation,** (Fig. 5) a low current electrical field of about 15,000 volts alternating at 20 megacycles is applied between the two discharge electrodes. This intense electrical field tends to strip electrons from the outer orbits of the gas atoms of the air in the chamber. By this process, called ionization, many of the gas atoms are left positively charged ions. Since these ions are of the same charge, they tend to repel each other and their increased activity increases the total mass of the molecules in the cell, creating a sound pressure within the ion chamber and emitting a violet light. The opening in one end of this quartz chamber leads directly into the throat of a horn which efficiently radiates the air-cloud sound pressure into the surrounding area.

The number of ions is modulated by modulating the 20 Mc field. This field is developed by a single 6146 tube used as a self-excited oscillator. The 6146 is arranged to be screen modulated by the amplified audio input. Only about 1/10 of a volt of audio is needed to get the Ionovac's full acoustic output. At peaks the oscillator is modulated only about 60% to minimize distortion.

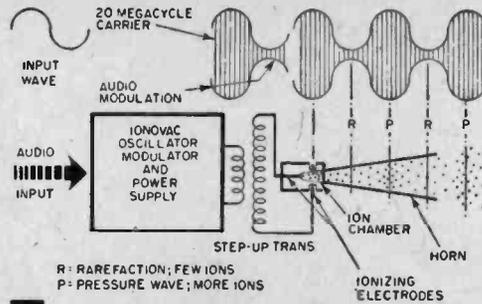As the audio signal rises, the modulated oscil-



**5 HOW IONOVAC WORKS**

Diagram of Ionovac operation traces progress and reproduction of modulated sound waves from audio input (left) through oscillator and circuitry to ion chamber and finally out into the horn and room beyond. Note fewer ions where dipping waves show decreasing sound.

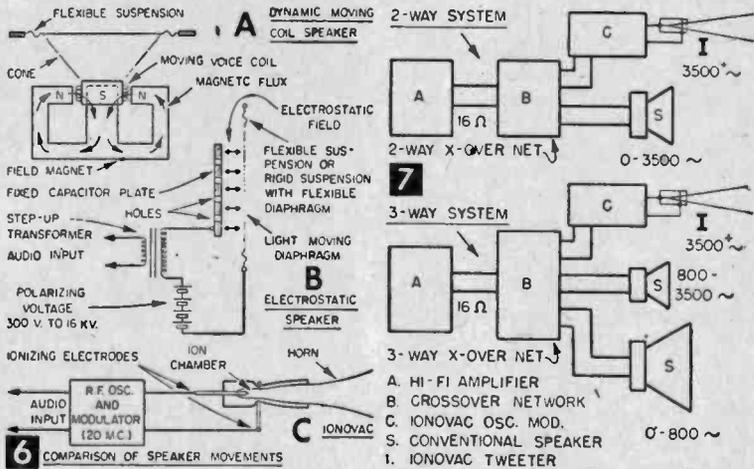


Fig. 6. Comparison of (A) moving coil speaker (B) electrostatic speaker (C) Ionovac, shows the much greater simplicity of the ion-cell's sound reproducing structure. Connecting to hi-fi layouts (Fig. 7) would not be difficult.

ator output increases. This rise in ionizing voltage boosts the number of ions available. The oscillation activity among the ions also increases, and the positive sound pressure wave which this action swells out spreads down the throat of the horn.

Then when the audio signal is modulating downwards the intensity of the ionizing field lessens. The number of ions is reduced and the sound pressure created

at the throat of the horn is less than the moment before. This is heard as a negative sound pressure wave.

**Sounds, of course,** not violet lights and ions are what you want once you've settled down for an evening of Brahms or John Philip Sousa. The elimination of mechanically moving parts lets sound be reproduced clearly; frequency response is excellent. When used as a tweeter the Ionovac has a soft, almost silky sound. There are no metallic overtones or resonances in its high sounds. Tones, harmonics and transients up to the limit of hearing come through clearly.

The output level of the Ionovac compares very favorably with that of other "super-tweeters." Good balance between treble, mid-range and bass tones should be possible in quality speaker units.

In the next few years inevitable competition between ionic speakers and electrostatic speakers should result in better units of both types.

In both audio and ultrasonic application, we stand to hear—or not hear—much more about the tiny, ionized cloud and the work it does.


# ELECTRONIC TIC-TAC-TOE

By  
BERNARD  
DICKMAN



IT'S also spelled Ticktacktoe and also called Tit-Tat-Toe (in England, they call it Naughts and Crosses), but by whatever name it goes under, chances are you've played it—two horizontal lines, two vertical on a piece of paper. One player takes the naughts (O); the other, the crosses (X), and each takes his turn placing his symbol in one of the spaces on the paper until—either vertically, horizontally or diagonally—he has three crosses (or three naughts) in a row, or until it becomes impossible for either player to make such a combination. And, of course, while one player is attempting to place three of his symbols in a row, the other player—in addition to trying to do the same—must attempt to block his opponent. Actually, it's a fairly simple struggle of wits (with 15,120 possible combinations of moves). Simple enough, however, for an assortment of switches built into a panel to have mastered it.

The device in Fig. 1 contains those switches and, as originally built, a human being was doomed to a draw or worse in every encounter with the unit. (As modified, you and I now stand a chance of winning; but more of the modification later.) The "brains" of the device are two rotary switches. Its move-signaling apparatus consists of nine slide switches and nine GE222 flashlight bulbs powered by two 1½-v. 935C dry cells in series.

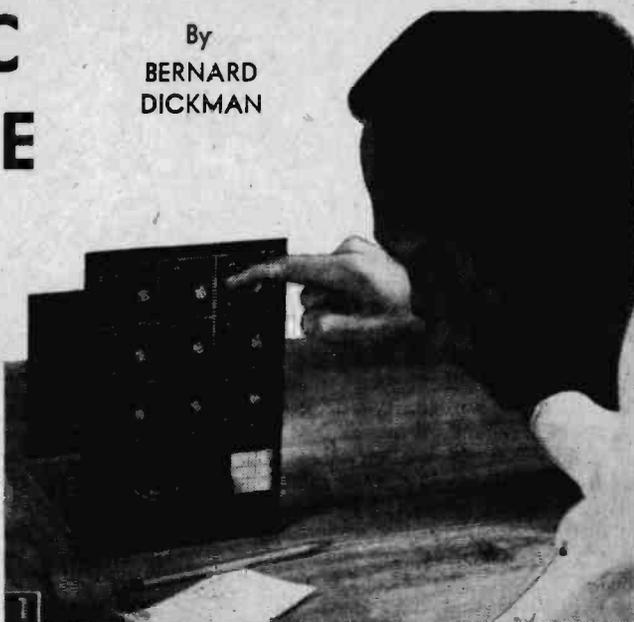To construct this electronic Tic-Tac-Toe, first saw out, sand smooth and shellac a ¾-in. piece of pine or plywood 6 x 6 in. square. This is the block chassis of the unit. The front



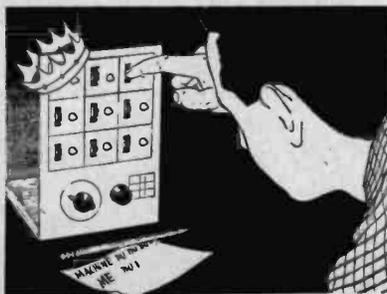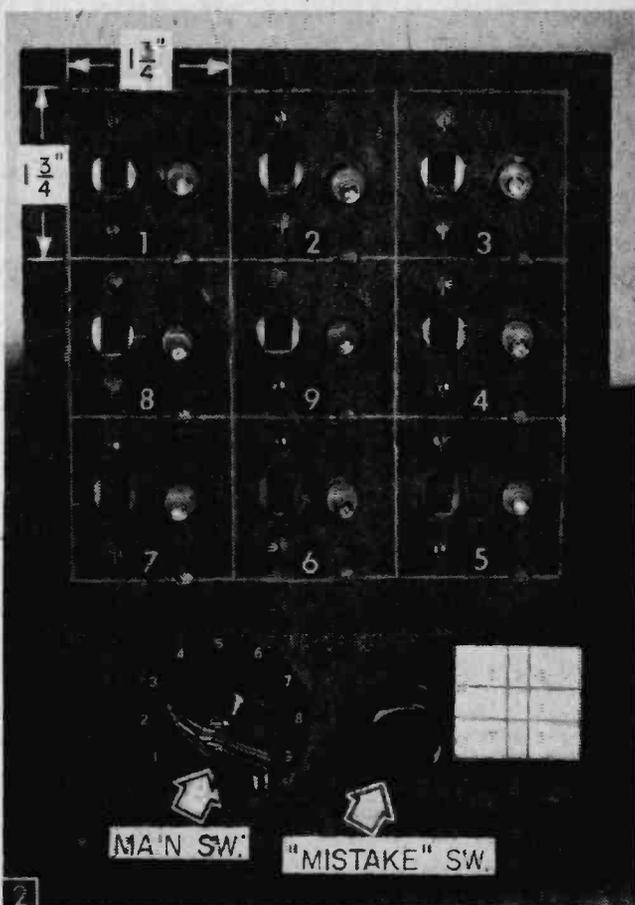
Man against Machine! And the odd thing is, the machine has to be handicapped in order to afford the man half a chance.




panel is made from 1/8-in. tempered hardboard to the dimensions given as shown in Fig. 2. Incise the square lines and fill them with white paint to make them stand out. The back panel is also 1/8-in. tempered hardboard, cut to a 6 x 6-in. square.

After cutting out chassis and panels, take the nine slide switches and paint white that area of the switch visible when it is turned on. Let dry and then install the slide switches and the nine bulb sockets, bending the Dialco 505 socket arms to a right angle (as shown in Fig. 3) for proper mounting on the front panel. Mount the nine-deck and the two-deck rotary switches and, using #20 wire or smaller, begin wiring. Wire as shown in Figs. 3 and 4, color-coding your wiring wherever possible to make any error tracing easier. In many cases, wiring on the deck switches can be stripped and brought directly from one terminal to the next.

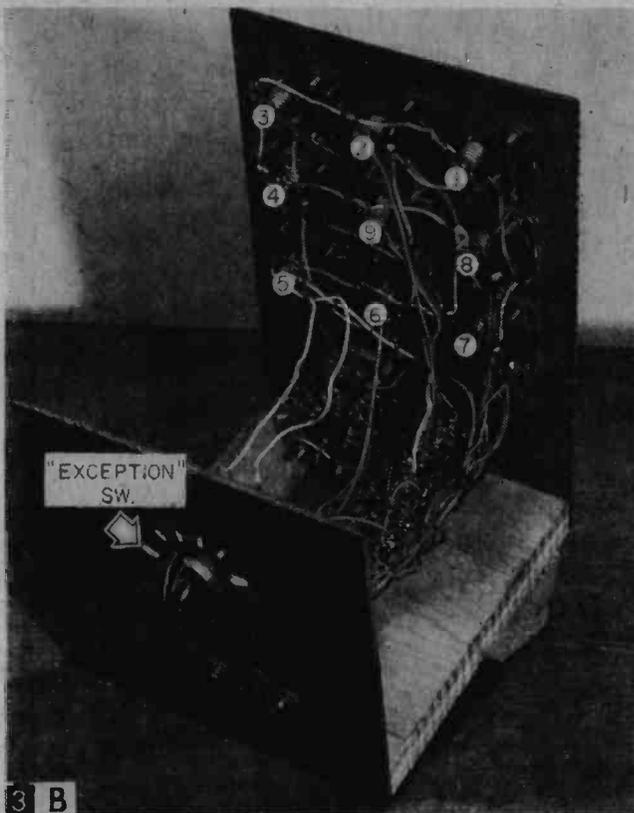The multi-gang, nine-deck, 10-position per deck rotary switch is the unit's main switch. The pole of each deck on this switch is connected to a slide switch (see Fig. 4A). Each of the nine other positions is wired into



Back of panel view of machine.

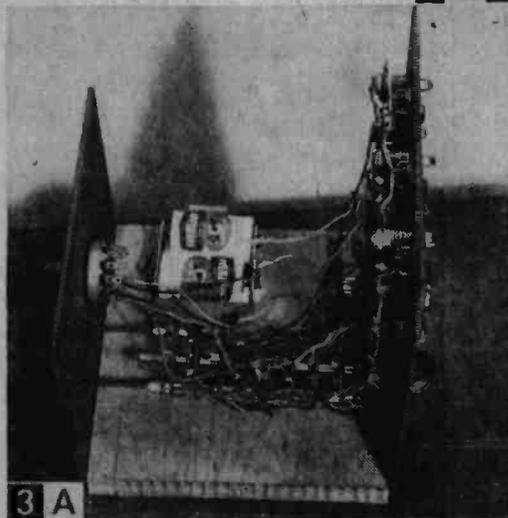

the circuit of one of the nine Tic-Tac-Toe squares.

Either you or the machine can make the first move in a game. If you are going to make the first move select a square, turn the rotary switch to that number and press down the slide switch.

**Machine's Turn First.** If the machine is to make the first move, turn the rotary switch to the 10th position (which you can label "M" on the dial plate of the rotary switch). Then flick the slide switches until a bulb in the same square as a

switch flicked lights: this is the machine's move. If you wish to modify the machine so that it makes its move automatically (without your flicking slide switches), add another phenolic deck section to the nine-deck switch and wire the 10th position of this deck directly to bulb nine, bypassing switch nine; the pole of this added deck goes directly to battery. With a 10th deck added, the machine will make its first move to the bulb of square nine automatically.


The single pole "off" plus four-position switch on the back panel is the "Exception" switch. The main circuit of the Tic-Tac-Toe is wired to reply

MATERIALS LIST—ELECTRONIC TIC-TAC-TOE

No.	Description
9	Non-shorting, one pole, 2-11 <sup>o</sup> pos. per pole, phenolic sections (Allied 35 B 085).
1	Shaft (9 sections) and index (30 <sup>o</sup> ) assembly (Allied 35 B 094).
1	two gang, 4 pole, 4** pos. per pole, non-shorting, switch (Allied 34 B 257).
9	SPST slide switches (Allied 34 B 422).
9	miniature screw pilot light sockets with socket arms (Allied 52 E 410).
9	miniature screw lamps—GE222 (Allied 52 E 330).
1	non-shorting, one pole, 5 pos. switch (Allied 34 B 350).
1	wood chassis (see text)
2	1 1/2-v. 935C dry cells.
	wire, solder, unmarked dial, dial plates

\* Only 10 pos. needed

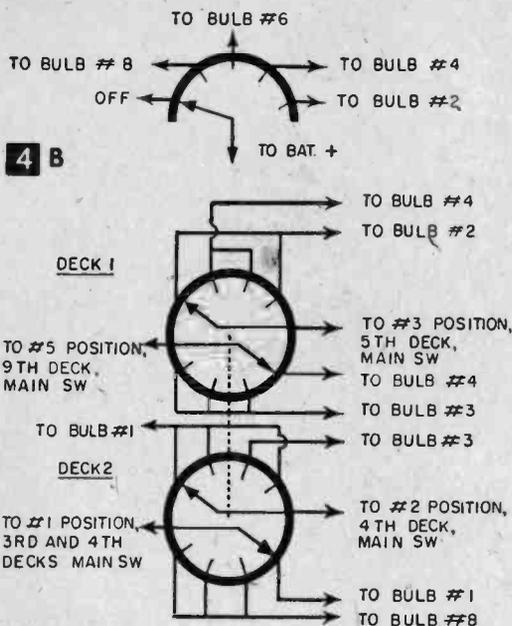\*\* Allied sw. is 5 pos.—one pos. not needed



**4 B** "MISTAKE" SWITCH


to logical moves. If you fail to play logically, it will occasionally happen that the machine will attempt to reply to such a move in a square already occupied. If this should occur—and such occasions are rare—flip the "Exception" switch to a different position. (If you have played in square 7, and need to use this switch, turn it directly to 4.)

The "Exception" switch is wired as shown in Fig. 4B. Its "exceptions" are for squares 8, 6, 4 and 2 for 1, 2, 3 and 4. For example, suppose you are occupying squares 1 and 7, the machine squares 8 and 9. Your *logical* move would be to square 4 to block the machine, but you move to square 6 instead. In such an instance, you would have to use the "Exception" switch.

The two-gang, two poles per gang, four positions per pole switch on the front panel (remove this switch's "off" position) is the "Mistake" switch. Without it, a player would be unable to win a game against the machine. It is wired as shown in Fig. 4C. Do not label the dial of this switch—so that you won't become familiar with the machine's mistakes—but occasionally flip it to a different position.

Extra mistakes can be introduced into the machine by modification of its circuitry. A three-deck, two poles per deck, six positions per pole switch, for example, would enable you to introduce six sets of mistakes into the machine's replies.

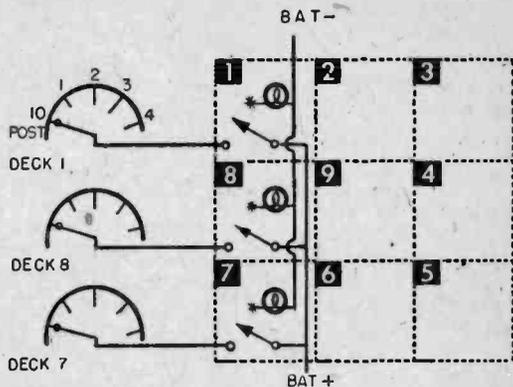For the machine as wired in Fig. 4, however, the mistakes are: 1) your play—corner 3, machine's reply—1 to 8 (instead of 2); 2) your play—side 4, machine's reply—1 to 8 (instead of 2), 2 to 3 (instead of 1); 3) your play—center 9, machine's reply—5 to 4 (instead of 3); 4) your



**4 A** BULB AND SLIDE SW SCHEMATIC (WIRING OF SLIDE SW # 2, 3, 4, 5, 6, AND 9 IS DONE IN THE SAME MANNER; SLIDE SW TO POLE ON ITS DECK AND TO PLUS OF BATTERY.)

\*AS SHOWN, ONE SIDE OF EACH BULB GOES TO MINUS SIDE OF BATTERY; THE OTHER SIDE OF EACH BULB IS WIRED AS FOLLOWS TO THE 9 DECK, 10 POSITION ROTARY SWITCH (POST IS #10 POSITION):

DECK	POSITION	DECK	POSITION
1	3 2	6	7 3, 4, 5
	2 3, 4, 10,		5 7, 8, 10
	8 3, 4, 5, 6, 7		2 9
	7 8		3 9
2	9 9	7	6 1, 2, 3, 4, 5
	3 7, 8		8 1, 2, 10
	1 3, 4, 10		5 6
3	6 9	8	1 8
	2 1, 5, 6, 7, 8		7* 1, 2, 10
	1 2		1 5, 6, 7
	5 4, 9		4 9
4	4 5, 6, 10	9	1 1
	7 9		2 2
	5 1, 2, 3,		3 3
5	8 9	4 4	
	3 5, 6, 10	5 5	
	4 1, 2, 3, 7, 8	6 6	
	3 4	7 7	
	7 6	8 8	
	6 7, 8, 10	9* 10*	
		10** 10**	

POS. #10 IS MACHINE'S TURN.  
 \* SEE TEXT: MACHINE'S TURN FIRST (NOT AUTOMATIC)  
 \*\* SEE TEXT: MACHINE'S TURN FIRST (AUTOMATIC)

play—corner 5, machine's reply—2 to 3 (instead of 4).

"Your play" indicates your first move. For example, the perfect reply to your moving first into square 4, then into square 1 (as in the second example above) would be square 2; but instead of this move, the machine mistakenly replies in square 8—and thus allows you to retain some vestige of self-respect. But, then, if you should lose too often in spite of this modification to handicap the machine, remember—you built the device, and you have only yourself to blame.



# 1 JUNIOR-SIZE RECORD PLAYER

By HOMER L. DAVIDSON

**T**HOUGH it won't reproduce sound quite so faithfully as a \$400 hi-fi radio-phonograph combination, this cigar box record player will deliver plenty of volume for the small one to play his favorite records by, and the quality of that volume is as good as that delivered by any one-tube phono.

A CK722 transistor, driven by an L12 crystal pickup, provides audio amplification, a 10 mfd capacitor isolates the pickup arm, the base return resistor is 220,000 ohms—a minimum of circuit components for the amplifier itself. The pickup arm (see Fig. 1) is a 1 x 11-in. piece of ¼-in. plywood fastened to a home-made, scrap-metal swivel, with the crystal cartridge bolted into place at the opposite end of the arm. Drill a hole at the bottom of the swivel's U-shape, insert a bolt through swivel and box, place a large washer top and bottom and then tighten the


Mostly for junior, this small record player has a minimum of circuit components compactly encased in a cigar box.

bolt's nut just enough so that the arm in the swivel swings freely. Then solder the nut to the bolt so that it will not loosen in use.


Wire as indicated in Fig. 3, connecting one side of the primary of a universal output transformer to the collector of the transistor, the center-tap to the resistor and back through the D.P.S.T. slide switch to the batteries.

There is no special way that the turntable motor, battery, circuit components and speaker should be mounted inside the cigar box, but the layout shown in Fig. 2 works well. Cover the opening for the speaker in the lid of the cigar box with grille screen and cloth, and after the unit is completed, nail the lid tightly shut so that there will be no danger of a child investigating the house-line connections to the turntable and switch.

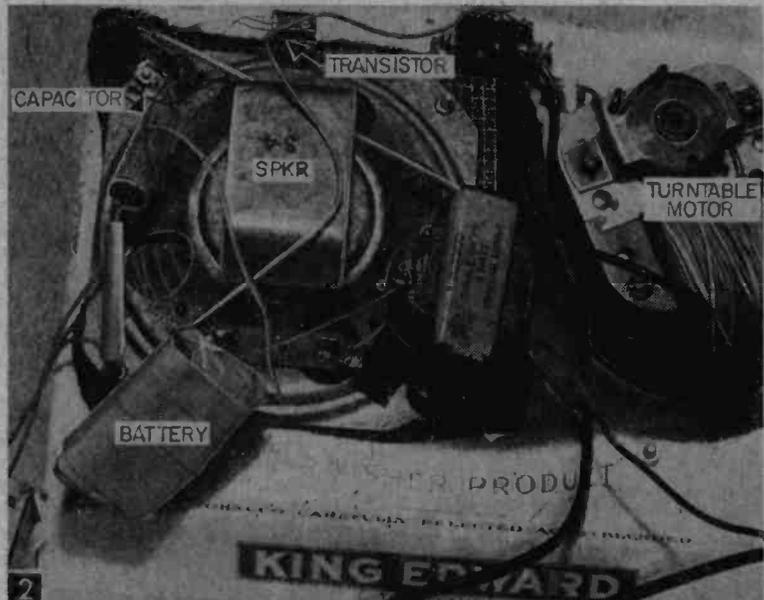This small phono has no volume control and



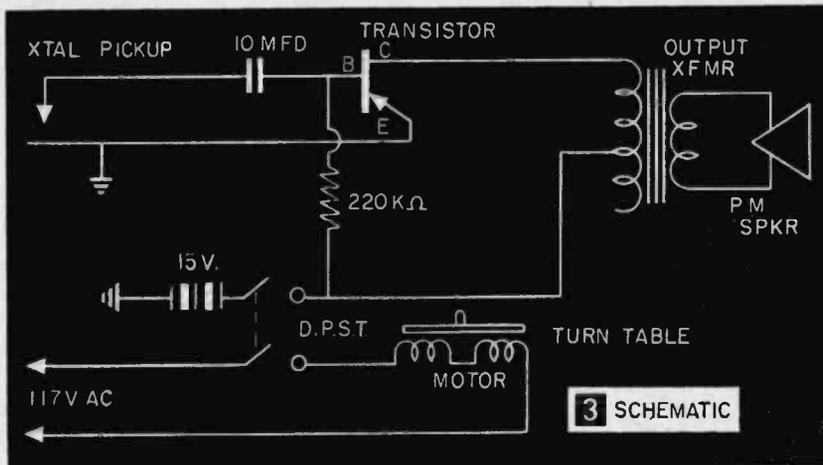Underside of lid shows location of circuit components and turntable motor. Line cord carrying house voltage enters through grommet in back of box.



3 SCHEMATIC

ordinarily its volume will not be disturbingly loud. But by changing the size of the 220K ohm resistor the volume and tone quality can be varied. Before experimenting with such a change, however, insert a 0 to 10 ma meter in series with the battery so that the transistor will not be damaged. The transistor should never pull over 5 ma; with the fixed value of resistance given in Fig. 3 and the Materials List, transistor current is slightly over 2 mills. Be sure to observe correct battery polarity.

MATERIALS LIST—JUNIOR-SIZE RECORD PLAYER

No.	Description	No.	Description
1	crystal pickup (L12 Astatic)	1	CK722 transistor (Raytheon)
1	10 mfd., 25 v. paper capacitor	1	D.P.S.T. slide switch
1	220,000 ohm, 1/2-watt resistor	1	78 rpm turntable
1	universal output transformer (Merit A2900)	1	4", permanent magnet speaker

Miscellaneous screws, nuts, bolts; 6' line cord; empty cigar box; grille screen and cloth; 1-15 v. battery.

BATTERIES FOR ELECTRONIC APPLICATIONS

This list contains all batteries in general use. Those not listed are special types not usually stocked by electronic supply shops. (Hearing aid type batteries are included, however, since many small radios use them.)

PORTABLE "A" BATTERIES							PORTABLE "AB" BATTERIES (Cont.)								
RCA Type	Volts	Size	Wt. Ea. Lbs.	Interchangeable with			VS064								
				Burgess	Eveready										
VS036	1	1 1/2 x 2 3/8"	6 oz.	2R											
VS004	1 1/2	2 3/8 x 2 3/8 x 4 1/8"	1	4F	742										
VS073	1 1/2	1 1/2 x 1 1/2"	2 oz.												
VS236	1 1/2	1 1/2 x 4 1/8"	7 oz.												
VS069	1 1/2	2 3/8 x 1 1/2 x 2 3/8"	3/4	2D	720										
VS072	4 1/2	3 1/2 x 1 1/2 x 2 1/8"	1	D3	726										
VS067	4 1/2	4 x 1 1/2 x 4 1/8"	1	F3	736										
VS009	6	1 3/8 x 2 3/8 x 4 1/8"	1 1/2	F4P1	744										
VS068	6	2 3/8 x 1 1/2 x 2 1/8"	1 1/2	Z4	724										
VS065	7 1/2	2 3/8 x 2 x 3 1/8"	1 3/4	C5	717										
PORTABLE "B" BATTERIES							PORTABLE "AB" BATTERIES (Cont.)								
VS084	22 1/2	1 1/4 x 5/8 x 1 3/8"	2 oz.	U16	412		VS064	1 1/2-90	7 1/4 x 2 1/8 x 3 3/8"	3 3/4					
VS085	30	1 1/4 x 5/8 x 2 1/8"	2 oz.	U20	413		VS050	6-7 1/2-75	8 3/8 x 2 1/8 x 3 11/16"	4					
VS013	45	3 3/8 x 1 1/2 x 5 1/8"	2	M30	482		VS046	8-75	12 3/8 x 2 3/4 x 4 1/8"	8					
VS014	45	3 3/8 x 2 1/8 x 4 3/8"	1 1/2	A30			VS019	7 1/2-9-90	8 1/2 x 2 1/8 x 4 3/8"	6					
VS015	45	3 x 2 1/8 x 4"	1 1/2	230	738		VS057	7 1/2-9-90	8 3/8 x 2 1/8 x 3 3/8"	4					
VS055	45	2 3/8 x 1 1/2 x 3 1/8"	3/4	XX30	455		VS057W	7 1/2-9-90	8 1/4 x 2 1/8 x 3 3/8"	4					
VS016	67 1/2	2 3/8 x 1 1/2 x 3 3/8"	1	XX45	487		VS119	7 1/2-9-90	8 3/8 x 4 1/8 x 1 3/8"	2 1/2					
VS218	67 1/2	1 1/2 x 1 1/2 x 5 1/8"	1				VS038	7 1/2-83	8 5/8 x 2 3/8 x 4 1/8"	5					
VS217	75	1 1/2 x 1 1/2 x 6 1/8"	1				VS047	9-90	13 3/8 x 2 3/8 x 4 1/8"	8					
VS090	90	3 1/2 x 1 1/2 x 3 3/8"	1	N60	490		VS058	9-90	8 1/2 x 2 1/8 x 4 3/8"	5					
PORTABLE "AB" BATTERIES							INDUSTRIAL BATTERIES								
VS052	1 1/2-61 1/2	8 3/8 x 2 1/8 x 3 3/8"	4	4GA41			VS034	1 1/2	1 1/4 x 2"	2 oz.	Z	915			
VS043	1 1/2-90	5 1/2 x 2 1/8 x 7 1/8"	5	41A4G			VS106	1 1/2	2 1/8 x 2 1/8 x 4 3/8"	1 1/4	4FH				
VS054	1 1/2-90	10 x 2 1/8 x 4 1/8"	5	5DA60			VS006S	1 1/2	2 3/8 x 8 3/8"	2 1/8		6			
				6TA60			VS130	1 1/2-3-4 1/2	3 1/8 x 1 1/8 x 3"	1	2370BP	761T			
							VS029	1 1/4-7 1/2	3 1/8 x 1 1/8 x 3 1/8"	2	515SC	778			
							VS028	4 1/2	4 1/8 x 1 1/8 x 2 3/8"	1 1/2	5360	781			
							VS040S	6	2 1/8 x 2 1/8 x 4 3/8"	1 3/4	F4BP				
							VS102	22 1/2	3 3/8 x 2 1/8 x 2 3/8"	1 1/4	4155	763			
							VS112	22 1/2-45	4 1/8 x 2 3/8 x 5 1/8"	3 1/4	5308	762S			

Batteries listed can be purchased at your local electronic supply shop or from the manufacturers: Burgess—The Burgess Battery Co., Dept. SM, Freeport, Ill. Eveready—National Carbon Co., Eveready Div., Dept. SM, 30 E. 42nd St. New York 17, N. Y. RCA—Radio Corp. of America, RCA Bldg., Dept. SM, 30 Rockefeller Plaza, New York 20, N. Y.



MATERIALS LIST—BATTERY CELL TESTER

No.	Description	Use
1	metal cabinet, gray finish, sloping panel $4\frac{1}{2} \times 4\frac{1}{4} \times 7\frac{1}{2}$ " ICA #3906 Allied Radio Cat. #86P381, \$1.72.	
1	$2\frac{1}{2}$ " panel meter, 0-1 ma. d-c; or d-c voltmeter 0-3 volts. Allied Radio, 100-SM N. Western Ave., Chicago 80, Ill. or from surplus stores.	
1	push button, momentary contact switch for panel mounting. Switchcraft "Littel Switches" Type #201. #34B947 from Allied Radio. Can also use Grayhill Type 4001 or 23-1 switch, stocked by most supply stores and mail-order houses such as Allied Radio (#34B870 and #34B890 respectively.)	
1	2000 ohm, $\frac{1}{2}$ -watt carbon resistor (not needed if voltmeter is used).	load resistor
1	8.2 ohm, 1-watt carbon resistor	
1	two-terminal chassis terminal strip (or tie-point)	
1 pc	birch plywood $\frac{3}{16} \times 7\frac{1}{2}$ "	back panel
1 pc	sheet copper .015 x $1\frac{3}{8} \times 7$ "	bottom contact strip
1 pc	phosphor bronze or hard brass .016 x $\frac{7}{16} \times 4$ " (can be scrap from metal working shops or electrical equipment)	spring contact clips (D, C and Z cells)
1 pc	phosphor bronze or hard brass .010 x $\frac{7}{16} \times 1$ " (see above)	spring contact clip (#7 cells)
14	4-40 roundhead plated machine screws with nuts	
	Dull black paint, hook-up wire	




Use a circle cutter or similar tool in the drill press to make opening in metal cabinet to fit meter. Fix a wood block inside and clamp the piece securely.


still further until a point is reached where they are no longer useful.

The meter used here (primarily because it is easily obtainable in surplus stores) is a 0-1 d-c milliammeter, with a 2000 ohm,  $\frac{1}{2}$ -watt resistor in series which serves as a voltmeter. Since a fresh cell indicated exactly .8 on this meter, this reading was used as a voltage standard for good cells. If a d-c voltmeter is used (without the 2000 ohm,  $\frac{1}{2}$ -watt resistor), a good cell will register about 1.5 volts.

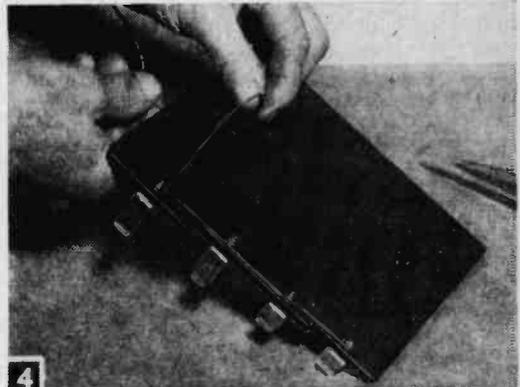In operation, cells are placed one at a time under the spring clip that gives the proper spacing from the contact strip attached to top of cabi-



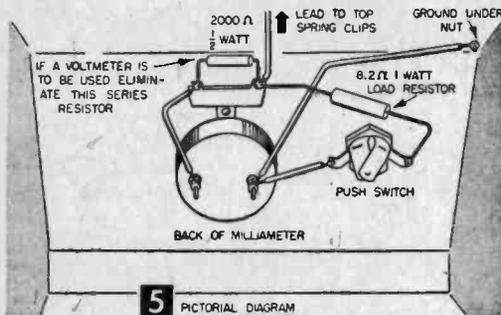Attach spring terminal clips loosely to back panel with short 4-40 screws and nuts, and wire clips together as shown. Carry the wire through a drilled hole to other side.



Wire connections inside the cabinet are very simple, with two resistors required as shown.

net. The cells accommodated by this tester are D, C, Z and No. 7, size designations used by Burgess and some other manufacturers. In general, these cells fit various flashlights including penlights and are used in flashgun equipment and in a number of laboratory and test equipment instruments.

The photoflash (D) cell shown in Fig. 1B shows about .7 on the meter or two divisions below the .8 standard for a good cell. An accurate voltmeter would show this value as about 1.4 volts. To find out if this cell is still usable, press the button at the left of the meter as shown in Fig. 1A. This places a load of 8.2 ohms across the battery. Take a quick reading and release push button immediately, since the load applied in this manner could run the cell down if applied for a prolonged period. With button depressed, the meter shows a drop to .45 on the scale, which indicates that the cell is in poor condition and should be discarded. In general, a drop of only one or two divisions on the scale is all that should be indicated for a usable cell.

Before placing cells in position on the tester, see that the bottom of the zinc cell is clean and

the outer paper casing is up a short distance from the lower edge so that good contact with the copper strip will be assured.

First step in building tester is to cut out the large opening in the purchased metal cabinet for the meter (Figs. 2 and 3). Next, cut bottom contact strip from sheet copper, clean up the piece thoroughly with fine sandpaper and attach it to the top of the cabinet with 4-40 screws and nuts through drilled holes (Fig. 2). Also drill holes at the edge of the meter opening for attaching meter and a 3/8 in. dia. hole to the left of the meter opening for the push-button switch. Attach meter with 4-40 screws and nuts, insert push-switch and tighten nut on switch neck.

Cut back panel from a piece of 3/16 in. birch plywood, bakelite or hardboard (Fig. 2), and sand carefully. Drill holes as indicated and apply two coats of dull black enamel.

Form spring contact clips from phosphor bronze or hard brass and attach to back panel with 4-40 screws and nuts, with nuts loosely in place. Connect clips together at the back side with #20 insulated wire, bared for a length rep-

resenting the spacing of the clips and attached under the 4-40 nuts. Carry the insulated portion of the wire through 1/8 in. dia. hole bored in panel to inside of cabinet (Fig. 4). Tighten screws to make firm contact with wire at back.

Complete wiring of components (Figs. 5 and 6), attaching a two-terminal strip under the nut of the top meter screw and connecting a 2000 ohm, 1/2-watt resistor across the terminals. Solder the wires going to these terminals in place. An 8.2 ohm, 1-watt load resistor connects from one side of the push-button switch to the terminal where the lead coming from the four contact clips is attached, which puts this resistor across the cells when the button is pressed. Attach the ground lead under one of the nuts used to secure the contact strip to cabinet.

The final step is to attach the board to the back of the cabinet with 4-40 screws (Fig. 2) in holes drilled and tapped in the cabinet edge. Take a no-load reading on the completed tester, using a new fresh cell, and glue a pointer cut from green paper to glass or dial to indicate this standard for future readings.

### Rule Doubles as Antenna


• A flexible steel rule, connected to the antenna lead of a small radio will improve reception in certain areas when used as a wand aerial. It may be extended to about 30 in. with stability and can be placed at the rear of the cabinet. A small alligator clamp or paper clip soldered to the lead from the set provides a handy removable connection.—R. L. HAY.


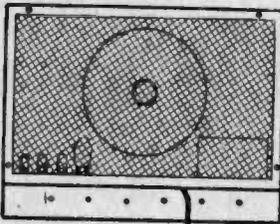
### Ventilate Your TV Set


• Television sets develop a lot of heat and sometimes the only provision for ventilation is a series of holes punched in the back panel. Continued overheating can shorten the life of those costly television tubes.

To get more ventilation, replace the panel with a simple frame covered with plastic screen such as is shown above.—W. H. McCLAY.



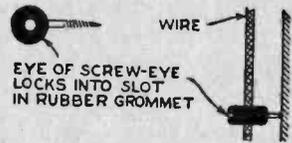
### Stand-Off Insulators from Screw Eyes

• Rubber grommets pressed into the eyes of screw-eyes make handy insulators for wires in radio and electrical work. Make up a collection of variously sized insulators.—A. TRAUFFER.




### Emergency Battery Clip

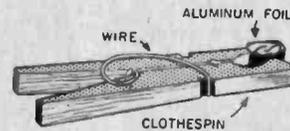

• If you run out of battery clips while doing an electrical project, make a substitute clip by wrapping aluminum foil around the tips of a spring-type clothespin. Wrap wire around foil.—J. HARVEY.
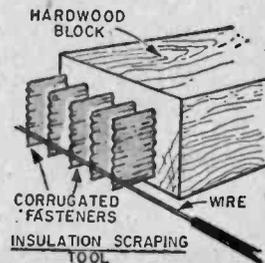
### Insulation Scraping Tool

• This simple and long-lasting tool is practical for scraping and cleaning insulated wire to make firm solder connections. To make it, simply drive several corrugated fasteners into the end of a hardwood block.—G. E. HENDRICKSON.



# Get All the Sound You Pay for with This Fidelity Amplifier

## FIDELITY AMPLIFIER SPECIFICATIONS

Full range Bass and Treble controls  
Self-balancing phase-inverter system  
Beam power push-pull output with inverse feedback  
Multi-impedance output transformer  
Built-in pre-amplifier for magnetic and reluctance pickups  
FREQUENCY RESPONSE:  $\pm 1.5$  db. from 20-20,000 cps at 2 watt output  
DISTORTION: Less than 2% at 2 watts  
OUTPUT: Maximum 10 watts  
POWER REQUIREMENTS: 70 watts on 105-125v., 60 cy. line.

**H**IGH-FIDELITY amplifiers bring out the best in present-day 33 and 45 rpm phonograph records. And a lot of "best" is built into these records. Phono pick-ups, and the right combination of speakers also add to the quality of sound reproduction, but these are packaged items that the audiophile should select himself.


This 10-watt amplifier (based on the Arkay brand A-12 Hi-Fi Kit), has all the features and the appearance of commercially made equipment and can be built in a few hours. Unlike many types of electronic apparatus, it does not require exacting circuit adjustments once wiring has been completed. If all connections have been made correctly, this amplifier is ready to go as soon as you connect a record player or radio tuner to the phono input jacks, and a PM speaker or speakers to the output terminals.

The pre-punched chassis measures  $11\frac{1}{4}$  in. long,  $6\frac{1}{4}$  in. wide, and  $2\frac{1}{4}$  in. high. The top of the chassis is punched with six 1-in. holes for mounting five octal pin tube sockets, and a three-section electrolytic filter capacitor. A rectangular opening,  $2\frac{3}{4}$  by 2-in. is provided for the power transformer.

Selector Switch, Volume, Bass, and Treble (line switch) controls mount on the front apron of the chassis (Fig. 1). The  $\frac{3}{8}$ -in. mounting holes for them are spaced  $2\frac{1}{4}$ -in. apart, and located so that the escutcheon plate holes will coincide with them. The rear apron of the chassis

For quality sound reproduction, build this 10-watt, true-fidelity amplifier

By THOMAS A. BLANCHARD

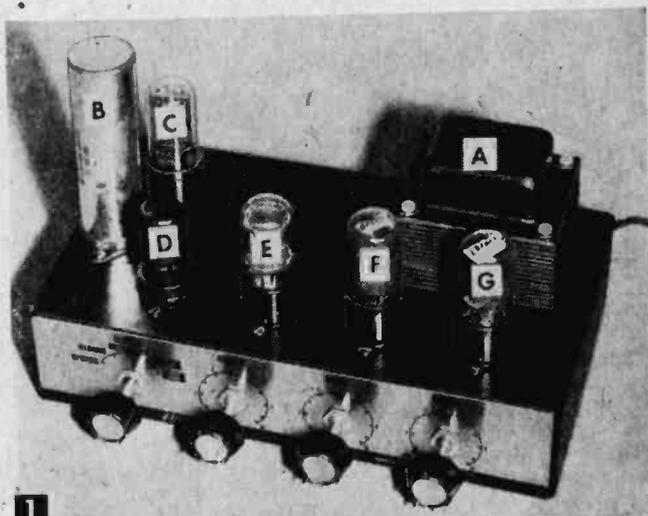

Completed amplifier. Controls, left to right, are: Selector Switch, Volume, Bass, and Treble (line switch) controls. Escutcheon plate may be removed from chassis and mounted on cabinet if unit is enclosed. Parts shown are: A) power transformer; B) electrolytic capacitor; C) 5Y3GT rectifier; D) 6SC7 dual pre-amplifier; E) 6SLF interstage amplifier and phase inverter; F & G) 6V6 beam power push-pull output amplifiers.

contains four  $\frac{3}{8}$ -in. holes, three of them for phono jacks and one for the line cord rubber grommet. The phono motor receptacle's size and shape will determine hole or slot size for it. The Na-ald receptacle shown in Fig. 3 fits the prepunched  $\frac{3}{8}$  by  $\frac{3}{4}$ -in. opening. The final chassis opening is a 2 by  $\frac{1}{2}$ -in. slot on the rear apron of the chassis for the output terminal strip.

The first step in assembling the amplifier is to mount all screw-down components to the chassis. The power transformer comes with its own nuts and bolts. The nuts are removed, then used to bolt the unit securely to the chassis so that the transformer's laminations will not chatter when power is applied. Tube sockets are mounted with 6-32 x  $\frac{1}{4}$ -in. machine screws and nuts as are all other components except the phono jacks. For these, 4-40 x  $\frac{3}{8}$ -in. screws and nuts are employed.

The advantage of using the saddle type tube







# Portable Hi-Fi Record Player

By ELMA WALTNER






in this portable phonograph are quite good, and relatively low in cost (the whole project, in fact, will run about \$10 for cabinet materials, and roughly \$100 for Hi-Fi components, depending on where you buy). You can't, of course, get perfect reproduction with any table top project, since the small size restricts both the tricks you can play with speakers, and the space you can use for sound-boarding layout. But we did find that cabinet resonance can be effectively

If you like hi-fi, you'll appreciate this phonograph. Its portable, table-top size makes it possible to enjoy superb orthophonic listening in any room of the house, or outdoors wherever a cord for supplying current will reach or can be plugged in. The hi-fi components used

damped out by a generous use of fiber glass insulation.

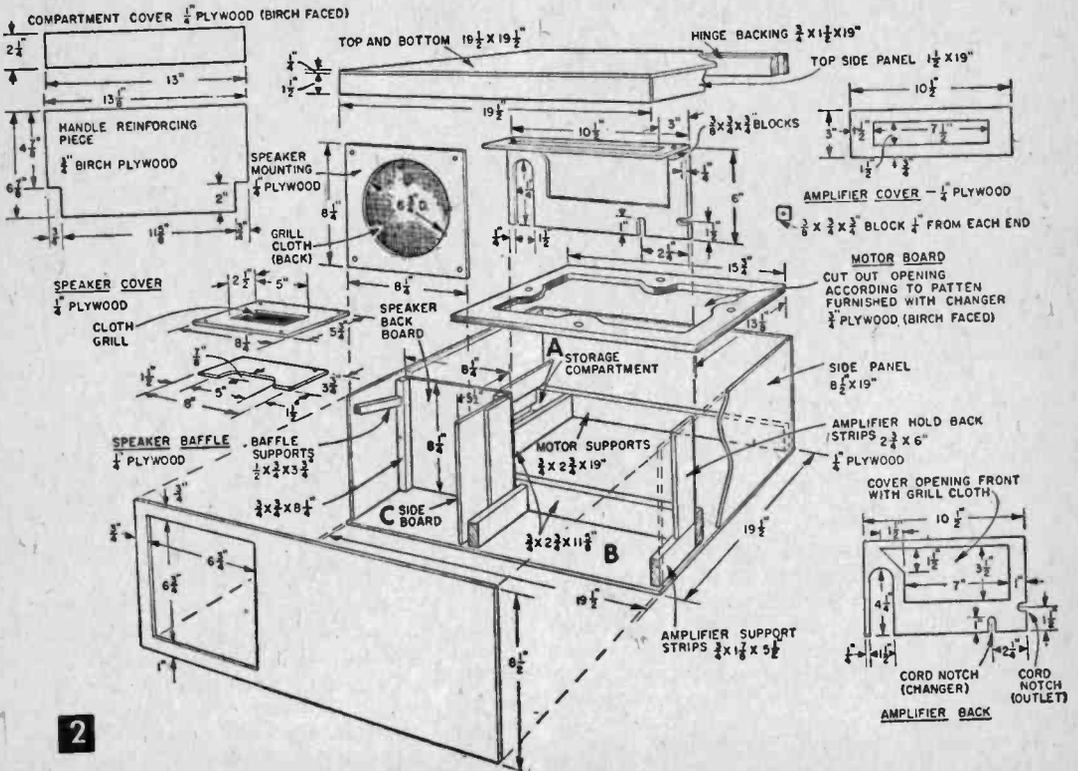
Be sure to cut the matching pieces for both the box walls and lids (Fig. 2) to length at the same time. This will give you an exact match, and a well fitting lid and box unit. The speaker open-



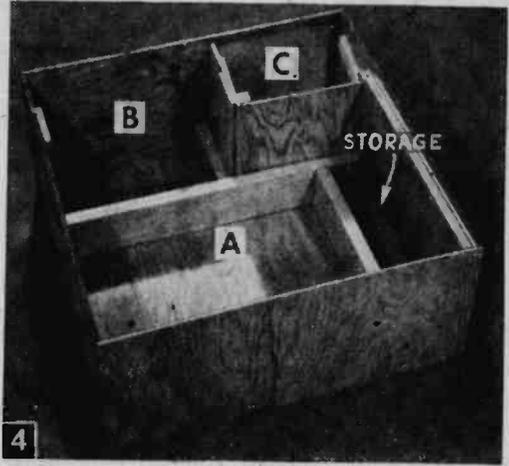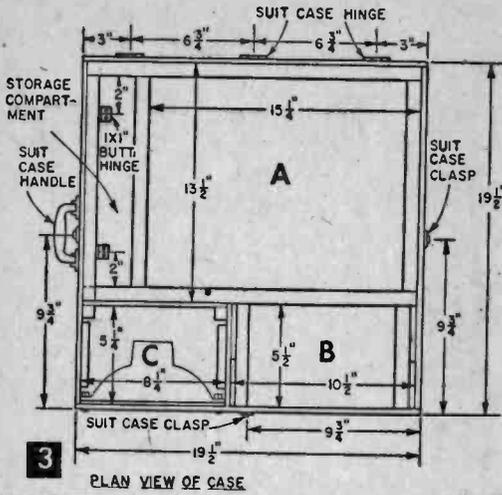

### MATERIALS LIST—PORTABLE HI-FI-RECORD PLAYER

No.	Size and Description	Use
<b>For Cabinet:</b>		
2 pcs	1/4 x 19 1/2 x 19 1/2" plywood	case top and bottom
2 pcs	1/4 x 8 1/2 x 19" plywood	case ends
2 pcs	1/4 x 8 1/2 x 19 1/2" plywood	case sides
2 pcs	1/4 x 1 1/2 x 19" plywood	lid ends
2 pcs	1/4 x 1 1/2 x 19 1/2" plywood	lid front and back
1 pc	1/4 x 3 x 10 1/2" plywood	amplifier top
2 pcs	3/4 x 1 7/8 x 5 1/2" solid stock	amplifier support
1 pc	3/4 x 1 1/2 x 19" solid stock	hinge backing
2 pcs	1/4 x 2 3/4 x 6" plywood	amplifier holdback
1 pc	1/4 x 6 x 10 1/2" plywood	amplifier cover
2 pcs	3/8 x 3/4 x 3/4" solid stock	amplifier blocks
2 pcs	3/4 x 2 3/4 x 19" solid stock	motor board support
1 pc	3/4 x 2 3/4 x 11 5/8" solid stock	motor board cross support
1 pc	3/4 x 1 3/8 x 15 3/4" birch-faced plywood	motor board
1 pc	1/4 x 2 1/4 x 13" plywood	compartment cover
1 pc	3/4 x 6 7/8 x 13 1/8" solid birch	handle reinforcement board
1 pc	1/4 x 5 3/4 x 8 1/4" plywood	speaker cover
1 pc	1/4 x 8 1/4 x 8 1/4" plywood	speaker mounting board
1 pc	1/4 x 3 1/4 x 8" plywood	speaker baffle
2 pcs	1/2 x 3/4 x 3 1/2" solid stock	baffle board support
1 pc	3/4 x 3/4 x 8 1/4" solid stock	back, side and top support
1 pc	1/4 x 5 1/2 x 8 1/4" plywood	speaker side board
1 pc	1/4 x 8 1/4 x 8 1/2" plywood	speaker side board
1 1/2 yds	54" wide plastic upholstery fabric with cloth back	(department or upholstery store)
3/8 yd	54" different color plastic upholstery with cloth back	(department or upholstery store)
	15 x 15" grille cloth (radio supply house)	
	24 x 24" fiber glass insulation (radio supply house)	
	1 suitcase carrying handle, 2 suitcase bolts with safety clasps (2 3/4 x 1 1/2"), 3 suitcase stop hinges, 1 surface suitcase lock (1 3/4 x 1 1/2"), 1 pair 3/4" long brass box hinges	
	No. 8 oval head wood screws, 1 3/4" long (nickel finish); No. 4 rh nickel wood screws, 3/4" long	
<b>For Record Player:</b>		
	Amplifier—Grommes, Model LJ2	
	Speaker—Jensen Extended Range, 8", P8-SX	
	Changer—Gerrard, Model RC 80	
	Cartridge—GE RPX 050 (3-speed); or GE RPX 061 (single play with diamond needle for microgroove; or GE RPX 040 (single play with sapphire needle for 78 rpm)	

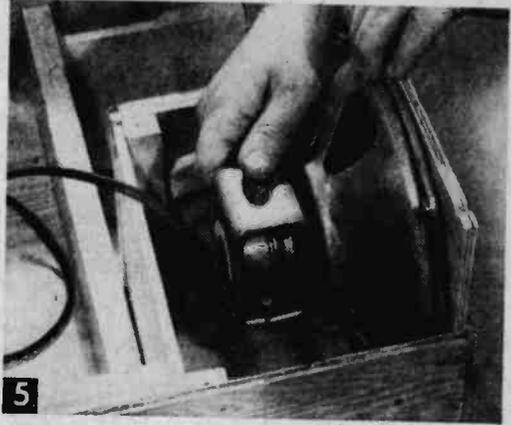

After mounting speaker on its board, test fit by slipping it into speaker compartment.

ing is cut in one of the 19 1/2-in. long box pieces (C in Fig. 3). After dressing these cut parts, check the lid and box fit, and then assemble the box and lid with brads and glue.

Next cut the motor-board support strips (A in Fig. 3) and the cross motor-board support strip (which is the inner wall of the record changer spindle compartment) of 3/4-in. pine stock. Use countersunk flathead wood screws to hold the three strips in place in the bottom of the box.

The speaker compartment pieces are 1/4-in. ply-

wood except for the two corner supports which are strips of 3/4-in. square pine stock, and the baffle board supports which are 1/2-in. stock (C in Fig. 3). Assemble the speaker compartment in the box with flathead wood screws.

Cut the amplifier support strips from 3/4-in. pine stock, and the amplifier hold-back strips of 1/4-in. plywood. Fasten these in place with flathead wood screws.


Cut the speaker mounting board of 1/4-in. plywood. Jigsaw out the circular speaker opening (Fig. 2) from 1/4-in. plywood and mount the speaker on its board with flathead stove bolts, passing the bolts through holes drilled through the speaker board, then through the mounting holes in the speaker frame. Countersink for the stove bolt heads so they will be flush with the front of the speaker mounting board.

Slip the speaker, mounted on its board, into the speaker compartment to be sure it fits (Fig. 5). Fit the speaker baffle board (Fig. 2) down over the speaker and fasten to the slant baffle board support strips with small flathead wood screws (Fig. 6). After fitting the speaker in place

to check the assembly, dis-assemble again, removing baffle board and speaker from the compartment.

Unscrew the nuts from the bolts holding speaker to speaker board and lift off the speaker, but leave stove bolts in place on speaker mounting board. Return speaker to its packing carton until you are ready for final assembly. Give front of speaker mounting board a coat of flat black paint.

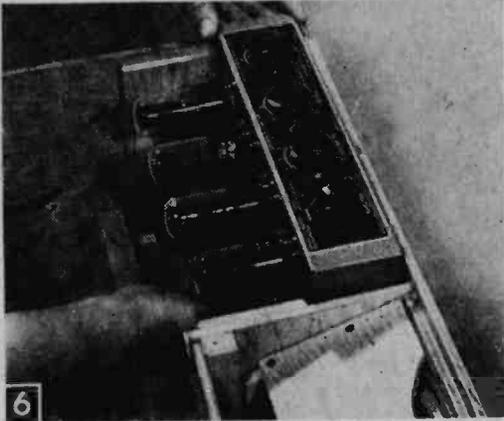Next, test fit the amplifier in place in its compartment (B in Fig. 3). Note that support strips on which amplifier rests, also hold amplifier up



6 Trying out fit of amplifier in its compartment. Baffle board in place over speaker.

flush with the top of the box, at the same time creating a compartment below the amplifier for the plugs and cords that connect amplifier to speaker and changer. Test fit both the amplifier back board and amplifier cover board in place. Then disassemble amplifier cover and back board, lift out amplifier and return it to its shipping carton.

The motor board (Fig. 2) is cut from  $\frac{3}{4}$ -in. birch stock. Test fit the board on its support strips. The cross support strip forming the inner wall of changer spindle compartment, extends about  $\frac{1}{4}$  in. beyond edge of motor board, and the compartment cover projects over this extension. Drill holes through motor board so it may be



8 Attaching fiber glass insulation to insides of speaker compartment with stapler-tacker. Insulation on sides extends only up to baffle board supports.


screwed to support strips at the four corners. Then remove motor board from box and jigsaw out an opening in its center to match the mounting diagram furnished with your record changer.

Cut the handle reinforcing board (Fig. 2) of  $\frac{3}{4}$ -in. birch stock and fasten to box side with wood screws screwed through from outside box. Also locate two screws to engage the board at the edge where it fits into the corner of the box.

Cut the changer spindle compartment cover of  $\frac{1}{4}$ -in. birch-faced plywood (Fig. 2). Also cut two  $2\frac{1}{4}$ -in. lengths of  $\frac{3}{4}$ -in. square stock and glue these to the motor board support strips under the cover. These blocks hold the compartment cover up flush with the motor board. Hinge this cover to handle support board with brass hinges.

For covering the box, buy plastic upholstery material with a fabric back. Cut a  $20\frac{1}{2}$ -in. square piece for the box bottom. Spread a good grade of liquid glue evenly on the bottom of the box. Lay the covering square on the bottom so that the material extends  $\frac{1}{2}$  in. beyond the bottom on all four sides. Then smooth and roll the upholstery material to the wood for a good bond.

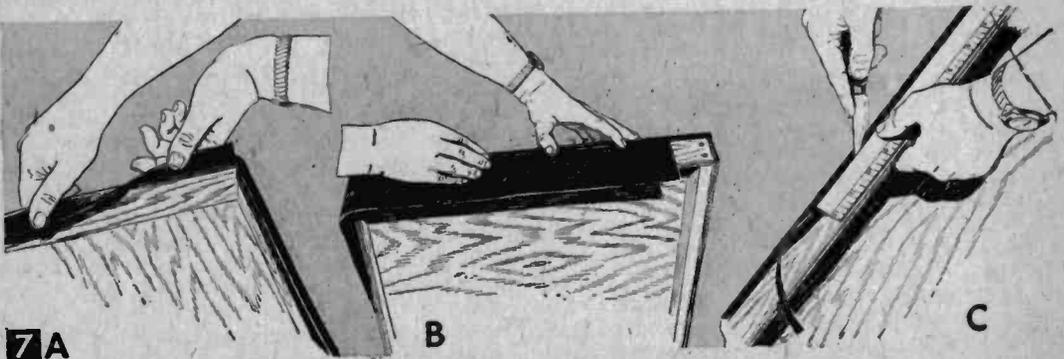Notch out the four corners as shown where they extend beyond the bottom, then glue material to four sides of box, making sure corners



7A Covering lid of record player with plastic insulating material.

come together. Before glue hardens completely, use a straight edge ruler and razor blade or sharp pointed knife to trim material to a straight edge around the four box sides.

Cut the material for covering the box sides in strips wide enough to extend  $\frac{3}{4}$  in. beyond top edge of box when it is fitted against cut edge of covering material glued to box sides. Spread glue on one side at a time and fit and roll the edge of the covering material snugly against the glued-on material. Repeat this procedure around all four sides of the box. Miter the corners and bring covering material over top edges and down against the inside of the box. On the section faced by the birch handle reinforcing board, however, glue covering only over the top plywood edge of the board.

When glue has set but is still tacky, again use straight edge razor to cut a clean edge on the covering material. Line inside of box with a contrasting plastic material, running the lining down to top of the motor board support strips. The birch handle reinforcing board, and the inside of the amplifier and speaker compartments are all left unlined. Cover and line the lid as you did the box (Fig. 7).

Also cover the speaker and amplifier cover boards with the material that is used for lining the case, carrying the covering material over both




9 Placing changer, mounted on the motor board, down onto motor board support strips.

the outside edges of the board and the inside edges of the cutout holes, and gluing it so it laps over onto the back about  $\frac{1}{4}$  in. You'll have to miter the corners, of course. Cut pieces of plastic grille cloth and fasten to the back of the boards to cover the openings, using either screen cloth staples or a regular tacker-stapler fitted with wire staples. Cut a piece of grille cloth the same size as the speaker mounting board. After making sure stove bolts used for mounting speaker are in place, lay the cloth over the opening and fasten to the front side of the board with screen staples or wire staples.

Glue a piece of the plastic used for the lining, to the amplifier back board. Cut out the oblong opening but leave plastic covering material over the upright opening. Tack a piece of grille cloth, with raw edges folded under, to the outside of the

opening. (The amplifier tubes, which give off considerable heat, would be too close to grille cloth fastened to the inside).

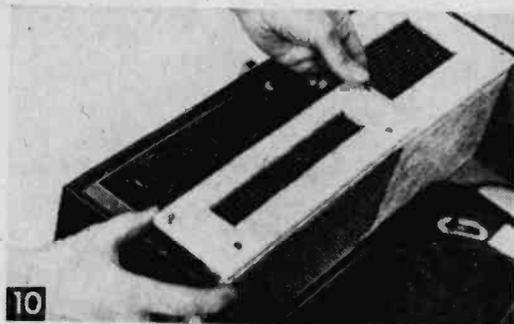Finish motor board, compartment cover and handle reinforcing board with several coats of shellac or other preferred finish. Allow to dry, then wax. Attach handle to outside of case (Fig. 2) using screws that drive nearly through box and handle reinforcing board. Fit lid in place and attach three safety clasp suitcase-type fasteners,




10 Fitting amplifier compartment back and cover in place. Below is the finished record player.

centering them on the front and two sides of the record player where the lid meets the base. Hinge the fourth side of the lid to the box using three evenly spaced stop hinges.

Fasten pieces of spun fiber glass acoustic insulation to the bottom, back and sides (below the baffle board supports) of the speaker compartment with a stapler-tacker (Fig. 8). Mount the speaker on the back of the speaker mounting board and draw up the stove bolt nuts until they are so tight the speaker will not vibrate during playing. Slip mounted speaker into its compartment and fasten speaker board to box frame with four nickel plated, roundhead machine screws passed through matching holes in the box and speaker mounting board. Draw nuts tight against back of speaker mounting board to eliminate vibration. Fasten baffle board and then speaker compartment cover in place.

Set changer, mounted on its motor board, into its compartment on the motor board support strips (Fig. 9). Tighten the screws at the four corners of the motor board to secure it to the support strips.

Make the wiring connections from changer to amplifier and amplifier to speaker. Cord passes through a hole cut in the wall between the two compartments. Instructions for making these connections come with the amplifier. Slip amplifier into its compartment with the wires in the open space beneath the amplifier. Slip amplifier compartment back board into place, then fit cover into position (Fig. 10) and screw down. The outlet plug cord is carried over the top of the box for playing and fitted around the changer when the box is closed for carrying. Spare equipment is stored in the spindle compartment.

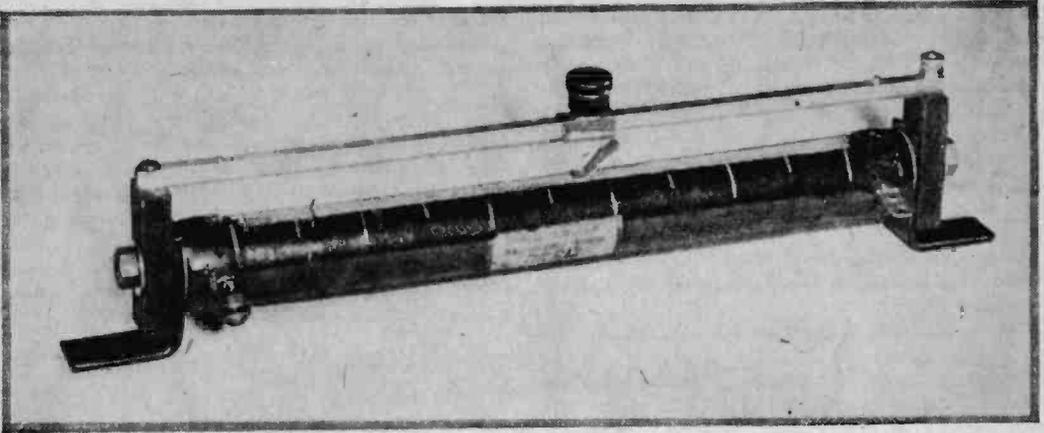


The finished slide wire resistor. This one has a value of 5000 ohms, 200 watts, .2 amperes.

# Try Making Slide Wire Resistors

These are just what you need when you are adjusting voltage or creating special loads during testing operations

By HAROLD P. STRAND

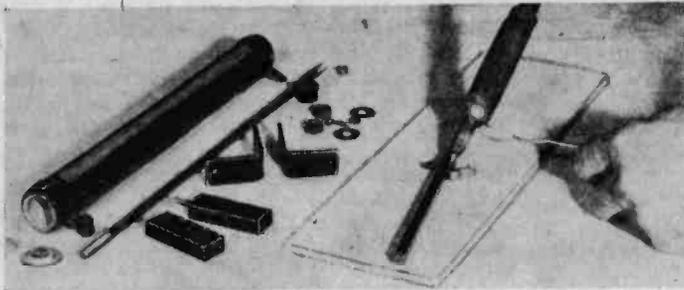


The complete parts of the slide wire resistor are shown on the bench ready for assembly. The sliding piece has been made and the phosphor bronze contact spring is shown here being soldered in place.

sort from a tubular adjustable resistor, or one that is equipped with an adjusting band. These can be purchased in most any radio supply store and many of them are included in surplus equipment. The advantage of a slide wire resistor is that the resistance can be adjustable in very gradual steps by simply sliding the movable unit along the wire to the point desired.

In selecting resistance tubes for this job, remember that two factors are involved—resistance and current carrying capacity. For example, a resistor may have a resistance of 500 ohms, but be able to carry but .2 amperes. If 1 ampere were the value of the current in the circuit, this resistor would quickly overheat and burn out. Therefore, we must provide an assortment of resistances with various cur-

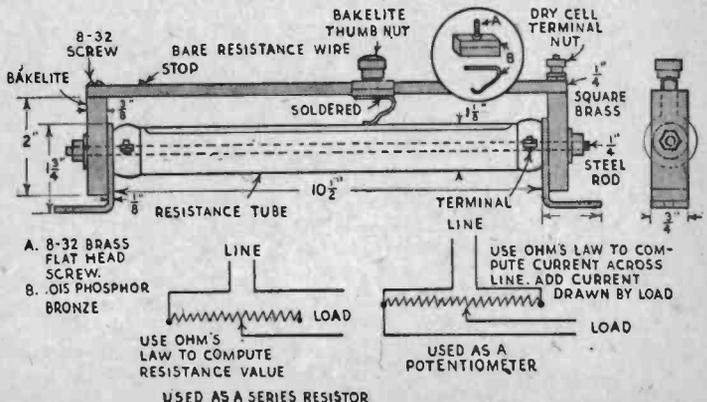**H**AVING an assortment of slide wire resistors on hand for electrical or radio testing is a great advantage. Technicians all use them for adjusting voltage and creating special loads on apparatus they are testing or developing. It is quite simple to make a good resistor of this



rent values, so as to be able to supply one within the limits of the demand. Generally speaking, those of high resistance and low current capacity will be comparatively small tubes, both in length and diameter, and the wire with which they are wound will be of small size. As the current value goes up, larger wire is required and in order to get the specified resistance on the tube, the latter will have to be both longer and somewhat greater in diameter.

In estimating the required amount of resistance for a given case, Ohm's Law is usually employed—

$$R = \frac{E}{I},$$

meaning that resistance equals the voltage divided by the current.

Suppose, for example, that the voltage is 110 and .5 ampere is the current desired in the circuit, how much resistance will be required? Dividing 110 by .5 = 220 ohms. Therefore, if a resistance of 220 ohms is connected in series on 110 volts, .5 amperes will flow in the circuit. This tells us that a slide wire resistor of at least 220 ohms (preferably a little more to allow for top adjustment) which is capable of carrying .5 amperes, will be required.

On the other hand suppose that we want to know how much current will flow in the circuit, if a resistance of some value is connected in.

$$I = \frac{E}{R}$$


Ohm's Law is again employed—

gives us the current value. On this basis, as an example, if a resistance of 150 ohms is used on 110 volts, the current will be .733. Again, when selecting the resistance to be used, make sure it will carry at least this current value, and preferably more so it will run cooler. These resistance tubes can be had in a large variety of values in both resistance and current. They are also often rated in watts, which shows the watt limit that can be dissipated without damage. Watt values are found by the formula  $I^2R$  (the current squared times the resistance). For example, in the previous problem with 110 volts and .5 amperes as known values, .5 times .5 equals .25 multiplied by 220 ohms equals 55 watts. Therefore, in this particular case, the resistor must be rated at 55 watts or better.

To get down to making these slide wires, note that the photos and drawings show all necessary steps. The resistor illustrated is rated at 5000 ohms and 0.2 amperes, 200 watts. It is a tube about 10½ inches long and 1½ inch in diameter. A ¼ inch steel rod is cut 12¼ inches long and threaded at both ends for ¼ inch-20. Two steel brackets are also made as indicated in the drawing and photos. The rod passes through drilled holes in these brackets and pieces of ⅝ inch bakelite, which also have holes drilled to receive the rod, are made and fitted as shown. With the aid of two ¼ inch nuts and washers, the assembly is tightly clamped together. If cup shaped or recessed washers are supplied with the tube, these are used in the open ends to center the

rod and make a better job of it.

The slide rod is made from a piece of ¼ inch square brass rod, drilled at the ends to receive an ⅝ screw at one end and a threaded stud, also ⅝, at the other end. These are used in tapped holes in the ends of the Bakelite pieces. Stops are made on the slide rod so the movable unit cannot go beyond the bared section of the wire. These are ⅝ screws fitted in tapped holes in the rod, with their heads cut off. An ⅝ nut and thumb nut from a dry cell are fitted to the threaded stud, so as to form a convenient terminal post for attachment of the lead wire.

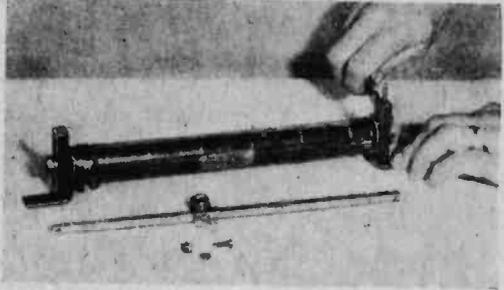

Assembly of the resistor is simple. A nut on each end of the tie rod clamps parts together. Final job is to place square rod in position and secure it with a screw and binding post nuts.

The sliding member is made by taking some thin phosphor bronze and bending it up in the form of a square tube around the rod as a guide. The seam is soldered as shown in one of the photos. A piece of the same material is also used as the wiping spring contact, which is also soldered in place to the square tube. The final job is to solder a flat head ⅝ brass screw to the top center of the tube. Screw an insulated thumb nut or binding post terminal on the screw. Tension on the wire should be positive at every point but should not have excessive pressure, which might damage the fine wires.


Only one end of the resistance will be used, unless the slide wire is to be used as a potentiometer, in which case both ends will be in use. It is a simple matter to either solder or fit suitable terminal posts through the holes for attachment of the leads.

These finished slide wire resistors can be made more stable on the bench, by attaching pieces of ¼ inch hard asbestos board under the brackets.

Dimensions given in the drawings and some details shown will have to be modified according to the size of the unit under construction. However, the method of converting them will be the same and if carefully done, the result will be well worth the trouble.
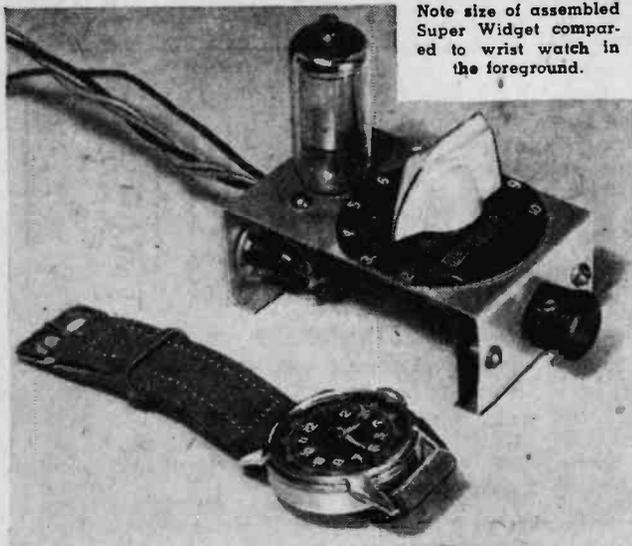
### Cut Power Interference

- Erect your radio aerial at right angles to telephone and power lines in order to eliminate interference or static.—I. M. FENN.



## SUPER WIDGET

Want to build a pep-packed pocket set? Here is a simple yet powerful circuit for a one-tube radio that's easy to build, easy to listen to, and easy on the pocketbook

By T. A. BLANCHARD

**F**OR THE radio experimenter who wants to try his hand at something simple yet exciting, the *Super Widget* is it! The *Super Widget* has been designed along straight-forward lines, but our pictorial wiring plan is arranged so that the builder may install the set in a cigarette case, plastic compact, or any other small, non-metallic case. The result is a truly powerful and selective pocket set.

Only six radio components are used. The circuit employs the super-regenerating system working around a tiny Impax coil. This coil is about the size of


a dime, and  $\frac{1}{8}$  in. thick. By means of a vernier adjustment knob, the set builds up a remarkable amount of sensitivity and power without any of the usual objections to super-regenerating circuits such as lack of sensitivity, continuous oscillation, whistles, howls, etc. The knob control on the Impax coil serves as both sensitivity and volume control and is free of critical adjustment and noise, as is often the case where potentiometers and condensers are used to control feedback.


To conserve space, a compression type capacitor is used as tuning control. The capacitor has a maximum capacity of about 200 mmf, and when used with the Impax coil, covers the entire broadcast band. As compression capacitors are ordinarily adjusted with a screwdriver, we attached a  $\frac{1}{4}$  in. bushing to the screw so that it could be fitted with a small Bakelite knob. Three complete revolutions of the knob cover the broadcast band. The components list is completed with a 20 megohm resistor and 75 mmf. Ceramicon capacitor in the grid circuit. A midjet electron tube, a type 1T4 pentode, is used in the compact hookup. The original model was assembled on a simple aluminum chassis  $1\frac{1}{4}$  in. wide,  $2\frac{3}{4}$  in. long and 1 in. high.

The *Super Widget* obtains power from a  $22\frac{1}{2}$  or 45 volt midjet B battery or an ultra-compact Mini-max 30 volt cell. An ordinary penlight cell provides  $1\frac{1}{2}$  volt for the tube filament. The antenna lead is soldered in to the circuit. We used a 3 ft. length of thin hook-up wire. Bringing this wire within close
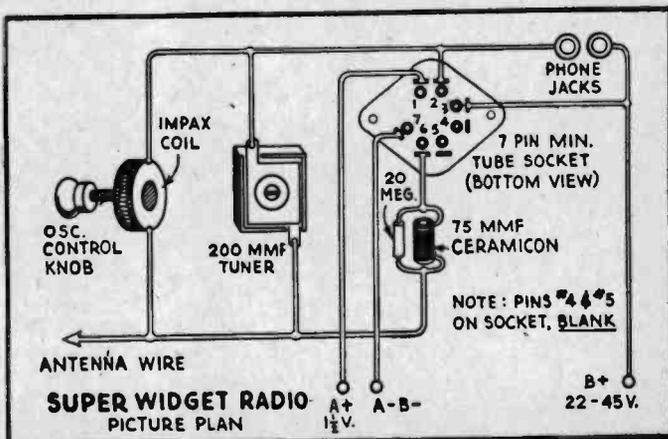
### MATERIALS LIST—SUPER WIDGET

- 1 200 mmf. compression type capacitor
- 1 75 mmf. Ceramicon fixed capacitor
- 1 20 megohm,  $\frac{1}{4}$  watt resistor
- 1 Impax BC band coil assembly
- 1 7-pin miniature tube socket
- 2 phone jacks
- 2 Bakelite knobs
- 1 Type 1T4 Pentode tube




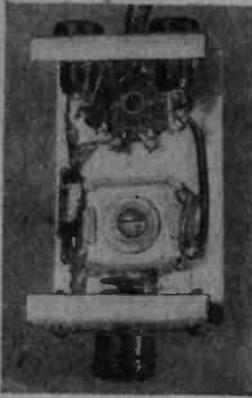

Note tuning capacitor (center) and above it, tube sockets and phone jacks.

range of a telephone or other metallic object gave ample pick-up. Greater signal strength may be obtained by connecting a ground wire to the A-B connection on the set.

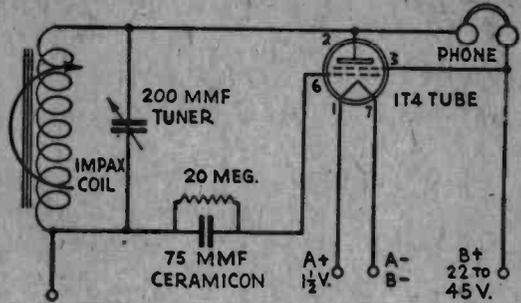This unique circuit offers numerous design possibilities. Earphone reception is bell-clear and plenty loud. We suggest that the headphones used with this set have a 2000 ohm impedance. With the proper out-




**SUPER WIDGET - SCHEMATIC PLAN**

put transformer a regular hearing-aid receiver works fine.


In many locations good loudspeaker volume may be expected. This is particularly true if you are located in the vicinity of high-powered radio stations.

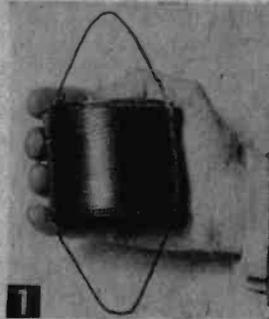**Portable Coil Antenna**

• Those amusing metal coils that "walk" down the steps make handy portable antennas for standard broadcast and/or short-wave receivers. Simply hang the coil from the ceiling to the floor, or stretch it across the room, and when you want to take it down it will snap back into a neat and compact unit.



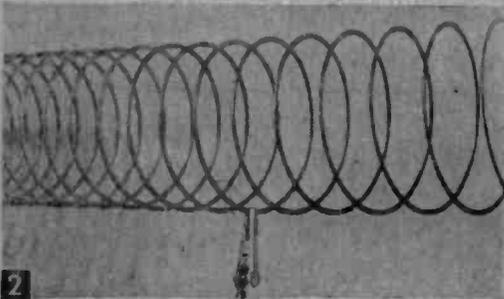*Slinky* (Fig. 1) consists of 70 ft of copper-plated metal band about 3/32 in. wide. The coil is about 3 in. wide and stands about 2 1/4 in. high.



Fasten a hanger on each end of the coil using short lengths of wire or cord twisted or tied to end loops, so you can hang the coil from hooks or nails.

An alligator clip and a length of wire connect the coil, hung from the ceiling, to your receiver's antenna post. These coils are made of copper-coated spring-steel, and one cost me 85¢ in a dime store.—ARTHUR TRAUFFER.

**Weather-Resistant Antenna Coating**

• Despite the use of non-rusting elements for outdoor TV antennas, they deteriorate rapidly under exposure to the weather, with such results as pitted contacts at the transmission-line insulator connections and cracked insulators which cause signal losses. Extend the life of your out-



door antenna with a weather-resistant coating obtained by applying a clear plastic spray such as Krylon Crystal Clear. After the antenna has been assembled but before it is mounted on the mast, spray reflector, crossarm mast-section, the twin-lead section which extends from the insulator to the first stand-off insulator, the stand-off insulator, bolts, nuts and other important terminals.

# The Care of Electric Soldering Irons



An assortment of irons; ratings range from 20 to 135 watts. All have universal shaped tips, or chisel points, except the gun-type (right center) which has a shorted turn, alloy-wire tip. Dual-rated for 100-135 watts, the gun-type iron is designed for instant-heat electronics work. The pencil iron (lower right) is for use in cramped quarters.

**M**OST home handymen have an investment in one or more soldering irons. Properly used and cared for, an iron will give long years of dependable, efficient service. Improperly used and cared for, it will give weak and imperfect soldered joints and will soon be valueless as a tool. In other words, it pays to take care of your soldering irons.

Often, a large iron can do a small job; a small iron can never do a large job. Figure 1 shows a variety of irons; Table A gives the uses to which the different sizes of irons are usually put. In addition to using the proper size iron on a job—an iron that will generate and transmit enough heat to insure a good joint—you should remember that it is the tip of the iron that transmits the heat and that, unless the tip is kept properly "tinned," an oxidized crust will form that will impede the flow of heat to the work.

To tin an iron, first see that the tip is smooth and free from pits. If necessary, use a file to recondition the four faces. Then apply solder to the tip (Fig. 2), just before it reaches maximum heat. Rosin-core solder is best for this purpose as it eliminates the necessity of using an external flux.

When using the iron, watch the tinning on the tip. If it becomes discolored, dip it into clean water and instantly withdraw it. This will not only expose the bright tin, but also restore the iron to a safe temperature if the discoloration is due to overheating. Tinning may also be cleaned by rubbing the iron on steel wool (Fig. 3); and overheating may be remedied by disconnecting the iron briefly when necessary.

When you're through using an iron, wipe it clean with an oily cloth. This will help prevent corrosion. Never use sal ammoniac (ammonium chloride) to clean a tip; it spreads rapidly and will corrode the rest of the iron. It may also be deposited on the work when doing electrical or electronic soldering and later cause trouble.

Don't abuse your iron by hammering or prying with it. Don't forge the tip; use a file, or grind it, to restore its shape. And don't kink its cord sharply, yank it, twist it, or drag it. A good

TABLE A SOLDERING IRON

Type	Watt Rating	Length	Weight	Use
Pencil	20-35	7-8 in.	3/4-8 oz.	Quick heat, for short intervals; Small wire soldering in crowded places
Conventional	40-75	9-12 in.	8 oz.-1 lb.	General light work (radio or jewelry soldering)
Conventional	85-100	10-13 in.	10 oz.-1 1/4 lbs.	Common type household and general purpose iron; also for appliance repairs
Conventional	150	11-13 in.	12 oz.-1 1/2 lbs.	Same as above, but for slightly heavier work
Conventional	200	12-14 in.	1-2 lbs.	Used in shops for medium heavy jobs and in homes for heavy tasks
Conventional	300	12-15 in.	2-3 lbs.	Factory production soldering and any very large surface soldering
Gun	100-135	10-12 in.	1 1/2-2 lbs.	Where quick heating is required
Gun	200	10-12 in.	2-2 1/2 lbs.	Where quick heating is required
Gun	200-250	10-12 in.	2-2 1/2 lbs.	Where quick heating is required, also permits soldering wires directly to large surface (such as radio chassis)

way to protect the cord of an iron is to wind a plastic spiral cover around the end nearest the iron's handle, the end most flexed. Such covers are available at hardware and variety stores.

If the heating element of your iron burns out, obtain a replacement unit from the manufacturer or at a hardware store and make the installation yourself. To remove the defective element from a conventional type iron, slip the handle back on the cord, after loosening it from the metal barrel, and remove the cord wires and the wire leads to the heating element from beneath the threaded screws in the fiber support. Remove the tip (by loosening the set screw) and drive out the small

drift pin in the end section of the barrel. The end section then pulls out, complete with heating element, porcelain insulator and lead-in wires attached (Fig. 4). Reverse the removal procedure to install the new element.

In taking care of the gun-type iron, its tip should also, of course, be kept well tinned. With such guns, overheating should be strictly avoided. Since this type of iron heats in about five seconds there is no need to leave it turned on when not immediately in use. With the dual heat gun type models, the higher ranges should be used as little as possible to prevent overheating of tip and transformer.—H. LEEPER.




## LEFT

On a new iron, or with an old iron where the tinning has burned off, tin to clear copper on all four iron faces with flux and solder. Rosin-core solder is used here.
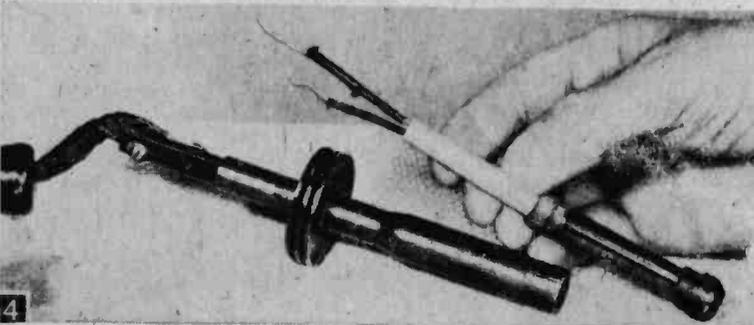
## RIGHT

A wad of steel wool forced inside solder spool is useful for tip cleaning while working.



## BOTTOM

Conventional iron disassembled for installation of new heating element. With irons in which the tips are held in place with a set screw, regular loosening of the screw and removal of tip for cleaning of the shank will prevent sticking and insure good heat conduction from element to tip.




# Twin Speakers Improve Fidelity

**I**F YOU have twin 6 or 8 in. P.M. type speakers, it's an easy job to connect them in series at their voice coils, and their combined performance will sound very much like one expensive speaker of twice the diameter. The two-speaker combination will, in fact, reproduce any audio signal with less distortion. Costwise, the two small 6 in. P.M. speakers cost about the same as one large 12 in. speaker.

To connect the small speakers in series, first mount them on a single baffle of suitable size (preferably of  $\frac{1}{2}$  in. insulating board).

The important thing to consider when connecting the voice coils is their correct polarity with respect to the operation of the cones. They must work in phase, that is, both cones must be pulled in and pushed out together, on each impulse of the signal, or vibrate together, rather than have one pull in and the other push out. To do this, use a flashlight cell and 2 clip leads to test the operation of each cone (Fig. 1). With the positive, (top of cell) connected to a certain voice coil terminal, the cone will be pulled in. If you reverse the battery polarity, the cone will be pushed out. Mark the terminal used when the cone is pulled in with positive polarity on that terminal. Do the same thing to the other speaker. It is now a simple job to connect the two voice coils in series (Figs. 2 and 3), connecting a positive to a negative. Solder on long leads for connection to the output transformer! Then double-check by attaching the battery to the long leads, and make sure that both cones pull in and push out together, with a reversal of the battery leads. The two speakers will now operate as a single unit, each taking half the power output, which doubles the capacity of a single speaker of the same size.

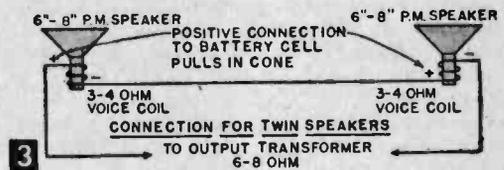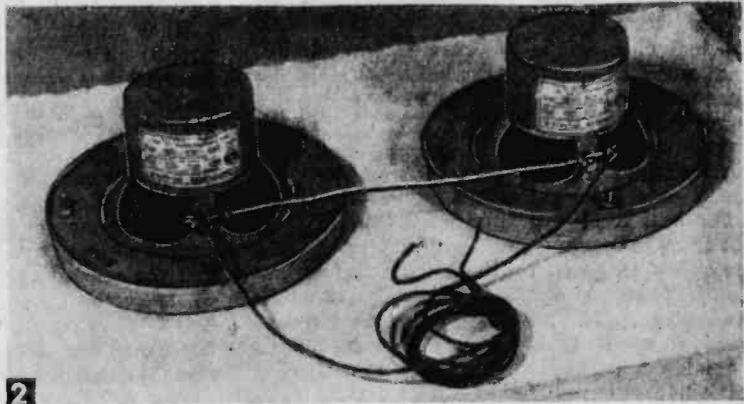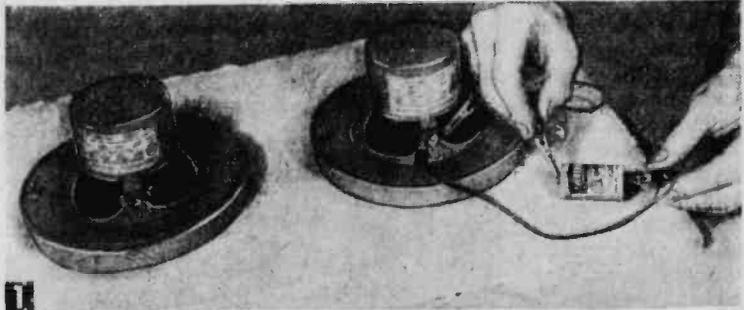For good bass reception, speakers should have a rather flexible cone mounting, since bass is at the lower frequencies where the maximum cone movement is evident. Many speakers will be found with very stiff working cones, easily determined by gently pushing in at the center with a finger. Such speakers work all right at the higher frequencies, but may lack good bass re-




sponse. In the past, speakers were made with a flexible leather mounting ring at the edges of the cone to improve the bass. The two shown in Figs. 1 and 2 have bellows-like construction at the edge, rather than the usual direct mounting to the frame, to provide a more flexible operation of the cones.

For good fidelity choose a good quality output transformer of generous size, since a cheap, small transformer will often fail to cover the wide frequency band of the signals delivered to it, if the full range of the musical scale is desired. The transformer must also match the rated load resistance of the amplifier output tube or tubes in the circuit, to the voice coil impedance. For example, a 6V6 with 250 volts on the plate requires 5000 ohms load resistance. Using the twin speakers, each with a 3-4 ohm voice coil, this becomes 6-8 ohms in series. Thus, you must match 5000 ohms to 6-8 ohms on the secondary of the transformer.—HAROLD P. STRAND.
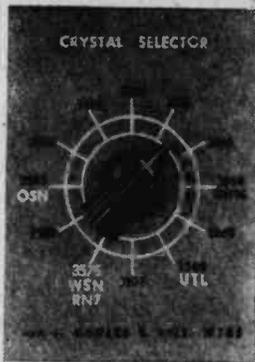
# How to Apply Small Decals

IT HAS now become common practice to put the professional touch on experimenter-made amplifiers, record players, other hi-fi equipment, amateur radio apparatus, etc., by using decalcomania transfer labels. Tweezers are recommended by most manufacturers for handling the individual words and letters, but you'll have much more success, using a tiny paint brush of the variety found in children's water color boxes—the smaller, the better.



Both black and white decals were used here, the most frequently used frequencies on this selector appearing in white.

For best results in applying decals, first lay out all of your supplies and materials so that you are ready to go to work without interruption. You will need, in addition to the book or sheets of decals themselves, a small pair of scissors with which to cut out the various words and letters; a small shallow dish or pan; (the cover from a glass jar works well) a small paint brush; and a soft, lint-free cloth.

Locate the word or letter you are going to use from the sheet, then carefully clip it out with the scissors, taking care to stay very close to the lettering so that a small spot of decal from the next letter does not mar the finished work. Drop this word or letter in the shallow water container and let it float while you look up and cut out the next word or letter. About 30 seconds in the water is enough for the average manufacturer's decals, although a full minute in water will do no harm. Sometimes it will be found that the decal will separate from the paper in the water and float free. When this happens, lift the decal itself from the water, using the point of the art brush and picking it up *only* at one end. (Picking it up in the middle will result in its curling around itself.) If the decal has not separated from the paper backing (good, dry decals will not), then pick up the word or letter—paper backing and all—with the tip of the brush and lay it in approximate position on the surface to which it is to be applied. Drop it about half an inch above or below, or a little more than the equivalent of its own length to one side, not over the final position it will occupy. This, too, is somewhat contrary to manufacturer's suggestions, but makes for far easier handling. Then (again in disagreement with printed instructions) do *not* attempt to pull the paper out from beneath the decal. Instead, take the pointed handle of the brush and gently "tease"

the decal from the paper—after first providing a moistened path for it to follow to its final

position by means of the brush and a little water. Use the pointed handle of the brush to push the decal into its proper position, re-wetting it slightly if it moves with difficulty. Don't attempt to float it in with an excess of water, particularly when it is to be located adjacent to other recently placed decals.

When you have positioned the word or letter in its final position, carefully pat it lightly with a lint-free cloth and, after absorbing the excess water, press it firmly into the surface with the cloth. Then leave it alone and proceed with the next word or letter!

When placing the larger dial scales and similar circular patterns, note that most of the better decal makers provide a "plus" sign in the exact center of the circle. In cutting out this decal do *not* cut out the inside of the circular area, but preserve the plus mark in its printed position. Before soaking the decal in water, place it in proper position and, using a prick punch or similar tool, puncture the exact intersection of the horizontal and vertical lines of the plus sign so that the mark is transferred to the surface of whatever the decal is to appear on. This will enable exact centering of the circular design when applied. (The plus mark is usually concealed behind a knob or dial anyway.)

Once you have completed lettering your panel or cabinet or other piece of gear, set it aside for a full 24 hours. Meanwhile, provide yourself with a small can of a high-grade lacquer. I have experimented with dozens of different brand names of various "clear" lacquers with varying degrees of success. For best all-round results, use "SYNALAC" clear white lacquer (made by W. P. Fuller Co.).

The first coat will dry hard within 20 minutes and then a second light coat should be applied. If the decals will be subject to rubbing fingers or other hard usage, a third, and thicker coat will also be needed and sometimes as many as five coats in all.—HOWARD S. PYLE.

## Answers to Electronics Numbers Quiz On Page 58

- 1) c—CK705
- 2) b—1X2
- 3) c—4:3
- 4) b— $3\frac{3}{4}$ " and  $7\frac{1}{2}$ "
- 5) a (and c)—60 c.p.s.  
(and .06 kilocycles)
- 6) TV channels VHF (a) and UHF (b)
- 7) a—40 (40 parts tin to 60 parts lead)
- 8) b—60
- 9) c—746
- 10) Record player speeds
- 11) c—6 Megacycles
- 12) b—6 Megacycles



# WHITE'S RADIO LOG

An up-to-date broadcasting directory  
AM, FM, TV and Short-Wave Stations

Vol. 35

No. 1

Every effort has been made to ensure accuracy of the information listed in this publication, but absolute accuracy is not guaranteed and of course, only information available up to press-time could be included. Copyright 1958 by Science and Mechanics Publishing Co., 450 East Ohio St., Chicago 11, Ill.

## QUICK REFERENCE INDEX

<b>U.S. AM Broadcasting Stations</b> Listed Alphabetically by Call Letters.....162	<b>Canadian Short-Wave Stations</b> Listed by Frequency.....186
<b>Canadian AM Broadcasting Stations</b> Listed Alphabetically by Call Letters.....168	<b>U.S. FM Broadcasting Stations</b> Listed Alphabetically by Location.....186
<b>U.S. and Canadian AM Stations</b> Grouped According to Frequency.....169	<b>Canadian FM Broadcasting Stations</b> Listed Alphabetically by Location.....188
<b>U.S. and Canadian AM Stations</b> Listed Alphabetically by Location.....177	<b>U.S. Television Stations</b> Listed Alphabetically by Location.....188
<b>World-Wide Short-Wave Stations</b> Listed by Frequency.....184	<b>Canadian Television Stations</b> Listed Alphabetically by Location.....190

## History of White's Radio Log

White's Radio Log was founded in Providence, R. I., by Charles DeWitt White as an extension of his earlier publishing activities which, in turn, were a continuation of the business established by his father: the publication of city directories, street guides and municipal tax guides.

In the early days of broadcasting, the compilation of a list of operating stations and their frequencies was no simple task. Prior to the Dill-White Radio Act of 1927, if a feed merchant, auto dealer, barber or undertaker wanted to advertise his wares or services, he had only to select a frequency and go on the air. A great many experimenters and business men did just that.

Nevertheless, Mr. White's directory publishing experience had convinced him that he could successfully assemble a radio log, and in 1924 he justified this conviction with *The Rhode Island Radio Call Book*, following this shortly after with *White's Triple List of Radio Broadcasting Stations*.

In 1927 the two publications were merged, nation-wide distribution was established and in ensuing years related publications, such as *Sponsored Radio Programs*, *Radio Announcer's Guide*, *Short-Wave Schedule Guide* and a special Canadian edition of the Log (which had had its title shortened to the one it bears today), were also issued.

The Log itself reached a combined circulation of well over 1,000,000 copies at one time, in 1929-31 was distributed as the *Enna Jettick Radio Log* (to promote the sale of shoes), in 1938-39 was distributed as the *General Electric Radio Log* (to promote General Electric's "sensational 1939 receivers with push-button tuning").

The Fall-Winter number of the 1927 Log listed 701 U.S. Stations. Most powerful were WEAJ (now WRCA), N.Y., with 50,000 watts, KDKA, Pittsburgh, WGY, Schenectady,

and WJZ (now WABC), N. Y., each with 30,000 watts; WGN-WLIB, Chicago, with 15,000 watts; and Boston's WBZ, also with 15,000. Five stations listed (one a Junior High School in Norfolk, Va.) operated on a mighty 5 watts, more than 100 stations had outputs of less than 100 watts.

The current Log cross-indexes over 3000 U.S. standard-broadcast (AM) stations, separately lists U.S. frequency-modulation (FM) and television stations, has a complete compilation of Canadian broadcasters and, in addition, has a comprehensive world-wide roster of short-wave stations.

With the success of his Log, Charles DeWitt White (a direct descendant of Peregrine White, the first child born on the Mayflower's historic crossing and bearer of the name of another illustrious ancestor, DeWitt Clinton) disposed of his city directory and street guide interests and transferred his editorial operations to Bronxville, N. Y., a suburb of New York City, where he could remain in close touch with the broadcasting industry. On April 6, 1957, having only recently completed revising and updating the 34th consecutive year of his Log, Mr. White died in his sleep. He was 76 years old.

Charles DeWitt White's daughter and heir, Mrs. W. R. Washburn, has sold all rights in and to the Log to Science and Mechanics Publishing Co., and entrusted us with continuing her father's work. This we are proud to do, beginning with the present edition, Vol. 35, No. 1, of *White's Radio Log*.

*W.D. Engeman*  
Publisher

Science and Mechanics

# United States

Standard Broadcast (AM) Broadcasting Stations Listed Alphabetically by Call Letters  
C.L., call letters; Kc., frequency in kilocycles (for watt power of station, see list arranged by frequency, p. 169)

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
DYBU	Cebu, P.I.	1260	KBNZ	Lajunta, Colo.	1400	KDAN	Eureka, Calif.	790	KFVJ	Modesto, Calif.	1360
DZPR	Manila, P.I.	800	KBDA	Kennett, Mo.	830	KDAB	Lubbock, Tex.	1580	KFIZ	Fond du Lac, Wis.	1450
DRRH	Manila, P.I.	710	KBDE	Oskalesoa, Iowa	740	KDAY	Santa Monica, Calif.	1580	KFJB	Marshalltown, Iowa	1230
KAAA	Kinsman, Ariz.	1210	KBDF	Madison, Ohio	950	KDBE	Santa Barbara, Calif.	1490	KFJI	Klamath Falls, Oreg.	1150
KABC	Los Angeles, Calif.	790	KBDO	Malvern, Ark.	1360	KDBF	Mansfield, La.	1360	KFJM	Grand Forks, N.Dak.	1440
KABI	Ketchikan, Alaska	580	KBDM	Boulder, Colo.	1490	KDBS	Alexandria, La.	1410	KFJZ	Ft. Worth, Tex.	1270
KABR	Aberdeen, S. Dak.	1220	KBDM	Mandan, N.Dak.	1270	KDDA	Dumas, Tex.	800	KFKU	Greeley, Colo.	1310
KACT	Andrews, Tex.	1360	KBDM	Omaha, Nebr.	1490	KDEC	Decorah, Iowa	1240	KFLD	Floydada, Tex.	900
KADA	Ada, Okla.	1230	KBOP	Pleasanton, Tex.	1380	KDEF	Albuquerque, N.Mex.	1150	KFLV	Klamath Falls, Oreg.	1450
KAFB	Colo. Sprngs., Colo.	1480	KBOW	Butte, Mont.	1600	KDEM	Dillon, Mont.	800	KFLY	Corvallis, Oreg.	1240
KAFP	Pataluma, Calif.	1490	KBOW	Medford, Oreg.	730	KDES	Palm Sprngs., Calif.	920	KFMA	Davenport, Iowa	1580
KAFY	Bakersfield, Calif.	550	KBPS	Portland, Oreg.	1430	KDET	Dexter, Mo.	930	KFMB	San Diego, Calif.	540
KAGH	Crossett, Ark.	1340	KBPS	Portland, Oreg.	1430	KDHL	Faribault, Minn.	1590	KFMI	Tulsa, Okla.	1050
KAGT	Anacortes, Wash.	1340	KBRK	Mt. Vernon, Wash.	1430	KDIA	Auburn, Calif.	1490	KFMO	Flower, Mo.	1240
KAGR	Yuba City, Calif.	1450	KBRK	Brookings, S.Dak.	1430	KDIO	Ortonville, Minn.	1350	KFNF	Shenandoah, Iowa	920
KAHU	Waipahu, Hawaii	920	KBRL	McCook, Nebr.	1300	KDIX	Dickinson, N.Dak.	1230	KFNV	Ferriday, La.	1000
KAIM	Kaimuki, Hawaii	870	KBRB	Bremerton, Wash.	1490	KDJI	Holbrook, Ariz.	1460	KFNR	Fargo, N.Dak.	900
KAKC	Tulsa, Okla.	970	KBRB	Springdale, Ark.	1340	KDJK	Pittsburgh, Pa.	1020	KFNR	Lincoln, Nebr.	1240
KAKE	Wichita, Kan.	1240	KBRZ	Freeport, Texas	1460	KDKD	Gilnton, Mo.	1280	KFOX	Long Beach, Calif.	1280
KALB	Alexandria, La.	1410	KBSF	Springhill, La.	1480	KDKL	DeRider, La.	1010	KFVJ	Ft. Smith, Ark.	1250
KALE	Richland, Wash.	960	KBST	Big Spring, Tex.	1340	KDKL	Del Rio, Tex.	1230	KFVW	Anchorage, Alaska	730
KALG	Alamogordo, N.Mex.	1230	KBTA	Batesville, Ark.	1340	KDLM	Detroit Lakes, Minn.	1340	KFRB	Fairbanks, Alaska	900
KALI	Pasadena, Calif.	1430	KBTK	Missoula, Mont.	1340	KDLR	Devils Lake, N.Dak.	1240	KFRS	San Francisco, Calif.	610
KALL	Salt Lake City, Utah	910	KBTM	Jonesboro, Ark.	1230	KDMA	Montevideo, Minn.	1450	KFRD	Rosenberg, Tex.	980
KALM	Thayer, Mo.	1290	KBTN	Neosho, Mo.	1420	KDME	Carthage, Mo.	1490	KFRE	Fresno, Calif.	940
KALT	Atlanta, Tex.	900	KBTO	El Dorado, Kans.	1360	KDMS	El Dorado, Ark.	1290	KFRM	Kansas City, Mo.	1570
KALV	Alva, Okla.	1430	KBUC	Corona, Calif.	1370	KDNT	Denton, Tex.	1440	KFRN	Longview, Tex.	1300
KAMD	Camden, Ark.	1430	KBUN	Big Spring, Utah	800	KDOK	Tyler, Colo.	1330	KFRU	Columbia, Mo.	1400
KAMO	Rogers, Ark.	1390	KBUN	Bemidji, Minn.	1450	KDON	Sallinas, Calif.	1460	KFSB	Ft. Smith, Ark.	950
KAMP	El Centro, Calif.	1430	KBUR	Burlington, Iowa	1490	KDQW	DaQueen, Ark.	1390	KFSJ	Jobin, Minn.	1310
KAMQ	Amarillo, Tex.	1010	KBUS	Mexia, Tex.	1590	KDRD	Sedalia, Mo.	1490	KFSC	Denver, Colo.	1220
KANA	Anaconda, Mont.	1230	KBVM	Lancaster, Calif.	1380	KDRS	Paragould, Ark.	1490	KFSD	San Diego, Calif.	600
KANC	Corsicana, Tex.	1340	KBWD	Brownwood, Tex.	1380	KDSJ	Deadwood, S.Dak.	980	KFSG	Los Angeles, Calif.	1150
KANE	New Iberia, La.	1240	KBWE	Okla. City, Okla.	890	KDSE	Denison, Iowa	1580	KFST	Ft. Stockton, Tex.	860
KANI	Oahu, Hawaii	1150	KBWY	Anchorage, Alaska	1270	KDSE	Denison, Iowa	1580	KFTM	Ft. Morgan, Colo.	1400
KANN	Sinton, Tex.	1580	KBYZ	Lawton, Okla.	1490	KDTH	Delta, Colo.	1400	KFTV	Fort, Tex.	1250
KANO	Anoka, Minn.	1470	KCCF	Redlands, Calif.	1410	KDTA	Delta, Colo.	1400	KFUN	Las Vegas, N.Mex.	1230
KANS	Wichita, Kan.	1480	KCAL	Helena, Mont.	1340	KDUB	Luibock, Tex.	1340	KFUD	St. Louis, Mo.	850
KANV	Shreveport, La.	1050	KCBG	Des Moines, Iowa	1390	KDUZ	Hutchinson, Minn.	1260	KFVS	Cape Girardeau, Mo.	960
KADK	Lake Charles, La.	1340	KCBD	Lubbock, Tex.	1590	KDWT	Stamford, Tex.	1400	KFWB	Los Angeles, Calif.	980
KAPA	Raymond, Wash.	1340	KCBS	San Diego, Calif.	1170	KDYL	Salt Lake City, Utah	1320	KFXD	Nampa, Idaho	580
KAPB	Marksville, La.	1370	KCBQ	San Fran., Calif.	740	KDZA	Pueblo, Colo.	1050	KFXM	San Bernardino, Calif.	590
KAPK	Minden, La.	1240	KCCD	Lawton, Okla.	1050	KEAN	Brownwood, Tex.	1230	KFYN	Bonham, Tex.	1420
KARE	Atchison, Kan.	1470	KCCF	Corpus Christi, Tex.	1130	KEBE	Jacksonville, Tex.	1400	KFYB	Lubbock, Tex.	790
KARK	Little Rock, Ark.	920	KCCU	Cuero, Tex.	1600	KECC	Pittsburg, Calif.	990	KGAB	Bismark, N.Dak.	550
KARM	Fresno, Calif.	1430	KCHA	Charles City, Iowa	580	KECK	Odessa, Tex.	920	KGAF	Spokane, Wash.	1510
KART	Jerome, Idaho	1400	KCHE	Cherokee, Iowa	1440	KEED	Springfield, Oreg.	1050	KGAK	Gainesville, Tex.	580
KARY	Prosser, Wash.	1310	KCHI	Chillicothe, Mo.	1010	KEEN	San Jose, Calif.	1370	KGAL	Galveston, N.Mex.	1330
KASA	Elk City, Okla.	1430	KCHJ	Delano, Calif.	1010	KEER	Twin Falls, Idaho	1450	KGAL	Lebanon, Oreg.	920
KASH	Eugene, Ore.	1600	KCHR	Charleston, Mo.	1350	KELA	Centralia, Wash.	1470	KGAY	Salem, Oreg.	1430
KASI	Ames, Iowa	1430	KCHS	Truth or Consequences, N.Mex.	1400	KELD	El Dorado, Ark.	1400	KGB	San Diego, Calif.	1360
KASL	Newcastle, Wyo.	1240	KCHV	Coachella, Calif.	970	KELC	Sioux Falls, S.Dak.	1320	KGBH	Hanford, Tex.	1260
KASM	Albany, Minn.	1150	KCIO	Caldwell, Idaho	1490	KELK	Elko, Nev.	1240	KGBX	Springfield, Mo.	1380
KAST	Astoria, Ore.	1370	KCJH	Shreveport, La.	980	KELP	El Paso, Tex.	920	KGCX	Sidney, Mont.	1480
KATE	Albert Lea, Minn.	1450	KCIL	Houma, La.	1490	KELT	Electra, Tex.	1050	KGDE	Perry Falls, Minn.	1250
KATI	Casper, Wyo.	1400	KCJM	Carroll, Iowa	1380	KENA	Mena, Ark.	1450	KGDN	Edmonds, Wash.	630
KATL	Miles City, Mont.	1340	KCJN	Minot, N.Dak.	910	KENF	Kennett, Wash.	1490	KGEB	Bakersfield, Calif.	1290
KATO	Reno, Nev.	1340	KCJN	Kansas City, Kans.	1380	KENI	Anchorage, Alaska	1340	KGEE	Stirling, Colo.	1230
KATR	Corpus Christi, Tex.	1030	KCKY	Coolidge, Ariz.	1150	KENL	Arcata, Calif.	1340	KGEM	Borlase, Idaho	1140
KATY	San Luis Obispo, Cal.	1340	KCLA	Pine Bluff, Ark.	1400	KENM	Portales, N.Mex.	1450	KGEN	Turkey, Ariz.	1370
KATZ	St. Louis, Mo.	1600	KCLE	Clbourne, Tex.	1120	KENS	Las Vegas, Nev.	1460	KGER	Long Beach, Calif.	1390
KAUS	Austin, Minn.	1480	KCLF	Clifton, Ariz.	1400	KENT	San Antonio, Tex.	680	KGEZ	Kalispell, Mont.	600
KAVE	Carlsbad, N.Mex.	1240	KCLN	Clenton, Iowa	1390	KENT	Shreveport, La.	1550	KGFF	Shawnee, Okla.	1450
KAVL	Lancaster, Calif.	1340	KCLN	Leavenworth, Kans.	1410	KEPR	Fort Dodge, Iowa	540	KGFJ	Los Angeles, Calif.	1230
KAVR	Apple Valley, Calif.	1370	KCLS	Clarksburg, Ariz.	600	KERB	Kermitt, Tex.	810	KGFL	Roswell, N.Mex.	1400
KAWL	York, Neb.	1450	KCLV	Clavis, N.Mex.	1240	KERC	Eastland, Tex.	1590	KGFV	Ferris, S.Dak.	650
KAWT	Douglas, Ariz.	1490	KCLW	Hamilton, Tex.	900	KERN	Eugene, Oreg.	1280	KGGF	Coffeyville, Kans.	650
KAYE	Puyallup, Wash.	1450	KVLX	Colfax, Wash.	1450	KERN	Bakersfield, Calif.	1410	KGHF	Albuquerque, N.Mex.	610
KAYL	Storm Lake, Iowa	1100	KCMC	Texarkana, Tex.	1230	KEUV	Kerrville, Tex.	1230	KGHI	Pueblo, Colo.	1350
KAYD	Seattle, Wash.	1150	KCMJ	Palm Sprngs., Calif.	1340	KEVE	Minneapolis, Minn.	1440	KGHL	Little Rock, Ark.	1250
KAYS	Hays, Kans.	1400	KCMK	Kansas City, Mo.	810	KEVA	Eureka, La.	1490	KGHL	Billings, Mont.	790
KAYT	Rupert, Idaho	970	KCNA	Tucson, Ariz.	580	KEVL	White Castle, La.	1590	KGIB	Brookfield, Mo.	1470
KBAB	El Cajon, Calif.	910	KCNC	Ft. Worth, Tex.	1280	KEVT	Tucson, Ariz.	690	KGIB	Bremerton, Wash.	1540
KBAL	San Saba, Tex.	1410	KCNY	San Marcos, Tex.	1470	KEVW	Portland, Oreg.	1190	KGIC	Sharon, Calif.	1260
KBAM	Longview, Wash.	1220	KCOB	Newton, Iowa	1280	KEXO	Grand Junc., Colo.	1230	KGID	Alamosa, Colo.	1450
KBAR	Benton, Ark.	690	KCOG	Centerville, Iowa	1400	KEXX	San Antonio, Tex.	1250	KGKJ	Tyler, Tex.	1490
KBBS	Buffalo, Wyo.	1450	KCOH	Houston, Tex.	1430	KEYE	Ferris, Tex.	1400	KGKL	San Angelo, Tex.	960
KBCH	Oeanlake, Oreg.	1400	KCOI	Tulare, Calif.	1270	KEYJ	Jonestown, N.Dak.	1440	KGKO	Dallas, Tex.	1480
KBEC	Waxahachie, Tex.	1390	KCOL	Colville, Colo.	1410	KEYS	Corpus Christi, Tex.	1400	KGKM	Miami, Okla.	910
KBEE	Waxahachie, Tex.	1390	KCOM	Sioux City, Iowa	620	KEYZ	Pocatello, Idaho	1240	KGLN	Glenwood Sprngs., Colo.	980
KBEL	Idabel, Okla.	1240	KCON	Conway, Ark.	1230	KEYZ	Williston, N.Dak.	1450	KGLM	Mason City, Iowa	1300
KBEN	Carrizo Sprngs., Tex.	1450	KCOR	San Antonio, Tex.	1390	KFAB	Omaha, Nebr.	1110	KGLN	Grand Rapids, Oreg.	1480
KBHM	Branson, Mo.	1220	KCOA	Alliance, Nebr.	1400	KFAL	Los Angeles, Calif.	1330	KGMB	Honolulu, Hawaii	590
KBHS	Hot Springs, Ark.	590	KCOY	Santa Maria, Calif.	1400	KFAD	Fairfield, Iowa	1570	KGMC	Englewood, Colo.	1150
KBIA	Columbia, Mo.	1580	KCRA	Sacramento, Calif.	1320	KFAL	Fulton, Mo.	980	KGMD	Cape Girardeau, Mo.	1220
KBIF	Centerville, Calif.	900	KCRB	Chesnut, Kans.	1380	KFAM	St. Cloud, Minn.	1450	KGMS	Sacramento, Calif.	1380
KBIG	Avalon, Calif.	740	KCRB	Chesnut, Kans.	1380	KFAR	Fairbanks, Alaska	660	KGNB	New Braunfels, Tex.	1420
KBIM	Roswell, N.Mex.	970	KCRD	Clinton, Oreg.	1400	KFBF	Great Falls, Mont.	1310	KGNC	Amarillo, Tex.	710
KBIS	Bakersfield, Calif.	970	KCRE	Crecent City, Calif.	1400	KFCB	Cheyenne, Wyo.	1240	KGND	Ogden, Kans.	1370
KBIX	Muskogee, Okla.	1490	KCRS	Cedar Rapids, Iowa	1600	KFCB	Wichita, Kans.	1070	KGOL	Golden, Colo.	1250
KBIZ	Ottumwa, Iowa	1240	KCRS	Midland, Tex.	550	KFCB	Sacramento, Calif.	1530	KGON	Oregon City, Oreg.	1520
KBKO	Portland, Oreg.	1290	KCRT	Trinidad, Colo.	1240	KFCB	Amarillo, Tex.	1440	KGOT	Torrington, Wyo.	1490
KBKR	Baker, Oreg.	1490	KCRV	Caruthersville, Mo.	1370	KFCB	Beaumont, Tex.	560	KGRM	Fayetteville, Ark.	1400
KBKW	Aberdeen, Wash.	1450	KCSB	San Bernardino, Calif.	1350	KFCB	Grand Coulee, Wash.	1400	KGRH	Henderson, Tex.	1000
KBLA	Burbank, Calif.	1490	KCSB	San Bernardino, Calif.	1350	KFCB	Pueblo, Colo.	970	KGRS	Gresham, Oreg.	1230
KBLF	Red Bluff, Calif.	1490	KCTG	Chadron, Nebr.	1450	KFFA	St. Joseph, Mo.	680	KGRT	Las Cruces, N.Mex.	570
KBLI	Blackfoot, Idaho	1490	KCTG	Springfield, Oreg.	1400	KFFA	Helena, Ark.	1360	KGST	Fresno, Calif.	1600
KBLO	Hot Springs, Ark.	1470	KCTI	Gonzales, Tex.	1450	KFFG	Fargo, N.Dak.	790	KGUH	Honolulu, Hawaii	760
KBMI	Henderson, Nev.	1490	KCTX	Childress, Tex.	1510	KFFG	Boone, Iowa	1260	KGVF	Greenville, Tex.	1400
KBMN	Bozeman, Mont.	1230	KCUE	Red Wing, Minn.	1250	KFFG	Forest Grove, Oreg.	1370	KGVO	Missoula, Mont.	1280
KBMO	Benon, Minn.	1290	KCVL	Fort Worth, Tex.	1540	KFFG	Forest Grove, Oreg.	1370	KGWA	Portland, Oreg.	620
KBMW	Breckinrdg., Minn.	1450	KCYR	Lodi, Calif.	1480	KFFG	Forest Grove, Oreg.	1370	KGYA	Enid, Okla.	960
KBWX	Coal Bluffs, Calif.	1470	KCYL	Lampasas, Tex.	1450	KFFG	Forest Grove, Oreg.	1370	KGYO	Olympia, Wash.	1240
KBMY	Billings, Mont.	1240	KDAC	Ft. Bragg, Calif.	1230	KFFG	Forest Grove, Oreg.	1370	KGYN	Gwynne, Okla.	1220
KBND	Bend, Oreg.	1110	KDAL	Duluth, Minn.	610	KFFG	Forest Grove, Oreg.	1370			

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KGYW	Vallejo, Calif.	1190	KLGR	Redwood Falls, Minn.	1490	KOA	Denver, Colo.	850	KQV	Pittsburgh, Pa.	1410
KHAM	Albuquerque, N. Mex.	1580	KLIC	Monroe, La.	1230	KOAC	Corvallis, Oreg.	550	KRAI	Craig, Colo.	350
KHAS	Hastings, Nebr.	1230	KLIF	Dallas, Tex.	1190	KOAL	Price, Utah	1230	KRAK	Stockton, Calif.	1140
KHBC	Hilo, Hawaii	970	KLJJ	Jefferson City, Mo.	950	KOAM	Pittsburg, Kans.	860	KRAL	Reinolds, W. Va.	1240
KHBM	Okmulgee, Okla.	1240	KLJL	Estherville, Iowa	1340	KOBE	Albuquerque, N. Mex.	1450	KRAM	Las Vegas, Nev.	970
KHBB	Monticello, Ark.	1430	KLIN	Lincoln, Nebr.	1400	KOBS	Las Cruces, N. Mex.	1450	KRAY	Amarillo, Tex.	1360
KHBR	Hillsboro, Tex.	1560	KLIR	Denver, Colo.	1310	KOCB	San Francisco, Calif.	1550	KRBA	Lufkin, Tex.	1340
KHCD	Clifton, Ariz.	1450	KLIX	Idaho Falls, Idaho	1310	KOCA	Kilgore, Tex.	1240	KRBC	Abilene, Tex.	1470
KHEM	Big Springs, Tex.	1270	KLIZ	Brainerd, Minn.	1380	KOCC	Ontario, Calif.	1510	KRBI	St. Peter, Minn.	1310
KHEN	Honolulu, Okla.	1590	KLKC	Parsons, Kans.	1540	KOCD	Oklahoma City, Okla.	1340	KRBO	Las Vegas, Nev.	1050
KHEY	El Paso, Tex.	690	KLKA	Leesville, La.	1570	KODE	Joplin, Mo.	1230	KRCK	Ridgecrest, Calif.	1380
KHIL	Brighton-Ford Lupton, Colorado	800	KLMO	Longmont, Colo.	1050	KODI	Cody, Wyo.	1400	KRCD	Baytown, Tex.	690
KHIT	Wallis Wallis, Wash.	1320	KLMM	Lamar, Colo.	920	KODL	The Dalles, Oreg.	1440	KRDE	Baytown, Tex.	620
KHEP	Phoenix, Ariz.	1280	KLMS	Lincoln, Nebr.	1480	KODY	North Platte, Nebr.	1240	KRDD	Colo. Springs, Colo.	1240
KHFS	Vancouver, Wash.	1150	KLNX	Clayton, N. Mex.	1450	KOEL	Oswego, Iowa	950	KRDU	Dinuba, Calif.	1240
KHJ	Los Angeles, Calif.	930	KLOG	Kelo, Wash.	1490	KOFA	Yuma, Ariz.	1240	KRE	Berkeley, Calif.	1400
KHMO	Hannibal, Mo.	1070	KLOG	Pikestone, Minn.	1050	KOFI	Kalispell, Mont.	980	KREN	Oakdale, La.	800
KHOB	Hobbs, N. Mex.	1280	KLOK	San Jose, Calif.	1170	KOFO	Ottawa, Kans.	1220	KREI	Farmington, Mo.	1360
KHON	Honolulu, T. H.	1380	KLOO	Corvallis, Oreg.	1340	KOGA	Ogallala, Nebr.	930	KREM	Spokane, Wash.	1360
KHOZ	Harrison, Ark.	1240	KLOS	Albuquerque, N. Mex.	1450	KOGT	Orange, Tex.	630	KREO	Indio, Calif.	1400
KHQ	Spokane, Wash.	590	KLOU	Lake Charles, La.	1580	KOH	Reno, Nev.	1570	KRES	St. Joseph, Mo.	1550
KHSL	Chico, Calif.	1290	KLOV	Loveland, Colo.	1578	KOHU	Horiston, Oreg.	1290	KREW	Sunnyside, Wash.	1230
KHUB	Watsonville, Calif.	1310	KLPM	Mont. N. Dak.	1390	KOIL	Omaha, Nebr.	970	KREX	Grand Junc., Colo.	920
KHUE	Eureka, Calif.	980	KLPR	Okla. City, Okla.	1140	KOIN	Portland, Oreg.	1200	KRFC	Rocky Ford, Colo.	1320
KHUZ	Borgher, Ariz.	1490	KLPW	Union, Mo.	1220	KOJM	Havre, Mont.	610	KRGV	Owatonna, Minn.	1390
KHYH	Honolulu, Hawaii	1040	KLRA	Little Rock, Ark.	1010	KOKO	Warrensburg, Mo.	1450	KRGT	Weslaco, Tex.	1290
KIBE	Palo Alto, Calif.	1220	KLRS	Mountain Grove, Mo.	1360	KOKX	Keokuk, Iowa	1310	KRGF	Grand Island, Neb.	1430
KIBH	Seward, Alaska	1340	KLTF	Little Falls, Minn.	960	KOL	Seaside, Wash.	1900	KRHD	Unstun, Okla.	1350
KIBL	Beeville, Tex.	1490	KLTR	Longview, Tex.	1280	KOLE	Port Arthur, Tex.	1340	KRIB	Mason City, Iowa	1490
KIBS	Blisph, Calif.	1230	KLTI	Blackwell, Okla.	1580	KOLJ	Quincy, Tex.	1150	KRIC	Beaumont, Tex.	1400
KICG	Clovis, N. Mex.	980	KLTZ	Glasgow, Mont.	1240	KOLS	Pryor, Okla.	1570	KRIG	Odessa, Tex.	1410
KICD	Spencer, Iowa	1240	KLUB	Salt Lake City, Utah	1370	KOLT	Scottsbluff, Nebr.	1320	KRIO	McAllen, Tex.	910
KICK	Springfield, Mo.	1340	KLUE	Shreveport, La.	1400	KOLY	Moberly, S. Dak.	1300	KRIS	Corpus Christi, Tex.	1360
KICG	Calixico, Calif.	1490	KLUF	Galveston, Tex.	1400	KOMA	Okla. City, Okla.	1520	KRIV	Camas, Wash.	1480
KID	Idaho Falls, Idaho	590	KLUV	Evanson, Wyo.	1240	KOMB	Cottage Grove, Oreg.	1400	KRIZ	Phoenix City, Mont.	1340
KIDD	Monterey, Calif.	630	KLUV	Haynesville, La.	1580	KOME	Tulsa, Okla.	1300	KRKD	Los Angeles, Calif.	1150
KIDO	Boise, Idaho	630	KLVA	Leadville, Colo.	1230	KOMF	Seattle, Wash.	1000	KRKO	Everett, Wash.	1380
KIEM	Eureka, Calif.	1480	KLVL	Pasadena, Tex.	1480	KOMW	Omak, Wash.	680	KRKS	Ridgecrest, Calif.	1240
KIEV	Glendale, Calif.	870	KLVT	Levelland, Tex.	1230	KONE	Reno, Nev.	1450	KRLC	Lewiston, Idaho	1350
KIFI	Idaho Falls, Idaho	1060	KLWN	Lawrence, Kans.	1240	KONI	Phoenix, Ariz.	1400	KRLD	Dallas, Tex.	1080
KIFB	Phoenix, Ariz.	860	KLWT	Lebanon, Mo.	1210	KONO	San Antonio, Tex.	860	KRLN	Canon City, Colo.	1400
KIFW	Sitka, Alaska	1230	KLX	Oakland, Calif.	930	KONP	Port Angeles, Wash.	1450	KRLW	Walnut Ridge, Ark.	1340
KIHN	Hugo, Okla.	1340	KLYN	Amarillo, Tex.	940	KOOK	Billings, Mont.	970	KRMJ	Shrewport, La.	1340
KIHO	Sioux Falls, S. Dak.	1270	KLYZ	Denver, Colo.	560	KOOL	Phoenix, Ariz.	960	KRMG	Tulsa, Okla.	740
KIHR	Hood River, Oreg.	1340	KMA	Shenandoah, Iowa	960	KOOS	Coos Bay, Oreg.	630	KRMO	Monett, Mo.	990
KIJV	Huron, S. Dak.	1340	KMAC	San Antonio, Tex.	630	KOPR	Tuam, Ariz.	1490	KRMS	Osage Beach, Mo.	1150
KIKS	Sulphur, La.	1310	KMAE	McKinney, Tex.	1600	KOPR	Butte, Mont.	350	KRMS	The Dalles, Oreg.	1300
KIKI	Honolulu, Hawaii	630	KMAK	Fresno, Calif.	1600	KOPY	Allice, Tex.	1070	KRND	San Bernardino, Calif.	1240
KILL	Lubbock, Tex.	1460	KMAN	Frankfort, Kans.	1340	KORA	Bryan, Tex.	1240	KRNR	Roseburg, Oreg.	1490
KILO	Grand Forks, N. Dak.	1060	KMAP	Bakersfield, Calif.	1490	KORC	Mineral Wells, Tex.	1140	KRNT	Des Moines, Iowa	1490
KILT	Houston, Tex.	610	KMAR	Winnabro, La.	1570	KORD	Pasco, Wash.	910	KRNY	Kearney, Nebr.	1460
KIMA	Yakima, Wash.	1460	KMBC	Kansas City, Mo.	980	KORE	Eugene, Oreg.	1450	KROC	Rochester, Minn.	1340
KIMM	Independence, Mo.	1510	KMBJ	Junta, Tex.	1240	KORK	Las Vegas, Nev.	1340	KROD	El Paso, Tex.	600
KIMN	Denver, Colo.	950	KMCM	McMinville, Oreg.	1260	KORN	Midvale, S. Dak.	1430	KROF	Abbeville, La.	960
KIMP	Mt. Pleasant, Tex.	860	KMCO	Conroe, Tex.	1260	KOSA	Little Rock, Ark.	1440	KROG	Sonora, Calif.	1450
KIND	Independence, Kans.	1010	KMCT	Medford, Oreg.	1440	KOSY	Odessa, Tex.	1230	KROP	Brawley, Calif.	1300
KING	Kingsville, Tex.	1090	KMED	Medford, Oreg.	1440	KOSE	Oseola, Ark.	860	KROS	Clinton, Iowa	1340
KING	Seattle, Wash.	1090	KMEL	Wenatchee, Wash.	1340	KOSF	Nacogdoches, Tex.	1230	KROW	Clarksburg, W. Va.	960
KIYA	Juneau, Alaska	940	KMHL	Marshall, Minn.	1400	KOTA	Aurora, Okla.	790	KROY	Sacramento, Calif.	1240
KIYO	Des Moines, Iowa	800	KMHT	Marshall, Tex.	1450	KOTA	Rapid City, S. Dak.	1380	KRPL	Moscow, Idaho	1400
KIOX	Bay City, Tex.	1270	KMIL	Cameron, Tex.	1330	KOTN	Pine Bluff, Ark.	1490	KRRV	Sherman, Tex.	910
KIPA	Hilo, Hawaii	1110	KMIN	Grants, N. M.	960	KOTS	Delmar, N. M.	1230	KRSC	Seattle, Wash.	1150
KIRK	Kirksville, Mo.	1450	KMN	Monroe, La.	1440	KOVC	Vailley City, N. Dak.	1430	KRSD	Rapid City, S. Dak.	990
KIRO	Seattle, Wash.	710	KMJ	Frederick, Md.	560	KOVE	Lander, Wyo.	1390	KRSL	Russell, Kans.	1490
KISD	Sioux Falls, S. Dak.	1230	KML	Marlin, Tex.	1010	KOVO	Provo, Utah	1300	KRSM	Los Angeles, N. Mex.	1490
KIST	Santa Barbara, Calif.	1340	KMLW	Grand Island, Nebr.	750	KOWB	Laramie, Wyo.	1390	KRTN	Raton, N. Mex.	1490
KIT	Yakima, Wash.	1280	KMMS	Marshall, Mo.	1300	KOWH	Omaha, Nebr.	660	KRRR	Thermopolis, Wyo.	1490
KITE	San Antonio, Tex.	930	KMNS	Sioux City, Iowa	620	KOWL	Blju, Calif.	1490	KRUS	Ballinger, Tex.	1490
KITI	Chehalis, Wash.	1420	KMOC	Moapa, Utah	1360	KOXR	Ornard, Calif.	910	KRUS	Ruston, La.	1490
KITN	Olympia, Wash.	1440	KMON	Tacoma, Wash.	1360	KOY	Phoenix, Ariz.	550	KRVN	Lexington, Nebr.	1010
KITP	San Bernardino, Calif.	1290	KMOO	Mont. Falls, Mont.	580	KOYL	Odessa, Tex.	1310	KRVX	Glendale, Ariz.	1370
KITL	Garden City, Kans.	1240	KMOV	Oreville, Calif.	1340	KOYN	Billings, Mont.	910	KRXK	Reburg, Idaho	1230
KIUN	Pecos, Tex.	1400	KMOX	St. Louis, Mo.	1120	KOZE	Lewiston, Idaho	950	KRXL	Roseburg, Oreg.	1240
KIUP	Durango, Colo.	930	KMPC	Los Angeles, Calif.	710	KPAC	Port Arthur, Tex.	1250	KSAC	Manhattan, Kans.	1150
KIUV	Crockett, Tex.	1290	KMRC	Morgan City, La.	1430	KPAD	Pampa, Tex.	1240	KSAM	Huntsville, Tex.	1490
KIWW	San Antonio, Tex.	1540	KMRS	Morris, Minn.	1570	KPAM	Portland, Oreg.	1450	KSAN	San Francisco, Calif.	1380
KIXL	Dallas, Tex.	1040	KMUL	Muldoon, Tex.	1380	KPAN	Hereford, Tex.	860	KSBJ	Salinas, Calif.	1270
KIXP	Provo, Utah	1400	KMUR	Murray, Utah	1250	KPAS	Banning, Calif.	1230	KSCJ	Sioux City, Iowa	1360
KIYI	Shelby, Mont.	1150	KMUS	Missoula, Okla.	1390	KPAT	Pampa, Tex.	740	KSDC	Santa Cruz, Calif.	1080
KJAM	Vernal, Utah	1340	KMY	Walluku, T. H.	550	KPDN	Pampa, Tex.	1340	KSDL	St. Louis, Mo.	550
KJAN	Atlantic, Iowa	1220	KMYR	Marysville, Calif.	1410	KPDP	Portland, Oreg.	800	KSDA	Redding, Calif.	1490
KJAY	Topeka, Kans.	1440	KMYR	Denver, Colo.	710	KPEP	San Angelo, Tex.	1420	KSDS	San Diego, Calif.	1130
KJBC	Midland, Tex.	1150	KNAF	Fredericksburg, Tex.	1340	KPET	Lamesa, Tex.	690	KSDT	Abbeville, N. Dak.	930
KJBS	San Francisco, Calif.	1100	KNAK	Salt Lake City, Utah	1280	KPHO	Phoenix, Ariz.	1510	KSEK	Pittsburg, Kans.	1340
KJCF	Festus, Mo.	1010	KNAV	Victoria, Tex.	1410	KPIN	Casa Grande, Ariz.	1260	KSEL	Lubbock, Tex.	950
KJKC	Juncton City, Kans.	1420	KNBC	San Francisco, Calif.	1050	KPKG	Pasco, Wash.	1470	KSEM	Moses Lake, Wash.	1450
KJCK	Jennett, Mo.	1290	KNEC	Newark, Wash.	730	KPLC	Lake Charles, La.	1470	KSED	Durant, Okla.	750
KJET	Beaumont, Tex.	1380	KNEB	Newark, Ark.	1030	KPLK	Dallas, Oreg.	1460	KSEI	El Paso, Tex.	1440
KJFJ	Webster City, Iowa	1570	KNCC	Concordia, Kans.	1390	KPMC	Bakersfield, Calif.	1560	KSEW	Sitka, Alaska	1340
KJLT	North Platte, Nebr.	970	KNCD	Moberly, Mo.	1230	KPOC	Pocahontas, Ark.	1420	KSF	Seymour, Tex.	1230
KJNO	Juneau, Alaska	630	KNCG	Garden City, Kans.	1450	KPOJ	Portland, Oreg.	1330	KSFE	Needles, Calif.	1340
KJOE	Shreveport, La.	1480	KNDC	Hettinger, N. Dak.	1090	KPKA	Portland, Oreg.	1440	KSFO	San Francisco, Calif.	560
KJOY	Stockton, Calif.	1280	KNDY	Marysville, Kans.	1370	KPKB	Carlsbad, N. Mex.	1450	KSFT	Trinidad, Colo.	1280
KJRG	Newton, Kans.	950	KNEA	Newark, Mo.	970	KPOL	Los Angeles, Calif.	1540	KSGB	Reinold, Oreg.	1240
KJKS	Columbus, Nebr.	920	KNEB	Scottsbluff, Nebr.	960	KPOO	San Francisco, Calif.	1010	KSGM	Ste. Genevieve, Mo.	990
KJUN	Redmond, Oreg.	1240	KNEC	McAlester, Okla.	1150	KPOP	Los Angeles, Calif.	1020	KSIB	Creston, Iowa	1340
KKIN	Visalia, Calif.	1400	KNEL	Brady, Tex.	1490	KPPC	Pasadena, Calif.	1260	KSIG	Crowley, La.	1450
KKOG	Ogden, Utah	730	KNEV	Nevada, Mo.	1250	KPRC	Houston, Tex.	560	KSII	Gladewater, Tex.	1320
KLAC	Los Angeles, Calif.	570	KNEP	Palestine, Tex.	1450	KPRK	Livingston, Mont.	1340	KSIS	Silver City, N. Mex.	1340
KLAD	Klamath Falls, Oreg.	900	KNEU	Provo, Utah	1450	KPRP	Paso Robles, Calif.	1230	KSIM	Sikeston, Mo.	1400
KLAK	Lakewood, Colo.	1600	KNEW	Spokane, Wash.	1540	KPRL	Riverside, Calif.	1440	KSIS	Sedalia, Mo.	1050
KLAM	Cordova, Alaska	1450	KNEK	Newark, Kans.	1040	KPRS	Kansas City, Mo.	1590	KSJB	Jamestown, N. Dak.	600
KLAS	Las Vegas, Nev.	1010	KNGS	Hanford, Calif.	620	KPST	Preston, Idaho	1400	KSJO	San Jose, Calif.	1590
KLBM	La Grande, Oreg.	1450	KNIM	Marysville, Mo.	1580	KPUG	Carrollton, Wash.	1170			
KLCB	Libby, Mont.	1230	KNLR	N. Little Rock, Ark.	1380	KQIK	Lakewood, Oreg.	1230			
KLCN	Blytheville, Ark.	910	KNOC	Natchitoches, La.	1450	KQUE	Albuquerque, N. Mex.	920			
KLCO	Poteau, Okla.	1280	KNOE	Monroe, La.	1390						
KLEA	Livingston, N. Mex.	630	KNOG	Nogales, Ariz.	1340						
KLEB	Knoxville, Tenn.	1480	KNOF	Ft. Worth, Tex.	970						
KLEE	Ottumwa, Iowa	1480	KNOR	Norman, Okla.	1400						
KLEM	LeMars, Iowa	1410	KNOW	Austin, Tex.	1490						
KLEN	Killeen, Tex.	1050	KNOX	Grand Forks, N. Dak.	1310						
KLER	Lewiston, Idaho	1300	KNPT	Newport, Oreg.	1310						
KLEX	Lexington, Mo.	1570	KNUJ	New Ulm, Minn.	1300						
KLFT	Golden Meadow, La.	1600	KNUZ	Houston, Tex.	1260						
KLGA	Algonia, Iowa	1600	KNWS	Waterloo, Iowa	1090						
			KNX	Los Angeles, Calif.	1070						

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
KSJV	Sanger, Calif.	900	KTXN	Austin, Tex.	1370	KWJC	Northtoches, La.	1450	WACE	Chicago, Mass.	730
KSJY	Dallas, Tex.	860	KTYL	Mesa, Ariz.	1310	KWJL	Portland, Oreg.	1080	WACV	Waycross, Ga.	570
KSLM	Salt Lake City, Utah	1160	KUBA	Yuba City, Calif.	1600	KWIP	Merced, Calif.	1580	WACO	Waco, Tex.	1460
KSLM	Salem, Oreg.	1390	KUCB	Monrovia, Colo.	1260	KWIQ	Moses Lake, Wash.	1260	WACR	Columbus, Miss.	1050
KSLD	Opeolous, La.	1230	KUBE	Pendleton, Oreg.	1050	KWK	St. Louis, Mo.	1380	WADC	Akron, Ohio	1350
KSLR	Oceanside, Calif.	1230	KUDI	Grand Falls, Mont.	1450	KWKS	Shreveport, La.	1340	WAD	Wadesboro, N.C.	1210
KSMA	Santa Maria, Calif.	1430	KUDL	Kansas City, Mo.	1380	KWKP	Padonia, Calif.	1130	WADK	Newport, R.I.	1540
KSM	San Jose, Calif.	1250	KUDU	Ventura, Calif.	1590	KWLC	Decorah, Iowa	1300	WADP	Kane, Pa.	960
KSNN	Mason City, Iowa	1010	KUEN	Wenatche, Wash.	1410	KWLD	Longview, Wash.	1400	WAE	Ansonia, Conn.	690
KSNM	Salem, Mo.	1450	KUGN	Eugene, Oreg.	390	KWLF	Wilmington, N.C.	1240	WAG	Albion, Pa.	790
KSNY	Snyder, Tex.	1340	KUIK	Hillsboro, Oreg.	1360	KWLM	Willmar, Minn.	1840	WAGL	Mayaguez, P.R.	600
KSD	Des Moines, Iowa	1460	KUIN	Grants Pass, Oreg.	1340	KWNA	Winemucca, Nev.	1400	WAEW	Crossville, Tenn.	1330
KSOK	Arkansas City, Kans.	1280	KUJ	Wallia Walla, Wash.	1420	KWNO	Winona, Minn.	1230	WAGA	Atlanta, Ga.	590
KSON	San Diego, Calif.	1140	KUKI	Ukiah, Calif.	1400	KWOW	Worthington, Minn.	730	WAGC	Chattanooga, Tenn.	1560
KSOO	Sioux Falls, S. Dak.	1370	KULA	Honolulu, H.	1490	KWOC	Poplar Bluff, Mo.	930	WAGD	Dothan, Ala.	1320
KSOB	Salt Lake City, Utah	1240	KULE	Ephrata, Wash.	730	KWON	Bartlesville, Okla.	1320	WAGF	Franklin, Tenn.	950
KSPA	Santa Paula, Calif.	1400	KULP	El Campo, Tex.	1290	KWOR	Worland, Wyo.	1400	WAGG	Presque Isle, Maine	1450
KSPI	Stillwater, Okla.	780	KUMA	Pendleton, Oreg.	1390	KWOS	Jefferson City, Mo.	1240	WAGN	Menomonee, Mich.	1340
KSPR	Casper, Wyo.	1470	KUNO	Corpus Christi, Tex.	1400	KWPA	Pomona, Calif.	1600	WAGR	Lumberton, N.C.	1480
KSPS	Sandpoint, Idaho	1400	KUOA	Siloam Springs, Ark.	1290	KWPC	Muscatine, Iowa	860	WAGS	Bishopville, S.C.	1380
KSRD	Santa Rosa, Calif.	1350	KUOM	Minneapolis, Minn.	710	KWPM	West Plains, Mo.	1450	WAGR	Miami Beach, Fla.	1490
KSRV	Ontario, Oreg.	1380	KURV	Edinburg, Tex.	770	KWRC	Pendleton, Oreg.	1240	WAIM	Baton Rouge, La.	1460
KSTP	Sulphur Springs, Tex.	1230	KUSD	Cummins, S. Dak.	690	KWRD	Henderson, Tex.	1470	WAIN	Columbia, S.C.	1230
KSTA	Coloman, Mo.	1000	KUSC	Canton, Mo.	1500	KWRW	Warrenton, Wyo.	730	WAIR	Richard, Ala.	1270
KSTB	Breckenridge, Tex.	1430	KUSN	St. Joseph, Mo.	600	KWRW	Warrenton, Wyo.	860	WAIR	Waycross, Ga.	1340
KSTL	St. Louis, Mo.	690	KUTI	Yakima, Wash.	980	KWRW	Riverton, Wyo.	1450	WAJF	Chicago, Ill.	820
KSTN	Stockton, Calif.	1420	KUVR	Holdrege, Nebr.	1380	KWRN	Reno, Nev.	1230	WAJF	Decatur, Ala.	1490
KSTP	St. Paul, Minn.	1500	KUZN	W. Monroe, La.	910	KWRO	Coquille, Oreg.	1450	WAK	Morgantown, W.Va.	1290
KSTT	Davenport, Iowa	1170	KVAN	Vancouver, Wash.	1310	KWRT	Boonville, Mo.	1370	WAKE	Atlanta, Ga.	1340
KSTV	Stephenville, Tex.	1510	KVAS	Astoria, Oreg.	1230	KWRT	Guthrie, Okla.	1490	WAKN	Aiken, S.C.	890
KSUB	Cedar Falls, S. Dak.	1240	KVC	Carrollton, N. Mex.	1270	KWSE	Wagon Wheel, Wash.	1250	WAKR	Akron, Ohio	1590
KSUE	Susanville, Calif.	1370	KVCL	Winfield, La.	1270	KWSD	Mid. Shasta, Calif.	1340	WALB	Mobile, Ala.	1570
KSUM	Fairmont, Minn.	1370	KVCC	Redding, Calif.	600	KWSD	Wewoka-Seminole, Okla.	1260	WALB	Albany, Ga.	1590
KSUM	Bisbee, Ariz.	1230	KVEC	San Luis Obispo, Calif.	920	KWSK	Pratt, Kans.	1570	WALD	Waterboro, S.C.	1220
KSVK	Riethland, Utah	980	KVEN	Ventura, Calif.	1450	KWSO	Wasco, Calif.	1050	WALE	Fall River, Mass.	1400
KSPV	Artesia, N. Mex.	990	KVER	Albuquerque, N. Mex.	1340	KWTC	Barstow, Calif.	1290	WALF	Patchogue, N.Y.	1370
KSWA	Graham, Tex.	1330	KVET	Austin, Tex.	1300	KWTF	Springfield, Mo.	560	WALL	Middletown, N.Y.	1340
KSWB	Conroe, Bluffs, Iowa	1560	KVFD	F. Dodge, Iowa	1400	KWTX	Waco, Tex.	1490	WALM	Albion, Mich.	1260
KSWD	Lawton, Okla.	1380	KVGB	Great Bend, Kans.	1590	KWVB	Walla Walla, Wash.	1490	WALN	Warren, Pa.	1110
KSWS	Roswell, N. Mex.	1230	KVGR	Homestead, Kans.	1320	KWVL	Waterloo, Iowa	1330	WALY	Herkimer, N.Y.	1420
KSYC	Yreka, Calif.	1490	KVI	Seattle, Wash.	570	KWVN	Wynne, Ark.	1400	WAMI	Opp, Ala.	860
KTAC	Tacoma, Wash.	850	KVIC	Victoria, Tex.	1340	KWVO	Sheridan, Wyo.	1410	WAML	Laurel, Miss.	1340
KTAE	Taylor, Tex.	1260	KVIN	New Iberia, La.	1360	KXAR	Seattle, Wash.	1490	WAMM	Flint, Mich.	1420
KTAN	Sherman, Tex.	1500	KVIN	Vinita, Okla.	1470	KXAR	Hope, Ark.	1490	WAMO	Homestead, Pa.	860
KTAR	Phoenix, Ariz.	620	KVKM	Cimarron, Tex.	1570	KXBL	Portland, Iowa	1440	WAMS	Wilmington, Del.	1360
KTAT	Fredonia, Okla.	1370	KVLB	Cleveland, Tex.	1410	KXBL	Bozeman, Mont.	1230	WAMY	Waynesburg, Pa.	1580
KTBB	Tyler, Tex.	600	KVLC	Little Rock, Ark.	1050	KXGL	Fort St. Madison, Iowa	1360	WAMY	Amory, Miss.	1580
KTBC	Austin, Tex.	590	KVLF	Alpine, Tex.	1240	KXGL	Glendive, Mont.	1400	WANA	Anniston, Ala.	1490
KTBS	Shreveport, La.	710	KVLS	Pauls Valley, Okla.	1470	KXIA	Daingerfield, Tex.	810	WANB	Waynesburg, Pa.	1580
KTCA	Malden, Mo.	1470	KVMA	Magnolia, Ariz.	690	KXIA	Corraet City, Ark.	950	WAND	Canton, Ohio	900
KTCS	Fort Smith, Ark.	1410	KVNA	Flagstaff, Ariz.	630	KXIA	Portland, Oreg.	750	WANE	Fl. Wayne, Ind.	1450
KTED	Laguna Beach, Calif.	1520	KVNC	Colorado City, Tex.	1320	KXLB	Butte, Mont.	1240	WANF	Annapolis, Md.	1190
KTEL	Walla Walla, Wash.	1490	KVND	Denver, Colo.	1480	KXLF	Helena, Mont.	970	WANP	Anderson, S.C.	1280
KTEM	Tempe, Tex.	1400	KVNE	Coeur d'Alene, Idaho	1240	KXLL	Helena, Mont.	1400	WAOK	Atlanta, Ga.	1380
KTER	Terrill, Tex.	1570	KVNU	Logan, Utah	1290	KXLL	Great Falls, Mont.	1450	WAOP	Vincennes, Ind.	1450
KTFI	Twin Falls, Idaho	1270	KVOA	Tucson, Ariz.	1290	KXLL	Missoula, Mont.	1230	WAPA	San Juan, P.R.	680
KTFB	Texarkana, Tex.	1400	KVOB	Alexandria, La.	970	KXLL	Bozeman, Mont.	1450	WAPP	McComb, Miss.	980
KTFY	Brownfield, Tex.	1300	KVOC	Casper, Wyo.	1230	KXLL	Bozeman, Mont.	1450	WAPR	Arad, Fla.	1480
KTME	Thermopolis, Wyo.	1240	KVOD	Denver, Colo.	1480	KXLL	Bozeman, Mont.	1450	WAPL	Birmingham, Ala.	1070
KTKL	Little Rock, Ark.	1090	KVOM	Omaha, Neb.	1490	KXLL	Bozeman, Mont.	1450	WAPM	Appleton, Wis.	1570
KTKH	Houston, Tex.	730	KVON	Ogden, Utah	1490	KXLL	Little Rock, Ark.	1150	WAPN	Chattanooga, Tenn.	1150
KTIB	Thibodaux, La.	800	KVOL	Lafayette, La.	1330	KXLL	Clayton, Mo.	1120	WAPX	Montgomery, Ala.	1600
KTIL	Tillamook, Oreg.	1240	KVOM	Morrilton, Ark.	800	KXLY	Spokane, Wash.	1230	WARA	Axtellboro, Mass.	1320
KTIM	San Rafael, Calif.	1510	KVON	Napa, Calif.	1440	KXLY	El Centro, Calif.	920	WARB	Covington, La.	730
KTIP	Porterville, Calif.	1450	KVON	Tulsa, Okla.	1170	KXMA	Sacramento, Calif.	1470	WARD	Johnston, Tex.	1490
KTIS	Minneapolis, Minn.	900	KVPI	Plainville, Tex.	1400	KXOC	Chicago, Ill.	1060	WARF	Waynes, Mass.	1250
KTIS	Seattle, Wash.	1520	KVPS	Bellevue, Wash.	1300	KXOK	St. Louis, Mo.	630	WARK	Hagerstown, Md.	1490
KTIS	Hot Springs, Ark.	1340	KVPS	Bellevue, Wash.	1300	KXOK	St. Louis, Mo.	630	WARM	Arlington, Va.	790
KTKN	Ketchikan, Alaska	930	KVPS	Bellevue, Wash.	1300	KXRA	Alexandria, Minn.	1240	WARP	Scranton, Pa.	580
KTKR	Taft, Calif.	1310	KVPS	McGehee, Ark.	1220	KXRR	Russellville, Ark.	1490	WARQ	Fort Pierce, Fla.	1330
KTKT	Tucson, Ariz.	990	KVPS	Santa Fe, N. Mex.	1260	KXRR	Renton, Wash.	910	WARU	Peru, Ind.	1600
KTLD	Tululahu, La.	1360	KVPS	San Mateo, Calif.	1050	KXSB	Shelton, Wash.	1320	WASA	Havre de Grace, Md.	1330
KTLN	Denver, Colo.	1280	KVPS	Armore, Okla.	1240	KXSB	Shelton, Wash.	1320	WASF	Waynesville, Ind.	1450
KTLO	Mtn. Home, Ark.	1490	KVPS	Vernon, Tex.	1010	KXSB	Shelton, Wash.	1320	WATB	Benton, S.C.	1280
KTLS	Rusk, Tex.	920	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATC	Gaylord, Mich.	900
KTLL	Texarkana, Tex.	1490	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATE	Knoxville, Tenn.	1260
KTMC	McAlester, Okla.	1400	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATG	Ashland, Ohio	1340
KTML	Marked Tree, Ark.	1580	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATH	Athens, Ohio	970
KTMS	Santa Barbara, Calif.	1250	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATK	Antigo, Wis.	900
KTNC	Falls City, Nebr.	1230	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATM	Attmore, Ala.	1590
KTND	Tucumcari, N. Mex.	1400	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATN	Watertown, N.Y.	1240
KTNT	Tacoma, Wash.	1400	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATO	Oak Ridge, Tenn.	1320
KTOD	Mankato, Minn.	1420	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATR	Waterbury, Conn.	1320
KTOL	Lihue, Hawaii	1490	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATS	Sayre, Pa.	990
KTOK	Oklahoma City, Okla.	1000	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATT	Cadillac, Mich.	1240
KTOD	Henderson, Nev.	1280	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATW	Ashland, Wis.	1400
KTOP	Topeka, Kans.	1490	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATX	Alpena, Mich.	1450
KTOW	Oklahoma City, Okla.	800	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WATY	Auburn, Ala.	1230
KTRE	Modesto, Calif.	860	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAUX	Waukesha, Wis.	1510
KTRE	Santa Fe, N. Mex.	1400	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAVE	Louisville, Ky.	970
KTRE	Lufkin, Tex.	1420	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAVI	Dayton, Ohio	1210
KTRE	Thief River Falls, Minn.	1230	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAVL	Apollo, Pa.	910
KTRH	Houston, Tex.	740	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAVN	Stillwater, Minn.	1220
KTRI	Sioux City, Iowa	1470	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAVU	Albertville, Ala.	630
KTRM	Beaumont, Tex.	990	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAVV	New Haven, Conn.	1300
KTRN	Wichita Falls, Tex.	290	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAWZ	Waycross, Ga.	1380
KTRY	Bastrop, La.	730	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAYB	Waynesboro, Va.	1490
KTSA	San Antonio, Tex.	550	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAYE	Dundalk, Md.	860
KTSD	El Paso, Tex.	1380	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAYN	Rockingham, N.C.	900
KTSE	Tranton, Mo.	1690	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAYS	Charlotte, N.C.	610
KTTR	Rolla, Mo.	1400	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAYX	Waycross, Ga.	1230
KTTS	Springfield, Mo.	1400	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAYZ	Waynesboro, Pa.	1380
KTUC	Tucson, Ariz.	1400	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAZP	Waycross, Ga.	1380
KTUE	Tulia, Tex.	1260	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAZR	Waycross, Ga.	1380
KUDU	Ventura, Calif.	1590	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAZS	Waycross, Ga.	1380
KTUL	Lookout Mountain, Okla.	1430	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAZT	Waycross, Ga.	1380
KTUR	Turlock, Calif.	1390	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAZU	Waycross, Ga.	1380
KTUT	Tooele, Utah	990	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAZV	Waycross, Ga.	1380
KTW	Seattle, Wash.	1250	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAZW	Waycross, Ga.	1380
KTXC	Big Spring, Tex.	1400	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAZX	Waycross, Ga.	1380
KTXX	Jasper, Tex.	1350	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAZY	Waycross, Ga.	1380
KTXL	San Angelo, Tex.	1340	KVPS	Shawnee, Okla.	1050	KXSB	Shelton, Wash.	1320	WAZZ	Waycross, Ga.	1380
			KWJR	Globe, Ariz.	1240	KWAC	Kittanning, Pa.	1380	WBAW	Barrow, S.C.	740

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WBAY	Green Bay, Wis.	1360	WCBT	Benton, Ky.	1290	WDBF	Delray Beach, Fla.	1420
WBBA	Pittsfield, Ill.	1580	WCBM	Baltimore, Md.	680	WDBI	Roanoke, Va.	960
WBBC	Burlington, N.C.	1280	WCBN	New York, N.Y.	380	WDBL	Springfield, Tenn.	1430
WBBC	Filint, N.Y.	1330	WCBY	Chesapeake, Va.	1230	WDBO	Orlando, Fla.	580
WBFB	Rochester, N.Y.	950	WCBZ	Roanoke Rapids, N.C.	1240	WDBQ	Buque, Iowa	1400
WBBI	Abingdon, Va.	1230	WCC	Hartford, Conn.	1290	WDCF	Dade City, Fla.	1350
WBBL	Richmond, Va.	1480	WCCM	Lawrence, Mass.	800	WDDT	Tarpon Sprgs., Fla.	1400
WBBC	Chicago, Ill.	780	WCCO	Minneapolis, Minn.	830	WDDT	Greenville, Miss.	900
WBBC	Perry, Ga.	980	WCCP	Savannah, Ga.	1450	WDDY	Gulcoaster, Va.	1420
WBBO	Forest City, N.C.	780	WCDL	Carbondale, Pa.	1440	WDEB	Gulport, Miss.	1400
WBBC	Augusta, Ga.	1340	WCDJ	Edenton, N.C.	1340	WDEE	American, Ga.	1290
WBBC	Youngstown, Ohio	1240	WCDT	Winchester, Tenn.	900	WDEF	Chattanooga, Tenn.	1370
WBBC	Ponca City, Okla.	1230	WCEE	Rock Mount, N.C.	810	WDEH	Sweetwater, Tenn.	800
WBBC	Bay Minette, Ala.	1300	WCEB	DuBois, Pa.	1420	WDEL	Wilmington, Del.	1150
WBCK	Battle Creek, Mich.	930	WCEH	Hawkinsville, Ga.	610	WDEV	Waterbury, Vt.	550
WBCC	Bay City, Mich.	1440	WCEM	Cambridge, Md.	1240	WDGY	Minneapolis, Minn.	1130
WBCC	Bessemer, Ala.	1450	WCEN	Mt. Pleasant, Mich.	1150	WDHL	Bradenton, Fla.	1400
WBCC	Christiansburg, Va.	1260	WCER	Charlotte, Mich.	1390	WDIA	Memphis, Tenn.	1490
WBCC	Union, S.C.	1460	WCFL	Chicago, Ill.	900	WDIG	Dolph, Ala.	1450
WBCC	Pittsfield, Mass.	1420	WCGA	Calhoun, Ga.	1270	WDK	Orangeburg, S.C.	1310
WBEE	Harvey, Ill.	1570	WCGC	Belmont, N.C.	1200	WDK	Dingstree, S.C.	1260
WBEE	Elizabethton, Tenn.	1380	WCHA	Chambersburg, Pa.	820	WDKN	Kingsport, Tenn.	1470
WBEL	Bella, Wis.	930	WCHB	Inkster, Mich.	1440	WDLA	Walton, N.Y.	1270
WBEL	Buffalo, Wis.	1360	WCHF	Chippewa Falls, Wis.	1150	WDLB	Marshfield, Wis.	1450
WBET	Brockton, Mass.	1460	WCHI	Chillicothe, Ohio	1350	WDLCP	Jervis, N.Y.	590
WBEU	Beaufort, S.C.	960	WCHJ	Brookhaven, Miss.	1470	WDMF	Buford, Ga.	1460
WBEV	Beaver Dam, Wis.	1430	WCHK	Wanton, Ga.	1290	WDMJ	Douglas, Ga.	860
WBEX	Chillicothe, Ohio	1490	WCHO	Washington Court House, Ohio	1250	WDM	Marquette, Mich.	1320
WBFC	Freemont, Mich.	1490	WCHL	Chapel Hill, N.C.	1360	WDNC	Durham, N.C.	620
WBFD	Bedford, Pa.	1240	WCHN	Norwich, N.Y.	970	WDNE	Elkins, W.Va.	1240
WBGC	Chillicothe, Fla.	1370	WCHS	Charleston, W.Va.	580	WDOB	Canton, Miss.	1370
WBGR	Jesup, Ga.	1240	WCHV	Charlottesville, Va.	1260	WDD	Chattanooga, Tenn.	1260
WBHB	Fitzgerald, Ga.	1450	WCIL	Carbondale, Ill.	1020	WDDN	Wheaton, Md.	1540
WBHF	Cartersville, Ga.	1230	WCIN	Cincinnati, Ohio	1450	WDDR	Sturgeon Bay, Wis.	910
WBHP	Huntsville, Ala.	1230	WCJU	Columbia, Miss.	780	WDOO	Oneonta, N.Y.	730
WBIA	Augusta, Ga.	1050	WCK	Green, S.C.	1300	WDOT	Burlington, Va.	1400
WBIE	Marletta, Ga.	1400	WCKR	Miami, Fla.	610	WDQV	Dover, Del.	1410
WBIG	Greensboro, N.C.	1240	WCKY	Cincinnati, Ohio	1530	WDOQ	Quakertown, Pa.	980
WBIP	Brownsville, Miss.	1470	WCLA	Colonial Hts., Va.	1290	WDR	Hartford, Conn.	1360
WBIR	Knoxville, Tenn.	1400	WCLB	Camilla, Ga.	1220	WDRC	Chester, Pa.	1590
WBIS	Bristol, Conn.	1340	WCLD	Cleveland, Miss.	1490	WDS	Dillon, S.C.	800
WBIV	Bedford, Ind.	950	WCLG	Morgantown, W.Va.	1300	WDSG	Dyersburg, Tenn.	1450
WBIZ	Eau Claire, Wis.	1470	WCLH	Clinton, N.Y.	1450	WDSM	Superior, Wis.	710
WBKH	Hattiesburg, Miss.	930	WCLJ	Clinton, N.Y.	1230	WDSP	Defunick Springs, Fla.	1280
WBKV	West Bend, Wis.	1470	WCLM	Lawrenceville, Ga.	1430	WDSR	Lake City, Fla.	1340
WBLA	Elizabethtown, N.C.	1290	WCLN	Clinton, N.Y.	1230	WDSU	New Orleans, La.	1280
WBLE	Batesville, Miss.	1230	WCLS	Columbus, Ga.	1380	WDTV	St. John, V.I.	1190
WBLL	Dalton, Ga.	1230	WCLT	Newark, Ohio	1430	WDUN	Gainesville, Ga.	1240
WBLC	Kirksburg, W.Va.	1400	WCMA	Corinth, Miss.	1230	WDUX	Waupeca, Wis.	800
WBLS	Batesburg, S.C.	1430	WCMB	Harrisburg-Lemoyne, Pennsylvania	1460	WDVA	Green Bay, Wis.	1400
WBLL	Bedford, Va.	1350	WCME	Wildwood, N.J.	1230	WDV	Danville, Va.	1250
WBLL	Salem, Va.	1480	WCMI	Ashtand, Ky.	1340	WDVH	Gainesville, Va.	1400
WBLY	Springfield, Ohio	1600	WCML	Ashtand, Ky.	1340	WDVM	McCombe City, Md.	540
WBMA	Beaufort, N.C.	1400	WCMM	Arcelco, P.R.	1280	WDW	Dorland, Ga.	990
WBMC	McMinnville, Tenn.	750	WCMS	Norfolk, Va.	1050	WDWB	Chattanooga, Tenn.	1450
WBMD	Baltimore, Md.	950	WCMT	Canton, Ohio	1060	WDXE	Lawrenceburg, Tenn.	1370
WBML	Macon, Ga.	1240	WCMT	Ottawa, Ill.	1430	WDXI	Jackson, Tenn.	1310
WBMS	Boston, Mass.	1090	WCNB	Connersville, Ind.	1540	WDXL	Lexington, Tenn.	1490
WBNL	Boonville, Ind.	1450	WCNC	Charlotte, N.C.	1240	WDYN	Durham, N.C.	1050
WBNS	Columbus, Ohio	1560	WCNH	Quincy, Fla.	1230	WEAB	Greer, S.C.	800
WBNX	New York, N.Y.	1340	WCNI	Centralla, Ill.	910	WEAM	Arlington, Va.	1390
WBNY	Buffalo, N.Y.	1360	WCNR	Bloomsburg, Pa.	920	WEAN	Providence, R.I.	790
WBBO	Galax, Va.	1600	WCNT	Centralla, Ill.	1210	WEAR	Pensacola, Fla.	1230
WBCC	Salisbury, Md.	960	WCNU	Crestview, Fla.	1010	WEAS	Decatur, Ga.	850
WBCC	Virginia Beach, Va.	1600	WCNX	Middletown, Conn.	1150	WEAW	Washington, Wis.	790
WBCK	New Orleans, La.	800	WCOC	Pensacola, Fla.	1370	WEAW	Plattsburg, N.Y.	960
WBOP	Pensacola, Fla.	800	WCOC	Clinton, Miss.	910	WEAV	Evanston, Ill.	1330
WBOS	Brookline, Mass.	1600	WCOD	Greensboro, N.C.	1320	WEBB	Dundalk, Md.	560
WBOW	Terrace, Ind.	1230	WCCH	Newnan, Ga.	1400	WEBC	Duluth, Minn.	1240
WBPC	Lock Haven, Pa.	1230	WCCL	Coatesville, Pa.	1420	WEBJ	Brewton, Ala.	1240
WBRC	Mt. Clemens, Mich.	1430	WCCL	Columbus, Ohio	1230	WEBK	Harrisburg, Ill.	970
WBRC	Birmingham, Ala.	960	WCCL	Parkersburg, W.Va.	1230	WEBL	Buffalo, N.Y.	1330
WBRC	Wilkes-Barre, Pa.	1340	WCOC	Cornelia, Ga.	1450	WEBC	Millon, Fla.	1330
WBRC	Lynchburg, Va.	1050	WCOC	Cornelia, Ga.	1450	WECC	Chicago, Ill.	1240
WBRC	Pittsfield, Mass.	1340	WCOR	Lebanon, Tenn.	1290	WEDC	McKeesport, Pa.	810
WBRC	Big Rapids, Mich.	1460	WCOS	Columbia, S.C.	1240	WEDR	Birmingham, Ala.	1220
WBRO	Waynesboro, Ga.	1310	WCOW	Lewiston, Maine	1170	WEEB	Southern Pines, N.C.	1390
WBRT	Bardonia, Ky.	1320	WCOW	Montgomery, Ala.	1400	WEED	Rocky Mount, N.C.	990
WBRY	Boonville, N.Y.	900	WCOW	Sparta, Wis.	1290	WEFC	Boston, Mass.	590
WBXX	Beekick, Pa.	1280	WCPC	Clearfield, Pa.	900	WEEK	Peoria, Ill.	1350
WBRY	Waterbury, Conn.	1590	WCPC	Houston, Miss.	1320	WEED	Reading, Pa.	850
WBSC	Bennsville, S.C.	1550	WCPC	Cumberland, Ky.	1490	WEEX	Easton, Pa.	1230
WBSE	Hillsdale, Mich.	1340	WCPO	Cincinnati, Ohio	1230	WEGA	Newton, Miss.	1410
WBSP	New Bedford, Mass.	1420	WCPS	Tarboro, N.C.	760	WEGO	Concord, N.C.	1450
WBSP	Pensacola, Fla.	1450	WCRA	Emingham, Ill.	1090	WEHH	Elmhurst Heights, N.Y.	1590
WBST	Charlotte, N.C.	1110	WCRB	Waltham, Mass.	1330	WEIC	Charleston, Ill.	1270
WBTA	Batavia, N.Y.	1490	WCRE	Cheraw, S.C.	1420	WEIM	Fitchburg, Mass.	1280
WBTH	Williamson, W.Va.	1400	WCRI	Scottsboro, Ala.	1050	WEIR	Weirton, W.Va.	1430
WBTM	Danville, Va.	1330	WCRI	Morristown, Tenn.	1450	WEJL	Seranton, Pa.	630
WBTV	Berlin, N.J.	1370	WCRL	Oneonta, Ala.	1570	WEKR	Fayetteville, Tenn.	1240
WBTO	Linton, Ind.	1600	WCRO	Johnstown, Pa.	1230	WEKY	Richmond, Ky.	840
WBUD	Trenton, N.J.	1260	WCRS	Greenwood, S.C.	1450	WEK	Monroe, La.	1260
WBUT	Butler, Pa.	1050	WCRT	Birmingham, Ala.	1260	WEK	Welch, W.Va.	1150
WBUX	Doylesstown, Pa.	1440	WCRT	Washington, N.J.	1580	WELD	Fisher, W.Va.	690
WBUX	Lexington, N.C.	1440	WCRT	Washington, N.J.	1580	WELI	New Haven, Conn.	960
WBVL	Barboursville, Ky.	1230	WCRC	Chicago, Ill.	1390	WELK	Charlottesville, Va.	1010
WBVP	Beaver Falls, Pa.	1560	WCRC	Portland, Maine	970	WELL	Battle Creek, Mich.	1400
WBYS	Camden, Ill.	1010	WCSC	Columbus, Ind.	1010	WELM	Elmira, N.Y.	1400
WBZ	Boston, Mass.	1030	WCSS	Columbus, Ind.	1010	WELP	Tupelo, Miss.	1360
WBZA	Springfield, Mass.	1250	WCST	Amsterdam, N.Y.	1490	WELR	Roanoke, Ala.	1360
WBZA	Pittsburgh, Pa.	1030	WCCT	Andalusia, Ala.	920	WELS	Kingston, N.C.	1010
WBAL	Northfield, Minn.	770	WCCT	New Brunswick, N.J.	1450	WELY	Ely, Minn.	1450
WBAM	Camden, N.J.	1310	WCCT	Corbin, Ky.	680	WEMB	Erwin, Tenn.	1420
WBAP	Baltimore, Md.	600	WCUE	Akron, Ohio	680	WEMP	Millwaukee, Wis.	1250
WBAR	Detroit, Mich.	980	WCUM	Cumland, Md.	1230	WENA	Bayamon, P.R.	1560
WBAS	Gadsden, Ala.	1450	WCVA	Cuiper, Va.	1490	WENC	Whiteville, N.C.	1220
WBAC	Orange, Mass.	1390	WCVA	Connellsville, Pa.	1340	WEND	Baton Rouge, La.	1430
WBAC	Philadelphia, Pa.	1210	WCVS	Springfield, Ill.	1450	WENE	Endot, N.Y.	1380
WBAC	Charleston, W.Va.	1300	WCVB	Crystal, Va.	680	WENT	Union City, Tenn.	1240
WBAC	Burlington, Vt.	820	WCYD	Cynthiana, Ky.	1450	WENT	Gloversville, N.Y.	1340
WBAC	Carthage, Mo.	1350	WCYD	Indiana, Pa.	1250			
WBAC	Cornell, N.Y.	1350	WDAA	Kansas City, Mo.	610			
WBAC	Anderson, Ind.	820	WDAN	Danville, Ill.	1490			
WBAC	Chicago, Ill.	820	WDAS	Philadelphia, Pa.	1480			
WBAC	Chambersburg, Pa.	1500	WDAY	Fargo, N. Dak.	970			
WBAC	Columbus, Miss.	550	WDDB	Escanaba, Mich.	680			

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WGAN	Portland, Maine	560	WHER	Memphis, Tenn.	1430	WINN	Louisville, Ky.	1240	WJRD	Tuscaloosa, Ala.	1150
WGAP	Warfield, Tenn.	1400	WHFB	Benton Harbor, Mich.	1080	WINS	Binghamton, N.Y.	680	WJSB	Crestview, Fla.	1050
WGAR	Cleveland, Ohio	1220	WHFC	Cfarc, Ill.	1400	WIS	New York, N.Y.	1010	WJTN	Jamestown, N.Y.	1240
WGAU	Athens, Ga.	1340	WHGB	Harrisburg, Pa.	1400	WINZ	Miami, Fla.	1600	WJUN	Mexico, Pa.	1280
WGAW	Gardner, Mass.	1340	WHRG	Houghton L., Mich.	1290	WISN	Madison, Wis.	1480	WJVA	South Bend, Ind.	1520
WGAY	Silver Springs, Md.	1050	WHHH	Warren, Ohio	1440	WIOK	Sanford, Fla.	1360	WJWC	Cleveland, Ohio	1450
WGBA	Columbia, S.C.	1270	WHHM	Montgomery, Ala.	1440	WIOK	Tampa, Fla.	1430	WJWG	Conway, N.H.	850
WGBB	Fresport, N.Y.	1240	WHIM	Memphis, Tenn.	1340	WIOU	Jonla, Mich.	1430	WJWL	Georgetown, Ool.	900
WGBF	Evansville, Ind.	1280	WHIE	Griffin, Ga.	1320	WIP	Kokomo, Ind.	1350	WJWS	South Hill, Va.	1370
WGBG	Greensboro, N.C.	1400	WHIM	Worcester, Mass.	1110	WIP	Philadelphia, Pa.	610	WJXN	Jackson, Miss.	1450
WGBR	Seranton, Pa.	910	WHIN	E. Providence, R.I.	1010	WIPR	Annapolis, Md.	810	WJZM	Clarksville, Tenn.	1400
WGBS	Goldboro, N.C.	1150	WHIN	Gallatin, Tenn.	1010	WIPR	San Juan, P.R.	940	WKAB	Mobile, Ala.	840
WGBT	Miami, Fla.	710	WHIO	Dayton, Ohio	1290	WIPR	Ticonderoga, N.Y.	1250	WKBC	Wm. Westboro, N.C.	610
WGBU	Rehoboth, Pa.	1440	WHIP	Mooreville, N.C.	1350	WIRA	Fort Pierce, Fla.	1400	WKAL	Rome, N.C.	1510
WGCO	Chester, S.C.	1440	WHIR	Danville, Ky.	1230	WIRE	Enterprise, Ala.	1430	WKAM	Goshen, Ind.	1450
WGCM	Gulfport, Miss.	1240	WHIS	Bluefield, W.Va.	1440	WIRK	Hickory, N.C.	630	WKAN	Kanakee, Ill.	1320
WGEE	Geneva, Ala.	1150	WHIT	New Bern, N.C.	1450	WIRK	Indianapolis, Ind.	1430	WKAP	Allentown, Pa.	1320
WGEE	Indianapolis, Ind.	1590	WHIZ	Zanesville, Ohio	1240	WISK	St. Paul, Minn.	1590	WKAQ	San Juan, P.R.	580
WGEM	Quincy, Ill.	1440	WHJB	Greensburg, Pa.	620	WIRJ	Humbolt, Tenn.	740	WKAR	East Lansing, Mich.	870
WGES	Chicago, Ill.	1390	WHJK	Matawan, W.Va.	1350	WIRL	Palmer, Mass.	1290	WKAT	Miami Beach, Fla.	1360
WGET	Cattysburg, Pa.	1450	WHKK	Cleveland, Ohio	1420	WIRL	Peoria, Ill.	1290	WKAT	Glascow, Ky.	1490
WGEZ	Belleville, Mo.	1360	WHKK	Akron, Ohio	640	WIRO	Ironton, Ohio	1230	WKBC	Wm. Westboro, N.C.	610
WGFJ	Kalamazoo, Mich.	1360	WHKP	Hendersonville, N.C.	1450	WIRY	Plattsburg, N.Y.	1340	WKBB	La Crosse, Wis.	1410
WGFJ	Covington, Ga.	1430	WHKY	Hickory, N.C.	1290	WISC	Columbia, S.C.	560	WKBI	St. Mary's, Pa.	1400
WGA	Gainesville, Ga.	550	WHLD	Virgilia, Minn.	1400	WISC	Madison, Wis.	1480	WKBJ	Millan, Tenn.	1250
WGG	Gainesville, Fla.	1230	WHLE	North Falls, N.Y.	1270	WISE	Ashville, N.C.	1310	WKBL	Covington, Tenn.	1600
WGH	Marion, Ill.	1150	WHLF	South Boston, Va.	1400	WISH	Indianapolis, Ind.	1310	WKBN	Youngstown, Ohio	570
WGH	Newport News, Va.	1310	WHLL	Hempstead, N.Y.	1100	WISH	Indianapolis, Ind.	1310	WKBO	Harrisburg, Pa.	1230
WGHM	Skowegan, Maine	1150	WHLL	Wheeling, W.Va.	1600	WISN	Shamokin, Pa.	1480	WKBR	Hanchester, N.H.	1240
WGHN	Grand Haven, Mich.	1370	WHLM	Bloomsburg, Pa.	550	WISN	Milwaukee, Wis.	1150	WKBS	Wm. Westboro, N.C.	610
WGHG	Brunswick, Ga.	440	WHLM	Harlan, Ky.	1280	WISO	Ponce, P.R.	1260	WKBW	Buffalo, N.Y.	1520
WGIL	Galesburg, Ill.	1400	WHLP	Centerville, Tenn.	1570	WISP	Kinston, N.C.	1230	WKBS	Muskegon, Mich.	850
WGIR	Manchester, N.H.	610	WHLP	Port Huron, Mich.	1450	WISR	Butler, Pa.	680	WKCT	Bowling Green, Ky.	930
WGIV	Charlotte, N.C.	1600	WHMA	Annapolis, Md.	1350	WIST	Charlotte, N.C.	930	WKO	Nashville, Tenn.	1240
WGKA	Atlanta, Ga.	1600	WHMI	Howell, Mich.	1450	WITF	Baltimore, Md.	1140	WKO	Newbury, S.C.	1200
WGKY	Charleston, W.Va.	1300	WHMP	Northampton, Mass.	1400	WITF	Danville, Ill.	980	WKO	Clarksdale, Miss.	1600
WGL	Fort Wayne, Ind.	1420	WHNC	Henderson, N.C.	890	WITF	Jasper, Ind.	980	WKO	Lynch, N.C.	800
WGLC	Centerville, Miss.	1580	WHNY	McComb, Miss.	1250	WIV	Christiansd., V.I.	1230	WKE	Kewanee, Ill.	1450
WGM	Hollywood, Fla.	480	WHO	Des Moines, Iowa	1040	WIV	Charlottesville, Va.	1230	WKEU	Griffin, Ga.	1450
WGM	Washington, D.C.	570	WHO	San Juan, P.R.	1400	WIVK	Knoxville, Tenn.	860	WKEY	Covington, Va.	1340
WGN	Chicago, Ill.	720	WHOC	Philadelphia, Miss.	1480	WIVK	Vieques, P.R.	1370	WKEN	Knoxville, Tenn.	1340
WGN	Wilmingon, N.C.	1340	WHOK	Lancaster, Ohio	1320	WJ	Jacksonville, Fla.	1050	WKHM	Jackson, Mich.	970
WGN	Murfreesboro, Tenn.	1400	WHOL	Allentown, Pa.	1230	WJ	Springfield, Ohio	1340	WKIC	Hazard, Ky.	1430
WGN	Greenville, N.C.	1270	WHOM	New York, N.Y.	1480	WJ	St. Paul, Minn.	1250	WKIC	Lynch, N.C.	1580
WGLD	Goldboro, N.C.	1300	WHOO	Orlando, Fla.	990	WJ	St. Paul, Minn.	1250	WKIK	Leonardtown, Md.	1370
WGOV	Yaldosta, Ga.	950	WHOP	Hopkinsville, Ky.	1230	WJ	Norfolk, Nebr.	780	WKIN	Kingsport, Tenn.	1320
WGP	Bothlehem, Pa.	1100	WHOP	Decatur, Ala.	800	WJ	Jackson, Tenn.	1460	WKIP	Poughkeepsie, N.Y.	1450
WGPC	Albany, Ga.	1450	WHOT	Campbell, Ohio	1570	WJ	Marion, Ala.	1310	WKIT	Minneapolis, N.Y.	1520
WGR	Buffalo, N.Y.	550	WHOT	Clinton, Pa.	1520	WJ	Sparksburg, S.C.	1400	WKJ	Raleigh, N.C.	850
WGRA	Calro, Ga.	790	WHOT	Clinton, Pa.	1520	WJ	Providence, R.I.	920	WKJ	Mayaguez, P.R.	710
WGR	Louisville, Ky.	790	WHOT	Harrisburg, Pa.	380	WJ	Pittsburgh, Pa.	1320	WKJ	Fort Wayne, Ind.	1380
WGRD	Grand Rapids, Mich.	1440	WHOT	Harrisburg, Pa.	380	WJ	Lake Wales, Fla.	1280	WKO	Cocoa, Fla.	860
WGRF	Aquadella, P.R.	1430	WHPE	High Point, N.C.	1070	WIPR	Santure, P.R.	940	WKLA	Ludington, Mich.	1450
WGRM	Greenwood, Miss.	1240	WHRT	Hartselle, Ala.	860	WJ	Swainsboro, Ga.	800	WKLC	St. Albans, W.Va.	1300
WGRV	Greenville, Tenn.	1340	WHSC	Hartselle, S.C.	1450	WJ	Jacksonville, Fla.	930	WKLE	Washington, Ga.	1370
WGRY	Gary, Ind.	1370	WHSY	Hattiesburg, Miss.	1230	WJ	Mullins, S.C.	1260	WKLF	Cianton, Ala.	980
WGSA	Savannah, Ga.	1370	WHUB	lalladega, Ala.	1370	WJ	Albany, Ga.	1050	WKLK	Clouet, Minn.	1230
WGSC	Huntington, N.Y.	740	WHUN	Huntington, W.Va.	800	WJ	Haleyville, Ala.	1230	WKLM	Wilmingon, N.C.	980
WGSM	Atlanta, Ga.	920	WHUB	Cookeville, Tenn.	1400	WJ	Bloomington, Ill.	1270	WKLO	Lynch, N.C.	1060
WGSV	Guntersville, Ala.	920	WHUC	Hudson, N.Y.	1230	WJ	Bld Salem, Ill.	1350	WKLY	Blacksburg, Va.	1440
WGSW	Greenwood, S.C.	1350	WHUM	Reading, Pa.	1240	WJ	Detroit, Mich.	1500	WKLY	Blacksburg, Va.	1440
WGTA	Summerville, Ga.	950	WHUN	Huntington, Pa.	1150	WJ	Baton Rouge, La.	1150	WKLY	Hartwell, Ga.	980
WGTC	Greenville, N.C.	1350	WHVF	Wausau, Wis.	1290	WJ	DeLand, Fla.	1490	WKLY	Kalamazoo, Mich.	1470
WGTL	Kannapolis, N.C.	890	WHVH	Henderson, N.C.	1450	WJ	New Orleans, La.	1230	WKMF	Rointing Sprgs., Pa.	1370
WGTM	Wilson, N.C.	590	WHVR	Hanover, Pa.	1340	WJ	Sobring, Ind.	1390	WKMF	Flint, Mich.	1470
WGTR	Georgetown, S.C.	1400	WHWR	Rutland, Vt.	1000	WJ	Quincy, Mass.	1300	WKMG	Dearborn, Mich.	1310
WGTO	Hainesville, Fla.	1240	WHWL	Nanticoke, Pa.	730	WJ	Thomasville, Ala.	630	WKMG	Kumazoo, Mich.	1360
WGUY	Bangor, Maine	1230	WHXY	Bogalusa, La.	960	WJ	Jackson, Miss.	620	WKMG	Kings Mtn., N.C.	1240
WGVA	Geneva, N.Y.	1240	WHYL	Carlisle, Pa.	960	WJ	Grand Rapids, Mich.	1230	WKNA	Charleston, W.Va.	950
WGVN	Greenville, Miss.	1260	WHYN	Springfield, Mass.	560	WJ	Hagerstown, Md.	1240	WKNB	Brownmont, Conn.	840
WGC	Seima, Ala.	1340	WIAC	San Juan, P.R.	900	WJ	Gallipolis, Ohio	990	WKNE	Keene, N.H.	840
WGR	Ashesboro, N.C.	810	WIAM	Wilkesboro, N.C.	900	WJ	Fagerstown, Md.	1240	WKNE	Saginaw, Mich.	1210
WGR	Schenectady, N.Y.	1260	WIBA	Madison, Wis.	1310	WJ	Yadlow, Ga.	1150	WKNY	Kingston, N.Y.	1490
WGRV	Yorkville, Ala.	1380	WIBB	Macon, Ga.	1280	WJ	Dover, Ohio	1400	WKOA	Hopkinsville, Ky.	1480
WH	Madison, Wis.	970	WIBC	Indianapolis, Ind.	1070	WJ	Eric, Pa.	1500	WKOA	Pa.	1240
WHAB	Baxley, Ga.	1240	WIBG	Philadelphia, Pa.	990	WJ	Columbia, Tenn.	1280	WKOP	Binghamton, N.Y.	1560
WHAI	Greenfield, Mass.	920	WIBK	Knoxville, Tenn.	800	WJ	Talladega, Ala.	1580	WKOP	Wellston, Ohio	1570
WHAK	Rogers City, Mich.	1260	WIBM	Jackson, Mich.	1450	WJ	Johnson City, Tenn.	910	WKOW	Madison, Wis.	1070
WHAL	Shelbyville, Tenn.	1400	WIBR	Baton Rouge, La.	1300	WJ	Opelika, Ala.	1400	WKOX	Framingham, Mass.	1190
WHAM	Rochester, N.Y.	1180	WIBU	Buffalo, P.R.	740	WJ	Jacksonville, Fla.	1240	WKPY	Bluefield, W.Va.	1240
WHAN	Charleston, S.C.	1340	WIBU	Poynette, Wis.	1240	WJ	Tulahoma, Tenn.	740	WKQZ	Kosciusko, Miss.	1350
WHAP	Hopedale, Va.	1340	WIBV	Bellefonte, Ill.	1280	WJ	Lansing, Mich.	1320	WKRP	New Kensington, Pa.	1150
WHAR	Clarksburg, W.Va.	1340	WIBW	Topeka, Kans.	580	WJ	JV Savannah, Ga.	900	WKRP	Kingsport, Tenn.	1400
WHAS	Louisville, Ky.	840	WIBX	Utica, N.Y.	950	WJ	Chicago, Ill.	1160	WKRC	Cincinnati, Ohio	550
WHAT	Philadelphia, Pa.	1340	WICA	Ashtabula, Ohio	900	WJ	Niagara Falls, N.Y.	1440	WKRC	Mobile, Ala.	710
WHAV	Haverhill, Mass.	1480	WICC	Bridgport, Conn.	670	WJ	Leasburg, Tenn.	1490	WKRM	Columbia, Tenn.	1340
WHAW	Weston, W.Va.	1450	WICD	Providence, R.I.	1290	WJ	Springfield, Mass.	1600	WKRO	Cairo, Ill.	1400
WHAY	New Britain, Conn.	910	WICH	Norwich, Conn.	1310	WJ	Detroit, Mich.	1400	WKRS	Waukegan, Ill.	1220
WHBZ	Troy, N.Y.	1330	WICK	Seranton, Pa.	1400	WJ	Homer, N.Y.	710	WKRT	Corlanti, N.Y.	920
WHB	Kans City, Mo.	1480	WICO	Sallsburg, Md.	1420	WJ	Asbury Park, N.J.	1310	WKRT	Clay City, Mo.	800
WHBB	Selma, Ala.	1490	WICY	Malone, N.Y.	1390	WJ	Beckley, W.Va.	560	WKSB	Milford, Del.	930
WHBC	Canton, Ohio	1480	WIDE	Biddeford, Maine	1400	WJ	Orange, Va.	1340	WKSR	Pulaski, Tenn.	1420
WHBF	Rock Island, Ill.	1270	WIEL	Elizabethtown, Ky.	1400	WJ	Brookhaven, Miss.	1340	WKST	New Castle, Pa.	1280
WHBG	Harrisburg, Va.	1360	WIEK	Elkin, N.C.	1540	WJ	Rise Lake, Wis.	1240	WKTG	Thomasville, Ga.	730
WHBI	Newark, N.J.	1280	WIEP	Cambridge, Wis.	1490	WJ	Philadelphia, Pa.	1540	WKTL	Kendallville, Ind.	1570
WHBL	Sheboygan, Wis.	1390	WIEB	Sartore, Pa.	1420	WJ	Madison, Ohio	1490	WKTM	Mayfield, Ky.	1050
WHBO	Harrisburg, Pa.	1420	WIKB	Iron Ridge, Mich.	1490	WJ	New Orleans, La.	930	WKTY	Paris, Ky.	580
WHBT	Tampa, Fla.	1050	WIKC	Bogalusa, La.	1490	WJ	Ironwood, Mich.	690	WKTY	LaCrosse, Wis.	930
WHBQ	Memphis, Tenn.	920	WIKK	Eric, Pa.	1490	WJ	Athens, Ala.	730	WKUL	Cullman, Ala.	1340
WHBS	Huntsville, Ala.	1550	WIKY	Evansville, Ind.	820	WJ	Florence, S.C.	970	WKVA	Lewisstown, Pa.	920
WHBT	Harrisburg, Tenn.	1230	WIL	St. Louis, Mo.	1450	WJ	Jacksonville, N.C.	1240	WKVM	San Juan, P.R.	810
WHBU	Anderson, Ind.	1240	WILD	Birmingham, Ala.	830	WJ	N. Palm Beach, Fla.	1230	WKWF	Key West, Fla.	1600
WHBY	Appleton, Wis.	1230	WILC	Cambria, Ohio	1270	WJ	Hammond, Ind.	1230	WKWK	Wheeling, W.Va.	1400
WHCC	Waynesville, N.C.	1400	WILK	Wilkes-Barre, Pa.	980	WJ	Jamestown, N.Y.	1570	WKXL	Concord, N.H.	1450
WHCO	Sparta, Wis.	1230	WILM	Urbans, Ill.	980	WJ	Ward Ridge, Fla.	870	WKY	Swainsboro, N.C.	900
WHCU	Ithaca, N.Y.	870	WILM	Wilmington, Del.	1450	WJ	Florence, Ala.	1340	WKY	Sarasota, Fla.	930
WHDF	Houghton, Mich.	1400	WILF	Frankfort, Ind.	1570	WJ	Joliet, Ill.	1340	WKY	Oklahoma City, Okla.	930
WHOH	Boston, Mass.	850	WILS	Lansing, Mich.	1020	WJ	St. Cloud, Minn.	1240	WKY	Paducah, Ky.	570
WHDL	Olean, N.Y.	1450	WILP	Pittsburgh, Pa.	1380	WJ	Lake City, S.C.	1260	WKY	Keyser, W.Va.	1270
WHDM	McKenzie, Tenn.	1440	WILM	Lincoln, Mo.	1150	WJ	Burlington, Vt.	1230	WKYV	Louisville, Ky.	900
WHEB	Portsmouth, N.H.	750	WIMO	Wilder, Ga.	1420	WJ	Washington, Pa.	1240	WKZO	Kalamazoo, Mich.	590
WHEC	Rochester, N.Y.	1460	WIMS	Michigan City, Ind.	1420	WJ	Washington, Pa.	1240	WLAC	Nashville, Tenn.	1510
WHED	Washington, N.C.	1340	WINA	Charlottesville, Va.	1400	WJ	Herrin, Ill.	1440	WLAD	Daur, Conn.	800
WHEN	Syracuse, N.Y.	620	WINC	Winchester, Va.	1400	WJ	Green Bay, Wis.	1340	WLAF	LaFollette, Tenn.	1450
WHEE	Martinsville, Va.	1370	WIND	Chicago, Ill.	560	WJ	Greenville, Miss.	1330	WLAK	La Grange, Ga.	1240
			WING	Dayton, Ohio							

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.			
WLAP	Lexington, Ky.	630	WMFC	Mcgroeville, Ala.	1360	WNLA	Indianola, Miss.	1380	WPIC	Sharon, Pa.	790
WLAQ	Rome, Ga.	1410	WMFD	Wilmington, N.C.	630	WNLC	New London, Conn.	1490	WPID	Piedmont, Ala.	1280
WLAR	Athens, Tenn.	1450	WMFG	Hibbing, Minn.	1240	WNLK	Norwalk, Conn.	1240	WPJL	Alexandria, Va.	730
WLAT	Conway, S.C.	1330	WMFH	Daytona Beach, Fla.	1450	WNMP	Evanston, Ill.	1230	WPJN	St. Petersburg, Fla.	680
WLAU	Laurel, Miss.	1490	WMFR	High Point, N.C.	1230	WNM	Newark, N.J.	1260	WPJT	Pittsburgh, Pa.	730
WLAV	Grand Rapids, Mich.	1340	WMFS	Chattanooga, Tenn.	1440	WNNT	Warsaw, Va.	690	WPKE	Pikeville, Ky.	1240
WLAY	Muscle Shoals, Ala.	1450	WMGA	Mount Airy, Ga.	1250	WNOE	New Orleans, La.	1060	WPKO	Waverly, Ohio	1980
WLBA	Gainesville, Ga.	1450	WMGE	Pelican, Ga.	1250	WNOG	Naples, Fla.	1270	WPKY	Princeton, Ky.	1580
WLBB	Garrison, Ga.	1100	WMGM	New York, N.Y.	1050	WNOK	Columbia, S.C.	1230	WPLA	Plant City, Fla.	1470
WLBC	Muncie, Ind.	1340	WMGR	Balbridge, Ga.	930	WNOP	Newport, Ky.	740	WPLH	Huntington, W.Va.	1470
WLBE	Leesburg, Fla.	790	WMGW	Meadvale, Pa.	1400	WNOR	Norfolk, Va.	1230	WPLJ	Jackson, Tenn.	1490
WLBG	Laurens, S.C.	860	WMGY	Montgomery, Ala.	800	WNOS	High Point, N.C.	1590	WPLM	Plymouth, Mass.	1490
WLBH	Mattoon, Ill.	1170	WMIC	Monroe, Mich.	560	WNOW	York, Pa.	1250	WPLY	Plymouth, Wis.	1320
WLBJ	Bowling Green, Ky.	1410	WMID	Atlantic City, N.J.	1340	WNOX	Knoxville, Tenn.	990	WPME	Punxsutawney, Pa.	1580
WLBK	DeKalb, Ill.	1360	WMIE	Miami, Fla.	940	WNPT	Tuscaloosa, Ala.	1280	WPMP	Pascagoula, Miss.	1540
WLBL	Auburndale, Wis.	1590	WMIK	Widdowsoho, Ky.	560	WNRF	Woonsocket, R.I.	990	WPNF	Brevard, N.C.	1270
WLBN	Lebanon, Ky.	1380	WMIL	Millwaukee, Wis.	1290	WNRI	Woonsocket, R.I.	1360	WPON	Phenix City, Ala.	1270
WLBR	Lebanon, Pa.	1270	WMIN	Mpls.-St. Paul, Minn.	1400	WNRO	New Rochelle, N.Y.	1250	WPOT	Portland, Conn.	1410
WLBS	Birmingham, Ala.	900	WMIS	Natchez, Miss.	1240	WNRR	Grundy, Va.	990	PPOR	Portland, Maine	1490
WLBT	Bangor, Maine	620	WMIT	Iron Mountain, Mich.	1450	WNRS	Verona Beach, Fla.	1370	PPWA	Brooklyn, N.Y.	1330
WLCK	Campbellville, Ky.	1450	WMIX	Mt. Vernon, Ill.	940	WNVA	Norton, Va.	1350	PPWB	Pottsville, Pa.	1360
WLCO	Lancaster, S.C.	1380	WMJM	Cordoba, Ga.	1230	WNXX	New York, N.Y.	830	PPRA	Mayaguez, P.R.	990
WLCS	Baton Rouge, La.	990	WMJF	Pinville, Ky.	1230	WNXT	Portsmouth, Ohio	1260	PPRS	Lincoln, Ill.	1270
WLDB	Atlantic City, N.J.	910	WMJP	Millon, Pa.	1570	WOAI	San Antonio, Tex.	1200	PPRT	Prestonsburg, Ky.	630
WLDC	LaCross, Wis.	1490	WMJS	Sylvauga, Ala.	1290	WOAP	Owosso, Mich.	1080	PPRO	Providence, R.I.	910
WLDS	Jacksonville, Ill.	1180	WMLT	Dublin, Ga.	1330	WOAS	Oak Hills, W.Va.	860	PPRY	Paris, Ill.	1440
WLDT	Ladysmith, Wis.	1340	WMLV	Millville, N.J.	1440	WOBS	Jacksonville, Fla.	1360	PPRY	Perly, Fla.	1400
WLEA	Hornell, N.Y.	1480	WMMB	Melbourne, Fla.	1460	WOC	Davenport, Iowa	1420	WPTF	Raleigh, N.C.	680
WLEC	Sandusky, Ohio	1450	WMMH	Marshall, N.C.	920	WOCB	W. Yarmouth, Mass.	1240	WPTG	Albany, N.Y.	1540
WLEE	Richmond, Va.	1170	WMMN	Fairmont, W.Va.	920	WOCH	North Vernon, Ind.	1460	WPTT	Pittston, Pa.	1540
WLED	Pene, P.R.	1430	WMMW	Meriden, Conn.	1470	WOHI	E. Liverpool, Ohio	1590	WPTV	Piqua, Ohio	920
WLET	Toccoa, Ga.	1420	WMMX	Gretna, Va.	730	WOHO	Toledo, Ohio	1390	WPTX	Lexington, Pa.	1580
WLEU	Erie, Pa.	1340	WMNB	No. Adams, Mass.	1230	WOIS	Shelby, N.C.	730	PPVL	Painesville, Ohio	1460
WLEW	Bad Axe, Mich.	1300	WMNC	Morgantown, N.C.	1360	WOJ	Ames, Iowa	640	WQAM	Miami, Fla.	360
WLEX	Lexington, Ky.	1300	WMNE	Memorone, Wis.	1360	WOIC	Lexington, S.C.	1470	WQBS	Vicksburg, Miss.	1420
WLFA	Lafayette, Ga.	1230	WMNS	Olean, N.Y.	1490	WOK	Oak Ridge, Tenn.	1290	WQK	Jacksonville, Fla.	1280
WLFL	Little Falls, N.Y.	1590	WMOD	Marion, Ohio	1370	WOKK	Meridian, Miss.	1450	WQK	Greenville, S.C.	1440
WLFB	New York, N.Y.	1190	WMOG	Bruswick, Ga.	1490	WOKJ	Jackson, Miss.	1590	WQSN	Charleston, S.C.	1230
WLIC	Newport, Tenn.	1270	WMOH	Hamilton, Ohio	920	WOKO	Albany, N.Y.	1460	WQUA	Macon, Ga.	790
WLID	Lenoir, Tenn.	730	WMOI	Metropolis, Ill.	790	WOKW	Sturgeon Bay, Wis.	1280	WRI	Tiann, Pa.	790
WLIP	Kenosha, Wis.	1050	WMON	Montgomery, W.Va.	1490	WOKX	Milwaukee, Wis.	920	WQXR	New York, N.Y.	1560
WLIS	Old Saybrook, Conn.	920	WMOO	Millford, Mass.	900	WOKZ	Alton, Ill.	1570	WQXT	Palm Beach, Fla.	1340
WLIV	Livingston, Tenn.	920	WMOF	Ocala, Fla.	1330	WOL	Washington, D.C.	1450	WRAC	Racine, Wis.	1460
WLH	Lowell, Mass.	1280	WMOR	Hershey, Ky.	1200	WOLF	Syracuse, N.C.	1490	WRAD	Radford, Va.	1460
WLJ	Richmond, Va.	1320	WMOU	Berlin, Md.	1230	WOLS	Florence, S.C.	1230	WRAG	Carrollton, Pa.	1440
WLJM	Jackson, Ohio	1420	WMOX	Meridan, Miss.	1240	WOM	Owensboro, Ky.	1430	WRAN	Anne, Ill.	1400
WLNA	Peekskill, N.Y.	1420	WMOB	Mobile, Ala.	960	WOMT	Mansfield, Ohio	1240	WRAP	Newport, Pa.	1400
WLNH	Laconia, N.H.	1350	WMPC	Aberdeen, Miss.	1240	WONS	Wassantville, N.J.	1400	WRAL	Raleigh, N.C.	1240
WLOA	Bradock, Pa.	1550	WMP	Lapeer, Mich.	1230	WONE	Dayton, Ohio	920	WRAP	Norfolk, Va.	850
WLOB	Portland, Maine	1310	WMPA	Hancock, Mich.	1270	WONG	Onida, N.Y.	1600	WRAY	Reading, Pa.	1340
WLOE	Leaksville, N.C.	1490	WMPM	Smithfield, N.C.	680	WONN	Lakeland, Fla.	1230	WRAY	Princeton, Ind.	1250
WLOF	Oriando, Fla.	950	WMPB	Greenville, S.C.	1490	WONW	Defiance, Ohio	1280	WRBC	Jackson, Miss.	1300
WLOG	Logan, W.Va.	1230	WMPG	McGroeville, Ga.	1490	WOOF	Dothan, Ala.	860	WRBL	Columbus, Ga.	960
WLON	Princeton, W.Va.	1540	WMRF	Leiwistown, Pa.	1490	WOOG	Washington, D.C.	1340	WRCA	Altoona, N.Y.	660
WLOR	Memphis, Tenn.	1480	WMRI	Marion, Ind.	860	WOOD	Deland, Fla.	1410	WRCD	Dalton, Ga.	1430
WLON	Lincolnton, N.C.	1330	WMRN	Marion, Ohio	1280	WOOW	New Bern, N.C.	1490	WRCO	Rieland, Wis.	1430
WLOS	Ashville, N.C.	1380	WMRO	Aurora, Ill.	1570	WOPA	Oak Park, Ill.	1490	WRCS	Ashokle, N.C.	970
WLOU	Louisville, Ky.	1350	WMRY	New Orleans, La.	600	WOP	Bristol, Tenn.	1490	WRCV	Philadelphia, Pa.	1060
WLOV	Portsmouth, Va.	1400	WMSA	Massons, N.Y.	1340	WOR	New York, N.Y.	710	WRD	Reedsburg, Wis.	1450
WLOX	Biloxi, Miss.	1490	WMSC	Columbia, S.C.	1320	WORA	Mayaguez, P.R.	1750	WRD	Augusta, Maine	1400
WLPM	Suffolk, Va.	1450	WMSS	Deatler, Ala.	1460	WORD	Worcester, Mass.	1310	WRD	Augusta, Maine	1400
WLPO	LaSalle, Ill.	1220	WMSN	Raleigh, N.C.	570	WORD	Spartanburg, S.C.	910	WRD	Augusta, Ga.	1480
WLPR	New Albany, Ind.	1570	WMT	Cedar Rapids, Iowa	600	WORX	York, Pa.	1350	WRB	Holyoke, Mass.	930
WLS	Chicago, Ill.	890	WMTA	Cent. City, Ky.	1380	WORL	Boston, Mass.	950	WRB	Memphis, Tenn.	600
WLSB	Big Stone Gap, Va.	1220	WMTB	Vanleue, Ky.	730	WORM	Savannah, Tenn.	1010	WRE	Lexington, Va.	1450
WLSE	Wallace, N.C.	1400	WMTB	Manistee, Mich.	1340	WORX	Madison, Ind.	1270	WREN	Topoka, Kans.	1250
WLSH	Lansford, Pa.	1410	WMTM	Moultrie, Ga.	1300	WORZ	Orlando, Fla.	1250	WREY	Reidsville, N.C.	1220
WLSP	Pikesville, Pa.	900	WMTT	Morrilton, N.J.	860	WOSC	Fulton, N.Y.	1300	WRX	Gluth, Minn.	980
WLSM	Louisville, Miss.	1270	WMTS	Murfreesboro, Tenn.	610	WOSH	Oshkosh, Wis.	1490	WRFC	Athens, Ga.	1060
WLSV	Wellsville, N.Y.	790	WMUR	Manchester, N.H.	1090	WOSH	Columbus, Ohio	820	WRFD	Worthington, Ohio	880
WLTC	Gastonia, N.C.	1370	WMUS	Union, Mich.	1090	WOTR	Corry, Pa.	1370	WRFS	Alexander City, Ala.	1050
WLTR	Bloomsburg, Pa.	690	WMVA	Greenville, S.C.	1260	WOTR	Nashua, N.H.	1500	WRFW	Eau Claire, Wis.	1050
WLVA	Lynchburg, Va.	950	WMVA	Martinsville, Va.	1450	WOW	New York, N.Y.	1280	WRGA	Rome, Ga.	1470
WLW	Cincinnati, Ohio	1050	WMVG	Milledgeville, Ga.	1450	WOW	New York, N.Y.	1280	WRGS	Roxbury, Tenn.	1370
WLWC	Wilmington, Pa.	700	WMVO	Mt. Vernon, Ohio	1300	OWL	Florida, Ala.	590	WRH	Jacksonville, Fla.	1340
WLWY	Lynn, Mass.	1380	WMYR	Myrtle Beach, S.C.	1450	OWF	Wayne, Ind.	1190	WRH	Rock Hill, S.C.	1400
WLXB	Munising, Mich.	1400	WMYB	Fl. Myers, Fla.	1450	WOXF	Oxford, N.C.	1340	WRH	Cagus, P.R.	1450
WLXF	Madison, Fla.	1230	WNAB	Bartlett, Conn.	1410	WOZ	Ozark, Ala.	900	WRIB	Providence, R.I.	1230
WMAA	Forest, Miss.	860	WNAC	Lawrence, Mass.	680	WPAK	Ponce, P.R.	1380	WRIC	Richlands, Va.	340
WMAJ	State College, Pa.	1450	WNAD	Norman, Okla.	640	WPAC	Patchogue, N.Y.	1450	WRIO	Rio Piedras, P.R.	1410
WMAK	Nashville, Tenn.	630	WNAE	Warren, Pa.	1310	WPAD	Patterson, N.Y.	1450	WRIS	Rosnoke, Va.	1340
WMAL	Washington, D.C.	630	WNAF	Gretnada, Miss.	1400	WPAG	Ann Arbor, Mich.	1050	WRIV	Riverhead, N.Y.	1390
WMAN	Marinette, Wis.	570	WNAH	Nashville, Tenn.	1280	WPAL	Charleston, S.C.	730	WRJN	Racine, Wis.	1400
WMAN	Manfield, Ohio	1400	WNAM	Neenah, Wis.	1110	WPAM	Pottsville, Pa.	1450	WRJW	Ploayne, Miss.	1320
WMAP	Menroe, N.C.	1060	WNAR	Norristown, Pa.	1450	WPAP	Mount Airy, N.C.	740	WRKD	Rockland, Maine	1450
WMAQ	Chicago, Ill.	670	WNAS	Norfolk, Mass.	1470	WPAR	Parkersburg, W.Va.	930	WRKE	Rockland, Va.	380
WMAA	Springfield, Mass.	1450	WNAU	New Albany, Miss.	1430	WPAT	Patterson, N.J.	1450	WRKH	Rockport, Tenn.	1490
WMAX	Grand Rapids, Mich.	1480	WNAW	Annapolis, Md.	860	WPAY	Port Jervis, N.Y.	550	WRMA	Montgomery, Ala.	950
WMAZ	Macon, Ga.	970	WNAW	North Adams, Mass.	860	WPAY	Portsmouth, Ohio	1400	WRM	Elgin, Ill.	1410
WMB	Macon, Miss.	1400	WNAW	Yankton, S.Dak.	1290	WPAY	Pottstown, Pa.	1370	WRNL	Richmond, Va.	910
WMBD	Peoria, Ill.	1470	WNBH	Binghamton, N.Y.	1340	WPBB	Jackson, Ala.	1290	WRNO	Orangeburg, S.C.	1150
WMBG	Richmond, Va.	1380	WNBW	New Bedford, Mass.	1470	WPBC	Minneapolis, Minn.	980	WRNY	Rochester, N.Y.	920
WMBH	Joplin, Mo.	1450	WNBW	Newburyport, Mass.	1470	WPCC	Panama City, Fla.	1590	WRB	West Point, Miss.	1400
WMBI	Chicago, Ill.	1110	WNBW	Newburyport, Mass.	1470	WPCC	Putnam, Conn.	1350	WRB	Rockledge, Fla.	1340
WMBJ	Atlantic City, N.C.	740	WNBW	Saranac Lake, N.Y.	1240	WPCC	Putnam, Conn.	1350	WRK	Rockford, Ill.	1400
WMBM	Miami Beach, Fla.	800	WNCA	Siler City, N.C.	1370	WPDM	Potsdam, N.Y.	1470	WRM	Rome, Ga.	710
WMBN	Potoski, Mich.	1340	WNCC	Barnesboro, Pa.	1150	WPDM	Jacksonville, Fla.	600	WRM	Ronecerverte, W.Va.	1400
WMBO	Auburn, N.Y.	1340	WNDB	Bedford, Pa.	1260	WPDR	Portage, Wis.	1350	WRSS	Scottsboro, Ala.	1330
WMBR	Jacksonville, Fla.	1460	WNDS	Syracuse, N.Y.	1498	WPDX	Clarksburg, W.Va.	750	WRV	Rosnoke, Va.	1240
WMBU	Uniontown, Pa.	730	WNEB	Worcester, Mass.	1230	WPEL	Montrose, Pa.	1250	WRW	Albany, N.Y.	580
WMC	Memphis, Tenn.	590	WNEG	Taccoa, Ga.	1320	WPH	Philadelphia, Pa.	950	WRX	Rockledge, Miss.	1450
WMC	New York, N.Y.	570	WNER	Live Oak, Fla.	1250	WPH	Perth, N.Y.	1800	WRY	Carmi, Ill.	1460
WMC	Welch, W.Va.	1340	WNER	Central City, Ky.	1130	WPET	Taunton, Mass.	1570	WRP	Warner Robbins, Ga.	1350
WMC	Church Hill, Tenn.	1260	WNEW	New York, N.Y.	1400	WPET	Grensboro, N.C.	950	WR	Dallas, Tex.	1310
WMC	McKeesport, Pa.	1600	WNEK	New York, N.Y.	1400	WPFA	Pensacola, Fla.	910	WR	Washington, N.C.	930
WMC	Hoylehurst, Miss.	1220	WNGO	Mayfield, Ky.	1320	WPFB	Middletown, Ohio	790	WR	Rockford, Ill.	1390
WMD	Fajardo, P.R.	1490	WNHC	New Haven, Conn.	1340	WPFD	Darlington, S.C.	1350	WR	Clinton, N.C.	880
WMD	Midway, Mich.	1490	WNIA	Cheektowaga, N.Y.	1230	WPFF	Park Falls, Wis.	1450	WR	Warsaw, Ind.	1480
WME	Eau Gallie, Fla.	920	WNIL	Niles, Mich.	1290	WPGC	Bradbury Hgts., Md.	1580	WRTA	Altoona, Pa.	1240
WME	Marion, Va.	1010	WNIX	Springfield, Va.	1480	WPGW	Portland, Ind.	1440			
WME	Boston, Mass.	1510	WNJR	Newark, N.J.	1430	WPHE	Phillipsburg, Pa.	1250			
			WNKY	Neon, Ky.	1450	WPB	Prairie du Chen, Wis.	980			

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
WRUF	Gainesville, Fla.	850	WSPC	Anniston, Ala.	1390	WTMV	E. St. Louis, Ill.	1490	WVMC	Mt. Carmel, Ill.	1360
WRUM	Rumford, Maine	790	WSPD	Toledo, Ohio	1310	WTNC	Thomasville, N.C.	790	WVMI	Biloxi, Miss.	570
WRUN	Utica, N.Y.	1150	WSPR	Saratoga Sprngs., N.Y.	900	WTND	Orangeburg, S.C.	920	WVNA	Tusculum, Ala.	1590
WRVA	Russellville, Ky.	800	WSPR	Springfield, Mass.	1270	WTNJ	Trenton, N.J.	1300	WVNW	Newark, N.J.	620
WRVK	Nt. Vernon, Ky.	1140	WSSC	Durham, N.C.	1410	WTNS	Coshocton, Ohio	1450	WVOK	Birmingham, Ala.	690
WRWB	Kistimes, Fla.	1460	WSSC	Cleveland Hgts., Ohio	1400	WTNT	Tallahassee, Fla.	1560	WVOP	Durham, N.C.	620
WRWX	Selma, Ala.	1220	WSSR	Hillsboro, Ohio	1590	WTOB	Winston-Salem, N.C.	1380	WVOS	Liberty, N.C.	970
WRXO	Roxboro, N.C.	1570	WSSS	Durham, N.C.	1490	WTOC	Savannah, Ga.	1290	WVOT	Wilson, N.C.	1420
WRYO	Rochester, Pa.	1050	WSSG	Summit, S.C.	1340	WTOE	Toledo, Ohio	1560	WVPO	Logan, W.Va.	1290
WSAC	Radcliff, Ky.	1470	WSSO	Starkville, Miss.	1290	WTOI	Toledo, Ohio	1240	WVWV	Grafton, W.Va.	1260
WSAI	Cincinnati, Ohio	1360	WSSP	Petersburg, Va.	1248	WTON	Staunton, Va.	1500	WVWB	Dearborn, Mich.	1350
WSAJ	Grove City, Pa.	1340	WSTA	Charlotte Amalie, Virgin islands	1340	WTOP	Washington, D.C.	1470	WVWC	Stroudsburg, Pa.	840
WSAL	Lagonsport, Ind.	1230	WSTC	Stamford, Conn.	1400	WTOR	Torrington, Conn.	1490	WVWD	Somerset, Pa.	900
WSAM	Saginaw, Mich.	1400	WSTK	Woodstock, Va.	1230	WTRP	Towson, Md.	1570	WVWF	Warrenton, Ore.	1260
WSAN	Allentown, Pa.	1350	WSTL	Emeline, Ky.	1600	WTRR	Paris, Tenn.	1470	WVWG	Waco, Tex.	1260
WSAP	Portsmouth, Va.	1350	WSTM	St. Augustine, Fla.	1420	WTRT	New Orleans, La.	940	WVWH	Washington, D.C.	1260
WSAR	Fall River, Mass.	1480	WSTN	Salisbury, N.C.	1280	WTRU	Lafayette, La.	1340	WVWI	New Orleans, La.	690
WSAT	nr. Salisbury, N.C.	1280	WSTR	Sturgis, Mich.	1420	WTRV	Ripley, Tenn.	1480	WVWJ	Sanford, N.C.	1050
WSAU	Wausau, Wis.	1400	WTSU	Suart, Fla.	1450	WTRW	Clarksville, Tenn.	1370	WVWK	Titusville, Fla.	1340
WSAV	Savannah, Ga.	630	WSTV	Steubenville, Ohio	1340	WTRX	Bradenton, Fla.	1490	WVWL	Fort Lauderdale, Fla.	1320
WSAZ	Huntington, N.Y.	1370	WSTW	Oxford, Miss.	1420	WTRN	Tyrons, Pa.	1290	WVWN	Baltimore, Md.	1400
WSAZ	Huntington, W.Va.	930	WSUI	Iowa City, Iowa	910	WTRD	Dyersburg, Tenn.	1330	WVWO	Wilmington, N.C.	970
WSB	Atlanta, Ga.	910	WSUJ	St. Petersburg, Fla.	620	WTRP	LaGrange, Ga.	620	WVWP	Baltimore, Md.	1400
WSBA	York, Pa.	910	WSUK	Sarasota, Fla.	1280	WTRR	Sanford, Fla.	1440	WVWQ	Wichita, Kan.	950
WSBB	New Smyrna Beach, Fla.	1230	WSVA	Harrisonburg, Va.	800	WTRM	Muskegon, Mich.	1600	WVWR	Detroit, Mich.	970
WSBC	Chicago, Ill.	1240	WSVN	Bella Glade, Fla.	900	WTRW	Two Rivers, Wis.	1290	WVWS	Winchester, Ky.	1380
WSBS	Gt. Barrington, Mass.	860	WSWV	Platteville, Wis.	1590	WTRY	Troy, N.Y.	980	WVWX	New Orleans, La.	670
WSBT	South Bend, Ind.	960	WSYB	Rutland, Vt.	1380	WTSB	Brattleboro, Vt.	1450	WVWY	Fayetteville, N.C.	970
WSCR	Scranton, Pa.	1590	WSYI	St. Albans, N.C.	1900	WTSV	Lumberton, N.C.	1340	WVWN	Rochester, N.H.	1270
WSDC	Marine City, Mich.	1240	WSX	Sarasota, Fla.	1280	WTSX	Clarendon, N.H.	1230	WVWR	Beckley, W.Va.	620
WSDR	Sterling, Ill.	1240	WSVA	Harrisonburg, Va.	800	WTTA	Port Huron, Mich.	1380	WVWS	Staunton, Va.	1260
WSEV	Selma, Tenn.	930	WSVW	Greve, Va.	800	WTTB	Madisonville, Ky.	1310	WVWT	Wilmington, N.C.	970
WSEB	Quintana, Ga.	1490	WSWV	Boila Glade, Fla.	900	WTTM	Trenton, N.J.	920	WVWU	Waco, Tex.	1260
WSEC	Somersel, Ky.	1240	WSYB	Rutland, Vt.	1380	WTTN	Waterbury, Wis.	1580	WVWX	Manitowish, Wis.	980
WSEF	Thomasboro, Ga.	1310	WTAQ	Worcester, Mass.	580	WTTV	Westminster, Md.	1370	WVWY	Woodstock, Va.	1590
WSGA	Ephrata, Pa.	1220	WTAL	Tallahassee, Fla.	1270	WTTW	Port Huron, Mich.	1380	WVWZ	Charlotte, N.C.	1120
WSGC	Elberton, Ga.	1400	WTAM	Decatur, Ga.	970	WTTX	Madisonville, Ky.	1310	WVWA	Buffalo, N.Y.	1120
WSGN	Birmingham, Ala.	610	WTAN	Cambridge, Fla.	1340	WTTX	Trenton, N.J.	920	WVWB	Woonsocket, R.I.	1240
WSGW	Saginaw, Mich.	790	WTAR	Cambridge, Mass.	740	WTTX	Waterbury, Wis.	1580	WVWC	Williamsport, Pa.	1340
WSHC	Sheboygan, Wis.	950	WTAW	Norfolk, Va.	790	WTTT	Bloomington, Md.	1470	WVWD	Patuxent, R.I.	1450
WSHS	Statesville, N.C.	1400	WTAX	College Sta., Tex.	1150	WTTU	Coral Gables, Fla.	1490	WVWE	Frankfort, Ky.	1600
WSID	Baltimore, Md.	780	WTAX	Springfield, Ill.	1240	WTTU	Union City, Tenn.	1580	WVWF	St. Albans, N.Y.	1420
WSIG	Mount Vernon, Va.	1490	WTBY	Robinson, Ill.	1570	WTTU	Tupelo, Miss.	1380	WVWG	Waco, Tex.	1260
WSIP	Paintsville, Ky.	1490	WTB	Tuskegee, Ala.	1230	WTTU	Tuskegee, Ala.	580	WVWH	Waco, Tex.	1260
WSIR	Winter Haven, Fla.	1490	WTB	Troy, Ala.	1450	WTTU	Wilmington, Del.	1290	WVWI	Pittsburgh, Pa.	970
WSIV	Pekin, Ill.	1140	WTBO	Cumberland, Md.	990	WTTU	Waterbury, Wis.	1580	WVWJ	Tampa, Fla.	1300
WSIX	Nashville, Tenn.	980	WTBC	Florence, Ala.	990	WTTU	Coldwater, Mich.	610	WVWK	Wheeling, W.Va.	1170
WSJM	St. Joseph, Mich.	1400	WTCD	Campbellsville, Ky.	1450	WTTU	Waterbury, Wis.	1580	WVWL	Waco, Tex.	1260
WSJS	Winston-Salem, N.C.	600	WTCH	Shawano, Wis.	960	WTTU	Columbia, Ohio	1240	WVWM	Waco, Tex.	1260
WSKB	Miami, Fla.	1450	WTCL	Tell City, Ind.	1230	WTTU	Waco, Tex.	1260	WVWN	Waco, Tex.	1260
WSKI	Montpelier-Barre, Vt.	1240	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWO	Waco, Tex.	1260
WSKN	Saugerties, N.C.	920	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWP	Waco, Tex.	1260
WSKY	Ashville, N.Y.	1280	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWQ	Waco, Tex.	1260
WSLB	Dyersburg, N.Y.	1400	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWR	Waco, Tex.	1260
WSLI	Jackson, Miss.	830	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWS	Waco, Tex.	1260
WSLM	Salem, Ind.	1220	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWT	Waco, Tex.	1260
WSLS	Roads, N.C.	650	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWX	Waco, Tex.	1260
WSM	Nashville, Tenn.	810	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWY	Waco, Tex.	1260
WSMB	New Orleans, La.	1350	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWZ	Waco, Tex.	1260
WSMI	Litchfield, Ill.	1540	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWA	Waco, Tex.	1260
WSMT	Sparta, Tenn.	1050	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWB	Waco, Tex.	1260
WSNJ	nr. Bridgeton, N.J.	1240	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWC	Waco, Tex.	1260
WSNT	Sandersville, Ga.	1190	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWD	Waco, Tex.	1260
WSNU	Sandy, Wash., S.C.	1430	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWE	Waco, Tex.	1260
WSNY	Schenectady, N.Y.	1240	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWF	Waco, Tex.	1260
WSOC	Charlotte, N.C.	1240	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWG	Waco, Tex.	1260
WSOK	Nashville, Tenn.	1470	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWH	Waco, Tex.	1260
WSQN	Henderson, Ky.	860	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWI	Waco, Tex.	1260
WSOY	St. Ste. Marie, Mich.	1230	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWJ	Waco, Tex.	1260
WSOY	Decatur, Ill.	1340	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWK	Waco, Tex.	1260
WSPA	Spartanburg, S.C.	950	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWL	Waco, Tex.	1260
WSPB	Sarasota, Fla.	1450	WTCT	Traverse City, Mich.	1480	WTTU	Waco, Tex.	1260	WVWN	Waco, Tex.	1260
			WTM	Milwaukee, Wis.	620	WTLN	Diney, Ill.	740	WZVX	Cowan, Tenn.	1440

## Canadian

Amplitude-Modulation (AM) Broadcasting Stations Listed Alphabetically by Call Letters  
 C.L., call letters; Kc., frequency in kilocycles (for watt power of station, see list arranged by frequency, p. 169)

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
CBA	Sackville, N.B.	1070	CFCL	Timmins, Ont.	580	CHAB	Moose Jaw, Sask.	800	CJAV	Port Alberni, B.C.	1240
CBF	Moncton, N.B.	1300	CFCA	Calgary, Alta.	1060	CHAD	Amos, Que.	1340	CJBC	Toronto, Ont.	860
CBE	Windsor, Ont.	1550	CFCH	Chatham, Ont.	630	CHAE	Medicine Hat, Alta.	1270	CJBD	Beauville, Ont.	800
CBF	Montreal, Que.	690	CFCC	Camrose, Alta.	1230	CHAF	Edmonton, Alta.	1080	CJBR	Brimouski, Que.	900
CBG	Gander, Nfld.	1450	CFCD	Charlottetown, P.E.I.	1300	CHAG	Grandy, Que.	1430	CJCS	Edmonton, Alta.	830
CBH	Halifax, N.S.	1330	CFCE	Victoria, B.C.	1380	CHAE	Peterborough, Ont.	1430	CJCB	Sydney, N.S.	1270
CBU	Sydney, N.S.	1140	CFCF	Victoria, B.C.	1380	CHAF	Edmonton, Alta.	1480	CJCH	Halifax, N.S.	1270
CBF	Chicoutimi, Que.	1580	CFCG	Gravelbourg, Sask.	1230	CHAG	St. Anne de la Pocatiere, Que.	1350	CJCS	Stratford, Ont.	1240
CBK	Regina, Sask.	840	CFCH	St. Joseph d'Alma, Que.	1270	CHLN	Three Rivers, Que.	550	CJOC	Oawson Creek, B.C.	1350
CBL	Toronto, Ont.	740	CFCH	Brampton, Ont.	1080	CHLO	St. Thomas, Ont.	680	CJEM	Edmundston, N.B.	570
CBM	Montreal, Que.	940	CFCH	Kamloops, B.C.	1090	CHLP	Montreal, Que.	1410	CJFT	Smiths Falls, Ont.	1070
CBN	St. John's, Nfld.	640	CFCH	Brookville, Ont.	1450	CHLT	Sherbrooke, Que.	900	CJFX	Riviere du Loup, Que.	1400
CBQ	Ottawa, Ont.	910	CFCH	Saskatoon, Sask.	1170	CHML	Hamilton, Ont.	900	CJGW	Yorkton, Sask.	940
CBT	Grand Falls, Nfld.	890	CFCH	Fredericton, N.B.	550	CHNC	New Carlisle, Ont.	610	CJJB	Vernon, B.C.	940
CBU	Vancouver, B.C.	690	CFCH	Saskatoon, Sask.	1170	CHNO	Sudbury, Ont.	900	CJJC	Sault Ste. Marie, Ont.	1490
CBV	Quebec, Que.	880	CFCH	Fredericton, N.B.	550	CHNS	Halifax, N.S.	960	CJJK	Kirkland Lake, Ont.	560
CBW	Winnipeg, Man.	990	CFCH	Fredericton, N.B.	550	CHOD	Barnia, Ont.	1070	CJLS	Yarmouth, N.S.	1340
CBX	Edmonton, Alta.	1010	CFCH	Fredericton, N.B.	550	CHOE	Edmonton, Alta.	1350	CJMS	Montreal, Que.	1280
CBXA	Edmonton, Alta.	740	CFCH	Fredericton, N.B.	550	CHOF	Sherbrooke, Que.	1350	CJNB	N. Battleford, Sask.	1450
CBY	Corner Brook, Nfld.	790	CFCH	Fredericton, N.B.	550	CHOC	Quebec, Que.	1340	CJNB	N. Battleford, Sask.	1450
CBZ	Windsor, N.S.	1450	CFCH	Fredericton, N.B.	550	CHOD	Edmonton, Alta.	1350	CJOC	Winnipeg, Man.	1340
CFAC	Calgary, Alta.	960	CFCH	Fredericton, N.B.	550	CHOR	Drummondville, Que.	1340	CJOC	Lethbridge, Alta.	1220
CFAM	Altona, Man.	1290	CFCH	Fredericton, N.B.	550	CHRS	St. Jean, Que.	1090	CJON	St. John's, Nfld.	930
CFAR	Flin Flon, Man.	590	CFCH	Fredericton, N.B.	550	CHSJ	Saint John, N.B.	1570	CJOR	Vancouver, B.C.	800
CFBC	Saint John, N.B.	930	CFCH	Fredericton, N.B.	550	CHUB	Moncton, B.C.	1050	CJQY	Guelph, Ont.	1450

C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.	C.L.	Location	Kc.
CJSP	Leamington, Ont.	710	CKEY	Toronto, Ont.	580	CKOK	Pentliston, B.C.	800	CKSM	Shawinigan Falls, Quebee	1220
CJVI	Victoria, B.C.	900	CKFH	Toronto, Ont.	1400	CKOM	Saskatoon, Sask.	1420	CKSO	Sudbury, Ont.	790
CKAC	Montreal, Que.	730	CKGB	Timmins, Ont.	680	CKOT	Thillsonburg, Ont.	1810	CKSW	Swift Current, Sask.	1400
CKBB	Barrie, Ont.	1230	CKGR	Galt, Ont.	1110	CKOY	Kelowna, B.C.	830	CKTB	St. Catharines, Ont.	620
CKBC	Bathurst, N.B.	1400	CKIL	St. Jerome, Que.	900	CKOX	Woodstock, Ont.	1340	CKTR	Three Rivers, Que.	1350
CKCI	Prince Albert, Sask.	900	CKLB	Oshawa, Ont.	1350	CKOY	Ottawa, Ont.	1310	CKTS	Sherrbrooke, Que.	1240
CKBL	Matane, Que.	1250	CKLC	Kingston, Ont.	1380	CKPC	Brantford, Ont.	1380	CKTA	Edmonton, Alta.	580
CKBM	Montmagny, Que.	1490	CKLD	Theftord Mines, Que.	1230	CKPG	Prinee George, B.C.	550	CKVD	Val d'Or, Que.	1230
CKBW	Bridgewater, N.S.	1000	CKLG	N. Vancouver, B.C.	1070	CKPR	Fort William, Ont.	580	CKVM	Ville Marie, Que.	950
CKCH	Hull, Que.	970	CKLN	Nelson, B.C.	1240	CKRB	Ville St. Georges, Que.	1490	CKWV	Kingston, Ont.	980
CKCK	Regina, Sask.	620	CKLS	LaSarre, Que.	1240	CKRC	Winnipeg, Man.	630	CKWX	Vancouver, B.C.	980
CKCL	Truro, N.S.	680	CKLW	Windsor, Ont.	800	CKRD	Red Deer, Alta.	980	CKX	Brandon, Man.	1150
CKCR	Kitchener, Ont.	1490	CKLY	Lindsay, Ont.	910	CKRM	Regina, Sask.	1400	CKXL	Calgary, Alta.	1140
CKCV	Quebec, Que.	1280	CKMR	Newcastle, N.B.	790	CKRN	Rouyn, Que.	590	CKY	Winnipeg, Man.	580
CKCW	Moncton, N.B.	1220	CKMX	Gorse Crown, Nfld.	600	CKRS	Jonquiere, Que.	1150	CKYL	Pease River, Alta.	630
CKCY	Sault Ste. Marie, Ont.	1400	CKNB	Campbellton, N.B.	950	CKSA	Lloydminster, Alta.	1250	VGAR	St. John's, Nfld.	1230
CKDA	Victoria, B.C.	1280	CKNW	New Westminster, British Columbia	1320	CKSB	St. Boniface, Man.	1230	VOCM	St. John's, Nfld.	590
CKDM	Dauphin, Man.	1050	CKNX	Wingham, Ont.	920	CKSF	Cornwall, Ont.	1290	VQWR	St. John's, Nfld.	800
CKEC	New Glasgow, N.S.	1230	CKOC	Hamilton, Ont.	1150	CKSL	London, Ont.	1290			
CKEN	Kentville, N.S.	1350									

## United States and Canadian

Amplitude-Modulation (AM) Broadcasting Stations Grouped by Frequency; U.S. stations listed alphabetically by location within groups, Canadian stations precede U.S.

Abbreviations: Kc., frequency in kilocycles; W.P., watt power—Wave length is given in meters (all AM stations broadcasting at a higher frequency than 1600 Kc. are listed under Short-Wave Stations, see p. 184 and p. 186)

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
<b>540—555.5</b>			WSYR	Syracuse, N.Y.	5000	WPDQ	Jacksonville, Fla.	5000	WSAV	Savannah, Ga.	5000
CBK	Regina, Sask.	5000	WWNC	Ashville, N.C.	5000	WMT	Cedar Rapids, Iowa	5000	KIDO	Boise, Idaho	5000
KFMB	San Diego, Calif.	5000	WMSN	Raleigh, N.C.	5000	WST	Caribou, Maine	1000	WLAF	Lexington, Ky.	5000
WGTO	Orlando, Fla.	10000	WKBN	Youngstown, Ohio	5000	WCAD	Baltimore, Md.	5000	KTIB	Thibodaux, La.	500
KEOK	Ft. Dodge, Iowa	1000	WNAX	Yankton, S.Dak.	5000	WTAC	Flint, Mich.	1000	WJMS	Ironwood, Mich.	1000
WDVM	Pocomoke City, Md.	5000	WFAA	Dallas, Tex.	5000	KGEZ	KallsPELL, Mont.	1000	KKOK	St. Louis, Mo.	5000
WDXN	Clarksville, Tenn.	250	WBPAP	Ft. Worth, Tex.	5000	WMRY	New Orleans, La.	1000	KOH	Reno, Nev.	500
WRIC	Richlands, Va.	1000	KVLB	Salt Lake City, Utah	5000	WSJS	Winston-Salem, N.C.	5000	KLEA	Lexington, N.Mex.	500
			KVII	Seattle, Wash.	5000	KSJB	Jamestown, N.D.	5000	WIRC	Hickory, N.C.	500
			WMAM	Marinette, Wis.	250	CFRM	Camden, Pa.	1000	WMFD	Wilmington, N.C.	1000
						WAEI	Mayaguez, P.R.	1000	KOOS	Coos Bay, Oreg.	1000
<b>550—545.1</b>			<b>580—516.9</b>			WREC	Memphis, Tenn.	5000	WEIL	Seranton, Pa.	500
CFNB	Fredericton, N.B.	5000	CFCL	Timmins, Ont.	1000	KROD	El Paso, Tex.	1000	WPRO	Providence, R.I.	5000
CHLN	Three Rivers, Que.	5000	CJFX	Antigonish, N.S.	5000	KERB	Kermitt, Tex.	1000	KGFF	Pierre, S.Dak.	5000
CKPG	Pr. George, B.C.	250	CKFY	Toronto, Ont.	5000	KTBB	Tyler, Tex.	1000	KPOA	Honolulu, T.H.	5000
KENI	Anchorage, Alaska	5000	CKPR	Ft. William, Ont.	1000				KNAC	San Antonio, Tex.	5000
KOY	Phoenix, Ariz.	1000	CKUA	Edmonton, Alta.	1000				KGDN	Edmonds, Wash.	1000
KAFY	Bakersfield, Calif.	1000	CKUJ	Winnipeg, Man.	1000	<b>610—491.5</b>					
KRAI	Craig, Colo.	1000	CKY	Winnipeg, Man.	1000	CHNC	New Carlisle, Que.	5000	<b>640—468.5</b>		
WGGA	Gainesville, Ga.	5000	WBUS	Tuskegee, Ala.	500	CJAT	Trail, B.C.	1000	CBN	St. John's, N.F.	10000
WHYN	Springfield, Mass.	1000	KABI	Ketchikan, Alaska	1000	WGSN	Birmingham, Ala.	1000	KFI	Los Angeles, Calif.	50000
WCOB	Columbus, Miss.	1000	KMAJ	Tucson, Ariz.	5000	KFRS	San Francisco, Calif.	5000	WOI	Ames, Iowa	5000
KOPR	Butte, Mont.	5000	KMJJ	Fresno, Calif.	5000	WCKR	Miami, Fla.	2000	WHKK	Akron, Ohio	5000
KFRM	Kansas City, Mo.	5000	WDBO	Orlando, Fla.	5000	WFRM	Hawkinsville, Ga.	500	KNAD	Norman, Okla.	1000
KSD	St. Louis, Mo.	5000	WGAA	Waco, Tex.	1000	KESE	Iowa Falls, Iowa	250			
WGR	Buffalo, N.Y.	5000	WFDN	Nampa, Idaho	5000	KDAL	Duluth, Minn.	5000			
KFYR	Bismarck, N.Dak.	5000	WILL	Urubans, Ill.	5000	WDAF	Kansas City, Mo.	5000	<b>650—461.3</b>		
WKRC	Cincinnati, Ohio	5000	KSAC	Manhattan, Kans.	5000	KOJM	Havre, Mont.	1000	WSM	Nashville, Tenn.	50000
KOAC	Corvallis, Oreg.	5000	WIBW	Topeka, Kans.	5000	WGIR	Manchester, N.M.	5000	KRCT	Baytown, Pa.	250
WHLM	Bloomsburg, Pa.	500	KALB	Alexandria, La.	5000	KGGM	Albuquerque, N.Mex.	5000			
WPAB	Ponce, P.R.	5000	WTAG	Worcester, Mass.	5000	WAYS	Charlotte, N.C.	5000	<b>660—454.3</b>		
WPAP	Pawket, R.I.	1000	WTEL	Tupelo, Miss.	5000	WTVN	Columbus, Ohio	5000	KFAR	Fairbanks, Alaska	10000
KMWI	Waukegan, Ill.	1000	WELB	Elmira, N.Y.	5000	WIP	Philadelphia, Pa.	5000	KOWH	Omaha, Nebr.	500
KCRS	Midland, Tex.	5000	WIAQ	San Juan, P.R.	5000	KILT	Houston, Tex.	1000	WRCA	New York, N.Y.	50000
KTSA	San Antonio, Tex.	5000	WIAQ	San Juan, P.R.	5000	KNVU	Logan, Utah	5000	WESC	Greenville, S.C.	5000
WDEV	Waterbury, Vt.	1000	WRKH	Rockwood, Tenn.	500	WBSL	Roanoke, Va.	5000	SKSY	Dallas, Tex.	1000
WSVA	Harrisburg, Va.	1000	KDAV	Lubbock, Tex.	500	KEPR	Kennebec, Wash.	5000			
WOSA	Wausau, Wis.	5000	WCHS	Charleston, W.Va.	5000						
			WKTY	LaCrosse, Wis.	1000	<b>620—483.6</b>					
<b>560—535.4</b>			<b>590—508.2</b>			CKCK	Regina, Sask.	5000	<b>670—447.5</b>		
CFRA	Ottawa, Ont.	1000	CFAR	FlinFlon, Man.	1000	CKTC	St. Katharine, Ont.	1000	WMAQ	Chicago, Ill.	50000
CJKL	Kirkland Lake, Ont.	5000	CKRS	Jonquiere, Que.	5000	KTAR	Phoenix, Ariz.	5000			
WOOF	Dothan, Ala.	5000	COCM	St. Johns, N.F.	1000	KNGS	Hanford, Calif.	1000	<b>680—440.9</b>		
KYUM	Yuma, Ariz.	1000	WRAG	Carrollton, Ala.	1000	WSUN	St. Petersburg, Fla.	5000	CHFA	Edmonton, Alta.	5000
KSFQ	San Fran., Calif.	5000	KFKM	San Bernardino, Cal.	5000	WTRP	LaGrande, Ga.	1000	CHLO	St. Thomas, Ont.	1000
KWFO	Denver, Colo.	5000	WDLF	Panama City, Fla.	1000	KWAL	Wallace, Idaho	1000	CKGB	Timmins, Ont.	5000
WQAM	Miami, Fla.	5000	WAGA	Atlanta, Ga.	5000	KCOM	Sioux City, Iowa	1000	KNBC	San Fran., Calif.	50000
WIND	Chicago, Ill.	5000	KGMB	Honolulu, Hawaii	5000	KMNS	Sioux City, Iowa	1000	WPIN	St. Petersburg, Fla.	1000
WMIK	Middlesboro, Ky.	500	KIDL	Idaho Falls, Idaho	5000	WLBZ	Bangor, Maine	5000	WCTT	Corbin, Ky.	1000
WGAN	Portland, Maine	5000	WELX	Lexington, Ky.	5000	WBJX	Jackson, Miss.	5000	WCBM	Baltimore, Md.	10000
WHYN	Springfield, Mass.	1000	WELX	Lexington, Ky.	5000	WRCB	Jackson, Miss.	5000	WLAN	Lawrence, Mass.	5000
WMIC	Monrois, Mich.	5000	WKZO	Kalamazoo, Mich.	5000	WVNI	Newark, N.J.	5000	WDBC	Escanaba, Mich.	5000
WEOB	Duluth, Minn.	5000	WVOM	Omaha, Nebr.	5000	KGW	Portland, Oreg.	5000	WIFR	Binghamton, N.Y.	1000
KWTO	Springfield, Mo.	5000	WRWB	Albany, N.Y.	5000	WHJB	Greensburg, Pa.	1000	WRNY	Rochester, N.Y.	250
KMON	Great Falls, Mont.	5000	WGTW	Wilson, N.C.	5000	WKAG	San Juan, P.R.	5000	WPTF	Raleigh, N.C.	50000
WGAI	Elizabeth City, N.C.	1000	KUGN	Eugene, Oreg.	5000	WATE	Winston-Salem, N.C.	5000	WISR	Butler, Pa.	250
WFIL	Philadelphia, Pa.	5000	WARM	Seranton, Pa.	5000	WCAX	Burlington, Vt.	5000	WAPA	San Juan, P.Rleo.	10000
WIS	Columbia, S.C.	5000	WABS	Boston, Mass.	10000	WNRN	Beckley, W.Va.	1000	WMPS	Memphis, Tenn.	10000
WHBB	Memphis, Tenn.	5000	KTBC	Austin, Tex.	1000	WTMJ	Milwaukee, Wis.	5000	KENS	San Antonio, Tex.	50000
KFDM	Beaumont, Tex.	5000	KTBB	Tyler, Tex.	1000				KOMW	Omaha, Wash.	1000
KPQ	Wenatchee, Wash.	5000	KSUB	Cedar City, Utah	1000	<b>630—475.9</b>					
WJLS	Beckley, W.Va.	5000	WLVA	Lynchburg, Va.	1000	CFCD	Chatham, Ont.	1000	<b>690—434.5</b>		
			KHQ	Spokane, Wash.	5000	CFNY	Charlottetown, P.E.I.	5000	CBU	Vancouver, B.C.	10000
<b>570—526.0</b>			<b>600—499.7</b>			CKRC	Winnipeg, Man.	5000	CBF	Montreal, Que.	50000
CJEM	Edmonton, N.B.	1000	CFCF	Montreal, Que.	5000	CKDY	Kelowna, B.C.	800	CKNA	Flintastaf, Ariz.	1000
WCAS	Gadsden, Ala.	1000	CFCH	North Bay, Dnt.	1000	CKYL	Pease River, Alta.	1000	WYDK	Birmingham, Ala.	50000
CKNO	Alturas, Calif.	1000	CFCC	Saskatoon, Sask.	5000	WAYU	Albertville, Ala.	1000	KEVT	Tucson, Ariz.	250
KLAC	Los Angeles, Calif.	5000	CJDR	Vancouver, B.C.	5000	WDB	Thomasville, Ala.	1000	KBBA	Benton, Ark.	250
WGMS	Washington, D.C.	5000	CKCL	Truro, N.S.	1000	KND	Idaho Falls, Idaho	1000	WADS	Ansonia, Conn.	500
WACL	Waycross, Ga.	1000	CKCS	Truro, N.S.	1000	KVMA	Magnolia, Ark.	1000			
WKYB	Paducah, Ky.	1000	CKCS	Truro, N.S.	1000	KIDD	Monterey, Calif.	1000			
WYMI	Biloxi, Miss.	1000	CKCS	Truro, N.S.	1000	KVOD	Denver, Colo.	5000			
KGRT	Los Cruces, N.Mex.	1000	WICC	Bridgeport, Conn.	500	WMAL	Washington, D.C.	5000			
WMCA	New York, N.Y.	5000									

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
(690-434.5)			<b>770—389.4</b>			<b>840—356.9</b>			WAND	Canton, Ohio	500
KGFF Coffeyville, Kans.	10000		KUDM Minneapolis, Minn.	5000	WKAB Mobile, Ala.	1000		WFRO	Fremont, Ohio	500	
WWEZ New Orleans, La.	5000		WGL Northfield, Minn.	5000	WKNB Bownmont, Conn.	1000		KLAD	Klamath Falls, Oreg.	1000	
KSTL St. Louis, Mo.	1000		KEW St. Louis, Mo.	1000	WHAS Louisville, Ky.	50000		WCPA	Clearfield, Pa.	1000	
KRCO Grinnville, Dreg.	1000		KOB Albuquerque, N. Mex.	5000	WFPD Stroudsburg, Pa.	250		WKXY	Knoxville, Tenn.	1000	
WLTR Bloomsburg, Pa.	1000		WABC New York, N.Y.	5000				WCDR	Lebanon, Tenn.	250	
KUDS Vermillion, S.Dak.	1000		WJZ New York, N.Y.	5000				KALT	Atlanta, Tex.	41000	
KULA Honolulu, T.H.	10000		KXA Seattle, Wash.	1000	<b>850—352.7</b>			KOLW	Hamilton, Tex.	250	
KHEY El Paso, Tex.	1000				CKVL Verdun, Que.	10000		KFLD	Floydada, Tex.	250	
KPET Lamesa, Tex.	250		<b>780—384.4</b>		CKRD Red Deer, Alta.	10000		KMCO	Conroe, Tex.	500	
WCBY Bristol, Va.	10000		WBBC Chicago, Ill.	50000	WILD Birmingham, Ala.	10000		WATK	Antigo, Wis.	250	
WNNW Warsaw, Va.	250		WJAG Norfolk, Neb.	1000	KDA Denver, Colo.	50000					
WELD Fisher, W.Va.	500		WCKB Dunn, N.C.	1000	WRUF Gainesville, Fla.	5000		<b>910—329.5</b>			
<b>700—428.3</b>			WBD Forest City, N.C.	1000	WROT W. Palm Beach, Fla.	1000		CKLY	Lindsay, Ont.	1000	
WLW Cincinnati, Ohio	50000		KSPI Stillwater, Okla.	250	KILA Hilo, Hawaii	1000		CBTO	Ontario, Ont.	5000	
			WARR Arlington, Va.	1000	WHDH Boston, Mass.	50000		CFJC	Kamloops, B.C.	1000	
<b>710—422.3</b>			<b>790—379.5</b>		WKBZ Muskegon, Mich.	5000		CHRL	Reberval, Que.	1000	
CJSP Leamington, Ont.	250		CBY Corner Brook, N.F.	1000	KFUD St. Louis, Mo.	5000		KLCN	Blytheville, Ark.	5000	
CFRG Gravelbourg, Sask.	5000		CBRM Newcastle, N.B.	1000	WKIX Raleigh, N.C.	10000		KAMD	Camden, Ark.	1000	
CKVM Ville Marie, Que.	1000		CKSO Sudbury, Ont.	5000	WJW Cleveland, Ohio	5000		KOAB	Orlando, Calif.	1000	
WKRK Mobile, Ala.	1000		KOS Texarkana, Ark.	1000	WYAT W. Palm Beach, Fla.	1000		KPHO	Phoenix, Ariz.	5000	
KMPC Los Angeles, Calif.	50000		KDAN Eureka, Calif.	1000	WABA Aguadilla, P.R.	1000		KBAB	El Centro, Calif.	1000	
KMYR Denver, Colo.	5000		KABC Los Angeles, Calif.	5000	WRAP Norfolk, Va.	1000		KLX	Oakland, Calif.	5000	
WGBS Miami, Fla.	50000		WLBE Leesburg, Fla.	1000	KTAC Tacoma, Wash.	1000		KPOF	Nr. Denver, Colo.	1000	
WROM Roma, Ga.	1000		WPFA Pensacola, Fla.	1000				WHAY	New Britain, Conn.	5000	
KTBS Shreveport, La.	10000		WXI Atlanta, Ga.	5000	<b>860—348.6</b>			WPLA	Plant City, Fla.	1000	
WHB Kansas City, Mo.	10000		WGRA Cairo, Ga.	1000	CJBC Toronto, Ont.	50000		WGAF	Valdosta, Ga.	5000	
WOR New York, N.Y.	50000		KXXX Colby, Kans.	5000	WHRT Hartsville, Ala.	250		WSUI	Iowa City, Iowa	5000	
DZRH Manila, P.I.	10000		WGRG Louisville, Ky.	5000	WAMI Opp, Ala.	1000		WLCB	Baton Rouge, La.	1000	
WKJB Mayaguez, P.Rico	1000		WRUM Rumford, Me.	1000	KIFN Phoenix, Ariz.	5000		WABI	Boston, Maine	1000	
WTPR Paris, Tenn.	250		WWSG Saginaw, Mich.	1000	KOSE Osceola, Ark.	1000		WDFD	Flint, Mich.	1000	
KGNC Amarillo, Tex.	10000		KGHL Billings, Mont.	5000	WRFW Warren, Ark.	250		WCOC	Meridian, Miss.	1000	
KURV Edinburg, Tex.	250		WNNY Watertown, N.Y.	5000	KTRB Modesto, Calif.	10000		KOYN	Billings, Mont.	1000	
KIRO Seattle, Wash.	50000		WLSV Wellsville, N.Y.	500	WKPD Cocoa, Fla.	1000		KBIM	Roswell, N.Mex.	5000	
WDSM Superior, Wis.	10000		WTNC Thomasville, N.C.	1000	WERD Atlanta, Ga.	10000		WLAS	Jacksonville, N.C.	1000	
KFCB Cheyenne, Wyo.	10000		KFNO Fargo, N.D.	5000	WDMG Douglas, Ga.	5000		WPPF	Wadsworth, Ohio	1000	
			KWIL Albany, Oreg.	1000	WKPC Muscatine, Iowa	250		KGCL	Miami, Okla.	1000	
<b>720—416.4</b>			WAEB Allentown, Pa.	1000	WMRI Marion, Ind.	250		WAVL	Apollon, Pa.	1000	
WGN Chicago, Ill.	50000		WPIC Sharon, Pa.	1000	KOAM Pittsburg, Kans.	10000		WGBI	Seranton, Pa.	1000	
			WEAN Providence, R.I.	5000	WSDN Henderson, Ky.	500		WSPA	York, Pa.	1000	
<b>730—410.7</b>			WETB Johnson City, Tenn.	1000	WAYE Waukegan, Ill.	500		WPRP	Ponca, P.R.	5000	
CKAC Montreal, Que.	10000		WHMC Memphis, Tenn.	5000	SBSB St. Bangington, Mass.	500		WRBK	Spartanburg, S.C.	1000	
KFGQ Anchorage, Alaska	10000		KTHC Houston, Tex.	5000	WNAW N. Adams, Mass.	250		WJHL	Joliet, Tenn.	1000	
WJMW Athens, Ala.	1000		KFFO Lubbock, Tex.	5000	KNUJ New Uim, Minn.	1000		WEPG	S. Pittsburg, Tenn.	500	
KNBY Newport, Ark.	1000		WSIG Mount Jackson, Va.	1000	WMAG Forest, Miss.	500		KRIO	McAllen, Tex.	1000	
WKTG Thomasville, Ga.	1000		WTAR Norfolk, Va.	5000	WFMQ Fairmont, N.C.	1000		KRRV	Sherman, Tex.	1000	
KWGB Goodland, Kans.	1000		KVOS Bellingham, Wash.	1000	WAMD Homestead, Pa.	250		WRNL	Richmond, Va.	5000	
WFNW Madisonville, Ky.	1000		KNEW Spokane, Wash.	5000	WTEL Philadelphia, Pa.	250		KALL	Salt Lake City, Utah	1000	
WMTG Vanelev, Ky.	1000		WMON Montgomery, W.Va.	5000	WLBG Laurans, S.C.	250		WRKE	Reno, Va.	1000	
KTRY Bastrop, La.	250		WEAU Washington, Wis.	5000	WIVK Knoxville, Tenn.	1000		KXRN	Renton, Wash.	1000	
WARB Covington, La.	250		<b>800—374.8</b>		WMTS Murfreesboro, Tenn.	250		KVAN	Vancover, Wash.	1000	
WACE Chicopee, Mass.	1000		CHAB Moose Jaw, Sask.	5000	KFTN Ft. Stockton, Tex.	250		WGOR	Sturgeon Bay, Wis.	500	
KWRE Warrenton, Mo.	1000		CKOK Pasleton, B.C.	1000	KSPA Nacogdoches, Tex.	1000					
KWOA Worthington, Minn.	1000		CFBF Ft. Frances, Ont.	1000	KSNF San Antonio, Tex.	5000		<b>920—325.9</b>			
WFMG Goldsboro, N.C.	1000		CHRC Quebec, Que.	5000	KWHQ Salt Lake City, Utah	1000		CJCH	Halifax, N.S.	5000	
WDHS Shelby, N.C.	1000		CJAD Montreal, Que.	10000	WEVA Emporia, Va.	1000		CKNX	Wingham, Ont.	1000	
WTLG Bowling Green, Ohio	250		CKLW Windsor, Ont.	5000	WOYA Oak Hill, W.Va.	10000		WCTA	Adulusia, Ala.	5000	
KBOY Medford, Oreg.	1000		VOWR St. Johns, N.F.	1000	WFOX Milwaukee, Wis.	250		WWRW	Russellville, Ala.	1000	
WHWL Nanticoke, Pa.	1000		WHOS Decatur, Ala.	1000	<b>870—344.6</b>			KARK	Little Rock, Ark.	5000	
WPIT Pittsburgh, Pa.	1000		WMGY Montgomery, Ala.	1000	KIJE Glendade, Calif.	250		KIUR	Durango, Colo.	5000	
WPAL Charleston, S.C.	1000		KINY Juneau, Alaska	5000	KAIM Kalmuki, Hawaii	1000		KREX	Gr. June., Colo.	5000	
WDLR Lenoir, Tenn.	1000		KYOM Morrilton, Ark.	250	WNL New Orleans, La.	50000		WMEG	Engle, Colo.	500	
KBCS Grand Prairie, Tex.	500		KHIL Ft. Lupton, Colo.	500	WKAR E. Lansing, Mich.	5000		WSKN	Saugerties, N.Y.	1000	
KKOG Ogden, Utah	1000		WLAD Danbury, Conn.	250	WVCU Ithaca, N.Y.	1000		KVEC	San Luis Obispo, Cal.	500	
WPIK Alexandria, Va.	1000		WMBM Miami Beach, Fla.	1000	WGTL Kannapolis, N.C.	1000		KLMR	Lamar, Colo.	1000	
WMNA Gretna, Va.	1000		WJAT Swainsboro, Ga.	1000	KCNC Ft. Worth, Tex.	250		WAGU	Atlanta, Ga.	1000	
KULE Ephrata, Wash.	1000		KDBM Dillon, Mont.	1000	WFO Farmville, Va.	1000		KAHU	Walpahu, Hawaii	1000	
			KXIC Iowa City, Iowa	1000	<b>880—340.7</b>			WMOK	Metropolis, Ill.	1000	
<b>740—405.2</b>			WRUS Russellville, Ky.	1000	WCBS New York, N.Y.	50000		WBAA	W. Lafayette, Ind.	1000	
CBXA Edmonton, Alta.	250		WBOK New Orleans, La.	1000	WRRZ Clinton, N.C.	1000		KFB	Shelby, Iowa	500	
CBL Toronto, Ont.	50000		WCCM Lawrence, Mass.	1000	WRFD Worthington, Ohio	5000		WTCW	Whitesburg, Ky.	1000	
WBAM Montgomery, Ala.	50000		KREI Farmington, Mo.	1000				WHXY	Bogalusa, La.	1000	
KBIG Avallon, Calif.	10000		WKDN Camden, N.J.	1000	<b>890—336.9</b>			WPTX	Lexington Pk., Md.	500	
KCBS San Francisco, Calif.	10000		KTOW Okla. City, Okla.	250	WLS Chicago, Ill.	50000		WMLP	Hancock, Mich.	1000	
KWBV Colo. Sprs., Colo.	250		KPOD Portland, Oreg.	1000	WHNC Henderson, N.C.	1000		KDHL	Fairbault, Minn.	1000	
KVFC Cortez, Colo.	1000		WCHA Chambersburg, Pa.	1000	KBYE Okla. City, Okla.	1000		KWAD	Wadena, Minn.	1000	
KYME Boise, Idaho	500		DZPI Manila, P.I.	10000				KJSK	Columbus, Nebr.	1000	
WORZ Orlando, Fla.	5000		WOSC Dillon, S.C.	1000	<b>900—333.1</b>			KWAM	Farmington, W.Va.	5000	
WNOP Newport, Ky.	1000		WEAB Greer, S.C.	250	CHLT Sherbrooke, Que.	1000		KOLE	Reno, Nev.	1000	
WLN Olney, Ill.	250		WIBK Knoxville, Tenn.	1000	CHML Hamilton, Ont.	5000		KQUE	Albuquerque, N.Mex.	1000	
KBDE Oskaloosa, Iowa	250		WDEH Sweetwater, Tenn.	500	CHND Sudbury, Ont.	5000		WTTM	Trenton, N.J.	1000	
KPBM Cambridge, Mass.	250		KODO Gumas, Tex.	250	CJRB Rimouski, Que.	10000		WKRT	Cortland, N.Y.	1000	
WGSN Huntington, N.Y.	1000		KBUH Brigham City Utah	250	CKJL St. Jerome, Que.	1000		WBBS	Burlington, N.C.	5000	
WMBL Morehead City, N.C.	1000		WSVS Crews, Va.	1000	CJVI Victoria, B.C.	5000		KGIL	Lebanon, Oreg.	1000	
WPAQ Mount Airy, N.C.	10000		WHTN Huntington, W.Va.	1000	CKBI Prince Albert, Sask.	10000		WKVY	W. Ky.	1000	
KRMG Tulsa, Okla.	50000		WDUX Waupaca, Wis.	1000	CKJX Yorkton, Sask.	10000		WPRV	Providence, N.I.	5000	
WVGH Chester, Pa.	10000		<b>810—370.2</b>		WLSB Birmingham, Ala.	1000		WTND	Orangeburg, S.C.	1000	
WBAW Barnwell, S.C.	250		KGO San Francisco, Calif.	50000	WZKZ Stark, Ala.	1000		WLIV	Livingston, Tenn.	1000	
WIRJ Humbolt, Tenn.	250		WIPA Annapolis, Md.	250	KFRB Fairbanks, Alaska	10000		KELP	El Paso, Tex.	1000	
WJG Tullahoma, Tenn.	250		KWMA Kansas City, Mo.	50000	KBIF Canterville, Calif.	1000		KECK	Odesa, Tex.	1000	
KTRH Houston, Tex.	50000		WGY Schenectady, N.Y.	50000	KSJV Sanger, Calif.	1000		KT LW	St. Louis City, Tex.	1000	
			WKBC N.Wilkesboro, N.C.	1000	WJWL Georgetown, Del.	10000		KXLY	Spokane, Wash.	5000	
<b>750—399.8</b>			WCEC Rocky Mount, N.C.	1000	WSWN Belle Glade, Fla.	1000		WOKY	Milwaukee, Wis.	5000	
WSB Atlanta, Ga.	50000		WEDO Waco, Tex.	1000	WMOA Ocala, Fla.	1000					
WBMD Baltimore, Md.	1000		WKVM San Juan, P.R.	25000	WCPA Calhoun, Ga.	1000		<b>930—322.4</b>			
KMNJ Grand Island, Neb.	1000		KIKI Honolulu, Hawaii	1000	WYLV Savannah, Ga.	1000		CFBC	Saint John, N.B.	5000	
KSEO Durant, Okla.	250		<b>820—365.6</b>		WYLV Savannah, Ky.	1000		CJON	Edmonton, Alta.	5000	
KXL Portland, Oreg.	10000		WAIT Chicago, Ill.	5000	WLSI Pikesville, Ky.	1000		WETO	Gadsden, Ala.	1000	
WHEB Portsmouth, N.H.	1000		WCBD Chicago, Ill.	5000	KREH Oakdale, La.	250		KTKN	Ketchikan, Alaska	1000	
WPDJ Clarksburg, W.Va.	1000		WKY Evansville, Ind.	250	WCMR Brunswick, Maine	500		KHJ	Los Angeles, Calif.	5000	
			WOSU Columbus, Ohio	5000	WATC Gaylord, Mich.	1000		WMLF	Milford, Del.	500	
<b>760—394.5</b>			WFAA Dallas, Tex.	50000	KTIS Minneapolis, Minn.	1000		WJAX	Jacksonville, Fla.	5000	
KGU Honolulu, Hawaii	2500		WBAP Ft. Worth, Tex.	50000	KFAL Fulton, Mo.	1000		WKXY	Sarasota, Fla.	1000	
WJR Detroit, Mich.	50000		<b>830—361.2</b>		KDOT Des Moines, Miss.	1000		WGRJ	Bainbridge, Ga.	5000	
WCPS Tarboro, N.C.	1000		KIKI Honolulu, Hawaii	250	WOTW Nashua, N.H.	1000		KSEI	Parkersburg, W.Va.	5000	
			WCCO Minneapolis, Minn.	50000	WSPN Saratoga Sprogs., N.Y.	250		WADQ	Quincy, Ill.	5000	
			KBOA Kennett, Mo.	1000	WBRV Boonville, N.Y.	500		WKCT	Bowling Green, Ky.	1000	
			WNYC New York, N.Y.	1000	WAYN Rockingham, N.C.	1000		WFMJ	Frederick, Md.	1000	
					WIAM Williamston, N.C.	1000		WREB	Holyoke, Mass.	500	
					KFNW Fargo, N.Dak.	1000		WBCK	Battle Creek, Mich.	1000	
								WBSL	Jackson, Miss.	5000	

</



Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
(1150-260.7)			WFAX Falls Church, Va.	500	KDIX Dickinson, N.Dak.	250	WCEM Cambridge, Md.	250	WCEM Cambridge, Md.	250	
KIYL Shelby, Mont.	1000		KBAM Longview, Wash.	1000	WCPO Cincinnati, Ohio	250	WJEZ Hagerstown, Md.	250	WJAI Greenfield, Mass.	250	
KDEF Albuquerque, N.Mex.	1000		<b>1230-243.8</b>		WCOL Columbus, Ohio	250	WCOB W. Yarmouth, Mass.	250	WATT Cadillac, Mich.	250	
WRUN Utica, N.Y.	5000		CFCW Camrose, Alta.	250	WTRD Tronton, Ohio	250	WCBY Cheboygan, Mich.	250	WJPD Ishpeming, Mich.	250	
WFNS Burlington, N.C.	1000		CFGR Gravelbourg, Sask.	250	WTRD Toledo, Ohio	250	WJIM Lansing, Mich.	250	WFMF Hibbing, Minn.	250	
WGBR Goldsboro, N.C.	5000		CFBQ Belleville, Ont.	250	KADA N. of Ada, Okla.	250	WJON St. Cloud, Minn.	250	WMPA Aberdeen, Miss.	250	
WCUE Akron, Ohio	1000		CFPA Port Arthur, Ont.	250	KVAS Astoria, Oreg.	250	WGRM Greenwood, Miss.	250	WGRM Greenwood, Miss.	250	
WIMA Lima, Ohio	1000		CKLD Theford Mines, Que.	250	KGRO Gresham, Oreg.	100	WMOX Gulfport, Miss.	250	WMOX Gulfport, Miss.	250	
WMAE McAlester, Okla.	1000		YOAR St. John's, Nfld.	100	KYJC Medford, Oreg.	250	WMIS Natchez, Miss.	250	KFMO Flat River, Mo.	250	
KFJI Klamath Falls, Oreg.	1000		CKSF Cornwall, Ont.	250	KQK Beaver, Oreg.	250	KNEM Nevada, Mo.	250	KBMY Billings, Mont.	250	
WHUN Huntington, Pa.	1000		CKVD Val D'Or, Que.	100	WADJ Alhambra, Pa.	250	KLTX Glasgow, Mont.	250	KXLI Hono, Mont.	250	
WKPA New Kensington, Pa.	250		WAUP Auburn, Ala.	250	WBVP Lakeview, Pa.	250	KFOR Lincoln, Neb.	250	KODY North Platte, Nebr.	250	
WORA Mayaguez, P.R.	5000		WJBB Hialeah, Fla.	250	WEEX Easton, Pa.	250	KELK Elko, Nev.	250	WKBR Manchester, N.H.	250	
WTRC Rock Hill, S.C.	1000		WBHP Huntsville, Ala.	250	WKBO Harrisburg, Pa.	250	WNSJ Bridgeton, N.J.	250	KAVE Carlsbad, N.Mex.	250	
WSNW Orangeburg, S.C.	500		WHTB Talldega, Ala.	250	WCRO Johnstown, Pa.	250	KCLO Clovis, N.Mex.	250	KVCB Clovis, N.Mex.	250	
South Carolina	1000		WTBC Tuscaloosa, Ala.	250	WPZJ Lock Haven, Pa.	250	WGBB Freeport, N.Mex.	250	WGBA Geneva, N.Y.	250	
WAPD Chattanooga, Tenn.	1000		KFJW Sitka, Alaska	250	WERI Westerly, R.I.	250	WJTN Jamestown, N.Y.	250	WJON Liberty, N.Y.	250	
WTAW College Station, Tex.	1000		KFNU Bisbee, Ariz.	250	WAND Anderson, S.C.	250	WVOS Saranac Lake, N.Y.	250	WNBZ Schenectady, N.Y.	250	
KCTC Corpus Christi, Tex.	1000		KAAA Kingman, Ariz.	1000	WNOK Columbia, S.C.	250	WATN Watertown, N.Y.	250	WPNF Brevard, N.C.	250	
KIBC Midland, Tex.	1000		KRBI Wichita, Ariz.	250	WISD Florence, S.C.	250	WSPC Charlotte, N.C.	250	WCNC Elizabeth City, N.C.	250	
KOLJ Quanah, Tex.	500		KCON Conway, Ark.	250	KSLD Sioux Falls, S.Dak.	250	WJNC Jacksonville, N.C.	250	WRAL Raleigh, N.C.	250	
KRSC Seattle, Wash.	5000		KKFW Ft. Smith, Ark.	250	WHBT Harriman, Tenn.	250	WRAL Raleigh, N.C.	250	WBLI Devils Lake, N.Dak.	250	
WELC Wichita, W.Va.	1000		KBTM Jonesboro, Ark.	250	WMMT McMinnville, Tenn.	250	WVOT Vicksburg, Miss.	250	WHIZ Zanesville, Ohio	250	
KOFE Pullman, Wash.	5000		KGEE Bakersfield, Calif.	250	KSIX Corpus Christi, Tex.	250	KASA Elk City, Okla.	250	KVSO Ardmore, Okla.	250	
KAYO Seattle, Wash.	5000		KWTC Barstow, Calif.	250	KDLK Del Rio, Tex.	250	KBEL Idabel, Okla.	250	KASB Elk City, Okla.	250	
KHFS Vancouver, Wash.	1000		KIBS Bishop, Calif.	250	KERV Houston, Tex.	250	KHBB Okmulgee, Okla.	250	KFLX Corvallis, Oreg.	1000	
WCHF Chippewa Falls, Wis.	5000		KDCE Ely, Nev.	250	KLVV Lewistown, Pa.	250	KWPC Portland, Oreg.	250	KTIL Timonium, Md.	250	
WISN Milwaukee, Wis.	5000		KDGF Los Angeles, Calif.	5000	KOSF Nacogdoches, Tex.	250	KJUN Redmond, Oreg.	250	KSGA Redmond, Oreg.	250	
<b>1160-258.5</b>			KSJR Jacksonville, Fla.	5000	KOSA Odessa, Tex.	250	KRXL Roseburg, Oreg.	250	WRTA Altoona, Pa.	250	
WJJD Chicago, Ill.	5000		KPRL Paso Robles, Calif.	250	KPAT Pampa, Tex.	250	WHUM Reading, Pa.	250	CJAV Port Alberni, B.C.	250	
KSL Salt Lake City, Utah	5000		KRGG Redding, Calif.	250	KSEY Seymour, Tex.	250	WBAJ Wilkes-Barre, Pa.	250	CJCS Stratford, Ont.	250	
<b>1170-256.3</b>			KWV Stockton, Calif.	250	KSST Sulphur, La.	250	WVON Woonsocket, R.I.	250	CJRW Summerside, P.E.I.	250	
CFNS Saskatoon, Sask.	1000		KXED Leadville, Colo.	250	KWTX Waco, Tex.	250	WKDK Newberry, S.C.	250	CKLN Nelson, B.C.	250	
WCOV Montgomery, Ala.	1000		KDZA Pueblo, Colo.	250	KMUR Murray, Utah	250	WBEJ Elizabethton, Tenn.	250	CKLS LaSarre, Que.	250	
KCBQ San Diego, Calif.	5000		KGEK Sterling, Colo.	250	KOAL Price, Utah	250	WKEK Fayetteville, Tenn.	250	CKSS Sherbrooke, Que.	250	
KLOK San Jose, Calif.	5000		WGGG Gainesville, Fla.	250	WJOY Burlington, Vt.	250	WBIR Knoxville, Tenn.	250	WULA Waukegan, Ill.	250	
WLBH Mattoon, Ill.	250		WONN Lakeland, Fla.	250	WBEI Abingdon, Va.	250	WKDA Nashville, Tenn.	250	WOWL Florence, Ala.	250	
KSTT Davenport, Iowa	1000		WMAF Madison, Fla.	250	WDR Norfolk, Va.	250	WVOT Vicksburg, Miss.	250	WCOV Montgomery, Ala.	250	
KVOD Tulsa, Okla.	5000		WWSB W. Smyrna Sch., Fla.	250	WDR Norfolk, Va.	250	WVOT Vicksburg, Miss.	250	KWJB So. of Globe, Ariz.	250	
WED Portland, Oreg.	250		WDEP Pensacola, Fla.	250	WVIV Christiansted, V.I.	250	WVOT Vicksburg, Miss.	250	KOFA Yuma, Ariz.	250	
KPUG Bellingham, Wash.	1000		WCNH Quincy, Fla.	250	KQTY Everett, Wash.	250	WVOT Vicksburg, Miss.	250	KVRC Arkadelphia, Ark.	250	
WVVA Wheeling, W.Va.	5000		WJNO W. Palm Beach, Fla.	250	KREW Sunnyside, Wash.	250	WVOT Vicksburg, Miss.	250	KHOZ Crossart, Ark.	250	
<b>1180-254.1</b>			WDEC Americus, Ga.	250	WLOG Logan, W.Va.	250	WVOT Vicksburg, Miss.	250	KWAK Stuttgart, Ark.	250	
WLDS Jacksonville, Ill.	1000		WBLJ Dalton, Ga.	250	WJAR Morgantown, W.Va.	250	WVOT Vicksburg, Miss.	250	KRDU Dinuba, Calif.	250	
WHAM Rochester, N.Y.	5000		WDFM Marietta, Ga.	250	WDM Parkersburg, W.Va.	250	WVOT Vicksburg, Miss.	250	KMBY Monterey, Calif.	250	
<b>1190-252.0</b>			WFRP Savannah, Ga.	250	WDM Parkersburg, W.Va.	250	WVOT Vicksburg, Miss.	250	KPPC Pasadena, Calif.	250	
KGYW Vallejo, Calif.	250		WYXK Waco, Ga.	250	WCLD Jansville, Wis.	250	WVOT Vicksburg, Miss.	250	KRKS Ridgecrest, Calif.	250	
WQWO Ft. Wayne, Ind.	5000		KBAR Burley, Idaho	250	WVHF Wausau, Wis.	250	WVOT Vicksburg, Miss.	250	KROY Sacramento, Calif.	250	
WANN Annapolis, Ind.	1000		KDRT Grandview, Idaho	250	KVOC Casper, Wyo.	250	WVOT Vicksburg, Miss.	250	KXON San Bernardino, Calif.	250	
WKOX Framingham, Mass.	1000		KRXX Rexburg, Idaho	250	<b>1240-241.8</b>		WVOT Vicksburg, Miss.	250	KSON San Diego, Calif.	250	
WLIB New York, N.Y.	1000		WJBC Bloomington, Ill.	250	CFPR Prince Rupert, B.C.	250	WVOT Vicksburg, Miss.	250	KSUE Susanville, Calif.	250	
KEX Portland, Oreg.	5000		WQCA Morlaix, Ill.	250	CJAV Port Alberni, B.C.	250	WVOT Vicksburg, Miss.	250	KRDO Colo. Sprngs., Colo.	250	
WDTV St. John, V.I.	1000		WHQA Sparta, Ill.	250	CJCS Stratford, Ont.	250	WVOT Vicksburg, Miss.	250	KCRT Trinidad, Colo.	250	
KLIF Dallas, Tex.	5000		WIOB Hammond, Ind.	250	CJRW Summerside, P.E.I.	250	WVOT Vicksburg, Miss.	250	WCGD Waterbury, Conn.	250	
<b>1200-249.9</b>			WSAL Logansport, Ind.	250	CKLN Nelson, B.C.	250	WVOT Vicksburg, Miss.	250	WGB Chipeley, Fla.	250	
WDAI San Antonio, Tex.	5000		WTCJ Tell City, Ind.	250	CKLS LaSarre, Que.	250	WVOT Vicksburg, Miss.	250	WMB Melbourne, Fla.	250	
<b>1210-247.8</b>			WBOW Terre Haute, Ind.	250	CKSS Sherbrooke, Que.	250	WVOT Vicksburg, Miss.	250	WLCO Eustis, Fla.	250	
WCNT Centalla, Ill.	1000		KFJB Marshalltown, Iowa	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WINK Fort Myers, Fla.	250	
WKXN Saginaw, Mich.	1000		WHIR Danville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WFDY St. Augustine, Fla.	250	
WADE Wadesboro, N.C.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WBHB Fitzgerald, Ga.	250	
WAVI Dayton, Ohio	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WDUN Gainesville, Ga.	250	
WCAU Philadelphia, Pa.	5000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WLAG LaGrange, Ga.	250	
<b>1220-245.8</b>			WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WMAJ Macon, Ga.	250	
CJOC Lethbridge, Alta.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WVNS Statesboro, Ga.	250	
CJRL Kenosha, Ont.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WPAX Thomsville, Ga.	250	
CKEC New Glasgow, N.S.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WTWA Thomson, Ga.	250	
CKVC Weston, N.B.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KVNI Coeur d'Alene, Idaho	250	
CKSM Shawinigan Falls, Quebec	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KEYY Pocatello, Idaho	250	
WEDR Birmingham, Ala.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KWEI Weiser, Idaho	250	
KVSA McGehee, Ark.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WCRW Chicago, Ill.	250	
KIBE Palo Alto, Calif.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WEDC Chicago, Ill.	250	
KFCO Denver, Colo.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WBCB Chicago, Ill.	250	
WRWB Kissimmee, Fla.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WBTX Harrisburg, Ill.	250	
WFEC Miami, Fla.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WETA Springfield, Ill.	250	
WCLB Camilla, Ga.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WSDR Sterling, Ill.	250	
WSFT Thomason, Ga.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WHBU Anderson, Ind.	250	
WLPO LaSalle, Ill.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KDEC Decatur, Iowa	250	
WKRS Waukegan, Ill.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KDCC Decatur, Iowa	250	
WLSM Salem, Ind.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KDCC Decatur, Iowa	250	
KJAN Atlantic, Iowa	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KIDC Spencer, Iowa	250	
KOFO Ottawa, Kans.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KIUL Garden City, Kans.	250	
WFKN Franklin, Ky.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KAKE Wichita, Kans.	250	
WAVN Stillwater, Minn.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WINN Louisville, Ky.	250	
WMDC Hazlehurst, Miss.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WFTM Maysville, Ky.	250	
KBHM Branson, Mo.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WPKE Pikeville, Ky.	250	
KMD Cape Girardeau, Mo.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KAPN Minden, La.	250	
KLPW Union, Mo.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	KANE New Iberia, La.	250	
WGNU Newburgh, N.Y.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250	WCOU Lewiston, Maine	250	
WKMT Kings Mtn., N.C.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250			
WREB Reidsville, N.C.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250			
WENC Whiteville, N.C.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250			
WGAR Cleveland, Ohio	5000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250			
KYGN Guyton, Okla.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250			
WIUN Mexico, Colo.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250			
WRIB Providence, R.I.	4000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250			
WALD Waterboro, S.Dak.	1000		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250			
KABR Aberdeen, S.Dak.	250		WHOP Hopkinsville, Ky.	250	WVOT Vicksburg, Miss.	250	WVOT Vicksburg, Miss.	250			

Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
WPCL	Montrose, Pa.	5000	KZUN	Opportunity, Wash.	1000	WMTM	Moultrie, Ga.	5000	WRIO	Rio Piedras, P.R.	500
WCAE	Pittsburgh, Pa.	5000	WKYR	Keyser, W.Va.	5000	WIMO	Winder, Ga.	1000	WMSC	Columbia, S.C.	1000
WNOW	York, Pa.	1000	<b>1280-234.2</b>			KLER	Lewiston, Idaho	5000	KELO	Stour Falls, S.Dak.	5000
WTMA	Charleston, S.C.	5000	CHED	Edmonton, Alta.	10000	WTAQ	La Grange, Ill.	5000	WKIN	Kingsport, Tenn.	5000
WKBL	Covington, Tenn.	500	CJMS	Montreal, Que.	5000	WFRX	W. Frarfort, Ill.	1000	KVNC	Colo. City, Tex.	1000
KFTX	Paris, Tex.	500	CKCV	Quebec, Que.	1000	KGLO	Mason City, Iowa	5000	KSJ	Gladeview, Tex.	1000
KPAC	Port Arthur, Tex.	5000	CKDA	Victoria, B.C.	5000	WLEX	Lexington, Ky.	1000	KXYZ	Houston, Tex.	5000
KEXX	San Antonio, Tex.	500	WPID	Piedmont, Ala.	1000	WIBR	Baton Rouge, La.	1000	KDYL	Salt Lake City, Utah	5000
KSML	Seminole, Tex.	5000	WNPT	Tuscaloosa, Ala.	1000	KLUE	Shreveport, La.	1000	WLLY	Richmond, Va.	1000
WDVA	Danville, Va.	5000	KHEP	Phoenix, Ariz.	1000	WFBF	Baltimore, Md.	5000	KXRO	Aberdeen, Wash.	1000
WYSR	Franklin, Va.	1000	KFOX	Long Beach, Calif.	1000	WJDA	Quincy, Mass.	5000	KHIT	Wallia Wallia, Wash.	1000
WNRG	Grundy, Va.	1000	KJYO	Stockton, Calif.	1000	WODD	Grand Rap. Mich.	5000	<b>1330-225.4</b>		
KWSC	Pullman, Wash.	5000	KXOB	Stockton, Calif.	1000	WRBC	Jackson, Miss.	5000	CBH	Halifax, N.S.	100
KTW	Seattle, Wash.	1000	KTLN	Denver, Colo.	5000	KMMO	Marshall, Mo.	1000	WRFS	Scottsboro, Ala.	1000
WEMP	Milwaukee, Wis.	5000	KSFT	Trinidad, Colo.	1000	KBRL	McCook, Nebr.	1000	KFAC	Los Angeles, Calif.	5000
<b>1260-238.0</b>			WSUX	Seaford, Del.	1000	WTNJ	Tronton, N.J.	250	WARF	Flt. Pierce, Fla.	1000
CFRN	Edmonton, Alta.	5000	WDSQ	DeFuniak Sprgs., Fla.	5000	WOSC	Fulton, N.Y.	1000	WBYN	Millon, Fla.	1000
DYBU	Cebu, P.I.	1000	WQIK	Jackville, Fla.	1000	WGOL	Goldsboro, N.C.	1000	WBYN	Tallahassee, Fla.	5000
WCRT	Birmingham, Ala.	1000	WIPC	Lake Wales, Fla.	1000	WSDY	Mt. Airy, N.C.	5000	WMLT	Dublin, Ga.	1000
KFIN	Casa Grande, Ariz.	1000	WIBB	Macon, Ga.	1000	WRE	Cleveland, Ohio	5000	WEAW	Evansville, Ill.	1000
KGA	San Fernando, Calif.	1000	WMRO	Aurora, Ill.	250	KOME	Tulsa, Okla.	5000	WRRR	Rockford, Ill.	1000
KYS	San Francisco, Calif.	1000	WGBF	Evansville, Ind.	5000	KRMW	The Dalles, Oreg.	1000	WJPS	Evansville, Ind.	5000
KUBC	Montrose, Colo.	1000	KCOB	Newtown, Iowa	1000	WTLI	Mayaguez, Puerto Rico	1000	KWWL	Waterloo, Iowa	5000
WDDC	Washington, D.C.	5000	KSCB	Arkansas City, Kans.	1000	KOLY	Mobridge, S.Dak.	1000	KFPH	Wichita, Kans.	5000
WFTW	Fort Walton, Fla.	1000	WHLN	Harlan, Ky.	1000	WCKI	Greer, S.C.	1000	WDRR	Morhead, Ky.	1000
WPPF	Palatka, Fla.	1000	WDSU	New Orleans, La.	1000	WAKA	Nashville, Tenn.	5000	KVOI	Fort Collins, Colo.	1000
WHAB	Baxley, Ga.	5000	WEIM	Fitchburg, Mass.	5000	KVET	Austin, Tex.	1000	WASA	Havre de Grace, Md.	1000
WTJH	East Point, Ga.	5000	WFCY	Alma, Mich.	1000	KTFY	Brownfield, Tex.	1000	WCRB	Waltham, Mass.	5000
WTJH	Bellefonte, Ill.	1000	WTCN	Minneapolis, Minn.	1000	KOL	Seattle, Wash.	5000	WBBC	Flint, Mich.	1000
WFBM	Indianapolis, Ind.	5000	KVOD	Moorhead, Minn.	1000	WCAW	Charleston, W.Va.	1000	WLOL	Minneapolis, Minn.	5000
KFGQ	Boone, Iowa	250	KDCK	Clinton, Mo.	1000	WKVY	Charleston, W.Va.	1000	WJPR	Greenville, Miss.	1000
KWHK	Hutchinson, Kans.	1000	KCNI	Henderson, Nebr.	1000	WCLG	Morgantown, W.Va.	1000	KGAK	Gallup, N.Mex.	5000
WXOK	Baton Rouge, La.	1000	KTOD	Henderson, Nev.	5000	WKLK	St. Albans, W.Va.	1000	WFOV	Brooklyn, N.Y.	5000
WVDA	Boston, Mass.	5000	WHBI	Newark, N.J.	5000	<b>1310-228.9</b>			WEVD	New York, N.Y.	1000
WALM	Albion, Mich.	1000	WQV	New York, N.Y.	5000	CKOY	Ottawa, Ont.	5000	WHAZ	Troy, N.Y.	1000
KROX	Crookston, Minn.	1000	WVET	Rochester, N.Y.	1000	WHEP	Foley, Ala.	5000	WFIN	Findlay, Ohio	1000
KDUZ	Hutchinson, Minn.	1000	WSAT	Salisbury, N.C.	1000	WJAM	Marion, Ala.	5000	KPOJ	Portland, Oreg.	5000
WGYM	Greenville, Miss.	1000	WNON	Defiance, Ohio	500	KTYL	Mesa, Ariz.	5000	WIKK	erie, Pa.	5000
KGBX	Springfield, Mo.	5000	WLMJ	Jackson, Ohio	1000	KBOK	Malvern, Ark.	5000	WLAB	Conway, S.C.	1000
WBUD	Trenton, N.J.	5000	KLCO	Poteau, Okla.	1000	KWBX	Galveston, Calif.	5000	WFBS	Greenville, S.C.	1000
KVSF	Santa Fe, N.Mex.	5000	KEGG	Eugene, Oreg.	500	KTKR	Taft, Calif.	500	WAEW	Wilmington, N.C.	1000
WNSR	Syracuse, N.Y.	5000	WHVR	Hanover, Pa.	5000	KFKA	Greeley, Colo.	1000	WTRO	Dyersburg, Tenn.	500
WDRR	Asheboro, N.C.	1000	WKST	New Castle, Pa.	5000	WICH	Norwich, Conn.	1000	KMIL	Camden, Tex.	500
WCDJ	Edenton, N.C.	1000	WCMN	Arcelbio, P.R.	1000	WOOD	Deland, Fla.	1000	KSWA	Graham, Tex.	500
WDDK	Cleveland, Ohio	5000	WANS	Anderson, S.C.	1000	WBRO	Waynesboro, Ga.	1000	KINE	Kingsville, Tex.	1000
WNXT	Portsmouth, Ohio	5000	WJAY	Mullins, S.C.	1000	WISH	Indianapolis, Ind.	5000	KDKK	Tyler, Tex.	500
KWSH	Wewaka-Seminole, Okla.	1000	WJGD	Columbia, Tenn.	1000	WJAM	Arion, Ala.	5000	WBTM	Danville, Va.	5000
KMCM	McMinnville, Oreg.	1000	KWHI	Brenham, Tex.	1000	KOKX	Keokuk, Iowa	5000	WETZ	New Market, Va.	1000
WERC	Erie, Pa.	5000	KLTI	Longview, Tex.	1000	WLIX	Twin Falls, Idaho	5000	WBEL	Sheboygan, Wis.	1000
WPHB	Phillipsburg, Pa.	1000	KNAK	Salt Lake City, Utah	5000	WTLI	Madisonville, Ky.	5000	KOVE	Lander, Wyo.	1000
WISZ	Ponca, P.R.	1000	WYVE	Waltville, Va.	1000	KJKS	Sulphur, La.	500	<b>1340-223.7</b>		
WUOU	Greenville, S.C.	1000	KIT	Yakima, Wash.	5000	KUZN	W. Monroe, La.	1000	CFSL	Wayburn, Sask.	250
WJOT	Lake City, S.C.	1000	WNAM	Neenah, Wis.	1000	WLOB	Portland, Maine	1000	CHAD	Amos, Que.	250
WMFS	Chattanooga, Tenn.	1000	<b>1290-232.4</b>			KRBI	St. Peter, Minn.	1000	CSL	Ypsilanti, Mich.	250
WMCH	Church Hill, Tenn.	1000	CFAM	Altoona, Man.	1000	WROR	Worcester, Mass.	5000	CHRD	Drummondville, Que.	250
WDKN	Dickson, Tenn.	1000	CKSL	London, Ont.	5000	WKMH	Dearborn, Mich.	5000	CJQC	Quebec, Que.	250
KBLP	Fairfurlas, Tenn.	500	WPBB	Jackson, Ala.	1000	KFSB	Joplin, Mo.	5000	CJOB	Winnipeg, Man.	250
KWFR	San Angelo, Tex.	1000	WMLS	Sylacauga, Ala.	1000	WJLK	Asbury Park, N.J.	250	CKOX	Woodstock, Ont.	250
KTUE	Tulsa, Tex.	1000	KVOA	Tucson, Ariz.	1000	WCAM	Camden, N.J.	250	WKUL	Gulfport, Ala.	250
KTAE	Taylor, Tex.	1000	KDMS	El Dorado, Ark.	5000	WTLB	Utica, N.Y.	5000	WJOI	Florence, Ala.	250
WCHV	Charlottesville, Va.	5000	KUGA	Silviam Sprngs., Ark.	5000	WAGB	Asheville, N.C.	1000	WGWG	Wilmington, N.C.	250
WBCR	Christiansburg, Va.	1000	KLTL	Chico, Calif.	5000	WTK	Durham, N.C.	5000	WFEF	Sylacauga, Ala.	250
KWIG	Moses Lake, Wash.	5000	KITO	San Bernardino, Calif.	5000	KNOX	Grand Forks, N.Dak.	5000	KIBB	Seward, Alaska	250
WVWV	Grafton, W.Va.	1000	WCCC	Hartford, Conn.	500	WFAH	Alliance, Ohio	1000	KRUX	Glendale, Ariz.	250
WCKZ	Edenton, Wis.	1000	WTUX	Wilmington, Del.	1000	KNPT	Newport, Oreg.	1000	KNOG	Nogales, Ariz.	250
WOKW	Sturgeon Bay, Wis.	1000	WTMC	Ocala, Fla.	5000	WBFD	Bedford, Pa.	1000	KBTA	Batesville, Ark.	250
KPOW	Powell, Wyo.	5000	WTRK	W. Palm Beach, Fla.	5000	WWSA	Ephrata, Pa.	1000	KAGB	Greenwood, Ark.	250
<b>1270-236.1</b>			WDFC	Delaware, Ga.	1000	WAGC	Warren, Pa.	1000	KERS	Springdale, Ark.	250
CHAT	Medicine Hat, Alta.	1000	WCH	Canton, Ga.	1000	WDKD	Kingstree, S.C.	5000	KENL	Arcata, Calif.	250
GHWK	Chillicothe, B.C.	1000	WTOC	Savannah, Ga.	5000	WDDO	Chattanooga, Tenn.	5000	KMAK	Fresno, Calif.	250
CJCB	Sydney, N.S.	5000	KYTE	Pocatello, Idaho	1000	WDXI	Jackson, Tenn.	1000	KAVL	Lancaster, Calif.	250
CFGT	St. Joseph d'Alma, Quebec	1000	WIRL	Peoria, Ill.	5000	KZIP	Amarillo, Tex.	1000	WSDM	Mt. Shasta, Calif.	250
WGSV	Guntersville, Ala.	1000	WCBL	Benton, Ky.	1000	WRR	Dallas, Tex.	5000	KSFE	Needles, Calif.	250
WPNX	Phenix City, Ala.	1000	KJEF	Jennings, La.	500	WRCF	Fairfax, Va.	5000	KOBV	Bozeman, Mont.	250
AJIP	Prichard, Ala.	1000	WHG	Houghton Lake, Mich.	1000	WGH	Newport News, Va.	5000	KDAN	Oroville, Calif.	250
KBYR	Anchorage, Alaska	1000	WNIL	Niles, Mich.	500	KARY	Prosser, Wash.	5000	KCMJ	Palm Sprngs., Calif.	250
KDJI	Holbrook, Ariz.	1000	KBMO	Benson, Minn.	500	WIBA	Madison, Wis.	5000	KATY	San Luis Obispo, Calif.	250
KCOK	Tulare, Calif.	1000	WBLE	Batesville, Miss.	1000	<b>1320-227.1</b>			KIST	Santa Barbara, Calif.	250
WNOG	Naples, Fla.	500	KALM	Thayer, Mo.	1000	CKNW	New Westminster, British Columbia	5000	KMSA	Santa Maria, Calif.	250
WTAL	Tallahassee, Fla.	5000	KYVA	Missoula, Mont.	1000	CJSO	Sorel, P.Q.	1000	KBN	Ben Watsonville, Calif.	250
WGBA	Columbus, Ga.	5000	KIL	Oberlin, Ohio	5000	WAGF	Dothan, Ala.	1000	KVRH	Salida, Colo.	250
KTFI	Twin Falls, Idaho	5000	WNE	Keene, N.H.	5000	WEZB	Homewood, Ala.	1000	WNHC	New Haven, Conn.	250
WKYR	Keyser, W.Va.	1000	WNBF	Binghamton, N.Y.	5000	KWHN	Fort Smith, Ark.	5000	W00K	Washington, D.C.	250
WEC	Charleston, Ill.	1000	WHKY	Hickory, N.C.	1000	KRLW	Walnut Ridge, Ark.	5000	WTAN	Clearwater, Fla.	250
WHBF	Rock Island, Ill.	5000	WEYE	Sanford, N.C.	1000	KCRS	Sacramento, Calif.	5000	WROD	Daytona Beh., Fla.	250
WWCA	Gary, Ind.	1000	WTRX	Bellaire, Ohio	1000	WRCO	Rocky Ford, Colo.	1000	WDSR	Lake City, Fla.	250
WORX	Madison, Ind.	1000	KUMA	Dayton, Ohio	5000	WATR	Waterbury, Conn.	1000	WTFY	Fort Worth, Tex.	250
KSCB	Liberal, Kans.	5000	KBKO	Portland, Oreg.	1000	WJHP	Jacksonville, Fla.	5000	WQXT	Palm Beach, Fla.	250
WAIN	Columbia, Ky.	1000	WTRN	Tyrone, Pa.	500	WHIE	Griffin, Ga.	1000	WJCM	Sebring, Fla.	250
WFL	Fulton, N.Y.	1000	WICE	Providence, R.I.	500	WNEG	Tacoza, Ga.	1000	WGAU	Athens, Ga.	250
WPRP	Prestonsburg, Ky.	5000	WFIG	Sumter, S.C.	1000	WKAN	Kankakee, Ill.	1000	WAKE	Atlanta, Ga.	250
KVCL	Winfield, La.	1000	W0KVE	Oak Ridge, Tenn.	1000	KLWN	Lanark, Kans.	5000	WBBO	Augusta, Ga.	250
WSPR	Springfield, Mass.	1000	W0KY	Crockett, Tex.	5000	WRBR	Brownsville, Ky.	1000	WGAA	Cedarhurst, Ga.	250
WXYZ	Detroit, Mich.	1000	KTRN	Wichita Falls, Tex.	5000	WNGO	Mayfield, Ky.	1000	WDAK	Delbart, Ind.	250
WLSN	Louisville, Miss.	1000	WCLA	Colonial Hgts., Va.	1000	KVHL	Homer, La.	1000	W0WGS	Tifton, Ga.	250
KUSN	St. Joseph, Mo.	5000	WVOW	Logan, W.Va.	5000	WICO	Salisbury, Md.	500	KPST	Preston, Idaho	250
WTSN	Dover, N.H.	5000	WML	Milwaukee, Wis.	1000	WARA	Attleboro, Mass.	1000	WSOY	Deatur, Ill.	250
WHLD	Niagara Falls, N.Y.	5000	WCOW	Sparta, Wis.	1000	WILS	Lansing, Mich.	5000	WJPF	Herrin, Ill.	250
WLIK	Newport, Tenn.	5000	<b>1300-230.6</b>			W0DMJ	Marsquette, Mich.	1000	WJOL	Joliet, Ill.	250
WIOX	Bay City, Tex.	1000	CBAF	Moncton, N.B.	5000	W0WPC	Houston, Miss.	1000	WBW	Bedford, Ind.	250
WHEM	Big Spring, Tex.	1000	CJRH	Richmond Hill, Ont.	500	W0WRIJ	Pleatayne, Miss.	5000	W0WBC	Bloomington, Ind.	250
KEPS	Eagle Pass, Tex.	1000	W0TLS	Tallahassee, Ala.	1000						



Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
WEST	Easton, Pa.	250	KBTN	Neosho, Mo.	500	CHEF	Granby, P.Q.	250	WLEU	Erle, Pa.	250
WJET	Erle, Pa.	250	WALY	Herkimer, N.Y.	1000	CJMT	Chicoutimi, Que.	250	WGET	Gettysburg, Pa.	250
WHGB	Harrisburg, Pa.	250	WLNA	Peekskill, N.Y.	1000	CJOY	Guelph, Ont.	250	WBAD	Indiana, Pa.	250
WJAC	Johnstown, Pa.	50	WYOT	Wilson, N.C.	1000	WHMA	Anniston, Ala.	250	WPAM	Portville, Pa.	250
WKBI	St. Marys, Pa.	250	WHK	Cleveland, Ohio	500	WBED	Doemer, Ala.	250	WPAJ	Monte College, Pa.	250
WICK	Seranton, Pa.	250	KYNG	Hobart, Okla.	2500	WDIG	Dothan, Ala.	250	WJPA	Washington, Pa.	250
WRAK	Williamsport, Pa.	250	WTJS	Keosauqua, Mo.	1000	WFUN	Huntsville, Ala.	250	WRDL	Caguas, P.R.	250
WMOA	San Juan, P.R.	250	WCOJ	Coca Bay, Oreg.	5000	WLAY	Muscle Shoals City, Ala.	250	WRRI	Caguas, P.R.	250
WCOS	Columbia, S.C.	250	WCED	DuBols, Pa.	5000	KLAM	Cordova, Alaska	250	WRIA	Warwick, R.I.	250
WGTN	Georgetown, S.C.	250	WCRE	Cheraw, S.C.	1000	KMCD	Cifton, Ariz.	250	WQSN	Charleston, S.C.	250
WJAN	Spartanburg, S.C.	250	WEMB	Erwin, Tenn.	1000	KAWT	Douglas, Ariz.	250	WCBS	Greenwood, S.C.	250
WJZM	Clarksville, Tenn.	250	WKFS	Pulaski, Tenn.	250	KNOT	Prescott, Ariz.	250	WMBY	York, S.C.	250
WHUB	Cookeville, Tenn.	250	KFVN	Bonham, Tex.	1000	KOLD	London, Ariz.	250	WMSD	Artistsville, S.C.	250
WKPT	Kingsport, Tenn.	250	KTRF	Lufkin, Tex.	1000	KGRH	Fayetteville, Ark.	250	WDXI	Orangeburg, S.C.	250
WGAP	Maryville, Tenn.	250	KCNB	New Braunfels, Tex.	1000	KENA	Mena, Ark.	250	KDSJ	Deadwood, S.Dak.	250
WHAL	Shelbyville, Tenn.	250	KPEP	San Angelo, Tex.	1000	KYDR	Blitha, Calif.	250	KYNT	Yankton, S.Dak.	250
KRUN	Baileys, Tex.	250	WWSR	St. Albans, Vt.	1000	KPAL	Palm Springs, Calif.	250	WLAR	Athens, Tenn.	250
KTXC	Big Spring, Tex.	250	WDDY	Gloucester, Va.	1000	KPTP	Porterville, Calif.	250	WDXB	Chattanooga, Tenn.	250
KUNO	Corpus Christi, Tex.	250	KITI	Chenails, Wash.	1000	KSAN	San Francisco, Calif.	250	WDSG	Dyersburg, Tenn.	250
KLUF	nr. Galveston, Tex.	250	KUJ	Walla Walla, Wash.	5000	KVEN	Ventura, Calif.	250	WTRD	Dyersburg, Tenn.	250
KGVL	Greenville, Tex.	250	WPLY	Plymouth, Wis.	500	KAGR	Yuba City, Calif.	250	WLAF	LaFollette, Tenn.	100
KEBE	Jacksonville, Tex.	250				KYOA	Alamosa, Colo.	250	WCRK	Morristown, Tenn.	250
KIUN	Pecos, Tex.	250				KYOU	Greeley, Colo.	250	WGNS	Murfreesboro, Tenn.	250
KEYE	Perry, Tex.	250				WNAB	Bridgeport, Conn.	250	KRIC	Beaumont, Tex.	250
KIYB	Plainview, Tex.	250				WILM	Wilmington, Del.	1000	KBEN	Carrollton Sprgs., Tex.	250
KDWT	Stamford, Tex.	250				WLSH	Washington, D.C.	250	KCTI	Gonzales, Tex.	250
KTEM	Temple, Tex.	250				WFJ	Dayton Beach, Fla.	250	WMBJ	Junction, Tex.	250
KTFS	Texaskana, Tex.	250				WSBK	Miami, Fla.	250	KCYL	Lampasas, Tex.	250
KVOU	Uvalde, Tex.	250				WBSR	Pensacola, Fla.	250	KMHT	Marshall, Tex.	250
KIXX	Provo, Utah	250				WSPB	Sarasota, Fla.	250	KNET	Palestine, Tex.	250
WDOT	Burlington, Vt.	250				WSTU	Stuart, Fla.	1000	KSNY	Snyder, Tex.	250
WVIA	Clarkston, Va.	250				WTNT	Tallahassee, Fla.	250	KNEU	Provo, Utah	250
WLWD	Portsmouth, Va.	250				WGFC	Albany, Ga.	250	WTA	Brattleboro, Vt.	250
WHLF	So. Boston, Va.	250				WBHF	Bartlesville, Ga.	250	WFR	Fort Loyal, Va.	250
WINC	Winchester, Va.	250				WCON	Cornelia, Ga.	250	WRE	Landon, Va.	250
KFRD	Grand Coulee, Wash.	250				WKEU	Griffin, Ga.	250	WVVA	Martinsville, Va.	250
KWTK	Longview, Wash.	250				WMYG	Milldeville, Ga.	250	WLEE	Richmond, Va.	250
KNLK	Tacoma, Wash.	250				WCCP	Savannah, Ga.	250	WLPM	Suffolk, Va.	250
KYAK	Yakima, Wash.	250				KEEP	Twin Falls, Idaho	250	KBKW	Aberdeen, Wash.	250
KWBL	Clarkston, W. Va.	250				WFPC	Cicero, Ill.	1000	KCLX	Colfax, Wash.	250
WRON	Roncoevette, W. Va.	250				WEL	Wheat Ridge, Ill.	100	KSEM	Moses Lake, Wash.	250
WBWK	Wheeling, W. Va.	250				WCVS	Springfield, Ill.	250	KWBI	Wentworth, Wash.	250
WBTH	Williamson, W. Va.	250				WANE	Ft. Wayne, Ind.	250	KAYE	Puyallup, Wash.	250
WATW	Ashland, Wis.	250				WASK	Lafayette, Ind.	250	WNNR	Beckley, W. Va.	250
WBIZ	Eau Claire, Wis.	250				WAOV	Vincennes, Ind.	250	WPAP	Parkersburg, W. Va.	250
WDUZ	Green Bay, Wis.	250				KPIG	Cedar Rapids, Iowa	250	WHAW	Weston, W. Va.	250
WRJN	Racine, Wis.	250				KCRB	Chanute, Kans.	1000	KFJZ	Fond du Lac, Wis.	250
WRDB	Reedsburg, Wis.	250				WHG	Hutchinson, Kans.	250	WDLB	Marshfield, Wis.	250
WSAU	Wausau, Wis.	250				WTGO	Campbellville, Ky.	1000	WRCO	Rifland, Wis.	250
KATI	Casper, Wyo.	250				WNKY	Neon, Ky.	1000	KBBS	Buffalo, Wyo.	250
KODI	Cody, Wyo.	250				WPAD	Paducah, Ky.	250	KWRL	Riverton, Wyo.	250

**1410-212.6**

CFUN	Vancouver, B.C.	1000
CHLP	Montreal, Que.	1000
WALA	Mobile, Ala.	5000
KTCS	Ft. Smith, Ark.	500
KWCB	Searcy, Ark.	1000
KERN	Bakersfield, Calif.	5000
KMYO	Marysville, Calif.	5000
KCAL	Redlands, Calif.	1000
WPDP	Hartford, Conn.	5000
KCOL	Ft. Collins, Colo.	1000
WDOV	Dover, Del.	1000
WMYR	Ft. Myers, Fla.	5000
WLAG	Rome, Ga.	1000
WRMN	Elgin, Ill.	500
WTIM	Taylorville, Ill.	1000
KLEM	LeMars, Iowa	1000
KCLO	Leavenworth, Kans.	1000
KWBB	Whiteta, Kans.	5000
WLBJ	Bowling Green, Ky.	5000
KDBS	Alexandria, La.	1000
WGRD	Grand Rap., Mich.	5000
WEGA	Newtown, Miss.	1000
WFCB	Dunkirk, N.Y.	500
WEGD	Concord, N.C.	1000
WSRC	Durham, N.C.	5000
ING	Dayton, Ohio	1000
KPAM	Portland, Oreg.	1000
WLSN	Lansing, Pa.	5000
KBUD	Pittsburgh, Pa.	5000
KBUD	Athens, Tex.	250
KVLB	Cleveland, Tex.	500
KXIT	Dalhath, Tex.	500
KRIG	Odessa, Tex.	500
KBAL	San Saba, Tex.	500
KNAL	Victoria, Tex.	500
WRIS	Rohanoke, Va.	5000
KUEN	Wenatchee, Wash.	1000
WKBB	LaCrosse, Wis.	5000
KWYO	Sheridan, Wyo.	500

**1420-211.1**

KCDM	Saskatoon, Sask.	5000
KPCD	Pocahontas, Ark.	1000
KSTN	Stockton, Calif.	1000
WLSB	Djd Saybrook, Conn.	500
WDBF	Delray Beh., Fla.	500
WSTN	St. Augustine, Fla.	5000
WRBL	Columbus, Ga.	5000
WLET	Toledo, Ga.	5000
WINI	Murphysboro, Ill.	500
WIMS	Michigan City, Ind.	1000
WOC	Davenport, Iowa	5000
WTCR	Ashland, Ky.	5000
WHBN	Harrisburg, Ky.	1000
WVJS	Owensboro, Ky.	1000
KJAL	Junction City, Kans.	1000
KLFY	Lafayette, La.	1000
WBSM	New Bedford, Mass.	1000
WBEC	Pittsfield, Mass.	500
WAMM	Flint, Mich.	1000
KTOE	Mankato, Minn.	1000
WSUM	Oxford, Miss.	5000
WQBC	Vicksburg, Miss.	1000

**1430-209.7**

CHEX	Peterborough, Ont.	1000
WFHK	Pell City, Ala.	1000
KWMB	Monticello, Ark.	1000
KAMP	EI Centro, Calif.	1000
KARM	Fresno, Calif.	5000
KKLI	Pasadena, Calif.	5000
KOSI	Aurora, Cal.	5000
WLAS	Lakeland, Fla.	5000
WGFS	Covington, Ga.	1000
WRCD	Dalton, Ga.	1000
WCMT	Ottawa, Ill.	500
WIRE	Indianapolis, Ind.	5000
KASI	Ames, Iowa	1000
WKIG	Indianapolis, Ind.	1000
KMRC	Moran City, La.	500
WNAV	Annapolis, Md.	5000
WIL	St. Louis, Mo.	1000
WHIL	Medford, Mass.	5000
WION	onia, Mich.	5000
WBRB	St. Clemens, Mich.	1000
KRGI	Grand Island, Nebr.	5000
KALY	Alva, Mich.	250
WNJR	Newark, N.J.	5000
WENE	Endicott, N.Y.	5000
WMNC	Morportant, N.C.	5000
WRXO	Roxboro, N.C.	1000
WFOB	Newark, Ohio	1000
WCLT	Fostoria, Ohio	500
KTUL	Lookout Mountain, Okla.	5000

**1440-208.2**

WHHY	Montgomery, Ala.	5000
KPOK	Scottsdales, Ariz.	1000
KDKY	Little Rock, Ark.	5000
KYOD	York, Pa.	1000
KPRD	Riverside, Calif.	1000
WBIS	Bristol, Conn.	500
WABR	Winter Park, Fla.	1000
WWCC	Bremen, Ga.	500
WGIG	Brunswick, Ga.	1000
KWIK	Pocostello, Idaho	5000
KALY	Alva, Mich.	250
WPRS	Paris, Ill.	500
WQMC	Quincy, Ill.	1000
WROK	Rockford, Ill.	500
WPGW	Portland, Ind.	500
KCHE	Cherokee, Iowa	500
KJAY	Topeka, Kans.	500
KFLX	Flint, Kans.	500
KMLB	Monroe, La.	5000
WAAB	Worcester, Mass.	5000
WBGM	Bay City, Mich.	500
WCHB	Inkster, Mich.	5000
KEUE	Minneapolis, Minn.	5000
KFJM	Grand Forks, N.Dak.	500
WALV	Millville, N.J.	1000
WJLL	Niagara Falls, N.Y.	1000
WBUY	Lexington, N.C.	5000
WHMH	Warren, Ohio	5000
KMED	Medford, Oreg.	5000
KDDL	The Dalles, Oreg.	5000
WCDL	Carbondale, Pa.	5000
WOCB	Red Lion, Pa.	5000
WQDK	Greenville, S.C.	5000
WZYX	Cowan, Tenn.	500
WDMO	McKenzie, Tenn.	500
KFDA	Amarillo, Tex.	5000
KEYS	Corpus Christi, Tex.	1000
KDNT	Denton, Tex.	5000
WKLV	Blackstone, Va.	5000
KITN	Dlympla, Wash.	5000
WHIS	Bluffton, W. Va.	5000
WJPG	Green Bay, Wis.	5000

**1450-206.8**

CBG	Gander, Nfld.	250
CFAB	Windsor, N.S.	250
CFJR	Brookville, Ont.	250

**1460-205.4**

WTIX	New Orleans, La.	250
WRAC	Presque Isle, Maine	250
WRKD	Rockland, Maine	250
WRUM	Rumford, Maine	250
WKTO	South Paris, Maine	250
WTBO	Cumberland, Md.	250
WMAS	Springfield, Mass.	250
WATZ	Alpena Township, Mich.	250
WHGJ	Holland, Mich.	250
WMIQ	Iron Mtn., Mich.	250
WKLA	Ludington, Mich.	250
WIBM	Jackson, Mich.	250
WHLS	Port Huron, Mich.	250
KATE	Albert Lea, Minn.	250
KJUN	Jackson, Minn.	250
KBNW	Breckenridge, Minn.	250
WELY	Ely, Minn.	250
KDMA	Montevideo, Minn.	100
KFAM	St. Cloud, Minn.	250
WROX	Clarksdale, Miss.	1000
WCJA	Columbia, Miss.	250
WJXN	Jacksn, Miss.	250
WOKK	Meridian, Miss.	250
WNAT	Natchez, Miss.	250
WRBD	West Point, Miss.	250
KIRK	Kirksville, Mo.	250
KOKO	Warrensburg, Mo.	250
KXLQ	Bozeman, Mont.	250
KJLI	Great Falls, Mont.	250
WMBH	Joplin, Mo.	250
KWPM	West Plains, Mo.	250
KXLL	Missoula, Mont.	250
KWBE	Beatrice, Nebr.	250
KCSR	Chadron, Nebr.	250
KONE	Concord, Nev.	250
WPKL	Concord, N.H.	250
WFGP	Atlantic City, N.Y.	250
WCTC	New Brunswick, N.J.	250
KLOS	Albuquerque, N.Mex.	250
KENM	Portales, N.Mex.	250
WHDL	Allegany, N.Y.	250
KLWX	Clayton, N.Mex.	250
KOBE	Las Cruces, N.Mex.	250
WCLI	Corning, N.Y.	250
WWSG	Glen Falls, N.Y.	250
WKIP	Poughkeepsie, N.Y.	250
WKAL	Rome, N.Y.	250
WATA	Boone, N.C.	250
WGNC	Greensboro, N.C.	250
WBLE	Elizabethtown, N.C.	250
WHVH	Henderson, N.C.	250
WHKP	Hendersonville, N.C.	250
WHIT	New Bern, N.C.	250
KEYS	Williston, N.Dak.	250
WJER	Dover, Ohio	250
WMDH	Hamilton, Ohio	250
WEDC	Saxtus, Ohio	250
WHWS	Altus, Okla.	250
KGFF	Shawnee, Okla.	250
KSIW	Woodward, Okla.	250
KWRD	Coquille, Oreg.	250
KORE	Eugene, Oreg.	250
KFLW	Klamath Falls, Oreg.	250
KLBM	La Grande, Oreg.	250
KBPS	Portland, Oreg.	250

**1470-204.0**

CJNB	N. Battleford, Sask.	1000
WFMM	Cullman, Ala.	5000
KDON	Sullins, Calif.	5000
KABA	Colorado Sprrs., Colo.	1000
WBAR	Bartow, Fla.	1000
WFNM	DeFuniak Sprrs., Fla.	1000
WBBR	Jacksonville, Fla.	1000
WHFJ	Hanford, Ga.	1000
WROJ	Carroll, Ill.	1000
KSO	Des Moines, Iowa	5000
WKAM	Goshen, Ind.	500
WOCH	North Vernon, Ind.	500
WRVK	Mt. Vernon, Ky.	500
WAIL	Baton Rouge, La.	5000
WVGH	Greenhill, La.	1000
WBET	Brookton, Mass.	1000
WBRN	Big Rapids, Mich.	1000
WPON	Pontiac, Mich.	500
KRNY	Kearney, Nebr.	5000



Rc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.	Kc.	Wave Length	W.P.
KWOW	Pomona, Calif.	1000	KMDO	Ft. Scott, Kans.	500	WTRU	Muskegon, Mich.	5000	KASH	Eugene, Oreg.	1000
KUBA	Yuba City, Calif.	1000	WNES	Central City, Ky.	500	WKDL	Clarksdale, Miss.	1000	WFIS	Fountain Inn, S.C.	1000
KLAK	Lakewood, Colo.	1000	WSTL	Emmence, Ky.	500	KATZ	St. Louis, Mo.	500	WKBJ	Milan, Tenn.	1000
WKAF	Key West, Fla.	500	KFNV	Ferriday, La.	1000	KTTN	Trenton, Mo.	1000	KBDR	Brownsville, Tex.	500
WGKA	Atlanta, Ga.	1000	KLFT	Golden Meadow, La.	1000	WONG	Oneida, N.Y.	5000	KCFH	Cuero, Tex.	1000
WMCW	Harvard, Ill.	500	KLVI	Livian, La.	500	WVRL	Woodside, N.Y.	500	KMAE	McKinney, Tex.	1000
WBTO	Pertin, Ind.	500	WINX	Rockville, Md.	500	WGLV	Charlotte, N.C.	100	KOGT	Orange, Tex.	1000
WARU	Luru, Ind.	1000	WBOS	Brockline, Mass.	5000	WFRC	Roldsville, N.C.	250	WBOF	Virginia Bch., Va.	1000
KLGA	Algonia, Iowa	5000	WJKO	Springfield, Mass.	5000	WBLV	Springfield, Ohio	1000	WHLL	Wheeling, W.Va.	5000
KCRG	Cedar Rapids, Iowa	5000	WHRY	Ann Arbor, Mich.	1000	KUSH	Cushing, Okla.				

## United States and Canadian

Amplitude-Modulation (AM) Broadcasting Stations Listed Alphabetically by Location

Abbreviations: C.L., call letters; Kc., frequency in kilocycles; N.A., network affiliation—A: American Broadcasting Co., C: Columbia Broadcasting System, Inc.; M: Mutual Broadcasting System; N: National Broadcasting Co., Inc. (For watt power of station, see list arranged by Frequency, p. 169)

Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.	Location	C.L.	Kc.	N.A.
Abbeville, La.	KRF	960		Anderson, Ind.	WCBC	1470		Bainbridge, Ga.	WMGR	930	M	Bethlehem, Pa.	WGPA	1100	
Abbeville, S.C.	WBYB	1590		Anderson, S.C.	WHBU	1240	A-C	Baker, Oreg.	KBKR	1490		Biddeford, Maine	WIDE	1400	M
Aberdeen, Md.	WAMD	970			WAIM	1230	C	Bakersfield, Calif.	KAFY	550	M	Big Rapids, Mich.	WBRN	1460	
Aberdeen, Miss.	WMPA	1240			WANS	1280	M	Barrie, Ont.	WBAW	970		Big Sprs., Tex.	KBST	1490	A
Aberdeen, S.Dak.	KABR	1220		Andrews, Tex.	KACT	1360			KERN	1410	C		KHEM	1270	
Aberdeen, Wash.	KSDN	930	A	Annapolis, Md.	WANN	1980			KGEE	1230	N		KTXC	1400	
	KBKW	1450	A	Ann Arbor, Mich.	WHRY	1600	A	Balesburg, S.C.	KMPK	1490		Big Stone Gap, Va.	WLSD	1220	
	KXRO	1320	M		WPAG	1050		Ballingier, Tex.	KBPM	1560	A		KOWL	1490	
Abilene, Tex.	KRBC	1470	A	Anna, Ill.	WRAJ	1440		Baltimore, Md.	KRBN	1400		Biloxi, Miss.	WLQX	1490	M
	KWBC	1340	M	Anniston, Ala.	WANA	1490	A		WBMD	750			WYMI	570	
Abingdon, Va.	WBBI	1230			WHMA	1450	A		WCAO	600	C	Billings, Mont.	KBMY	1240	M
Ada, Okla.	KADA	1230	A		WSPC	1470	M		WCBM	680	M		KGHL	1290	M
Adalusia, Ala.	WCTA	920		Anoka, Minn.	WADS	690			WCFB	1300	A		KODK	970	C
Adel, Ga.	WAAG	1470		Ansonia, Conn.	WATK	900			WISD	1230		Binghamton, N.Y.	KOYN	910	
Adrian, Mich.	WABJ	1490		Antigo, Wis.	WATP	900			WISD	1010			WINR	680	N
Ahoskie, N.C.	WRCS	970		Artesia, N.M.	KSPV	990	M		WITD	1010			WKPD	1360	M
Alken, S.C.	WAKN	990		Antigonish, N.S.	CJFX	580		Bangor, Maine	WABI	910	A		WBNF	1290	C
Akron, Ohio	WAKR	1590	A	Apollon, Pa.	WAVI	910			WGUY	1230	C	Birmingham, Ala.	WAPI	1070	C
	WACR	1350	C	Apple Valley, Cal.	WAVR	950			WLBZ	620	N		WBRG	960	N
	WCUE	1150		Appleton, Wis.	WAPL	1570		Banning, Calif.	WPAS	1490			WCRT	1260	
	WHKK	640	M		WHBY	1230	M	Barboursville, Ky.	WBVL	950			WELN	1210	
Alamogordo, N.M.	KALG	1230	M	Aguaquilla, P.R.	WABA	850		Bardstown, Ky.	WBRT	1320			WILD	850	M
Alamosa, Colo.	WALB	1590	M		WGRF	1340		Barnesboro, Pa.	WNCC	400			WLBS	900	
Albany, Ga.	WGPC	1450	C	Albemarle, N.Dak.	KZKY	1580		Barnwell, S.C.	WBAW	740			WSGN	610	A
	WJAZ	1050		Arcadia, Fla.	WAPG	1480		Barstow, Calif.	CKBB	1230		Bisbee, Ariz.	KSUN	1290	M
Albany, Minn.	KASM	1150		Arcata, Calif.	KENL	1340		Barstow, Calif.	KWTC	1230		Bishop, Calif.	KIBS	1230	
Albany, N.Y.	WABY	1400		Ardmore, Okla.	WCRN	1280	A	Bartlesville, Okla.	KWON	1400		Bishopville, S.C.	WAGS	1380	
	WOKO	1460	M	Arcelbo, P.R.	KVRC	1240	M	Bartow, Fla.	WBAR	1460		Bismarck, N.Dak.	KFYR	550	N
	WPTF	1540	M	Arkadelphia, Ark.	KSKO	1280		Bastrop, La.	WBYR	730		Bismarck-Mandan, N.Dak.	KGCU	1270	A-M
	WROW	580	A	Arlington, Va.	WARL	780		Batavia, N.Y.	WBTA	1490	M		KBOM	1270	M
Albany, Oreg.	WABZ	1010		Asbury Park, N.J.	WLJK	1310		Batesville, Ark.	WBLE	1290	M	Blackfoot, Idaho	KBLI	1490	M
Albermarle, N.C.	WABZ	1010		Asheboro, N.C.	WGVB	1250		Bathurst, N.B.	CKCG	1400		Blackstone, Va.	WKLV	1430	A
Albert Lea, Minn.	KATE	1450	A	Asheville, N.C.	WISF	1310	N	Batavia, N.Y.	WAIL	1460	A	Bloomington, Ill.	WJBC	1290	A
Albertville, Ala.	WAVU	630			WLOS	1380	N	Baton Rouge, La.	WEND	1380		Bloomington, Ind.	WCNR	930	
Albion, Mich.	WALM	1260			WSKY	1230			WIBR	1300		Bloomingsburg, Pa.	WHLM	550	
Albuquerque, N.M.	KABQ	1340	M		WWNC	570	C		WILS	910	A		WLTR	690	
	KDEF	1150		Ashland, Ky.	WCMI	1340	C	Battle Creek, Mich.	WXOK	1260			WHIS	1440	N
	KGGM	610	C		WTGR	1420			WBCK	930	M	Blythe, Calif.	KYOR	1250	M
	KOAT	860	A	Ashland, Ohio	WATG	1340	M		WELL	1400	A	Blytheville, Ark.	WLCN	1210	
	KOB	770	N	Ashland, Oreg.	KWIN	1400	M	Baxley, Ga.	WHAB	1260		Boalsus, La.	WIKC	1490	N
	KQUE	920		Ashland, Wis.	WATW	1400	M	Bay City, Mich.	WBOM	1440	A		WHXY	920	
	KLOS	1450		Astoria, Oreg.	KAST	1370	M	Bay City, Tex.	WJES	1250		Boise, Idaho	KBQI	950	C
	KHAM	1580		Atchinson, Kans.	KARE	1470		Bay Minette, Ala.	WBCA	1150			KIDO	630	N
Alexander City, Ala.	WRFS	1050		Atkins, Ala.	WJMW	730		Bayamon, P.R.	WENA	1560		Bonham, Tex.	KYME	740	
Alexandria, La.	KDBS	1410		Atkins, Ga.	WGAU	1340	C	Baytown, Tex.	KRCT	550		Boone, Iowa	KFGQ	1200	
	KVOB	970		Athens, Ohio	WRFC	960			KREL	1360			KBVG	1590	
Alexandria, Minn.	KXRA	1490		Athens, Tenn.	WATH	970		Beatrice, Neb.	KWBE	1450	M	Boone, N.C.	WATA	1450	
Alexandria, Va.	WPIK	730		Athens, Tex.	WOUB	1340		Beaufort, S.C.	WBMA	960		Booneville, Ind.	WBNI	1540	
Algonia, Iowa	WPKF	1800		Athens, Wis.	WLAR	1450	M	Beaufort, S.C.	WBEU	960		Booneville, Mo.	KWRT	1370	
Alieca, Tex.	KOPY	1070	M	Atlanta, Ga.	KBUD	1410		Beaumont, Tex.	KFDM	560	A	Booneville, Miss.	WBIP	1400	
Allegany, N.Y.	WHDL	1450	A		WAGA	590	C		KJET	1380			WBRY	900	
Allentown, Pa.	WHOL	1230	C		WAKE	1340	C		KRIC	1450		Boonville, N.Y.	KHUZ	1490	M
	WAEB	790	A		WQK	1380		Beaver Dam, Wis.	KTRM	990		Boston, Mass.	WBZ	1030	N
	WKAP	1320	N		WERD	860		Beaver Falls, Pa.	WBVP	1230			WCOP	1150	
Alliance, Neb.	WSAN	1470	N		WGKA	1600		Beckley, W. Va.	WJLS	560	C		WBMS	1090	
Alliance, Ohio	KCOW	1400			WGST	920	A		WWRN	620			WDBA	1260	A
Alma, Mich.	WFAH	1310			WQXT	790	M	Bedford, Ind.	WBNI	1340	M		WELI	590	C
Alpena Township, Mich.	WFYC	1280			WYBZ	1480	N	Bedford, Pa.	WBFD	1310			WMT	850	
	WATZ	1450	M	Atlanta, Tex.	KALT	900		Bedford, Va.	WBFL	1350	M		WMEX	1510	
Alpine, Tex.	KVLF	1240	M	Atlantic, Iowa	KJAW	1220		Bellefonte, Pa.	KBNG	1170	M		WORL	950	
Alton, Ill.	WOKZ	1570		Atlantic City, N.J.	WFPG	1450	C	Belleville, Tex.	WTRX	1290		Boulder, Colo.	KBOL	1490	
Altona, Man.	CFAM	1290			WLDB	1490		Bellevue, Ohio	WOHP	1390		Bowling Green, Kentucky	WKCT	930	A
Altonpa, Pa.	WFBG	1340	N	Atmore, Ala.	WATM	1550		Belle Glade, Fla.	WSWN	900			WBJI	1540	M
	WRTA	1240	A-M	Attleboro, Mass.	WABA	1320		Bellefonte, Ont.	CJBC	1230		Bowl Green, Ohio	WTB	730	
	WVAM	1430	C	Auburn, Ala.	WAUD	1230	A	Belleville, Ill.	KIBV	1250		Bowman, Conn.	WKNB	840	N
Alturas, Calif.	KCNO	570		Auburn, Calif.	KDIA	1490	A	Bellingham, Wash.	KVGO	790	A	Bozeman, Mont.	KXLL	1450	N
Altus, Okla.	KALV	1430		Auburn, N.Y.	WMBO	1340	M		KVGO	790	A		KBMN	1230	
Alva, Okla.	KAMQ	1010		Auburndale, Fla.	WTWB	1570		Belmont, N.C.	WCGC	1270		Bradbury Hots., Md.	WPGC	1580	
Amarillo, Tex.	KDAS	1440	N	Auburndale, Wis.	WLBL	930		Beloit, Wis.	WBEL	1380			WLOA	1550	
	KGNC	710	C	Augusta, Ga.	WBUG	1050			WGEZ	1490	M	Braddock, Pa.	WTRL	1490	
	KLYN	940	C		WBIA	1230		Belton, S.C.	WHPB	1390		Bradenton, Fla.	WESL	1490	
	KRAY	1360			WGAC	580	A	Bemidji, Minn.	KBUN	1450	M	Bradford, Pa.	WESL	1490	
	KZIP	1310			WRDW	1480	C	Bend, Oreg.	KBNB	1170	M	Brady, Tex.	KXLS	1490	
Americus, Ga.	WDEC	1290	M	Augusta, Maine	WRDO	1400	N	Bennington, Vt.	WBST	1550	M	Brainerd, Minn.	KLIZ	1380	M
Ames, Iowa	WOI	640			WFAU	1340	M	Benson, Minn.	KBMO	1290		Brampton, Ont.	CFJB	1090	
	WABL	1570		Aurora, Colo.	KQSI	1540	M	Benton, Ark.	KBBA	690		Brantford, Ont.	CKX	1150	
Amory, Miss.	WAMY	1580		Aurora, Ill.	WMBR	1280		Benton, Ky.	KBBA	690		Brantford, Ont.	CKPC	1360	
Amos, Que.	CHAD	1340		Austin, Minn.	KAUS	1480	A	Benton Harbor, Mich.	WCBL	1290			WTSA	1450	A
Amsterdam, N.Y.	WCSS	1490			KTBC	590	C		WHFB	1050		Brawley, Calif.	KROP	1300	A





Location	C.L. Ke. N.A.	Location	C.L. Ke. N.A.	Location	C.L. Ke. N.A.	Location	C.L. Ke. N.A.
Hawkinsville, Ga.	WCEH 610	Iron Mtn., Mich.	WMIQ 1450 A	Kingstree, S.C.	WKDK 1310	Lewiston, Maine	WCOU 1240 M
Hays, Kans.	WJAYS 1400	Iron River, Mich.	WIKB 1230 M	Kingsville, Tex.	KINE 330		WLAM 1470 A
Hazard, Ky.	WKIC 1430 M	Ironton, Ohio	WIRO 1230 M	Kinston, N.C.	WELS 1010	Lewiston, Mont.	WKXO 1230 M
Hazlehurst, Miss.	WHD 1420	Ironwood, Mich.	WJMS 630 M		WFTC 960 A	Lewiston, Pa.	WWRP 1490 N
Hazleton, Pa.	WAZI 1490 N-M	Ishpeming, Mich.	WJPD 1240		WNSP 1230	Lexington, Ky.	WLP 930 A
Helena, Ark.	KFFA 1360 M	Ithaca, N.Y.	WTKO 1470 C	Kirkland, Wash.	WIB 1050		WLEX 1300 M
Helena, Mont.	KCAP 1340			Kirkland Lake, Ont.			WVWK 590 M
	KXLI 1240 N	Jackson, Ala.	WPBB 1290				WVWK 1570
Hempstead, N.Y.	WHLI 1100	Jackson, Mich.	WIBM 1450 A	Kirksville, Mo.	CJKL 560	Lexington, Nebr.	KRVN 1010
Henderson, Ky.	WSON 860 M		WKHM 970 M	Kitchener, Ont.	CKCR 1490	Lexington, N.C.	WBUX 1440
Henderson, Nev.	KBM1 1400	Jackson, Miss.	WJDX 620 M	Klassimmo, Fla.	WRWB 1220	Lexington, Tenn.	WDXL 1490
	KR 1280		WJQS 1400 C	Kittanning, Pa.	WACB 1380	Lexington, Va.	WREL 1450 N
Henderson, N.C.	WHNC 890 M		WJXN 1450	Klamath Falls, Ore.		Lexington Park, Md.	KLCB 1330 M
	WHVH 1450		WOKJ 1590		KFLJ 1150 M	Liberal, Kans.	KSCB 1270
Henderson, Tex.	KGRI 1000	Jackson, Ohio	WRBC 1300 M		KFLW 1450 M	Liberty, N.Y.	WYOS 1240
	KWRD 1470	Jackson, Tenn.	WSLI 930 A	Knoxville, Tenn.	KLAD 900	Lihue, T.H.	KTOH 1490
Hendersonville, N.C.	WHKP 1450 A		WLMI 1280		WBIR 1250 M	Lima, Ohio	WIMA 1150 A
	WHEN 1590		WDXI 1310 N		WIBK 800	Lincoln, Ill.	WPRC 1370
Henryetta, Okla.	XHEN 880		WJAK 1460		WIVK 860	Lincoln, Nebr.	KFOR 1240 A
Hereford, Tex.	KPAL 860		WPLI 1490		WATE 620 N		KLIN 1400
Herkimer, N.Y.	WYAN 1420	Jacksonville, Fla.	WJAS 1390 A-N		WKGK 1340 M		KLMS 1480
Herkimer, N.Y.	KOHU 1570		WJHP 1320 M		WKXY 900		KLMS 1050 A
Herrin, Ill.	WJPF 1340 M		WJVS 1050		WNOX 990 C		CKLY 910
Hettinger, N.Dak.	KNDC 1490		WMBR 1460		WKOZ 1350 C		WBTO 1600
Hibbing, Minn.	WMTG 1240 N		WOBBS 1360		WLNH 1350		WSMI 1460
Hickory, N.C.	WHK 1290 A		WPDQ 600		WLBH 1410 N		WVLS 950
	WIBC 630 N	Jacksonville, Ill.	WRHC 1400		WLDL 1490 M		WVLS 1540
High Point, N.C.	WMFR 1230 A	Jacksonville, N.C.	WLOS 1180		WKTY 580 A		WVLS 1230 M
	WNOS 1050	Jacksonville, N.C.	WLNS 1240		WLDY 1340		WVLS 1490
	WHPE 1570	Jacksonville, N.C.	WLAS 910		WLFV 1590		WVLS 920 M
Hillsboro, Ohio	WSRW 1590	Jacksonville, Tex.	WKEB 1400		WLFY 1420 A		WVLS 1250 A
Hillsboro, Ohio	KUIK 1360	Jacksonville, Tex., Fla.	WKEB 1400		KVFL 1330 N		WVLS 1050
Hillsboro, Tex.	KRBR 880	Jamestown, N.Dak.	KEYJ 1400		WLFV 1450		WVLS 1440
Hillsdale, Mich.	WBBC 1340	Jamestown, N.Y.	KSBJ 600		WLRG 1450		WVLS 1090 C
Hilo, Hawaii	KHBC 970 C		WJTN 1240 A		WLAG 1240 M		WVLS 1050
	KILA 850	Jamestown, N.Y.	WJOC 1340 M		WTR 1300		WVLS 1150 M
	KTJS 1420	Janesville, Wis.	WCLO 1230 M		WTAQ 1300		WVLS 1250
Hobart, Okla.	KWEH 1480 M	Jasper, Ala.	WVWB 1380 M		KTED 1520		WVLS 1340
Hobbs, N.Mex.	KDJI 1270	Jasper, Ind.	WWTZ 890		KBNZ 1400		WVLS 1250
Hoboken, N.J.	KULA 890	Jasper, Tex.	WJAS 950		KLOU 1580 C		WVLS 1150
Holland, Mich.	WHTC 1450	Jefferson City, Mo.	WKIK 950		KPLC 1470 N		WVLS 1230 M
Hollywood, Fla.	WGMA 1320	Jennings, La.	WKWS 1240 M		KQAK 1400		WVLS 1130
Holyoke, Mass.	WREB 930	Jerome, Idaho	KJEF 1290		KLAF 1346		WVLS 1250
Homer, La.	KVHL 1320	Jesup, Ga.	KART 1400		WJOT 1260		WVLS 1570
Homestead, Pa.	WAMO 860	Johnson City, Tenn.	WBGR 1370		WLAK 1430 N		WVLS 610 M
Homewood, Ala.	WEZB 1320				WONN 1230 M		WVLS 1230 M
	WUBA 1400				KQIK 1230		WVLS 400
Honolulu, Hawaii	KGMB 580 C				WIFC 1280		WVLS 980
	KHON 1380				WIPR 1280		WVLS 1290
	KIKI 850				WJOP 1260		WVLS 1280
	KGU 760 N				WLAK 1430 N		WVLS 1050
	KHVV 1040				WONN 1230 M		WVLS 1280
	KPOA 630 M				KQIK 1230		WVLS 1280
	KR 1280				WIPR 1280		WVLS 1280
Hood River, Ore.	KIHR 1340				WJOP 1260		WVLS 1280
Hope, Ark.	KXAR 1490 M				WLAK 1430 N		WVLS 1050
Hopewell, Va.	WHAP 1340				WONN 1230 M		WVLS 1280
Hopkinsville, Ky.	WHOP 1230 C				KQIK 1230		WVLS 1280
	WKOA 1480				WIPR 1280		WVLS 1280
Hornell, N.Y.	WHHG 1320				WJOP 1260		WVLS 1280
	WLEA 1480 M				WLAK 1430 N		WVLS 1050
Hot Springs, Ark.	KWFC 1350 A-M				WONN 1230 M		WVLS 1280
	KBHS 590				KQIK 1230		WVLS 1280
	KBLO 1470				WIPR 1280		WVLS 1280
	WHDE 1400				WJOP 1260		WVLS 1280
Houghton, Mich.	WHGR 1290				WLAK 1430 N		WVLS 1050
Houghton Lake, Mich.	WVWB 1340				WONN 1230 M		WVLS 1280
Houlton, Maine	WVWB 1340				KQIK 1230		WVLS 1280
Houma, La.	KCIL 1490 N				WIPR 1280		WVLS 1280
Houston, Miss.	WCPC 1320				WJOP 1260		WVLS 1280
Houston, Tex.	KCOH 1430				WLAK 1430 N		WVLS 1050
	KLBS 610				WONN 1230 M		WVLS 1280
	KPUB 1230				KQIK 1230		WVLS 1280
	KPR 950 N				WIPR 1280		WVLS 1280
	KTRH 740 C				WJOP 1260		WVLS 1280
	KXYZ 1320 A				WLAK 1430 N		WVLS 1050
	KYOK 1590				WONN 1230 M		WVLS 1280
	WHMI 1350				KQIK 1230		WVLS 1280
	WHUC 1230				WIPR 1280		WVLS 1280
	WHUG 1340				WJOP 1260		WVLS 1280
	WHUL 970				WLAK 1430 N		WVLS 1050
	WHUR 740				WONN 1230 M		WVLS 1280
	WHUN 1150				KQIK 1230		WVLS 1280
	WPLH 1470				WIPR 1280		WVLS 1280
	WHTN 800				WJOP 1260		WVLS 1280
	WSAZ 930 A				WLAK 1430 N		WVLS 1050
Huntsville, Ala.	WBHP 1230 M				WONN 1230 M		WVLS 1280
	WFUN 1450				KQIK 1230		WVLS 1280
	WHBS 1550 A				WIPR 1280		WVLS 1280
	WKAM 1490 M				WJOP 1260		WVLS 1280
Huntsville, Tex.	KIJS 1340 N-M				WLAK 1430 N		WVLS 1050
Huron, S.Dak.	KIJJ 1340 N-M				WONN 1230 M		WVLS 1280
Hutchinson, Kan.	KWHK 1250				KQIK 1230		WVLS 1280
Hutchinson, Minn.	KDUZ 1260				WIPR 1280		WVLS 1280
Idabel, Okla.	KBEL 1240				WJOP 1260		WVLS 1280
Idaho Falls, Idaho	KID 590 C				WLAK 1430 N		WVLS 1050
	KIFI 1060 A-M				WONN 1230 M		WVLS 1280
Independence, Kans.	KIND 1010 M				KQIK 1230		WVLS 1280
	KIMO 1510				WIPR 1280		WVLS 1280
Independence, Mo.	WDAD 1450 C				WJOP 1260		WVLS 1280
Indiana, Pa.	WFBN 1260 C				WLAK 1430 N		WVLS 1050
Indianapolis, Ind.	WGEE 1590				WONN 1230 M		WVLS 1280
	WIBC 1070 M				KQIK 1230		WVLS 1280
	WIRE 1430 N				WIPR 1280		WVLS 1280
	WXLW 950				WJOP 1260		WVLS 1280
Indianola, Miss.	WNL 1390				WLAK 1430 N		WVLS 1050
Indio, Calif.	KREO 1400 A				WONN 1230 M		WVLS 1280
Inkster, Mich.	WCHB 1440				KQIK 1230		WVLS 1280
Ionia, Mich.	WION 1430				WIPR 1280		WVLS 1280
Iowa City, Iowa	KXIC 800				WJOP 1260		WVLS 1280
	WSUI 910				WLAK 1430 N		WVLS 1050
					WONN 1230 M		WVLS 1280
					KQIK 1230		WVLS 1280
					WIPR 1280		WVLS 1280
					WJOP 1260		WVLS 1280
					WLAK 1430 N		WVLS 1050
					WONN 1230 M		WVLS 1280
					KQIK 1230		WVLS 1280
					WIPR 1280		WVLS 1280
					WJOP 1260		WVLS 1280
					WLAK 1430 N		WVLS 1050
					WONN 1230 M		WVLS 1280
					KQIK 1230		WVLS 1280
					WIPR 1280		WVLS 1280
					WJOP 1260		WVLS 1280
					WLAK 1430 N		WVLS 1050
					WONN 1230 M		WVLS 1280
					KQIK 1230		WVLS 1280
					WIPR 1280		WVLS 1280
					WJOP 1260		WVLS 1280
					WLAK 1430 N		WVLS 1050
					WONN 1230 M		WVLS 1280
					KQIK 1230		WVLS 1280
					WIPR 1280		WVLS 1280
					WJOP 1260		WVLS 1280
					WLAK 1430 N		WVLS 1050
					WONN 1230 M		WVLS 1280
					KQIK 1230		WVLS 1280
					WIPR 1280		WVLS 1280
					WJOP 1260		WVLS 1280
					WLAK 1430 N		WVLS 1050
					WONN 1230 M		WVLS 1280
					KQIK 1230		WVLS 1280
					WIPR 1280		WVLS 1280
					WJOP 1260		WVLS 1280
					WLAK 1430 N		WVLS 1050
					WONN 1230 M		WVLS 1280
					KQIK 1230		WVLS 1280
					WIPR 1280		WVLS 1280
					WJOP 1260		WVLS 1280
					WLAK 1430 N		WVLS 1050
					WONN 1230 M		WVLS 1280
					KQIK 1230		WVLS 1280
					WIPR 1280		WVLS 1280
					WJOP 1260		WVLS 1280
					WLAK 1430 N		WVLS 1050
					WONN 1230 M		WVLS 1280
					KQIK 1230		WVLS 1280
					WIPR 1280		WVLS 1280
					WJOP 1260		

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Magnolia, Ark.	KVMA 630 M	Miami, Fla.	WFEC 1220	Moultrie, Ga.	WMTM 1300	New Rochelle, N.Y.	WNRC 1460
Malden, Mo.	KTCB 1470	MIAMI 1140	WMBE 1140	Moundsville, W.Va.	WMOD 1370	New Smyrna Beach, Fla.	WSBB 1230
Malone, N.Y.	WCIY 1480 M	WQAM 560 A	WSKB 1450	Mountain Grove, Mo.	KLRS 1360	Newton, Iowa	KQGB 1280
Malvern, Ark.	KBOK 1370	WINZ 940	WZBK 1450	Mt. Airy, N.C.	WVAG 740	Newton, Kans.	KJRG 950
Marion, Va.	KDAS 1420	KGCL 910	WZLN 940	Mt. Carmel, Ill.	WWSI 1300	Newton, Miss.	WEGA 1410
Manchester, Ky.	WMEV 1010 A	WHRH 1490	WZLN 940	Mt. Clemens, Mich.	WVMC 1360	Newton, N.C.	WNNC 1360
Manchester, N.H.	WWEA 1580 C	WKAT 1360 M	WZLN 940	Mt. Vernon, Ky.	WVRK 1460	New Ulm, Minn.	KNUJ 860
	WGR 610	WBBM 800	WZLN 940	Mt. Vernon, Ohio	WVVO 1300	New Westminster, B.C.	CKNW 1320
	WKBR 1240	WIMS 1420	WZLN 940	Mt. Vernon, Wash.	KBRC 1430	New York, N.Y.	WABC 770 A
	WUR 610 A-M	WIMK 560	WZLN 940	Mt. Pleasant, Mich.	WCEN 1150		WABC 770 A
Manhattan, Kans.	KCAC 580	WCN3 1150	WZLN 940	Mt. Pleasant, Tex.	WIMP 960		WCSB 880 C
	KMAN 1350	WALL 1340	WZLN 940	Mt. Shasta, Calif.	KWSD 1340		WEVD 1330
Manila, P.I.	DZPI 1800 M-C	WPF6 1150	WZLN 940	Mt. Vernon, Ind.	WPCO 1590		WHOM 1480
	DZRH 710 M	WPDN 950	WZLN 940	Mt. Vernon, Ky.	WVRK 1460		WINS 1010
Manitowish, Mich.	WMTA 1340	WZLN 940	WZLN 940	Mt. Vernon, Ohio	WVVO 1300		WLIB 1190
Manitowish, Wis.	WVOC 980	KJCB 1150	WZLN 940	Mt. Vernon, Ohio	WVVO 1300		WMCA 570
	WQMT 1240 M	WKBJ 1600	WZLN 940	Mt. Vernon, Wash.	KBRC 1430		WMGO 1050
	KYSM 1230 N	KRJJ 1340 M	WZLN 940	Muleshoe, Tex.	KMUL 1380		WNEH 1130
	WZLN 1420 A	KATL 1340	WZLN 940	Mullins, S.C.	WLBY 1280		WVVO 830
Mansfield, La.	KDBC 1360	WKBS 930	WZLN 940	Murfreesboro, Tenn.	WVMS 1450		WOR 710 M
Mansfield, Ohio	WMAN 1400 A	WMOO 1480	WZLN 940	Murphy, Ga.	WVMS 1450		WOY 1280
Marianna, Fla.	WTYS 1340 M	WMLV 1440	WZLN 940	Murphy, Ga.	WVMS 1450		WQXR 1560
Marietta, Ga.	WFOM 1230	WMLV 1440	WZLN 940	Murphy, Ga.	WVMS 1450		WRCA 660 N
	WBIE 1050	WMLV 1440	WZLN 940	Murphy, Ga.	WVMS 1450		
Marietta, Ohio	WMOA 1490 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marine City, Mich.	WSDC 1590	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marquette, Wis.	WMFM 1310	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marion, Ala.	WJAM 1310	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marion, Ill.	WGGH 1150	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marion, Ind.	WBAT 1400 C	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WMRI 860	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marion, N.C.	WBRM 1250	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marion, Ohio	WMRN 1490	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marion, Va.	WMEV 1010 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marked Tree, Ark.	WKFY 1580 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marksville, La.	KAPB 1370	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marlin, Tex.	KMLW 1010	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marquette, Mich.	WDMJ 1320 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marshall, Minn.	KMHL 1400 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marshall, Mo.	KMMO 1300	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marshall, N.C.	WMMH 14670	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marshall, Tex.	KMFL 1450 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marshalltown, Iowa	KFBJ 1230 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marshfield, Wis.	WDLB 1450	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Martinsburg, W.Va.	WEPM 1340 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WHEE 1370	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Martinsville, Va.	WVVA 1450 N	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KMZY 1410 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marysville, Calif.	KMZY 1410 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marysville, Kans.	KMZY 1410 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marysville, Mo.	KNIM 1580	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Marysville, Tenn.	WGAP 1400	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Mason City, Iowa	KGLO 1300 C	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KRIB 1490 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KSMN 1010	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Massena, N.Y.	WMSA 1340	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Massillon, Ohio	WTTG 1370	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Matane, Que.	KCF 1250	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Matawan, W.Va.	WHJC 1360	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Mattoon, Ill.	WLBH 1170	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Mayaguez, P.R.	WAEI 500	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WKJB 710	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WORA 1150	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WVOC 980	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WTIL 1300	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Mayfield, Ky.	WKTM 1050 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WNGO 1320	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Maysville, Ky.	WFTM 1240 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McAlester, Okla.	KTMC 1400 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KNEB 1130	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McAllen, Tex.	KRIG 910 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McComb, Miss.	WNNY 1250 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WAFP 980	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McCook, Neb.	KBRL 1300 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McGehee, Ark.	KVSA 1220	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McKeesport, Pa.	WEDO 810	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WMCK 1360	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McKenzie, Tenn.	WVOC 980	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McKinney, Tex.	KMAE 1600	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McMinnville, Ore.	KMCM 1260	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McMinnville, Tenn.	WBMC 960	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WMMT 1230 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
McPherson, Kans.	KNEK 1540	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Meadville, Pa.	WGMV 1490 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Medford, Mass.	WHIL 1430	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Medford, Ore.	KMED 1440 N	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KBOY 730	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KYJC 1230 A-C	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Medford, Wis.	WIGM 1490 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Medicine Hat, Alta.	CHAT 1270	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Melbourne, Fla.	WMBB 1240	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Memphis, Tenn.	WHBQ 560 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WHBY 1430	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WMC 790 N	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WDIA 1070	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WMPS 680 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WHHH 1340	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WLK 1480	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WFEC 600	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WVOC 980	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Mena, Ark.	KENA 1450 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Menominee, Mich.	WAGN 1340 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Menomonie, Wis.	WMMN 1360	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Merced, Calif.	KYOS 1480 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WKIP 1580	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Meriden, Conn.	WMMW 1470	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Meridian, Miss.	WOC 910 C	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WMOX 1240 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WQKK 1450 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KTYL 1310	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Mesa, Ariz.	KBUS 1590	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Mexia, Tex.	KXED 1340	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Mexico, Mo.	WUN 1220	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Mexico, Pa.	GBS 710 C	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
Miami, Fla.	WCKR 810 N	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WFEC 1220	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WMBE 1140	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WQAM 560 A	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WSKB 1450	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WINZ 940	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KGCL 910	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WHRH 1490	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WKAT 1360 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WBBM 800	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WIMS 1420	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WIMK 560	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WCN3 1150	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WALL 1340	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WPF6 1150	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WPDN 950	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WZLN 940	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KJCB 1150	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	WKBJ 1600	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KRJJ 1340 M	WMLP 1570	WZLN 940	Murphy, Ga.	WVMS 1450		
	KATL 134						

Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.	Location	C.L. Kc. N.A.
Opportunity, Wash.	KZUN 1270	Philadelphia, Pa.	WPN 950	Prineville, Oreg.	KRCO 690	Rochester, N.Y.	WSAY 1370
Orange, Mass.	WGAT 1390		WRVC 1060	Proser, Wash.	KARY 1310		WVET 1280 A-M
Orange, Tex.	KOJT 1600		WTEL 860	Providence, R.I.	WHIM 1110	Rochester, Pa.	WRYO 1050
Orange, Va.	WJMA 1340 M	Phillipsburg, Pa.	WPHB 1200		WICE 1290	Rockford, Ill.	WRON 1440 A
Orangeburg, S.C.	WDIX 1450 A-M	Phoenix, Ariz.	KIFN 860		WJAR 920 N	Rock Hill, S.C.	WRHI 1340 M
	WRNO 1150 A-M		KHEP 1280		WPRO 630 C		WYTC 1150
	WTNO 920		KOH 550 M	Provo, Utah	WRIB 1220	Rockingham, N.C.	WAYC 1150
Oregon City, Oreg.	KGO 1350		KOOL 620		KIXX 1400	Rock Island, Ill.	WRFD 1270 C
Orilla, Ont.	CFOR 1570		KPHD 910 A		KWXR 1450	Rockland, Maine	WRBK 1450 A
Orlando, Fla.	WDBD 580 C		KRIZ 1230		KOVQ 960 M	Rock Springs, Wyo.	KVRS 1360 M
	WHOO 990 A		KTAR 620 N	Pryor, Okla.	KOLS 1570	Rockville, Md.	WRKH 580
	WLOF 950 M	Picayune, Miss.	WRJW 1320	Pueblo, Colo.	KOZA 1230	Rockwood, Tenn.	WRKH 580
	WORZ 740 N	Piedmont, Ala.	WPID 1280		KFEI 970	Rocky Ford, Colo.	KRFC 1320
Oroville, Calif.	KMOR 1340	Pierre, S.Dak.	KGFS 630		KGHF 1350 A	Rocky Mount, N.C.	WCFC 810
Oroville, Minn.	KDIO 1350	Pikeville, Ky.	WLSI 900		KCSR 590 A		WEED 1390 A
Osgage Bch., Mo.	KRMS 1240		WPKE 1240	Pulaski, Tenn.	WVUW 1580 N	Rocky Mount, Va.	WYTI 1570
Oseola, Ark.	KOSE 890		KCLA 1400	Pulaski, Va.	KWSC 1250	Rogers, Ark.	KAMD 1390
Oshawa, Ont.	CKLB 1240		KOTN 1490 M	Pullman, Wash.	KOFE 1150	Rogers City, Mich.	WHAK 950
Oshkosh, Wis.	WOSH 1490 A		WMLF 1230	Punxsutawney, Pa.	WPXJ 1300 M	Rogersville, Tenn.	WRGS 1370
Ossa, Iowa	KBOE 740	Plaineville, Ky.	WWYO 970		WPCT 1350	Rolla, Mo.	KTRR 1490
Ottawa, Ill.	WCMY 1430	Plaineville, W.Va.	KLOH 1050		KATJ 1450	Rollins, Wis.	WTKR 900
Ottawa, Kans.	KOFO 1220	Piqua, Ohio	WPTD 1570		KYJE 980	Rome, Ga.	WLAQ 1410 A
Ottawa, Ont.	CBQ 910	Pittsburg, Calif.	KECC 990		CBV 980		WRGA 1470 M
	CFRA 560	Pittsburg, Kans.	KOAM 860 N		CHRC 800	Rome, N.Y.	WRON 710
	CKOY 1310		KDKA 1020 N		CJQC 1340	Roseburg, Ore.	WRON 1350
Ottumwa, Iowa	KBIZ 1240 M		KQV 1410 C		CKCV 1280		KRRR 1490C-M
	KLEE 1480		WCAE 1250 A	Quincy, Fla.	WGNH 1230 M		KRLX 1240
	KRFQ 1390		WJAS 1320 M	Quincy, Ill.	WGEM 1440	Rosenberg, Tex.	KFRD 980
Owensboro, Ky.	WDMI 1490 M		WJAS 1320 M		WJQA 1300	Roswell, N.Mex.	KSWB 1230 A
	WJIS 1420		WPIT 730		WSFB 1490		KGFL 1400 M
Owen Sound, Ont.	CFOS 1470		WBBA 1580		WRIN 1400 A		KBIM 910
Oxford, Mich.	WOAP 1080	Pittsfield, Ill.	WBEC 1420 A		WSAC 1470		CKRM 1450
Oxford, Miss.	WOXF 1340	Pittsfield, Mass.	WBRK 1340 M		WRAD 1460	Rouyn, Que.	WRXO 1430
Oxford, N.C.	WOXF 1340		WPTD 1570		WRAD 1460	Royal Oak, Mich.	WEXL 1340
Oxnard, Calif.	KOXR 910	Pittsfield, Pa.	WPIT 730		WRAD 1460	Rumford, Me.	WRUM 790
Ozark, Ala.	WOZK 900	Plainview, Tex.	KVOP 1400 M		WTFE 680 N	Rupert, Idaho	KAYT 970
Paducah, Ky.	WKYV 570 N	Plant City, Fla.	WPLA 910		WMSN 570	Rushon, La.	KRUS 1490
	WPAD 1450 C	Platteville, Wis.	WSEW 1590		WRLA 1240 M	Rusk, Texas	KTLU 1580
	WPVL 1460	Plattsburgh, N.Y.	WEAV 960 A		KOTA 1380 C	Russell, Kans.	KRUS 990
Painesville, Ohio	WSPJ 1490 A		WIRY 1340 M	Rapid City, S.Dak.	KRSD 1340 M	Russellville, Ala.	WVWR 920
Paiskatka, Fla.	WPAT 1260	Pleasanton, Tex.	KBOJ 1380		KRAN 1490 M	Russellville, Ark.	KXRI 1490 M
Palatine, Ill.	KNET 1450	Pleasantville, N.J.	WPLM 1390		KAPA 1340	Russellville, Ky.	WRUS 800
Palmetto, Fla.	WQXT 1340 A	Plymouth, Mass.	WPLY 1420		WUUU 850 A	Rutland, Vt.	WSYB 1380 M
Palm Bch., Fla.	KCMJ 1340 C	Plymouth, Wis.	WPLY 1420		WHUM 1240	Sackville, N.B.	CBA 1070
Palm Sprngs., Calif.	KDES 920	Pocahontas, Ark.	KPOC 1420		WRWA 1340 N	Sacramento, Calif.	KSTN 1420 N
	KPAL 1450	Pocatello, Idaho	KEYY 1240 M		KRDG 1230		KFBK 1530 A
Palo Alto, Calif.	KIBE 1220		KSEI 930 N	Red Bluff, Calif.	KSA 1400		KGMS 1380
Pampa, Tex.	KPAT 1340 M	Pocomoke City, Md.	WDMV 540		KVCY 670 C		KROY 1240 C
	WPAT 1340 M	Pomona, Calif.	KWOW 1600	Red Deer, Alta.	KBFL 1490	Safford, Ariz.	KXOA 1470 M
Pañama City, Fla.	WDLP 580 N	Ponca City, Okla.	WBBZ 1230 M	Redlands, Calif.	CKRD 850	Saginaw, Mich.	KGLU 1480 N
	WPFC 1400 A-M	Ponce, P.R.	WPRP 910	Red Lion, Pa.	KCAL 1410		KWLN 1210
Paragould, Ark.	KDRS 1490		WPAB 550	Redmond, Oreg.	WGCB 1440		WVSR 970 M
Paris, Ill.	WPRS 1440		WLEO 1170	Red Wing, Minn.	KJUN 1240 A	St. Albans, Vt.	WRSR 1420
Paris, Ky.	WKLX 1440		WLOD 1280	Redwood Falls, Minn.	KSGA 1240	St. Albans, Vt.	WVSR 1420
Paris, Tenn.	WTPR 710 M		WPON 1460		KLGR 1490	St. Anne de la	WVSR 1420
Paris, Tex.	KPLT 1490 A	Portage, Mich.	WPOR 1350		WRDB 1400	Pocatigue, Que.	CHQB 1350
	KFTV 1250	Portage, Wis.	WPOR 1350	Reedsburg, Wis.	CKBK 540	St. Augustine, Fla.	WFOY 1240 C
Parkersburg, W.Va.	WCEF 1450	Port Arthur, B.C.	CFRY 1570	Regina, Sask.	CKBK 620	St. Boniface, Man.	CKSB 1250
	WCOM 1230 A	Portales, N.Mex.	CJAV 1240	Reidsville, N.C.	CKRM 980	St. Catharine, Ont.	CKTB 620
	WFPF 1450	Port Angeles, Wash.	KONF 1450		WRE 1220 A	St. Cloud, Minn.	KFAM 1450 N
Parsons, Kans.	KLKC 1540	Port Arthur, Tex.	CFPA 1230	Reno, Nev.	KOH 630 N		WJON 1240 A
Pasadena, Calif.	KALI 1430	Port Arthur, Tex.	KOLE 1340		KATO 1340 M	St. Jean, Que.	CHRS 1090
	KPPC 1240	Portersville, Calif.	KPCAC 1250 M		KOLO 920 C	St. Jerome, Que.	CKJL 900
	KKLA 1110	Port Huron, Mich.	WHL 1450 M		KONE 1450	Saint John, N.B.	CFB 830
	KWKW 1300	Port Jervis, N.Y.	WTH 1380	Renton, Wash.	KWRN 1230 A	St. John, V.I.	WDTV 1190
Pasadena, Tex.	KLVJ 1480	Portland, Ind.	WPW 1440	Reuburg, Idaho	KWLC 910	St. John's, Nfld.	CBN 640
Pasagoula, Miss.	WPMP 1580	Portland, Maine	WGAN 560 C	Rhineclander, Wis.	CKRX 1230		CJON 930
Pasco, Wash.	KORD 910		WCSH 970 N	Rice Lake, Wis.	WOBT 1240 M		VOCR 1230
	KPKW 1340 A		WGAN 560 C	Richfield, Utah	KVC 980 M	St. Johnsbury, Vt.	WVOR 800
Paseo, Wash.	KPKW 1340 A		WDOB 1310	Richland, Wash.	KAYE 960	St. Joseph, Mich.	WTWN 1340
	KPRL 1230 M	Portland, Oreg.	WPOR 1490 A-M	Richland, Wis.	WRCD 1450	St. Joseph, Mo.	KFEQ 680 A-M
	WALK 1370		KBPS 1450	Richland, Va.	WRIC 1320		KRES 1550 M
Paterson, N.J.	WPA 930		KEX 1190	Richmond, Ind.	WBKY 1490 A	St. Joseph d'Alma, Que.	KUN 1270
Pauls Valley, Okla.	KVLH 1470		KGIN 970 C	Richmond, Ky.	WEKY 1340		CFPT 1270
Pawtucket, R.I.	WPWA 550		KPM 1410	Richmond, Va.	WENT 990	St. Louis, Mo.	KATZ 1600
Peace River, Alta.	CKYL 630		KPDQ 800		WBLL 1480 M		KFUD 850
Pecos, Tex.	KIUN 1400 M		KPOJ 1350 M	Richmond Hill, Ont.	WLLY 1320		KMDX 1120 C
Peekskill, N.Y.	WLNA 1420	Portsmouth, N.H.	KWJ 1080	Ridgecrest, Calif.	WMB 1350 N		KSD 550 N
Pekin, Ill.	WFHK 1430	Portsmouth, Ohio	KXL 750		WRNL 910 A		KSTL 690
Pell City, Ala.	CHOV 1350		WHEB 750 M	Richmond, N.C.	WRXA 1140 C		KWK 1380 M
Pembroke, Ont.	KWRC 1240 A	Portsmouth, Va.	WLOW 1400	Ridgester, Calif.	WVGI 950		KXOK 630 A
Pendleton, Oreg.	KUBE 1050		WWSA 1350 M	Rilmouski, Ky.	CKRS 1240	St. Mary's, Pa.	WEL 770
	KUMA 1290	Post, Tex.	KWJ 1080	Rio Piedras, P.R.	CKRS 1240	St. Paul, Minn.	KSTP 1500 N
	WBOP 980	Potsdam, N.Y.	KXJ 750	Ripley, Tenn.	WVW 1520		WFSK 1890
	WBSR 1450 C-M	Pottstown, Pa.	WPAZ 1370	Riverhead, N.Y.	WTRB 1570	St. Peter, Minn.	WFB 1310
	WEAR 1230 A	Pottsville, Pa.	WPAM 1450 M	Riverside, Calif.	WRIV 1390	St. Petersburg, Fla.	WSUN 620 A
	WCOA 1370 N	Poughkeepsie, N.Y.	WPPA 1360	Riverton, Wyo.	KPRO 1440		WTSP 1380 M
Pentleton, B.C.	CKOK 800		WPK 1450 A	Riviere du Loup, Que.	KWRL 1450 A		CKLO 680
Peoria, Ill.	WEEK 1350 N	Powell, Wyo.	KPOW 1280 M	Roanoke, Ala.	CJPF 1400	St. Genevieve, Mo.	CHGM 980
	WMBD 1470 C	Poynter, Wis.	WIBU 1240	Roanoke, Va.	WELR 1360	Salem, Ill.	WJBD 1350
	WIRL 1290 A-M	Prairie du Chien, Wis.	WPRE 980		WDBJ 960 C	Salem, Mass.	WELN 1220
	WPEO 1020		KYCA 1490 N		WRIS 1410	Salem, Mo.	KSMO 1340
Perry, Fla.	WPRY 1400	Pratt, Kans.	KWSK 1570		WRKE 910	Salem, Oreg.	KSLM 1390 M
Perry, Ga.	WBBN 980	Prescott, Ariz.	KYCA 1490 N		WVRO 1240 A-M		KBZY 1490
Perryton, Tex.	WPRY 1400	Presque Isle, Me.	WAGM 1420	Roanoke Rapids, N.C.	WCBT 1230 M	Saldia, Colo.	KVRH 1340
Perru, Ind.	WARU 1600	Preston, Idaho	KPST 1340	Roaring Sprngs., Pa.	WKMC 1370	Salina, Kans.	KSLR 1150 M
Petaluma, Calif.	KAFP 1490	Prestronburg, Ky.	WPRT 1270	Roberval, Que.	CHRL 910	Salinas, Calif.	KDON 1460
Peterborough, Ont.	CHEX 1430	Price, Utah	KOAL 1230 M	Robinson, Ill.	WTAY 1570		KBSW 1380 M
Petersburg, Va.	WSSV 1240 M	Richard, Ala.	WAIP 1270	Rochester, Minn.	KROC 1340	Salisbury, Md.	WBCC 960 M
Petoskey, Mich.	WMBN 1340 M	Prince Albert, Sask.	CKBI 900	Rochester, N.H.	KRCS 1340	Salisbury, N.C.	WICO 1320
Phenix City, Ala.	WPNX 1270 M	Prince George, B.C.	CKPG 550	Rochester, N.Y.	WBF 950 M		WSAT 1490 M
Philadelphia, Miss.	WHOC 1490	Prince Rupert, B.C.	CFPR 1240		WHAM 1180 N		WSAT 1280 A
Philadelphia, Pa.	WDS 1210 C	Princeton, Ind.	WRAY 1250		WHEC 1160 C	Salt Lake City, Utah	KALL 910 M
	WDFL 560 A	Princeton, Ky.	WRKY 1580		WRNY 680		
	WHAT 1340	Princeton, W.Va.	WLOH 1490 A				
	WIBG 990						
	WIP 610 M						
	WJMJ 1500						





**Kc. C.L. Location**

6120 HC2FB Guayaquil, Ecu. 6120 ZJ14 Limassol, Cyprus 6120 Tangler, Tangler 6120 WRCA New York, U.S.A. 6122 HP5H Panama, Pan. 6124 HRQ San Pedro Sula, Hond. 6125 GWA London, England 6130 XUZ Mexico, U.S.S.R. 6130 COCO Havana, Cuba 6130 Port Moresby, New Guinea 6135 HJED Cali, Colombia 6140 Munich, Germany 6145 HJDE Medellin, Col. 6147 PRL9 Rio de Janeiro, Br. 6150 GRW London, England 6150 GRAZ Guatemala, Guat. 6160 HJKJ Bogota, Colombia 6160 Honolulu, Hawaii 6160 Munich, Germany 6165 GWK London, England 6165 HER3 Bern, Switzerland 6167 4VCH Port-au-Prince, H. 6170 Munich, Germany 6170 GSZ London, England 6170 KCBR Delano, Cal., U.S.A. 6170 YKBO Caracas, Venez. 6172 ZJMS Limassol, Cyprus 6175 XEXA Mexico, Mex. 6180 LRM Mendoza, Argentina 6180 Askabad, U.S.S.R. 6180 GRAZ London, England 6182 TGWB Guatemala, Guat. 6185 KRCA San Fran., U.S.A. 6185 HJCT Bogota, Colombia 6190 Frankfurt, Germany 6190 HIBT Puerto Plata, D.R. 6190 WLWD Cincinnati, U.S.A. 6190 WRCA New York, U.S.A. 6195 GRN London, England 6195 Honolulu, Hawaii 6200 Paris, France 6215 SP13 Warsaw, Poland 6235 HRD2 La Ceiba, Hond. 6235 Karachi, Pakistan 6248 Budapest, Hungary 6285 TGTQ Guatemala, Guat. 6295 DTM1 Leopoldville, Belgian Congo

6295 TGLA Guatemala, Guat. 6320 Baden-Baden, Germany 6322 COCV Havana, Cuba 6335 TGT A Guatemala, Guat. 6351 HRP1 San Pedro Sula, Hond. 6374 CSA21 Lisbon, Port. 6405 TGQA Quetzaltenango, Guat. 6632 HC2RL Guayaquil, Ecu. 6450 COCV Santa Clara, Cuba 6660 HRD9 Tegucigalpa, Hond. 6758 NYVP New York, U.S.A. 6790 ZJMS Limassol, Cyprus 6830 4XB21 Tel Aviv, Israel 6870 HC4EB Manta, Ecuador 7105 Paris, France 7112 CR4AA Praia, Cape V. Isla. 7120 GRN London, England 7135 EED7 New York, U.S.A. 7135 MCM London, England 7145 Radio Free Europe, Lisbon, Portugal

7145 Radio Free Europe 7150 GRT London, England 7165 Moscow, U.S.S.R. 7175 VUD Delhi, India 7180 JOA Tokyo, Japan 7185 GRK London, England 7200 GWZ London, England 7205 Warsaw, Poland 7210 GWL London, England 7210 HE13 Bern, Switzerland 7222 Budapest, Hungary 7230 GSW London, England 7240 Moscow, U.S.S.R. 7240 Paris, France 7250 GWI London, England 7257 JKH Tokyo, Japan 7260 GSU Cambridge, England 7280 Moscow, U.S.S.R. 7280 GWN London, England 7285 JKI Tokyo, Japan 7285 TAS Ankara, Turkey 7290 Hamburg, Germany 7290 VUD Delhi, India 7295 Moscow, U.S.S.R. 7300 Radio Free Europe, Munich, Germany

7300 SVD2 Athens, Greece 7315 YSO San Salvador, Salv. 7320 GRJ London, England 7335 EC36E Taipei, Formosa 7360 Moscow, U.S.S.R. 7670 Sofia, Bulgaria 7850 ZAA Tirana, Albania 7865 SPX Carlo, Egypt 7933 HLKA Pusan, S. Korea 7951 Alicante, Spain 8036 FCE Beirut, Lebanon 8664 COJK Camaguey, Cuba 8825 COC Havana, Cuba 8955 COC Santiago, Cuba 9007 Voice of Zion, Tel Aviv, Israel

9026 COBZ Havana, Cuba 9236 COBQ Havana, Cuba 9252 Bucharest, Rumania 9290 PRN9 Rio de Janeiro, Brazil

9316 LRS Buenos Aires, Arg. 9340 OAX4J Lima, Peru

**Kc. C.L. Location**

9363 COBC Havana, Cuba 9369 Madrid, Spain 9380 Khabarovsk, U.S.S.R. 9400 OTM2 Leopoldville, Belgian Congo

9410 GRI London, England 9440 Brazzaville, Fr. Eq. Africa 9452 LRY1 Buenos Aires, Arg. 9463 TAP Ankara, Turkey 9480 Moscow, U.S.S.R. 9490 KUJ39 Agana, Guam. 9500 XEWW Mexico, Mex. 9504 DLR3B Prague, Czech. 9505 MDL3A Colon, Panama 9505 MDL3A Kowachi, Japan 9510 VYHJ Barquisimeto, Ven. 9510 GSB London, England 9515 KRCA San Fran., Calif. 9515 TAT Ankara, Turkey 9520 Colombo, Ceylon 9520 HJKF Bogota, Colombia 9520 OFZ Frankfurt, Denmark 9520 VLT9 Port Moresby, British New Guinea

9520 WLWO Cincinnati, U.S.A. 9525 GWJ London, England 9525 ZBW3 Victoria, Hong Kong 9527 Warsaw, Poland 9530 Honolulu, Hawaii 9535 Manila, Philippines 9530 KCBR Delano, Cal., U.S.A. 9530 WABC New York, U.S.A. 9535 WGEO Schenectady, U.S.A. 9535 COCO Havana, Cuba 9535 HER4 Bern, Switzerland 9535 SBU Stockholm, Sweden 9540 GSW London, England 9540 VL99 Melbourne, Aus. 9540 ZL2 Wellington, N. Zeal 9543 XYZ Rangoon, Burma 9548 XEFT Vera Cruz, Mex. 9550 HVI Vatican City 9550 Paris, France 9550 LRB3 Prague, Czech. 9555 OIX2 Porv, Finland 9555 XETT Mexico, Mex. 9560 JBD2 Kowachi, Japan 9560 London, England 9560 Paris, France 9560 Tangler, Tangler 9560 WLWD Cincinnati, U.S.A. 9830 WRCA New York, U.S.A. 9565 Kosmosol, U.S.S.R. 9565 ZYK3 Recife, Brazil 9570 Algiers, Algeria 9570 GWX London, England 9570 KUID San Fran., U.S.A. 9570 JKL2 Tokyo, Japan 9570 Bucharest, Rumania 9575 Rome, Italy 9580 GSC London, England 9580 VLB9 Shepparton, Aus. 9585 Madrid, Spain 9590 CJ Hilversum, Neth. 9590 WBC New York, U.S.A. 9600 GRV London, England 9600 KCBR Delano, Cal., U.S.A. 9600 KRCA San Fran., U.S.A. 9600 Leningrad, U.S.S.R. 9605 HP3 Panama, Pan. 9605 JKL2 Tokyo, Japan 9605 Radio Free Europe, Lisbon, Portugal

9607 Athens, Greece 9610 VLX9 Perth, Australia 9610 ZYC8 Rio de Janeiro, Brazil 9610 LLG Oslo, Norway 9610 XERQ Mexico, Mex. 9615 Tangler, Tangler 9615 VLB9 Shepparton, Aus. 9615 WRCA New York, U.S.A. 9618 TIDCR San Jose, C.Rica 9620 Horby, Sweden 9620 Paris, France 9620 ZL8 Wellington, N.Z. 9625 XEBT Mexico, Mex. 9625 GWO London, England 9625 VPARD Port-au-Spain, Trinidad

9630 HJKC Bogota, Colombia 9630 VUD4/10 Delhi, India 9630 Roma, Italy 9635 Munich, Germany 9635 Tangler, Tangler 9640 Accra, Ghana 9640 DZH2 Manila, P.I. 9640 GVD London, England 9645 Karachi, Pakistan 9645 LKH Oslo, Norway 9645 TFC San Jose, C.Rica 9646 HVJ9 Vatican City 9650 Honolulu, Hawaii 9650 Moscow, U.S.S.R. 9650 Tangler, Tangler 9650 WABC New York, U.S.A. 9652 ZJMS Limassol, Cyprus 9654 OTM2 Leopoldville, Belgian Congo

9655 JK12 Nakazi, Japan 9656 4VEH Cap-Haitien, Haiti 9660 EQC Teheran, Iran 9660 GWP London, England 9660 VL99 Brisbane, Aus. 9665 MEI8 New York, U.S.A. 9668 TGNB Guatemala, Guat. 9670 Munich, Germany 9670 Tangler, Tangler 9670 WGEO Schenectady, U.S.A.

**Kc. C.L. Location**

9670 KGEI San Fran., U.S.A. 9670 Moscow, U.S.S.R. 9675 GWT London, England 9675 JOB3 Tokyo, Japan 9680 Paris, France 9680 XEQQ Mexico, Mex. 9680 VUD Delhi, India 9680 Moscow, U.S.S.R. 9680 Tangler, Tangler 9680 VLR9/VLH9 Melbourne, Australia

9685 Paris, France 9685 WLWO Cincinnati, U.S.A. 9690 YKBO Caracas, Arg. 9690 GRX London, England 9690 Moscow, U.S.S.R. 9690 Singapore, Malaya 9695 JKM2 Kowachi, Japan 9700 GWY London, England 9700 WRCA New York, U.S.A. 9700 Sofia, Bulgaria 9700 Tangler, Denmark 9700 WLWO Cincinnati, U.S.A. 9700 KCBR Delano, Cal., U.S.A. 9700 WCBR Delano, Calif., USA 9700 FZF6 Ft. de France, Mart. 9710 Moscow, U.S.S.R. 9710 Dakar, Fr. W. Africa 9710 YDF3 Djakarta, Indonesia 9710 Rome, Italy 9715 Cairo, Egypt 9716 Moscow, U.S.S.R. 9717 Radio Free Europe, Ger. 9720 PRL7 Rio de Janeiro, Brazil 9730 Nanking, China 9730 DZH7 Leningrad, U.S.S.R. 9735 H12T Ciudad Trujillo, D.R. 9741 CSA27 Lisbon, Portugal 9743 HCJB Quito, Ecuador 9745 ORU Brussels, Belgium 9760 CR7B Loureux, Marquis, Moz. 9764 TGWA Guatemala, Guat. 9770 London, England 9770 ORU Brussels, Belgium 9770 PRL4 Rio de Jan., Brazil 9780 Rome, Italy 9785 Monte Carlo, Monaco 9825 GRN London, England 9830 Budapest, Hungary 9830 COBL Havana, Cuba 9865 YDF8 Djakarta, Indonesia 9915 GRU London, England 9966 Brazzaville, Fr. Eq. Africa

10058 SUV Cairo, Egypt 10220 PSM Rio de Janeiro, Brazil 10258 Peking, China 10280 SDB2 Motala, Sweden 1027 CSA29 Lisbon, Portugal 1090 CSA92 PontaDelgada, Azores 1030 Leningrad, U.S.S.R. 11630 Peking, China 11670 Bangkok, Thailand 11680 HJC Bogota, Colombia 11680 GRG London, England 11685 Peking, China 11695 HP5A Panama, Panama 11700 GWV London, England 11702 Paris, France 11705 JOA Tokyo, Japan 11705 SBP Motala, Sweden 11710 Moscow, U.S.S.R. 11710 Tangler, Tangler 11710 VUD5/7 Delhi, India 11710 WLWD Cincinnati, U.S.A. 11714 ZJMF Limassol, Cyprus 1175 H13 Bern, Switzerland 11718 Athens, Greece 11720 PRL8 Rio de Janeiro, Brazil 11720 Radio Canada (Montreal) 11720 OTM4 Leopoldville, Belgian Congo

11720 ORY2 Brussels, Belgium 11724 HNG Baghdad, Iraq 11725 COCY Havana, Cuba 11730 GVV London, England 11730 KGEI San Fran., U.S.A. 11730 PHI Hilversum, Nether. 11730 CEI73 Santiago, Chile 11735 BEDE Taipei, Formosa 11735 KLF Freetstad, Nor. 11735 Radio Free Europe, Ger. 11740 Moscow, U.S.S.R. 11740 Warsaw, Poland 11740 WRUL Boston, U.S.A. 11742 CEI174 Santiago, Chile 11750 GSD London, England 11755 Moscow, U.S.S.R. 11760 QLR4B Prague, Czech. 11760 Tangler, Tangler 11760 VLA11/VLBI1 Shepparton, Aus.

11770 VUD7/11 Delhi, India 11764 CR7B Loureux, Mozambique 11770 GVV London, England 11770 YDE/YDF7 Djakarta, Indonesia

11775 WRCA New York, U.S.A. 11780 Moscow, U.S.S.R. 11780 XEQH Mexico, D.F. 11780 ZL8 Wellington, N.Z. 11790 WABC New York, U.S.A. 11790 GVV London, England 11790 VUD Delhi, India 11790 KRCA San Fran., U.S.A. 11790 WRUL Boston, U.S.A.

**Kc. C.L. Location**

11790 Tangler, Tangler 11795 Cologne, Germany 11795 YDF3 Djakarta, Indonesia 11795 WRUL Boston, U.S.A. 11800 GWA London, England 11800 Brussels, Belgium 11810 Moscow, U.S.S.R. 11810 Rome, Italy 11810 VLA11 Shepparton, Aus. 11810 VLC11 Shepparton, Aus. 11815 Warsaw, Poland 11820 GSN London, England 11820 GRCA New York, U.S.A. 11825 JK16 Tokyo, Japan 11825 Moscow, U.S.S.R. 11825 ZYK3 Recife, Brazil 11830 FZS4 Saigon, Fr. Indo-C. 11830 Moscow, U.S.S.R. 11830 Tangler, Tangler 11830 WABC New York, U.S.A. 11835 XA19 Montevideo, Uru. 11840 VLW11 Perth, Australia 11840 OLRA4 Prague, Czech. 11840 LRT Tucuman, Argentina 11845 Karachi, Pakistan 11847 Paris, France 11850 VLB11 Shepparton, Aus. 11850 GRU Brussels, Belgium 11850 TGNB Guatemala, Guat. 11850 VUD11 Delhi, India 11850 LLK Oslo, Norway 11855 DZH9 Manila, Philippines 11855 Radio Free Europe, Lisbon, Portugal

11860 GSE London, England 11860 KUID San Fran., U.S.A. 11865 CR6RA Luanda, Angola 11865 HER5 Bern, Switzerland 11870 Munich, Germany 11870 KRCA San Fran., U.S.A. 11870 KUID San Fran., U.S.A. 11870 WBOS Boston, U.S.A. 11870 WRUL Boston, U.S.A. 11875 DLR4C Prague, Czech. 11880 Moscow, U.S.S.R. 11880 LRS Buenos Aires, Arg. 11880 VLG11/VLH11 Melbourne, Aus.

11880 Horby, Sweden 11880 XEHM Mexico, Mex. 11880 GRE London, England 11880 SBP Stockholm, Sweden 11885 APK3 Karachi, Pakistan 11890 Moscow, U.S.S.R. 11890 GVV London, England 11890 KZJ Manila, P.I. 11890 WRCA New York, U.S.A. 11895 HE3 Dakar, Fr. W. Af. 11895 Manila, Philippines 11900 CEI10 Valparaiso, Chile 11900 CXA10 Montevideo, Uru. 11900 HCB Calvary Radio, Ministry

11900 WGEO Schenectady, U.S.A. 11900 XEXE Mexico City, Mex. 11905 Rome, Italy 11910 Budapest, Hungary 11910 Karachi, Pakistan 11910 Damascus, Syria 11915 HCJB Quito, Ecuador 11918 BED4 Taipei, Formosa 11924 FZS4 Saigon, Vietnam 11930 GVV London, England 11935 Warsaw, Poland 11937 Bucharest, Rumania 11955 GVV London, England 11960 Moscow, U.S.S.R. 11950 YSOX San Salvador, Salv. 11963 Lisbon, Portugal 11970 Brazzaville, Fr. Eq. Africa 11972 TIHH San Jose, C.Rica 11975 Colombo, Ceylon 11980 Moscow, U.S.S.R. 11985 CSA32 Lisbon, Portugal 11998 CEI180 Santiago, Chile 12040 GRV London, England 12095 GRV London, England 12175 TFJ Reykjavik, Iceland 14492 Radio Moscow 14690 PSF Rio de Janeiro, Brazil 15050 FAF Addis Ababa, Eth. 15050 V3USE Forest Side, Mauritius

15060 Peking, China 15070 GVC London, England 15095 HVJ Vatican City 13100 CSA39 Lisbon, Portugal 15110 Moscow, U.S.S.R. 15116 CJB Rio de Janeiro, Ecuador 15120 Colombo, Ceylon 15120 Moscow, U.S.S.R. 15120 Rome, Italy 15120 Warsaw, Poland 15125 CSA36 Lisbon, Portugal 15130 Tangler, Tangler 15130 WABC New York, U.S.A. 15130 WLWO Cincinnati, U.S.A.

Kc.	C.L.	Location
15130	KRCA	San Fran., U.S.A.
15130	WRCA	New York, U.S.A.
15135	PRB23	Sao Paulo, Brazil
15140	GSF	London, England
15145	YDC	Djakarta, Indonesia
15145	ZYK2	Recife, Brazil
15150	OKAR	Lima, Peru
15150	CE1515	Santiago, Chile
15155	SBT	Motala, Sweden
15156	ZYB9	Sao Paulo, Brazil
15160	VUD5/7	Delhi, India
15160	VLB15	Shepparton, Aus.
15180	TAB	Tartessus, Spain
15180	TAU	Ankara, Turkey
15185	WLW	Cincinnati, U.S.A.
15185	ZYN7	Fortaleza, Brazil
15170	LKV	Oslo, Norway
15170	TGWA	Guatemala, Guat.
15170	Moscow	U.S.S.R.
15175	LLM	Oslo, Norway
15180	GSD	London, England
15180	Moscow	U.S.S.R.
15180	OZHZ	Shamlebak, Den.
15190	VUD5/5	I/I Delhi, India
15190	OIX4	Porl, Finland
15195	TAQ	Ankara, Turkey
15200	Moscow	U.S.S.R.
15200	VLA15/VLC15	Shepparton, Aus.
15205	XESC	Mexico, Mexico
15205	XEXE	Mexico, Mexico
15210	Munich	Germany
15210	GWU	London, England
15210	WRCA	New York, U.S.A.
15210	VLG15	Melbourne, Aus.
15210	Tangier	Tangier
15220	PCJ	Hilversum, Neth.
15220	XESC	Mexico, Mexico
15220	ZL10	Wellington, N.Z.
15225	JBD3	Kawachi, Japan
15228	Komsomolsk	U.S.S.R.
15230	GWU	London, England
15230	Moscow	U.S.S.R.
15230	QLR5A	Prague, Czech.
15230	VLH15	Melbourne, Aus.
15230	WRUL	Boston, U.S.A.
15235	BED3	Taipei, Formosa
15235	JBD4	Kawachi, Japan
15235	JDA4	Tokyo, Japan
15235	JDB5	Tokyo, Japan

Kc.	C.L.	Location
15240	Belgrade	Yugoslavia
15240	KRCA	San Fran., U.S.A.
15240	Paris	France
15240	VLH15	Melbourne, Aus.
15240	WLW	Cincinnati, U.S.A.
15250	Manila	P.I.
15250	WLW	Cincinnati, U.S.A.
15250	Tangier	Tangier
15260	GSI	London, England
15270	Karachi	Pakistan
15270	KCRB	Delano, Cal., U.S.A.
15270	Munich	Germany
15270	WABC	New York, U.S.A.
15280	Sverdlovsk	U.S.S.R.
15280	Munich	Germany
15280	ZL4	Wellington, N.Z.
15280	Moscow	U.S.S.R.
15280	Tangier	Tangier
15285	CR7BG	Lourenco Marques, Mozambique
15285	WRCA	New York, U.S.A.
15290	WLW	Cincinnati, U.S.A.
15290	LRU	Buenos Aires, Arg.
15290	VUD5/9	Delhi, India
15295	Tangier	Tangier
15300	DZ8	Manila, P.I.
15300	GRP	London, England
15300	Singapore	Malaya
15300	Geneva	Switzerland
15305	RV97	Novosibirsk, U.S.S.R.
15310	KCRB	Delano, Calif.
15310	GSP	London, England
15320	VLG15	Melbourne, Aus.
15320	VLG15	Shepparton, Aus.
15320	Moscow	U.S.S.R.
15320	DLRB	Bosque, Czech.
15325	Rome	Italy
15330	KGEI	San Fran., U.S.A.
15330	Sofia	Bulgaria
15330	WLW	Cincinnati, U.S.A.
15330	WGED	Schenectady, U.S.A.
15335	Brussels	Belgium
15335	Karachi	Pakistan
15340	Moscow	U.S.S.R.
15340	KCRB	Delano, Cal., U.S.A.
15340	Tangier	Tangier
15345	Athens	Greece
15347	LRA	Buenos Aires, Arg.
15350	Paris	France
15350	WRUL	Boston, U.S.A.

Kc.	C.L.	Location
15350	WLW	Cincinnati, U.S.A.
15350	VUD8	Delhi, India
15352	Luxemburg	
15360	London	England
15360	Moscow	U.S.S.R.
15364	ZYCS	Rio de Jan., Brazil
15390	Moscow	U.S.S.R.
15400	Paris	France
15400	Rome	Italy
15405	PZC	Paramaribo, Surinam
15410	Moscow	U.S.S.R.
15420	Radio	Netherlands
15435	GWE	London, England
15440	Moscow	U.S.S.R.
15450	GRD	London, England
15595	Brazzaville	Fr. Eq. Africa
15620	Madrid	Spain
17700	GVP	London, England
17710	GRA	London, England
17720	LRA5	Buenos Aires, Arg.
17730	GVQ	London, England
17735	WRUL	Boston, U.S.A.
17760	Lisbon	Portugal
17760	WGED	Schenectady, U.S.A.
17760	KGEI	San Fran., U.S.A.
17760	VUD	Delhi, India
17770	KCRB	Delano, Cal., U.S.A.
17770	Rome	Italy
17775	Tangier	Tangier
17775	Hilversum	Netherlands
17780	VUD/I0/I1	Delhi, India
17780	WRCA	New York, U.S.A.
17780	Manila	P.I.
17784	HER7	Bern, Switzerland
17780	GSG	London, England
17785	WRUL	Cincinnati, U.S.A.
17800	HCJB	Calcutta, India
17800	KRCA	San Fran., U.S.A.
17800	WLW	Cincinnati, U.S.A.
17800	KRH0	Honolulu, Hawaii
17800	Stockholm	Sweden
17802	OIX5	Porl, Finland
17804	Rome	Italy
17805	DZ16	Manila, P.I.
17810	GSV	London, England
17810	Moscow	U.S.S.R.
17815	WRUL	Boston, U.S.A.
17820	Colombo	Ceylon
17825	LLN	Oslo, Norway

Kc.	C.L.	Location
17830	TAV	Ankara, Turkey
17830	Moscow	U.S.S.R.
17830	WABC	New York, U.S.A.
17835	Karachi	Pakistan
17840	Brazzaville	Fr. Eq. Africa
17840	Moscow	U.S.S.R.
17840	VLG17	Shepparton, Aus.
17840	GRP	London, England
17852	Paris	France
17885	Damascus	Syria
17870	CSA44	Lisbon, Portugal
17890	HCJB	Quito, Ecuador
18025	GRQ	London, England
18080	GVO	London, England
18130	GVP	London, England
21460	KRCA	San Fran., U.S.A.
21470	GSH	London, England
21480	Hilversum	Netherlands
21490	Paris	France
21500	WRCA	New York, U.S.A.
21510	VUD5	Delhi, India
21520	HER7	Bern, Switzerland
21520	WLW	Cincinnati, U.S.A.
21530	GSD	London, England
21530	Moscow	U.S.S.R.
21540	VLB2	Shepparton, Aus.
21550	GST	London, England
21560	Moscow	U.S.S.R.
21560	Rome	Italy
21570	WABC	New York, U.S.A.
21580	Horby	Sweden
21590	WGED	Schenectady, N.Y.
21610	WRCA	New York, U.S.A.
21620	Colombo	Ceylon
21640	GRZ	London, England
21650	WLW	Cincinnati, U.S.A.
21660	WRUL	Cincinnati, U.S.A.
21670	LLP	Oslo, Norway
21675	GVR	London, England
21680	VLG21	Shepparton, Aus.
21690	Tangier	Tangier
21700	VUD10	Delhi, India
21710	GSV	London, England
21730	WABC	New York, U.S.A.
21740	KCRB	Delano, Cal., U.S.A.
21740	KGEI	San Fran., U.S.A.
21740	Paris	France
21750	GVT	London, England
23570	GSQ	London, England
26100	GSK	London, England

## Canadian Short-Wave Stations

Listed by Frequency

Abbreviations: Kc., frequency in kilocycles (to change to megacycles, divide by 1000); C.L., call letters

Kc.	C.L.	Location
5970	CBNX	St. John's, Nfld.
6100	CKNA	Sackville, N.B.
5990	CHAY	Sackville, N.B.
6005	CFXC	Montreal, Que.
6010	CJXC	Sydney, N.S.
6030	CFVP	Calgary, Alta.
6060	KCRZ	Sackville, N.B.
6070	CFRX	Toronto, Ont.
6080	CKFX	Vancouver, B.C.
6090	CBFW	Montreal, Que.
	CKOB	Sackville, N.B.

Kc.	C.L.	Location
6130	CHNX	Halifax, N.S.
6150	CKRO	Winnipeg, Man.
6160	CBXC	Vancouver, B.C.
	CHAC	Sackville, N.B.
9520	CBFR	Montreal, Que.
9585	KCPL	Sackville, N.B.
9610	CBFX	Montreal, Que.
	CHLS	Sackville, N.B.
9630	CBFO	Montreal, Que.
	CKDO	Sackville, N.B.
9710	CHLR	Sackville, N.B.

Kc.	C.L.	Location
9740	CHFO	Sackville, N.B.
11705	CBFY	Montreal, Que.
	CKXA	Sackville, N.B.
11720	CBFL	Montreal, Que.
	CHOL	Sackville, N.B.
	CKRX	Winnipeg, Man.
11760	CBFA	Montreal, Que.
	CKRA	Sackville, N.B.
11900	CKEX	Sackville, N.B.
11940	CKEY	Sackville, N.B.
15090	CKLX	Sackville, N.B.

Kc.	C.L.	Location
15190	CBFZ	Montreal, Que.
	CKCX	Sackville, N.B.
15320	CKSC	Sackville, N.B.
17710	CHSB	Sackville, N.B.
17735	CHRX	Sackville, N.B.
17820	CKNC	Sackville, N.B.
17865	CHYS	Sackville, N.B.
21800	KCRP	Sackville, N.B.
21710	CHLA	Sackville, N.B.
	Note:	Sackville, N.B., is often transmitter location only.

## United States

Frequency-Modulation (FM) Stations

(Territories and possessions follow states) Abbreviations; C.L., call letters, Mc, megacycles (for frequency in kilocycles, change decimal point to comma and add two zeros); asterisk (\*) indicates educational station

Location	C.L.	Mc.
<b>ALABAMA</b>		
Albertville	WAVU-FM	105.1
Alexander City	WRFS-FM	106.1
Andalusia	WCTA-FM	98.1
Anniston	WHMA-FM	100.5
Birmingham	WAFM	93.7
	WJLN	104.7
	WSGN-FM	93.7
Clanton	WKLF-FM	100.9
Cullman	WFHM-FM	101.1
Decatur	WHOS-FM	92.5
Lawnet	WRLD-FM	102.9
Mobile	WABB-FM	102.1
	WKRQ-FM	99.9
Talladega	WHTB-FM	97.1
Tuscaloosa	WTBC-FM	95.7
Tuscaloosa	WUOA	91.7
<b>ARIZONA</b>		
Mesa	KTYL-FM	104.7
Phoenix	KELE	95.5
	KFCA	88.5
Tucson	KTKT-FM	99.5
<b>ARKANSAS</b>		
Blytheville	KLON-FM	96.1
Ft. Smith	KFPW-FM	94.9
Jonesboro	KBTM-FM	101.9

Location	C.L.	Mc.
<b>CALIFORNIA</b>		
Mammoth Springs	KAMS	105.9
Poeahontas	KPOC-FM	97.7
Siloam Springs	KUOA-FM	105.7
<b>Bakersfield</b>		
	KERN-FM	94.1
	KQXR	101.5
Berkeley	KPFA	94.1
	KPFH	89.3
	KRE-FM	102.9
Beverly Hills	KCBH	98.7
	KPAL	104.3
Claremont	KSTP	90.7
Eureka	KRED-FM	96.3
Fresno	KARM-FM	101.9
	KMJ-FM	97.9
	KRFM	93.7
	KBMS	105.9
	KFMU	97.1
	KHOF-FM	99.5
Hollywood	KFWB-FM	94.7
	KHJ-FM	101.1
	KNX-FM	99.1
Long Beach	KFOX-FM	102.3
	KLON	88.1
	KNDB	103.1
Los Angeles	KABC-FM	95.5
	KCBH	98.7
	KFAC-FM	104.3
	KNX-FM	93.1
	KRHM	94.7

Location	C.L.	Mc.
<b>Los Angeles</b>		
	KRKO-FM	96.3
	KSRT	93.9
	KUSC	91.5
	KXLU	88.7
Marysville	KMYC-FM	99.9
Modesto	KBB-FM	103.3
	KTRB-FM	104.1
Mt. Diablo	KSBR	100.5
Oceanside	KOEN	89.7
Ontario	KEDO	93.5
Sacramento	KCRA-FM	96.1
	KFBK-FM	96.9
	KJML	95.3
	KXDA-FM	107.9
Sausalito	KDFC	102.1
Stockton	KCVN	91.3
San Bernardino	KVCR	91.9
San Diego	KFSD-FM	94.1
	KSDS	88.3
	KSON-FM	104.7
San Francisco	KALW	91.7
	KCBS-FM	103.7
	KEAR	97.3
	KGO-FM	103.7
	KNBC-FM	99.7
	KRON-FM	96.5
	KSJO-FM	93.3
San Jose	San Mateo	90.9
Santa Anna	KWIZ-FM	96.7
Santa Clara	KSCU	90.1
Santa Monica	KCRW	89.9
Stockton	KCVN	91.3

Location	C.L.	Mc.
<b>COLORADO</b>		
Boulder	KRNW	97.3
Colorado Springs	KRCC	91.3
	KBHS	90.5
Denver	KFEL-FM	97.3
	KFML-FM	98.5
Manitou Springs	KCMS-FM	102.7
<b>CONNECTICUT</b>		
Brookfield	WGHF	94.5
Danbury	WLAD-FM	98.3
Hartford	WHCN	93.7
	WITC-FM	96.5
Meriden	WMWF-FM	95.7
New Haven	WNHC-FM	99.1
Stamford	WSTC-FM	96.7
<b>DELAWARE</b>		
Dover	WDOV-FM	94.7
Wilmington	WDEL-FM	93.7
	WJBR	99.9
<b>DISTRICT OF COLUMBIA</b>		
Washington	WASH-FM	97.1
	WCFM	99.5
	WFAN	100.3
	WGMS-FM	103.5
	WMAL-FM	107.3

Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.	Location	C.L.	Mc.
Washington, D.C.	WOL-FM	98.7	Muncie	WWHI	*91.5	Detroit	WDET-FM	*101.9	Poughkeepsie	WKIP-FM	104.7
	WRC-FM	93.9		WYNS	91.1		WDTR	*90.9	Rochester	WHFM	98.9
	WTOP-FM	96.3	New Albany	WNAS	*88.1		WJBK-FM	93.1	Schenectady	WGFN	99.5
	WWDC-FM	101.1	New Castle	WCTW	102.5		WJLB-FM	97.9	South Bristol	WRFB	101.1
<b>FLORIDA</b>				WNSN	*91.1		WJRF-FM	96.3	Springfield	WSPE	*88.1
Daytona Beach	WNDB-FM	94.5	South Bend	WNFS	101.3		WYJ-FM	97.1	Syracuse	WAER	*88.1
Gainesville	WRUF-FM	*104.1	Terre Haute	WBOW-FM	101.1	E. Lansing	WYXZ-FM	101.1		WDDS-FM	93.1
Jacksonville	WJAX-FM	95.1		WTHI-FM	99.9	Flint	WKAR-FM	*90.5		WYSR-FM	94.5
	WJHP-FM	96.9	Wabash	WSKS	*91.3		WFBE	*95.1	Troy	WFLY	92.3
	WMBR-FM	98.1	Warsaw	WRSW	107.3	Grand Rapids	WFUM	*107.1	Utica	WRUN-FM	95.7
Lakeland	WFBI	*88.1	Washington	WFML	106.5		WFRS	92.5	Watertown	WRNY-FM	100.5
Miami	WCHR-FM	97.3	<b>IOWA</b>				WJEF-FM	93.7	Wethersfield	WRFB	101.1
	WGBS-FM	96.3	Ames	WOFI-FM	*90.1	Highland Pk.	WLAV-FM	96.9	White Plains	WFAS-FM	103.9
	WLRD	93.9	Boone	KFGQ	*99.3	Hillsdale	WHPR	*88.1	Woodside	WRRL-FM	105.1
	WTHS	*91.7	Clinton	KROS-FM	96.1	Kalamazoo	WBSF-FM	103.9	<b>NORTH CAROLINA</b>		
	WWPB-FM	101.5	Davenport	WOC-FM	103.7	Oak Park	WMCR	*102.1	Asheboro	WGWV-FM	92.3
Miami Beach	WKAT-FM	93.1	Des Moines	KDPS	*88.1	Royal Oak	WDM	95.5	Asheville	WLOS-FM	104.3
Orlando	WDBO-FM	92.3	Dubuque	KSO-FM	87.3		WQAK	*98.3	Burlington	WBBB-FM	93.9
	WDDO-FM	96.3	Iowa City	WHOF-FM	100.3	Saginaw	WQMG	94.3		WFNS-FM	93.9
	WDFW	90.3	Mason City	KSUI	*91.7	Sturgis	WSTR-FM	103.1	Chapel Hill	WUNC	*91.5
Palm Beach	WQXT-FM	97.9	Muratin	KGLO-FM	101.1	<b>MINNESOTA</b>			Charlotte	WSOC-FM	103.5
Panama City	WDXL-FM	98.9	Storm Lake	KGPC-FM	99.7	Duluth	WEEB-FM	92.3	Clingman's Pk.	WMIT	106.9
St. Petersburg	WTSP-FM	102.5	Waverly	KAYL-FM	101.5	Mankato	KYSM-FM	103.5	Durham	WDNC-FM	105.1
Tallahassee	WFSU-FM	91.5	Emporia	KWAR	89.1	Minneapolis	KTIS-FM	*98.5	Elkin	WIFM-FM	100.9
Tampa	WDAE-FM	100.7	<b>KANSAS</b>				WLOL-FM	97.1	Fayetteville	WFNC-FM	98.1
	WFLA-FM	93.3	Lawrence	KSTE	*88.7		WMNS-FM	99.5	Forest City	WFMY-FM	98.1
	WTKM	104.7	Manhattan	KANU	*91.5		WTCN-FM	97.1	Gastonia	WGNC-FM	101.9
	WTPN	*88.9	Ottawa	KSDB-FM	*88.1		KFAM-FM	104.7	Greensboro	WEQR	96.9
Winter Park	WPRK	*91.5	Wichita	KTJO-FM	*88.1	St. Cloud	WMIN-FM	99.5	Greenville	WWVS	*91.3
<b>GEORGIA</b>				KMUW	*89.1	St. Paul	WNOV	89.1	Henderson	WHNC-FM	92.5
Athens	WGAU-FM	99.5	<b>KENTUCKY</b>			Winona	KWNO-FM	97.5	High Point	WHPE-FM	95.3
Atlanta	WABE	*90.1	Ashland	WCMI-FM	93.7	<b>MISSISSIPPI</b>				WMFR-FM	99.5
	WAGA-FM	103.9	Bowling Green	WBDN	101.1	Gulfport	WGCM-FM	101.5		WNOS-FM	100.3
	WGKA-FM	92.3		WLBJ-FM	101.1	Jackson	WJDX-FM	102.9	Laurinburg	WEVO-FM	96.5
	WWSB-FM	98.5		WNES-FM	101.9	Meridian	WMMI	*88.1	Lexington	WBUY-FM	94.3
Augusta	WAUG-FM	105.7	Central City	WFUL-FM	104.9	<b>MISSOURI</b>			Raleigh	WKIX-FM	98.1
	WBBO-FM	93.7	Fullton	WSDO-FM	98.7	Clayton	KFUO-FM	99.1		WRFT-FM	94.7
Columbus	WRBL-FM	103.3	Henderson	WPOP-FM	98.7	Jefferson City	WKOS-FM	98.5		WRLE-FM	101.5
Gainesville	WDUN-FM	103.7	Lexington	WBKY	*91.3	Joplin	WMBH-FM	96.1	Reidsville	WREY-FM	102.1
Galvanage	WLAC-FM	104.1	Louisville	WLPF	*88.3	Kansas City	KCMO-FM	94.9	Roanoke Rapids	WKFK	98.5
Macon	WMAZ-FM	98.1		WPKP	*91.9	Kennett	KBOA-FM	98.9	Rocky Mount	WEED-FM	92.1
Newnan	WCOH-FM	96.7	Madisonville	WFMW-FM	93.9	Poplar Bluff	KWOC-FM	94.5		WFMA	100.7
Rome	WRGA-FM	106.5	Mayfield	WFTM-FM	107.1	Springfield	KTTS-FM	94.7	Salisbury	WSTP-FM	106.5
Savannah	WSAV-FM	100.3	Owensboro	WOM-FM	92.5	St. Louis	KCFM	95.7	Sanford	WNSN	103.1
	WTQC-FM	97.3	Paducah	WVIS-FM	98.1	West Plains	KSLH	*91.5		WWVP-FM	105.3
Swainsboro	WJAT-FM	101.7	<b>LOUISIANA</b>			Reno	KWPM-FM	97.3	Shelby	WVHS-FM	96.1
Toocoo	WLET-FM	106.1	Alexandria	KALB-FM	96.9	<b>NEVADA</b>			Statesville	WSDC-FM	105.7
			Baton Rouge	WAIL-FM	104.3		KNEV	95.5	Tarboro	WPCS-FM	104.3
Pocastello	KSEI-FM	96.3		WBRL	98.1	<b>NEW HAMPSHIRE</b>			Thomasville	WTNC-FM	98.3
<b>ILLINOIS</b>				WLSL	*91.7	Berlin	WMOU-FM	103.7	Winston-Salem	WAIR-FM	93.1
Bloomington	WJBC-FM	101.5	Monroe	KMBL-FM	104.1	Claremont	WTSV-FM	106.1	WSIS-FM	104.1	
Canton	WBYS-FM	100.9	New Orleans	WBEB	89.3	Manchester	WKBR-FM	95.7	Akron	WAKR-FM	87.5
Carbondale	WSRV	91.9		WDSU-FM	105.3	Nashua	WOTW-FM	106.3	WAPS	*89.1	
Carmi	WRDY-FM	97.3		WRMC	95.7	<b>NEW JERSEY</b>			Alliance	WFAN-FM	101.7
Champaign	WBBM-FM	96.3	Shreveport	WRMT	95.7	Asbury Park	WJLK-FM	94.3	Ashland	WATG-FM	101.3
Chicago	WBEZ	*91.5		KRMD-FM	96.5	Brigdeton	WNSJ-FM	98.9	Ashtabula	WICA-FM	103.7
	WCLM	101.9		KTBS-FM	96.5	Newark	WAAT-FM	94.7	Bethesda	WFOU	100.5
	WEFM	99.5		KWKH-FM	94.5		WBGO	*88.3	Baltimore	WTRX-FM	100.5
	WENR-FM	94.7	<b>MAINE</b>			New Brunswick	WCTC-FM	98.3	Bowling Green	WBGU	*88.1
	WFJL	100.3	Brunswick	WBOR	*91.1	South Orange	WSOU	*89.5	Canton	WHBC-FM	94.1
	WFML	101.1	Caribou	WFST-FM	97.7	Trenton	WTOA	97.5	Cincinnati	WCPO-FM	105.1
	WFMT	98.7	Lewiston	WCOU-FM	93.9	Zarpath	WAWZ-FM	99.1	Cleveland	WKRC-FM	101.9
	WMAQ-FM	101.1	<b>MARYLAND</b>			<b>NEW MEXICO</b>			Cleveland Hts.	WSAI-FM	102.7
	WMFT	98.7	Annapolis	WNAV-FM	99.1	Albuquerque	KANW	*89.1	Columbus	KYV-FM	105.7
	WNIB	97.1	Baltimore	WBIC	*88.1	Los Alamos	KHFM	96.3		WBOE	98.3
	WSEL	104.1		WCAO-FM	102.7	Mountain Park	KRSN-FM	98.5		WDOK-FM	102.1
Decatur	WSOY-FM	102.3		WTH-FM	104.3		KMFM	97.9		WERE-FM	98.5
DeKalb	WNIC	*91.3	Bothesda	WUST-FM	106.3	<b>NEW YORK</b>				WGAR-FM	99.5
Emingham	WSE	95.7	Bradbury Heights	WFRN	102.0	Auburn	WMBD-FM	96.1		WHK-FM	100.7
Elgin	WEPS	*88.1	Cumberland	WCUM-FM	102.0	Allengay	WHDL-FM	95.7		WJW-FM	104.1
Elmwood Park	WXFM	105.9	Hagerstown	WJEF-FM	104.7	Bay Shore	WMBD-FM	96.1		WWSR-FM	95.3
Evanson	WEAW	105.1	Oakland	WBUZ	95.5	Binghamton	WRBS	105.9		WCOL-FM	82.3
Harrisburg	WEBC-FM	99.9	<b>MASSACHUSETTS</b>			Binghamton	WRBS	105.9	Dayton	WVKK	94.7
Jacksonville	WLDS-FM	100.5	Amherst	WAMF	*88.1		WRBF-FM	98.1	Delaware	WHIO-FM	99.1
Macomb	WWKS	*91.3	Boston	WUOA	*91.1	Brooklyn	WKOP-FM	91.5	Delaware	WLSN	*91.1
Mattoon	WLBH-FM	96.3		WUBR	90.9	Buffalo	WNYE	*91.5	Elyria	WEOL-FM	107.3
Mt. Vernon	WMIX-FM	94.1		WCOP-FM	100.7		WNYE	91.5	Findlay	WFIL-FM	100.5
Oak Park	WOPA-FM	102.3		WEEI-FM	103.3	Cherry Valley	WRBC	103.3	Fosteria	WFOB	96.7
Olney	WVLN-FM	92.9		WERS	*88.9	Corning	WRRC	101.9	Freemont	WFRO-FM	99.3
Paris	WPRS-FM	98.3		WHDH-FM	94.5	Cortland	WCLI-FM	106.1	Kent	WKSU-FM	*88.1
Peoria	WMBD-FM	92.5		WRKO-FM	98.5		WKPD-FM	99.9	Lima	WIMA-FM	102.1
Quincy	WGM-FM	105.1		WDET-FM	97.7	DeRuyter	WRD	105.1	Marion	WMRN-FM	106.9
	WROK-FM	97.5		WGBH-FM	*99.7	Floral Park	WSHS	*90.3	Mt. Vernon	WMVO-FM	93.7
Rockford	WHBF-FM	98.9		WHRB-FM	107.1	Hempstead	WHLI-FM	98.3	Newark	WMLB-FM	98.5
Rock Island	WTAX-FM	103.7		WXHR	96.9	Hornell	WHHG-FM	105.3	Oxford	WVMB	*88.3
Springfield	WILL-FM	*90.9		WHAI-FM	98.5	Ithaca	WHCU-FM	97.3	Portsmouth	WPCY-FM	104.1
Urbana				WLLH-FM	99.3		WIFI	*91.7	Stebenville	WSTV-FM	103.5
				WLYN-FM	105.5		WJTN-FM	93.3	Toledo	WSPD-FM	101.5
Bloomington	WFLU	*103.7		WBSF-FM	97.3		WJTN-FM	93.3		WTDS	*91.3
Connorsville	WCNB-FM	100.3		WNBH-FM	98.7		WMSA-FM	105.3		WTOL-FM	104.7
Crawfordsville	WBBS	106.5		WBEC-FM	94.3		WNRG-FM	93.5		WTRT	99.9
Elkhart	WCMR-FM	95.1		WMHC	88.5		WABC-FM	95.5		WWSW-FM	105.8
	WTRC-FM	100.7		WBZA-FM	97.1		WBAI	99.5		WVBC	96.5
Evansville	WKY-FM	104.1		WEDK	*91.7		WBAM	101.9		WVKK	94.7
	WEVC	*91.5		WHYN-FM	93.1		WBFB	101.9		WVVO-FM	99.3
	WFSR	90.7		WNA-FM	94.7		WCBF-FM	101.1		WVVO-FM	99.3
Gary	WGVE	98.3		WCRE-FM	102.5		WVUW	*90.7		WVVO-FM	99.3
Greencastle	WGRE	*91.7		WCOB-FM	94.3		WGHE	101.9		WVVO-FM	99.3
Hammond	WJOB-FM	92.3		WCFM	*90.1		WHOM-FM	92.3		WVVO-FM	99.3
Hartford City	WHCI	*91.9		WHRF-FM	107.1		WKCR-FM	*89.9		WVVO-FM	99.3
Huntington	WVSH	*91.9		WHSR-FM	*91.9		WNGM-FM	100.3		WVVO-FM	99.3
Indianapolis	WAJC	*104.5		WTAG-FM	98.9		WNYC-FM	93.9		WVVO-FM	99.3
	WFMS	102.3					WDR-FM	88.7		WVVO-FM	99.3
	WIAN	*90.1					WQXR-FM	96.3		WVVO-FM	99.3
Jasper	WITZ-FM	104.7					WRCA-FM	97.1		WVVO-FM	99.3
Madison	WORX-FM	96.7					WRCA-FM	97.1		WVVO-FM	99.3
Marion	WMRI-FM	106.9					WRCA-FM	97.1		WVVO-FM	99.3
Muncie	WMUN	104.1					WRCA-FM	97.1		WVVO-FM	99.3
							WRCA-FM	97.1		WVVO-FM	99.3
							WRCA-FM	97			



Location	C.L. Chan.	Location	C.L. Chan.	Location	C.L. Chan.	Location	C.L. Chan.
Panama City	WJDM-TV 7	Presque Isle	WGAN-TV 13	Carthage	WCNY-TV 7	WPRO-TV	12
Pensacola	WEAR-TV 7		WAGM-TV 8	Elmira	W5YE-TV 18	<b>SOUTH CAROLINA</b>	
St. Petersburg	WSPN-TV 38	<b>MARYLAND</b>		Hagsman	W5YD 29	Anderson	WAIM-TV 40
Tampa	WFLA-TV 8	Baltimore	WAAM 13	New York	WABC-TV 7	Charleston	WCSC-TV 5
W. Palm Beach	WTVT 12		WBAL-TV 11		WABD 5	WUSN-TV	2
<b>GEORGIA</b>					WATV 13	Columbia	WIS-TV 10
Albany	WALB-TV 10	Salisbury	WMAR-TV 2		WCBS-TV 2	Greenville	WNOX-TV 67
Aithens	WJAT-TV 8		WBOC-TV 16		WDR-TV 9	Florence	WBTW 11
Atlanta	WAGA-TV 5	<b>MASSACHUSETTS</b>		Plattsburg	WRCA-TV 4	Greenville	WFBC-TV 7
	WWSB-TV 2	Adams	WCDC 19	Poughkeepsie	WPTZ-TV 5	Spartanburg	WSPA-TV 4
	WETV 30	Boston	WBZ-TV 4	Rochester	WHEC-TV 10	<b>SOUTH DAKOTA</b>	
	WLW-A 11		WGBH-TV 2		WRDQ-TV 5	Florence	KDLO-TV 3
Augusta	WJBF 6		WNACTV 7		WVET-TV 10	Rapid City	KOTA-TV 3
	WRDW-TV 12	Greenfield	WRFL 32	Schenectady	WVRB 6	Sioux Falls	KELO-TV 11
Columbus	WRBW-TV 4	Springfield	WHYN-TV 22	Syracuse	WHEW-TV 3	<b>TENNESSEE</b>	
	WRTM 28		WWLP 22	Utica	WKTV 13	Chattanooga	WDEF-TV 12
Macon	WMAZ-TV 13	<b>MICHIGAN</b>		<b>NORTH CAROLINA</b>			
Rome	WRDM-TV 9	Ann Arbor	WPAG-TV 20	Asheville	WISE-TV 62	Jackson	WDRP-TV 3
Savannah	WSAV-TV 3	Bay City	WNEM-TV 13	Charlotte	WLOS-TV 13	Johnson City	WJHL-TV 11
Thomasville	WTOC-TV 11	Cadillac	WWTY 15	Charlotte	WUNV-TV 2	Knoxville	WVBC-TV 6
	WCTV 6	Detroit	WJBL-TV 56	Charlotte	WBTV 3	Memphis	WHBQ-TV 13
<b>IDAHO</b>					WSOC-TV 9		WKNO 10
Boise	KBOI 2		WWJ-TV 4		WTVF 11		WMCT 5
	KIDO-TV 7		WXYZ-TV 7		WFLB-TV 16		WREC-TV 3
Idaho Falls	KID-TV 3	(Windsor, Ont.)	CKLW-TV 9		WFMY-TV 2		WLAC-TV 5
Lewiston	KLEW-TV 5	East Lansing	WKAR-TV 60		WNCT 9		WSIX-TV 8
Twain Falls	KLIJ-TV 11	Flint	WJRT 12		WNAO-TV 28		WSM-TV 4
<b>ILLINOIS</b>				Grand Rapids	WOD-TV 23		WSM-TV 4
Champaign	WCIA 3	Kalamazoo	WKZO-TV 3	Washington	WITN 7	<b>TEXAS</b>	
Chicago	WBDM-TV 2	Lansing	WJIM-TV 6	Wilmington	WMFD-TV 6	Ablene	KRBC-TV 9
	WBKB 7	Marquette	WDMJ-TV 6	Winston-Salem	WSJS-TV 12	Alpine	KAMT-TV 12
	WGN-TV 9	Saginaw	WDMJ-TV 6			Amarillo	KFDA-TV 10
	WNBQ 5	Traverse City	WPNB-TV 57	<b>NORTH DAKOTA</b>			
	WTTW 21			Bismarck	KBMB-TV 12		KGNC-TV 4
Danville	WDAN-TV 24	<b>MINNESOTA</b>			KFYR-TV 2		KTBC-TV 6
Decatur	WTVF 17	Austin	KMMT 6	Dickinson	KDIX-TV 2		KFD-TV 6
Harrisburg	WVTV 43	Duluth	KDAL-TV 3	Farlo	WDAY-TV 6		KFTX-TV 3
Peoria	WTVH 19	Minneapolis	WDSM-TV 6	Grand Forks	KNX-TV 10		KRIS-TV 6
	WGEM-TV 10		KMGW-TV 9	Minot	KCJB-TV 13		KSIX-TV 10
Rockford	WRFX-TV 13		WCCO-TV 4	Valley City	KXJB-TV 4		KRLD-TV 4
	WTO 39		WTGN-TV 4	Williston	KUMV-TV 8		WFAB-TV 13
Rock Island	WHBF-TV 4		KROC-TV 10	<b>OHIO</b>			
Springfield	WICS 20	Rochester	KSTP-TV 8	Akron	WAKR-TV 49		KRSD-TV 9
Urbana	WILL-TV 12	St. Paul	KTCa-TV 8	Cincinnati	WCET 48		KTSM-TV 4
<b>INDIANA</b>					WCPO-TV 9	(Ciudad Juarez, Mex.)	XEJ-TV 5
Bloomington	WTTV 4	Columbus	WCBI-TV 4		WKRC-TV 12	Ft. Worth	KFJZ-TV 11
Elkhart	WSJV-TV 52	Hattiesburg	WDAI-TV 9	Cleveland	WLW-TV 7		WPAB-TV 5
Evansville	WFIE-TV 62	Jackson	WJTV 12		KYU-TV 2	Galveston	WGB-TV 11
	WTVW 7		WLBT 3		WEWS 5	Harlingen	KGBT-TV 4
Ft. Wayne	WANE-TV 33	Meridian	WTOK-TV 11	Columbus	WJW-TV 8	Houston	KPRC-TV 2
	WKJG-TV 15	Tupelo	WTWV 9		WBNS-TV 10		KTRK-TV 13
Indianapolis	WFBM-TV 8	<b>MISSISSIPPI</b>			WLW-C 4		KUHT 8
	WLWI 13	Cape Girardeau	KFVS-TV 12		WOSU-TV 34	Laredo	KHAD-TV 8
	WISH-TV 8	Columbia	KOMU-TV 8	Dayton	WTVN-TV 6	Lubbock	KCBN-TV 11
Lafayette	WFAN-TV 59	Hannibal	KHQA-TV 7		WHIO-TV 7		KDUB-TV 13
Muncie	WLBC-TV 49	Jefferson City	KRCG-TV 13	Lima	WLW-D 2	Lufkin	KTRE-TV 9
South Bend	WNOU-TV 46	Joplin	KODE-TV 12	Steubenville	WIMA-TV 35	Midland	KMID-TV 2
	WSBT-TV 34	Kansas City	KCMO-TV 5	Toledo	WSTV-TV 9	Odessa	KOSA-TV 7
Terre Haute	WTHI-TV 10		KMBC-TV 9	Youngstown	WSPD-TV 13	Port Arthur-Beaumont	KPCATV 4
<b>IOWA</b>					WFMJ-TV 21		KCTV 8
Ames	WOI-TV 5	Kirkaville	KTVO 2		WKBN-TV 18	San Angelo	KCOR-TV 41
Cedar Rapids	KCRG-TV 9	St. Joseph	KFEQ-TV 2	Zanesville	WHIZ-TV 18	San Antonio	KENS-TV 5
	WMT-TV 2	St. Louis	KETC 9				KONO-TV 12
Davenport	WOC-TV 6		KSD-TV 2	<b>OKLAHOMA</b>			
Des Moines	KRRT-TV 8		KTVI 2	Ada	KTEN 10	Sweetwater	KPAR-TV 4
	WHQ-TV 19		KWK-TV 6	Ardmore	KVSO-TV 12	Temple	KCEN-TV 6
Fort Dodge	KQT-TV 21		KWV-TV 2	Enid	KGE-TV 5	Texasarkana	KCMC-TV 8
Mason City	KGLO-TV 3	Sedalia	KDRO-TV 8	Muskogee	KSWO-TV 5	Tyler	KCLT-TV 7
Ottumwa	KTVO 3	Springfield	KTTT-TV 10	Oklahoma City	KETA 13	Waco	KWTV-TV 10
Sioux City	KTVJ 4		KYTV 3		KWTN 9	Weslaco	KRGV-TV 5
	KTVT 9	<b>MONTANA</b>			WKY-TV 4	Wichita Falls	KFDX-TV 3
Waterloo	KWWL-TV 7	Billings	KOOK-TV 2	Tulsa	KOTV 6		KSYD-TV 6
<b>KANSAS</b>				Butte	KXLF-TV 5	<b>UTAH</b>	
Great Bend	KCKT 12	Glenview	KXGN-TV 5	Coos Bay	KDSS-TV 16	Salt Lake City	KSL-TV 5
Hutchinson	KTVH 12	Great Falls	KFBB-TV 13	Corvallis	KOAC-TV 97		KTVT 4
Manhattan	KSAC-TV 8	Missoula	KGVD-TV 13	Eugene	KVAL-TV 13		KUED 7
Pittsburg	KOAM-TV 7	<b>NEBRASKA</b>		Madford	KOTI 2		KUTV 2
Topoka	KBW-TV 13	Hastings	KHAS-TV 5	Klamath	KBS-TV 5	<b>VERMONT</b>	
Wichita	KARD-TV 3	Hayes Center	KHPL-TV 13	Portland	KBES-TV 8	Burlington	WCAX-TV 3
<b>KENTUCKY</b>				Lincoln	KGW-TV 8	<b>VIRGINIA</b>	
Ashland	WALN-TV 59	Omaha	KOLN-TV 10		KOIN-TV 6	Bristol	WCYB-TV 5
Henderson	WEHT 50	Scottsbluff	KUON-TV 12	Roseburg	KPTV 12	Harrisonburg	WWSA-TV 3
Lexington	WLFX-TV 18		KMTV 3		KPIC-TV 4	Newport News	WACH-TV 33
Louisville	WWE-TV 3	<b>NEVADA</b>		Altoona	WFBG-TV 10	Lyndonville	WVBC-TV 15
	WHS-TV 11	Henderson	KLRJ-TV 2	Erie	WICU 12	Hampton	WVEC-TV 3
Paduach	WPSO-TV 6	Las Vegas	KLAS-TV 2	Harrisburg	W5EE-TV 35	Norfolk	WTRF-TV 3
<b>LOUISIANA</b>					WCMB-TV 27	Petersburg	WTOV-TV 27
Alexandria	KALB-TV 3	Reno	KSHO-TV 13		WHP-TV 55	Richmond	WXEX-TV 8
Baton Rouge	WAFB-TV 2		KOLO-TV 8		WTPA 71		WVRA-TV 12
	WBRZ 2	<b>NEW HAMPSHIRE</b>			WVTV 58	Roanoke	WTVR 6
Lafayette	KLFY-TV 10	Manchester	WMUR-TV 9		WJAC-TV 6		WVSL-TV 10
Lake Charles	KPLC-TV 7	<b>NEW MEXICO</b>			WALB-TV 8	<b>WASHINGTON</b>	
	KTAG-TV 25	Albuquerque	KGGM-TV 13		WBR-TV 15	Bellingham	KVOS-TV 12
	KNOE-TV 8		KOAT-TV 7		WCAU-TV 10	Ephrata	KBAS-TV 43
Monroe	KLSE 13		KOB-TV 4		WFIL-TV 6	Georgetown	KBPR-TV 19
	WJMR-TV 20	Carlsbad	KAYE-TV 12		WHYY-TV 35	Issaquah	KCTS 9
New Orleans	WWSU-TV 13	Clovis	KICA-TV 12	Pittsburg	WKYC-TV 3	Kingston	KING-TV 5
	WWEZ-TV 32	Roswell	KSWs-TV 8		WKDK-TV 2	KOMO-TV 4	KHQ-TV 6
	WYES 8	<b>NEW YORK</b>			WENS 16	KRMV-TV 2	KXLY-TV 4
Shreveport	KSLS-TV 12	Albany	WCDA-TV 41		WQED 13	KTNV-TV 11	KXII-TV 4
	KTBS-TV 3	Binghamton	WTRI 35		WARM-TV 18	Tacoma	KTNT-TV 11
<b>MAINE</b>				Buffalo	WDAU-TV 22	Walla Walla	KTVW 13
Bangor	WABI-TV 5		WBRE-TV 28	York	WDLK-TV 34	Yakima	KRTV 8
	W-TWO 2		WNLK-TV 43		WBSA-TV 43		KIMA-TV 29
Poland Spring	WMT 8		WVBA-TV 43	<b>RHODE ISLAND</b>			
Portland	WCSH-TV 6		WGR-TV 2	Providence	WJAR-TV 10	<b>WHITE'S RADIO LOG</b>	



Broadcast stations are assigned call letters beginning with K or with W.

During radio's infancy, most of the broadcast stations were in the East. As inland stations developed, the Mississippi River was made the dividing line of K and W calls. KDKA, Pittsburgh, was assigned the K letter before the present system was put into effect.

**Broadcast Operation.** In AM broadcast the audio waves are impressed on the carrier wave in a manner to cause its amplitude (or power) to vary with the audio waves. The frequency of the carrier remains constant. This is known as "amplitude modulation". In "frequency modulation" (FM), the amplitude remains unchanged but the frequency is varied in a manner corresponding to the voice or music to be transmitted.

AM broadcast stations use "medium waves". That is to say, they transmit 540,000 to 1,600,000 waves a second. At 540,000 waves a second, the distance between the crests is approximately 1,800 feet. This is known as "wave length". A station transmitting 540,000 waves a second is said to have a "frequency" of 540,000 cycles or 540 kilocycles.

The so-called "short-wave" (long-distance) broadcast stations transmit from 6,000,000 to 25,000,000 waves per second. These waves are sent out one after another so rapidly that the distance between their crests (wave length) is only about 37 to 150 feet. Under international agreement, certain high frequency bands are allocated for broadcasts directed between nations. Frequencies used by international broadcast stations are in the bands between 6000 and 21700 kilocycles.

The modulated radio wave from the radio station is picked up by the home receiving antenna; in the receiver the audio and carrier waves are separated by a device called a detector or demodulator, and the audio wave is relayed to the loud speaker where it is transformed back into the sound that you hear.

**AM Broadcast.** The 535 to 1605 kilocycles portion of the radio spectrum is now used for AM broadcast. The band consists of 107 channels, each 10 kilocycles in width. Individual stations are assigned to frequencies in the center of each channel, such as 540 kilocycles, 550 kilocycles, etc. AM broadcast stations use power of from 100 watts up to 50 kilowatts (50,000 watts).

"Clear channels" are set apart by international agreement for the operation of maximum powered AM stations to serve remote rural areas. The other channels are shared by so many regional and local stations that people living outside populous communities must at night depend largely upon the strong signals of distant clear channel stations which are protected against night-time interference.

**FM Broadcast.** FM (frequency modulation) broadcast has several advantages over the older AM broadcast. FM has higher fidelity characteristics and is ordinarily free of static, fading and background overlapping of other station programs.

FM's greater tonal range capability is due primarily to the fact that it uses a channel 20 times wider than that employed for AM broadcast. Then, too, FM occupies a higher portion of the radio spectrum where static and other noise is less prevalent than at lower frequencies.

Most FM stations serve areas within a radius of approximately 35 to 75 miles, although high-powered FM stations sometimes reach out 100 miles or more. Low-power stations have a limited local coverage.

The principle of frequency modulation has long been known but its advantages for broadcasting were not realized until shortly before World War II. Largely as a result of interest evoked by extensive FM development work by Edwin H. Armstrong in the 1930's, the Commission authorized increased FM experimentation and in 1940, after extensive public hearings, provided for commercial FM operation to start January 1, 1941.

There was no "first" individual commercial FM grant because, on October 31, 1940, the Commission authorized construction permits to 15 such stations simultaneously. The first commercial FM station licensed by the Commission was WSM-FM Nashville (May 29, 1941), which operated until 1951.

FM stations were initially assigned call letters with added

numerals, but in 1943 the present letter system was adopted. There is optional use of the suffix "FM" to distinguish FM stations from AM stations under joint operation.

Because of skywave interference experienced on the then FM band of 42-50 megacycles, the Commission in 1945, after public hearing, moved FM to its present higher and less vulnerable position in the radio spectrum—88 to 108 megacycles—providing 80 channels for commercial FM and 20 channels for nonprofit educational broadcast.

**TV Broadcast.** The TV transmitter is, in effect, two separate units. One sends out the picture and the other the sound. Visual transmission is by amplitude modulation (AM). The sound portion employs frequency modulation (FM). The frequency space used for the combined video and sound transmission is about 600 times larger than for an AM program.

Like other forms of radio, TV was made possible by electronic discoveries in the late 19th century and early 20th century. In 1884, Nipkow, a German, patented a scanning disk for transmitting pictures by wireless. In our own country, Jenkins began his study of the subject about 1890. Rignoux and Fournier conducted "television" experiments in France in the 1900's. In 1915 Marconi predicted "visible telephone". In 1923 Zworykin applied for a patent on the iconoscope (TV camera tube). Two years later Jenkins demonstrated mechanical TV apparatus. There were experiments by Alexanderson, Farnsworth, and Baird in 1926-1927. An experimental TV program was sent by wire between New York and Washington by the Bell Telephone Laboratories in 1927, in which Herbert Hoover, then Secretary of Commerce, participated.

The Federal Radio Commission reported that "a few" broadcast stations were experimenting with video in 1928. In that year, WGY, Schenectady, experimentally broadcast the first drama by TV. Large-screen TV was demonstrated by RCA at a New York theatre in 1930, and RCA tested outdoor TV pickup at Camden, N. J., in 1936.

Seventeen experimental TV stations were operating in 1937. The first United States President seen on TV was Franklin D. Roosevelt, when he opened the New York World's Fair in 1939. That year also saw the first telecast major league baseball game, college football game and professional boxing match.

The first grant looking to regular TV operation was issued to WNBT, New York, on June 17, 1941, effective July 1 of that year. One June 24, 1941, WCBW (now WCBS-TV), New York, was authorized to commence program tests July 1 thereafter. By May of 1942 ten commercial TV stations were on the air.

As predicted by the Commission in 1945 it became increasingly evident that the few available VHF channels were inadequate to provide a truly nationwide competitive TV service. Also, operating stations developed interference which had not been anticipated when TV broadcasting began. As a result, the Commission on September 30, 1948, stopped granting new TV stations pending a study of the situation. This was the so-called television "freeze" order.

On April 14, 1952, the Commission announced the lifting of the TV "freeze", the addition of 70 UHF channels (between 470-890 megacycles) to the 12 VHF channels (between 54-216 megacycles) then in use, and the adoption of a table making more than 2,000 channel assignments (over 1,400 UHF and over 500 VHF) to nearly 1,300 communities throughout the United States and its territories, including 242 assignments for noncommercial educational use.

The first commercial TV grants following the lifting of the freeze were made on July 11, 1952, simultaneously, to three Denver, Colo. stations—KFEL-TV, KDEN and KBTU. KFEL-TV began program operation on July 19 thereafter. The first UHF commercial TV station to go on the air was KPVT, Portland, Oregon, on September 20, 1952.

The initial commercial grant to the territories and possessions was made on July 23, 1952, to WKAQ-TV, San Juan, Puerto Rico.

The first noncommercial educational TV grant was made July 23, 1952, to the Kansas State College of Agriculture and Applied Science (KSAC-TV), at Manhattan, Kans.—Condensed from FCC Information Bulletin No. 2.



**THE MOST EXCITING HIGH-FIDELITY PERFORMANCES EVER OFFERED  
TO NEW MEMBERS OF THE COLUMBIA LP RECORD CLUB**

**FREE-ANY 3**  
OF THESE SUPERB HIGH-FIDELITY  
**12" COLUMBIA LP RECORDS**

If you join the Club now—and agree  
to purchase 4 selections during  
the coming 12 months



- ☆ You receive, at once, any 3 of these records—FREE. One is your gift for joining, and the other two are your Bonus records "in advance"
- ☆ After you have purchased only four records, you receive a 12" Columbia LP Bonus record of your choice FREE for every two additional selections you purchase from the Club
- ☆ You enroll in any one of the four Club Divisions: Classical; Jazz; Listening and Dancing; Broadway, Movies, Television and Musical Comedies
- ☆ Every month you receive, FREE, a new issue of the Columbia LP Record Club Magazine — which describes all forthcoming selections
- ☆ You may accept or reject the selection for your Division . . . take records from other Divisions or take NO records in any one month
- ☆ Your only membership obligation is to buy four selections from the more than 100 to be offered in the coming 12 months. You may cancel membership any time thereafter
- ☆ The records you want are mailed and billed to you at only \$3.98 (original cast Musical Shows somewhat higher), plus small mailing charge
- ☆ You must be delighted with membership or you may cancel it by returning the free records within 10 days



© Columbia. ® LP. ℗ Marces Reg.

**COLUMBIA LP RECORD CLUB Terre Haute, Indiana**

**FREE—ANY 3—VALUE UP TO \$12.94—MAIL ENTIRE COUPON NOW!**

COLUMBIA LP RECORD CLUB, Dept. 514  
TERRE HAUTE, INDIANA

Please send me as my FREE gift the 3 records whose numbers I have circled at the right — and enroll me in the following Division of the Club:

(check one box only)

- Classical
- Listening and Dancing
- Jazz
- Broadway, Movies, Television and Musical Comedies

I agree to purchase four selections from the more than 100 to be offered during the coming 12 months . . . at regular list price, plus small mailing charge. For every two additional selections I accept, I am to receive a 12" Columbia LP Bonus record of my choice FREE.

Name .....  
(Please Print)

Address .....

City ..... Zone ..... State .....

CANADA: Prices slightly higher. Address 11-13 Soho St. Toronto 2B  
If you wish to have this membership credited to an established Columbia Records dealer, authorized to accept subscriptions, please fill in the following information:

Dealer's Name .....

Dealer's Address .....85

**CIRCLE 3 NUMBERS BELOW:**

1. Eddy Duchin Story
2. Beethoven: 3 piano sonatas
3. Erroll Garner ("Caravan")
4. Gaité Parisienne; Les Sylphides
5. Easy To Remember—Luboff Choir
6. My Fair Lady—Orig. Broadway Cast
7. Brubeck and Jay & Kai
8. Gershwin Hits—Percy Faith
9. Sinatra—Adventures of the Heart
10. Ambassador Satch
11. Firebird; Romeo and Juliet
12. Day By Day—Doris Day
13. Johann Strauss—Waltzes
14. Lure of the Tropics—Kostelanetz
15. Ports Of Call
16. Oklahoma!
17. Levant Plays Gershwin
18. The Elgart Touch
19. The Great Melodies of Tchaikovsky
20. Suddenly It's the Hi-Lo's
21. King of Swing—Benny Goodman
22. Brahms: Symphony No. 3
23. The Merry Widow
24. Wonderful, Wonderful—Mathis PE-1

# THE ONLY COMPLETE ELECTRONIC COURSE

# Learn TELEVISION, RADIO, RADAR, SONAR, ELECTRONICS

Only CTS offers you *COMPLETE* training in all phases of Electronics. Why be satisfied with less? The new Christy Shop-Method Home Training makes learning interesting and easy. You learn Radar, Sonar, Electronics, Radio, Television. No previous experience needed. You learn by working with actual equipment. Makes learning fun. Speeds your progress. Helps you understand quicker and remember longer.

You get comprehensive training starting with your first CTS lesson! The complete knowledge CTS provides you with, gives you a broader knowledge, a greater understanding which will mean more jobs and a higher income for you for the rest of your life.

## HOME LABORATORY SENT! 19 TRAINING INSTRUMENTS INCLUDED

With CTS *COMPLETE* Home Training Course, you receive a Home Laboratory to assemble, use and keep for years of peak performance. You receive a Multi-Tester, Oscillator, Signal Tracer, Oscilloscope, Signal Generator, Electronic Timer, Regenerative Radio, Giant-size Television Receiver (optional) as well as many other valuable electronic devices. With these you will be able to make hundreds upon hundreds of exciting experiments.

## EARN WHILE YOU LEARN! EARN \$5.00—\$6.00 PER HOUR

Or *MORE* while still studying! Almost from the very first you receive training that enables you to repair radios and television sets for friends and neighbors. To install and service electronic computers, communication equipment, protective equipment for police and fire departments, etc., etc.

## FREE BOOK—SAMPLE LESSONS SENT

Get all there is to know about the Christy *COMPLETE* Electronic Course in Radio-Television-Radar-Sonar, etc. A complete, colorful, illustrated book on Electronics sent without obligation.

Also, we will send you Two sample lessons showing how the new CTS Shop-Method Home Training Course will train you for making big money in your spare time and for building a bright future for yourself.

CHRISTY TRADES SCHOOL, Dept. T-309, 4804 N. Kedzie Ave., Chicago 25

**SIGN, MAIL FOR THREE BOOKS**



Christy Trades School, Dept. T-309, 4804 N. Kedzie, Chicago 25, Ill.

Gentlemen:  
Please send me, without cost or obligation, two *FREE* lessons and the new 24-Page illustrated book telling all about the CTS Master Shop Method Home Training Course in Radar, Sonar, Television, Radio and Electronics, and the many opportunities this new field offers.

Name..... Age.....

Address .....

City..... Zone.... State.....

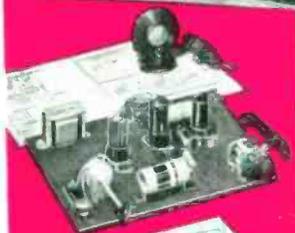
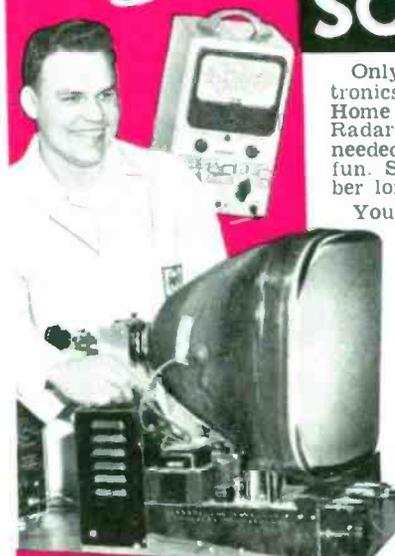


**MAIL COUPON  
TODAY FOR  
CATALOG !**

# Learn Radio-Television
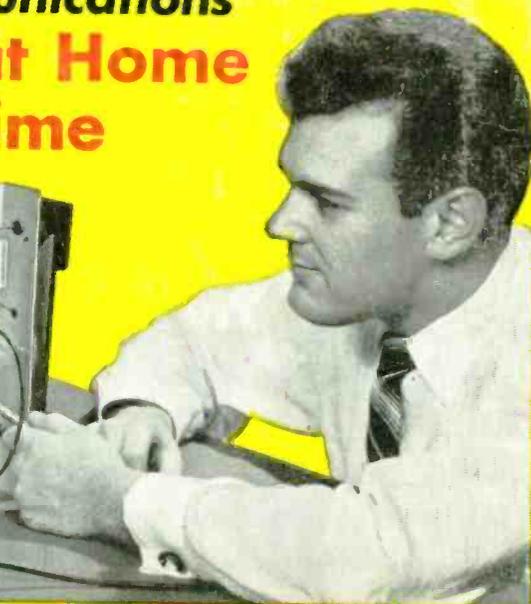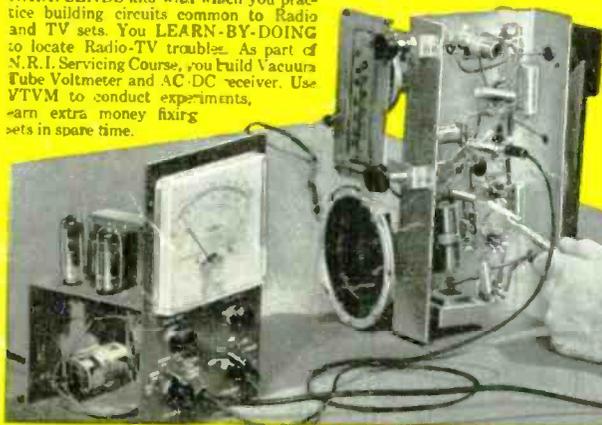
## Servicing or Communications by Practicing at Home in Spare Time

N. R. I. SENDS kits with which you practice building circuits common to Radio and TV sets. You LEARN-BY-DOING to locate Radio-TV troubles. As part of N. R. I. Servicing Course, you build Vacuum Tube Voltmeter and AC-DC receiver. Use VTVM to conduct experiments, earn extra money fixing sets in spare time.



**RADIO-TV BROADCASTING** (see above) offers important positions as Operators and Technicians. **RADIO-TV SERVICING** Technicians (see below) are needed in every community. Their services are respected, their skill appreciated.



## Fast Growing Field Offers You Good Pay, Success, Bright Future



**J. E. SMITH**  
Founder

Bigger than ever and still growing fast. That's why Radio-TV has special appeal to ambitious men not satisfied with their job and earnings. More than 4,000 Radio and TV stations. More than 150 million home and auto Radios, 40 million TV sets. Color TV promises added opportunities. For the trained man, there are good jobs, bright futures in Radio-TV Servicing or Broadcasting. Training PLUS opportunity is the ideal combination for success. So plan now to get into Radio-TV. The technical man is looked up to. He does important work, gets good pay for it. Radio-Television offers that kind of work. NRI can supply training quickly, without expense of going away to school. Keep your job while training. You learn at home in your spare time. NRI is the OLDEST and LARGEST home study Radio-TV school. Its methods have proved successful for more than 40 years.

### Added Income Soon - \$10, \$15 a Week in Spare Time

Soon after enrolling, many NRI students start to earn \$10, \$15 a week in spare time fixing sets. Some pay for their training and enjoy extra luxuries this way. Some make enough to start their own Radio-TV shops. NRI training is *practical*—gets quick results. Easy to understand, well illustrated lessons teach you basic principles. And you LEARN-BY-DOING by practicing with kits of equipment which "bring to life" things you study.

### Find Out What NRI Offers

NRI has trained thousands for successful careers in Radio-TV. Study fast or slow—as you like. Diploma when you graduate. Mail coupon now. Paste it on a postcard or mail in envelope. **ACTUAL LESSON FREE**. Also 64 page catalog that shows opportunities, shows equipment you get. Cost of NRI courses low. Easy terms. **NATIONAL RADIO INSTITUTE, Dept. 7MB3, Washington 16, D. C.**

### N.R.I. TRAINED THESE MEN FOR SUCCESS



"I was repairing Radios by 10th lesson. Now have good TV job." **M. R. LINDEMUTH**, Fort Wayne, Ind.



"Doing spare time repairs on Radio and TV. Soon servicing full time." **CLYDE HIGGINS**, Waltham, Mass.

"I had a successful Radio repair shop. Now I'm Engineer for WHPE." **V. W. WORKMAN**, High Point, N. C.



"There are a number of NRI graduates here. I can thank NRI for this job." **JACK WAGNER**, Lexington, N. C.



**VETERANS** Approved Under G. I. Bills

## SEND FOR BOTH FREE

### National Radio Institute

Dept. 7MB3, Washington 16, D. C.

Mail me Sample Lesson and 64-Page Catalog FREE. (No salesman will call. Please write plainly.)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Accredited Member National Home Study Council

