

PRACTICAL

ELECTRONICS

APRIL 1973

20p

SIMPLE ALL AROUND **SECURITY ALARM**



Also Inside: **NOVEL BATTERY ELIMINATOR**
P.E. Sound Synthesiser—**VOLTAGE CONTROLLED**
OSCILLATOR and INVERTER

is this the price you pay?

Probably, if you're still using an ordinary soldering iron. Ordinary soldering irons can cause damage to transistors and integrated circuits — damage which wastes time and costs money. Now, with the unique ANTEX X25 and CCN low leakage soldering irons no harm can come to the most delicate equipment, even when soldered 'Live'. **(You could be making quite a saving).**

All prices mentioned exclusive of VAT



MODEL X25
220-240 Volts or 100-120 Volts. The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C.

This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally-made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed.

PRICE: £1.75 (rec. retail)

Suitable for production work and as a general purpose iron.

MODEL CCN
220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage.

Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64".

PRICE: £1.80 (rec. retail)
OR Fitted with triple coated, iron nickel and Chromium bit 1/8".
PRICE: £1.95 (rec. retail)

MODEL G
18 watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110. **PRICE: £1.83** (rec. retail).

MODEL CN
Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24.
PRICE: £1.70 (rec. retail)

MODEL CN2
Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220.
PRICE: £1.70 (rec. retail)

MODEL MES.KIT
Battery-operated 12v. 25 watt iron fitted with 15" lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder"
PRICE: £1.95 (rec. retail)

MODEL SK.1 KIT
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.
PRICE: £2.75 (rec. retail)

MODEL SK.2 KIT
Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.
PRICE: £2.40 (rec. retail)



From radio or electrical dealers, car accessory shops or in case of difficulty direct from:—
ANTEX LTD. FREEPOST
(no stamp required) **PLYMOUTH**
PL1 1BR Tel: 0752 67377.

- Please send the ANTEX colour catalogue.
- Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME

ADDRESS

PRACTICAL ELECTRONICS

VOLUME 9 No. 4 APRIL 1973

CONSTRUCTIONAL PROJECTS

- P.E. SOUND SYNTHESISER—3** *by G. D. Shaw*
Voltage controlled oscillators and inverter 306
- NOVEL BATTERY ELIMINATOR** *by J. S. Goddard*
A stabilised 9V supply from the mains 313
- HI FI TAPE LINK** *by P. S. Ewer*
Constructional details 326
- ALL-AROUND SECURITY ALARM** *by J. Andrews*
Domestic burglar alarm with fail-safe features 338
- P.E. DIGI-CAL—10** *by R. W. Coles*
M counter board 342

GENERAL FEATURES

- ELECTRONIC TIMEPIECES—2** *by J. B. Dance*
Quartz crystal control and time displays 318
- DESIGNING WITH I.C.s—7** *by A. Foord*
Counters and displays 350

NEWS AND COMMENT

- EDITORIAL—Fashions In Building** 305
- BOOK REVIEWS**
Selected new books we have received 317
- SPACEWATCH** *by Frank W. Hyde*
Space budget—Lunokhod 2—Skylab 325
- ELECTRONORAMA**
Focus on Post Office telephone paging system 334
- STRICTLY INSTRUMENTAL** *by K. Lenton-Smith*
Comments on contemporary sounds 337
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry? 349

VALUE ADDED TAX

Prices quoted in this issue were correct at time of going to press. From 1st April 1973 there will be no purchase tax, but a large number of goods will carry Value Added Tax.

Our May issue will be published on Friday, April 13, 1973

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2-65.

Connoisseurs


SAU2 Pick-up Arm

Recognised as one of today's most advanced pickup arms it features.


- Auto-bias Compensator
- Hydraulic Lowering Device
- Precision Balance
- New Adjustable Head Shell



Precision Stylus Balance

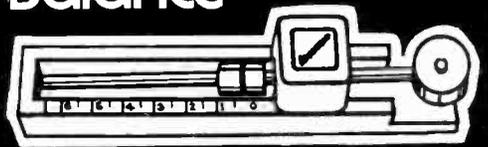

SCU1 Stereo Cartridge

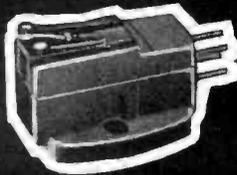

A quality cartridge designed specifically for the person who appreciates his equipment.

An inexpensive and useful gift for the hi-fi enthusiast. It's simplicity itself to work out and adjust the weight of the stylus so as to give correct working conditions and perfect results. Covers a range from 0.6 grams with 1/2 gram calibrations.

A.R. SUGDEN & CO. (ENGINEERS) LTD.


Atlas Mill Road, Brighouse, Yorkshire HD6 1ER. Telephone 2142

VISIT OUR STAND AT SONEX

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT! HANDY! TIDY!

DISCOUNT PRICES

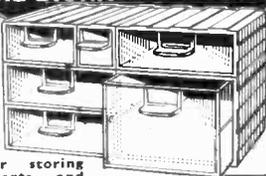

Ideal for storing small parts and components. Rigid plastic units. Countless vertical and horizontal combinations of sizes for wall, bench or table top. Transparent plastic drawers have label slots/handles. Trade prices: Single Units (2 1/2in x 2 1/2in x 5in deep) £1.35 for 12; Double Units: £2.25 for 12; Treble Units £2.35 for 8; Double Trebles (2 drawers) £3.65 for 8. Extra large, £3.30 for 8. Carr. 35p. Orders over £10, post free. Quantity Discounts: 5% in £1 for orders over £5, 7 1/2% over £10, 10% over £20. Quotations for larger quantities.

5 SIZES ALL INTERLOCK

4-WAY IN-LINE POWER PANEL PATENT CABLE LOCK



Modern, slimline power panel. Countless uses in home, office and factory. Perfectly safe and unbreakable. Can be mounted on wall or trailed anywhere in room. Neat, rubber base, smart P.V.C. outer cover. Black, £1.95, White, £2.40, p. & p. 30p. State cable length required at 10p yard with Free 13 amp plug.

IVORYET LIMITED (Dept. PE4) 124 Cricklewood Broadway, London, N.W.2 Tel. 01-450 4844

OSMABET LTD.

We make transformers amongst other things

AUTO-TRANSFORMERS
500W, £8.85; 750W, £12; 1,000W, £15; 1,500W, £21; 2,000W, £27; 3,000W, £37.50; 4,000W, £52.50.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6.3V 1.5A, £1.05; 3A, £1.30; 6A CT £2.05; 12V 1.5A, £1.35; 3A CT, £2.15; 6A CT, £2.80; 18V 1.5A CT, £2.15; 24V 1.5A CT, £2.15; 3A CT, £2.80; 3A, £2.30; 8A, £2.75; 12A, £2.40; 40V 3A CT, £3.75; 50V 6A CT, £10.

MIDGET RECTIFIER TRANSFORMERS
For FW rect., 200/240V a.c. 0-0-9V 0.3A, 12-0-12V 0.25A or 20-0-20V 0.15A, £1.45 each; 0-0-9V 1A, £1.15; 12-0-12V 1A or 20-0-20V 0.75A, £1.85 each.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec. tapped 3-7.5-15 ohms, A-A 6.6 K Ω 30W (KT86, etc.), £4.65; A-A 3K Ω 50W, £7.50; 100W (EL34, KT88, etc.), £12.50. Multi O/P 10W, £2.25.

MAINS TRANSFORMERS FOR POWER AMPLIFIERS
Prim. 200/240V a.c., T $\frac{1}{2}$ 6 sec, 425-0-425V 500 Ma, 6.3V CT 6A, 6.3V CT 6A, 0-5-6.3V 3A, £14.25; TX1 425-0-425V 250Ma, 6.3V CT 4A, 6.3V CT 4A, 0-5-6.3V 3A, £9; 250V 100Ma, 6.3V 2A, £2.70.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30 to 400W, with price list of transformers and choices specified. 30p. Bernard's Amplifier Manual, 5 to 1,000W, 75p.

LOUDSPEAKERS FOR POWER AMPLIFIERS
FANE 15W w/tweeter, £4.99; 50W, £10.90; 60W, £12.90; 100W, £22.50; BAKER 25W, £6.40; 35W, £7.20. Hi-Fi Major Module, 20W W/Tweeter and Xover 30-17KHz, £9.20; EM1 13in x 8in, £2.25; 8in x 5in 8 Ω , £1.85; Goodmans Tweeter 3 Ω , £2.

LOUDSPEAKERS
2 1/2in 16 Ω , 2 1/2in 25 Ω , 3in 30 Ω , 75p; 3 1/2in 3 or 15 Ω , 4in 8 or 15 Ω , 5in 3, 8, 15 or 25 Ω , 5in x 3in 3, 8, 15 or 25 Ω , £1.05 each; 6 1/2in 3 Ω , 6in x 4in 8 or 25 Ω , 7in x 4in 3 or 15 Ω , 8 x 2 1/2in 3 Ω , £1.25; 8in x 5in 3, 8, 15 or 25 Ω £1.50; 10in 15 Ω , £2.50; 10 x 6in 3 Ω , £2.25.

SPEAKER AUTO MATCHING TRANSFORMERS
12W, 24 or 8 or 15 Ω , up or down, £1.05.

BULK TAPE ERASERS
Instant erasure, tape spools, cassettes, demagnetises tape heads a.c. 200/240V, £2.50 plus 25p P. & P.

RELAYS Sub mini, 6/9V, 250 Ω .
15, 20 or 30V d.c., 2 C/O's 50p each.

12V DC FLUORESCENT LIGHTING
Silicon transistor inverter for 20W tube, £5.75.

PAPER CONDENSERS
Tubular W/E 2.2 mfd, 250V Xovers, etc., 16p, £6 100. Block 4 mfd, 800V, 75p, 1,500V, £1.25.
Carriage extra on all orders, etc.

S.A.E. ENQUIRIES-LISTS. MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YQ
Tel. 01-958 9314

4-STATION INTERCOM



Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 40p. **£7.25**

MAINS INTERCOM (new model)
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £14.40. P. & P. 55p extra.

INTERCOM/BABY ALARM




Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 14p. P. & P. 25p. **£3.35**

Transistor TELEPHONE AMPLIFIER

Why not boost your business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 14p extra. P. & P. 22p. Full price refunded if not satisfied in 7 days. **£2.99**

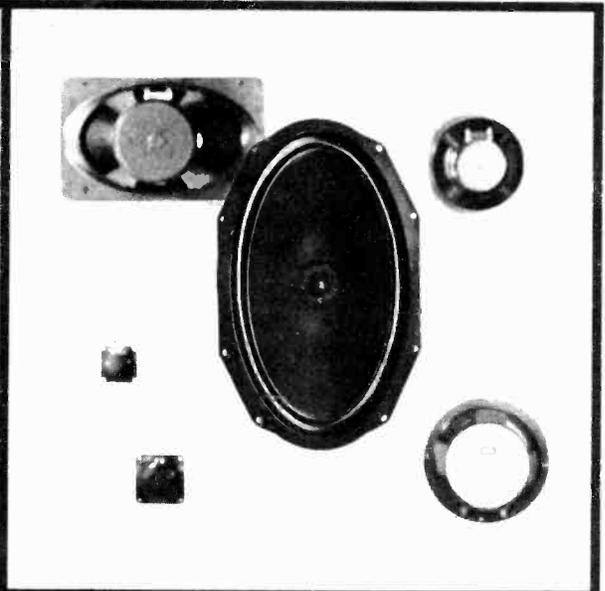WEST LONDON DIRECT SUPPLIES (PE/4)
169 KENSINGTON HIGH STREET, LONDON, W.8



A Speaker System to meet every need

EMI provides the speaker system to suit your needs and your budget, all with one thing in common, superb quality of sound over the full audio range. Choose from new elegant speaker enclosures for the connoisseur; home assembly enclosure kits and matched speaker kits and a range of basic chassis loudspeakers as used in the highest quality sound reproduction equipment.

Send for full details and name of your nearest stockist.

To: EMI Sound & Vision Equipment Limited, EMI Pathe Division, 252 Blyth Road, Hayes, Middlesex. 01-573 3888
Please send me details of EMI loudspeaker's and name of nearest stockist.

Name _____
Address _____

PE/4

EMI Perfection in Sound

A member of the EMI Group of Companies. International leaders in Electronics, Records and Entertainment.

JAMES SCOTT

SALE OF SURPLUS ELECTRONIC EQUIPMENT

The following items are available for immediate delivery at very competitive prices—

SCANNING ALARM INDICATOR

Can be used for Automatic Monitoring of All Types of Test Points (Up to 25)


Incorporates Auto and Manual Facilities Illuminated Digital Identification Double Pole Gold Plated Contacts on Uni-selector

Units Supplied Untested Less Indicating Meter. Price £25 00 Carriage and Insurance (U.K. only) £1 50



DOSIMETER CHARGING UNIT TYPE 200

PORTABLE INSTRUMENTS USED TO CHARGE QUARTZ FIBRE TYPE POCKET DOSIMETER TO ZERO. SUITABLE FOR USE WITH ALL STANDARD TYPES OF QUARTZ FIBRE DOSIMETERS HAVING A MAXIMUM OUTSIDE CHARGING END DIAMETER OF 0.605IN. TELEPHONE TYPE A.C. AND GENERATOR THE OUTPUT OF WHICH IS RECTIFIED AND CHARGES UP A RESERVOIR CAPACITOR TO A MAXIMUM POTENTIAL OF ABOUT 300 VOLTS D.C. SUPPLIED LESS GENERATOR HANDLES. PRICE £1 50. P & P 20p

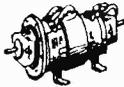

SEALED RELAYS (NATO APPROVED)

GE4 4 pole c/o 24V 670 ohm. GEC 2 pole on/off 24V 670 ohm. GEC 2 pole c/o 65V 5,000 ohm. STC 2 pole c/o 12V 170 ohm. Price each 75p. P & P 10p.



PC102 Supply voltage 220-250V a.c. Output voltages 21 Volts d.c. at 330MA 21 Volts a.c. at 540MA

NEWMARKET TRANSISTORS

NKT361	73p	NKT12329	27p	2N2222	18p	NKT218	23p
NKT352	25p	NKT12429	27p	NKT12	30p	NKT221	30p
NKT406	80p	NKT13329	27p	NKT72	25p	NKT222	18p
NKT420	£1 80	NKT13429	27p	NKT73	22p	NKT223	25p
NKT450	30p	NKT15229	27p	NKT121	21p	NKT224	22p
NKT603	22p	NKT20329	28p	NKT124	28p	NKT227	25p
NKT613F	28p	NKT80111	85p	NKT125	38p	NKT237	29p
NKT674	30p	NKT80113	98p	NKT126	35p	NKT238	18p
NKT677	18p	NKT80125	80p	NKT127	23p	NKT249	29p
NKT713	27p	BC107	8p	NKT128	18p	NKT261	19p
NKT734	24p	BC108	8p	NKT129	22p	NKT270	18p
NKT736	30p	BCY70	13p	NKT135	24p	NKT271	16p
NKT773	23p	NKT15229	17p	NKT137	30p	NKT272	15p
NKT7916	20p	BSY95A	10p	NKT142	48p	NKT273	18p
NKT3055	23p	2N697	13p	NKT143	48p	NKT274	18p
NKT6917	27p	2N706	8p	NKT212	23p	NKT275	21p
NKT10339	23p	2N814	15p	NKT213	23p	NKT278	18p
NKT10419	17p	2N918	28p	NKT214	21p	NKT301	70p
NKT10439	25p	2N930	22p	NKT215	19p	NKT302	85p
NKT10519	20p	2N1990	22p	NKT217	48p	NKT303	70p
						NKT304	75p



S.T.C. RELAYS—BRAND NEW

TYPE	CONTACT FORM	NOMINAL COIL VOLTAGE	COIL RESISTANCE (OHMS)	PRICE EACH
250 ARO	4 CHANGEOVER	6V d.c.	52	£0 68
250 ABO	4 CHANGEOVER	48V d.c.	2,500	£0 68

TYPE	CONTACT FORM	COIL VOLTAGE	SWITCHING CURRENT	PRICE EACH
SL722212	3 Pole on/off	12V a.c.	10A at 440V a.c.	£1 00
SL762715	2 Pole C/O	220V a.c.	10A at 440V a.c.	£0 87

TYPE	CONTACT FORM	COIL VOLTAGE	COIL RESISTANCE	PRICE EACH
SP13372	Single Pole C/O	6V d.c.	140 ohm	£0 40
SP13366	Single Pole C/O	12V d.c.	350 ohm	£0 40
11301D	Single Pole C/O	18V d.c.	875 ohm	£0 40

UNISELECTOR SWITCHES

6 bank 25 way 75 coil 50V d.c. operation. Mounted on Modular Type Chassis with front panel containing 20 illuminated Push Button Switches. Completely wired for operation. Price £15 P & P £0 55



AUTOMATIC CYCLER UNIT

This unit generates stepping pulses (50V d.c.) at intervals of 6 pulses per min. to 120 pulses per min.—continuously variable. Can be used for Automatic Stepping of one or more uniselector switches shown above. Price £12 50 P & P £0 45

NEWMARKET PACKAGED AUDIO AMPLIFIER

PC1 150mW Audio Amplifier. Price £1 00 each. P & P £0 10
PC10 Magnetic replay head amplifier supply voltage 9V d.c. Input impedance 150. Price £0 90 each. P & P £0 10


WE HAVE A LARGE RANGE OF CAPACITORS AND RESISTORS. PLEASE SEND A STAMPED AND ADDRESSED FOOLSCAP ENVELOPE FOR YOUR CATALOGUE

POST & PACKING OVER £2—FREE OVER £1 AND UNDER £2—15p. UNDER £1—10p. UNLESS SPECIFICALLY MENTIONED. P & P U.K. ONLY

JAMES SCOTT (ELECTRONIC ENGINEERING) LIMITED
CARNYTE INDUSTRIAL ESTATE, GLASGOW G32 6AB
TEL: 041-778 4206

NOT JUST A RADIO BUT A COMPLETE COMMUNICATIONS RECEIVER BATTERY/MAINS PORTABLE RECEIVER

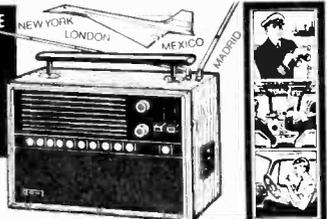What radio priced at under £120 gives you such a varied choice of transmissions?



Picks up ALL THE USUAL BBC Programmes. All the new local radio stations. Continental World-wide transmissions. Pop Pirates. Radio Hams. Aircraft. Shipping. Police. Taxis. RAC. AA. Fire Brigade. TV Sound. Ambulance and 1,000s more.

CASH PRICE £49.50 + 50p P. & P. or £14.50 dep. + 50p P. & P. and 6 months at £7 (£56.50)

THE BEST PORTABLE RADIO EVER MADE! We think so. As well as the standard long and medium wavebands it has three short wave bands (including the Marine and Trawler Band) AND NO LESS THAN THREE VHF BANDS. Listen to your favourite BBC programme and then—a flick of a switch—tune into the control tower and hear a "crippled airliner" being talked down to safety. Or listen to the trawlers and ocean-going liners—Eavesdrop on the taxi-cabs, fire brigades, ambulances, AA, RAC and 100s of other RT mobiles! Extensive shortwave coverage can give you Australia, Pakistan, North America, Far East, etc. World famous manufacturer. FULL 3-YEAR WRITTEN GUARANTEE. Beautifully finished in Teak Wood and Stainless Steel. Portable 12in x 9in x 4in, using standard batteries—or can be plugged directly into mains. 14 transistors, 6 diodes, 1 thermistor, internal ferrite rod aerial PLUS two external telescopic antennae—with sockets for additional aerials, or car aerials. Automatic Drift-Free Reception. Sliding tone control. Hi-Fidelity earphone for private listening. local DX switch. FREQUENCIES—Long W 150–350kHz. Medium W 540–1605kHz. Marine 1.6–4 MHz. Short W 3.7–9MHz. Short W 2 9–22MHz. F.M. (VHF) 88–108MHz. Aircraft (VHF) 108–136MHz. Public Service (VHF) 148–174MHz. NOTE—The Ministry of Posts & Telecommunications state a Licence (not generally available to the public) is required for the reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

PROFESSIONAL 2 CHANNEL WALKIE-TALKIE SYSTEM

JUST ARRIVED—a NEW system from Switzerland—the home of precision built electronics equipment. GENUINE 2-WAY WALKIE-TALKIE SYSTEMS. Ideal for all crowd control, doctors, fishermen and general marine use. The telescopic antenna pulls in the voice at the other end with crystal clear clarity—even 8 miles away! Frequency 29.9MHz (interchangeable according to your licence stipulation). Battery-operated—no wires. A tremendous time and money saver. 2 Units complete with FREE carrying cases. Credit terms available, details on request. NOTE: Licence required to operate.

Send 5p stamp for Discount Brochure of Unusual Frequency Radios SCIENTIFIC & TECHNICAL (PE4), TOWERFIELD TRADING ESTATE, SOUTHBEND, ESSEX



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME: _____ ADDRESS: _____ EB43

BLOCK CAPS please



There are 195 other good reasons for buying AMTRON electronic kits

Apart from the five items shown above, there are another 195 kits to choose from in the vast AMTRON range of electronic kits.

A few examples of equipment you can construct from AMTRON kits are: Power supplies, preamplifiers, amplifiers, accessories for

musical instruments, amateur and radio control transmitters and receivers, battery chargers, electronic car accessories, psychedelic lighting equipment, measuring instruments, tuners, receivers, I.C. digital equipment.

The unique quality of AMTRON kits is their simplicity of construction

which appeals to dabbler and expert alike.

Only 1st class fully guaranteed components are used — solder is included with every kit.

Prices range from £1.10 to £80 and each kit is sold in a protective blister pack containing complete instructions.

Write for catalogue.

Should you experience any difficulty in obtaining AMTRON kits please contact us direct.

TRADE & EDUCATIONAL ENQUIRIES WELCOME



AMTRON U.K. 4 & 7 CASTLE STREET, HASTINGS, SUSSEX. TEL: HASTINGS 2875


UNISOUND FOR THE NEW SOUND



AT
£26.12
INC.
VAT

It's the RT-VC system that screws together to save you pounds! Unisound comprises two superb speakers and an amplifier/record deck plinth—all beautifully finished in simulated teak. The stereo amplifier (4 watts per channel into 8 ohms) is based on the famous Mullard Unilex system brought up-to-date by RTVC using integrated circuits. Turntable is the proven Garrard 2025TC complete with stereo cartridge and tinted acrylic cover. Speakers are big EMI Twin-cone units all ready for mounting in their elegant cabinets, which simply need screwing and glueing together. Easy step-by-step instructions. £26.12 complete plus £1.40 packing + £1.40 post. Diamond Stylus £1.25 extra. Stereo headphones with adaptor £4 extra. Send for leaflet.

AN RTVC EXCLUSIVE DESIGN

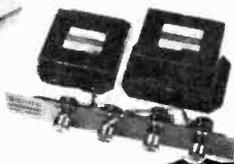

UNISOUND MODULES ONLY £6.95 + 50p. p. & p.

For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips very low distortion at all power levels, over the audio spectrum.

RTVC No price in

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

THE TOURIST PB CAR RADIO KIT AN INCREDIBLE BUY ONLY FROM **RTVC**



£7.70
inc. vat


The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modularised IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire. The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7" wide, 2" high and 4½" deep.

* Circuit diagram and comprehensive instructions 50p free with parts.

* Fully retractable lockable car aerial £1.25 post paid.

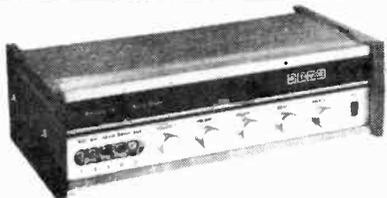PRICE ONLY £7.70 p. and p. 55p
Speaker with baffle and fixing strips £1.50. 25 p. & p., post free if bought with the kit. Send for leaflet.



RELIANT Mk IV


A GOOD QUALITY AMPLIFIER—12 Watts £10.50 (inc. VAT). 20 Watts £13.50 (inc. VAT)

*5 Electrically Mixed inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV Inputs. 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.) All 250mV sensitivity. Power output: 12/20 watts into 8 ohms. Size approx. 12½ x 6 x 3½ ins.

12W version **£10.50** plus 60p
20W version **£13.50** p & p

SOUND 50

50 WATT AMPLIFIER. Output Power: 45 watts R.M.S. (Sine Wave) Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K. Size: **£38.51** 19½ x 10½ x 8ins. Amplifier £31.85 plus £1.50 p. and p. (inc. VAT)

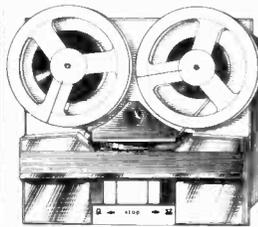

PE TAPE LINK CONSTRUCTORS

Suitable 3 speed tape deck, less leads. Caters up to 7ins. spools. Unused but store soiled hence no warranty. **£8** plus £1 p & p

* Denotes VAT has been absorbed in the price without increase on VISCOUNT audio systems.

crease with VAT!

VISCOUNT III AUDIO STILL ONLY £52* COMPLETE

14 + 14w. r.m.s. 40Hz to 40kHz ± 3dB. Total distortion at 10w. at 1kHz - 0.1%. This is real value for money! We have designed 2 systems and the heart of them both is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder.

For both systems we have chosen the famous Garrard SP25 Mk. III deck, with fitted magnetic cartridge, which comes complete with simulated teak plinth and tinted acrylic cover.


The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

PRICES: SYSTEM I
 Viscount III R 101 amplifier £24.20 + £1 p & p
 2 Duo Type II speakers £15.40 + £2.20 p & p
 Garrard SP25 Mk. III with MAG. cartridge plinth & cover £25.00 + £1.75 p & p
 total £64.60

Available complete for only £52* + £3.50 p & p

PRICES: SYSTEM 2
 Viscount R 101 amplifier £24.20 + £1 p & p
 2 Duo Type III speakers £35.20 + £3.30 p & p
 Garrard SP25 Mk. III with MAG. cartridge plinth & cover £25.00 + £1.75 p & p
 total £84.40

Available complete for £69* + £4 p & p

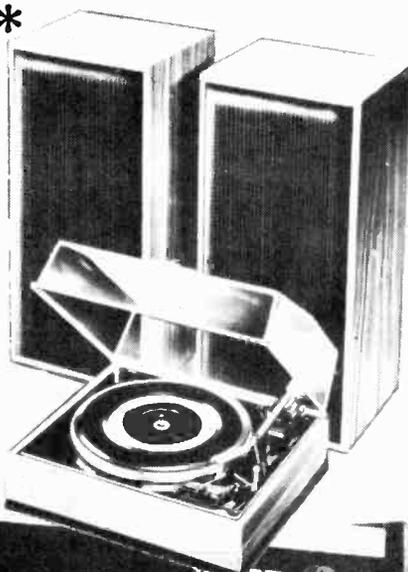

SPEAKERS: Duo Type II Size approx. 17in. x 10½in. x 6½in. Drive unit 13in. x 8in. with parasitic tweeter. Max. power 10 watts ohms. Simulated Teak cabinet. £15.40 a pair (inc. VAT), £3.30 p. and p. Duo Type III Size approx. 23½in. x 11½in. x 9½in. Drive unit 13½in. 8½in. with H.F. speaker. Max. power 20 watts ohms. Freq. range 20Hz to 20KHz. Teak veneer cabinet.

SPECIFICATION R101: 14 watts per channel into 3 to 4 ohms (suitable 3-15 ohms.) Total distortion @ 10W 1kHz @ 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within idB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. Signal-to-noise ratio: (all controls at max.)—P.U.1. and radio — 65dB, P.U.2 — 58dB. Cross talk better than — 35dB on all inputs. Size approx. 13½in. x 9in. x 3½in. Send S.A.E. for fully illustrated brochure. 12 month's written guarantee.

ONLY FROM US

TIMES OF OPENING: Acton—Mon.—Sat. 9.30-5.
 Closed all day Wed.
 Edgware Rd.—Mon.—Sat. 9.30-5. Closed all day Thurs

VISIT OUR SHOWROOMS **RTVC**
 Radio and TV Components (Acton) Ltd.
 21c High Street, Acton, London W3 6NG
 323 Edgware Road, London W2
 Mail orders to Acton. Terms C.W.O.
 Goods not despatched outside U.K.
 All enquiries S.A.E.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX. G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY 95p

POST & PACKING 35p EACH



TELEPHONE DIALS

Standard Post Office type
Guaranteed in working order.

ONLY 25p

POST & PACKING 15p

TESTED AND GUARANTEED PAKS

B79	4	1N4007 Sil. Rec. diodes, 1,000 PIV 1 amp. plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values	50p
H9	2	OCPT1 Light Sensitive Photo Transistor	50p
H28	20	OC200/1/2/3 PNP Silicon unceded TO-5 can	50p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6.8-43V	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	50p
H38	30	Short Lead Transistors, NPN Silicon Planar types	50p
H39	10	Integrated circuits 6 gates BMC 962, 4 flip flops BMC 945	50p
H40	20	BFY 50/2, 2N696, 2N1613, NPN Silicon unceded TO-5	50p
H41	2	BD131/BD132 Complementary Plastic Transistors	50p

UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	50p
B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	50p
H6	40	250mW Zener Diodes DO-7 Min. Glass Type	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	50p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev counter for any car with normal coil ignition system.

£1 each



OVER 1,000,000
TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very competitive prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc.

Audio NPN, similar to ZTX300, 2N3708/9 BC107/8/9, BC168/9, etc.

R.F. NPN and switching NPN Types also. Please state type of transistor required when ordering.

ALL AT 500 for £3, 1,000 for £5, 10,000 for £40

OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR VARIOUS TYPES P & P 25p £1

VALUE ADDED TO YOU On orders of £4 or over. See below:

Please read very carefully: We will give a discount to customers who send in an order for £4 or over. This discount will be equal to the V.A.T. rate current at this time. If your order does amount to £4 or over, all you need to send is the total cost of goods and postage as stated in this advertisement. No addition for V.A.T. is needed. V.A.T. for orders under £4: If the total cost of goods plus postage and packing is less than £4, kindly add 10% (10p in the £) to your remittance. Incorrect amounts will delay your order.

A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs **£3.50, post paid.**

A MUST for Colour T.V. Alignment.

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.I. Only 50p. 10p P & P on this Pak.

FREE CATALOGUE FOR TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS



100,000 Plastic Power Transistors in stock, more on way!
NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min. 15	HFE Min. 15	
	1-12	13-25	26-50
40 watt	20p	18p	16p
90 watt	24p	22p	20p

Range 2	VCE Min. 40	HFE Min. 40	
	1-12	13-25	26-50
40 watt	30p	28p	26p
90 watt	35p	33p	30p

Complementary pairs matched for gain at 3 amps. 10p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 10p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low

16 pin type at 16p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:
B.P.I. Transistor Equivalents and Substitutes: 40p
This includes many thousands of British, U.S.A., European and C.V. equivalents.
The Hifre Radio Valve & Transistor Data Book 9th Edition: 75p
Characteristics of 3,000 valves and tubes. 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. Post and Packing 21p
Send for lists of these English publications.

N.B.—Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BI-PRE-PAK LTD

DEPT 7 A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

Do it yourself comes to calculators.

The Advance Executive 8 is in kitform.

So, instead of paying £80.00, you need only pay £39.20 plus 75p postage and packing.

Moreover it should only take you three hours to build. (Dick Railton of Electronics Weekly holds the record at 2 hours 10 minutes – so far.)

Spend the time – and, we regret, the money and you'll have a calculator with: four functions; multiplication and division by a constant; chain calculations; automatic squaring; 8 digits.

It's superb value at twice the price.

Let alone half.



Please rush me your Executive 8 in kitform. I enclose my cheque for £39.20 and 75p postage and packing.

Name _____

Address _____

Post to Calculator Division,
Advance Electronics Limited,
Raynham Road, Bishop's Stortford, Herts.
Telephone: 0279 55155
Telex: 81510

Registered No.: 263834



IT'S FREE

FULLY ILLUSTRATED

ELECTRONIC COMPONENTS CATALOGUE

If you have not yet seen our latest catalogue, drop us a line right away and we will be delighted to forward a copy to you. In it you will find many useful components at very competitive prices, plus details of how you can receive **ONE POUNDS WORTH OF GOODS ABSOLUTELY FREE.**

MAPLIN ELECTRONIC SUPPLIES P.O. BOX 3, RAYLEIGH, ESSEX SS6 8LR

You may telephone any time of the day or night. Out of office hours your message may be left on our answering machine.

LOOK! HERE ARE JUST A FEW OF THE THOUSANDS OF LOW-PRICED ITEMS IN THE CATALOGUE.

EVERYTHING GUARANTEED BRAND NEW MARKED BY MANUFACTURER

BC107
BC108 only 10p each
BC109

115 Watt
Power Transistor 49p
2N3055.....
mounting kit supplied free

This very popular
FET 24p
2N 3819

Versatile Unijunction 28p
TIS 43 (SS43)

Until further notice
PRICE REDUCED
8 PIN DIL OP AMP

741C 36p

SPECIAL IC. for organ builders, 7 stage frequency divider in one 14 pin DIL package £2.63 or special price for pack of 12, £25.

Why not ask us to slip a data sheet in with your catalogue.

Postage and packing FREE in UK. But we have to ask you to send a 10p handling charge with order under 50p.



SOUND BARGAINS



GIANT POWER MULTI-WAVEBAND COMMUNICATIONS RECEIVER

WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

OUR PRICE £10-50
+40p P. & P.

No less than 3 VHF BANDS.

Picks up Aircraft Transmissions, Local

Radio, Continental and all BBC, VHF Stations plus

fascinating Public Service Transmissions we are not allowed to

mention! Even TV sound in certain areas. PLUS A SPECIAL

WEATHERBAND. Frequency ranges: MW340-1600kHz, FM88-108MHz,

Airband 108-135 MHz, VHF 145-175 MHz, 23 semiconductor 12 trans-

istors, 11 diodes and thermistors. Automatic frequency control 31in

telescopic aerial. Runs off mains a.c. 230/250V or off 4 F11 batteries, or


use re-chargeable nickel alkali cell. Finished in strong leather grained case with

carrying handle. Approx. size 10 1/2in x 6 1/2in x 3 1/2in. Written guarantee. Special

magnetic ear-piece for personal listening, dry batteries free. HURRY! Limited

quantity only from Sonic Sound.

OUR PRICE £28-95
+50p P. & P.

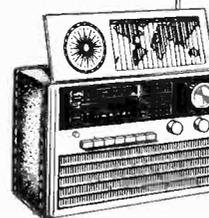

8 WAVEBANDS AND WORLD MAP & TIME ZONE DIAL

Tune into the world with this amazing communications receiver. A truly exceptional unit in performance and looks—leatherette with stainless steel trim. Looks good any-

where. Use either as a portable with standard batteries or plug it directly into 220-240V domestic mains supply. 14 transistors;

9 diodes; 1 thermistor. Internal ferrite rod antenna plus telescopic aerial. Separate tone, volume and

tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with Hi-Fi earphone for personal listening. Frequency

ranges: Long wave 150-350 kHz.

Medium 353-1605 kHz, Marine 1.6-4.5 MHz.

Short Wave 12-24 MHz, FM/VHF 88-108

MHz, Aircraft 108-135 MHz, PUBLIC SERVICE BANDS 135-174 MHz. Fully

guaranteed. N.B. The Ministry of Post &

Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.



SONIC SOUND AUDIO LTD.

(Dept. PE11), 372 EDGWARE ROAD LONDON, W.2. Tel. 01-723 0094
Callers welcome Mon. to Sat. 9 a.m.-6 p.m.

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way*.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified study method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.


You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

Specialist Booklet

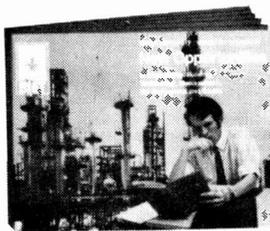If you wish to make a career in Electronics, send for your **FREE** copy of "NEW OPPORTUNITIES". This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. BPE14, ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

CL **BPE14**

NAME (BLOCK CAPITALS)

AGE...

ADDRESS

SUBJECT OF INTEREST

FERRANTI ZN414 MICROCIRCUIT RADIO

AS SEEN ON TV! **Only £1.32** WITH FREE DATA

WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS

BFS59	15p	ZTX310	9p	ZTX504	43p	ZS170	10p
BFS60	20p	ZTX311	10p	ZTX510	17p	ZS171	13p
BFS61	20p	ZTX312	10p	ZTX530	21p	ZS172	16p
BFS96	15p	ZTX313	11p	ZTX531	22p	ZS174	17p
BFS97	23p	ZTX314	13p	ZTX550	17p	ZS176	23p
BFS98	20p	ZTX320	31p	ZTX551	17p	ZS178	38p
ZTX107	9p	ZTX330	15p	2N3055	72p	ZS270	11p
ZTX108	8p	ZTX331	16p			ZS271	16p
ZTX109	11p	ZTX382	13p	DIODES		ZS272	18p
ZTX212	14p	ZTX383	15p	ZS120	8p	ZS274	19p
ZTX213	14p	ZTX384	18p	ZS121	10p	ZS276	26p
ZTX214	15p	ZTX450	17p	ZS122	13p	ZS278	37p
ZTX300	12p	ZTX451	17p	ZS123	16p		
ZTX301	13p	ZTX500	12p	ZS124	18p	ZENERS	
ZTX302	17p	ZTX501	13p	ZS140	25p	KS030A to	
ZTX303	14p	ZTX502	17p	ZS141	43p	KS180A—	
ZTX304	21p	ZTX503	14p	ZS142	33p	all types 19p	

ALL DEVICES TOP GRADE, BRAND NEW, AND FULLY GUARANTEED WE CAN SUPPLY ANY FERRANTI DEVICE. Send S.A.E. for quotation. R.C.A. CA3090Q £4.73; CA3075 £1.49. MOTOROLA, MJE2955 £1.17; MJE3055 72p; 2N4444 £2.48. P.E. TRIFFID. ZT1711 24p; 2N1132 25p. POSTAGE AND PACKING 10p. Free over £2. Send S.A.E. for our full price list and data sheet.

ALL PRICES INCLUDE V.A.T. 10% DISCOUNT IF YOU ORDER BEFORE MARCH 28th

DAVIAN ELECTRONICS
PO BOX 38, OLDHAM, LANCS. OL2 6XJ

Lasky's Audio-Tronics Catalogue 1973

The great 1973 edition of Lasky's famous Audio-Tronics catalogue is available—FREE on request. The 48 newspaper size pages—many in full colour—are packed with 1,000s of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape recording and Audio Accessories. See the great new Lasky's Credit Plan Scheme—enabling you to buy your ideal choice of equipment on easy terms.

FREE

Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME

ADDRESS

PE2

LASKY'S RADIO LIMITED, 3-15 CAVELL STREET, LONDON E.1.

SAXON ENTERTAINMENTS

STANDARD and CUSTOM-BUILT AUDIO and ELECTRONIC EQUIPMENT
NEW and SECONDHAND MUSICAL INSTRUMENTS. MAIN DISTRIBUTORS
FOR A.K.G. HIGH QUALITY MICROPHONES

SA25-SA35-SA100

LOW-PRICED AUDIO MODULES FOR
DOMESTIC and COMMERCIAL USE



THESE THREE MODULES HAVE ENJOYED UN-
PARALLELED SUCCESS DURING THE FIRST FEW
MONTHS OF THEIR BEING MADE AVAILABLE TO
THE GENERAL PUBLIC. WE ARE PLEASED TO
ANNOUNCE THAT WE CAN NOW OFFER FAST
DISPATCH ON MOST OF OUR ADVERTISED ITEMS,
INCLUDING THESE THREE MODULES.

SA25 £2.95 carr. free

25 WATTS R.M.S. 7 transistors, 7 diodes

SA35 £4.45 carr. free

35 WATTS R.M.S. 7 transistors, 7 diodes

SA100 £10.90 carr. free

100 WATTS R.M.S. 11 transistors, 6 diodes

ALL THREE MODULES HAVE OPEN AND SHORT
CIRCUIT PROTECTION, AND THE SA100 IS PROOF
AGAINST OVER-DISSIPATION AND FAULTY IN-
DUCTIVE LOADS.

ONLY ADVANCED DESIGN TECHNIQUES MAKE
THESE EXTRAORDINARILY LOW PRICES POSSIBLE.

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	20-40,000Hz ± 1dB
Distortion	0.2% at 1kHz
Loads	4 to 16 ohms
Quiescent current	15mA
Noise	Better than -75dB
Supply voltage	25-45V, SA25/35 40-70V, SA100
Size	4½in × 4in × 1in (SA100) 4in × 3in × 1in (SA25, SA35)

Circuits, connecting instructions and application data
are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 and SA100 AUDIO MODULES

PU45	Unstabilised supply for 2 SA25/35's, £4.90.
PU70	Unstabilised supply for one or two SA100's, £7.75, carr. 40p
MT45	Transformer for above, heavy duty, £2.85, carr. 20p
PS45	Stabilised module for 2 SA25's or two SA35's, £3.50, carr. free
MT70	Transformer for PS70, £4.90, carr. 40p
PS70	Stabilised supply module for one or two SA100's, £4.90, carr. free

ALL MODULES ARE BUILT ON GLASS FIBRE P.C.
BOARD

CALLERS AND MAIL
ORDER:
351 Whitehorse Road
Thornton Heath, Surrey
Tel. 01-689 3685

CALLERS ONLY:
OUR NEW DISTRIBUTORS.
CIRCLE SOUND
328-330 The Banks
Rochester.
Medway 404199

BUSINESS
HOURS:
9.30 a.m. to
5.30 p.m.

TERMS OF BUSINESS: C.W.O. or
C.O.D. (35p extra). All cash in regd.
envelopes please! Telephone orders
to our CROYDON BRANCH. TRADE
AND EXPORT ENQUIRIES
INVITED

OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE

Featuring a rugged class A driver stage, this module will run
from all our mixers etc., and most other makes of mixer. It
delivers 120W into an eight ohm load and employs 4 TO3
can (115W) output transistors.

SPECIFICATION

Power output	120W into 8 ohms
Freq. response	20-20,000Hz ± 2dB
Input sensitivity	200mV into 10K
Construction	Fibreglass board
Size	8in × 4in × 4in (5in with supply)
Low distortion parallel push-pull output stage.	

NEW: 160 Watt version & supply £27.90

£13.90+20p carr. or with
supply £18.95+40p carr.



SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with
outputs from 5-100W. Does not impose a heavy load on
the amplifier, or, if connected in the wrong polarity, cause
any damage, as with some units.

Operation is simplicity itself and the unit is fully fused. The
unit is supplied to function from bass notes but may easily be
converted to respond only to treble or mid-range notes by
the addition of components costing less than 5p.



£8.90 carr. free

THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3,000W (3kW) this unit is unique for its price in that not only bass middle
and treble but also master controls are provided. Two amplifier sockets eliminate the need for
split leads, etc. Supplied in tough white steel case with a blue
hooded cover. Fully guaranteed.

£19.75 carr. 30p

£15.80 carr. 30p
SAXON STEREO
CONTROL UNIT

MONO VERSION £6.50, carr. 20p
(As illustrated below, S.A.E. details. 9V operation)
OUTPUTS UP TO 1V RMS



Two decks, and full headphone monitoring. The unit is mains operated and measures 17½in × 3in
× 4in deep and is finished with a smart white on black fascia. The controls are: Left/Right deck
fader, volume, bass, treble, headphone selector and volume, microphone volume, bass, treble,
mains on/off. THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCO-
THEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE.

COMPLETE AMPLIFIERS

THE CS 100. £34.90 carr. free

This versatile unit is now available in a black vynide
case and so represents even better value than ever,
delivering speech and music powers of up to 100W
R.M.S. and continuous signal outputs of 70W.

Two individually controlled inputs with wide range
bass and treble controls. Ideal for small groups, D.J.'s, etc



The SAXON 100. £48.50, carr. free.

With an R.M.S. output of 120W speech and music,
100W continuous power, four individually controlled
F.E.T. input stages and wide range bass and treble
controls, this amplifier has established itself as a
unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains ! ! !

12in 25W 8/15 ohms £5.95, carr. 30p. 15in 50W 8/15 ohm, £14.50, carr. 50p.
12in 40W 15,000 gauss magnet system 8/15 ohm, £11.50, carr. 40p.

A.K.G. MICROPHONES suitable for disco, group or general P.A. use
D11DHL r.r.p. £11, our price £9.45 post free.

D190C High Z r.r.p. £21.50, our price £17.45 post free.

D1000C 24 ct. gold plate r.r.p. £37, our price £32 post free.

SEND S.A.E. FOR
OUR A.K.G. PRICE
LIST. DISCOUNTS
ON ALL MICS.

PCB'S FROM PHONOSONICS



TAPE NOISE LIMITER

All PCB's Fibreglass, Drilled, Roller Tinned Circuit Diagram and Assembly. Notes Free with each PCB. Rotary Pots supplied as standard except where stated. PCB's designed by Phonosonics except where stated otherwise.

DESIGNS PUBLISHED IN P.E.

AURORA (Apr./Aug. 71) Multichannel Sound Controlled Light S/c's (excl. SCR's), Rs, Cs, Cores, Pots., 8 ch., £17.75; 4 ch., £10.15. Power Supply (supplies 8 chans.), unstab., £2.85; stab., £3.65. PCB (4 1/2in x 11in) for P/A and 4 chans. incl. pots, £2.35. PCB (4 1/2in x 5in) for PSU, Sync. Gen. 8 cores, 8 SCR's, £1.35.

A.F. SIGNAL GENERATOR (Nov. 72) S/c's, Rs, Cs, Pots, Sw's, £2.25. PCB (2 1/2in x 4in) also holds Sw's, 90p.

AUDIO MIXER (Jan. 72) Rs, Cs, Pots (i.c. excl.), PCB (1 1/2in x 2in), £1.55.

BIOLOGICAL AMPLIFIER (Jan./Feb. 73)—Pre-amp Set S/c's, Rs, Cs, Pots (i.c.'s excl.) £2.05. PCB (1 1/2in x 3 1/2in), 85p.

CALLERCARD (Jul./Aug. 72) Automatic Answering Machine S/c's, Rs, Cs, Pots, Switches, Relays, Transformer, £12.15. PCB (4in x 7 1/2in) also holds relays, connectors, £1.50. Recorder, £6.95. Pips Gen with PCB, £1.50.

DOOR BELL YODELLER (Apr. 71)—S/c's, Rs, Cs, Pots, Transformer, Loudspeaker, PCB (3in x 3 1/2in), £7.70.

ELECTRONIC PIANO (Sept. 72/Jan. 73) PRICES DOWN! PA/Trem—Rs, Cs, Pots (excl. 2K), £1.70. PCB as publ., £1.50. Power Supply—Rs, Cs, £1.10. PCB as publ., 90p. Pitch 1—12—Rs, Cs, £1.90 each set. Pitch 13—Rs, Cs, £1.30. Pitch PCB as publ., £1.80 each. Combined sets for PA/Trem, PSU, all 13 Pitch—Rs, Cs, Pots (excl. 2K), £23.70; PCB's, £23.20.

GEMINI STEREO AMP (Nov. 70/Mar. 71) Stereo Sets and PCBs Pre-Amp—S/c's, Cs, Pots, Maka-Sw's—with 1/2W 2% M.O. Rs, £13.45—with 1/2W 5% C.F. Rs, £11.20—with 1/2W 5% C.F. Rs, £10.75. PCB (3 1/2in x 10 1/2in) for kits with M.O. or 1/2W C.F. Rs. Holds pots and Maka-Sw's, £2.10. Main Amp—Rs, Cs, Pots, £5.40. PCB (3 1/2in x 5in), £1.40. PSU—Rs, Cs, Pot, £3.70. PCB (2in x 4in), 75p.

GEMINI STEREO TUNER (Apr./Jun. 72) Rs, Cs, Pot, £3.80. PCB as published, £1.80.

LOGICAL RADIO CONTROL (Dec. 71/Jan. 72)—Sets incl. Rs, Cs, S/c's and Pots (where req.) but excl. I.C.'s. Coder 1 and Clock Pulse Gen., £2.95. Coder 2A, £2.80. Coder 2B, £3. Decoder, 55p. PCBs as pub., 75p each.

MODEL SERVO CONTROL (Feb./Mar. 72)—Sets incl. Rs, Cs, S/c's and Pots (where req.) but excl. I.C.'s. Servo Amps: "A", £1.40; "B", £2.55; "C", £1.30. Fail-Safe, 65p. PCBs as published: "A" and "B", 60p each; "C" and Fail-Safe, 50p each.

MICROPHONE MIXER (Apr. 69)—S/c's, Rs, Cs, Pots, £2.90. PCB (3 1/2in x 4 1/2in)—also holds pots, £1.20.

PHOTOPRINT PROCESS CONTROL (Jan./Feb. 72) Finds exposure, controls timing, stabilises mains voltage.

S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keyswitch, T/Former, £7.60. PCB (3 1/2in x 5 1/2in) also holds pots, relay, keyswitch, £1.20.

SOUND SYNTHESISER—Details on request.

TAPE NOISE LIMITER (Feb. 72)—Mono Circuit S/c's, Rs, Cs, Pot, PCB (1 1/2in x 3in), £2.20. Regulated Power Supply (will feed 2 units) and PCB (1 1/2in x 2 1/2in), £3.20.

ULTRASONIC TRANSMITTER-RECEIVER (May 72) Rs, Cs, Pot, S/c's, Transducers, Relay, £9.90. Dual PCB (2in x 5 1/2in), 75p.

VERSATILE LIGHT EFFECTS UNIT (Jun. 72)—Single Channel Sound Controlled Light—also has built-in variable strobe. S/c's (excl. SCR), Rs, Cs, Pots, T/formers, Keyswitch, £8.85. PCB (3 1/2in x 7 1/2in) also holds Pots, Sw, T/Former (T/T), £1.50.

SOME OTHER DESIGNS AVAILABLE

REVERBERATION UNIT (Practical Wireless Nov.-Dec. 72) S/c's, Rs, Cs, Slider Pots, T/Former, £6.80 (with rotary pots £3.70). PCB (2in x 1 1/2in) also holds sliders (compatible with publ. panel) £1.20.

8 WATT AMPLIFIER (Practical Wireless Nov. 72) Main Amplifier—S/c's, Rs, Cs, Pot (Mono Set), £3.90. PCB (2 1/2in x 3in) (Mono), 60p. Pre-amp—S/c's, Rs, Cs, Pots, Maka-Sw., Mono, £2.50; Stereo, £5.20. PCB (3 1/2in x 7 1/2in) (Stereo)—also holds all pots and Maka-Sw., £1.50.

AURORA AUXILIARY CONTROL UNIT (2 variable freq. strobe gens. and 4 variable amplitude freq. gens.), Rs, Cs, Pots, S/c's, £3.25. PCB (3 1/2in x 5 1/2in), also holds all pots, £1.35.

THYRISTORS (400V P.I.V.) 1A 50p, 3A 55p, 7A 70p, 16A 95p.


SLIDER POTS (PCB Mounting) Mono, 40p; Dual, 60p; Knobs, 13p.

S.A.E. for Free List of these and other designs.

Orders: U.K. 10p P. & P. Overseas P. & P. at cost. V.A.T.—All prices V.A.T. Exclusive

PHONOSONICS, Dept. P.E.4, 25 Kentish Road, Belvedere, Kent DA17 5BW. Mail Order only

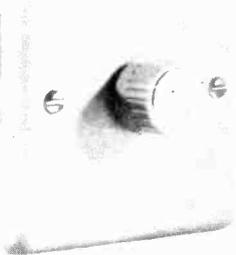Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300w or 600w of all lights except fluorescents at mains voltages from 200-250v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:

600 Watt—£3.20*. Kit Form £2.70*
300 Watt—£2.70*. Kit Form £2.20*


All plus 10p post and packing

*From 1st April please add the appropriate percentage of V.A.T. increase

Please send C.W.O. to:

DEXTER & COMPANY
ULVER HOUSE, 19 KING STREET
CHESTER CHI 2AH Tel. 0244-25883

VEROBOARD

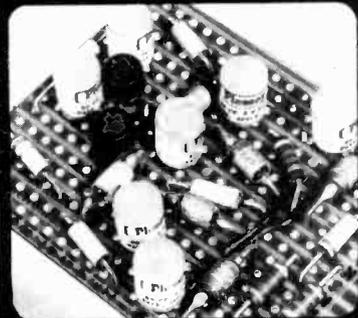

VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK

0.1" and 0.15" pitch, plain and copper clad universal circuit boards.

AVAILABLE FROM YOUR LOCAL RETAILER.

TRADE DISTRIBUTOR: N. Rose (Electrical) Ltd., London, W.C.1.



VERO ELECTRONICS LTD.
Industrial Estate, Chandler's Ford,
SO5 3ZR Tel: Chandler's Ford 2852

EX COMPUTER PRINTED CIRCUIT PANELS

2 x 4in packed with semiconductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p (8p). With a guaranteed min. of 35 transistors—data included.

SPECIAL BARGAIN PACK
25 boards for £1 (25p).

ELECTROLYTICS

10,000µ 75V, 33,000µ 40V, 4 1/2 x 2 1/2in dia., 25,000µ 25V, 20,000µ 30V, 8,000µ 55V, 4 1/2 x 3in dia. 50p (12p), 15,000µ 15V, 4 1/2 x 2in dia. 20p (10p), 2,000µ 25V wire ended, 3 x 1in dia. 15p (5p) or 12 for £1.50 (15p).

250 MIXED CAPACITORS 60p (8p)
250 MIXED RESISTORS 60p (8p)
3A STUD RECTIFIERS, 100 p.i.v. 4 for 50p (5p)

ASSORTED RELAYS 8 for £1 (25p)

SUB-MIN. CO-AX. PLUGS & SKTS. 4 pairs 50p (5p)

MINIATURE GLASS NEONS 12 for 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)

MICRO SWITCHES, MIXED 8 for 50p (8p)

PAPST EXTRACTOR/BLOWER FANS 100cfm 4 1/2 x 4 1/2 x 2in £3.50 (28p)

QUARTZ HALOGEN BULBS 12V 55W 50p (5p)

Postage and package for each item shown in brackets.

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD LONDON W8

01-478 8499

THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

AC107	0 20	AD162	0 88	BC148	0 10	BD137	0 45	BF188	0 40	OC19	0 35	2G371	0 16	2N2219	0 20	2N3054	0 46	2N4059	0 10
AC113	0 20	AD161		BC149	0 12	BD138	0 50	BF194	0 12	OC20	0 63	2G371B	0 12	2N2220	0 22	2N3055	0 50	2N4060	0 12
AC115	0 23	AD162 (MP)		BC150	0 15	BD139	0 55	BF195	0 12	OC22	0 38	2G373	0 17	2N2221	0 20	2N3091	0 14	2N4061	0 12
AC117K	0 20			BC151	0 20	BD140	0 60	BF196	0 14	OC23	0 42	2G374	0 30	2N2222	0 20	2N3092	0 14	2N4062	0 12
AC122	0 12	ADT140	0 60	BC152	0 17	BD155	0 80	BF197	0 14	OC24	0 56	2G377	0 30	2N2223	0 20	2N3093	0 14	2N4063	0 12
AC125	0 17	AF114	0 24	BC153	0 28	BD175	0 80	BF200	0 45	OC25	0 38	2G378	0 16	2N2224	0 20	2N3094	0 14	2N4064	0 12
AC128	0 17	AF115	0 24	BC154	0 30	BD176	0 80	BF222	0 95	OC26	0 25	2G381	0 16	2N2225	0 20	2N3095	0 14	2N4065	0 12
AC128	0 17	AF116	0 24	BC157	0 18	BD177	0 65	BF257	0 45	OC28	0 50	2G382	0 16	2N2411	0 24	2N3395	0 17	2N4287	0 17
AC128	0 17	AF117	0 24	BC158	0 12	BD178	0 65	BF258	0 40	OC29	0 50	2G401	0 30	2N2412	0 24	2N3396	0 17	2N4288	0 17
AC132	0 14	AF118	0 25	RC159	0 12	BD179	0 70	BF259	0 55	OC35	0 42	2G414	0 30	2N2413	0 24	2N3397	0 17	2N4289	0 17
AC134	0 14	AF124	0 30	RC160	0 45	BD180	0 70	BF262	0 40	OC36	0 50	2G417	0 25	2N2414	0 24	2N3398	0 17	2N4290	0 17
AC137	0 14	AF125	0 25	BC161	0 50	BD185	0 65	BF263	0 55	OC41	0 20	2N388	0 35	2N2415	0 24	2N3399	0 14	2N4291	0 17
AC141	0 14	AF126	0 28	BC167	0 12	BD186	0 65	BF270	0 35	OC42	0 24	2N388A	0 55	2N2416	0 24	2N3399	0 14	2N4292	0 17
AC141K	0 17	AF127	0 28	BC168	0 12	BD187	0 70	BF271	0 30	OC44	0 15	2N404	0 20	2N2417	0 24	2N3402	0 21	2N4293	0 17
AC142	0 14	AF131	0 30	BC169	0 12	BD188	0 70	BF272	0 30	OC45	0 12	2N404A	0 28	2N2418	0 24	2N3403	0 21	2N4294	0 17
AC142K	0 17	AF137	0 30	BC170	0 12	BD189	0 75	BF273	0 35	OC70	0 10	2N527	0 49	2N2419	0 24	2N3404	0 28	2N4295	0 17
AC151	0 15	AF179	0 50	BC171	0 14	BD190	0 75	BF274	0 35	OC71	0 15	2N527	0 49	2N2420	0 24	2N3405	0 28	2N4296	0 17
AC154	0 20	AF180	0 50	BC172	0 14	BD195	0 85	BF275	0 40	OC72	0 14	2N527	0 49	2N2421	0 24	2N3406	0 28	2N4297	0 17
AC155	0 20	AF181	0 45	BC173	0 14	BD196	0 85	BF276	0 40	OC73	0 14	2N527	0 49	2N2422	0 24	2N3407	0 28	2N4298	0 17
AC156	0 20	AF186	0 45	BC174	0 14	BD197	0 90	BF277	0 40	OC74	0 15	2N527	0 49	2N2423	0 24	2N3408	0 28	2N4299	0 17
AC157	0 24	AF239	0 37	BC175	0 22	BD198	0 90	BF278	0 40	OC75	0 15	2N527	0 49	2N2424	0 24	2N3409	0 28	2N4300	0 17
AC158	0 20	AF291	0 40	BC176	0 19	BD199	0 95	BF279	0 40	OC76	0 15	2N527	0 49	2N2425	0 24	2N3410	0 28	2N4301	0 17
AC166	0 20	AF292	0 40	BC177	0 19	BD200	0 95	BF280	0 40	OC81	0 15	2N706	0 08	2N2426	0 24	2N3411	0 28	2N4302	0 17
AC167	0 20	AS226	0 65	BC178	0 19	BD205	0 80	BF281	0 40	OC82	0 15	2N706A	0 09	2N2427	0 24	2N3412	0 28	2N4303	0 17
AC168	0 24	AS227	0 30	BC180	0 24	BD206	0 80	BF282	0 40	OC82	0 15	2N706A	0 09	2N2428	0 24	2N3413	0 28	2N4304	0 17
AC169	0 14	AS228	0 25	BC181	0 24	BD207	0 95	BF283	0 40	OC82D	0 15	2N708	0 12	2N2429	0 24	2N3414	0 28	2N4305	0 17
AC176	0 20	AS229	0 25	BC182	0 10	BD208	0 95	BF284	0 20	OC83	0 20	2N711	0 30	2N2430	0 24	2N3415	0 28	2N4306	0 17
AC177	0 24	AS230	0 25	BC182L	0 10	BD209	1 00	BF285	0 17	OC84	0 20	2N711	0 35	2N2431	0 24	2N3416	0 28	2N4307	0 17
AC178	0 20	AS231	0 25	BC183	0 10	BF115	0 24	BF286	0 15	OC139	0 20	2N718	0 24	2N2432	0 24	2N3417	0 28	2N4308	0 17
AC179	0 28	AS232	0 25	BC183L	0 10	BF117	0 45	BF287	0 15	OC140	0 20	2N718A	0 50	2N2433	0 24	2N3418	0 28	2N4309	0 17
AC180	0 17	AS233	0 25	BC184	0 12	BF118	0 70	BF288	0 15	OC203	0 25	2N726	0 28	2N2434	0 24	2N3419	0 28	2N4310	0 17
AC180K	0 20	AS234	0 25	BC184L	0 12	BF119	0 70	BF289	0 15	OC202	0 25	2N726	0 28	2N2435	0 24	2N3420	0 28	2N4311	0 17
AC181	0 17	AS235	0 25	BC186	0 28	BF121	0 45	BF290	0 15	OC203	0 25	2N727	0 28	2N2436	0 24	2N3421	0 28	2N4312	0 17
AC181K	0 20	AS236	0 25	BC187	0 28	BF123	0 50	BF291	0 15	OC204	0 25	2N727	0 28	2N2437	0 24	2N3422	0 28	2N4313	0 17
AC187	0 22	AS237	0 25	BC188	0 11	BF125	0 45	BF292	0 15	OC201	0 28	2N744	0 20	2N2438	0 24	2N3423	0 28	2N4314	0 17
AC187K	0 20	AS238	0 25	BC189	0 11	BF127	0 50	BF293	0 15	OC202	0 28	2N744	0 20	2N2439	0 24	2N3424	0 28	2N4315	0 17
AC188	0 22	BC107	0 09	BC209	0 12	BF129	0 55	BF294	0 18	OC203	0 25	2N744	0 20	2N2440	0 24	2N3425	0 28	2N4316	0 17
AC188K	0 20	BC108	0 09	BC212L	0 11	BF153	0 45	BF295	0 18	OC204	0 25	2N744	0 20	2N2441	0 24	2N3426	0 28	2N4317	0 17
ACY17	0 25	BC109	0 10	BC213L	0 11	BF154	0 45	BF296	0 18	OC205	0 35	2N1131	0 20	2N2442	0 24	2N3427	0 28	2N4318	0 17
ACY18	0 20	BC113	0 10	BC214L	0 11	BF155	0 70	BF297	0 28	OC309	0 40	2N1132	0 22	2N2443	0 24	2N3428	0 28	2N4319	0 17
ACY19	0 20	BC114	0 15	BC225	0 25	BF156	0 48	BF298	0 12	P346A	0 20	2N1302	0 14	2N2444	0 24	2N3429	0 28	2N4320	0 17
ACY20	0 20	BC116	0 15	BC226	0 25	BF157	0 55	BF299	0 12	P367	0 42	2N1303	0 14	2N2445	0 24	2N3430	0 28	2N4321	0 17
ACY21	0 20	BC116	0 15	BC227	0 25	BF158	0 55	BF300	0 12	OC7P1	0 43	2N1304	0 17	2N2446	0 24	2N3431	0 28	2N4322	0 17
ACY22	0 18	BC117	0 15	BC228	0 25	BF159	0 60	BF301	0 12	OC7P2	0 43	2N1305	0 17	2N2447	0 24	2N3432	0 28	2N4323	0 17
ACY22	0 18	BC118	0 10	BCY32	0 80	BF160	0 40	BF302	0 30	OC7P3	0 43	2N1306	0 17	2N2448	0 24	2N3433	0 28	2N4324	0 17
ACY28	0 19	BC119	0 30	BCY33	0 22	BF162	0 40	BF303	0 30	OC7P4	0 43	2N1307	0 21	2N2449	0 24	2N3434	0 28	2N4325	0 17
ACY29	0 35	BC120	0 80	BCY34	0 25	BF163	0 40	BF304	0 30	OC7P5	0 43	2N1308	0 23	2N2450	0 24	2N3435	0 28	2N4326	0 17
ACY30	0 28	BC125	0 12	BCY70	0 14	BF164	0 40	BF305	0 30	OC7P6	0 43	2N1309	0 23	2N2451	0 24	2N3436	0 28	2N4327	0 17
ACY31	0 28	BC126	0 18	BCY71	0 18	BF165	0 40	BF306	0 35	OC7P7	0 43	2N1310	0 23	2N2452	0 24	2N3437	0 28	2N4328	0 17
ACY34	0 21	BC132	0 12	BCY72	0 14	BF167	0 40	BF307	0 35	OC7P8	0 43	2N1311	0 23	2N2453	0 24	2N3438	0 28	2N4329	0 17
ACY35	0 21	BC134	0 18	BCZ10	0 20	BF173	0 22	BF308	0 30	OC7P9	0 43	2N1312	0 23	2N2454	0 24	2N3439	0 28	2N4330	0 17
ACY36	0 28	BC135	0 12	BCZ11	0 25	BF176	0 35	BF309	0 35	OC7P10	0 43	2N1313	0 23	2N2455	0 24	2N3440	0 28	2N4331	0 17
ACY40	0 17	BC136	0 15	RCZ12	0 25	BF177	0 35	BF310	0 35	OC7P11	0 43	2N1314	0 23	2N2456	0 24	2N3441	0 28	2N4332	0 17
ACY41	0 18	BC137	0 15	RD121	0 60	BF178	0 30	BF311	0 30	OC7P12	0 43	2N1315	0 23	2N2457	0 24	2N3442	0 28	2N4333	0 17
ACY44	0 35	BC139	0 40	BD123	0 65	BF179	0 30	BF312	0 30	OC7P13	0 43	2N1316	0 23	2N2458	0 24	2N3443	0 28	2N4334	0 17
AD130	0 35	BC140	0 30	BD124	0 60	BF180	0 30	BF313	0 30	OC7P14	0 43	2N1317	0 23	2N2459	0 24	2N3444	0 28	2N4335	0 17
AD140	0 48	BC141	0 30	BD131	0 60	BF181	0 30	BF314	0 30	OC7P15	0 43	2N1318	0 23	2N2460	0 24	2N3445	0 28	2N4336	0 17
AD142	0 48	BC142	0 30	BD132	0 60	BF182	0 40	BF315	0 30	OC7P16	0 43	2N1319	0 23	2N2461	0 24	2N3446	0 28	2N4337	0 17
AD143	0 38	BC143	0 30	BD133	0 65	BF183	0 40	BF316	0 30	OC7P17	0 43	2N1320	0 23	2N2462	0 24	2N3447	0 28	2N4338	0 17
AD149	0 50	BC145	0 45	BD135	0 40	BF184	0 25	BF317	0 30	OC7P18	0 43	2N1321	0 23	2N2463	0 24	2N3448	0 28	2N4339	0 17
AD161	0 30	BC147	0 10	BD136	0 40	BF185	0 30	BF318	0 30	OC7P19	0 43	2N1322	0 23	2N2464	0 24	2N3449	0 28	2N4340	0 17

DIODES AND RECTIFIERS

AA119	0 08	BY133	0 21	OA10	0 35
AA120	0 08	BY164	0 50	OA47	0 07
AA129	0 08	BYX38/30	0 42	OA70	0 07
AA130	0 09	BYX39	0 42	OA71	0 07
AA131	0 10	BZ10	0 35	OA81	0 07

The largest selection

NEW LOW PRICE TESTED S.C.R.'s

PIV 1A	3A	5A	5A	7A	10A	16A	30A
T05	T066	T066	T064	T048	T048	T048	T048
50	0-23	0-25	0-35	0-35	0-47	0-50	0-53
100	0-25	0-33	0-47	0-47	0-50	0-58	0-63
200	0-35	0-37	0-49	0-49	0-57	0-61	0-75
400	0-43	0-47	0-58	0-58	0-67	0-75	0-93
600	0-53	0-57	0-68	0-68	0-77	0-97	1-25
800	0-63	0-70	0-80	0-80	0-90	1-20	1-50

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0-04	0-05	0-05	0-07	0-14	0-21	0-60
100	0-04	0-06	0-05	0-13	0-16	0-23	0-70
200	0-05	0-09	0-06	0-14	0-20	0-24	1-00
400	0-06	0-13	0-07	0-20	0-27	0-37	1-25
600	0-07	0-16	0-10	0-25	0-34	0-45	1-86
800	0-10	0-17	0-11	0-25	0-37	0-55	2-00
1000	0-11	0-25	0-14	0-30	0-46	0-63	2-50
1200	—	0-33	—	0-38	0-57	0-75	—

TRIACS

VBO	2A	6A	10A
T0-1	TO-66	TO-88	
\$p	\$p	\$p	
100	80	50	76
200	50	60	80
400	70	75	1-10

DIACS

BR100	(D32)	37p	each
-------	-------	-----	------

FREE

One 50p Pak of your own choice free with orders valued \$4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS

Pak No.	EQVT
T1	8 2G3713 OC71
T2	8 D1874 OC75
T3	8 D1216 OC81D
T4	8 2G381T OC81
T5	8 2G382T OC92
T6	8 2G344B OC44
T7	8 2G345B OC45
T8	8 2G378 OC78
T9	8 2G399A 2N1302
T10	8 2G417 AF117

All 50p each pak

2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 25p each.

120 VOB MIXIE DRIVER TRANSISTOR.

Sim. HX211 & C407, 2N1803 FULLY TESTED AND CODED ND 120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 5p each. Any Qty.

POWER TRANS BONANZA!

GENERAL PURPOSE GERM. PNP CODED GP100. BRAND NEW TO-3 CASE. POSS. REPLACE.—OC25-28-29-30-35-36. NKT 401 403-404-405-406-430-451-452-453. T13027-3028. 2N260A. 2N466A-457A-458A. 2N511 A & B. 2N220-222. ETC. VCEO 80V VCEO 50V IC 10A PT. 30 WATTS Hfe 30-170. PRICE 1-24 43p each 25-99 40p each 100 up 35p each

SILICON High Voltage 250V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand new. Coded R 2400 VCEO 250V VCEO 100/IC 6A/30 Watts. HFE type 20/IT 5MHZ. OUR PRICE EACH: 1-24 80p 25-99 45p 100 up 40p

ADI61/162 PNP M/P COMP GERM TRANS. OUR LOWEST PRICE OF 65p PER PAIR

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE 2-33V. 400mW (DO-7 Case) 13p ea. 10W (80-10 Type) 25p ea. All fully tested 5% tol. and marked. State voltage required.

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 90p each

NEW LINE Plastic Encapsulated 2 AMP. BRIDGE RECTS.

50 v RMS 32p each 100 v RMS 37p each 400 v RMS 46p each Size 15 mm x 6 mm.

UNIJUNCTION

UT48. Eqvt. 2N2646. Eqvt. T1843. DEN3000 27p each, 25-99 25p 100 UP 20p.

CADMIUM CELLS

ORP12 43p ORP60, ORP61 40p each

GENERAL PURPOSE PNP SILICON SWITCHING TRANS. TO-18 SIM. TO 2N705/8, B5T-27/28/95A. All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BC170. When ordering, please state preference NPN or PNP.

\$p	20	For	0.50
\$p	50	For	1.00
\$p	100	For	1.75
\$p	500	For	7.50
\$p	1000	For	13.00

SIL. G.P. DIODES \$p

300mW 30. 0.50 40PIV(Min.) 100. 1.50 Sub-Min. 500. 5.00 Full Tested 1,000. 9.00 Ideal for Organ Builders.

NEW EDITION 1971

TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each.

2N3055 115 WATT SIL POWER NPN 50p EACH

SILICON 50 WATTS MATCHED NPN/PNP BIP 15 NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCEO 100V/VCEO 50/IC 10A. HFE type 100/IT 3mHz. OUR PRICE PER PAIR: 1-24 prs. 60p 25-99 prs. 55p 100 prs. 50p

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED In Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0.50
U 2	60 Mixed Germanium Transistors AF/RFP	0.50
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0.50
U 4	40 Germanium Transistors like OC81, AC128	0.50
U 5	60 200mA Sub-Min. Silicon Diodes	0.50
U 6	30 Sil. Planar Trans. NPN like B8T95A, 2N706	0.50
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTV. RANGE up to 1000V	0.50
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0.50
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0.50
U 10	20 BA750 charge storage Diodes DO-7 Glass	0.50
U 11	25 PNP Sil. Planar Trans. TO-5 like 2N1152, 2N2904	0.50
U 12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0.50
U 13	30 PNP-NPN Sil. Transistors OC200 & 28 104	0.50
U 14	150 Mixed Silicon and Germanium Diodes	0.50
U 15	25 NPN Sil. Planar Trans. TO-5 like BF751, 2N697	0.50
U 16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0.50
U 17	30 Germanium PNP AF Transistors TO-5 like ACV 17-22	0.50
U 18	8 6 Amp Silicon Rectifiers B7Z13 Type up to 600 PIV	0.50
U 19	25 Silicon NPN Transistors like BC108	0.50
U 20	12 1-5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0.50
U 21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0.50
U 23	30 MADT's like MHz Series PNP Transistors	0.50
U 24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0.50
U 25	25 300 MHz NPN Silicon Transistors 2N708, B5Y27	0.50
U 26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0.50
U 27	12 NPN Germanium AF Transistors TO-1 like AC127	0.50
U 29	10 1 Amp SCR's TO-5 can. up to 800 PIV CR81/25-600	1.00
U 30	15 Plastic Silicon Planar Trans. NPN 2N2926	0.50
U 31	20 Silicon Planar Plastic NPN Trans. Low Noise AMP 2N3707	0.50
U 32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0.50
U 33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0.50
U 34	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0.50
U 35	25 Silicon Planar Transistors PNP TO-18 2N2906	0.50
U 36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0.50
U 37	30 Silicon Alloy Transistors SO-2 PNP OC200, 28322	0.50
U 38	20 Fast Switching Silicon Trans. NPN 400 MHz 2N3011	0.50
U 39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0.50
U 40	10 Dual Transistors 6 lead TO-5 2N2060	0.50
U 41	25 RF Germanium Transistors TO-5, OC45, NKT72	0.50
U 42	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0.50
U 43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0.50
U 44	20 Sil. Trans. Plastic TO-5 BC115/NPN	0.50
U 45	7 3A SCR. TO66 up to 600PIV	1.00

Code No's. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to BP 23 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25 99 100 up Price each 45p 40p 35p

F.E.T.'S 2N3819 35p 2N5458 50p 2N3820 50p 2N5459 40p 2N3821 35p BF710 40p 2N3823 30p MPF105 40p

INTEGRATED CIRCUIT PAKS

Manufacturers "Full Outlets" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about IC's and experimental work.

Pak No.	Contents	Price
UIC00	12 x 7400	0.50
UIC01	12 x 7401	0.50
UIC02	12 x 7402	0.50
UIC03	12 x 7403	0.50
UIC04	12 x 7404	0.50
UIC05	12 x 7405	0.50
UIC06	8 x 7406	0.50
UIC07	8 x 7407	0.50
UIC10	12 x 7410	0.50
UIC13	8 x 7413	0.50
UIC20	12 x 7420	0.50
UIC30	12 x 7430	0.50
UIC40	12 x 7440	0.50
UIC41	5 x 7441	0.50
UIC42	5 x 7442	0.50
UIC43	5 x 7443	0.50
UIC44	5 x 7444	0.50
UIC45	5 x 7445	0.50

QUALITY TESTED SEMICONDUCTORS

Pak No.	Contents	Price
Q1	20 Red spot transistors PNP	0.50
Q2	16 White spot R.F. transistors PNP	0.50
Q3	4 OC 77 type transistors	0.50
Q4	6 Matched transistors OC44/45/81/D10	0.50
Q5	4 OC 75 transistors	0.50
Q6	5 OC 72 transistors	0.50
Q7	4 AC 128 transistors PNP high gain.	0.50
Q8	4 AC 126 transistors PNP	0.50
Q9	7 OC 81 type transistors	0.50
Q10	7 OC 71 type transistors	0.50
Q11	2 AC 127/128 Complementary pairs PNP/NPN	0.50
Q12	3 AF 16 type transistors	0.50
Q13	3 AF 117 type transistors	0.50
Q14	3 OC 171 H.F. type transistors	0.50
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0.50
Q16	2 GET880 low noise Germanium transistors	0.50
Q17	5 RPN 2 x ST 141 & 3 x ST 140.	0.50
Q18	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0.50
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0.50
Q20	4 OC 44 Germanium transistors A.F.	0.50
Q21	4 AC 127 NPN Germanium transistors	0.50
Q22	20 NKT transistors A.F. tested	0.50
Q23	10 OA 202 Silicon diodes sub-min.	0.50
Q24	8 OA 81 diodes	0.50
Q25	15 IN914 Silicon diodes 75 PIV 75mA	0.50
Q26	8 OA95 Germanium diodes sub-min IN69	0.50
Q27	2 OA PIV Silicon rectifiers IS42511	0.50
Q28	2 Silicon power rectifiers BZ 13	0.50
Q29	4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0.50
Q30	7 Silicon switch transistors 2N706 NPN	0.50
Q31	6 Silicon switch transistors 2N708 NPN	0.50
Q32	3 PNP Silicon transistors 2 x 2N1131, 1 x 2N1132	0.50
Q33	3 Silicon NPN transistors 2N1711	0.50
Q34	7 Silicon NPN transistors 2N2369, 500MHz (code F397)	0.50
Q35	3 Silicon PNP TO-5, 2 x 2N2904 & 1 x 2N2905	0.50
Q36	7 2N3646 TO-18 plastic 300 MHz NPN	0.50
Q37	3 2N3053 NPN Silicon transistors	0.50
Q38	7 NPN transistors 4 x 2N3703, 3 x 2N3702	0.50

ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales:— Conversion of Frequency and Wavelength. Calculation of L and Inductance of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and 'e' Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 2 cm x 4cm. Complete with case and instructions. Price each: £3-35

Pak No.	Contents	Price
UIC46	5 x 7446	0.50
UIC47	5 x 7447	0.50
UIC48	5 x 7448	0.50
UIC50	12 x 7450	0.50
UIC51	12 x 7451	0.50
UIC53	12 x 7453	0.50
UIC54	12 x 7454	0.50
UIC60	12 x 7460	0.50
UIC70	8 x 7470	0.50
UIC72	8 x 7472	0.50
UIC73	8 x 7473	0.50
UIC74	8 x 7474	0.50
UIC75	8 x 7475	0.50
UIC76	8 x 7476	0.50
UIC80	5 x 7480	0.50
UIC81	5 x 7481	0.50
UIC82	5 x 7482	0.50
UIC83	5 x 7483	0.50
UIC86	5 x 7486	0.50
UIC90	5 x 7490	0.50
UIC91	5 x 7491	0.50
UIC92	5 x 7492	0.50
UIC93	5 x 7493	0.50
UIC94	5 x 7494	0.50
UIC95	5 x 7495	0.50
UIC96	5 x 7496	0.50
UIC99	5 x 74100	0.50
UIC121	5 x 74121	0.50
UIC141	5 x 74141	0.50
UIC151	5 x 74151	0.50
UIC164	5 x 74164	0.50
UIC193	5 x 74193	0.50
UIC199	5 x 74199	0.50

UICX1 = 25 Assorted 74's 1-50

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES— 18 BALDOCK STREET (A10), WARE, HERTS. (STD 0920) 61593. MON.-SAT.

- the lowest prices!

74 Series T.T.L. I.C's

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS



SN7400	1	25	100	SN7489	1	25	100
SN7401	0.15	0.14	0.12	SN7490	£5.50	£5.25	£5.00
SN7402	0.15	0.14	0.12	SN7491	0.67	0.64	0.58
SN7403	0.15	0.14	0.12	SN7492	0.67	0.64	0.58
SN7404	0.15	0.14	0.12	SN7493	0.67	0.64	0.58
SN7405	0.15	0.14	0.12	SN7494	0.77	0.74	0.68
SN7406	0.35	0.31	0.28	SN7495	0.77	0.74	0.68
SN7407	0.35	0.31	0.28	SN7496	0.87	0.84	0.78
SN7408	0.18	0.17	0.16	SN74100	£1.65	£1.60	£1.55
SN7409	0.18	0.17	0.16	SN74104	0.97	0.94	0.88
SN7410	0.15	0.14	0.12	SN74105	0.97	0.94	0.88
SN7411	0.25	0.24	0.23	SN74107	0.40	0.38	0.36
SN7412	0.35	0.31	0.28	SN74110	0.55	0.53	0.50
SN7413	0.29	0.26	0.24	SN74111	£1.25	£1.15	£1.10
SN7416	0.43	0.40	0.38	SN74118	£1.00	0.95	0.90
SN7417	0.43	0.40	0.38	SN74119	£1.35	£1.25	£1.10
SN7420	0.15	0.14	0.12	SN74121	0.40	0.37	0.34
SN7422	0.50	0.48	0.45	SN74122	£1.40	£1.30	£1.20
SN7423	0.50	0.48	0.45	SN74123	£2.80	£2.70	£2.60
SN7425	0.50	0.48	0.45	SN74141	0.67	0.64	0.58
SN7427	0.45	0.42	0.40	SN74145	£1.50	£1.40	£1.30
SN7428	0.70	0.65	0.60	SN74150	£3.00	£2.70	£2.50
SN7430	0.15	0.14	0.12	SN74151	£1.00	0.95	0.90
SN7432	0.45	0.42	0.40	SN74153	£1.20	£1.10	£1.00
SN7433	0.80	0.75	0.70	SN74154	£1.80	£1.70	£1.60
SN7437	0.64	0.62	0.60	SN74155	£1.40	£1.30	£1.20
SN7438	0.64	0.62	0.60	SN74156	£1.40	£1.30	£1.20
SN7440	0.15	0.14	0.12	SN74157	£1.00	£0.90	£0.80
SN7441	0.67	0.64	0.58	SN74160	£1.80	£1.70	£1.60
SN7442	0.67	0.64	0.58	SN74161	£1.80	£1.70	£1.60
SN7443	£1.30	£1.25	£1.20	SN74162	£4.00	£3.75	£3.50
SN7444	£1.30	£1.25	£1.20	SN74163	£4.00	£3.75	£3.50
SN7445	£1.80	£1.77	£1.75	SN74164	£2.20	£2.15	£2.10
SN7446	0.97	0.94	0.88	SN74165	£2.25	£2.20	£2.15
SN7447	£1.00	0.97	0.95	SN74166	£3.50	£3.25	£3.00
SN7448	£1.00	0.97	0.95	SN74174	£2.30	£2.20	£2.10
SN7450	0.15	0.14	0.12	SN74175	£1.60	£1.50	£1.40
SN7451	0.15	0.14	0.12	SN74176	£2.50	£2.40	£2.30
SN7453	0.15	0.14	0.12	SN74177	£2.50	£2.40	£2.30
SN7454	0.15	0.14	0.12	SN74180	£2.00	£1.60	£1.40
SN7460	0.15	0.14	0.12	SN74181	£5.50	£5.00	£4.75
SN7470	0.29	0.26	0.24	SN74182	£2.00	£1.80	£1.60
SN7472	0.29	0.26	0.24	SN74184	£3.50	£3.25	£3.00
SN7473	0.35	0.32	0.32	SN74190	£1.95	£1.90	£1.85
SN7474	0.37	0.35	0.32	SN74191	£1.90	£1.85	£1.80
SN7475	0.45	0.43	0.42	SN74192	£1.95	£1.90	£1.85
SN7476	0.40	0.39	0.38	SN74193	£2.00	£1.80	£1.75
SN7480	0.67	0.64	0.58	SN74194	£2.70	£2.60	£2.50
SN7481	£1.20	£1.15	£1.10	SN74195	£2.00	£1.90	£1.80
SN7482	0.87	0.86	0.85	SN74196	£1.80	£1.70	£1.60
SN7483	£1.10	£1.05	0.95	SN74197	£1.80	£1.70	£1.60
SN7484	£1.00	0.95	0.90	SN74198	£5.50	£5.00	£4.50
SN7485	£3.60	£3.50	£3.40	SN74199	£5.50	£5.00	£4.50
SN7486	0.32	0.31	0.30				

ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C's

LINEAR I.C.'s—FULL SPEC	Price
Type No.	1-24 25-99 100 up
BP201C—SL201C	68p 50p 45p
BP701C—SL701C	68p 50p 45p
BP702C—SL702C	68p 50p 45p
BP702—72702	53p 45p 40p
BP709—72709	36p 34p 30p
LBP709P—µA709C	36p 34p 30p
BP710—72710	44p 42p 40p
BP711—µA711	45p 43p 40p
BP741—72741	75p 60p 50p
µA703C—µA703C	28p 26p 24p
TAA263—	70p 60p 55p
TAA293—	90p 75p 70p
TAA350—	170p 158p 150p
T.G.S. FA 000 2-6.3	


Type No.	1-24	25-99	100 up
BP930	12p	11p	10p
BP932	13p	12p	11p
BP935	13p	12p	11p
BP936	13p	12p	11p
BP944	25p	24p	22p
BP946	12p	11p	10p
BP948	25p	24p	22p
BP951	65p	60p	55p
BP962	12p	11p	10p
BP903A	40p	38p	35p
BP904	40p	38p	35p
BP907	40p	38p	35p
BP909	40p	38p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application (DTL 930 Series only).

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0.1% DISTORTION!
HI-FI AUDIO AMPLIFIER

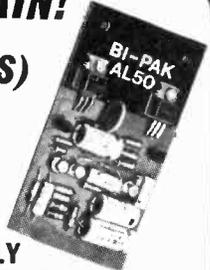

THE AL50

- ★ Frequency Response 15Hz to 100,000—1dB.
 - ★ Load—3, 4, 8 or 16 ohms.
 - ★ Distortion—better than 0.1% at 1KHz.
 - ★ Signal to noise ratio 80dB.
- ONLY £3.25p each**
- ★ Supply voltage 10-35 Volts.
 - ★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.
FULLY BUILT—TESTED—GUARANTEED.

STABILISED POWER MODULE SPM80



AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.a.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Discos Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £2-95**

TRANSFORMER BMT80 £1-95 p. & p. 25p.

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response	20Hz — 20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs : 1. Tape Head	1.25 mV into 50K Ω
2. Radio, Tuner	35 mV into 50K Ω
3. Magnetic P.U.	1.5 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters : Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than - 65dB
Input overload	+ 20dB
Supply	35 volts at 20mA
Dimensions	292mm x 82mm x 35mm



SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £23.00 FREE p. & p.

All prices quoted in new pence Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015P Minitron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2.3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.65	£1.90

All indicators 0.9 + Decimal point. All side viewing. Full data for all types available on request.

E.T.L. MICROLOGIC CIRCUITS

Price each
Epoxy TO-5 case 1-24 25-99 100 up
uL900 Dual 85p 83p 87p
uL914 Buffer 50p 47p 45p
gate
uL923 J-K flip-flop 85p 83p 87p
50p 47p 45p
Date and Circuits Booklet for IC's
Price 7p.

DUAL IN LINE SOCKETS. 14 & 16 Lead Sockets for use with

DUAL-IN-LINE I.C.'s. TWO Ranges PROFESSIONAL & NEW LOW COST. PROF. TYPE No. 1-24 25-99 100up.	TSO 14 pin type	80p	87p	25p
TBO 16 " " "	85p	82p	80p	
LOW COST No.				
BPS 14	16p	13p	11p	
BPS 16	16p	14p	12p	

DISCOUNTS UP TO

60%

Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE.

GARRARD SP25 Mk. III

Special Purchase. Limited number available.
Garrard SP25 Mk. III £17.45
Goldring G800
Teak plinth and tinted cover
All leads supplied.
Please add £1.25 P. & P. & Ins.

TURNTABLES

Please add 75p P. & P. & Ins.
Connoisseur BDI Chassis £12.75
Garrard SP25 Mk. III £9.90
Garrard AP76 £17.20
Garrard SL65B £13.95
Garrard 401 £28.75
Garrard Zero 100 (Auto) £36.90
Garrard Zero 100 (Single) £35.90
BSR MP60 £9.40
Goldring GL72 £20.90
Goldring GL72 P £27.45
Goldring GL75 £26.95
Goldring GL75 P £34.95
Goldring 101 P.C. £20.00
Wharfedale Linton + cart. £25.90
Thorens TD125AB Mk. II £27.95
Thorens TD150 Mk. II £91.45
Thorens TD160 AB & C £53.95

TUNERS

Please add 85p P. & P. & Ins.
Amstrad Multiplex 3000 £27.25
Armstrong 523 £39.50
Armstrong 524 £31.45
Rogers R/brook FET4 (Chassis) £35.75
Rogers R/brook FET4 (Cased) £38.95
Rogers R/bourne FET4 (Chassis) £45.00
Rogers R/bourne FET4 (Cased) £49.50
Sinclair PR060 (Module) £16.95
Sinclair 2000/3000 Tuner £29.90
Leak Delta FM (Cased) £53.60
Leak Delta AM/FM (Cased) £63.75
Alpha Highgate FT150 £37.95
Metrosound FMS 20 £38.65
Philips RH 690 £33.00

TUNER/AMPLIFIERS

Please add £1 P. & P. & Ins.
Alpha Highgate 150 £49.75
Armstrong 525 (Teak cased) £69.45
Armstrong 526 AM/FM (Teak cased) £77.25
Leak Delta 75 £119.00
Teleton 2100 £32.50
Goodmans One Ten £98.90
Goodmans Mod 90 £85.50
Rotel 150 £49.50
Rotel 400 £75.50
Rogers Ravensbrook (Teak cased) £72.00
Rogers R/brook (Chassis) £72.00
Alpha FR 3000. New product £72.00

All prices correct at time of press E. & O.E. and are subject to alterations.



GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE4), 174 Pentonville Road, London, N.1. Tel. 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue Ilford, Essex. Tel. 01-550 1086

Open Monday to Saturday 9.30 a.m. to

6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

AMPLIFIERS

Please add 85p P. & P. & Ins.
Amstrad 8000 Mk. II £14.95
Amstrad IC2000 £27.50
Amstrad Integra 4000 £22.50
Armstrong 521 (Teak cased) £43.90
Alpha Highgate 212 £24.85
Alpha Highgate FA300 £32.25
Alpha Highgate FA400 £35.65
Leak Delta 30 £44.85
Leak Delta 70 £54.90
Metrosound ST20E £24.20
Metrosound ST60 £45.95
Pioneer SA600 & 610 £57.25
Pioneer SA5000A £71.95
Pioneer SA1000 £96.95
Rogers R/brook (Chassis) £37.95
Rogers R/brook (Cased) £41.50
Rogers R/bourne (Chassis) £49.95
Rogers R/bourne (Cased) £52.75
Sinclair PR060 2 x Z30 PZ5 £14.70
Sinclair PR060 2 x Z30 PZ8 £16.70
Sinclair PR060 2 x Z50 PZ8 Trans £22.95
Sinclair AFU (Filter Unit) £4.20
Sinclair 605 £17.95
Sinclair 2000 Mk. II £21.50
Sinclair 3000 Mk. II £28.00
Wharfedale Linton £32.90
Teleton SAQ 307 £22.95
Rotel RA310 £34.95
Rotel RA610 £52.95

SPEAKERS

Please add £1.50 per pair P. & P. & Ins.
Price per pair
Amstrad 138 £13.90
Wharfedale Dencon 2 £28.40
Wharfedale Linton 2 £35.40
Wharfedale Melton 2 £45.90
Wharfedale Dovedale 3 £59.80
Celestion Ditton 120 £38.40
Celestion Ditton 15 £51.00
Celestion Ditton 25 £84.50
Celestion County (new prod) £34.50
Goodmans Double Maxim £47.40
Goodmans Mezzo 3 £45.95
Goodmans Magister £82.95

Special bulk purchase

£2.90*



Plus 65p P. & P. & Ins. Finished in teak veneer with tinted dust cover. (Fully assembled). For Garrard SP25; 2025TC; 3000; AT60; 2000; 2500; 3500; 5100; 1025; SL65B. Also for BSR McDonald MP60 and others. For AP76; AP75; SL72B; SL75; SL95B*. £3.90 + 65p. P. & P. & Ins. Also finished in walnut to match Japanese equipment—at no extra.

CARTRIDGES

Please add 10p P. & P. & Ins.
Goldring G850 £3.35
Goldring G800 £4.70
Goldring G800E £7.50
Goldring G800 Super E £14.15
Shure M3D £37.70
Shure M44E £47.75
Shure M55E £5.55
Ortofon SL15 £15.85
Sonnatone 9TAHC £1.35

ELECTROKIT

Now available from one company are complete kits for many of the articles published in the Electronics, Radio and TV Journals. Examples of our range are:

SCORPIO IGNITION SYSTEMS (P.E. Nov. 1971), £9.50. This kit includes all the parts for the assembly of this popular and reliable system. The hardware and instruction data are included.

ELECTRONIC PIANO (P.E. Sept. 1972). We can supply the various sections for this article in kit form. Power supply, price £6.60. Preamp and Tremolo £3.20. Main Amplifier (less speakers) £3.30. 13 Pitch boards £39.50 (less inductors).

DRILL SPEED CONTROLLER (E.E. Aug. 1972). Kit consists of resistors, rectifiers, thyristor and tag board as specified in the article, price £1.05. Kit with M.K. box, plate and switch, price £2.05.

LIGHT DIMMER. Kit contains all parts including circuit and construction data, 480 watts, fully suppressed, price £2.10.

We shall also be offering kits for most articles published in the P.E. and other popular electronics magazines and will be pleased to quote prices.

All kits sent Post FREE.


Send for details of all other kits available (please enclose S.A.E.).

ELECTROKIT

12 Lauderdale Road, London, W.9
Telephone 01-286 0011

Mon.-Fri. 9.30-5.30 Thurs. 9.30-6.30

Are you alright for Jacks?

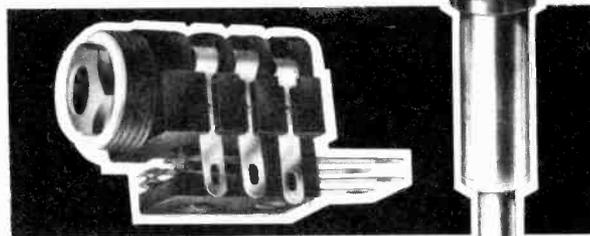

Ask for Rendar Jack plugs and sockets at your local stockist. They come in a wide variety of configurations, and in cases of difficulty can be ordered DIRECT from the Rendar factory.

Standard, mini and sub-miniature sizes... plugs in both screened and unscreened versions... socket bodies in high melting point thermoplastic... several unique features (some protected by UK and US Patents)... Post Office and NATO specifications.

If you want to study all the facts and figures, all the ingenious construction details, send for the Rendar Electronic Components Catalogue of technical data sheets covering their entire range of products.

The cost of the catalogue is 25p, including P & P, and it's money very well spent!



RENDAR®

Rendar Instruments Ltd., Victoria Road
Burgess Hill, Sussex. Tel. Burgess Hill 2642-4
Cables: Rendar, Burgess Hill

RIST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
Express postage 1p per transistor, over ten post free
INTEGRATED CIRCUITS 5p + 1p each added

Sp	Sp	Sp	Sp	Sp					
1N21	0-17	AF212	1-00	BY210	0-85	0A2211	0-82	Z8170	0-10
1N23	0-20	ASV26	0-85	BY211	0-82	0A2222	0-45	Z8271	0-18
1N85	0-88	ASV27	0-82	BY212	0-80	0A2223	0-46	ZT21	0-25
1N263	0-60	ASV28	0-85	BY213	0-85	0A2224	0-40	ZT43	0-25
1N264	0-60	ASV29	0-80	BY214	0-80	0A2241	0-82	ZTX107	0-15
1N645	0-85	ASV36	0-85	BY215	1-00	0A2242	0-82	ZTX108	0-12
1N725A	0-80	ASV50	0-17	BY216	0-82	0A2244	0-82	ZTX300	0-12
1N914	0-07	ASV51	0-40	BY288C/3V3		0A2246	0-82	ZTX304	0-82
1N4007	0-20	ASV53	0-80		0-15	0A2290	0-88	ZTX600	0-16
18113	0-15	ASV55	0-80	C111	0-65	0C116	0-60	ZTX603	0-17
18130	0-18	ASV62	0-85	CR81/05	0-25	0C16T	0-98	ZTX631	0-25
18131	0-15	ASV66	0-85	CR81/40	0-45	0C19	0-87		
18202	0-83	AS221	0-42	CS4B	2-60	0C20	0-85		
2G371	0-82	AS223	0-75	CS10B	3-18	0C22	0-60		
2G381	0-85	AUY10	0-80	DD000	0-16	0C23	0-60		
2G414	0-30	AU101	1-60	DD003	0-16	0C24	0-60		
2G417	0-82	BC107	0-10	DD006	0-18	0C25	0-87		
2N404	0-20	BC108	0-10	DD007	0-40	0C26	0-25		
2N697	0-16	BC109	0-10	DD008	0-88	0C28	0-80		
2N698	0-40	BC113	0-15	GD3	0-88	0C28	0-80		
2N706	0-10	BC115	0-20	GD4	0-05	0C29	0-80		
2N706A	0-12	BC116	0-25	GD5	0-88	0C30	0-40		
2N708	0-15	BC116A	0-80	GD8	0-25	0C35	0-50		
2N709	0-82	BC118	0-25	GD12	0-05	0C36	0-80		
2N1091	0-33	BC121	0-20	GET102	0-80	0C36	0-80		
2N1131	0-25	BC122	0-20	GET103	0-82	0C41	0-25		
2N1132	0-25	BC125	0-68	GET113	0-20	0C42	0-30		
2N1302	0-18	BC126	0-65	GET114	0-15	0C43	0-40		
2N1303	0-18	BC140	0-65	GET115	0-45	0C44	0-17		
2N1304	0-22	BC147	0-15	GET116	0-60	0C44M	0-17		
2N1305	0-22	BC148	0-13	GET120	0-25	0C45	0-12		
2N1306	0-25	BC149	0-15	GET872	0-30	0C45M	0-18		
2N1307	0-25	BC157	0-15	GET875	0-25	0C46	0-27		
2N1308	0-25	BC158	0-12	GET880	0-37	0C57	0-60		
2N2147	0-75	BC160	0-63	GET881	0-25	0C58	0-60		
2N2148	0-60	BC169	0-13	GET882	0-25	0C59	0-60		
2N2150	0-60	BCY31	0-35	GET885	0-25	0C66	0-50		
2N2218	0-20	BCY32	0-55	GEX44	0-08	0C70	0-12		
2N2219	0-20	BCY33	0-25	GEX45/1	0-10	0C71	0-12		
2N2369A	0-16	BCY34	0-25	GEX941	0-16	0C72	0-20		
2N2444	1-99	BCY34	0-30	GJ3M	0-25	0C73	0-80		
2N2445	0-22	BCY48	0-40	GJ4M	0-35	0C74	0-80		
2N2646	0-45	BCY39	1-00	GJ5M	0-25	0C75	0-85		
2N2904	0-20	BCY40	0-50	GJ7M	0-87	0C76	0-25		
2N2904A	0-25	BCY42	0-25	HG1005	0-50	0C77	0-40		
2N2906	0-20	BCY70	0-15	H8100A	0-20	0C78	0-20		
2N2907	0-23	BCY71	0-20	MAT100	0-25	0C79	0-22		
2N2924	0-23	BCZ10	0-40	MAT101	0-25	0C80	0-20		
2N2925	0-15	BD111	0-60	MAT120	0-25	0C81D	0-20		
2N2926	0-10	BD121	0-65	MAT121	0-30	0C81M	0-20		
2N3054	0-60	BD123	0-80	MJE2520	0-87	0C81DM	0-18		
2N3055	0-75	BD124	0-75	MJE2955	1-87	0C81Z	0-40		
2N3702	0-10	BDY11	1-62	MJE3055	0-87	0C82	0-25		
2N3706	0-10	BF115	0-25	NKT128	0-35	0C82D	0-20		
2N3708	0-23	BF117	0-60	NKT129	0-30	0C83	0-25		
2N3707	0-12	BF167	0-25	NKT211	0-25	0C84	0-25		
2N3709	0-10	BF173	0-25	NKT213	0-25	0C14	0-38		
2N3710	0-10	BF181	0-35	NKT214	0-15	0C122	0-60		
2N3711	0-10	BF184	0-20	NKT216	0-37	0C123	0-65		
2N3819	0-85	BF185	0-20	NKT217	0-35	0C138	0-25		
2N3927	0-35	BF194	0-17	NKT218	1-13	0C140	0-35		
2N5085	0-33	BF195	0-15	NKT219	0-33	0C141	0-60		
28301	0-60	BF196	0-15	NKT222	0-20	0C169	0-20		
28304	0-75	BF197	0-15	NKT224	0-22	0C170	0-25		
28501	0-37	BF861	0-28	NKT251	0-24	0C171	0-20		
28709	0-62	BF898	0-28	NKT271	0-25	0C200	0-40		
AA129	0-20	BFX12	0-20	NKT272	0-25	0C201	0-70		
AAZ12	0-30	BFX13	0-25	NKT273	0-15	0C202	0-80		
AAZ13	0-12	BFX29	0-25	NKT274	0-20	0C203	0-40		
AC107	0-37	BFX30	0-25	NKT275	0-25	0C204	0-40		
AC126	0-20	BFX35	0-98	NKT277	0-20	0C205	0-75		
AC127	0-25	BFX63	0-50	NKT278	0-25	0C206	0-40		
AC128	0-30	BFX65	0-25	NKT303	0-40	0C207	0-80		
AC187	0-25	BFX85	0-30	NKT304	0-75	0C460	0-20		
AC188	0-25	BFX86	0-25	NKT403	0-75	0C470	0-30		
ACY17	0-80	BFX87	0-25	NKT404	0-55	0CP71	0-87		
ACY18	0-25	BFX88	0-20	NKT678	0-30	ORP12	0-80		
ACY19	0-25	BFY10	1-00	NKT713	0-25	ORP60	0-40		
ACY20	0-20	BFY11	0-75	NKT719	0-25	ORP71	0-42		
ACY21	0-20	BFY17	0-25	NKT777	0-38	SI9T	0-80		
ACY22	0-10	BFY18	0-25	O78B	0-88	SAC40	0-25		
ACY27	0-25	BFY19	0-25	OA5	0-20	SFT308	0-88		
ACY28	0-17	BFY24	0-45	OA6	0-12	ST722	0-88		
ACY39	0-50	BFY44	1-00	OA7	0-10	ST7231	0-68		
ACY40	0-15	BFY50	0-22	OA70	0-10	8X58	0-20		
ACY41	0-15	BFY51	0-20	OA71	0-10	8X631	0-30		
ACY44	0-25	BFY52	0-22	OA73	0-10	8X635	0-40		
AD140	0-50	BFY53	0-17	OA74	0-10	8X640	0-60		
AD149	0-50	BFY64	0-42	OA79	0-10	8X641	0-55		
AD181	0-87	BFY90	0-65	OA81	0-06	8X642	0-60		
AD182	0-37	BSX27	0-49	OA85	0-12	8X643	0-75		
AF106	0-30	BSX60	0-98	OA86	0-15	8X645	0-75		
AF114	0-25	BSX78	0-15	OA90	0-08	V15/30P	0-60		
AF115	0-25	BSY26	0-18	OA91	0-07	V30/201P	0-75		
AF116	0-25	BSY27	0-17	OA95	0-07	V60/201	0-60		
AF117	0-25	BSY51	0-80	OA200	0-07	V60/201P	0-75		
AF118	0-62	BSY6A	0-12	OA202	0-10	XA101	0-10		
AF119	0-20	BSY95	0-12	OA210	0-25	XA102	0-18		
AF124	0-25	BT102/500R		OA211	0-30	XA151	0-15		
AF125	0-20		0-75	OA2200	0-55	XA152	0-15		
AF126	0-17	BTY42	0-92	OA2201	0-40	XA161	0-25		
AF127	0-17	BTY79/100R		OA2202	0-62	XA162	0-25		
AF139	0-30			OA2203	0-30	XB101	0-43		
AF178	0-65	BTY79/400R		OA2204	0-40	XB102	0-10		
AF179	0-65		1-25	OA2205	0-42	XB102	0-10		
AF180	0-62	BY100	0-15	OA2206	0-42	XB103	0-25		
AF181	0-42	BY126	0-15	OA2207	0-47	XB113	0-12		
AF186	0-40	BY127	0-17	OA2208	0-32	XB121	0-48		
AFY19	1-13	BY182	0-85	OA2209	0-32	ZR24	0-68		
AFZ11	0-80	BY213	0-25	OA2210	0-32				

P.E. SOUND SYNTHESISER

Get away to a flying start with this exciting Space Age project. Precision cut metal parts to form modular units as described in the March issue are available NOW.

A. Power supply subframe with tab drillings only £1-35 (P. & P. 25p).

B. Circuit board support plates fully drilled, 94p.

Details drilled with locating holes only: C. 20mm, 18p; D. 38mm, 21p; E. 60-5mm, 28p; F. 64mm, 31p; G. Module locking rods complete, £1-20. SAVE MONEY by obtaining a complete kit of hardware which comprises 1 off each A, C, D, F, 5 off E, and 7 off B, G £17-42, Post Free. REGULATED POWER SUPPLY fully assembled and GUARANTEED by "SCOPE" Designs & Mfg. Ltd. Voltage rails adjustable from 8-17V. Nom. 15-0-15V at 500mA per rail. Stab. ratio 250 : 1; Ripple and Noise 500µV at full load. Load regulation < 1% zero to full load, line regulation < 1% for 10% change in mains voltage. Size 4in x 2½in x 7in fits easily into power supply subframe. Terrific value at £19-50 Post Free. (Include 15p for insurance if required.)


High Quality components for oscillator and inverter module at highly competitive prices. SAE for free lists.

EATON AUDIO

P.O. Box No. 3
ST. NEOTS
HUNTINGDON
PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2. Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P. All prices subject to V.A.T. increases from 1st April.

Stereo radio from your existing tuner.

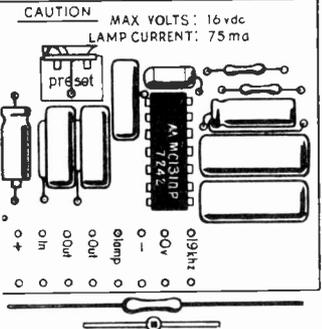

A complete set of parts from Jermyn to build a stereo decoder module that will convert your existing mono tuner for stereo reception whilst maintaining a high standard of reproduction.

The distortion is very low (typically 0.3% at 560 mV RMS composite input signal) with 40dB channel separation.

The stereo switching is automatic and there is a light emitting diode which acts as a stereo beacon. The kit requires no coil and there are no alignment problems.

Fitting. The module requires a 10-16 volt power supply which can normally be tapped off the existing tuner. The signal input is taken off before the de-emphasis circuit which in practice means disconnecting one, or at the most, two capacitors. Any radio engineer will be able to spot these capacitors, but if you're really stuck send the circuit with a SAE to us and one of our engineers will indicate the output point. (This is the full extent of our involvement, no hardware please.)

Of course, if you have a modern mono tuner with a multiplex output our module simply plugs in.

The outputs go via a screened twin cable to the tuner inputs of your stereo amplifier.

And the cost? £4.90 for the Kit with 100% tested integrated circuit. Also available assembled and aligned, checked and ready for use at £6.90 (includes 12 month guarantee). Beat that!

To Jermyn Industries
76 Vestry Estate
Sevenoaks
Kent

Please rush me Kit(s), made up Stereo decoders.
 I enclose cheque/postal order for £
Name
Address
Block Capitals Please

Open daily to callers : Mon.-Fri. 9 a.m.-5 p.m.
Valves, Tubes and Transistors - Closed Sat. 1 p.m.-3 p.m.
Terms C.W.O. only | Tel. 01-677 2424-7

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic ASTRAD 17 and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! THIS ONE SUPERSEDES ALL EARLIER MODELS! It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! *Send quickly, after receiving goods test 7 days, refund if not delighted. Or call. Elegant black & chrome finish fascia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer & sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. Yes, EVERY WAVEBAND instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions. VHF, FM/USW, AM: LW, MW, SW, gets, locally, local & new stations not yet operational, and messages from all over the world! Expensive TURRET TUNER side control waveband selection unit (as used on expensive T.V.'s!) Every waveband clicks into position giving incredible ease of station time push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39in approx. It's also a fabulous CAR RADIO. Can also be used through extension amplifier, tape recorder or public address system. SIZE 14in x 10in x 4in overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities & spares available for years & years to come, if ever necessary!) With WRITTEN GUARANTEE manual with simple operating instructions & circuit diagram. ONLY £20.75 (with mains/battery eliminator £1.48 extra). BOX, POST, ETC. 50p. *BUT WAIT, for only 55p extra you get the sensational "COMPUTERISED" WORLD TUNING GUIDE (it enables you to time, pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. NO GUESSING! NO MESSING!) PLUS Standard "longlife" batteries PLUS ultra sensitive earphone for personal listening. (Sorry—We cannot change these new radios for any earlier model purchased.) HURRY! SHOPERTUNITIES SAVE YOU £££'s & £££'s.

THOUSANDS OF MILES REDUCED TO INCHES? 1973 RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! *COMPUTERISED?

THIS FANTASTIC
EARTH SHRINKER

YES, 24,901 miles
SHRUNK TO ONLY 14" x 10½" x 4½"
inches approx?

28 TRANSISTORS AND DIODES!
WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW, LW, USW.)

BATTERY MODEL £20.75 BOX POST ETC. 50p
MAINS/BATTERY ELIMINATOR £1.48 extra

BRAND NEW FABULOUS **ASTRAD 17**
PORTABLE RADIO & COMMUNICATIONS

RECEIVER

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSION STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!



*COMPARE ITS PERFORMANCE with £80 RADIOS!

FIRST TIME EVER!

*NOW AVAILABLE WITH
fabulous "COMPUTERISED"
WORLD TUNING GUIDE!
NO MORE GUESSWORK—
INSTANT DATA at your fingertips—
enables you to TUNE IN A FLASH to
transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! Fabulous BRAND NEW **SOLID STATE** This equipment's got EVERYTHING!

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

WITH REMOTE CONTROL MICROPHONE

RECOMMENDED RETAIL PRICE £44

OUR PRICE £23.75 CARR. ETC. 35p

Shopertunities "thunder" ahead with an offer that's FANTASTIC (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord.) Record and play back anything, anywhere! RECOMMENDED RETAIL PRICE GENUINELY £44! WE OFFER AT ALMOST HALF PRICE! Wonderful features: * Press-button Keyboard Control Panel or latest MASTER SWITCH control! * "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveler! * Separate ON/OFF and HI-LO volume controls! * Heavy duty built-in speaker! * Earphone (for personal listening or "monitoring") and extension speaker sockets! * Remote control microphone! * Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. AND the amazing built-in full circuit VHF, AM/FM Radio gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets, locally, city and regional stations in every part of the country, plus B.B.C. National VHF. Picks up dozens of foreign stations. Fabulous in your car! You could pay £££'s more for a Car Radio or Car Cassette player ALONE! £23.75, CARR. ETC. 35p. Complete with simple instructions, remote control microphone with on/off switch and microphone stand. WITH WRITTEN GUARANTEE. Send quickly, after receiving goods, test 7 days, refund if not delighted. Or call. BONUS OFFER: Batteries and Cassette Tape 25p extra if required.

FIRST TIME EVER! SAVE £14.48!
BRAND NEW AC/DC BATTERY/MAINS

Cassette TAPE RECORDER & PLAYER FIRST GLASS MAKERS

With remote control microphone.

WE COULD CHARGE UP TO £26.97!

OUR PRICE £12.49 POST ETC. 31p

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb de-luxe portable BATTERY/MAINS tape recorder and player—and incredible Shopertunities bring it to you for ONLY £12.49! Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) AND AUTOMATIC LEVEL CONTROL. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere). Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—record anywhere, indoors or out! Runs on standard batteries AND 220/240V AC mains. Separate jacks for remote control microphone, etc. Size 9½in x 5in x 2½in approx. Design can vary slightly. With carry handle. WRITTEN GUARANTEE and full instructions. (Recommended selling price £26.97.) OUR PRICE ONLY £12.49 post, etc., 31p. * Send quickly, after receiving goods test 7 days, refund if not delighted, or call. BONUS OFFER (strictly rationed one per customer) = Cassette tape, set of standard batteries AND microphone stand all for 50p extra, if required.

Order by post to Uxbridge Road address or call at either store.
Bargains galore at both stores.—(COMMERCIAL TRAVELLERS PLEASE! NOTE: Merchandising office at Holborn Store.)

SHOPERTUNITIES LTD.

Dept. PE/27, 164 UXBRIDGE RD. (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.

SEW PANEL METERS

CLEAR PLASTIC PANEL METERS

TYPE SW.100 100mm x 80mm Fronts

30μA	£2-80
50-0-50μA	£2-80
100μA	£2-80
100-0-100μA	£2-70
500μA	£2-50
1mA	£2-40
20V d.c.	£2-40
300V d.c.	£2-40
300V a.c.	£2-40
1 amp. d.c.	£2-40



Type MR.85P. 4 1/4in. x 4 1/4in. Fronts

50mA	£2-10
100mA	£2-10
300mA	£2-10
1 amp.	£2-10
5 amp.	£2-10
15 amp.	£2-10
30 amp.	£2-20
20V d.c.	£2-10
50V d.c.	£2-10
150V d.c.	£2-10
300V d.c.	£2-10
15V a.c.	£2-10
300V a.c.	£2-10
15V a.c.	£2-10
300V a.c.	£2-10
200μA	£2-30
500μA	£2-30
1mA	£2-30
1-0-1mA	£2-10
5mA	£2-10
10mA	£2-10



Type MR.85P. 1 21/32in. square Fronts.

200μA	£1-75
300μA	£1-75
500μA	£1-75
750μA	£1-75
1 amp.	£1-75
2 amp.	£1-75
5 amp.	£1-75
10 amp.	£1-75
3V d.c.	£1-75
10V d.c.	£1-75
15V d.c.	£1-75
20V d.c.	£1-75
50V d.c.	£1-95
100V d.c.	£1-75
150V d.c.	£1-80
300V d.c.	£1-75
500V d.c.	£1-75
1-0-1mA	£1-75
2mA	£1-75
5mA	£1-75
10mA	£1-75
20mA	£1-75
30mA	£1-75
100mA	£1-75
150mA	£1-75



"SEW" BAKELITE PANEL METERS


Type SD.850 82-5mm x 110mm Fronts

10mA	£2-50
50mA	£2-50
100mA	£2-50
500μA	£2-50
1 amp.	£2-50
5 amp.	£2-50
10 amp.	£2-50
5V d.c.	£2-50
10V d.c.	£2-50
20V d.c.	£2-50
50V d.c.	£2-50
300V d.c.	£2-50
15V a.c.	£2-75
300V a.c.	£2-75
5mA	£2-50
10mA	£2-50
50mA	£2-50
100mA	£2-70
200μA	£2-70
500μA	£2-70
1mA	£2-50
5mA	£2-50




Type MR.52P. 2 1/2in. square Fronts.

50-0-50μA	£2-85
100μA	£2-85
100-0-100μA	£2-75
500μA	£2-55
1mA	£2-20
5mA	£2-20
10mA	£2-20
50mA	£2-20
100mA	£2-20
300mA	£2-20
1 amp.	£2-20
5 amp.	£2-20
10 amp.	£2-20
20 amp.	£2-20
30 amp.	£2-20

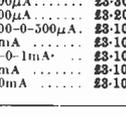

Type MR.45P. 2in. square Fronts.

50μA	£2-50
50-0-50μA	£2-80
100μA	£2-80
100-0-100μA	£2-80
200μA	£2-05
500μA	£1-95
500-0-500μA	£1-85
1mA	£1-85
5mA	£1-85
10mA	£1-85
20mA	£1-85
30mA	£1-85
100mA	£1-85
150mA	£1-85

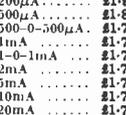


Type MR.65. 3 1/4in. square Fronts.

1 amp.	£2-15
5 amp.	£2-15
15 amp.	£2-15
30 amp.	£2-15
50 amp.	£2-15
5V d.c.	£2-15
10V d.c.	£2-15
20V d.c.	£2-15
50V d.c.	£2-15
150V d.c.	£2-15
300V d.c.	£2-15
50mV d.c.	£2-40
100mV d.c.	£2-40
30V a.c.*	£2-20
50V a.c.*	£2-20
150V a.c.*	£2-20
300V a.c.*	£2-20
500mA a.c.*	£2-15
1 amp. a.c.*	£2-15
5 amp. a.c.*	£2-15
10 amp. a.c.*	£2-15
20 amp. a.c.*	£2-15
30 amp. a.c.*	£2-15
50 amp. a.c.*	£2-15
100mA	£2-15
500mA	£2-15
VU Meter	£2-40




Type SD.640 63-5mm x 85mm Fronts

50μA	£2-60
50-0-50μA	£2-55
100μA	£2-55
100-0-100μA	£2-55
200μA	£2-55
500μA	£2-35
1mA	£2-35
5mA	£2-35
10mA	£2-35
50mA	£2-35
100mA	£2-35

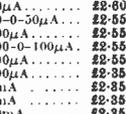


Type MR.65P. 3 1/4in. x 3 1/4in. Fronts

50μA	£2-70
50-0-50μA	£2-60
100μA	£2-60
100-0-100μA	£2-40
200μA	£2-90
300μA	£2-65
500-0-500μA	£2-40
1mA	£2-40
5mA	£2-40
10mA	£2-40
50mA	£2-40
100mA	£2-40
300mA	£2-40
1 amp.	£2-40
5 amp.	£2-40
10 amp.	£2-40
15 amp.	£2-40
20 amp.	£2-40
30 amp.	£2-40
50 amp.	£2-40
5V d.c.	£2-40

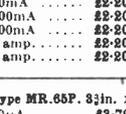

Type MR.45P. 2in. square Fronts.

50μA	£2-50
50-0-50μA	£2-80
100μA	£2-80
100-0-100μA	£2-80
200μA	£2-05
500μA	£1-95
500-0-500μA	£1-85
1mA	£1-85
5mA	£1-85
10mA	£1-85
20mA	£1-85
30mA	£1-85
100mA	£1-85
150mA	£1-85

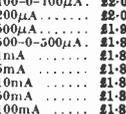


Type S-80 80mm square Fronts

50μA	£2-50
50-0-50μA	£2-40
100μA	£2-40
100-0-100μA	£2-30
300μA	£2-05
1mA	£2-85
20V d.c.	£2-85
50V d.c.	£2-85
300V d.c.	£2-85
1 amp. d.c.	£2-85
5 amp. d.c.	£2-85
300V a.c.	£2-85
VU Meter	£2-70




Type SD.460 46mm x 59-5mm Fronts

50μA	£2-40
50-0-50μA	£2-35
100μA	£2-35
100-0-100μA	£2-35
200μA	£2-35
500μA	£2-20
1mA	£2-15
5mA	£2-15
10mA	£2-15
50mA	£2-15
100mA	£2-15
500μA	£2-15

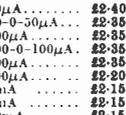

Type MR.65P. 3 1/4in. x 3 1/4in. Fronts

50μA	£2-70
50-0-50μA	£2-60
100μA	£2-60
100-0-100μA	£2-40
200μA	£2-90
300μA	£2-65
500-0-500μA	£2-40
1mA	£2-40
5mA	£2-40
10mA	£2-40
50mA	£2-40
100mA	£2-40
300mA	£2-40
1 amp.	£2-40
5 amp.	£2-40
10 amp.	£2-40
15 amp.	£2-40
20 amp.	£2-40
30 amp.	£2-40
50 amp.	£2-40
5V d.c.	£2-40

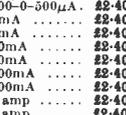

"SEW" EDGEWISE METERS

Type PE.70. 3 17/32in. x 1 15/32in. x 2 1/2in. deep.

50μA	£2-40
50-0-50μA	£2-80
100μA	£2-80
100-0-100μA	£2-20
200μA	£2-20
500μA	£2-30
1mA	£2-30
5mA	£2-30
10mA	£2-30
50mA	£2-30
100mA	£2-30
300μA	£2-30
500μA	£2-30
1mA	£2-30
5mA	£2-30
10mA	£2-30
50mA	£2-30
100mA	£2-30
300μA	£2-30
500μA	£2-30
1mA	£2-30
5mA	£2-30
10mA	£2-30
50mA	£2-30
100mA	£2-30
300μA	£2-30
500μA	£2-30
1mA	£2-30
5mA	£2-30
10mA	£2-30
50mA	£2-30
100mA	£2-30
300μA	£2-30
500μA	£2-30
1mA	£2-30
5mA	£2-30
10mA	£2-30

MULTIMETERS for EVERY purpose!



T360 POCKET MULTIMETER
High-precision at low cost.
Ranges: D.c. 15V, 150V, 1,000V (10,000 O.P.V.), A.c. 15V, 150V, 100V (1,000 O.P.V.).
D.c. Current 150mA. Resistance 100k ohms.
£1-85. Post 15p.

MODEL 1092 Testmeter.

5,000 O.P.V.
0/3/15/150/300/1,200V d.c.
0/6/30/300/600V a.c.
0/300 μ A/300mA
0/10K/1 meg Ω
Decibels -10 to +16 dB
£2-75. Post 15p.



HIOKI MODEL 720K
20,000 O.P.V.
Overload protection
3/25/100/500/1,000V d.c.
100/50/250/1,000V a.c.
50 μ A/250mA. 20K/2 meg. ohm. -5 to +62dB.
£4-97. Post 15p.

HIOKI MODEL 730K

30,000 O.P.V. Overload protection.
6/30/60/300/600/1,200V d.c. 12/60/120/600/1,200V a.c. 60 μ A/30mA/300 mA. 2K/200K/2 meg. ohm. -10 to +63 dB.
£6-50. Post 15p.



MODEL TE-12
20,000 O.P.V. 0/6/6/30/120/600/1,200/3,000/6,000V d.c. 0/6/30/120/600/1,200V a.c. 0/60 μ A/6/60/600mA. 0/8K/600K/6Meg. 160 Meg. Ω 50V.F. 0-2mFd. **£5-97. Post 17p.**

MODEL TE-500

20,000 O.P.V. Overload protection. Mirror scale, overload protection. 0/5/25/125/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50 μ A/250mA. 0/60K/6 meg Ω . -20 to +62dB. **£3-95. Post 15p.**



MODEL 500 30,000 O.P.V. with overload protection mirror scale 0/0-5/10/25/100/250/500/1,000V d.c. 0/2-5/10/25/100/250/500/1,000V a.c. 0/50 μ A/50/500/1,000V a.c. 0/50 μ A/50/500/1,000V a.c. 0/2Meg/60 Meg. Ω . 0/60K/6 Meg. Ω . **£3-87. Post paid.**

HIOKI MODEL 750K

50,000 O.P.V.
43 ranges 0-0.3 to 1,200V d.c. 0-3 to 1,200V a.c.
0-30A/300mA
0-3K/30 meg ohms. -10 to +17dB.
£8-97. Post 20p.



HT1008A MULTI-METER

Features a.c. current ranges. 100,000 O.P.V. Mirror Scale. Overload protection. 0/0-5/2-5/10/50/250/500/1,000V d.c. 0/2-5/10/50/250/500/1,000V a.c. 0/10/250 μ A/2-5/25/250mA/10 amp. d.c. 10 amp. a.c. 0/20K/200K/2MEG/20 MEG. -20 +62dB. **£12-50. Post 25p.**



370 WTR MULTIMETER

Features a.c. current ranges. 20,000 O.P.V. 0/0-5/2-5/10/50/250/500/1,000V d.c. 0/2-5/10/50/250/500/1,000V a.c. 0/50 μ A/1/10/100mA/1/10 amp. d.c. 0/100mA/1/10 amp. a.c. 0/5K/50K/500K/5MEG/50MEG. -20 +62dB. **£15. Post 25p.**



RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 O.P.V. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1,000V d.c. 2-5/10/50/250/500/1,000V a.c. D.c. current 100mA/1/10/100mA/1A. Resistance 300 ohms/300/300K/3M Ω . Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE **£5-97. Post 25p.**




ROUND SCALE TYPE PENCIL TESTER MODEL T9-68


Completely portable simple to use pocket sized tester. Ranges 0/3/30/300 a.c. and d.c. at 2,000 O.P.V. Resistance 0-20K ohms. **ONLY £1-97. Post 13p.**

LT 601 MULTI-METER

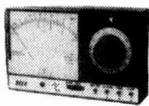New style 20,000 O.P.V. pocket multimeter. 5/25/50/250/500/2,500V d.c. 10/50/100/500/1,000V a.c. 50 μ A/250A. 6K/6 meg ohms. -20 to +22 dB. **£3-75. Post 20p.**



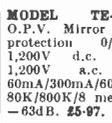MODEL TH-12
20,000 O.P.V. Overload protection. Slide switch selector. 0/0-25/2-5/10/50/250/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50 μ A/25/250mA d.c. 0/3K/30K/300K/3 meg. -20 to +50dB. **£4-97. Post 15p.**



MODEL TE-90
30,000 O.P.V. Mirror scale, overload protection. 0/0-6/3/15/60/300/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30 μ A/6mA/60mA/300mA/600mA. 0/8K/80K/800K/8 meg. ohm. -20 to +63dB. **£5-97. Post 15p.**



MODEL PL486
20k Ω /V d.c. 8k Ω /V a.c. Mirror scale. 0/0-6/3/15/60/300/1,200V d.c. 3/30/120/600V a.c. 50/600 μ A/60/600mA. 10/100K/1 Meg/10 Meg. Ω . -20 to +46dB. **£6-97. Post 12p.**



TMK MODEL TW-50K 46 ranges, mirror scale, 50K/V d.c. 5K/V a.c. D.c.: Volts 0-125, 0-25, 1-25, 2-5, 5, 10, 25, 50, 0-25, 250, 500, 1,000V. A.c. Volts: 1-5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. Current: 25, 50 μ A, 2-5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω . Decibels: -20 to +81-5 dB. **£3-50. Post 17p.**




MODEL K226A
Taut band suspension. Overload protection. Polarity reversing switch. 30,000 O.P.V. 0/0-3/2-5/15/50/250/500/1,000/2,000V d.c. 0/15/50/150/500/1,000V a.c. 0/50 μ A/50/500/1,000/2,000V a.c. 0/3K/300K/3meg. **£3-95. Post 20p.**



HIOKI MODEL 700K
100,000 O.P.V. Overload protection. Mirror scale. 0-3/0-6/1-2/1-5/3/6/12/30/60/120/300/600/1,200V d.c. 1-3/3/6/12/30/60/150/300/600/1,200V a.c. 15/30 μ A/3/6/30/60/150/300mA/6/12 amp. d.c. 2K/200K/2 Meg/20 Meg ohm -20 to +63dB. **£13-50. Post 20p.**



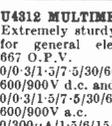MODEL C-7080 EN
Giant 6in mirror scale. 20,000 O.P.V. 0/0-25/1/2-5/10/50/250/1,000/5,000V d.c. 0/2-5/10/50/250/1,000/5,000V a.c. 0/50 μ A/1/10/100/500mA/10 amp. d.c. 0/2K/200K/20 meg. -20 to +50dB. **£13-95. Post 35p.**



U4312 MULTIMETER
Extremely sturdy instrument for general electrical use. 667 O.P.V. 0/0-3/1-5/7-5/30/60/150/300/600/900V d.c. and 75mV. 0/0-3/1-5/7-5/30/60/150/300/600/900V a.c. 0/300 μ A/1-5/6/15/60/150 600mA/1-5/6 amp. d.c. 0/1-5/6/15/60/150/600mA/1-5/6 amp. a.c. 0/200 Ω /3K/30K Ω . Accuracy Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. **£9-50. Post 35p.**

Selected TEST EQUIPMENT

FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and I.C.O. amp or pnp. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. **£7-50. Post 20p.**



MODEL S-100TR MULTIMETER/TRANSISTOR TESTER.

100,000 O.P.V. mirror scale/overload protection. 0/0-12/6-6/3/12/30/120/600V d.c. 0/6/30/120/600V a.c. 0/12/600 μ A/12/300mA/12 amp. d.c. 0/10 K/1 MEG/100 MEG. -20 to +50dB. 0-01-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. **£13-50. Post 25p.**



MODEL 449A IN-CIRCUIT TRANSISTOR TESTER

Checks true a.c. beta in/out. Checks lobo. Checks diodes in/out. Checks SCR, etc. Beta HI 10-300. LO 2-50. Ico Ico 0-5000 μ A. 220/240V a.c. operation. **£17-50. Post 25p.**



TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kHz-500 MHz on 6 bands. Directly calibrated Variable R.F. attenuator, audio output, Xtal socket for calibration. 220/240V a.c. Brand new with instructions. **£15. Carr. 37p. Size 140mm x 215mm x 170mm.**



MODEL L-55 FET V.O.M.

Input impedance 10 meg ohms. 0/0-3/1-2/6/30/120/600V d.c. 0/3/12/60/120/600V a.c. 0/120 μ A/120mA d.c. 0/1K/10K/10 meg/100 meg ohms. **£15-97. Post 25p.**



CI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100kHz V. RMS/mm. 0-1-25; HOR. AMP. Bandwidth 500kHz. Sensitivity at 100kHz V. RMS/mm. 0-3-25; Pre-set triggered sweep 1-3, 000 μ sec.; free running 20-200,000Hz in nine ranges. Calibrator pips, 220mm x 360mm x 430mm. 115-230V a.c. operation. **£39. Carr. paid.**



TO-3 PORTABLE OSCILLOSCOPE

3in tube, Y amp. Sensitivity 0-1V p-p/CM. Bandwidth 1-5cps-1.5MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0-9V. p-p/CM. Bandwidth 1-5cps-800KHz. Input imp. 2 meg Ω 20pF. Time base. 5 ranges 10cps-300KHz. Synchronisation. Internal/external. Illuminated scale 140mm x 215mm x 330mm. Weight 131lb. 220/240V a.c. Supplied brand new with handbook. **£40-00. Carr. 50p.**



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE


5MHz Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in x 4in C.R.T. Calibrated triggered sweep from 0-2 μ sec to 100 milli-sec per cm. Free running time base 50 Hz-1MHz. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual. **£27. Carr. paid.**



TE-16A Transistorized Signal Generator. 5 ranges 400KHz-30MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800KHz modulation. 5 1/2in x 3 1/4in x 3 1/4in. Complete with instructions and leads. **£7-97. Post 20p.**


TRANSISTORIZED L.C.R. A.C. MEASURING BRIDGE

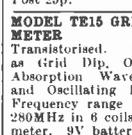A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1 Ω -11 Ω meg Ω . 6 Ranges \pm 1%. L.L. μ H - 1.1 I mFd. 6 Ranges -2%. C. 10pF \pm 1.1 I mFd. 1.1/1000-1.1/100. 6 Ranges \pm 1%. RATIO voltage at 1,000cps. Operated from 9V 100mA. Meter indication. Attractive 2 tone metal case. Size 7 1/2in x 5 1/2in x 2 1/2in. **£20. Post 25p.**



MODEL TE15 GRID DIP METER

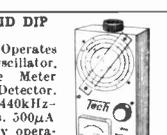Transistorized. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440KHz-280MHz in 6 coils. 500 μ A meter. 9V battery operation. Size 180mm x 80mm x 40mm. **£12-50. Post 20p.**



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.C. OSCILLATOR

Sine 18-200,000 Hz; Square 18-50,000 Hz. Output max. +10dB (10 K ohms) Operation internal batteries. Attractive 2-tone case 7 1/2in x 5 1/2in x 2 1/2in. Price **£17-50. Carr. 17p.**



MODEL MQ-100 SINE SQUARE WAVE AUDIO GENERATOR

Range 18-220,000 Hz. Sine Wave 19 - 100,000Hz. Square Wave. Output Sine or Square wave 10V. P. to P. Size 180mm x 90mm x 90mm. Operation 220/240V a.c. **£17-50. Post 37p.**



MODEL AT201 DECADE ATTENUATOR

Frequency range 0-200kHz. Attenuator 0-11dB. 0-1dB step. Impedance 600 ohms. Max. input power 30dBm. Size 180mm x 90mm x 55mm. **£12-50. Post 37p.**



TE-65 VALVE VOLTMETER

28 ranges. D.c. volts 1-5-1,500V a.c. volts 1-5-1,500V. Resistance up to 1,000 megohms. 200/240V a.c. operation. Complete with probe and instructions. **£17-50. Post 30p.** Additional probes available: R.F. **£2-12**; H.V. **£2-50.**



MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMMETER

Sensitivity 330 ohms/Volt a.c. and d.c. Accuracy 0-5% d.c. 1% a.c. Scale length 165mm. 0/300/750 μ A/1-5/3/7-5/15/30/75/150/300/750mA/1-5/3/7-5/15/30/75/150/300V/1-5/3/7-5/15/30/75/150/300V/1-5/3/7-5/15/30/75/150/300V a.c. Automatic cut. Supplied complete with test leads, manual and test certificates. **£49. Post 50p.**



G. W. SMITH & CO. (RADIO) LTD.
Also see opposite page and next two pages

UNE-30 RECEIVER



4 Bands covering 550kHz-30MHz. BFO. Built-in Speaker 220/240V a.c. Brand new with instructions. £15-75. Carr. 37p.



UR-1A SOLID STATE COMMUNICATION RECEIVER

4 Bands covering 550kHz-30MHz. FET. 8 Meter. Variable BFO for 8SB, Built-in Speaker, Bandsread, Sensitivity Control. 220/240V a.c. or 12V d.c. 12 1/2in x 4 1/2in x 7in. Brand new with instructions. £25. Carr. 37p.

SKYWOOD CX298 COMMUNICATION RECEIVER



Solid state. Coverage on 5 bands 200-420 kHz and 0-35 to 30MHz. Illuminated slide rule dial. Bandsread. Aerial tuning. BFO, AVC, ANL, "8" meter. AM/CW/8SB. Integrated speaker and phone socket. Operation 220/240V a.c. or 12V d.c. Size 325 x 266 x 150 mm. Complete with instructions and circuit. £32-50. Carr. 37p.

LAFAYETTE HA-600 SOLID STATE RECEIVER



General coverage 150-400kHz, 650 kHz-30MHz. FET front end. 2 mech. filters, product detector, variable BFO, noise limiter. 8 Meter, Bandsread, RF Gain. 15 1/2in x 9 1/2in x 8 1/2in. 18lbs. 220/240V a.c. or 12V d.c. Brand new with instructions. £50. Carr. 50p.



TRIO 9B59DS COMMUNICATION RECEIVER

4 band covering 550kHz-30MHz continuous and electrical bandsread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4 1/2 ohm output and phone jack. 8SB-CW. ANL. Variable BFO. 8 Meter. Sep. bandsread dial. HF frequency 450kHz. Audio output 1-5W. Variable RF and AF gain controls 115/250V a.c. Size 7 1/2in x 13 1/2in x 10 1/2in with instruction manual. £49-50. Carr. paid.

EMI LOUSPEAKERS

Model 350. 13in x 8in with single tweeter/crossover. 20-20,000Hz. 15W RMS. Available 8 or 16 ohms. £7-25 each. Post 37p.
Model 450. 13in x 8in with twin tweeter/crossover. 35-13,000Hz. 8W RMS. Available 8 or 16 ohms. £3-62 each. Post 25p.

HOWEYWELL DIGITAL VOLTMETER VT.100



Can be panel or bench mounted. Basic meter circuit. 4 1/2 ohm output and phone jack. 8SB-CW. ANL. Variable BFO. 8 Meter. Sep. bandsread dial. HF frequency 450kHz. Audio output 1-5W. Variable RF and AF gain controls 115/250V a.c. Size 7 1/2in x 13 1/2in x 10 1/2in with instruction manual. £49-50. Carr. paid.

SINCLAIR IC-12



SINCLAIR EQUIPMENT

Project 60 Package offers.
2 x Z30 amplifier, stereo 60 pre-amp, PZ6 power supply. £15-95. Carr. 37p. Or with PZ6 power supply. £18-00. Carr. 37p.
2 x Z30 amplifier, stereo 60 pre-amp, PZ8 power supply. £20-25. Carr. 37p.
Transformer for PZ8. £2-97 extra.
Add to any of the above £4-45 for active filter unit and £13-00 for pair of Q16 speakers. All other Sinclair products in stock.
2000 amp. £21-95. Carr. 37p.: 3000 amp. £23-50. Carr. 37p.: Neoteric Amp. £43-95. Carr. 37p. IC12. £1-80. P. & P. 10p.
NEW PROJECT 605-£20-97. Carr. 37p.

WHARFEDALE MID-RANGE HI-FI UNITS

As used in world famous system. 5 1/2 in dia. Impedance 4/8 ohms. High flux ceramic magnet. 20W RMS. Brand new £1-50. Carr. 37p.

SPECIAL OFFER! GOODMANS AXIOM 301

Hi-Fi 12in 20W twin cone full range speaker. 30-16,000Hz. 16,500 gauss. 8 ohm impedance. Brand new and boxed. (List price £21-72). OUR PRICE £12-50 each. Carr. 50p.

HA-10 STEREO HEADPHONE AMPLIFIER

All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 5MT/100MU. Output 50mW. £5-97. Post 15p.

SPECIAL PURCHASE! NEAT G30J STATIC BALANCE PICK-UP ARMS

Identical specification to NEAT G30 arm but with two-tone chrome and black finish. Complete with head shell, pick-up rest and plug in phono leads. BRAND NEW—FULLY GUARANTEED. ONLY £28-95. Post 25p.

KAMODEN HM-350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and D.C. current. Amplification factor of NPN, PNP, transistors, diodes, SCR's, etc. 4" x 4" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. £12-50. Post 30p.

KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1,000 Megohms, 500 Volt. Battery operated. Wide range clear meter 4 1/2" x 4". Complete with deluxe carrying case, batteries, instructions. £19-95. Post 30p.

ARE-300 AF/RF SIGNAL GENERATOR

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine/square 10V. P-P. RF 100 KHz to 200 MHz. Output 1V maximum. Operation 220/240V a.c. Complete with instructions and leads. £29-95. Post 50p.

AKAI BARGAINS

SUPER MONEY SAVING OFFERS—BUY NOW WHILE STOCKS LAST! ALL BRAND NEW AND FULLY GUARANTEED



- 1721 Tape Rec. £73-95
- X5000 Tape Rec. £99-95
- GX370 Tape Deck £259-95
- 4000DS Tape Deck £73-95
- 4000DS Dust Cover £4-75
- X201D Tape Deck £132-95
- GX221D Tape Deck £169-95
- GX220D Tape Deck £148-50
- GX280D Tape Deck £249-40
- X1810D Tape/8 track Deck £189-95
- GX1900D Tape/Cass. Deck £177-95
- X2000SD Tape/Cas/8 Rec. £223-30
- CR80DS 8 track £121-95
- CR11 8 track Rec. £280-95
- CR11 8 track Rec. £265-95
- CR11 8 track Receiver £118-90
- CR11 8 track system £145-00

- GXC40 Cassette Rec. £82-95
- GXC40D Cassette Deck £67-95
- GXC40T Cassette/Receiver £123-95
- GXC45D Cassette Deck £89-95
- GXC46D Cassette Deck £108-50
- GXC46 Cassette Recorder £115-95
- GXC50D Cassette Deck £111-25
- GXC55D Cassette Deck £110-25
- CR35D Cassette Deck £59-50
- AA6300 Receiver £79-95
- AA8030 Receiver £108-95
- AA8080 Receiver £144-95
- AA8500 Receiver £175-00
- ADM11 Microphones (Pair) £7-50

Carriage 50p extra (recorders and decks 75p).

GENUINE BARGAIN! KOBS SP.3XC STEREO HEADPHONES



Response 10-15,000Hz. Impedance 4-6 ohms. Brand new. Boxed and fully g' teed (List £9-50). OUR PRICE £6-50. Post 25p.

1021 STEREO LISTENING STATION



For balancing and gain selection of loudspeakers with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6in x 4in x 2 1/2in. £2-25. Post 15p.

M7 MIXER PREAMPLIFIER




5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2in x 5 1/2in x 3 1/2in. Inputs Mics: 3 x 3mV 50K: 2 x 3mV 600 ohm. Phono neg. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K. £8-97. Post 20p.

TE-1035 STEREO HEADPHONES



Low cost high performance stereo headphones. Foam rubber ear cups. Adjustable head-band. 8 ohm impedance. 25-18,000Hz. With lead and stereo jack plug. ONLY £1-97. Post 12p.

NEW GARRAD MODULES

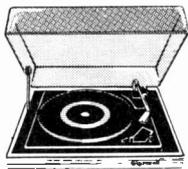

Popular range of Garrad decks with Shure cartridge fitted in deluxe plinth with hinged lid. SP25 III Module/M75-6 £23-50
AP78 Module/M75-6 £33-80
AP96 Module/M75-6 £38-75
Zero 1008 Module/M93E £52-60
Carr. 50p extra any item.

HOSIDEN DH-08 DE-LUXE STEREO HEADPHONES



Features unique mechanical 2 way units and fitted adjustable level controls. 8 ohm impedance 20-20,000cps. Complete with spring lead & stereo jack plug £7-97. Post 12p.

DOLBY SYSTEM NOISE REDUCTION UNIT



Improves the performance of cassette and semi-professional recorders. Reduces tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB at all frequencies above 3000Hz. Controls for input levels and noise reduction on record and replay. 2 meters for Dolby level. Off tape monitoring. Frequency response: 20Hz to 15kHz; 1dB 19kHz-35dB. Size 15 1/2in x 9in x 3 1/2in. A.c. £20/250V. OUR PRICE £32-50 Carr. 50p.

HOSIDEN DHO-28 STEREO HEADPHONES



Wonderful value and excellent performance combined. Adjustable head-band. 8 ohm impedance. 20-12,000 cps. Complete with lead and plug. ONLY £2-37. Post 12p.

TAPE CASSETTES



Top quality Hi-Fi Low Noise in Library cases.
C60 3 for 75p 10 for £2 35
C90 3 for £1 05 10 for £2 30
C120 3 for £1 35 10 for £4 20
Tape Head Cleaner 30p each.
Post 10p extra.

EA.41 REVERBERATION AMPLIFIER



Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2in x 3 1/2in x 4 1/2in. £5-97. Post 12p.

★ TRANSISTORISED FM TUNER ★



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in x 4in x 2 1/2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most 88-108MHz. Really built ready for use. Fantastic value for money. £6-37. Post 12p
Stereo multiplex adaptors £4-97.

TE 1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET




Sensitive, soft earpads, adjustable headband. Magnetic impedance 2,600 ohms. £1-97. Post 15p.

G. W. SMITH & CO. (RADIO) LTD.
Also see previous pages and opposite page

FANTASTIC OFFER!

NIKKO TRM50 STEREO AMPLIFIER

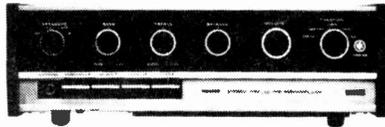

17+17W r.m.s. stereo amplifier with inputs for Magnetic and Crystal phono, Tuner, Tape, Aux and Tape Monitor. Outputs for two pairs of stereo speakers and tape. Stereo headphone socket. Full range of controls including loudness control, scratch filter, etc. Size 13in x 9 1/2in x 3 1/2in. Unrepeatable offer—limited stocks!

List price £59.50
OUR PRICE
£39.95
Carriage 50p

HI-FI EQUIPMENT

SAVE UP TO 33 1/2% OR MORE



SEND S.A.E. FOR FULL DISCOUNT PRICE LISTS AND PACKAGE OFFERS!

NIKKO TRM 50 SYSTEM



NIKKO TRM50 17+17W rms stereo amplifier, BSR MP60, plinth and cover, Goldring G800 cartridge, pair of Linton 2 speakers and all leads.

OUR PRICE **£104.90** Carr. and Ins. £1.50

WHARFEDALE LINTON SYSTEM



Wharfedale Linton Amplifier, Linton Turntable, pair of Linton 2 speakers and all leads.

OUR PRICE **£106** Carr. and Ins. £1.95
LINTON RECEIVER SYSTEM £155. Carr. and Ins. £1.50.

SAVE £££'s PHILIPS GA308 TRANSCRIPTION TURNTABLE

2 speeds 33 1/3 and 45 r.p.m. Lightweight tubular counterbalanced arm. Belt driven low speed synchronous motor. Viscous damped pick-up lift/lower device. Complete with teak plinth and hinged cover. GA308 PU with GP400 stereo magnetic cartridge (list £36.55). OUR PRICE £24.50. Post 75p. GA308 PU with GP400 stereo magnetic cartridge (list £47.65). OUR PRICE £29.95. Post 75p. LIMITED NUMBER ONLY!




RECORD DECKS

(Post 75p)	BBR McDONALD C114 Mini	£4.97	
	C129 Mono	£6.50	
	C137	£6.35	
	MP60	£9.50	
	610	£12.95	
	810	£31.25	
	210/TPD3	£5.75	
	MP60/G800	£12.95	
	MP60/TPD1/G800	£16.05	
	MP60/TPD2/G800	£16.05	
	610/TPD1	£18.95	
	310/TPD1	£17.95	
	HT70	£18.95	
	HT70/G800	£17.25	
	HT70/TPD1/G800	£20.35	
	HT70/TPD1/G800	£23.90	
	810 Plinth/Cover	£9.25	
	GOODMAN'S TD100 Teak	£51.95	
	GOLDRING GL69/2	£18.50	
	GL72	£29.95	
	GL72/P	£27.50	
	Plinth 69/72	£7.02	
	LD1 72	£3.25	
	GL75	£26.95	
	GL75P	£23.25	
	Plinth 75	£7.35	
	LD1 75	£3.00	
	G99	£19.25	
	GL85P/C	£56.95	
	GI01P/C	£20.50	



LEAK DELTA 30 SYSTEM

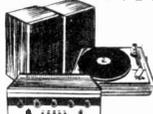

Leak Delta 30 stereo amplifier, Goldring GL75, plinth, cover and G800 cartridge. Pair of Leak 150 speakers and all leads.

OUR PRICE **£123.50** Carr. and Ins. £1.50

AMSTRAD 8000 II SYSTEM



Amstrad 8000 II 7+7W amplifier, BSR MP60, plinth and cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.

OUR PRICE **£48.25** Carr. and Ins. £1.50
Amplifier only, £16.95. Carr. 50p.

TELETON SAQ206B SYSTEM



Teleton SAQ206B 8+8W amplifier, BSR MP60, plinth and cover, Goldring G800 cartridge, pair of Apollo speakers and all leads.

OUR PRICE **£54.40** Carr. and Ins. £1.50
Amplifier only, £22.95. Carr. 50p.

SUPER BARGAIN!

AUDIOTRONIC ACP 8 8-TRACK CAR STEREO TAPE PLAYER



Tone, volume and balance controls. Track selector. Complete with matched pair of stereo speakers, connections and fittings.

ONLY **£15.95** Post 30p

HOMER INTERCOMS



Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station £2.97, 3 Station £5.25. Post 15p. 4 Station £6.62. Post 17p.

BH.001 HEAD SET AND BOOM MICROPHONE

Moving coil. Ideal for language teaching, communications. Headphone imp. 16 ohms. Microphone imp. 200 ohms. £4.62. Post 10p.



MONOTONE 6750 SYSTEM



Monotone AM/PM 4+4W stereo tuner amplifier, Garrard 2025 T/C, plinth and cover, stereo cartridge, pair of matching speakers and all leads.

OUR PRICE **£35.50** Carr. and Ins. £1

AUDIOTRONIC ACR 3500 MW/LW CAR RADIO



Fully transistorised, dual waveband. Size 6 1/2in x 4 1/2in x 2 1/2in. 12V d.c. Neg. or pos. earth. Complete with fixing kit, speaker and leads.

ONLY **£7.50** Post 20p



B.S.R. TD8S 8-TRACK STEREO TAPE PLAYER DECK

Integrated preamps (output 125mV) to feed into any stereo amplifier. Automatic and manual programme selector. 4 pole synchronous motor. 210/240V a.c. OUR PRICE **£16.25** Carr. 50p.

CREDIT TERMS FOR CALLERS ACCESS & BARCLAYCARD WELCOME

V.A.T.

INFORMATION

All mail orders received on or after April 1st will be subject to Value Added Tax.

THIS MUST BE ADDED TO THE TOTAL VALUE OF GOODS ORDERED (INCLUDING POSTAGE/CARRIAGE) AND ENCLOSED WITH ORDER.

ROTEL BARGAINS!

ALL BRAND NEW AND GUARANTEED




RA210 Amp.	£22.50
RA310 Amp.	£35.95
RA610 Amp.	£51.95
RX150 Receiver	£45.95
RX200 Receiver	£57.50
RX400 Receiver	£70.95

Post 50p extra any item.



SPECIAL OFFER! ROTEL RH700 STEREO HEADPHONES

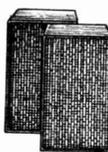20-20,000Hz. 8-16 ohm. (List £9.95). OUR PRICE **£6.75**. Post 25p.



SPECIAL OFFER! STEREO SPEAKERS

Matched pair of stereo bookshelf speakers. Deluxe teak veneered finish. Size: 14 1/2in x 9in x 7 1/2in. 8 ohms. 8W RMS. 16W peak. Complete with DIN lead. £12.95. Carr. 50p.

PLINTHS AND COVERS

Budget SP25, etc.	£3.00
Budget AP76/Zero 1008	£4.50
Budget B.S.R.	£3.25
SME 2000 System	£34.50

RECORD DECK PACKAGES (Post 75p)

Decks supplied with stereo cartridge ready wired in plinth with cover.	
GARRARD SP25TC/GTAHCD	£12.75
SP25 III/G800	£18.50
SP25 III/M75-6	£18.50
SP25 III/M44-7	£19.75
SP25 III/M44-E	£20.95
SP25 III/M55E	£22.40
AP76/G800	£27.95
AP76/M75-6	£20.25
AP76/M55E	£20.50
AP76/M75EJ	£22.50
AP76/G800E	£20.75
AP76/M44E	£20.50
AP76/M75ED	£23.95
B.S.R. McDONALD MP60/G800	£17.50
MP60/M44-7	£18.95
MP60/M44-E	£18.95
GOLDRING GL75/G800	£39.50
GL75/G800E	£42.50



G.W. SMITH & CO (Radio) LTD


Personal Callers Welcome—All Branches Open 9-6 Mon. to Sat.

10 TOTTENHAM CT. RD. LONDON, W.1
27 TOTTENHAM CT. RD. LONDON, W.1
257/258 TOTTENHAM CT. RD. LONDON, W.1
3 LISLE STREET, LONDON, W.C.2
34 LISLE STREET, LONDON, W.C.2
311 EDGWARE ROAD, LONDON, W.2

Tel: 01-637 2232
Tel: 01-636 3715
Tel: 01-580 0670
Tel: 01-437 8204
Tel: 01-437 9155
Tel: 01-262 0387

All Mail Orders to—
11-12, Paddington Green,
London, W.2
Tel: 01-262 6562

P.E. Sound Synthesiser

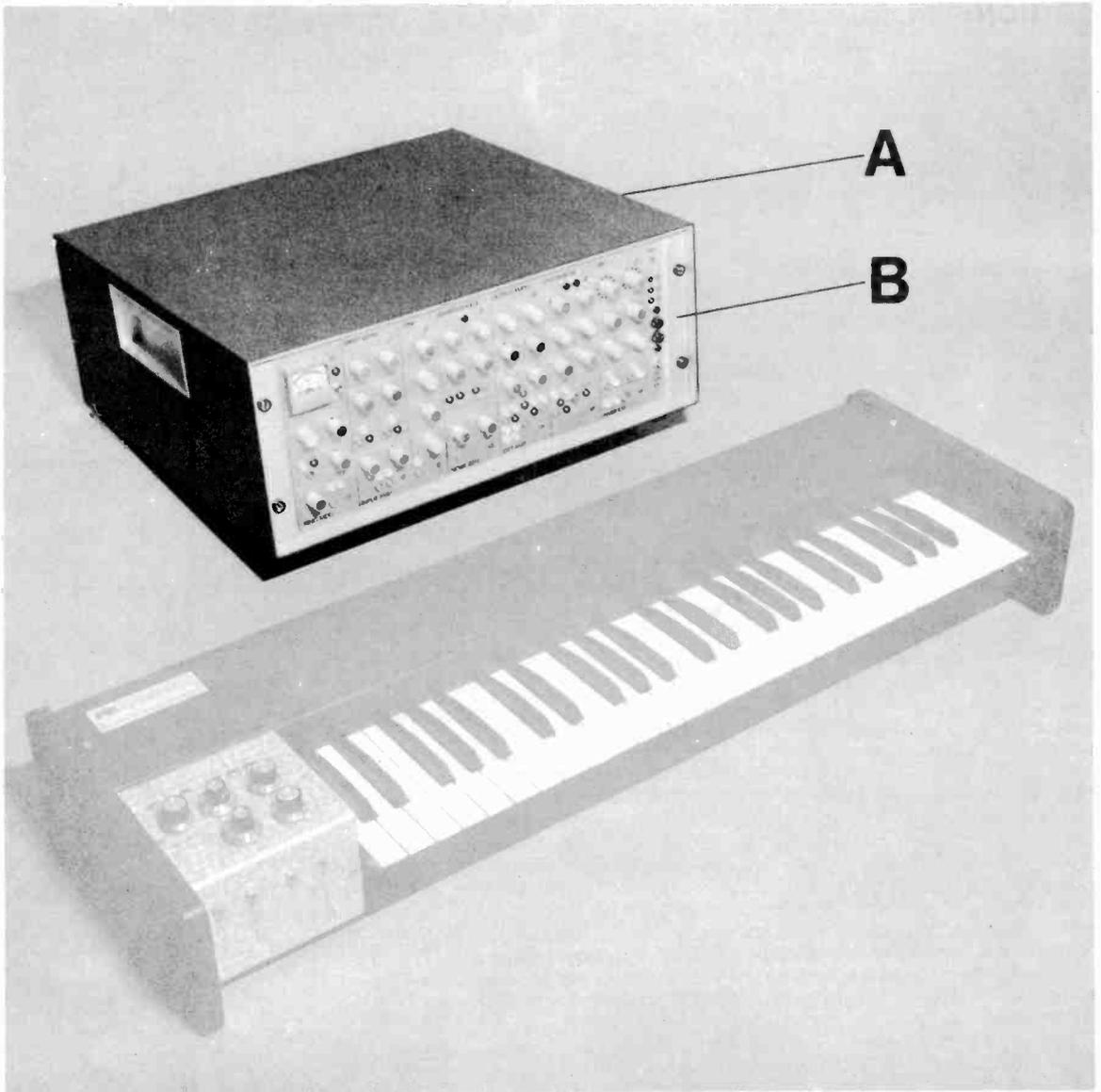

As featured in the current Practical Electronics articles.
Case and framework exclusively available from manufacturers.
Case Part No. 1CD/4U/215 ——— A
Framework Part No. CF/4U/13/D/MR1 ——— B
Total price inclusive of carriage and packing.
Send cash with order for immediate delivery.

VERO ELECTRONICS LTD.,
Industrial Estate,
Chandlers Ford, Eastleigh,
Hants. SO5 3ZR.

Registered No. 701364



FASHIONS IN BUILDING

As a constructors' magazine PRACTICAL ELECTRONICS is naturally very much concerned with building methods and materials. In its fairly short history, electronics has evolved through three distinct periods represented by different fashions in constructional techniques. First was the wood or original "breadboard" era; then the metal era dominated by the box-like chassis; now the plastics era is here with s.r.b.p. board (in some form or another) providing the main platform for the assembly of circuit components.

In many modern designs metalwork is no longer an essential part of the structure carrying the circuit components. Frequently, metalwork is used in a subservient role, merely to enclose or protect an electronic assembly which exists as a more or less self-contained entity built upon a piece of laminated plastics board.

The "plastics era" dawned soon after the arrival of the transistor. Right at the outset of this momentous technological event, industry was able to accommodate this newcomer by adopting printed circuit techniques. These techniques were already well established and in use with miniature valves. While the printed circuit was an ideal technique for mass production of electronic assemblies, it was not so ideal for the private constructor and his "one-off's". So when transistors became available to the individual, improvisation was called for, and a period of great inventiveness ensued. Many varied (and some quite unexpected) building techniques were tried out.

As a start, existing standard items such as component group boards and tag strips were commonly pressed into service as a platform for a transistorised circuit. Assemblies of varying degrees of elegance were built on odd scraps of s.r.b.p. laminate board, hardboard, and even cardboard. The arrival of perforated s.r.b.p. board helped towards a tidier form of construction and eliminated the drudgery of drilling countless holes. However, there was no universally adopted method for home construction until, some 12 years after the first transistor, there appeared in this country the first purpose-designed proprietary printed wiring board. Like many brilliant and successful ideas, this product was, in essence, beautifully simple and—after the event—so obvious. In due course this printed wiring board, though of course initially conceived with the professional user in mind, was to prove the answer to most private constructors' needs, and in time it rationalised the construction of electronic circuits.

PRACTICAL ELECTRONICS played not an insignificant part in bringing this constructional method to the attention of the amateur. This particular board was introduced to constructors in the very first issue of this magazine, and subsequently has been used in the majority of our projects.

Though very popular, the printed wiring board has no monopoly however, and the constructor has a fair choice of alternative methods, including home-made printed circuits. But practically all methods used today are based on the plastics board, the indispensable material which provides the foundations for modern electronic assemblies.—F.E.B.

Editor

F. E. BENNETT

Editorial

D. BARRINGTON

G. GODBOLD

S. R. LEWIS B.Sc.

Art Dept.

J. D. POUNTNEY *Art Editor*

J. A. HADLEY

R. J. GOODMAN

S. W. R. LLOYD

Advertisement Manager

D. W. B. TILLEARD

Phone: 01-634 4202

P. J. MEW

Phone: 01-634 4210

C. R. BROWN, *Classified*

Phone: 01-634 4301

Editorial & Advertising Offices:

Fleetway House, Farringdon St.,

London EC4A 4AD


Phone: Editorial 01-634 4452

Advertisements 01-634 4202

PE Sound Synthesiser 3

VOLTAGE CONTROLLED OSCILLATORS and INVERTER

By G.D. SHAW

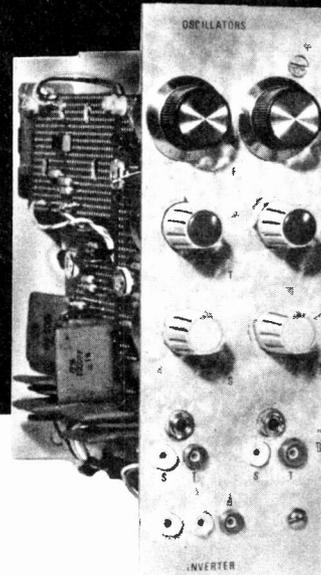

THIS month the voltage controlled oscillator and voltage inverter will be described as well as details for assembling them.

THE VOLTAGE CONTROLLED OSCILLATOR

Perhaps the most important reason for the employment of a voltage controlled oscillator lies in the resultant ability of the oscillator to produce tone patterns by application of varying voltages to its control input. If these voltages are derived from what is essentially another oscillator, or series of oscillators, running at ultra low frequency, then the performance of the tone generating oscillator becomes quite automatic and dependent only on the continued operation of the programming devices.

The oscillators in the Synthesiser are based on the operational linear integrator and the circuit is shown in Fig. 3.1. In this arrangement IC1 acts as the integrator while IC2 is connected as a comparator and serves to switch the direction of integration.

The integrator programming signal is applied across the diode bridge D1-D4 and it is important that the polarities are maintained as shown.

CIRCUIT ACTION

To describe the circuit action assume that the comparator is sitting at its positive saturation level then diodes D1 and D3 in the integrator input bridge are reverse biased. There is a current flow into the integrator summing junction through R1, D2 and similarly a current flow away from the bridge through D4, R2, shown by solid arrows, so that the integrator begins to ramp negatively. The negative excursion of the integrator output voltage will continue until the current driven through R5 is equal to or greater than the current driven through R4 as a result of the output voltage of the comparator. At this time the voltage at point P will go negative and the comparator will switch rapidly to its negative saturation level.

Under these conditions diodes D2 and D4 in the integrator input bridge are reverse biased and current flows are established as shown by the dotted arrows. In the case of the current flow away from the integrator summing junction, this causes the integrator to ramp positively.

WAVESHAPES DEVELOPED


Providing that R2 is the same value as R1 and both polarities across the input bridge are at the same potential then the rate of change of integrator

output voltage is the same as before and the result is a symmetrical triangular waveform appearing at point Q. The oscillogram of Fig. 3.1 shows the phase relationship between the triangular waveform generated by the integrator and the switching waveform generated by the comparator at point R in the circuit.

When the integrator output voltage is again equal to or greater than the level of positive feedback set by R4 the comparator switches back to its positive saturation level and the cycle repeats.

FREQUENCY CONTROL

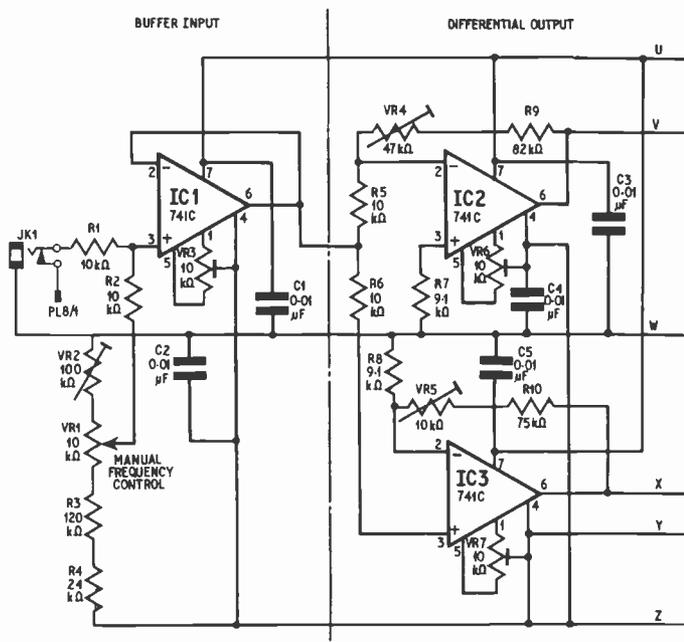Consideration of the foregoing reveals that R4 actually plays a part in the determination of fre-



quency by setting the point at which the integrator output causes the comparator to switch.

Lowering the value of this component has the effect of increasing the level of positive feedback to the comparator thereby requiring a higher integrator output voltage to switch the comparator and thus lowering the frequency of operation of the integrator..

Conversely, if the value of R4 is increased the overall frequency of operation is also increased.

PRACTICAL V.C.O.

The circuit shown in Fig. 3.2 is the three stage prototype v.c.o. arrangement. Starting from the output end, the third stage is a practical form of the oscillator shown schematically in Fig. 3.1. The second stage consists of two operational amplifiers arranged to provide a differential output across the oscillator input bridge. This particular stage is necessary since, in order to attain the full frequency range, the oscillator requires a drive potential greater than the individual power supply rails can provide.

The first stage of the circuit is a buffer/follower which serves to reduce the current drive required from the control source and which also provides a test-bed on which to try out various forms of circuit response without the necessity of disturbing the settings of the oscillator and differential driver. The type of input stage used in the v.c.o. is of some importance since it has a bearing, not only on the performance of the oscillator as a whole, but also on the design and operation of other circuits in the synthesiser. The response of the input stage may therefore be either linear or logarithmic and there are advantages and disadvantages attached to both methods.

LOGARITHMIC OSCILLATORS

Most commercially available synthesisers use logarithmic v.c.o.s in which the slope of the response

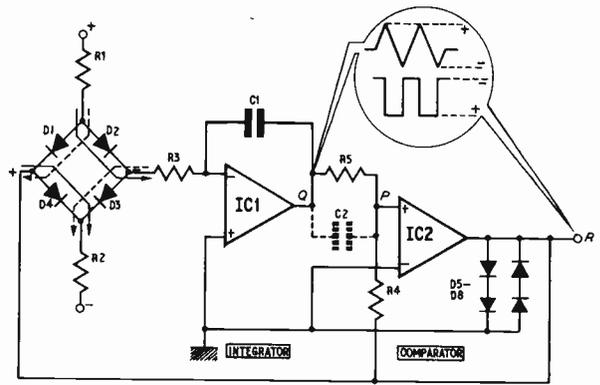


Fig. 3.1. Basic voltage controlled oscillator. Oscillogram shows phase relation between integrator and comparator outputs. The inclusion of the capacitor shown dotted linearises the input voltage/frequency relationship.

is adjusted so that equal increments of input voltage raise the frequency of oscillation by one semitone.

A typical response curve is shown in Fig. 3.3. This has the distinct advantage that if, say, three oscillators are programmed simultaneously by the same control voltage, two of the oscillators may be manually offset by fixed multiples of the semitonal voltage increment so that the effect of the mixed oscillator output is that of producing a chord by the depression of only one key.

The arrangement of having equal voltage increments per semitone also allows for a simplification in the construction of the keyboard divider network and some commercial instruments use a series chain of equal value resistors with a form of "tuning" control which varies the voltage across the chain.

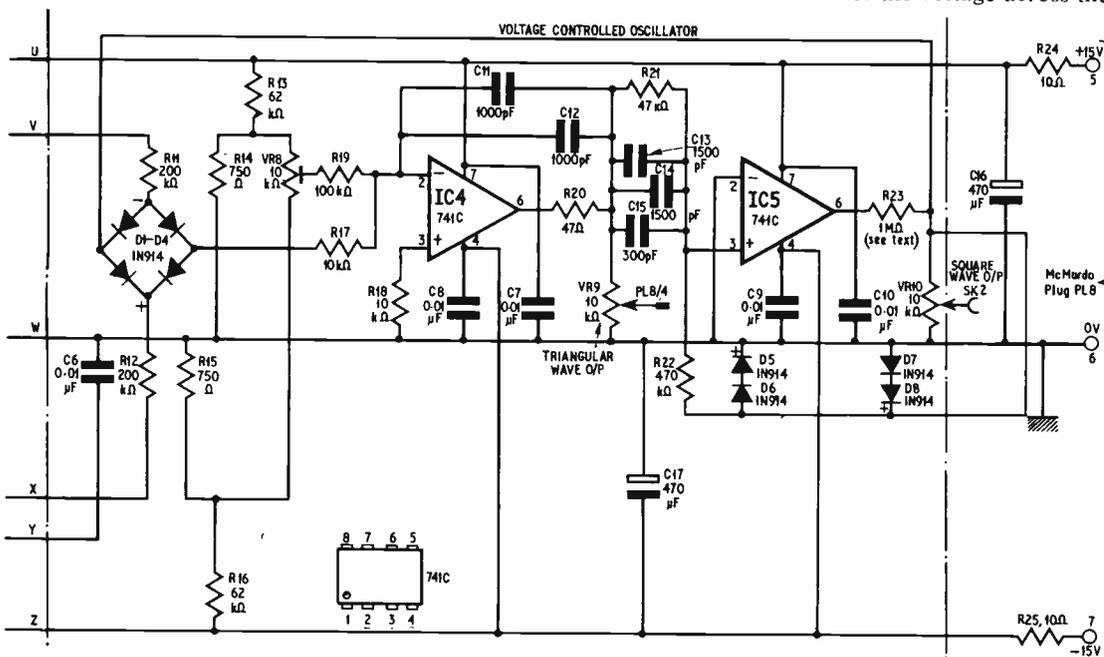


Fig. 3.2. Circuit diagram of the three stage voltage controlled oscillator

LINEAR V.C.O.'s COMPARED

The oscillators in this Synthesiser are arranged with an input stage having a linear performance such that the overall response is as shown in Fig. 3.4.

The resulting loss of the ability to play "chords" was not considered a disadvantage when weighed against the advantages of simplification in building and setting up. Furthermore, the use of linear characteristics in the oscillators provides greater justification for the use of a parallel divider network in the keyboard which, although rather more complex than the series arrangement, means that the accuracy of each semitone is dependent only on the accuracy and stability of its own resistors and not upon the remainder of the chain.

The overall performance of the oscillator, however, is solely dependent upon the response characteristic of the buffer/follower stage and it will be noted that space has been left on circuit board B (Fig. 3.6) for the benefit of constructors who may wish to try out their own ideas of logarithmic response.

The SN76502 manufactured by Texas Instruments is a logarithmic amplifier in integrated circuit form.

MAJOR COMPONENTS

The estimated total cost of this project is around £200. Obviously this figure can be reduced if bulk purchase of components which will appear in quantity is made. To make this possible, components in excess of 12 are listed below.

Resistors	Quantity
10kΩ	52
33kΩ	12
All 5% ½ watt carbon	
5.1kΩ	13
7.5kΩ	36
10kΩ	15
All 2% ½ watt metal oxide	
Potentiometers	Quantity
10kΩ carbon linear	19
All 25mm dia. midget moulded carbon types	
10kΩ carbon linear horizontal presets	12
100Ω linear horizontal Cermet presets	53
10kΩ linear horizontal Cermet presets	21
Integrated Circuits	Quantity
741C 8 pin D.I.L.	56
Diodes	Quantity
1N914	39
1SJ50	14
Capacitors	Quantity
470μF elect. 25V	12
0.01μF polyester	46
Sockets	Quantity
3.5mm miniature jack sockets	15
2mm miniature sockets	48

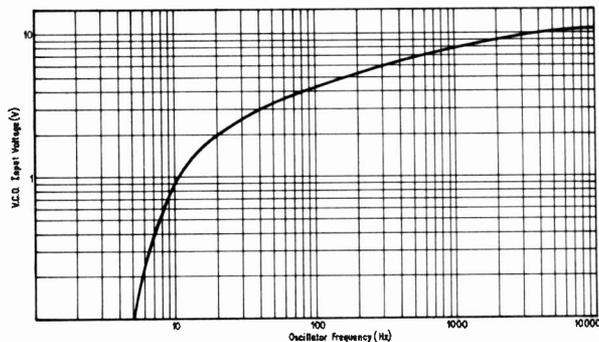


Fig. 3.3. Logarithmic response curve showing the positive exponential relationship obtained when control voltage required is IV/octave

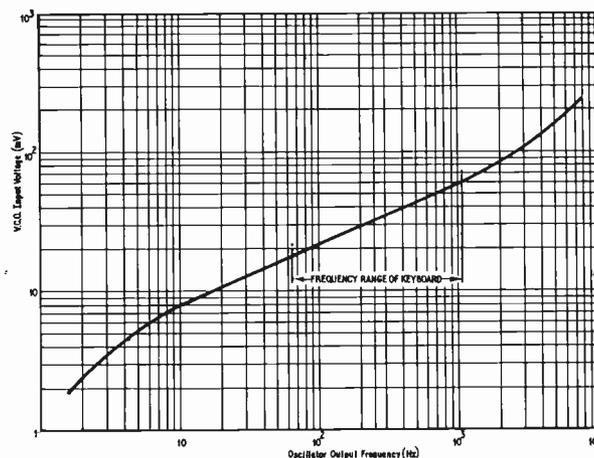


Fig. 3.4. Linear response curve of v.c.o. showing frequency range of keyboard

The advantage of this device is that its response slope may be varied by adjustment of one external component so that performance matching becomes a relatively simple matter.

BUILDING THE OSCILLATOR

Due to the restricted space in the finished module construction should start by assembly and wiring of all the components on to the front panel before the panel is mounted to the circuit board support plate. Figs. 3.5 and 3.6 give the front panel drilling details and component layout. The leads from the controls should be formed into a harness which passes down the centre of the panel between the potentiometers as shown, those for routing to the circuit boards being about ten inches long.

Next mount the McMurdo plug to the rear of the circuit board support plate complete with its wire leads already soldered into position. Fit the eight stand-off supports to the plate—transpillars are recommended but six B.A. screws with metallic spacers may be used providing that these are isolated from the conducting strips on the circuit boards.

The front panel should now be fixed to the circuit board support plate using a 4B.A. countersunk screw and nut in the upper hole, and the locking rod and bush in the lower one. If the assembly seems to be

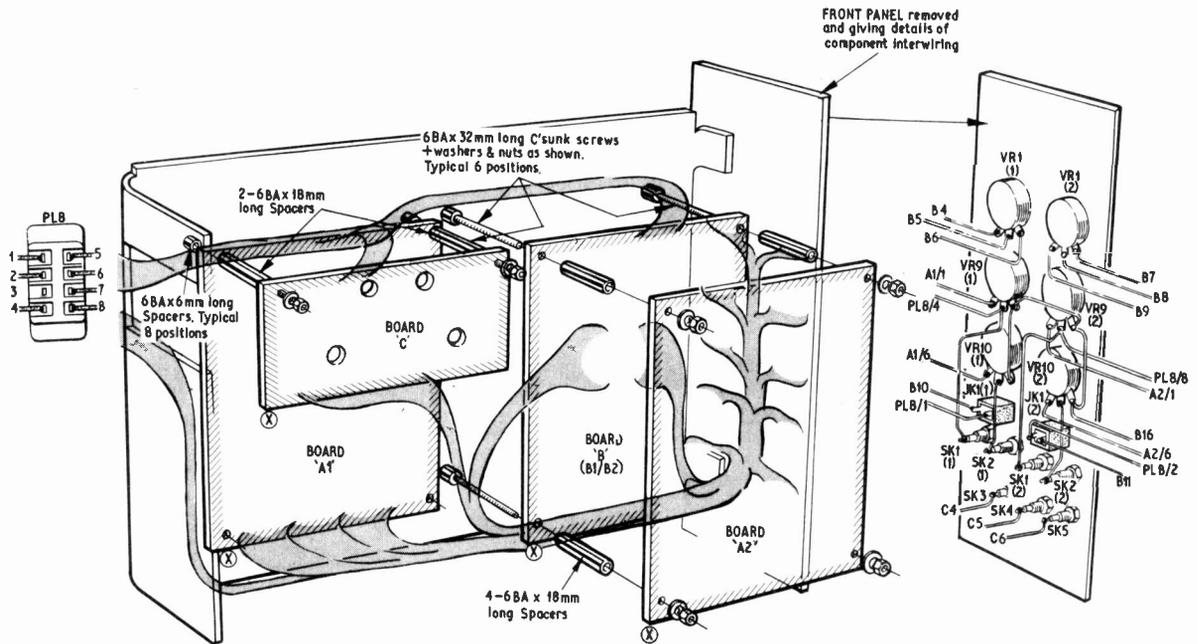



Fig. 3.5. Front panel component assembly and wiring with details of mounting and disposition of boards on the module support plate. The small ringed X at the board edges indicates orientation. (See board details)

on the slack side this may be corrected by fitting a thin steel washer between the bush and lug on the circuit board support plate.


It is useful, at this stage, to make up a jumper lead carrying power supplies from the main busbars so that modules may be tested and set up outside the main frame assembly. The lead should be about 24in (61 cms) in length terminated at one end by a McMurdo plug and at the other by a McMurdo socket wired to match the power supply outputs.

Figs. 3.7 and 3.8 show the circuit board layouts for the oscillator. Board A carries the differential output stage together with the oscillator itself and two of these boards are required.

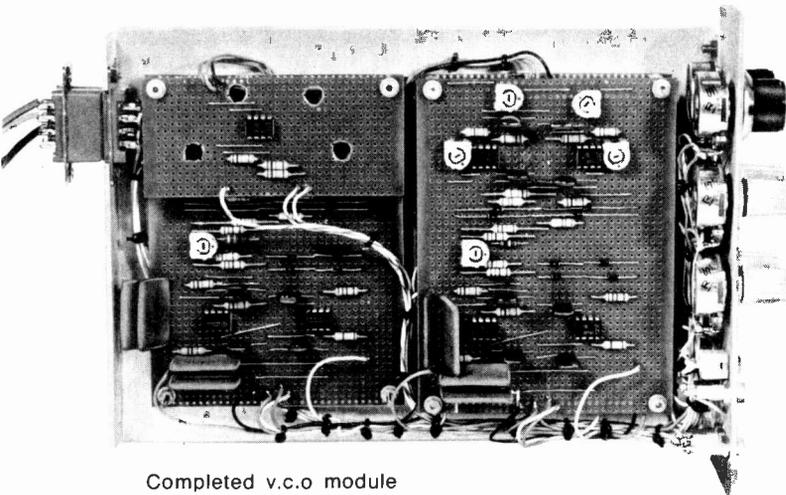Board B carries the buffer input stages and power supply decoupling stages for both the other boards.



Completed v.c.o module

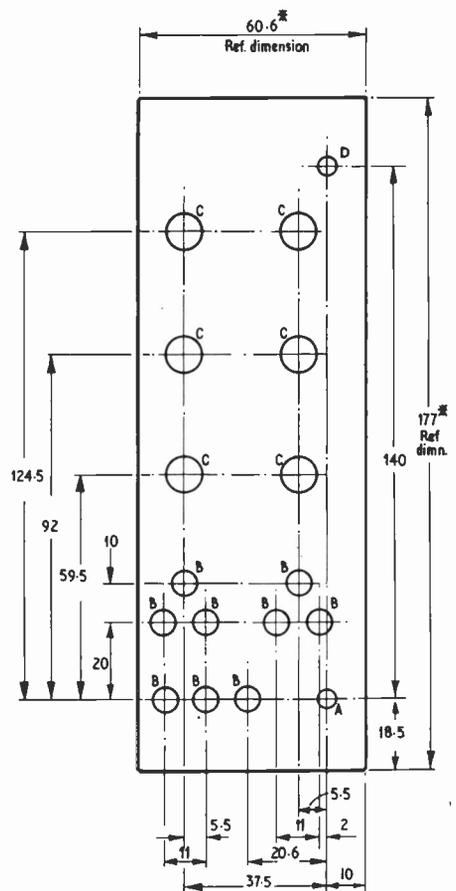

- 1 Hole 'A' 2BA clear
- 9 Holes 'B' 6 dia
- 6 Holes 'C' 9 dia
- 1 Hole 'D' 4BA c/s

* Ref dimensions (see Note Fig 2-2 March 1973)
All dimensions in mm
Material: 14S.W.G. Aluminium

Fig. 3.6. Drilling details for v.c.o. module front panel

BOARD B

The next stage of construction covers assembly of the buffer input stage and power supply decoupling Board B. Fig. 3.7 shows the recommended layout. Wiring of the completed board into the support frame is simplified if single ended Veropins are inserted into the boards at the indicated positions of the lead out wires.

Mount Board B to the support plate adjacent to the front panel and couple up the leads to the power supply, VR1 (manual frequency control) and external input sockets. The leads to Boards A may be omitted at this stage.

COMPONENTS . . .

VOLTAGE CONTROLLED OSCILLATOR (2 REQUIRED)

Resistors

R1	10k Ω	R13	62k Ω
R2	10k Ω	R14	750 Ω
R3	120k Ω	R15	750 Ω
R4	24k Ω	R16	62k Ω
R5	10k Ω	R17	10k Ω
R6	10k Ω	R18	10k Ω
R7	9.1k Ω	R19	100k Ω
R8	9.1k Ω	R20	47 Ω
R9	82k Ω	R21	47k Ω
R10	75k Ω	R22	470k Ω
R11	200k Ω	R23	1M Ω (see text)
R12	200k Ω	R24-R25	10 Ω (2 off)

All 2% $\frac{1}{2}$ watt metal oxide

Capacitors

C1-C10	0.01 μ F Polyester (10 off)
C11-C12	1,000pF Silver Mica (2 off)
C13-C14	1,500pF Silver Mica (2 off)
C15	300pF Silver Mica
C16-C17	470 μ F elect. 25V (2 off)

Diodes

D1-D8 1N914 (8 off)

Potentiometers

VR1	10k Ω carbon log	} miniature cermet types
VR2	100 Ω horizontal preset	
VR3	10k Ω horizontal preset	
VR4	47k Ω horizontal preset	
VR5	10k Ω horizontal preset	
VR6	10k Ω horizontal preset	
VR7	10k Ω horizontal preset	
VR8	10k Ω horizontal preset	
VR9	10k Ω midget moulded carbon linear	
VR10	10k Ω midget moulded carbon linear	

Integrated Circuits

IC1-IC5 741C 8 pin dual-in-line (5 off)

Miscellaneous

SK1—3.5mm jack socket, SK2-SK3 2mm miniature socket (2 off) 0.1in matrix Veroboards as required.

CHECK-OUT

Set VR3 to mid position and VR2 to the minimum position and attach the jumper lead. With the power supply switched on and VR1 at minimum position measure the voltage at VR1 wiper. Adjust VR2 on both drivers so that voltages are exactly the same.

The value is not critical at this stage but is preferably in the range -5mV to -10mV . Measure the output voltage of both drivers and adjust VR3 until it is equal to whatever voltage has been set on the wipers of VR1.

Connect a temporary link between the external input and ground on both drivers. The purpose of these links is to simulate a zero-voltage prewired programming connection and they will be removed on completion of the setting up of the oscillators. Finally, set VR1 to its maximum position and measure the voltage at the sliders. This should be about -750mV , depending on the actual potential of the power supply rails, any discrepancy between the two readings being corrected by adjustment of the values of R3 and/or R4.

BOARD A: ASSEMBLY AND CHECK-OUT

Assembly of Board A should commence with the differential output stage which should be constructed up to and including R11 and R12. This stage should now be set up before proceeding with the construction of the oscillator.

Make temporary power supply connections from Board B, attach an input lead to the differential output stage and connect this directly to ground. With VR4 and VR5 at their maximum settings and VR6 and VR7 at their mid positions switch on.

Monitor the output voltages of both halves of the stage and adjust VR6 so that the output of IC2 reads $+5\text{mV}$ and VR7 so that the output of IC3 reads -5mV . Now reconnect the input of the differential stage to the output of the driver from which the power supply is being taken and set the output voltage of the driver to -25mV by means of VR1.

Monitor the outputs of IC2 and IC3 and adjust VR4 and VR5 until these read $+255\text{mV}$ and -255mV respectively. Repeat the measurements at various settings of VR1 to ensure that the gain of each half of the stage is linear at $\times 10$ throughout the working range. Remember that the actual readings should be, in the case of IC2, $+ [5\text{mV} + (10 \times \text{driver output voltage})]$ and in the case of IC3, $- [5\text{mV} + (10 \times \text{driver output voltage})]$.

Having set the gain and offset of the differential output stage the assembly of the oscillator section may now be completed (Fig. 3.8).

CHOICE OF CAPACITOR

The type of capacitor used in the integrator is of some importance as far as frequency stability is concerned and it is best to use a type having low leakage and as low a value of inductance as possible. Silver mica is thus the best choice and the value shown may be made up of two or more parallel wired capacitors.

R23 serves to limit the current output of the comparator. With this omitted the comparator has only the forward resistance of D5-8 between its output and ground and, although IC5 is capable of handling the current involved, this means that a substantial ripple will be present on the oscillator power supply rails and could possibly be transmitted through to

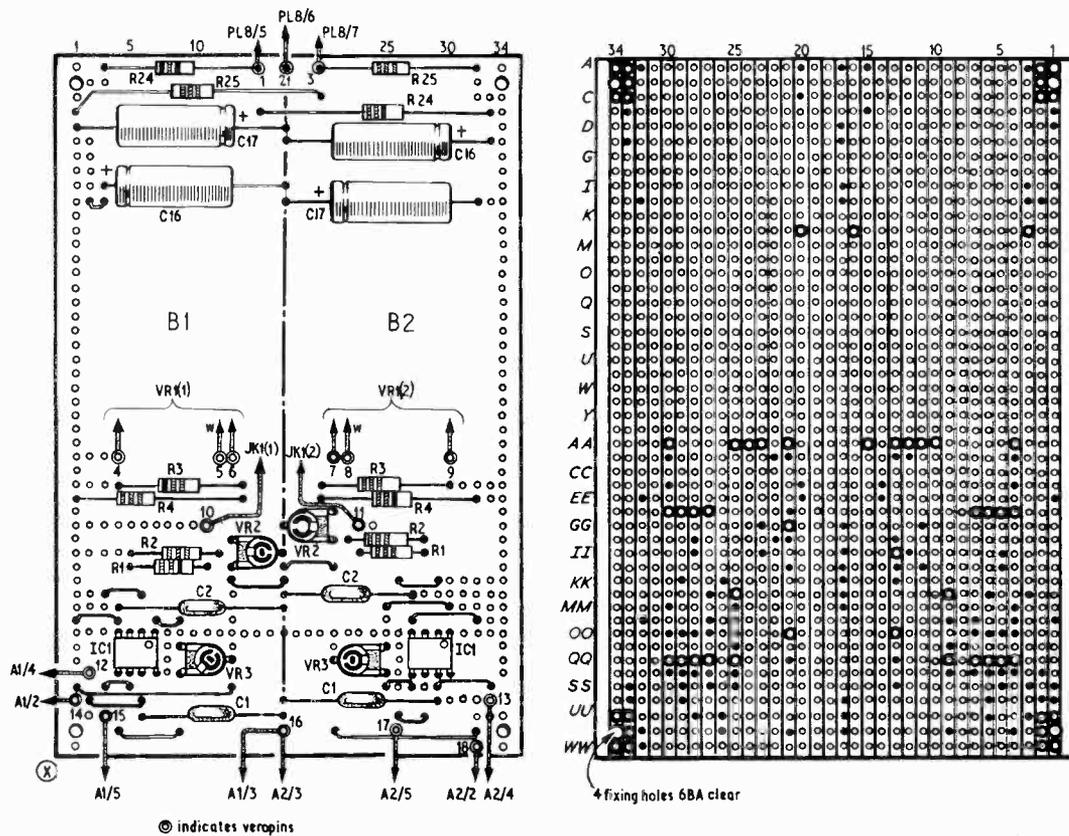


Fig. 3.7. Component layout and wiring for Board B. Since two v.c.o.'s are required, components for each are arranged in board areas B1 and B2

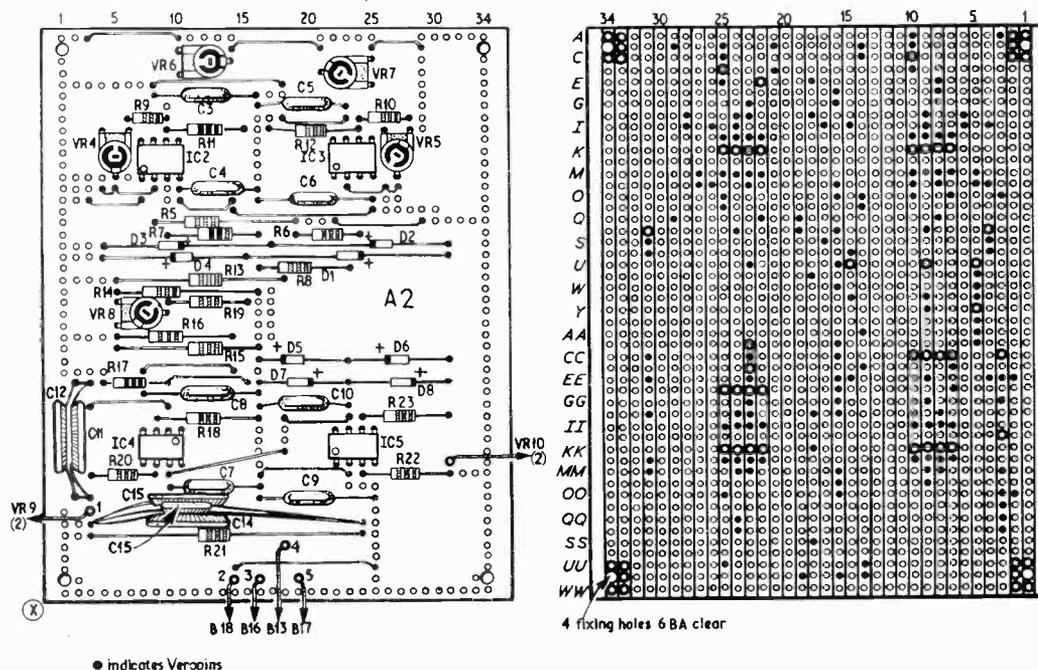


Fig. 3.8. Component layout and wiring for Board A. Two of these are required as shown in Fig. 3.5

the main bus-bars. Thus, where it is intended to use the comparator square wave output as a signal source the value of R23 should be 2.2 kilohms, that is, sufficient to reduce the ripple to an acceptable level. When the square wave output is not to be used, such as in the keyboard oscillators, the value may be increased to 1 Megohm to reduce ripple to negligible proportions. The inclusion of this resistor will however reduce the triangular wave voltage swing to 200mV p-p and limit the maximum frequency of the oscillator to about 8.3kHz.

R13 to R16 and VR8 form a divider network which provides a value of bias current to the summing junction of the integrator.

MOUNTING THE A AND B BOARDS

The completed A boards should be mounted on the support plate such that one is immediately

adjacent to the McMurdo plug and the other directly above Board B. It is best to mount and set-up the oscillator boards one at a time. When a board has been fully connected, set VR8 and VR1 to their mid positions and switch on the power supply. Observe the triangular waveform on the oscilloscope — the frequency of oscillation should be about 7kHz.

Gradually reduce the setting of VR1 until the waveform begins to exhibit marked signs of asymmetry. At this point adjust the setting of VR8 with great care to restore the symmetry, this latter operation also being seen to cause an increase in the frequency.

Continue reducing the setting of VR1, adjusting VR8 as necessary, until VR1 is at its minimum setting and the output waveform is symmetrical.

At very low frequencies the setting of VR8 is extremely critical, too large a shift in either direction causing IC4 to saturate. If this happens, VR1 should be set to its mid position again and the various steps repeated.

With VR1 in its minimum position final setting of the very low frequency end of the range is accomplished by adjustment of VR2 in conjunction with VR8 as before. If IC4 saturates at or before minimum setting of VR1 the setting of VR2 will have to be increased.

Very low frequency instability can be a problem with this type of oscillator and although it can be made to operate at less than 1Hz with the component values given it is best to set the minimum operating frequency to about 5Hz.

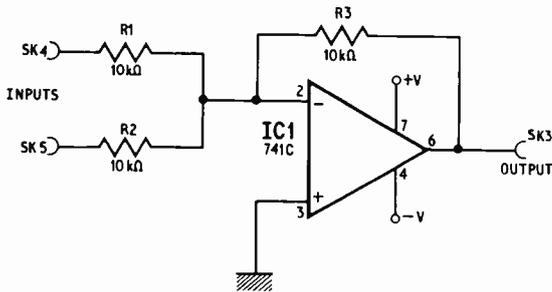


Fig. 3.9. Circuit diagram of voltage inverter

MATCHING THE OSCILLATORS

If the component values and tolerances specified have been adhered to, comparison of performance between both oscillators will show that the input voltage/frequency relationship is substantially similar, any differences in performance characteristic being due to tolerance variations in the components.

Extreme accuracy in the matching of oscillators is not necessary since linear response is involved.

INVERTER

Little need be said concerning the assembly of the voltage inverter which is essentially an inverting unity gain amplifier of the simplest kind. The circuit is shown in Fig. 3.9 while the recommended circuit board layout is shown in Fig. 3.10.

The completed board should be mounted directly over the A board furthest from the front panel.

USING THE MODULE

On completion of the whole module use the voltage inverter to investigate the effects of mixing triangular and square waves at varying frequencies.

The output may be fed to the high level input of most power amplifiers, but bear in mind that the output will be equal to the sum of the voltage swings at the inputs.

Additionally it is possible to carry out some simple experiments in frequency modulation by setting one of the oscillators to modulate the other. A low amplitude modulation at about 7Hz produces a true vibrato to the tone of the modulated oscillator whilst varying the amplitude and frequency of modulation can produce some strange, even bizarre effects.

Next month: the ramp generators and input amplifiers are described.

COMPONENTS . . .


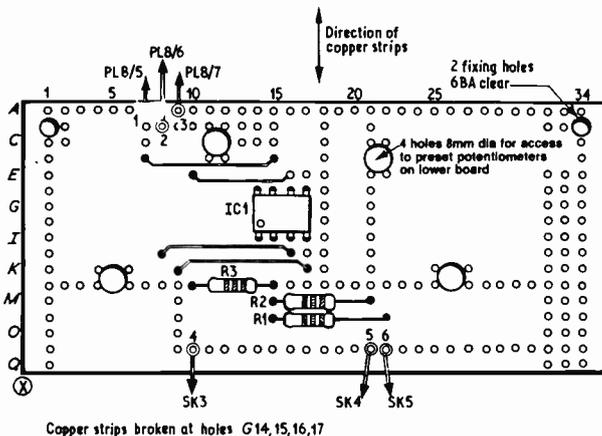
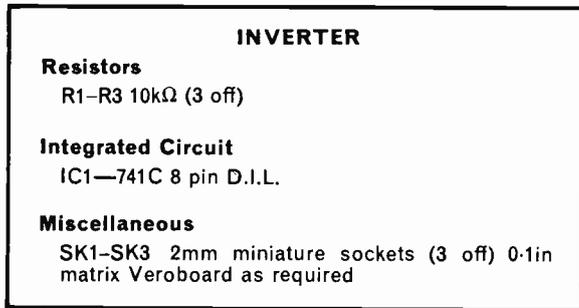


Fig. 3.10. Inverter component Board C layout and wiring

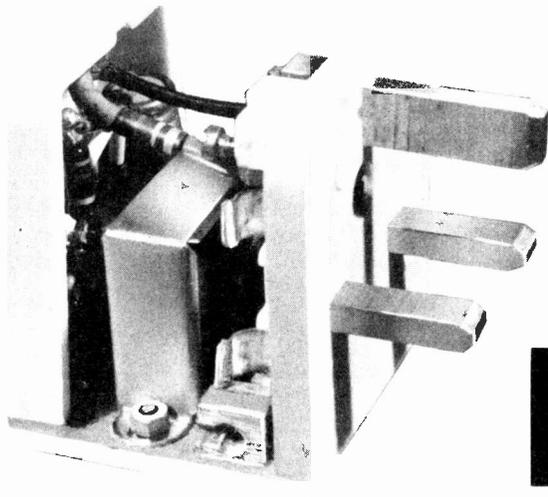

A Novel BATTERY ELIMINATOR

By J. S. GODDARD

THIS article describes a d.c. power supply unit with the unusual feature of being contained in a 13A flat pin mains plug. It will supply 60mA at 9V suitable for radio, cassette or record players.

UNIT ADVANTAGES

One of the disadvantages of conventional battery eliminators is that you are left with a box which must either be strung between plug and unit or replace the batteries in the battery compartment.

This design overcomes both problems. The lead from the mains plug goes directly to the unit and plugs in with a simple jack plug. The batteries of the unit are left in place but simply disconnected when the jack plug is attached. The batteries are reconnected when the plug is removed. The project becomes even easier if the unit has a socket for a battery eliminator.

CIRCUIT

The circuit diagram of the battery eliminator is given in Fig. 1 together with suitable battery cut-out circuit in cases where a socket is not available on the unit to be supplied.

The transformer has a 6-0-6V secondary with the centre tap unconnected. This feeds a four diode bridge rectifier, the output being smoothed by the reservoir capacitor C1 and R2. The Zener diode D5 provides a final 9V regulated output.

MODIFYING THE PLUG

The plug used for housing the circuit components is an Ever-Ready type which has to be modified. This is accomplished by cutting a $\frac{1}{8}$ in step at the bottom rear of the plug as in Fig. 2. A piece of $1\frac{1}{2}$ in \times $1\frac{1}{2}$ in \times $\frac{1}{4}$ in hardboard is cut to form a new base for the plug. This is Araldited into place ensuring that the ends of the plug are upright and parallel.

A $\frac{1}{8}$ in hole is drilled and countersunk in the upper half of the plug directly above the brass screw insert for the neon LP1.

For the d.c. leadout pair a $\frac{1}{4}$ in hole is drilled $\frac{1}{2}$ in up from the base at the centre rear of the plug.

ASSEMBLING THE COMPONENTS

The components may now be mounted in the expanded plug. First, the transformer is loosely held in position by two 6 B.A. screws.

The mains neon is now positioned and connected to the plug terminals together with the transformer primary windings.

With the capacitor and diodes in place the transformer is tightened down. The output lead is connected across the Zener diode after R2 has been added in series, in the positive line, as shown in the circuit diagram.

With all the components mounted in place care should be taken to see that none are touching the mains pins or their screws. If necessary more room can be made by discarding the screws on the back of the mains pins and soldering instead of clamping. Once all appears to be correct inside a cover has to be constructed for the plug.

COMPONENTS . . .

Resistors

- R1 220k Ω $\frac{1}{2}$ W carbon
- R2 82 Ω $\frac{1}{2}$ watt 10% carbon

Capacitor

- C1 400 μ F 10V elect.

Diodes

- D1-D4 1N4003 (4 off)
- D5 9.1V 400mW Zener

Transformer

- T1 Eagle miniature mains transformer 240V primary 6-0-6V secondary at 100mA.

Miscellaneous

- 13A fused mains plug (Ever Ready Type 7032), LP1 mains neon, $1\frac{1}{2}$ in \times $1\frac{1}{2}$ in \times $\frac{1}{4}$ in hardboard, $\frac{1}{4}$ in 6 B.A. countersunk screws (2 off), $\frac{1}{8}$ in self tapping (2 off), FS1 fuse to suit equipment. PL1 3.5mm jack plug.

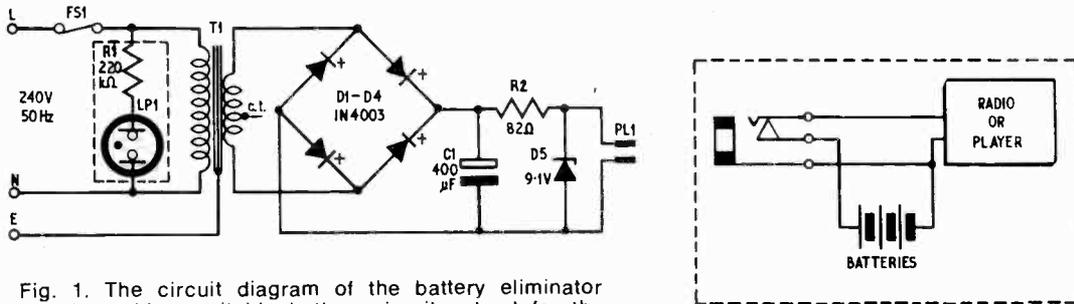


Fig. 1. The circuit diagram of the battery eliminator together with a suitable battery circuit cut-out for the equipment to be supplied


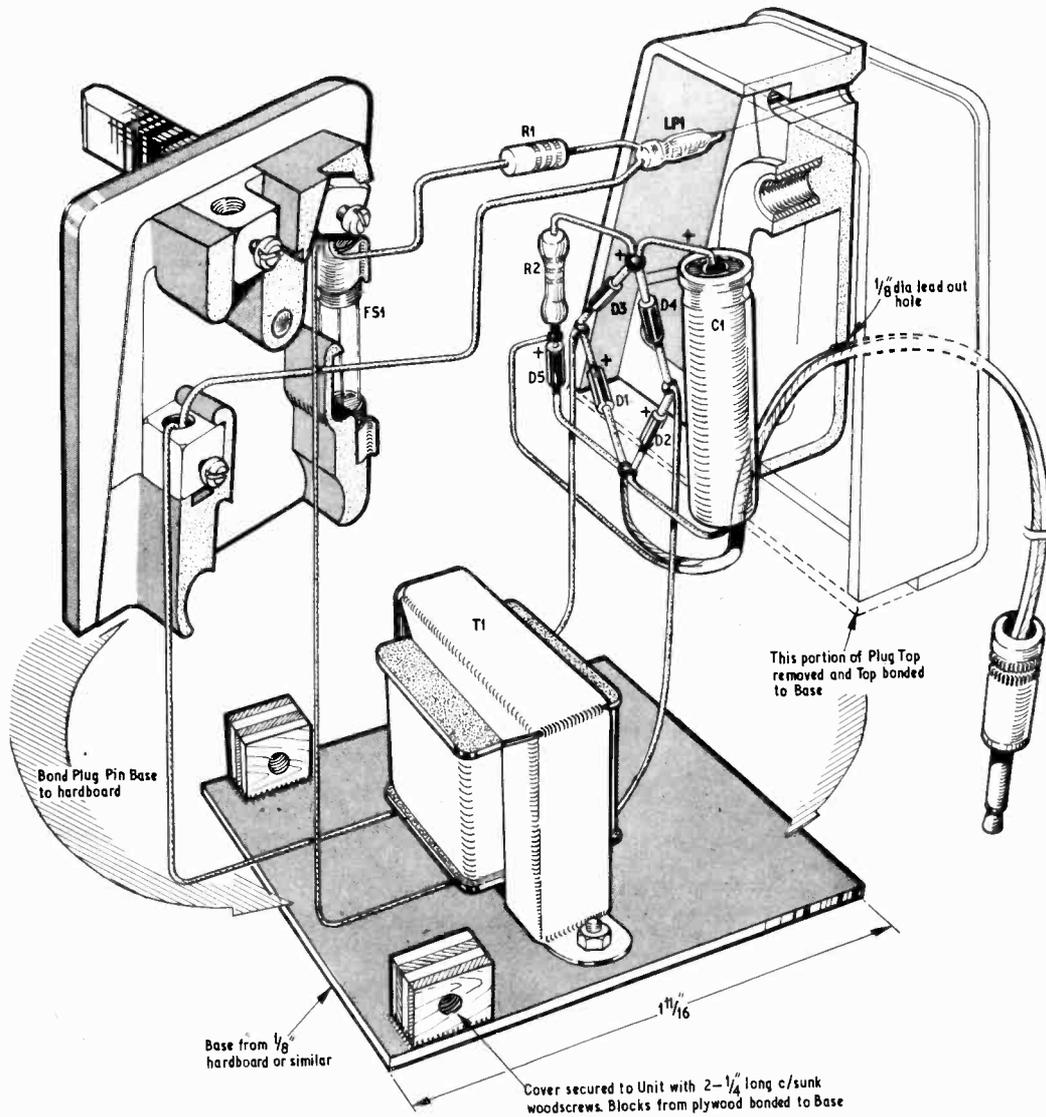


Fig. 2. Assembly and wiring details for the battery eliminator

look! electronics really mastered

... practical
... visual
... exciting!

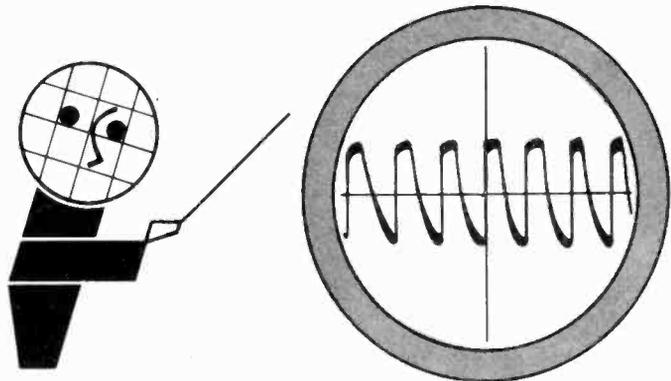no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

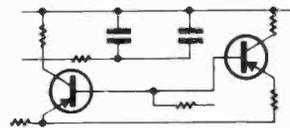2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW for BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: *we do not employ representatives*

NAME

BLOCK CAPS

ADDRESS

PLEASE EL43

special free gift also to all our students



BOOK REVIEWS

ELECTRONICS IN MUSIC

By F. C. Judd

Published by Neville Spearman

169 pages, 9in x 6in. Price £3.15

MR JUDD has condensed into this book the fruit of many years' experience in electronics. The six main chapter headings cover virtually every aspect of the subject ranging from the application of electronics in the production of music through a survey of electronic musical instruments, the production of synthetic sound and electronic music, the uses of the tape recorder in the field and, finally, a run-down on the parameters involved in the high fidelity reproduction of music.

The text throughout seems designed to guide the reader into this fascinating and ultra-technical subject without once getting bogged down in an excess of detail. Despite this tendency there is sufficient data presented to enable the home constructor to build and experiment with several interesting circuits. The book is well illustrated with sixteen pages of half tone plates and plenty of clear line diagrams and circuits. The author could have perhaps usefully expanded his treatment of the subjects of synthetic sound and electronic music in view of the current high level of interest although the shortfall in this respect does little to mar the overall presentation of the book which is excellent.

"Electronics in Music" is likely to be welcomed enthusiastically by technical and non-technical readers whose interest in the subject matter may be frustrated by the lack of definitive texts.

G.D.S.

TELEVISION INTERFERENCE MANUAL

By B. Priestley, B.Sc., G3JGO

Published by Radio Society of Great Britain


92 pages, 148mm x 210mm. Price 80p

TELEVISION interference from s.w. transmitters is something which many amateur radio enthusiasts find very difficult to eliminate. The Radio Society of Great Britain must therefore be congratulated for attempting to bring this problem to the notice of radio hams and for providing many hints on suppression which, if followed, could greatly reduce the annoyance of TV viewers near to a transmitter.

Television interference can arise from many sources and one of the main problems is tracking down the exact cause. Of course, a well-designed transmitter should include effective circuits for suppressing this unwanted output and transmitter design is included in the book. However, even the best transmitter can have a component failure and the book points out that a careful check on meter readings should be kept and any change in performance noted. R. F. injection into the mains and its suppression is also discussed.

This book has a spiral binding so that the pages lie flat on the bench. The manual may be obtained from RSGB Publications, 35 Doughty Street, London, WC1N 2AE, price 90p including postage.

S.R.L.

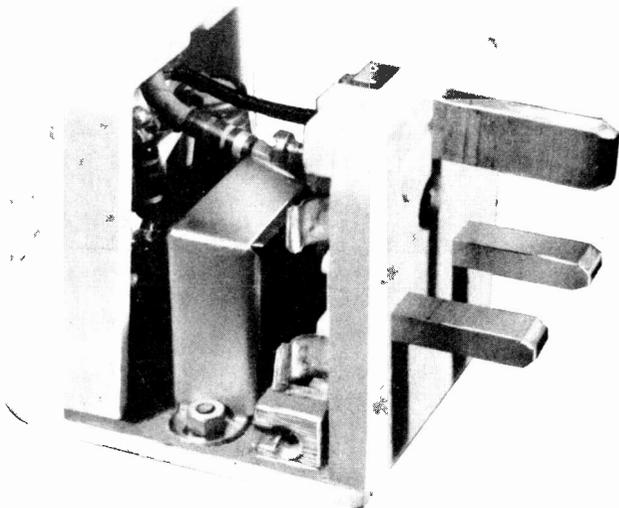

Good results can be obtained by using good quality card about $\frac{1}{8}$ in thick. The card is bent to fit around the top and two sides of the plug snugly. The inside of the card may be scored with a knife to make it bend more easily. With the card bent around the plug mark off, with a pencil, the exact dimensions. When cut to shape check to ensure a good fit, if necessary a former may be made to hold the card in the required shape.

The cover is held onto the plug by two self tapping screws. These screws tighten into $\frac{1}{8}$ in blocks of plywood about $\frac{1}{2}$ in square. The blocks must be drilled to accept the screws and glued in the bottom front of the plug as shown.

Now is the time to fill any gaps between plug and base. A plastic filler is used, which can be sanded smooth when dry. The cover and base may be painted to match the plug, sprayed paint gives good results on a suitable primer.

CONNECTING THE UNIT


Consideration now has to be given to the method of connecting the battery eliminator to the unit which it will power. A number of radio and cassette players on the market have facilities for battery eliminators, and in this case it is only necessary to obtain the correct plug. If your unit does not have facilities such as this, or you are unable to obtain the plug, the following will serve as an alternative.

A 3.5mm jack plug is connected to the eliminator's outlet lead with the matching socket in the unit. The jack plug is connected to the outlet lead wire with the positive line going to the tip. The socket may now be fitted to the unit, a suitable position must be found to ensure it will not interfere with any internal workings.

With the hole drilled and socket fitted the supply wiring must be adapted to cater for the new facility. The positive lead to the battery compartment must be broken and the jack socket connected in the break. The negative lead goes to the third contact on the socket as well as the battery compartment.

With the jack plugged into the socket the positive line from battery to unit is broken and connected instead to the outlet of the power supply.

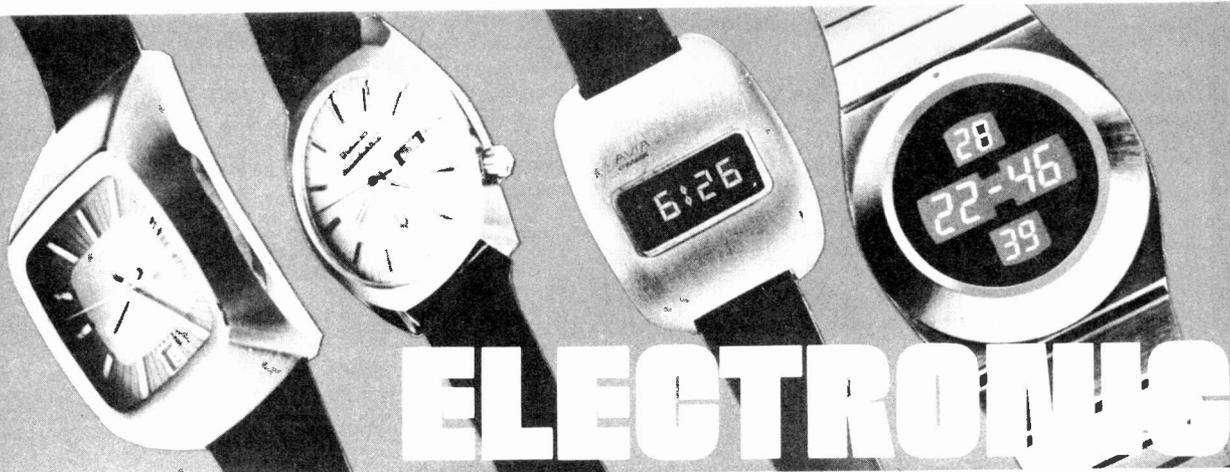The 400 μ F electrolytic capacitor may be difficult to obtain, but good results can still be obtained with a smaller one. ★



ELECTRONIC TIMEPIECES

By J. B. DANCE, M.Sc.

In this final part, quartz crystal controlled watches and clocks are examined together with various time displays.

QUARTZ TIMEPIECES

Quartz crystal piezo-electric oscillators are now well known for their great frequency stability. Although the piezo-electric effect was discovered by J. and P. Currie in 1880, it was not used for frequency control until 1921 by Cady. Natural quartz can be used, but synthetic quartz often gives a better performance.

CLOCKS

Various clocks using quartz crystal oscillators are available. For example, the General Time Company produce "Quartzmatic" clocks using 262,144Hz crystal oscillators with an integrated circuit to reduce the frequency to 64Hz. The Simplex Company produce quartz controlled master time centres for driving a number of clocks in an establishment with an accuracy of two seconds per month.

The Goly Company produce marine chronometers using a 12kHz oscillator which has a stability of 0.005 second per day at constant temperature or 0.1 second per day over the range 4 to 36°C: this clock employs about 29 transistors.

A quartz clock with a digital display is available from Girard-Perregaux; it is mains driven with stand-by battery power and provides an accuracy of 0.02 second per day. The Junghans 750 quartz movement is powered by a 1.5V battery which lasts a year.

QUARTZ CONTROLLED WATCHES

Quartz crystal controlled wrist-watches have been available since April 1971. Special CMOS (Complementary Metal Oxide Silicon) integrated circuits have been developed which consume a current only during the pulses and which are small enough to be fitted into a normal wrist-watch. In many cases a number of manufacturers have pooled their resources to produce quartz watch movements. The quartz

crystals used have to be specially aged so that they provide high accuracy at all times. They are normally sealed in a vacuum enclosure.

The first types of quartz wrist-watches to become available to the public employed the "Beta 21" movement developed by the Centre Electronique Horloger S.A. and marketed in various models under many brand names. The quartz crystal oscillator in this movement operates at 8,192Hz. An integrated circuit divides this frequency by a factor of 32 to produce a 256Hz signal. The current consumption averages about 16 μ A and the accuracy is about one minute per year.

CYBERNETIC WATCH

The Longines "Ultra-quartz" wrist-watch was first made available on 21st August, 1971. It is especially interesting because it does not contain any integrated circuits, but only a small printed circuit containing miniature electronic components.

The quartz resonator in this watch operates at 9,350Hz and a mechanical vibrator at 170Hz. The signals from the quartz oscillator are used to correct

The Girard-Perregaux quartz watch. The quartz crystal can be seen on the left-hand side, the integrated circuit near the top and the power cell on the bottom right-hand side



the mechanical vibrator 170 times per second. This correction is carried out by a relatively simple circuit employing only 14 transistors, 19 resistors and seven capacitors. The logical deductions made by this circuit are fed to the motor as correction signals. This watch is said to be the first cybernetic watch, since it employs a comparison circuit or "brain".

The vibrator motion is transformed into a rotary motion by means of a pawl system like that of Fig. 6. The toothed wheel rotates once per second. The centre second hand appears to rotate continuously without jumping. The accuracy is about one minute per year.

QUARTZ BALANCE WHEEL WATCH

The " μ -Quartz" or "TS Caliber" watch movement employs an electronically driven balance wheel having four magnets; the exact frequency of this balance wheel (about 4Hz) is controlled by a quartz crystal oscillator. The watch has been developed by B. Golay of Switzerland.

The hair spring fixed to the balance wheel has a special shape which results in the frequency of oscillation being somewhat dependent on the amplitude of movement; the frequency is slightly lower at small amplitudes and vice-versa. This effect is known as the isochronism defect.


The quartz oscillates at 32,768Hz. This frequency is divided down by part of a CMOS integrated circuit containing some 450 components. The strength of the pulse given to the balance wheel depends on the *phase* of its motion relative to the frequency divided signal from the quartz oscillator.

If the balance wheel is running too fast, the pulses to the coil which drives this wheel will be relatively weak, whereas if the wheel is running too slowly, they will be stronger. Thus the frequency of the balance wheel is stabilised at the value determined by the signals derived from the quartz oscillator.

If the isochronism defect amounts to 10 seconds per day for each degree of amplitude variation, the balance wheel frequency need only be adjusted to ± 100 seconds per day if an amplitude variation of ± 10 degrees is acceptable.

As in other quartz controlled watches, the regulation is effected by means of a trimmer capacitor which adjusts the exact frequency of the quartz oscillator. In this watch the capacitor is adjustable

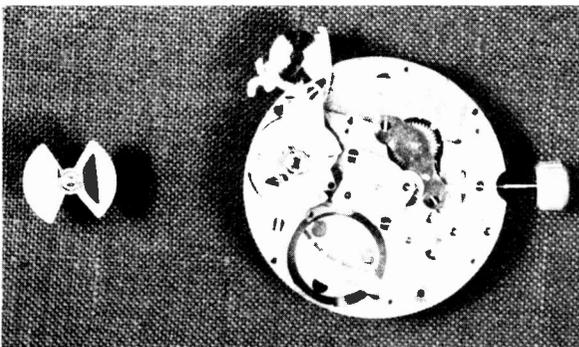The Golay μ -Quartz movement partially dismantled. The magnets can be seen fixed to the balance wheel in the lower part of the photograph, whilst the driving coil is seen above after it has been swung out from the movement. The quartz crystal, which has been removed, is fitted above this coil



in steps which correspond to a change of 0.25 second per day. The accuracy is about one minute per year.

QUARTZ WATCH WITH STEPPING MOTOR

The Girard-Perregaux "250" quartz watch employs a 32,768Hz quartz oscillator. The pulses from the latter are divided by an integrated circuit to produce 0.5Hz pulses. These operate a miniature stepping motor which causes the centre second hand to jump once per second.

QUARTZ WATCH KITS

The Motorola Company has a section which supplies kits of parts to large watch manufacturers. These kits each comprise a 32,768Hz NT cut quartz crystal, a CMOS integrated circuit and a miniature rotary stepping motor. The additional parts required are a power cell, a trimmer capacitor, a conventional watch dial and hands together with gearing to couple the motor to the hands.

The oscillator frequency chosen is a compromise between the size of the oscillator crystal and the current consumption of the integrated circuit. The use of a higher frequency would enable a smaller quartz crystal to be used, but the increased switching frequency results in a greater power consumption by the divider circuit.


The MC 6061 integrated circuit divides the oscillator frequency by a factor of 65,536 so as to produce 0.5Hz pulses which can drive the motor.

The integrated circuit contains 312 transistors in a six lead ceramic package, but consumes only about 4.5 μ A from a 1.3V cell or 5 μ A from a 1.5V cell. Motorola use ion implantation techniques to dope the semiconductor material used in their integrated circuits.

The 6mm diameter motor takes a mean current of about 7.2 μ A at 1.3V or 8.3 μ A at 1.5V. The 0.5Hz pulses from the integrated circuit have an amplitude of about 1V and a duration of about 31.25ms, successive pulses being of opposite polarity and separated by one second.

The motor rotates by 180 degrees at intervals of one second, all movements being in the same direction. It has a resistance of about 5 kilohms and contains about 50 metres of wire of a diameter about one-tenth of that of a human hair.

The three parts of the Motorola kit depicted inside an empty watch case. The quartz crystal is shown at the top, the integrated circuit on the left and the stepping motor on the lower right-hand side

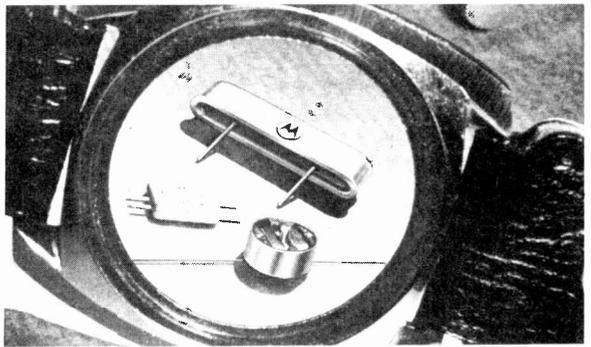

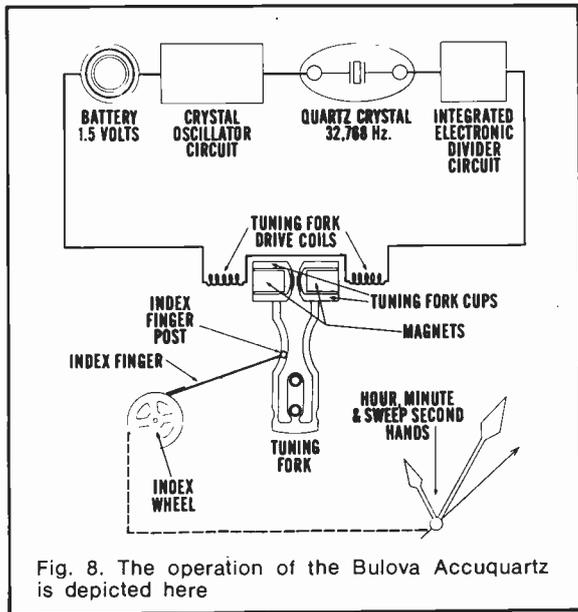


Fig. 8. The operation of the Bulova Accuquartz is depicted here

QUARTZ TUNING FORK WATCHES

The new Bulova "Accuquartz" watch is especially interesting because it contains a quartz oscillator which controls a tuning fork movement. This watch was introduced in the U.S.A. in December 1971 and became available in Europe towards the end of 1972 at prices from £115. It is much thinner than many other quartz models (including an earlier "Accuquartz" model which used the "Beta 21" movement). The new "Accuquartz" range for men and women display the day of the week and the date in addition to the time.

The "Accuquartz" crystal oscillates at 32,768Hz. This frequency is divided by an "Intersil" CMOS integrated circuit containing 126 transistors, etc. The tuning fork oscillates at 341 $\frac{1}{3}$ Hz, this being one-third of the frequency 1,024Hz. See Fig. 8.

The Bulova Accuquartz is shown in the foreground together with a much thicker Accuquartz model using the CHE movement



In this watch the tuning fork mechanism advances the gearing 341 $\frac{1}{3}$ times per second by the same type of mechanism as used in the Bulova "Accutron" range. Thus the centre second hand appears to move continuously instead of jumping once per second as in some types of watch.

The "Accuquartz" has an accuracy of about 1 to 2 seconds per week.

THE ASTROQUARTZ

The Junghans "Astroquartz" watch is said to be the smallest quartz watch being manufactured. It employs a 32,768Hz quartz oscillator, but the quartz crystal used is unusual in that it is in the shape of a tuning fork, the prongs of which vibrate like an ordinary tuning fork but at a much higher frequency.

As illustrated in Fig. 9, an integrated circuit acts as oscillator and frequency divider. The 15 cascaded binary stages divide the pulse rate by 2¹⁵ to produce one output pulse per second. The size of the integrated circuit is only 1.6 × 2.1mm.

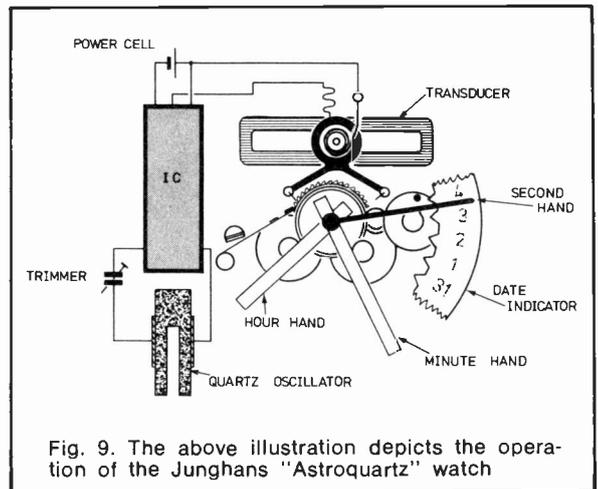


Fig. 9. The above illustration depicts the operation of the Junghans "Astroquartz" watch

The output pulses from this circuit drive an electro-magnetic transducer. The pulses are applied to the coil which turns in a strong magnetic field. The escapement fitted to the axis of this coil engages and turns a wheel with 60 teeth to which a centre second hand is fitted.

THE MEGAQUARTZ


The "Megaquartz" watch is probably the most accurate wrist-watch yet designed, although it is being produced only in small quantities. It has been designed by the Batelle Institute in collaboration with the Omega Watch Company. The accuracy is about 1 second per month.

The main feature of this watch is the use of a circular AT cut quartz crystal oscillating in a shearing mode at 2,359,296Hz—far higher than in any other design. An integrated circuit frequency divider is used.

Omega also offer a quartz watch which has an 8,192Hz oscillator. This frequency is divided by a factor of 32 to produce 256Hz pulses which drive an electro-magnetic motor. The accuracy is about 1 minute per year.

gspk

(sales)

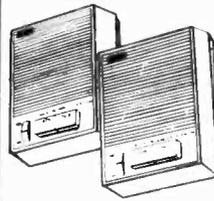

D1075 Wireless Intercom


The great merit of wireless intercoms is that separate connecting wires are not necessary providing the stations are on the same electrical mains circuit. Communication can be up to a distance of $\frac{1}{2}$ of a mile providing the power lines used are on the same side of the distribution transformer, and several stations can even be operated on the same circuit. Solid state model D1075 is fully transistorised and each unit incorporates a talk-listen button with locking bar; ON/OFF volume control and a pilot light. The lawn moulded cabinets can be desk located or wall mounted and are supplied already fitted with 1.25 metres of heavy duty lead. Operating Frequency: 160kHz. Speaker/Microphone: Dynamic 55mm. Power Output: 120mW. Size: 98 x 40 x 130mm. Printed Circuit: 3 transistors, 1 diode.

£11.60

SOLID STATE TACHOMETER

Functionally styled for under or over dashboard installation, this electronic tachometer fits all 4-cycle, 4-cylinder, or 2-cycle, 2-cylinder 12V vehicles. Negative or positive earth. Calibrated white on black 0-8,000 r.p.m. in 100 r.p.m. divisions, together with settable "danger" line, simple installation. 2 screws, 4 wires. 80mm (3in) dia. dial, 50mm deep. On adjustable angle bracket. Sealed black crackle finish.

£6.86

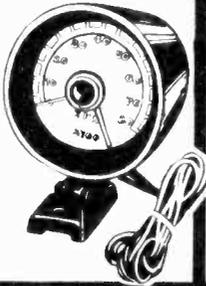

SPECIAL OFFER!

AUTO BURGLAR ALARM PLUS "POP-OUT" CIGARETTE LIGHTER

Designed for easy installation on any car (whether 6 or 12V) this device activates the horn when a theft is attempted of equipment or personal belongings. This neat unit reacts when the vehicle is disturbed or rocked and continues its warning for 15 sec. after tampering. The sensitivity of the device is adjustable and controlled by a separate ON/OFF panel which can be located wherever convenient. Supplied with connecting wires and screws in attractive bubble pack, containing installation instructions and diagrams. 150 x 65 x 20mm plus panel 65 x 45 x 20mm.

£2.10 FOR BOTH



FANTAVOX STEREO LOUDSPEAKER SYSTEM


These high quality speaker enclosures are made of tough black moulded plastic and have been designed for fitting on to almost any vehicle surface. The smart louvred fronts are silver trimmed and house heavy duty 5in (125mm) ceramic loudspeakers rated at 3/5 watts. 8 ohms impedance. Already wired with generous length connecting leads and supplied in packs of speaker pairs complete with fixing screws. Each cabinet measures 190 x 105 x 165mm.

1052 FADER CONTROL

Weight: 0.55 kg.

Neat, custom-made appearance slide fader control for balance of front and rear speaker volume. Simulated wood finish panel which can be quickly fitted below car dash. Supplied with generous connecting cable and fitting screws. Will suit 4, 8, 16 ohm installations. 100 x 38 x 30mm (including knob but excluding fitting bracket).

All for £4.70

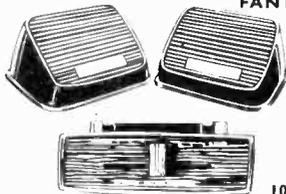

420ES MICROSCOPE

An extremely modestly priced yet efficient microscope capable of magnification up to 750 times with clear sharp images. This model is of the self-illuminating type and incorporates an easily rotatable four-position turret magnifying lens with rack and pinion focusing. The crackle black metal body houses the batteries for adjustable illumination. Packed in carton with built-in carrying handle and full notes for user. A sample slide also provided. 105mm at base; 180mm high. Weight: 0.40 kg.

£4.95



G5555 PROFESSIONAL STEREO HEADPHONE

Lightweight materials are skilfully used in the construction of this model in black crackle moulding and kid-soft leathercloth with contrasting bright metal. Each ear pad houses a highly efficient 60mm reproducer unit and features ear muffs removable for cleaning. 10-self-coiled lead plug fitted. Frequency Response: 20-20,000Hz. Impedance: 4-16 ohms. Sensitivity: 110dB. Power: 0.5W. Weight: 0.39kg.

£9.25




"SPRITE" LIGHTWEIGHT STEREO HEADPHONE

An outstanding achievement following lengthy development by one of the world's leading audio manufacturers, the T.T.C. "Sprite" offers the following specification: Extreme lightness (only 150 grammes) (5oz); Instant wearing adjustment with sliding ear-pieces and flexible headband; Highly efficient Mylar reproducer units; Removable, washable foam padded ear muffs; 3-metre lightweight lead with stereo plug fitted. Frequency Response: 30-13,000Hz. Sensitivity: 105dB. Power: 0.2W. Impedance: 4-16 ohms. Weight: 0.15kg.

£2.25



D1019 "Doorphone" with Metal Unit

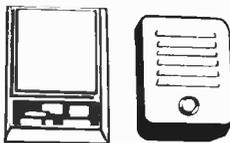

Three transistor solid state two-way intercom system with specially engineered weatherproof slave unit in heavy gauge metal. Sensible design features include rain protective speaker louvres, simple push-pull button, internal socket connecting lead and removable back plate for wall and door panel mounting. Master unit in high impact white moulding has complementary silver "pinhole" grille and silver/black panels with ON/OFF volume control and push-to-talk switch. 60mm dynamic speaker/microphones are used for both units. 120mW output. 9V internal battery operation. Master unit: 7.7 x 40 x 105mm. Slave unit: 70 x 32 x 90mm. Supplied with battery, lead and staples. £3.90

DF100 MICROPHONE

Bijou sized model in matt silver finish with machined capping to insert housing and supplied with unique pocket/lapel clip which also doubles as a desk support. Supplied with lavalier cord, 2 metre lead fitted 3.5mm moulded plug and packed in the latest style click-fast case manufactured from smart durable padded plastic.

Impedance: 200 ohms. Sensitivity: 82dB. Frequency: 100-9,000Hz. Size: 13mm dia. x 92mm.

£3.50



TI-C1000 MINI-METER

£2.70

This is the most compact and reliable multimeter on the market and features easy switch selection, 1,000 ohm/volt 2-jewel meter movement with zero and needle adjustment. Easy to read scale in two colours. Ranges: A.C. Voltage: 0-10V, 50V, 250V, 1,000V. D.C. Voltage: 0-10V, 50V, 250V, 1,000V. D.C. Current: 0-1-100mA. Resistance: 0-150K ohms.



Please fill in the coupon and send with 10p (refundable on ordering) for catalogue. ALL CALLERS WELCOME

To G.S.P.K. (Sales) Limited, Dept. P.E.,
Head Office, Hookstone Park, Harrogate, Yorkshire HG2 7BU.
Mon. to Fri. 9 a.m. - 5 p.m.

Name:
Address:

P.E.


constructing a digital multimeter

— exclusive **Wireless World** design in the April & May issues

See full construction details of the versatile multiple measurement meter which was first described in our March issue. Intended for both amateur and professional use, the design — based on integrated circuits — is arranged so that you can build either the whole instrument or just the particular measurement facilities you require. Measurements are shown in a "window" on a four digit numerical display.

Survey of the Compatibility of Audio Magnetic Tapes.

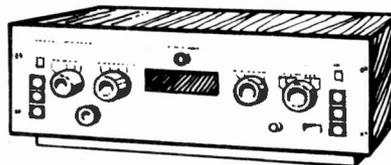
With the wide variety of tapes available, it is desirable to establish the compatibility of one type or brand against any other for a particular recording machine. Detailed tests have been made and the results interpreted to produce a table of interchangeable and compatible products.



The Wireless World digital multimeter will measure : voltage (199.9 millivolts to 199.9 volts, d.c. and a.c.) resistance (1.999k Ω to 1.999M Ω), capacitance (1999pF to 1.999 μ F), frequency (0 to 5MHz) and time intervals (20 microseconds minimum).

Wireless World

APRIL ISSUE On sale now 20p

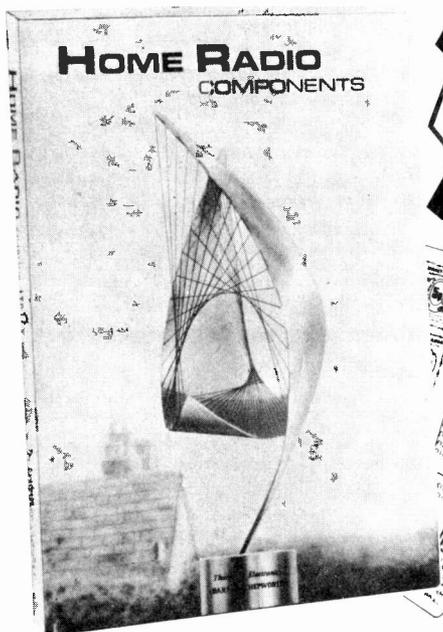

- 250 pages 11" x 8"
- 6,785 electronic components clearly listed and indexed
- 1,750 pictures
- 10 free Vouchers each worth 5p.
- Price list regularly updated
- Bookmark with useful list of technical abbreviations

The Catalogue you MUST have!

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Only 55p.
plus 20p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 75p.

Name _____ 

Address _____

HOME RADIO (Components) LTD. Regd. No. 912966 London
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

The price of 75p applies only to catalogues purchased by customers in the UK and to BFPO addresses.



(Right): the Avia watch which employs a liquid crystal display. This is expected to be available in the U.K. at about £135 soon

(Left): the Swissonic 2000 watch. This displays the date, the hours, minutes and seconds continuously by means of a liquid crystal system



DIGITAL WATCHES

Digital watches which employ no moving parts have just begun to appear on the market. They employ quartz oscillators and provide an accuracy of about one minute per year.

Two forms of display have been employed, namely electroluminescent diodes which provide a red display and liquid crystal displays.

ELECTROLUMINESCENT WATCHES

Watches employing gallium arsenide-phosphide electroluminescent diodes provide a display which shows the time in red digits. Unfortunately the display diodes require so much current that it is not possible for the time to be continuously displayed if the power cells are to have a reasonable life. A button on the watch must therefore be pressed each time the user wishes to read the time. The cell life is dependent on the number of times the time is displayed. The display may have to be shaded with the hand if the ambient light level is high.

The "Pulsar" watch manufactured by the Hamilton Company employs light emitting diodes. The brightness of the display is automatically adjusted to suit ambient lighting levels, although it requires shading from direct sunlight when the display is being read.

Each time the button is pressed, the hours and minutes are displayed for 1.25 seconds, but if the button is held down, the seconds are displayed for as long as it is depressed.

The watch employs a 32,768Hz oscillator and a CMOS integrated circuit containing over 1,200 transistors. It is powered by two silver oxide cells which have a life of over one year under normal use (about 25 time readouts per day).

A slight variation of this watch is offered by the Omega Company as their "Time Computer".

LIQUID CRYSTAL DISPLAYS

The other form of digital display used in watches employs liquid crystals. This type of display requires very little power, since it does not emit light. The liquid crystals simply reflect a different proportion of the incident light in regions where an electric field is applied to them. Thus the display cannot be

viewed in the dark. A moderately high ambient light intensity is desirable.

The thickness of the liquid crystal material may be about 0.5mm. The special nematic material is placed between two electrodes like a capacitor, but the electrode nearest the face of the watch must be transparent.

In the absence of any field, the liquid is perfectly clear and transparent, any incident light falling on it being absorbed by a black background. When an electric field is applied by suitably shaped electrodes in certain regions (which are in the shape of the digit to be displayed), the liquid becomes opalescent as the crystals come into mutual alignment. They reflect the incident light back from these regions to the observer.


Although watches using liquid crystal displays have the advantage over those using luminescent diode displays in that the digits can be made visible at all times, the life of the present liquid crystal systems seems somewhat doubtful. Even when an alternating voltage is applied, some degradation of the material may occur so that the display gradually becomes less clear. The life should be considerably over one year, but it is too early to estimate it accurately. At least one manufacturer feels that liquid crystals may have an indefinite life if contamination is avoided. The price of replacement units should fall rapidly during the next few years.

THE AVIA WATCH

One watch with a liquid crystal display is marketed by Avia-S.G.T., the liquid crystal system for this watch being produced by the Optel Corporation of the U.S.A. The hours and minutes are continuously displayed, but the seconds are shown by means of two flashing points appearing between the hours and the minutes digits.

The quartz oscillator operates at 32,768Hz. This frequency is divided by a factor of 512 and the 64Hz output operates counters. The latter control the decoders which feed the display.

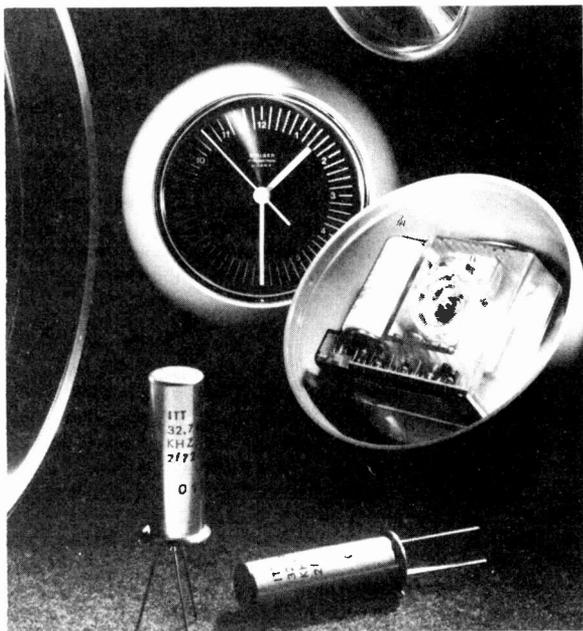The 1.5V power cell has a life of 14 months. A circuit is employed to convert the 1.5V from the cell to the 15V required for the decoder-display operation.



The Staiger 2000 quartz crystal controlled clocks. The ITT crystals used are shown at the front


A DETAILED DISPLAY

Another liquid crystal watch has been developed by Texas Instruments, Ebauches S.A. and Longines. The eight character display provides a continuous readout of the day of the month, hours, minutes and seconds. The accuracy is about 1 minute per year. The watch contains two integrated circuits containing about 700 transistors and is powered by two 1.35V mercury cells.

The hour display can be set by an internal switch to provide either a 12 hour or a 24 hour cycle. The indicated time is set by four micro-switches on the back of the watch which alter the seconds, minutes, hours and date respectively.

Another watch with a liquid crystal display has been produced by the Seiko Company; it displays hours, minutes and seconds.

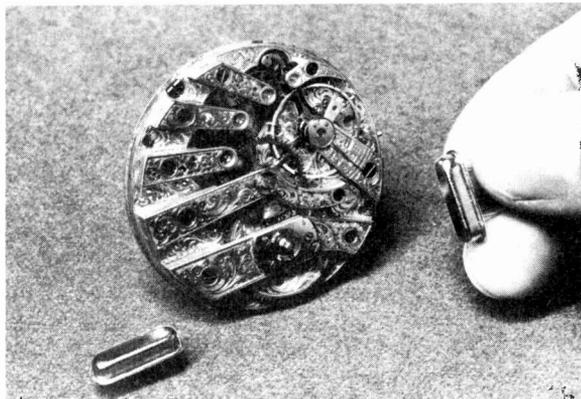A Geneva lever movement (about 100 years old) from the Science Museum being compared with an ITT quartz crystal designed for use in a watch



CLOCKS USING LIQUID CRYSTALS

A limited number of clocks with liquid crystal digital displays are available, for example, from the Seiko Company. An impressive digital alarm clock (type S1736) has been constructed on a single chip by American Microsystems; it is interfaced with their liquid crystal readout.

ATOMIC CLOCK

In a totally different sphere it may be mentioned that the standard of time is now based on the frequency of radiation emitted between two hyperfine levels of the caesium-133 atom. The second amounts to 9,192,631,770 cycles of this radiation. This definition provides a more accurate measure of this unit than the motion of the earth.

Ebauches S.A. have made precision time centres using caesium atomic clocks which have an error of less than one microsecond per day (corresponding to one second in about three thousand years!).

POWER CELLS

The cells used to drive electronic watches pose many manufacturing problems. Three of the main manufacturers are Union Carbide, Leclanche and, in England, Mallory.

A new area has recently been opened by Mallory at Crawley for the manufacture of special mercury button cells used in watches. Such cells must give satisfactory service for at least one year after a variable period of storage before sale.

Extreme care must be taken to prevent contamination of the materials used in cell manufacture. All air is filtered before it enters the watch cell manufacturing area at Crawley to prevent dust from being sealed in the power cells. Great care must be taken to prevent the possibility of internal leakage of current.

The electrolyte used in watch cells is chosen for the lowest practical seepage rate, since if it escaped from a cell it would probably damage the delicate watch mechanism.

In conclusion it may be mentioned that the tweezers used to fit new cells into watches should be made of a plastic material, since metal tweezers can easily short the cell. Care should be taken to fit new cells in the correct way so that they provide the circuits with a voltage of the correct polarity.

CONCLUSION

We are in the midst of a revolution in watch design. Although no manufacturer has really broken through the price barrier with a moderately priced quartz controlled watch, it may not be too long before one company does so and the "quartz war" will have begun. The developments in the last few years have been very rapid and it is expected that many of the estimated 300 million watches per annum required by 1980 will be electronic ones.

The traditional place of watch making, Switzerland, has played a large part in the development of electronic watches, but the U.S.A. has initiated much of the work.

The normal skills of the watchmaker will be required to attend to watches employing moving parts, but if digital watches become common, the watch repairer may have to have a very elementary knowledge of electronic engineering with micro-miniature equipment.



SPACE BUDGET

The United States space agency will have more money to spend this year, 74 million dollars in fact. A total of 3,136 million dollars is set aside for space matters. This amount will cover a number of NASA projects, for example two new projects as well as the programme for space stations and shuttles.

The two new projects are a new kind of satellite for geodesy known as a Terrestrial Reference Satellite, and an advanced version of the *Nimbus* weather satellite to monitor pollution.

The reference satellite, due for launch in 1976, will use laser beams for the measurement of distances between locations on different continents. The accuracy that can be achieved is of the order of a few inches so that small changes of movement of land masses will be detected.

The new *Nimbus* satellites will monitor both air and ocean pollution. The programme is for the launch of two satellites, one in 1974 and the other in 1976.

The current major projects will continue to be developed, but there will be a phasing out of communications satellite interests. This is because the space agency considers that the viability of these programmes has been proved and the time is now ripe for commercial responsibility for this activity.

The Science Foundation will increase their programme of investigations and some major projects involve visual and radio astronomy. Some 10 million dollars will go to the rail mounted mobile arrays of aerials in New Mexico for the large scale study of distant sources and the detection of signals from any civilisation that may exist in other parts of the Universe.

The visual telescope under construction at the Cerro Tololo inter-American Observatory in Chile, will be given 2.6 million dollars for the completion of the work on what will be the largest optical telescope in the southern hemisphere. The diameter of the mirror is 158 inches and the site offers spectacular advantages over other places for useful viewing time.

LUNOKHOD 2

The Russian moon vehicle, *Lunokhod 2*, which landed on the Moon in January has a special set of programmes. It was landed some 175km from the landing site of *Apollo 17*. The data obtained from the two sources should be complementary.

Landed in the Sea of Serenity, the *Lunokhod 2* task is to examine the boundary area where older



BY FRANK W. HYDE

rocks may be found. At the boundary area of the highland regions, from which the anorthites rise up, the floor of the mare is covered with basalt type lava.

Other experiments will measure and observe the Zodiacal light near the Sun, observe the Milky Way and the centre of the Galaxy with a space photometer. It is hoped also to decide whether there are traces of cosmic dust in the Lunar atmosphere. The possibilities of studying the Universe by optical means from stations on the moon is another experiment which the Soviet team are known to be considering.

The vehicle is also carrying a French laser reflector for measuring the Earth-Moon distance.

The *Lunokhod*, which is of a similar design to the previous vehicle, carries on its outside an orientation device, a lunar surface photometer, soil analysis experiment, a fixed television camera, a steerable television camera, the space photometer, a solar battery, a magnetometer, a photo receiver and aerials which include a corner reflector and a high gain system.

MOON GRAVITY

Analysis of the gravitational variations of the moon recorded by the command module of *Apollo 15* has yielded data about mascons, and the lunar orbiter added to this data when being precisely tracked.

This problem, to which selenologists have devoted considerable time and study, can now be set up as a model. The model now suggested agrees well with the idea that the mascon of Mare Serenitatis is a thin body with well defined boundaries. The previous speculations on

this theme have been borne out for Mare Nectaris also.

So far as Serenitatis is concerned the model fits the surface features extremely well. At the moment the data gives support to the volcanic hypothesis.

ORBITING WORKSHOP

As the launch date for the *Skylab*, the first orbiting space station, draws near it may be useful to describe the project and the sequence of events which will be the step in space that many have waited for almost impatiently.

The first crew will be an all Navy one and Charles Conrad, veteran of *Apollo 12*, is the only member of the team who has had astronaut experience. The other two men are J. P. Kerwen, a doctor, and P. J. Weitz, an aeronautical engineer.

Skylab will go into a 270-mile orbit. The sequence is to be the launch of the skylab unit unmanned into the prescribed orbit, the next day, May Day, the launch of the command module with the crew to the calculated rendezvous. When linked up the total length of the units will be 118ft. The diameter will be 22ft at the workshop section.

The arrangement of the airlock and docking sections allow normal joining of the command vehicle to the end of the whole unit. There is also a second docking point on the side of the docking module which could be used for a second command module to attach itself or for rescue purposes.

When the space station is launched the telescope covers the docking section. On attaining its correct location in orbit the telescope will swing to the side and the solar power paddles will open. The ports for docking will then be uncovered.

LIFE SUPPORT SYSTEMS

The station main body is 48ft by 22ft and there is an intermediate section next in the sequence which is 17ft long and is an airlock section. Here all the power control and distribution systems are located.

The air conditioning system, the life support system together with communications control and data management are also arranged there. There is room for two fully suited astronauts with personal life support systems in the section. From here the crew can pass to the docking module to work outside the vehicle or to pass to and from the command module.

The whole assembly with the launcher, a *Saturn 5* rocket, will stand 334 feet high at take off. The combined weight at the time will be 3,110 tons.



Hi-Fi Tape Link

By P. S. EWER

LAST month the circuit of the Tape Link was described in detail. In this the final part, the construction of the Tape Link, the fitting of the heads and the setting up procedure will be described.

TWO ASSEMBLIES

The Tape Link is made up of two assemblies (the amplifier and the power supply) in order to keep the mains transformer away from hum sensitive circuits and enabling the power supply to be positioned where it induces the minimum hum in the replay head.

The folding of the metal should present no problems to a handyman equipped with a vice. Cutting the metal to size is not quite so easy and is best done with a guillotine and a fly press for the cut out parts. Constructors may find it convenient to purchase the metal cut to size from a sheet metal shop.

POWER SUPPLY CONSTRUCTION

Dealing first with the power supply, drill the chassis and bend up as indicated in the photograph.

Next, affix the mains transformer using 4BA \times $\frac{1}{2}$ in screws and nuts. Do not tighten as they will have to be undone again when the power unit is finally mounted in the case. A tag strip carrying the rectifier diodes should now be assembled and bolted to the chassis.

Wiring between this and the mains transformer is best done at this stage as the tag strip will be difficult to get at once the smoothing capacitors are in place. These and the fuseholder can now be put into position and the wiring completed.

The power lead-out wires and the mains lead are secured by a plastic cable clip bolted down to the

mains transformer. Having completed the power supply it can now be tested.

With mains applied and no load imposed upon the outputs, the supplies should read 56 volts and 28 volts respectively. Provided that the voltages measured are within a couple of volts either way and that the mains transformer and capacitors do not get hot after a few minutes' operation, all should be well.

AMPLIFIER CHASSIS

Mark out the front panel to suit components (see Fig. 7). Drill all the holes starting first with an $\frac{1}{8}$ in drill. Next, open out the holes for the record indicator lamp, the switches and potentiometers with the appropriate drill.

The DIN sockets are mounted beneath the panel and the $\frac{1}{2}$ in hole required to allow entry of the plugs is most neatly cut with a chassis punch, e.g. a "Q-max cutter". The cut outs for the meters are made by drilling all round just inside the edge with a small drill, pushing out the centre and then truing up to the marked line with a file.

A similar technique should be used for the meter switch cut-out. Drill two holes side by side and open up to the required size with a needle file. Finally countersink all the screw holes.

The strap for mounting the meters, and the U-channel complete the metal work. To make the folding easier, the front panel fixing flanges should be bent over first. The sheet can then be bent up to complete the chassis. Once again, the use of a chassis punch is recommended for the larger holes (see Fig. 4).

The front panel can be finished in any way desired. One method which gives a pleasing appearance is to

satin finish it by stroking lengthwise with a wire brush such as is supplied for cleaning suede shoes. This results in a series of parallel scratches. The panel is then cleaned with a rag soaked in methylated spirit to remove loose material and grease.

Letraset may be used to label the panel, finally protecting the finish with two coats of lacquer.

After fixing the front panel to the chassis the B9A valve holders and the stand-off spacers are mounted and the components assembled to the front panel. The slider switch used by the author for the BIAS/VU selector was supplied with its mounting holes tapped at 8BA.

These were drilled out and retapped at 6BA. However if 8BA screws are used, allowance must be made for this in the front panel drilling.

COIL WINDING

Because many readers find it difficult to obtain specified coils, the author wishes to point out that virtually any 14mm coil is suitable for L1 and L101. Most catalogues specify the number of turns per millihenry and because inductance is proportional to the square of the number of turns, twice this number will give the number of turns required for 4mH. Some easily available pot cores and their turns per millihenry are given in Table 1.

Using 34 s.w.g. enamelled copper wire, wind the required number of turns onto the bobbin. On completion the winding should be secured with a layer of adhesive tape (not Sellotape).

Before assembling the two halves of the pot core, slightly rub the mating surfaces with a sheet of paper to remove any dust which could alter the inductance of the completed coil. The lead wires should be brought out separately through adjacent slots at 90 degrees.

Photograph showing construction of the power supply for the Tape Link. The switch and indicator neon are mounted near the mains input. Positioning of the power supply module within the finished tape deck is best found by trial and error being that which gives minimum hum.

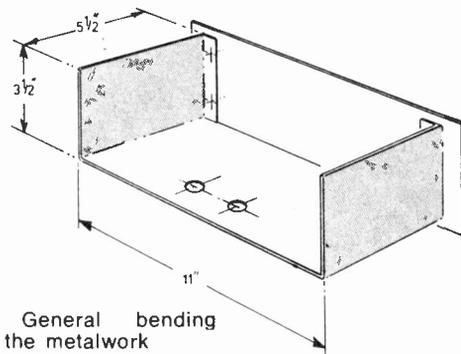
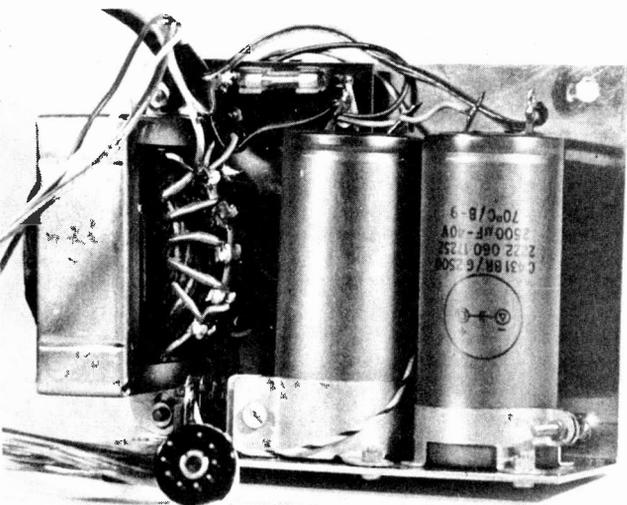


Fig. 4. General bending details of the metalwork


Table 1: ALTERNATIVE POT CORES FOR L1 AND L101

Type	Turns/mH	Turns required for 4mH
LA 2503	52	104
T26/2100R	47.5	95
FX 1636	34.8	70
FX 1011	24.3	49
FX 2236	32	64

Table 2: ALTERNATIVE POT CORES FOR BIAS AND ERASE OSCILLATOR T2

Type	Turns/mH	Turns required	
		Primary	Secondary
LA 2301	53.8	5 + 5	80
LA 2105	54.7	6 + 6	96
LA 2517	42	5 + 5	80
N22/250A	40	5 + 5	80

Fig. 5. Method of winding the primary of the bias and erase oscillator coil


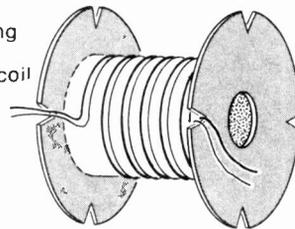


BIAS AND ERASE OSCILLATOR TRANSFORMER

Again the pot core used for this transformer is by no means critical. A 25mm type was used in the prototype but any high frequency 18mm type will do just as well provided the inductance is that specified (see Table 2 above).

Measure off two 20in lengths of 21 s.w.g. wire and twist them lightly together. Allowing a few inches for leadout wires, begin winding the required number of primary turns making sure that the first turn of one half of the primary lies adjacent to the first of the other half and so on (see Fig. 5). After the required turns have been wound the windings should be secured with adhesive tape.

The secondary should then be wound using 30 s.w.g. wire starting in the same place and winding in the same direction. Cover this layer with one layer of tape. Then assemble the pot core with the same precautions as for the previous coil.

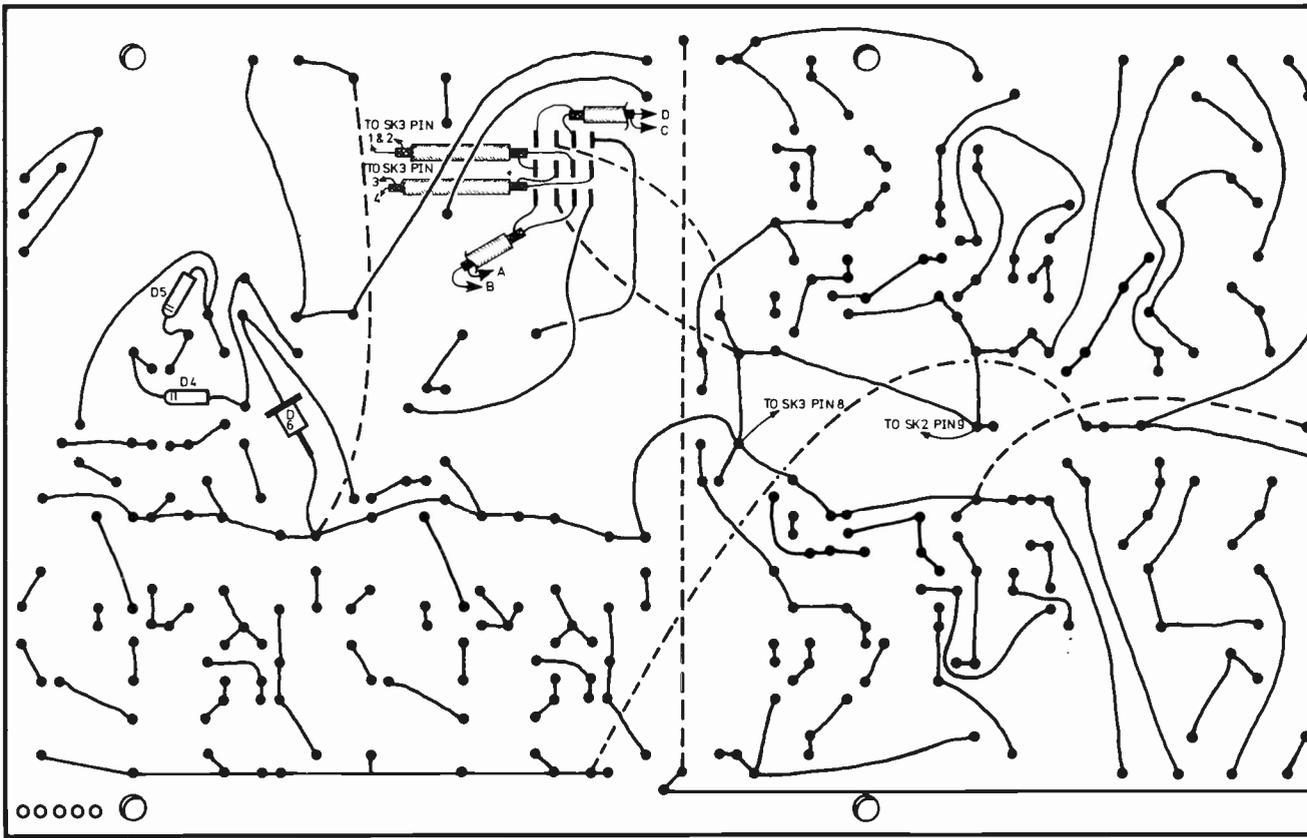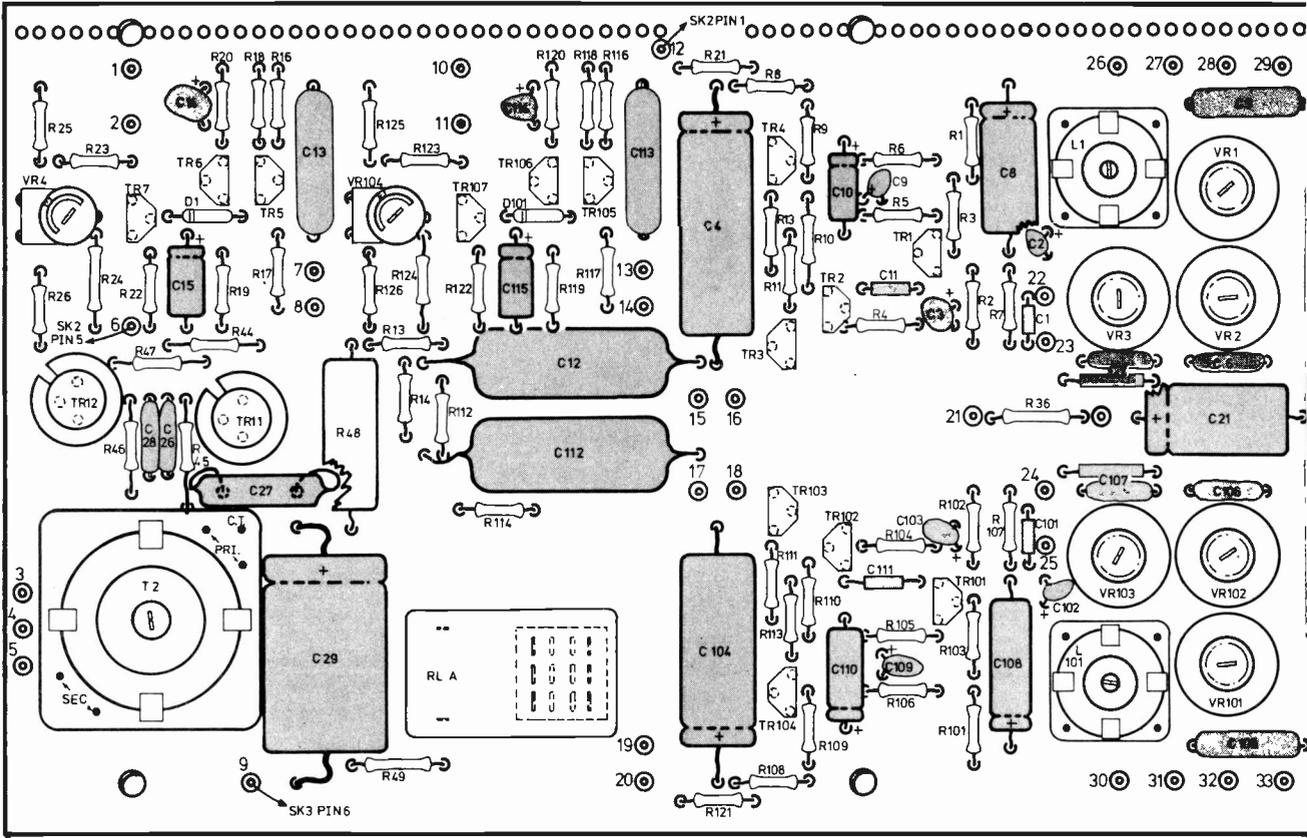


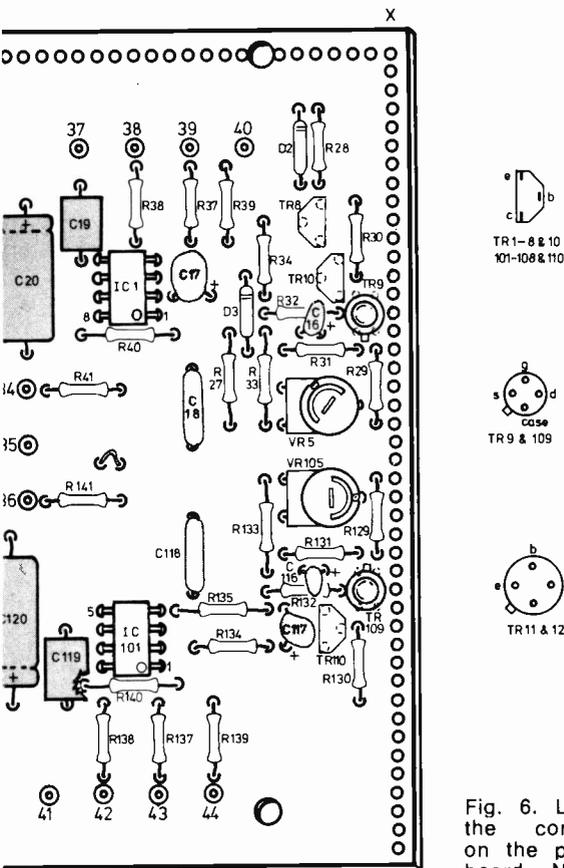


Fig. 6. Layout of the components on the perforated board. Note that there are some components under the board. C27 should be mounted away from board to avoid heat

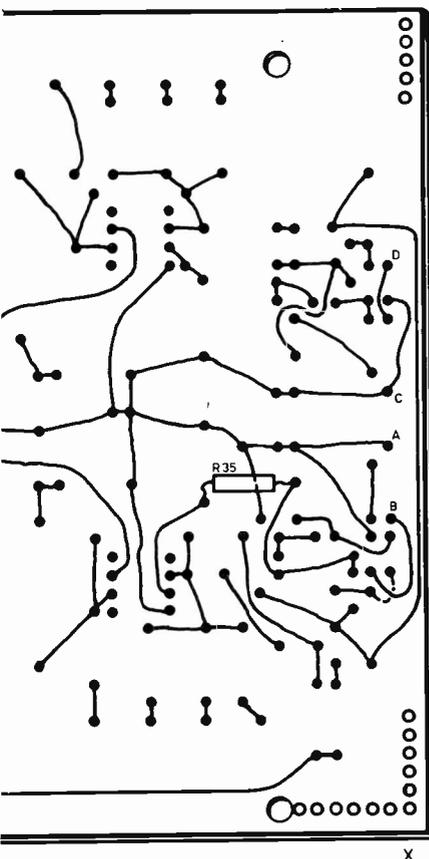

The primary windings must now be identified with some form of continuity tester such as a bulb and battery. After scraping the enamel from the four primary wires select one wire and call this the start.

Next find the other end of this wire with the continuity tester. If the method of winding shown is followed then the starts of both primary halves will be at the top of the coil and the other ends at the bottom. The end of the identified wire should then be soldered to the start of the remaining wire, this becoming the centre tap. The remaining wire then becomes the other end of the total primary.

CIRCUIT BOARD

The amplifier is constructed on perforated board which accommodates all the components with the exception of the relay for which a cut-out must be made (Fig. 6). The holes will also have to be opened out for some of the pots and for the fixing screws.

The wiring should proceed logically from one end of the board to the other inserting Veropins where the flying leads are to be soldered to the board. The oscillator tuning capacitor is mounted up in the air on Veropins to keep it away from the hot components near it.

TR11 and TR12 are fitted with clip-on heat sinks (TO5 can). There are four components mounted underneath the board which must not be forgotten.

CONSTRUCTION

Upon completion thoroughly check the board wiring. The connections from the underside of the board to the B9A sockets are then wired, allowing sufficient slack to enable the board to be tilted up through 90 degrees to facilitate servicing should it be required.

The board is next screwed into position and the wiring completed. To facilitate identification, the use of an assortment of colours for the connecting wires is suggested, and screened leads of low capacity *must* be used where indicated (see Fig. 7).

For ease of assembly it is suggested that the switch wafers nearest to the metalwork are wired first. Note the screen between the wafers and the spacers required to give good isolation between the two sections. In the prototype three-pole three-way wafers were used for S1 but the easier to obtain four-pole three-way wafers are perfectly suitable.

Prevention of earth loops is essential with this equipment and the constructor should note that there is only one connection between the chassis and amplifier earth.

At this stage the wiring on the front panel and the chassis should be completed as in Fig. 7.

TESTING

After having thoroughly checked the wiring (mistakes can be expensive) the power supply is plugged into the appropriate socket on the amplifier and mains applied. Providing that there is now no obvious indication of a fault, e.g. smoke, it can be assumed that there are no serious errors.

Measure the supply voltages with a multimeter. These should be 55 volts and 27 to 28 volts approximately. It is then prudent to go around the circuit

Table 3: APPROXIMATE VOLTAGE SETTINGS

Junction of R1 and R2	17.3
TR1 emitter	18.0
TR1 collector	0.7
Junction of R1 and R21	54.0
TR2 collector	25.3
TR2 base	0.7
Junction of R11 and R13	27.0
TR4 base	28.7
TR4 emitter	28.0
TR3 base	25.3
TR3 emitter	26.0
TR5 base	7.7
TR5 emitter	7.0
TR5 collector	18.3
TR6 base	18.3
TR6 emitter	19.0
TR6 collector	7.0
TR7 emitter	6.0
TR7 collector	26.0
VR4 wiper (dependent on setting)	6.0
Junction of R25 and VR4	8.0
Junction of R26 and VR4	4.0
TR8 base	28.0
TR8 emitter	28.7
TR8 collector	20.0
TR10 base	19.4
TR10 collector (dependent on VR4)	12.0
Terminal 6 IC1 (dependent on VR5)	12.0

checking voltages in accordance with Table 3. These are the design figures obtained by calculation and, generally speaking, provided that correlation within plus or minus 20 per cent is obtained all should be well.

When these checks have been made rotate VR4 and VR104 fully clockwise. The meters should now show a reading.

Disconnect the mains and temporarily short pins 5 and 6 of SK3 together. Set the meter switch to BIAS and the function switch to STEREO. Then reconnect the mains. The record indicator light should come on and the meter show an indication which is adjustable by means of the bias control. Failure of the meter to read suggests an oscillator fault and the power should be switched off immediately to prevent damage. Remove the temporary link.

TAPE TRANSPORT

With the old heads and/or electronics stripped out, the new heads have to be fitted to the base plates. Two methods of accomplishing this for the record/replay head are depicted in Fig. 8. It is essential that the tracks interleave correctly and the baseplate may need to be packed up or filed down accordingly.

When correctly positioned, the upper edge of the top track lies just below the edge of the tape (about 0.15mm). With regard to the Collaro deck the slot in the baseplate had to be widened with a file and the

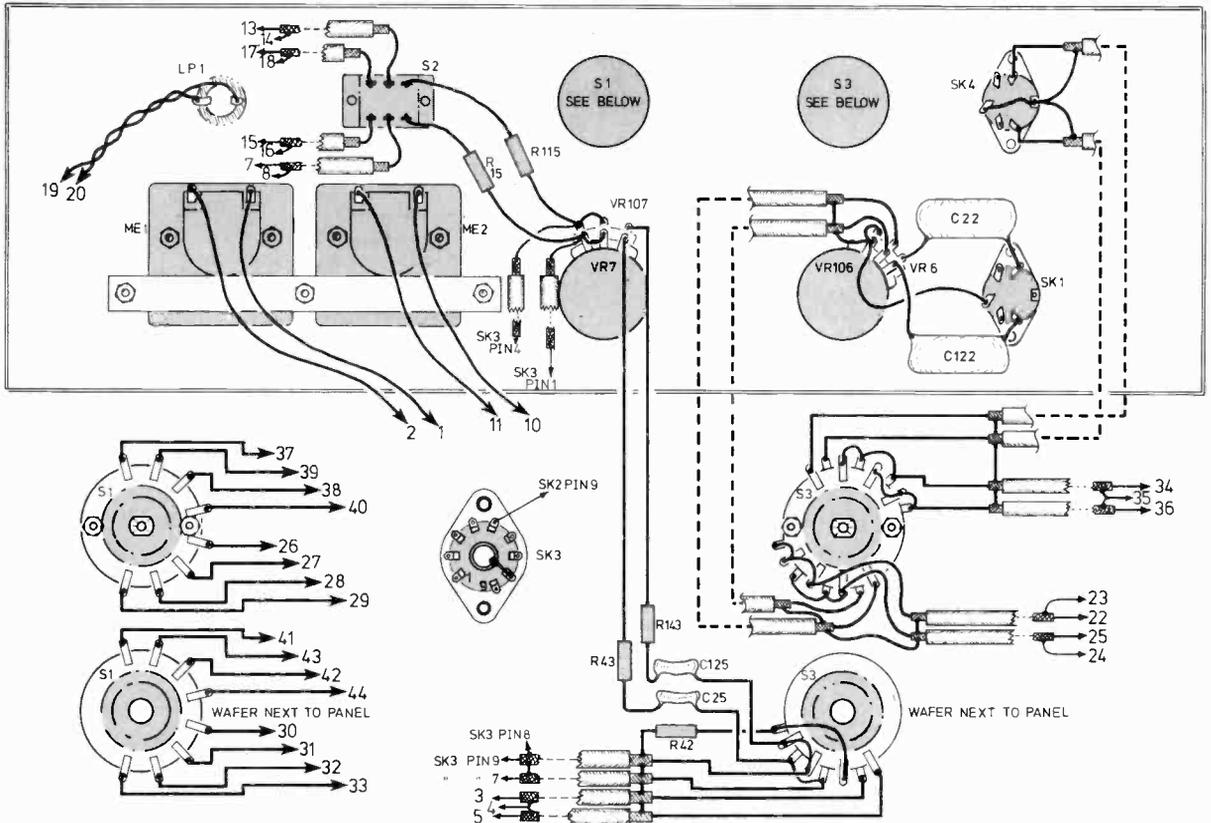


Fig. 7. Interwiring diagram showing the connections between the board and the other components. The numbers indicate the terminal pins on Fig. 6

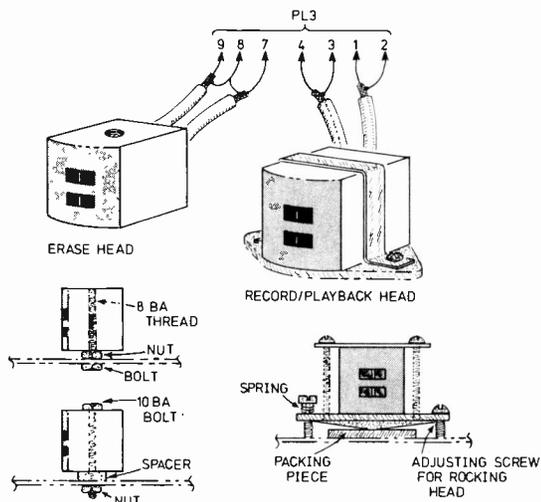


Fig. 8. Methods of fitting the new heads of the tape deck

baseplate packed up to raise the head. The dimensions of the strap are given and it was screwed to the baseplate with self-tapping screws.

The erase head has a single hole through it to clear 10BA, and this is the best means of securing it. The azimuth of the erase head gap is not critical and therefore a rocking plate is not required. On the author's deck this hole was tapped at 8BA and the head then secured directly to the head mounting plate stood-off by an 8BA nut drilled out to clear the thread. The top of the erase head upper track should extend to the edge of the tape.

PRESSURE PADS

A modification made by the author to his deck concerning the pressure pads may be of interest. The original pads were of hard felt requiring quite a high pressure to ensure contact between the tape and the head. These felt blocks were removed and replaced by a pad of composite construction, i.e. a layer of $\frac{1}{8}$ in thick foam plastic covered finally with a $\frac{1}{16}$ in layer of supple felt.

This gives improved contact at far less pressure thus reducing the wear on the heads and improving the flutter performance of the transport. At the same time a mu-metal screen cut from an old screening can was fixed to the rear of the RECORD/REPLAY head pressure pad to reduce the hum pick-up on playback.

RECORD/REPLAY SWITCH

Most tape recorders have their RECORD/REPLAY switch contacts interlocked with the function buttons. In order to change the function of the amplifier to RECORD, one set of "make" contacts are required. If these are not present on the recorder a switch must be provided and this should have contacts designed for switching capacitive loads.

The heads are wired up to the plug using low capacity screened lead. The deck chassis is earthed


to the screens of one of the record/play leads. Care should be taken to ensure that the metalwork of the amplifier does not touch the tape deck. If this is unavoidable the earth link mentioned above must be omitted.

The power supply should not be fixed down yet as its positioning is critical for minimum hum injection. To determine this position the deck should be set in motion as it would be when playing a tape. The power pack is then moved around the cabinet whilst listening to the replay hum level until it is subjectively at its lowest.

The recorder is now complete and ready for setting up.

SETTING UP PROCEDURE

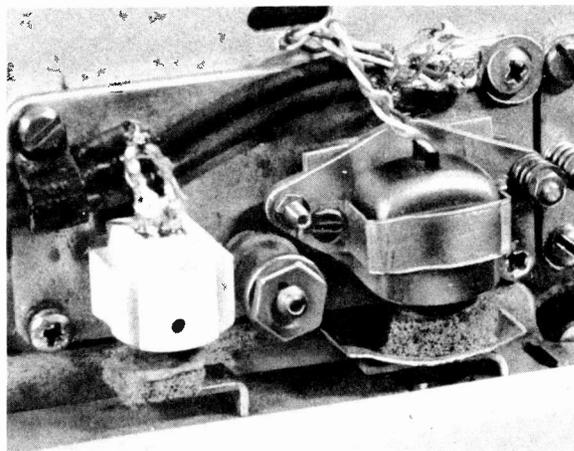The equipment required to set up the completed recorder is a d.c. voltmeter, an audio sine wave generator and an oscilloscope, or failing this an a.c.



Photograph showing the heads in position on the prototype

millivoltmeter. The setting up should follow the order outlined below as in some cases one stage depends on the setting of the previous.

AZIMUTH SETTING

Before the electronics are adjusted the heads must be correctly aligned with the tape. Adjustment of the record/replay head gap in relation to the tape is known as azimuth alignment and is essential in order to facilitate the interchangeability of recordings between machines. This is correctly done with the aid of a professional test tape but any commercially pre-recorded tape or a tape recorded on a machine with a known correct azimuth can be used. (Choose a tape with a good high frequency content.)

Whilst the tape is playing the head should be rocked up and down until the maximum high frequency output (measured simply by listening to the output) is obtained, then fixed in this position.



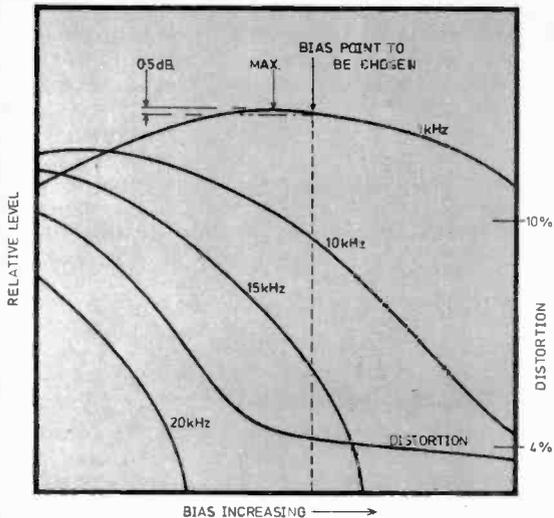


Fig. 9. Graph to show the dependence of frequency response and distortion on the bias level

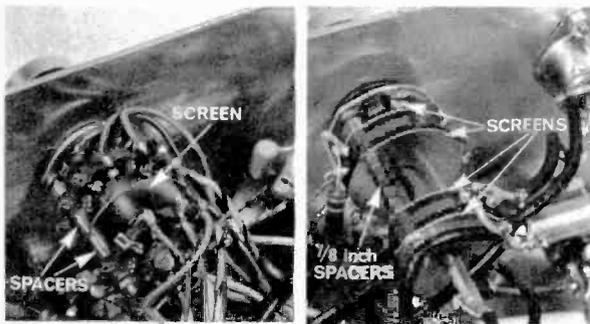

Photographs showing the two wafer switches

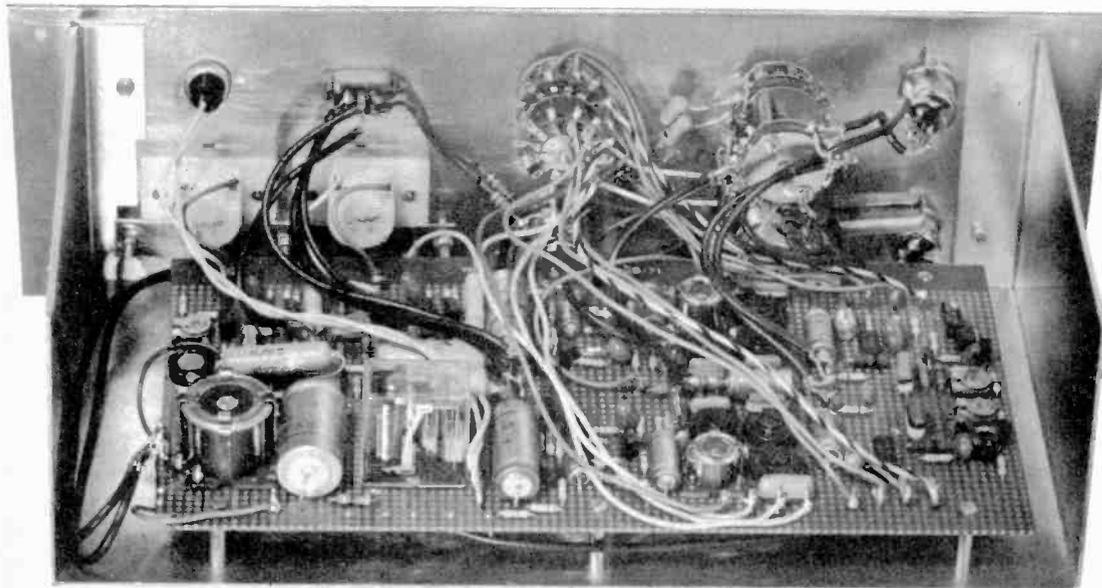Photograph of the completed Tape Link. The meters are held on to the front panel by a strap which is shown



REPLAY AMPLIFIER AND METERING ADJUSTMENTS

Using the voltmeter adjust VR5 and VR105 until the voltage at the emitters of TR9 and TR109 is 12 volts. Next rotate VR4 and VR104 fully clockwise (maximum resistance) then turn back so that the respective meters just read zero.

OSCILLATOR ADJUSTMENT

In the absence of suitable test equipment, a satisfactory result may be obtained by setting the adjuster to its mid position. The exact frequency of operation is not critical and in fact the tolerances of the frequency determining components are wider than the adjustment range.

If an oscilloscope or frequency meter is available then set the oscillator selector switch to STEREO, the bias control to mid range and the machine to the RECORD mode, then adjust the oscillator coil T2 until the frequency is as near to 100kHz as possible.

DETERMINATION OF BIAS SETTING

The correct bias setting is important as it affects many of the parameters of the recorder. The bias setting required depends on the tape speed, the tape in use and the mode of the recorder (MONO or STEREO). The settings should be determined as below and tabulated for reference.

7½ i.p.s.

Record a 1kHz sine wave at a level 6dB below the maximum modulation, adjusting the bias from -3dB to +3dB in ½dB steps. Replay the tape and note the amplitude of the output for each of the bias settings.

A series of results should be obtained which rise to a peak then fall off. The correct setting is that which gives a sensitivity ½dB (approximately 5 per cent) down from the maximum, i.e. slightly more bias than is required for maximum sensitivity (see Fig. 9).

continued on page 341

PE

NEXT MONTH... PUSHBUTTON VARICAP STEREO TUNER



Electronic tuning using varicap diode
Uses ready-built tuner and i.f. modules
I.C. stereo decoder which uses no coils
Pushbutton tuning to preset stations
Can be remotely tuned if desired
Needs no expensive equipment to set up
Compact design uses printed circuit board

Built in only a few hours, this low cost high quality tuner is the perfect unit to complete your hi-fi stereo system

FREE IN THE MAY ISSUE
DISPLAY
DEVICE IDENTICHART
At-a-glance information on many types of available readout devices

**ALSO IN
THIS
ISSUE...**

PE Sound Synthesiser - 4 RAMP GENERATORS AND INPUT AMPLIFIER


With the completion of this module it is now possible to create an enormous range of exciting sounds!

Don't miss out—Order from your newsagent now!

PRACTICAL ELECTRONICS

MAY ISSUE ON SALE APRIL 13

ELECTRONORAMA

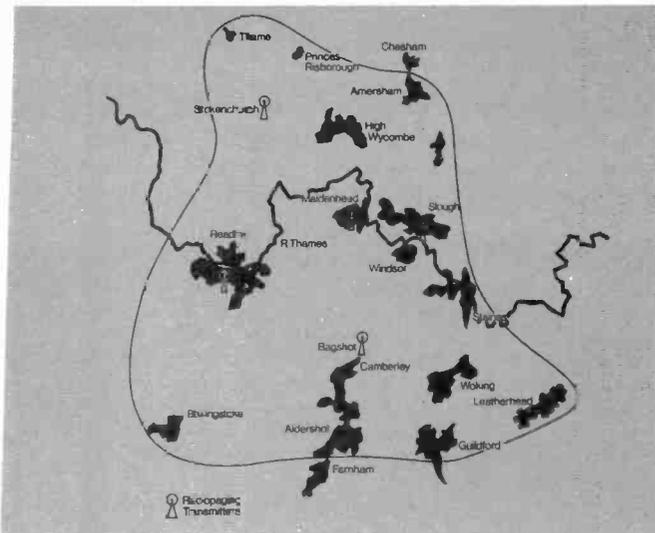

Area covered by the Post Office radio-paging service

Telephone Paging

WITH the aid of a new Post Office telephone paging system, the businessman, doctor, service engineer and many other people on call within a 500 square mile area of Reading can be easily contacted, even though their whereabouts is not known, simply by dialling a 10-digit telephone number.

The system consists of small "bleeper" pocket receivers; five f.m. transmitters, situated at Reading, Stokenchurch, Bagshot, Slough and Maidenhead; and computer-controlled terminal equipment at the Reading Trunk Exchange.

RECEIVERS

The receivers, small enough to be clipped into a pocket, give a high-pitched 10 second "bleep-bleep" signal when activated by a phone call. Powered by a 1.5V alkaline battery, each receiver will operate for approximately 900 hours, representing three months of average use.

The f.m. receivers are basically a double superhet built around six CMOS integrated circuit modules. Sensitivity is better than $10\mu\text{V}/\text{m}$ and reception is in the 150MHz band. Following detection, the paging tones are decoded by two plug-in active filter modules; 60 frequencies are employed in the range 288.5 to 1,433.5Hz and a two-tone sequence is used to provide a system usable by 3,540 customers. Later the system will cater for 100,000 customers.

Detection of the first coded tone switches the receivers on, reception of the second tone is decoded and once accepted will sound a 2kHz bleep note.

The only control on the receiver is a three position switch: "on", "off" and "memory". In the memory position, used when the person does not want to be disturbed, the incoming signal is stored in a CMOS bistable memory device and when the receiver is switched back to the on position the bleeper will emit its signal.

Each receiver has its own 10-digit number (the first four digits are an STD code common to all receivers) and dialling this number instructs the transmitting equipment to send a signal to activate the bleeper. Communication is one-way only, so the user must prearrange the action to be taken on receipt of a radio-paging call.

COMPUTER CONTROL

The heart of the system is a Digital Equipment, type PDP11, mini-computer with a basic storage capacity of 192,000 bits. Installed at the Reading Trunk Exchange, the computer receives the "telephone calls", converts them (by an interfacer between the telephone network and computer) into a binary-coded format.


The calls are queued and released in batches at 15 second intervals. When the number dialled is recognised and accepted an announcement to replace the telephone handset is given. Once accepted the call is converted to the pager code by the computer, and passed to a frequency synthesiser and then to the relevant transmitters.

The transmitters are switched by command signals from the control complex slightly ahead of the transmission of the pager-code modulation.

Although the system is only a feasibility study, plans have already been made to extend the service to other regions, such as London, Manchester and Birmingham.

More advanced pagers are already being developed and the present receivers are claimed to work inside buildings, cars and on trains. Engineers have, it is claimed, achieved more than a 95 per cent reception in the defined boundary limits.

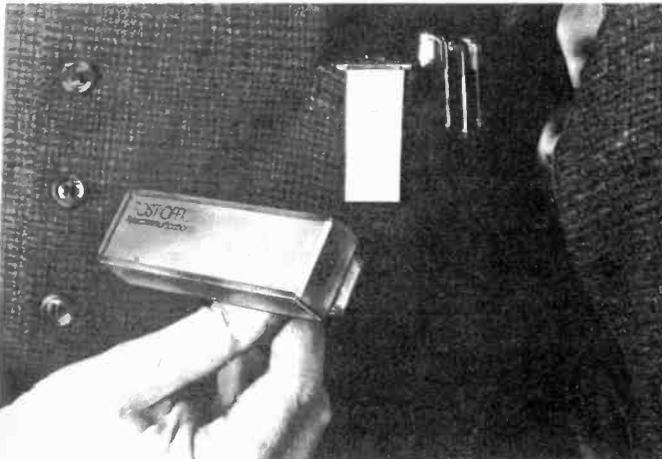The radio-paging receivers will cost £5 a month to rent, with an initial fee of £5. Call to a receiver will be free during the introductory service.



One of the miniature pocket pagers

Computer control complex at Reading Trunk Exchange



THE FREE HEATHKIT CATALOGUE

.....perhaps the most valuable stereo HiFi/Electronics kit publication available today



NEW MULTI-SPEAKER KIT

Features Four KEF Hi-fi Drive Units. Offers monitor quality at lowest cost.

NEW AM FM STEREO RECEIVER KIT

Solid State FM IF Circuitry, two IC's, two ceramic filters. Black magic lighting.

NEW PORTABLE ENGINE ANALYSER KIT

Versatile automotive testing and trouble-shooting.

LOW-PRICED TESTERS AND INSTRUMENTS

for the hobbyist and technician.

PLUS

all the models you have read about in international publications.

NEW 1214 SERIES STEREO HI-FI

Ideal for use for quadraphonic sound.

the HOW AND WHY OF KIT BUILDING

Electronics is fun the HEATHKIT way.

BUILD YOURSELF A PAIR OF SPEAKERS

in an evening - enjoy Stereo sound.

GET THE BEST IN HI-FI

Enjoy worthwhile kit savings.

SOMETHING FOR ALL THE FAMILY

even a battery charge for dad.

LOW COST STEREO RECORD PLAYER

amazing sound value.

It's Free... it's the latest Hi-Fi/Electronics catalogue from Heath the world-famous electronic kit manufacturers... and it's yours on request. This latest catalogue will appeal to all the family. Stereo Hi-Fi Transistor portables. Metal detectors. Electronic calculators etc. etc. You name it Heath can supply. All models offer unbeatable specifications for price. Excellent continuous credit and no deposit terms available... this even includes instruments. You cannot afford to miss reading this fine publication... hurry send off the coupon for your personal copy today.

Ask about our No Deposit Terms

Please send me a FREE Heathkit catalogue

Name _____

Address _____

HEATH
Schlumberger

Heath (Gloucester) Limited, Dept PE/4/73
Gloucester GL2 6EE Telephone 0452 29451

Heath (Gloucester) Limited, Gloucester GL2 6EE

**LARGE STOCKS,
ATTRACTIVE DISCOUNTS
DEPENDABLE SERVICE**

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power	60p
AC153K pnp germanium low power	25p
AC176K npn germanium low power	23p
AD161 npn germanium medium power	42p
AD162 pnp germanium medium power	40p
AF139 pnp germanium UHF	33p
NPN: BC107 13p, BC108 12p, BC109 13p, BC167 10p, BC168 9p, BC169 10p.	
PNP: BC177 15p, BC178 14p, BC179 15p, BC257 9p, BC258 8p, BC259 9p.	

Standard groupings available.

BD135 npn medium power	26p
BD136 pnp medium power	27p

DIODES

OA90, OA91, OA95, 6p each; OA200, 9p; OA202, 10p.

Other semiconductors: AC128, 17p; AF117, 35p; BFY51, 19p. Full lists and technical data will be found in Catalogue No. 6.


SIEMENS' THYRISTORS

0.8A 400V 56p, 600V 70p, 3A 400V 60p, 600V 88p.

ZENER DIODES full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

DIN PLUGS AND SOCKETS

by Hirshmann, 4A rating

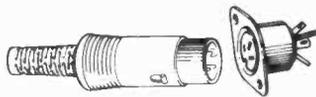


2 way LS — socket 10p, plug 12p
3 way scr.—socket 10p, plug 12p
5 way scr.—socket 11p, plug 15p

TRANSISTOR ACCESSORIES

TO3 cover, 7p; Heat sinks 1°C/W, type 6W1, undrilled, 60p.

SWITCHES

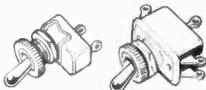1011 SPST toggle, 20p; 405 DPDT toggle, 29p (these are chrome plated, 2.5A rating); 7201 sub-miniature DPDT 250V a.c./2A, 48p.



ROTARY SWITCHES

Radiospares Miniature Make-switch (in assembly kit form). Shaft, 48p. Wafers, MBB-2P5W, 1P11W; BBM1P12W, 2P6W, 3P4W, 4P3W, 6P2W, 6p each.

WAVECHANGE SWITCHES

1P12W, 2P6W, 3P4W, 413W, 24p each.



ELECTROLYTIC CAPACITORS AXIAL LEAD

Rated voltage:	3V	6.3V	10V	16V	25V	40V	63V	100V
Capacity μ F	0.47	—	—	—	—	—	7p	7p
	1.0	—	—	—	—	7p	7p	7p
	2.2	—	—	—	7p	7p	7p	7p
	4.7	—	—	—	7p	7p	7p	7p
	10	—	7p	—	7p	7p	7p	7p
	22	—	7p	7p	7p	7p	7p	7p
	47	7p	7p	7p	7p	7p	7p	7p
	100	7p	7p	7p	7p	7p	7p	7p
	220	7p	7p	7p	7p	7p	7p	7p
	470	7p	7p	7p	7p	7p	7p	7p
	1,000	7p	7p	7p	7p	7p	7p	7p
	2,200	7p	7p	7p	7p	7p	7p	7p
	4,700	7p	7p	7p	7p	7p	7p	7p
	10,000	7p	7p	7p	7p	7p	7p	7p

POLYCARBONATE—5% TOLERANCE

250V up to 0.1 μ F; 100V, 0.1 μ F and above.
0.01; 0.012; 0.015; 0.018; 0.022; 0.027; 0.033; 0.047; 0.056; 4p each.
0.068; 0.082; 0.1; 0.12; 0.15; 4p each.
0.18; 0.22; 5p each. 0.27; 0.33; 6p; 0.39 7p; 0.47 8p; 0.56 10p; 0.68 11p; 1 μ F 13p.

RESISTORS — 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω —220K Ω	E12	9	8	7.5
C	1/8W	5%	4.7 Ω —470K Ω	E24	1	0.9	0.75 nett
C	1/4W	10%	4.7 Ω —10M Ω	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7 Ω —10M Ω	E24	1.2	1	0.8 nett
C	1W	10%	4.7 Ω —10M Ω	E12	2.5	2	1.6 nett
MO	1/2W	2%	10 Ω —1M Ω	E24	4	3	2 nett
WW	1W	10% \pm 1/20 Ω	0.22 Ω —3.9 Ω	E12	7	7	6
WW	3W	5%	1 Ω —10K Ω	E12	7	7	6
WW	7W	5%	1 Ω —10K Ω	E12	9	9	8

Codes: C = carbon film, high stability, low noise.
MO = metal oxide, ElectroSil TR5, ultra low noise.
WW = wire wound, Plessey.

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.


Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions on total value of resistor order.)

EVERYTHING BRAND NEW, GUARANTEED TO MAKERS' SPEC. NO SECONDS OR REJECTS

KNOB


All grub screw fitting for pin shafts. Black. For other types — see Catalogue No. 6, p. 54.

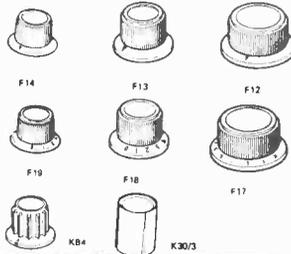F.14 (20mm) pack of 2, 32p; F.13 (26mm) pack of 2, 38p; F.12 (33mm) pack of 2, 40p; F.19 (20mm) pack of 2, 32p; F.18 (26mm) pack of 2, 38p; F.17 (33mm) pack of 2, 40p; KB.4 (20mm) pack of 4, 40p; K30/3 (17mm) aluminium, 24p each.



POTENTIOMETERS

Rotary, carbon track, double wiper
SINGLE P20 lin. 100 Ω to 2.2M Ω , 12p; JP20 Log. 4.7K Ω , to 2.2M Ω , 12p; Dual gang lin. 4.7K Ω to 2.2M Ω , 42p; Dual log/antilog, 10K, 22K, 47K, 1M Ω only, 42p; Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.
Only decades of 10, 22 and 47 available in ranges quoted.
DUAL CONCENTRIC DP20 in any combination of P20 values, 60p; with switch, 72p.
SLIDER
Lin. or log, 10K to 1 meg. in all popular values, each 26p.
Control knobs blk./white/red/yel./g./blue/dk. grey/lt. grey, 5p each.
CARBON SKELETON PRE-SETS

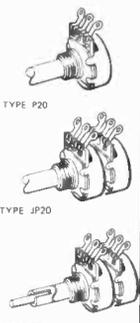

TRANSFORMERS—MAINS

MT3 30V/2A plus 4 taps	£2.85
MT103 50V/1A plus 4 taps	£2.55
MT104 50V/2A plus 4 taps	£3.50
MT127 60V/2A plus 4 taps	£3.80
13TOS 13V $\frac{1}{2}$ A, CT	£1.25
28TOS 12-12-2-0-2V $\frac{1}{2}$ A	£1.25

IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE

No. 6 (4th printing) contains details of 100's of semiconductors; ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc., information and equivalent tables, etc. Well illustrated (96 pages, 5 1/2 in x 8 1/2 in) 25p post free with refund voucher for 25p allowable on orders over £5 or more.

with
25p
refund
voucher

DISCOUNTS

All items offered for sale in accordance with our stated terms of business, copy of which available on request.
Not allowed a nett price items. 10% on orders for £5 or more. 15% on orders of £15 or more. Prices subject to alteration without prior notice. Prices quoted DO NOT include V.A.T. Orders received after 31st March must be accompanied by an additional 10% of the nett value for V.A.T.

POSTAGE AND PACKING FREE

SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost.

ELECTROVALUE

(Dept. PE4), 28 ST. JUDE'S ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB

Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 3603

Telex 264475

Eng. Reg. No. 1047789

Registered Office: 28 St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB

Strictly

by K. Lenton-Smith

POPULAR MUSIC is a lucrative and highly competitive field these days and the net is cast to take in an even younger age group each year. Ten-year-olds now have their own idols! To be successful in the "pop" field involves a constant search for new sounds by electronic processes, especially as there is a practical limit to what can be done with the vocal if the lyrics are to remain intelligible. (Some readers may query the use of the word "intelligible" in this context!)

The Survey of Electronic Musical Instruments, published as a supplement to the November 1972 edition (issues unobtainable), showed how manufacturers are catering for this search for new tonal ideas. Though initially featured by recording artists, new effects are copied by local groups as they struggle to keep abreast of the times. Amateur musicians, who prefer "pop" music though never play publicly, like to re-create at home some of the sounds they hear on radio, tape and discs. The younger generation has always, as a tradition, looked for change and new experience, the popular music field being no exception. Over the years, the specification of available electronic musical instruments has taken this into account increasingly.

LIGHT MUSIC TODAY

A certain line in "Fings ain't wot they used to be", referring to the light music scene at that time, mentioned musicians "backing themselves with three chords only". When that song was written, there was an element of truth in Lionel Bart's cynicism: a number of performers only seemed able to strum the tonic, sub-dominant and dominant seventh chords on their highly-amplified guitars. This deficiency was often covered up by a show of vocal and physical gymnastics!

The advent of the Beatles brought more tuneful melodies and the use of less closely related chords. Though the Beatles, as a group, no longer exist they underlined the fact that, if a song is to survive, the melody must be original and tuneful. Many modern "pop" numbers will be forgotten a few months hence, but the Lennon and McCartney compositions have already taken their place with those of the established Old Masters such as George Gershwin, Cole Porter, Jerome Kern and Richard Rodgers.

Burt Bacharach is today's prime example of a composer who writes enjoyable music which will be remembered many years hence: Antonio Carlos Jobim is in the same category, specialising in the Latin-American field. The reader who plays their music, or attempts the transcriptions of Dave Brubeck or Dudley Moore, will appreciate that the days of "three chords only" have long passed and things certainly ain't what they used to be! These composers frequently use complex chord sequences which demand a high degree of musical ability to perform them.

Whereas our sphere of electronics—especially integrated circuitry—has enjoyed a spin-off from space research, classically trained musicians who have turned to lighter music have also benefited that field. The music for a number of West End shows running currently has come from composers with classical backgrounds, whilst we have previously commented on Walter Carlos, Robert Moog and the music for "Clockwork Orange".

RETROGRADE

Today's standard of compositions and the requisite musicianship in light music is higher than it was a generation ago. At the same time, the true standard of many electronic musical instruments has fallen.

Manufacturers appear to be attempting to get the proverbial quart into a pint pot, especially where organs are concerned. Perhaps this is understandable where many instruments are sold to be installed in clubs, or other public places, where the audience expects a really professional performance—by their standards.

The organ studio demonstrator will show convincingly what a wonderful instrument you are about to purchase. It will no doubt have many extras such as a built-in rhythm unit, waa waa, percussion, arpeggiator, automatic chord unit, Leslie speaker, cassette tape recorder and perhaps a small synthesiser keyboard, to name but a few. Underneath all this, how much real organ is there? All these additions are expensive and the makers are probably working to a given price range, so something has to give.

The accompaniment manual is usually the victim, and the buyer is lucky if he is offered more than one pitch on that keyboard. We should perhaps remember that not all users of electronic organs are light music orientated or require the help of automatic chord/rhythm units. No serious organist would consider a single-pitch manual, or for that matter a short spinet manual of 44 notes and a set of stub-pedals. A number of users are primarily interested in baroque music or are simply church organists who require a home organ for practice purposes which will produce conventional pipe-organ tonal quality.

SOUND SYNTHESISER

For those who wish to experiment with unusual effects, the synthesiser is ideal. Mr Shaw's P.E. Sound Synthesiser should prove to be a fascinating project for readers seeking new musical sounds: we hope it will also alert organ makers to the fact that organs should sound as such and not attempt to compete with the synthesiser. Both are separate and distinct musical devices with identities of their own.

Incidentally, readers who went to the Audio Fair to hear Mr Shaw's synthesiser last year might also have listened to some of the stereo demonstrations on various stands. One of the records used for this purpose was "Moog Indigo" (VSD 6549) featuring Jean Jacques Perrey, is recommended to those who like the Moog and can appreciate the performer's skill and have a strong sense of humour.

Simple All-Around SECURITY ALARM

By J. Andrews

THIS alarm system was developed to protect the house and buildings remote from it, for example, garage, workshop, etc., which might be subject to burglary or vandalism. It can of course be used to protect all other types of property.

SEARCH LOOP SYSTEM

Many alarms use the search loop system in which the doors and windows have micro-switches fitted. The switches are wired in series and should any one switch be opened the circuit is broken. When the loop is connected to a simple alarm breaking the search loop will cause a bell or other device to sound. However, if the loop can be shorted out before the switches the alarm can be rendered inoperative.

This is particularly easy if the building protected is remote from the house as the search loop wires may be run back together and offer an opportunity for short circuit. Short circuits could be caused in a number of ways, by accident, fire or deliberately.

BALANCED BRIDGE

To overcome these problems a simple bridge was devised for the prototype security alarm as seen in Fig. 1.

Here, one arm is made up of the search loop wire resistance R_x . With the bridge balanced, that is, when $R_x \times R_2 = R_1 \times R_3$, no voltage will appear at the alarm input points XY. If the search loop is made either open or short circuit, outputs will appear at these points but of opposing polarity.

POLARISING DIODES

To overcome this and to provide voltages of a single polarity for the open and short circuit conditions, a diode bridge was arranged so that any change of balance in the resistance bridge provides a negative going input to the alarm circuit as in Fig. 2.

In this, the finalised circuit of the Security Alarm, the resistance bridge is made up of R_1 , R_2 , R_3 , $VR1$ and the loop resistance R_x .

Arm resistances are made 150 kilohms so that the standing current is low. $VR1$ is included to balance any difference in the bridge arms and also provides a test facility as described later.

LATCH CIRCUIT

As the output resistance of the bridge is relatively high it is necessary to multiply the input impedance


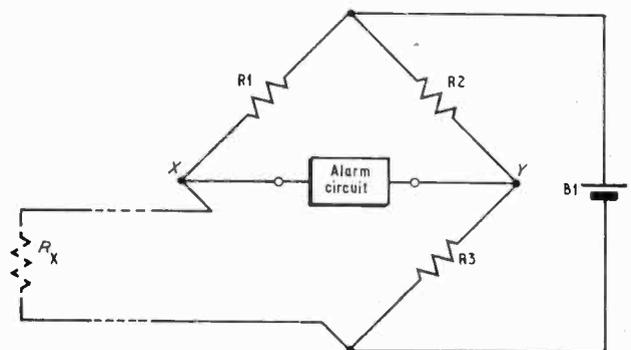


Fig. 1. Basic bridge system

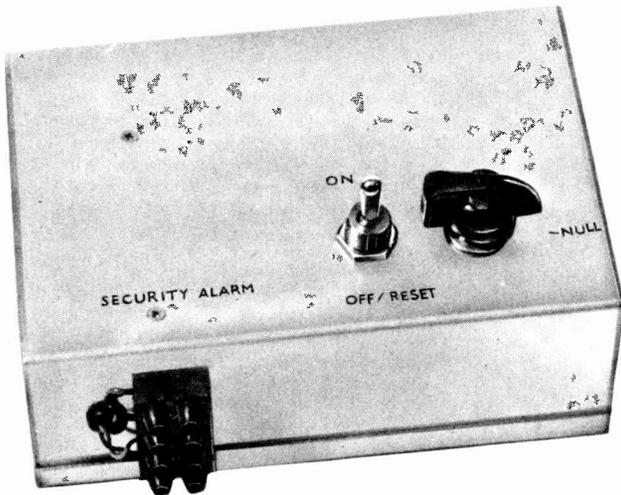

The completed security alarm control unit

of any device connected across it. In the latch circuit this is achieved by connecting TR1 and TR2 as a Darlington pair.

TR2 output drives TR3 which is a higher power device suitable for driving a relay or lamp up to 800 milliamps when saturated.

Latching or hold on is achieved as follows. When TR3 is turned on by TR2 the collector voltage falls due to the drop across the relay and when TR3 is saturated is approximately 0.3V.

As TR3 collector goes negative, this turns TR2 on harder and positive feedback holds TR2 and TR3 in saturation regardless of input current to TR1.

The current to TR3 base is limited by R5. Once tripped the circuit will stay on until the supply is interrupted. C2 is included to ensure the circuit resets.

In the prototype a relay was used to switch on an external bell. It could also be used to turn on lights or activate other warning systems.

CONSTRUCTION

Most of the small components given in the circuit diagram can be assembled on a piece of 3in × 1½in Veroboard as is Fig. 3. When assembled and wired, 6in sleeved flying leads should be connected where indicated.

The choice of housing for the board and ancillary pieces was a 4in × 6in × 2½in standard aluminium chassis. First the mounting holes for VR1 are drilled together with those for the double-pole switch and Veroboard spacers.

With these items fitted interwiring can be completed as in Fig. 4.

TESTING

To test the assembled alarm connect up batteries B1 and B2 only and fit a 200 kilohm resistor across the loop terminal. If a high impedance multimeter is available connect across capacitor C1 as seen in Fig. 2.

Set the meter to the ten volt range, and switch the unit on. If now VR1 is rotated from end to end a null should be found.

If all is in order, connect B3 and switch on. The relay should stay out. If this is not so check that the null balance is correct.

Now rotate VR1 in a clockwise direction and the relay should pull in. If the null is now reset the relay should remain in.

Now reset the alarm by flicking switch S1 off and on, then rotate VR1 anticlockwise when the

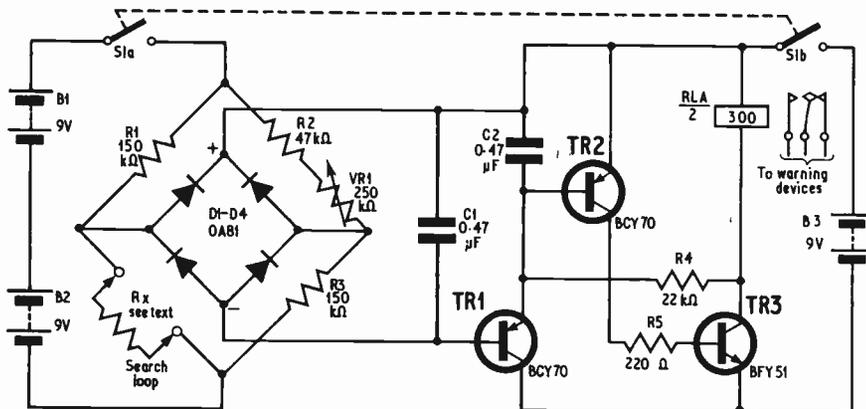


Fig. 2. Circuit diagram of the security alarm

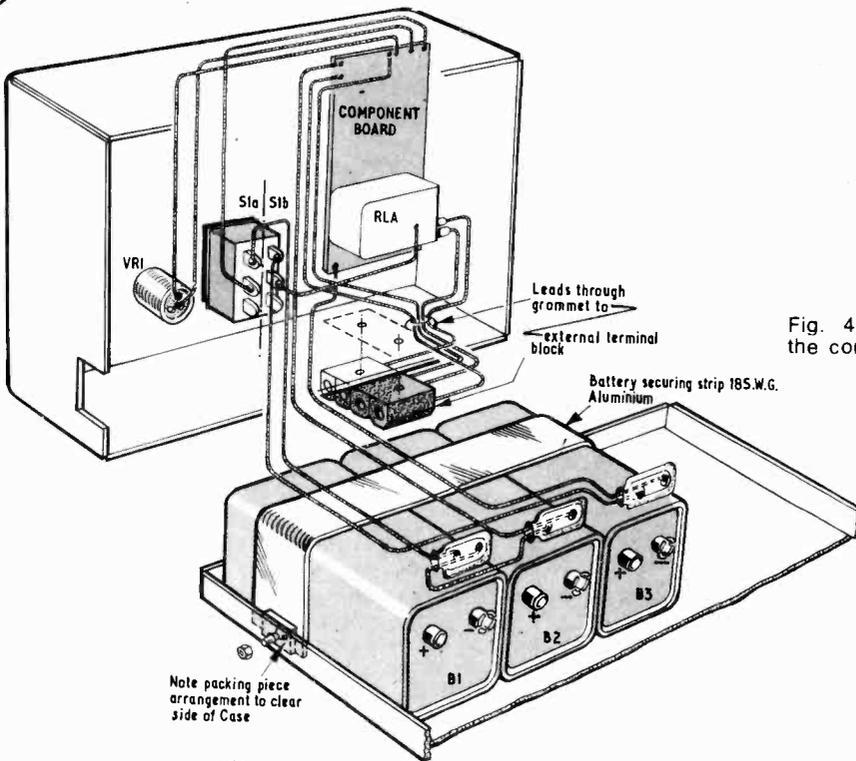


Fig. 4. Interwiring details of the control unit

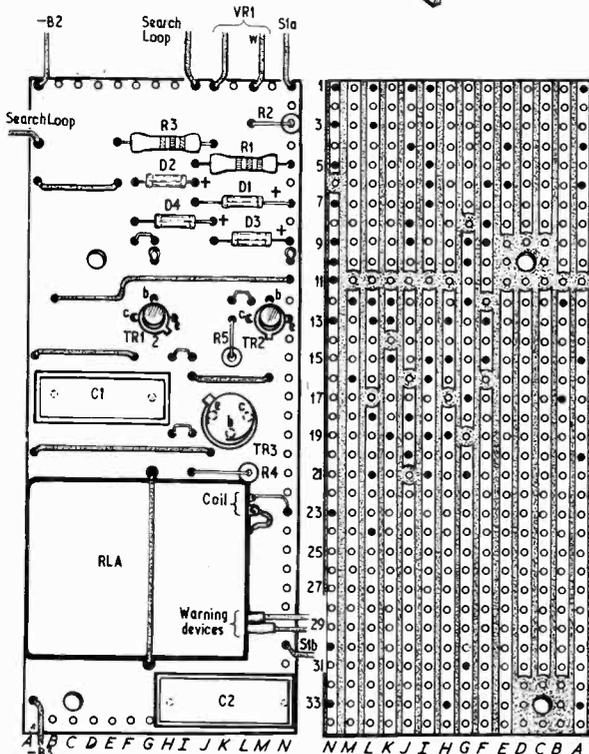


Fig. 3. Component board layout and wiring

COMPONENTS . . .

Resistors

- | | |
|------------------|-----------------|
| R1 150k Ω | R4 22k Ω |
| R2 47k Ω | R5 220 Ω |
| R3 150k Ω | |
- All $\frac{1}{2}$ watt 10% carbon

Capacitors

- | | |
|-----------|-----------|
| C1 0.47uF | C2 0.47uF |
|-----------|-----------|

Potentiometer

- VR1 250k Ω carbon lin.

Transistors

- TR1-TR2 BCY70 (2 off) TR3 BFY51

Diodes

- D1-D4 OA81 (4 off)

Switch

- S1 Double-pole, single throw mains on/off

Relay

- RLA 100-300 Ω coil, 6V with contacts to suit application

Miscellaneous

- B1-B3 9V Vidor VT6 (3 off), aluminium chassis 4in \times 6in \times 2 $\frac{1}{2}$ in, Veroboard and wire to suit

relay should again pull in. Return VR1 to null and reset the alarm with the switch.

Note that the relay cannot be reset unless VR1 is at null.

TESTING WITHOUT A METER

Disconnect R4 from the base of TR2 and connect a 200k Ω resistor across the loop terminals as before. Connect all batteries and switch on.

Rotate VR1 until the relay pulls in, then back off until the relay drops out. Note the point at which the relay pulled in.

Rotate VR1 in the opposite direction until the relay pulls in again, and note this point. The centre of the two points at which the relay pulled in is the null point of the bridge.

Reconnect R4 and check that when VR1 is rotated in either direction the relay pulls in and remains when VR1 is set to null.

FINISH

Once the instrument has been checked and the null and test points have been determined, Letraset may be used to apply a legend to the front panel. A coat of clear varnish will ensure the case stays bright.

INSTALLATION

As explained previously the search loop resistance must total 150k Ω -200k Ω . This is extremely high and any amount of wire used to make up the search loop will not affect this figure, therefore it is necessary to insert resistance in the form of two 100k Ω resistors in the loop.

Arrangement of switches in the loop need not be confined to microswitches on doors and windows. Switches can be placed under carpets, etc., depending on the amount of security required. One further idea to protect windows apart from microswitches, is to fix a screen of fine copper with tape or clear varnish directly to the glass. This is included in the search loop; should the window be broken, the alarm will sound.

The alarm control unit would normally be installed in some part of the house, perhaps in a cupboard or concealed behind furniture. However, when siting the alarm, bear in mind the wires will have to run to parts of the house or outbuildings to be protected.

WARNING DEVICE

No actual warning device is shown as this will be governed by personal requirements, possibly only a warning light will be required, however the relay could turn on house lights or ring a large bell.

Once installed and assuming the alarm has been tested as above, no difficulty should be encountered. Before connecting the search loop check with an ohmmeter for continuity and correct resistance. Connect the search loop to the control unit and set VR1 to null; switch on the alarm and check that both shorting and open-circuiting the search loop cause the alarm to operate.

When in use periodically check the alarm by rotating VR1 first clockwise and then anticlockwise. In both cases the alarm should sound. This forms a test of battery condition. Batteries should operate the unit for their shelf life. ★

HI-FI TAPE LINK

continued from page 332

3 $\frac{1}{2}$ i.p.s.

Repeat as for 7 $\frac{1}{2}$ i.p.s. using a test frequency of 500Hz.

1 $\frac{7}{8}$ i.p.s.

As for 7 $\frac{1}{2}$ i.p.s. but using 250Hz.

The bias must be determined separately for mono and stereo modes.

PRE-EMPHASIS

Adjustment of the pre-emphasis gives a maximally flat overall frequency response.

7 $\frac{1}{2}$ i.p.s.

Apply an input signal from a signal generator at 15.4kHz and adjust L1 until peak output is obtained at the output of the replay amplifier (junction of R11 and R13). Next set the generator frequency to 4kHz and record at a level of -10dB. Replay the tape and note its output as this is to be used as a reference.

Reset the frequency to 15.4kHz and make another recording leaving the level control untouched. Note the playback level and then make successive recordings adjusting VR1 to give a playback level at 15.4kHz which is $\frac{1}{2}$ dB greater than at 4kHz. The overall response should now be reasonably flat. However, a check should be made at a number of points between 4kHz and 15.4kHz adjusting VR1 so that the undulations in the response curve lie equally about the 4kHz figure.

Then repeat this procedure for the other channel.

3 $\frac{1}{2}$ i.p.s.

Record a 800Hz reference level once again at -10dB. Set the generator to 9.6kHz and repeat the above procedure but this time adjusting VR2 then VR102.

1 $\frac{7}{8}$ i.p.s.

In this case a 200Hz reference level is used at -10dB. The generator is set initially to 6.0kHz and VR3 then VR103 are set up as above.

MODIFICATIONS

Readers wishing to save the expense of two meters can parallel the outputs of the meter drive amplifiers into one storage capacitor. The meter will then show the larger of the two input signals.

If this design is to be used with the P.E. Gemini amplifier then it is advisable to fit attenuators to the input and output sockets. This allows reasonable use of the gain control to be made when recording and on playback gives an output consistent with the input sensitivity of the Gemini. ★

Correction: In the first part (March 1973) Figs. 2b and 2c should be transposed.

PE Digi-Cal

By R.W. COLES
PART 10

M COUNTER BOARDS

THIS month's article deals with the M(COUNTER) boards which are the last of the arithmetic unit plug-in cards to be described.

M COUNTER FUNCTION

The basic system used to enable the MULTIPLICATION and DIVISION operations to be carried out was described in Part 1, where it was mentioned that the successive additions and subtractions carried out were counted in a counter circuit.

It is this counter which is housed on the two identical M boards, together with the COMPARATOR circuit required during MULTIPLICATION to register an equality between the count and the contents of the E REGISTER.

BLOCK DIAGRAM

A block diagram of the COUNTER/COMPARATOR circuits and their related data paths is shown in Fig. 10.1, which can be placed in context by reference to the overall system block diagram, Fig. 1.3 of Part 1.

The counter itself consists of a serial string of six, four-bit, decade counter units which have a maximum count capacity of 999999.

The COUNTER can be cleared or preset by appropriate control signals from the programme, and is triggered by the PLUS/MINUS COMPLETE signal from board CB, which is produced during each addition and subtraction.

The six, four-bit, B.C.D. outputs from the counter are fed to the comparator circuit and also to the A REGISTER into which they can be entered at the end of a DIVISION sequence as required.

When the COMPARATOR registers an equality between the count and the E REGISTER contents during a multiplication, it sets a latch which produces the COMPARATOR EQUAL signal, which in turn stops the arithmetic clock.

Before a MULTIPLICATION sequence, the EQUALS LATCH is cleared by a signal from the PROGRAMME.


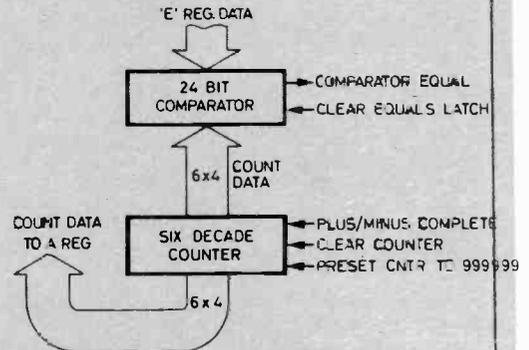


Fig. 10.1. Block diagram of the COUNTER/COMPARATOR circuits and their related data paths

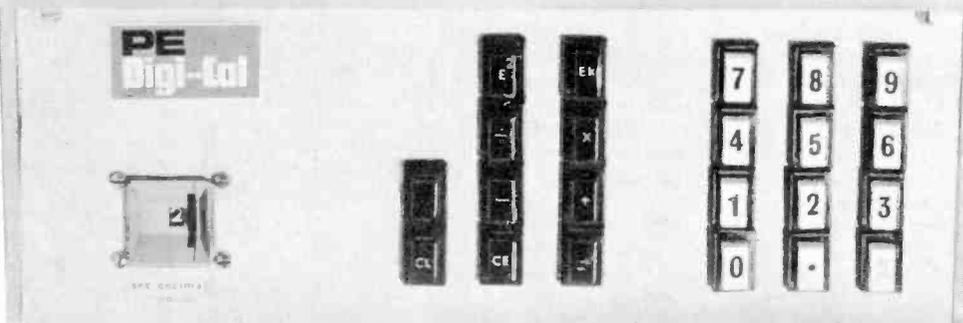

PARTITIONING

A six decade counter and comparator requires too many i.c.s, even when using M.S.I. devices, for it to be housed on a single DL109 card, so the circuit is split into two identical sections, each comprising a three decade counter and a commensurate amount of comparator circuitry. This is described more fully in Fig. 10.2.

Only one EQUALS LATCH is required, but in practice a latch is incorporated on each board to ensure interchangeability, which is an advantage in fault finding, and initial testing.

The latch in use is determined by the external edge connector wiring, no connection being made to the latch inputs and outputs on the board in the M2 position.

FULL CIRCUIT

The full circuit of one of the M COUNTER boards is shown in Fig. 10.3. The counter chain is easily identified as IC's 123, 124 and 125 which are SN7490 devices connected to count in a B.C.D. code by connection on the A output to the B input.

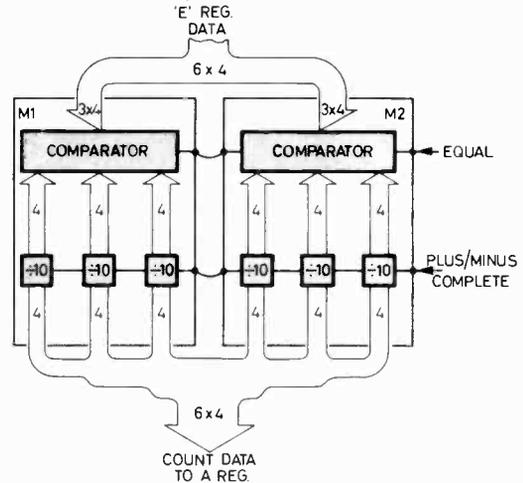


Fig. 10.2. Partitioning of the COUNTER/COMPARATOR between the two M boards

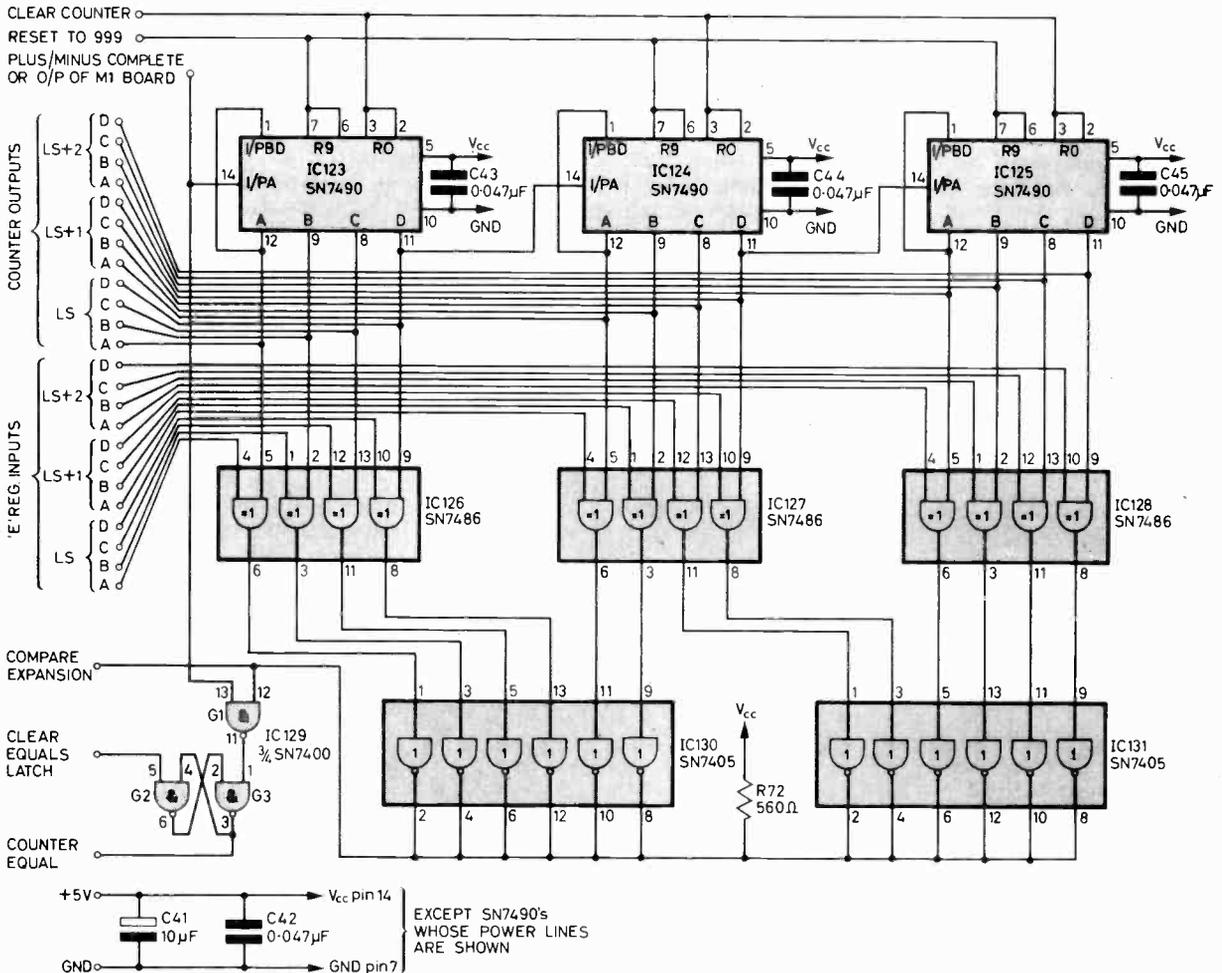


Fig. 10.3. Circuit diagram of one of the M boards. The other board is identical to this, both being built on DL109/44 boards

The count input to the board comes either from the PLUS/MINUS COMPLETE line (in the case of M1) or from the LS+2, D output of board M1 (in the case of M2).

Each of the SN7490 devices has a decoupling capacitor connected between its power supply lines, in addition to the two standard board decoupling capacitors C41 and C42.

LINE DRIVING

Special precautions are necessary for absolute integrity of the count, without false triggering or commutation, because the ABCD counter outputs are taken off the board as inputs to the A REGISTER.

Line driving from counters in this way can cause problems due to the high peak current required to charge the stray capacitance of the line during a 0 to 1 transition. Having an extra reservoir of charge available directly across the i.c. power pins goes a long way toward preventing the mistripping problems which could result.

COUNTER PRESETS

The RESET 0 (R0) and RESET 9 (R9) inputs to the SN7490 set the COUNTER outputs to 0000 or 1001 respectively.

The R0 inputs are connected together to form the CLEAR COUNTER line, controlled by the PROGRAMME, and the R9 inputs together make up the RESET to 999 line.

As mentioned in Part 1, it is necessary to preset the M COUNTER to 999999 before a division so that the final number of subtractions counted when the A REGISTER contents go negative and stop clock generation, is not the full number of subtractions performed, but the full number minus one.

Setting the count to 999999 is the same as starting to count from minus one, since on the first PLUS/MINUS COMPLETE pulse, the count will change to 000000, the number registered by the counter always being one behind the true number of subtractions performed.

During MULTIPLICATION the true number of additions performed has to be counted—the PROGRAMME ensuring this by energising the CLEAR COUNTER input and not the RESET to 999 input.

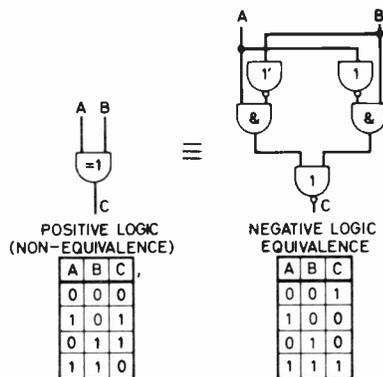


Fig. 10.4. Equivalent logic for an EXCLUSIVE-OR gate and truth tables for both positive and negative logic conventions

COMPONENTS . . .

Resistors

R72, R73 560Ω ¼W ±10% (2 off)

Capacitors

C41, C46 10μF 15V elect. (2 off)

C42-45, C47-50 0.047μF (8 off)

Integrated Circuits

IC123-125, IC132-134 SN7490 (6 off)

IC126-128, IC135-137 SN7486 (6 off)

IC129, IC138 SN7400 (2 off)

IC130, IC131, IC139, IC140 SN7405 (4 off)

Printed Circuit Boards

Type DL109/44 Shirehall (2 off)

In each case components are divided equally between the two M boards

COMPARATOR

The COUNTER as described is all that is needed to allow the DIVISION operation to take place, but during MULTIPLICATION comparison of the count with the E REGISTER contents is required.

The COMPARATOR is made up of the remaining i.c.s on each board and is concerned solely with detecting the equality of E REGISTER and COUNTER outputs so that a control signal can be produced to stop the clock at this point.

The 24 bits of E REGISTER data and the 24 bits of COUNTER data are individually compared on a one-to-one basis in a series of 24 EXCLUSIVE-OR gates formed from six SN7486 packages, housed three to a board.

EQUIVALENCE GATE

The SN7486 package is a member of the M.S.I. family and is described as a quad EXCLUSIVE-OR gate in TTL literature. The very useful EXCLUSIVE-OR function has its own logic symbol, but is in fact made up of a series of simpler gates, as has its own logic symbol, but is in fact made up of a series of simpler gates, as shown in Fig. 10.4.

Readers may recognise the equivalent logic as being simply the common AND-OR-INVERT function together with a couple of inverters to produce the NOT version of the A and B inputs.


The reason for the EXCLUSIVE-OR name becomes obvious when the basic (positive logic) truth table is examined. The output from the gate is a logic 1 if either input A OR input B is a logical 1 but *not* if both are logical 1's.

This response is that of a non-equivalence gate since a logic 1 output is produced only when the inputs are different, but the situation is changed when the gate is examined in operation as a negative logic system, as the second truth table demonstrates.


NEGATIVE LOGIC

In the second truth table we can see that when a low voltage is interpreted as a logic 1, rather than as a logic 0, the output of an SN7486 gate is a logic 1 when the inputs are identical, giving the equivalence function.

M COUNTER BOARDS

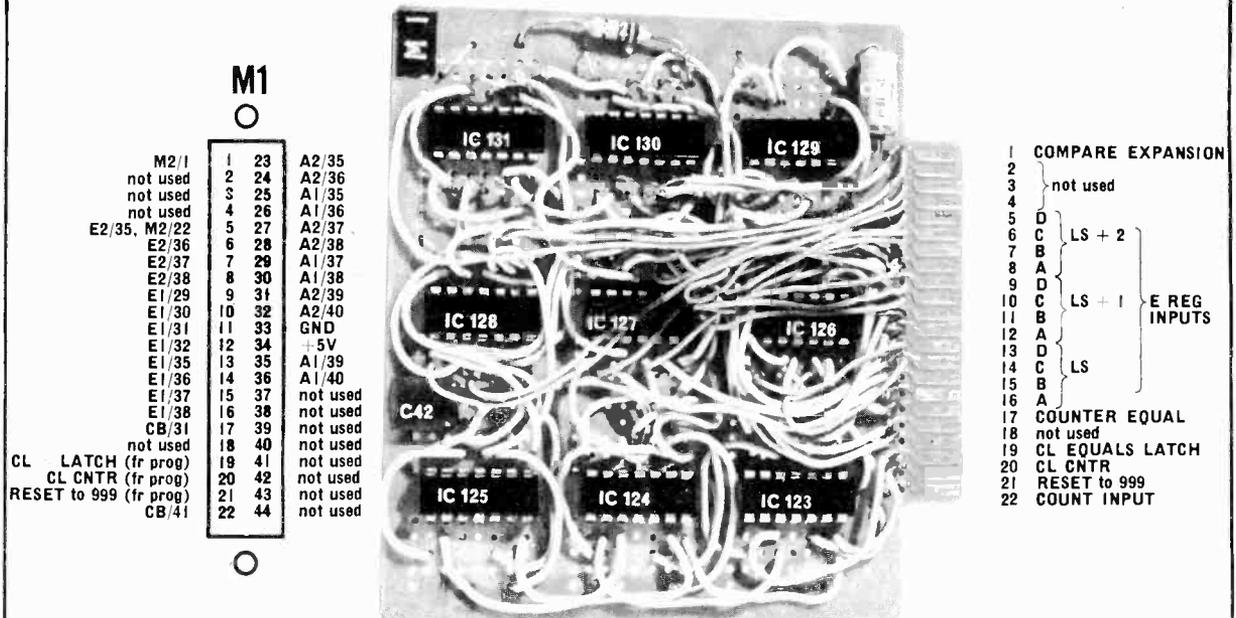

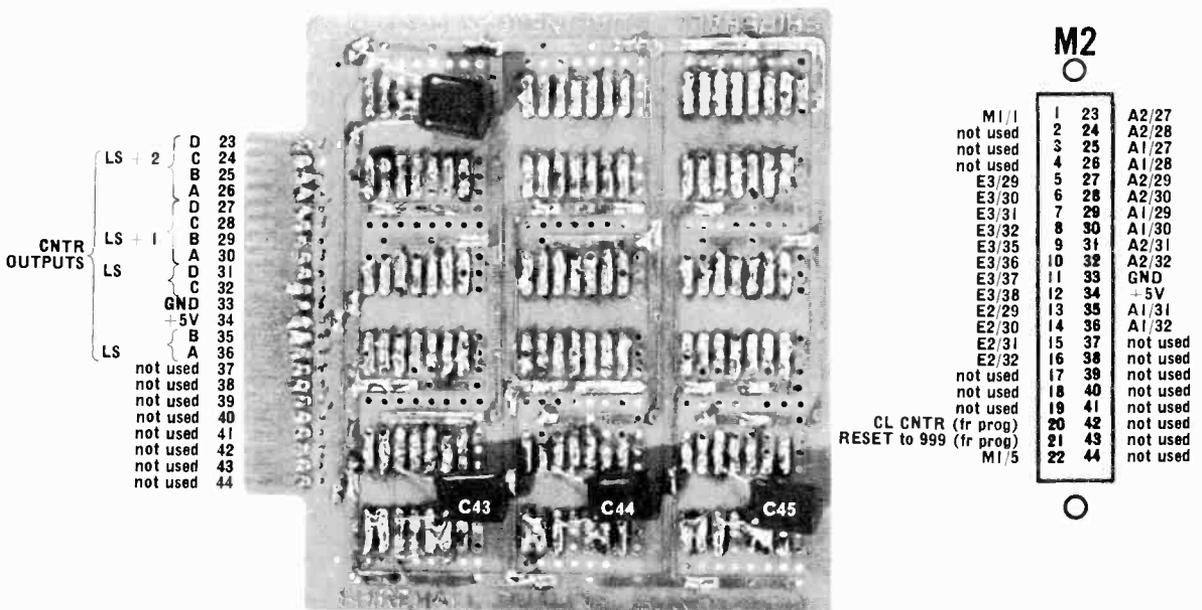Layout of components on upper side of M COUNTER board, and interconnection details of the M1 edge connector. See Fig. 6.9 for disposition of edge connectors



Layout of capacitors on underside (ignore unmarked capacitor) and interwiring details of M2 socket

To disbelievers, all this talk of switching logic conventions to suit the circumstances can be confusing, and really it is only a convenient way of looking at things.

In practical terms, the output of an SN7486 gate will go low when its inputs are identical, so to determine when all 24 gates have low outputs, i.e. when M equals E , we need a 24 input NAND gate which responds to negative logic inputs.

NEGATIVE LOGIC NAND GATE

No such gate is available in the standard TTL range, but if it were, it would be listed as a NOR gate because TTL is described in the positive logic convention.

All is not lost however since by using an open-collector inverter connected in the input of each SN7486, and then joining all the open collectors through a single common resistor to V_{CC} , i.e. by performing the WIRED-OR function at their outputs, a negative logic NAND gate of virtually unlimited size can be formed (Fig. 10.5).

The way a gate operates is fairly straightforward: if all SN7486 outputs are low, i.e. if M equals E , then the output of all inverters will be high, and the common resistor ensures a high voltage output.

If any one or more of the SN7486 outputs is high, however, one or more of the inverter outputs will go low and pull the common output to a low level.

INVERTERS

The inverters used on the M boards are type SN7405, which have the required open collector output circuitry. Note that the SN7404 devices are not suitable for use in this position due to their standard totem-pole outputs.

Although only one "pull-up" resistor is required for the full 24 inverters, electrically speaking in fact a separate resistor is used on each board to allow the boards to operate autonomously when required.

The inverter outputs from the two boards are united by means of the COMPARE EXPANSION input/output line, so that the two resistors are effectively in parallel.

LATCH FUNCTION

When an equality is registered by the comparator, the common output line rises to a high level and this signal is used to set the simple latch flip-flop made from cross-coupled SN7400 gates G2 and G3.

Setting the latch is carried out via another gate G1, which is controlled by the clock input line to

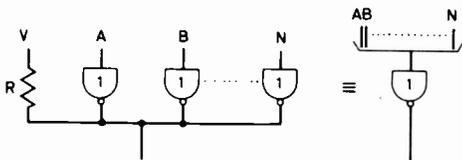


Fig. 10.5. The use of inverters to form a 24 input NOR gate

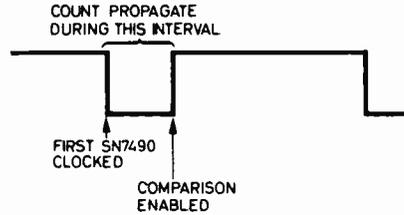


Fig. 10.6. PLUS/MINUS COMPLETE waveform from the COUNTER board

the first SN7490. In practice this line will carry the PLUS/MINUS COMPLETE waveform, since only the latch on the M1 board is wired into circuit.

The reason for this gated latch input circuit is explained in Fig. 10.6, which shows the PLUS/MINUS COMPLETE waveform from the COUNTER board.

The SN7490 counters are triggered from the negative going signal, but because these devices operate in the ripple count mode, there will be a significant count propagation delay time down the chain which can and will lead to transient spurious outputs from the COMPARATOR gating.

Using the PLUS/MINUS COMPLETE signal to gate the COMPARATOR output prevents the spurious outputs from setting the EQUALS LATCH until count propagation is complete, since G1 is enabled by the positive going edge of the waveform.

EQUALITY

When a genuine state of equality exists between the COUNTER and E REGISTER the latch is set, energising the COUNTER EQUAL line which in turn stops the supply of clock pulses to the A , Z and ADDER boards.

Before a further MULTIPLICATION sequence is initiated, the PROGRAMME clears the EQUALS LATCH ready for a new comparison.

CONSTRUCTION

Construction of the two M boards follows the by now familiar pattern, two DL109/44 cards being used. All wiring should be kept as short as possible whilst avoiding "bird's nests".

Speed problems decrease by a factor of ten for each stage of the COUNTER meaning in effect that only the first stage could be a problem in this respect. For this reason it is best to select which board is to be installed in the M1 position during test calculations, since the first stage of one board might perform better than the other at speed.

TESTING

The M boards are easy to check in isolation if required, but if the recommended sequence of construction has been followed and the calculator is operational on ADD/SUBTRACT, it is easier to test the boards in situ, using the MULTIPLY/DIVIDE programmes—but more of this next month.

Next month: E^2 Logic, Error Detection and Testing


MAIL ORDERS: Some items have a postage and handling charge shown against them. Where p. & p. is not shown the charge is 13p for any selection. When both classes of goods are ordered the charge is 13p plus any p. & p. charges shown. (Overseas extra). Telephone 01-682 4412.

GARLAND BROS. LTD.

DEPTFORD BROADWAY, LONDON, SE8 4QN

SWITCHES

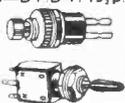Standard toggle switches:
SW20—S.P.S.T. 20p; SW21—D.P.D.T. 25p.
Miniature toggle switches:
SW18—S.P.S.T. 51p; SW19—D.P.D.T. 64p.
Slider switches, SW3—D.P.D.T. 15p.
Wafer switches (rotary)—26p each
SW4—1 pole, 12 way
SW5—2 pole, 6 way
SW6—3 pole, 4 way
SW7—4 pole, 2 way
SW8—4 pole, 3 way



PLINTH

to suit Garrard 2025, SP25 etc. Teak finish, complete with Perspex cover. Very attractive appearance. £3.95 plus 55p p. & p.




J-BEAM FM4S AERIAL

4 element, all channel aerial for stereo radio. £6.10 plus 50p p. & p.



PLASTIC BOXES

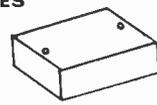for constructional projects. White, with lid and screws. BP1 4½ins x 3ins x 1½ins—37p.
BP2 6ins x 4ins x 2½ins—37p.



BATTERY HOLDERS

for 4 x HP7. Long or short—22p.
Press studs, ready wired PP3 size—10p; PP9 size—13p.



EQUIPMENT CASES

in plain aluminium with sloping front panel.

Type	H.	W.	D.	Price p. & p.
SF1	2in	5½in	2½in	50p 13p
SF2	2in	7½in	3in	66p 17p
SF3	2in	9½in	4½in	83p 20p



MINIATURE SPEAKERS

2½in 8Ω
2½in 8Ω
2½in 80Ω
All at 60p each.



GROOV-KLEEN

de luxe model 42. £2.15



V.A.T.

Prices in this advertisement include V.A.T. If ordering before April 1st please deduct 10% from total order.

CONSOLE CASES

in plain aluminium, ideal for mixers, instruments, etc.

Type	W.	A	B	C	D	Price p. & p.
GB20	10	9	3½	2	3	£1.56 33p
GB21	10	9	3½	2	3	£1.74 33p
GB22	12	9	3½	2	3	£1.89 33p



ALUMINIUM BOXES

with lids and screws

Type	L.	W.	D.	Price p. & p.
GB7*	5½in	2½in	1½in	42p 16p
GB8*	4in	4in	1½in	42p 16p
GB9*	4in	2½in	1½in	42p 14p
GB10*	5½in	4in	1½in	49p 19p
GB11	4in	2½in	2in	42p 14p
GB12	3in	2in	1in	36p 15p
GB13	6in	4in	2in	57p 20p
GB14	7in	5in	2½in	69p 21p
GB15	8in	6in	3in	89p 29p
GB16	10in	7in	3in	£1.00 29p

* These sizes fit standard veroboards

STEREO HEADPHONES

Eagle SES. 8Ω
40—16,000Hz
Complete with cable and stereo jack plug
£3.43 Plus 24p p. & p.



10 WATT AMPLIFIER module

Input: 30mV into 10kΩ for 10W, 40—16,000 Hz
Output: 3-8-16Ω
Power Supply 12V £4.70 plus 24p p. & p.



DYNAMIC MICROPHONE UD130HL

This sensitive, quality microphone is uni-directional and is complete with mute switch and 20 feet of cable and plug. 100-12,000Hz. Dual impedance 600Ω and 50kΩ.
£6.60 plus 24p p. & p.



MICROPHONE FLOOR STAND

Professional, heavy quality with folding tripod base. Telescopic stem extends to 59ins. Chrome finish. £6.25 plus 45p p. & p.



MINIATURE ELECTROLYTICS

1.0μF	63V	7p	150μF	25V	8p
1.5μF	63V	7p	150μF	40V	13p
2.2μF	63V	7p	150μF	63V	15p
3.3μF	63V	7p	220μF	4V	7p
4.7μF	63V	7p	220μF	10V	7p
6.8μF	40V	7p	220μF	16V	8p
6.8μF	63V	7p	220μF	25V	13p
10μF	25V	7p	220μF	40V	15p
10μF	63V	7p	220μF	63V	22p
15μF	16V	7p	330μF	4V	7p
15μF	40V	7p	330μF	10V	8p
15μF	63V	7p	330μF	16V	13p
22μF	10V	7p	330μF	63V	26p
22μF	25V	7p	470μF	6.3V	8p
22μF	63V	7p	470μF	10V	13p
33μF	6.3V	7p	470μF	25V	15p
33μF	16V	7p	470μF	40V	22p
33μF	40V	7p	680μF	6.3V	13p
47μF	4V	7p	680μF	16V	15p
47μF	10V	7p	680μF	25V	22p
47μF	25V	7p	1000μF	40V	26p
47μF	40V	7p	1000μF	4V	13p
47μF	63V	8p	1000μF	10V	15p
68μF	6.3V	7p	1000μF	16V	22p
68μF	16V	7p	1000μF	25V	26p
68μF	63V	13p	1500μF	6.3V	15p
100μF	4V	7p	1500μF	10V	22p
100μF	10V	7p	1500μF	16V	26p
100μF	25V	7p	2200μF	6.3V	22p
100μF	40V	8p	2200μF	10V	26p
100μF	63V	15p	3300μF	6.3V	26p
150μF	6.3V	7p	4700μF	4V	26p
150μF	16V	7p			

VEROBOARD

Size
2½in x 3½in
3½in x 5in
3½in x 3½in
3½in x 5in
17in x 2½in
17in x 3½in

Spot face cutter—43p
Pins, either size, pack of 36—21p

Edge connectors:
24 way, 0.1—37p
24 way, 0.15—37p

36 way, 0.1—48½p
16 way, 0.15—25p

BONDED ACRYLIC FIBRE

B.A.F. wadding, 18in wide, lin thick. The ideal lining for speaker enclosures. 33p per yard. P. & p. 1yd 14p; each extra yard 4p.

CONTROLS

Log. or Lin.
Single, less switch, 15p
Single, D.P. switch, 26p
Tandem, less switch, 44p
5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ

BATTERY ELIMINATORS

suitable for transistor radios and similar light current equipment. Input 240V A.C. Output: PP6—6V D.C.; PP9—9V D.C. Price £1.65 plus 15p p. & p.

CASSETTE OWNERS!

For Philips and similar cassette recorders. PU12 power unit for connection to 12V + or - E cars, giving 7½V stabilised output—£3.55 + 16p p. & p.
PP75 mains power supply, output 7½V D.C.—£2.15 + 16p p. & p.
Both units are complete with cables and 5 pin D.I.N. plug.

CASSETTE MICROPHONE

Low impedance dynamic with remote control switch. Fitted 2½mm and 3½mm jacks. £2.20 plus 15p p. & p.




ELECTROLYTICS

1μF	450V	21p	1000μF	50V	46p
2μF	450V	22p	2000μF	25V	43p
4μF	350V	15½p	2000μF	50V	58p
8μF	450V	18½p	2500μF	25V	50p
16μF	450V	20p	2500μF	50V	66p
25μF	25V	7½p	3000μF	25V	53p
25μF	50V	11p	5000μF	25V	66p
32μF	450V	30p	5000μF	50V	£1.21
50μF	50V	11p	8-8μF	450V	20p
100μF	50V	12p	8-16μF	450V	22p
250μF	25V	15½p	16-16μF	450V	30p
250μF	50V	19p	16-32μF	450V	69p
500μF	25V	20p	32-32μF	450V	54p
500μF	50V	27½p	50-50μF	350V	42p
1000μF	25V	30p			

PLUGS

Car aerial 15p
Co-axial 10p
D.I.N. 2 pin (speaker) 11p
D.I.N. 3 pin 15p
D.I.N. 4 pin 15p
D.I.N. 5 pin, 180° 14p
D.I.N. 5 pin, 240° 16p
D.I.N. 6 pin 16p
Jack, 2½mm unscreened 10p
Jack, 2½mm screened 11p
Jack, 3½mm unscreened 9p
Jack, 3½mm screened 13p
Jack, ¼in unscreened 13p
Jack, ¼in screened 22p
Jack, stereo, unscreened 22p
Jack, stereo, screened 38p
Phono, plastic top 5p
Phono, plated metal 3p
Wander, red or black 3p
Banana 4mm, red or black 6p

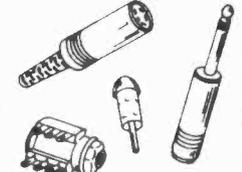

SOCKETS

Car aerial 9p
Co-axial, surface 9p
Co-axial, flush 10p
D.I.N. 2 pin (speaker) 11p
D.I.N. 3 pin 10p
D.I.N. 5 pin, 180° 10p
D.I.N. 5 pin, 240° 10p
Jack, 2½mm 11p
Jack, 3½mm 11p
Jack, ¼in unswitched 16p
Jack, ¼in switched 18p
Jack, stereo, switched 26p
Phono, single 5p
Phono, 2 on a strip 7p
Phono, 3 on a strip 10p
Phono, 4 on a strip 11p
Wander, single, red or black 5p
Wander, twin strip 7p
Banana 4mm red, or black 6p

LINE SOCKETS

Car aerial 15p
Co-axial 10p
D.I.N. 2 pin (speaker) 16p
D.I.N. 3 pin 19p
D.I.N. 5 pin, 180° 17p
D.I.N. 5 pin, 240° 17p
Jack, 3½mm 16p
Jack, ¼in screened 5p
Jack, stereo, screened 37p
Phono, plated metal 15p

CATALOGUE

15p
POST FREE

TRANSFORMERS

all with 0-250 Volt primaries.

Miniature
MM6 6V, 500mA + 6V, 500mA.
MM12 12V, 250mA + 12V, 250mA.
MM20 20V, 150mA + 20V, 150mA.
£1.42 plus 14p p. & p.

L.T.
LT1 6.3V, 1.5A—82p plus 20p p. & p.
LT2 6.3V, 3A—96p plus 20p p. & p.
LT3 12V, 1.5A—96p plus 28p p. & p.
LT4 12V, 3A—£1.76 plus 33p p. & p.
LT5 9-0-9V, 0.5A—83p plus 23p p. & p.
LT6 12-0-12V, 1A—£1.04 plus 29p p. & p.

Multi-tapped
MT30/2 0-12-15-20-24-30V, 2A—£2.15 plus 33p p. & p.
MT60/1 0-5-20-30-40-60V, 1A—£2.31 plus 33p p. & p.
MT60/2 0-5-20-30-40-60V, 2A—£3.25 plus 37p p. & p.

Charger
CT/01 1A—£1.16 plus 28p p. & p.
CT/02 2A—£1.43 plus 33p p. & p.
CT/03 4A—£1.76 plus 33p p. & p.
Secondaries: 0.5-11-17V.
Speaker Matching: 3-8-16Ω
Example: 16Ω speaker to 8Ω amplifier. 99p plus 22p p. & p.

Build yourself a TRANSISTOR RADIO

WITH AFTER SALES SERVICE

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS. MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND.

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Fine tone moving coil speaker. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS


£8.50

P.P. & INS. 50p
(OVERSEAS P. & P. £1)



ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

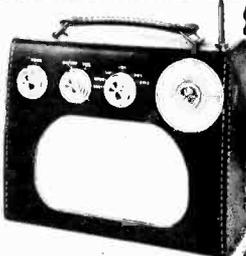

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.


TOTAL BUILDING COSTS **£6.98** P.P. & INS. 45p
(OVERSEAS P. & P. £1)

ROAMER SEVEN Mk. IV

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND.

Extra medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

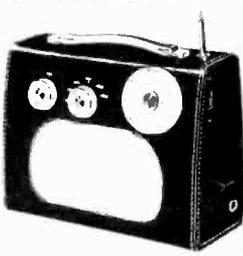TOTAL BUILDING COSTS **£5.98** P.P. & INS. 45p
(OVERSEAS P. & P. £1)




ROAMER SIX

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC.

Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Easy build plans and parts price list 25p (FREE with parts).

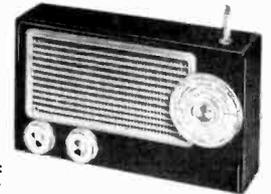
TOTAL BUILDING COSTS **£3.98** P.P. & INS. 30p
(OVERSEAS P. & P. £1)



POCKET FIVE

3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2in x 1 1/2in x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts).

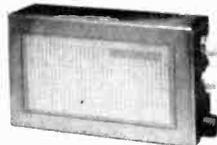TOTAL BUILDING COSTS **£2.29** P.P. & INS. 23p
(OVERSEAS P. & P. 63p)



TRANSONA FIVE

5 TRANSISTORS AND 2 DIODES

3 TUNABLE WAVEBANDS: MW, LW AND TRAWLER BAND. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2in x 4 1/2in x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2.50** P.P. & INS. 24p
(OVERSEAS P. & P. 63p)




TRANS EIGHT

8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

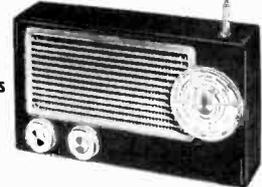TOTAL BUILDING COSTS **£4.48** P.P. & INS. 32p
(OVERSEAS P. & P. £1)



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC. FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 3in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and easy build plans 25p (FREE with parts).

ALL PARTS INCLUDING CASE AND PLANS **£5.50** P.P. & INS. 32p
(OVERSEAS P. & P. £1)

RADIO EXCHANGE LTD

61a HIGH ST., BEDFORD MK40 1SA. Tel. 0234 52367

I enclose £..... please send items marked

- | | | | |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER TEN | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| ROAMER EIGHT | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | ROAMER SIX | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | EDU-KIT | <input type="checkbox"/> |

Parts price list and plans for.....


Name.....

Address.....

P.E. 52

FULL AFTER SALES SERVICE

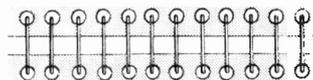★ Callers side entrance "Lavelle" Shop
★ Open 10-1, 2.30-4.30 Monday-Friday, 9-12 Saturday
★ VAT PRICE ADJUSTMENTS AS FROM APRIL 1, 1973



INDUSTRY NOTEBOOK

By Nexus

FIRST AWARDS

The Society of Radio and Electronic Technicians, now almost 6,000 strong, has awarded its first three Honorary Fellowships. Proud recipients were Lord Orr-Ewing, Edwin Spreadbury and Kenneth Tempest, all of whom have played a major role in establishing the Society.

The awards were made at a dinner in The Cholmondeley Room, House of Lords, with this year's SERT president, James Redmond, director of engineering BBC, in the chair. Among the distinguished guests were Sir Eric Eastwood, chief scientist and director of research GEC, and Sir Cyril English, director general of the City and Guilds of London Institute.

Of the three Honorary Fellows it was probably "Spread" who enjoyed the distinction most keenly for it was he who helped in the formation of the Radio Trades Examination Board back in 1941 and, later, as chairman of RTEB, he was instrumental in founding SERT of which he became first chairman.

Lord Orr-Ewing, top man in Ultra Electronics, was first president of SERT in 1966 and gave influential support. Immediate past chairman Kenneth Tempest had the satisfaction of seeing membership pass the 5,000 mark during his term of office.

SERT has not wavered in its policy of insisting on good qualifications for members and thus has helped raise the status of technicians and brought them into the professional class of employment.

The properly qualified electronic technician engineer deserves his

professional status and quite clearly the work of SERT and the IEETE (which caters more broadly for the electrical technician engineer although many members are in electronics) is important in establishing a better business and industrial status for members.

MAGIC MILLION

A million pounds is a nice round figure for turnover—indeed a magic figure to aim at for those with the guts to go it alone without benefit of shelter from working within a big group.

Bill Coates, top man in Leicester-based component distributor Townsend-Coates gets his taste of magic this year. He started up in 1961 with a first year sales turnover of £2,500, largely to local concerns. Now he has a staff of 46, stocks 16,000 different items from nearly a dozen manufacturers and sells on a nation-wide basis.

Two go-it-aloners who are working on the magic million, although still with some way to go, are Ray Vincent and Jim Griffith. In 1966 they took over ailing Plastronics Ltd., at Watford, a moulding and sub-assembly shop serving the electronics industry. Staff today is 40 after a move to new premises in 1969 and, says Jim, it will be necessary to make another move for expansion before long.

Among the more important customers for Plastronic moulded products are Garrard, BSR, British Radio Corporation, Lotus cars and Scammell lorries. The computer industry is also a big customer.

EXHIBITION NEWS

The first commercial full scale exhibition and conference on Automatic Testing Equipment—fastest growing sector of the instrument industry—will take place at the popular Metropole Convention Centre, Brighton, opening on November 26. Stands are already being booked by leading manufacturers and a call for papers has gone out.

Microwave 73, also at the Metropole is a sell-out. It will be opened officially on June 19 by His Royal Highness the Duke of Kent in his capacity as a member of the National Electronics Council and a Companion of the IERE.

Sir Gerald Narbarro is to hop over to the USA to open Coil Winding-Chicago 73 organised by British-based Electromation Exhibitions Ltd. and opening on March 27. Sir Gerald is first president of the International Coil Winding Association.

The International London Electronic Components Show opening at Olympia on May 22 is to have 350 exhibitors. Biggest stand is occupied by a consortium of

French companies who are clearly determined to cash in on the opportunities of the enlarged EEC.

The Soviet Union will be showing valves, passive components and test gear through British agents Z & I Aero Services. Previous showings of Russian components both in the UK and France have left me totally unimpressed—perhaps there will be more of interest this year.

BIPOLAR PROCESS

Plessey's Bipolar Process III technology for integrated circuits has now moved from pilot production at the Allen Clark Research Centre at Caswell, to full production at the main semiconductor plant at Swindon:

Whole families of new devices have been planned and with higher speeds now available a new range of applications has been opened up. Among the first commercially available products are high speed dividers capable of accepting an input of 1.2GHz, and a range of logic circuits compatible with Motorola's MECL III range. Selected variants, say Plessey, have a considerable performance gain over standard MECL III.

The production technique uses an epitaxial layer only 4 microns thick with emitter-base and base-collector junctions well under a micron deep. This is obviously not a cheap process but every milestone on the path to improved performance must exact its price.

HALF CENTURY

Eddystone Radio is approaching its 50th birthday with record growth and a firmer policy than it has had for years. Eddystone's Big Three, managing director Dick Carroll, chief engineer Bill Cooke, and sales manager Ken Wilkins are now dedicated to total solid state equipment and minimum production targets of 10,000 receivers on any new models.

The last of the Eddystone valve receivers, the popular 830, has been delivered and is being superseded by the new solid state 1830 range of general purpose receivers which have already won full approval from the British and a number of other PTT administrations.

During a visit to Eddystone's Birmingham works, I was told that the 958 Series of high-stability receivers, of which over 1,000 have now been delivered, is now available in nine versions. What has given Eddystone this flexibility in production is a big switch to modular construction and this has also had its effect on manufacturing and testing methods.

Designing with Integrated Circuits

BY A. FOORD

7

Counters and Displays

WE HAVE spoken in general about digital instrumentation and counters and this month will consider how the counters can be constructed. We will first examine in detail the individual integrated circuits used in a typical decade counter.

SN7490N DECADE COUNTER

The SN7490N consists of four master-slave bistables internally interconnected to provide a divide-by-five and a divide-by-two counter. There are also gated direct reset lines to inhibit the count inputs and return all the outputs to a logical 0 or binary coded decimal (BCD) count of nine.

The output from the first bistable is not internally connected to the next stage, and so three different count modes are possible, Fig. 7.1.

1. The BD input is externally connected to the A output, and the A input receives the incoming count. A count sequence is obtained as shown in the truth table. The outputs can be reset to a conventional zero or to a BCD count of nine for nines complement decimal applications.
2. Where a symmetrical divide-by-ten count is required (the previous arrangement divides by ten, but not symmetrically) the D output is connected to the A input. The input count is applied

to the BD input and a divided-by-ten symmetrical square wave is obtained at the A output. The circuit thus divides by five first and then by two.

3. For divide-by-two and divide-by-five operations the two counters can be used independently. Bistable A is used to divide-by-two while the BD input is used to obtain a divide-by-five operation at the B, C, and D outputs. However the

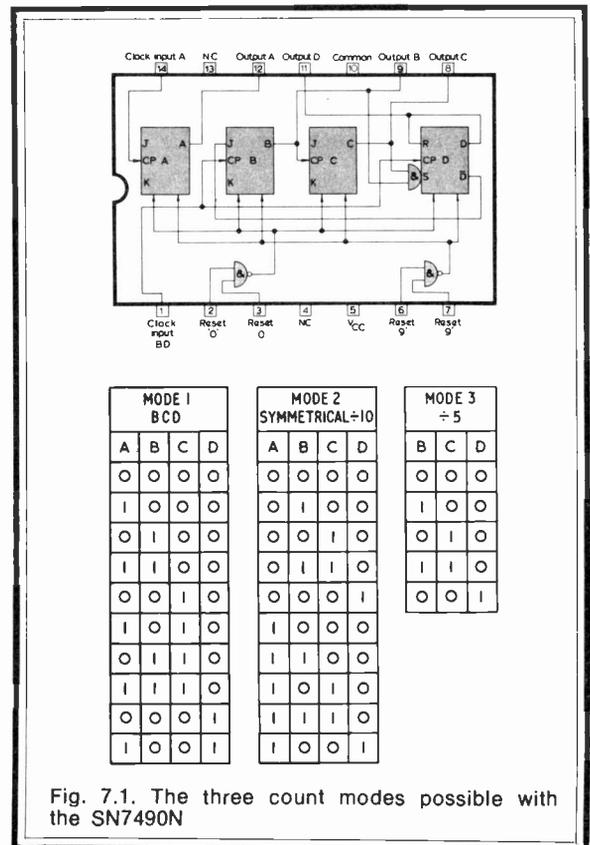


Fig. 7.1. The three count modes possible with the SN7490N

BINARY CODED DECIMAL

A binary numbering system for coding decimal numbers in groups of four bits. The binary value of these four-bit groups ranges from 0000 to 1001 and codes the decimal digits 0 to 9. To count to 9 takes four bits, to count to 99 takes two groups of four bits, etc.

RESET

Also called clear. It is an input which makes the output go to a desired state, usually 0 or 9.

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T. FAIR-CHILD



Type	1/11	12/24	26/99	Type	1/11	12/24	26/99	Type	1/11	12/24	26/99
SN7400	0.20	0.18	0.16	SN7450	0.20	0.18	0.16	SN74145	1.50	1.40	1.30
SN7401	0.20	0.18	0.16	SN7451	0.20	0.18	0.16	SN74150	3.85	2.95	2.15
SN7402	0.20	0.18	0.16	SN7453	0.20	0.18	0.16	SN74151	1.10	0.95	0.90
SN7403	0.20	0.18	0.16	SN7454	0.20	0.18	0.16	SN74153	1.85	1.27	1.20
SN7404	0.20	0.18	0.16	SN7460	0.20	0.18	0.16	SN74154	2.90	1.77	1.55
SN7405	0.20	0.18	0.16	SN7470	0.30	0.27	0.25	SN74155	1.55	1.47	1.35
SN7406	0.30	0.27	0.25	SN7472	0.30	0.27	0.25	SN74156	1.55	1.47	1.35
SN7407	0.30	0.27	0.25	SN7473	0.40	0.37	0.35	SN74167	1.80	1.70	1.55
SN7408	0.20	0.19	0.18	SN7474	0.40	0.37	0.35	SN74160	2.60	2.40	2.25
SN7409	0.45	0.42	0.35	SN7475	0.65	0.62	0.50	SN74161	2.60	2.40	2.25
SN7410	0.20	0.18	0.16	SN7476	0.45	0.42	0.39	SN74162	3.40	3.25	2.70
SN7411	0.25	0.24	0.20	SN7477	0.60	0.58	0.49	SN74163	3.40	3.25	2.70
SN7412	0.42	0.40	0.35	SN7478	0.75	0.72	0.67	SN74174	1.55	1.47	1.35
SN7413	0.30	0.27	0.25	SN7481	1.25	1.15	1.10	SN74165	4.00	3.80	3.00
SN7414	0.30	0.27	0.25	SN7482	0.87	0.80	0.70	SN74166	4.00	3.80	3.00
SN7416	0.30	0.27	0.25	SN7483	1.00	0.90	0.85	SN74168	4.00	3.80	3.00
SN7417	0.30	0.27	0.25	SN7484	1.00	0.90	0.85	SN74169	6.25	5.00	5.10
SN7420	0.20	0.18	0.16	SN7486	0.45	0.41	0.38	SN74170	4.10	3.55	3.05
SN7421	0.48	0.44	0.40	SN7490	0.75	0.70	0.65	SN74171	2.00	1.75	1.80
SN7422	0.48	0.44	0.40	SN7491	0.60	0.55	0.50	SN74172	1.35	1.27	1.15
SN7425	0.48	0.40	0.35	SN7492	0.75	0.70	0.65	SN74176	1.50	1.40	1.20
SN7427	0.42	0.39	0.35	SN7493	0.75	0.70	0.65	SN74177	1.80	1.35	1.20
SN7428	0.50	0.45	0.42	SN7494	0.80	0.75	0.70	SN74180	1.55	1.30	1.20
SN7430	0.20	0.18	0.16	SN7495	0.80	0.75	0.70	SN74181	7.00	6.00	5.50
SN7432	0.42	0.39	0.35	SN7496	1.00	0.97	0.95	SN74182	2.00	1.80	1.60
SN7433	0.70	0.61	0.44	SN7497	6.25	5.50	5.00	SN74184	2.40	2.00	1.80
SN7437	0.70	0.61	0.44	SN7498	0.60	0.50	0.40	SN74185A	2.40	2.00	1.80
SN7438	0.65	0.60	0.50	SN7499	1.45	1.15	1.10	SN74189	1.45	1.15	1.10
SN7440	0.20	0.18	0.16	SN74101	1.45	1.35	1.20	SN74191	1.95	1.85	1.75
SN7441AN	0.75	0.72	0.70	SN74107	0.50	0.45	0.40	SN74192	2.00	1.90	1.80
SN7442	0.75	0.72	0.70	SN74110	0.80	0.70	0.60	SN74193	2.00	1.90	1.80
SN7443	1.00	0.95	0.90	SN74118	1.00	0.95	0.90	SN74194	2.50	2.25	1.90
SN7445	2.00	1.75	1.60	SN74119	1.90	1.78	1.65	SN74195	1.85	1.70	1.60
SN7446	2.00	1.75	1.60	SN74121	0.60	0.55	0.50	SN74196	1.50	1.40	1.30
SN7447	1.75	1.60	1.45	SN74122	1.35	1.15	1.10	SN74197	1.50	1.40	1.30
SN7448	1.75	1.60	1.45	SN74123	2.70	2.55	2.47	SN74198	4.60	3.70	3.35
				SN74141	1.00	0.95	0.90	SN74199	4.60	3.70	3.35

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
LARGER QUANTITY PRICES PHONE (01) 402 4891
HIGH POWER SN 74 000 } Now in stock—send for list No. 36
LOW POWER SM 74 000 }

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AAY30 10p	BC147 12p	BU105 2.25	OC44 15p	TI843 35p	2N3055 55p
AAZ12 10p	BC189C 12p	BY100 15p	OC45 15p	V405A 15p	2N3440 75p
AZ107 10p	BC182 10p	BY126 15p	OC57 50p	ZTX108 12p	2N3442 75p
AC107 35p	BC214 15p	BY127 15p	OC71 15p	ZTX300 12p	2N3525 75p
AC126 25p	BCY32 75p	BYZ13 35p	OC72 25p	ZTX301 15p	2N3614 50p
AC127 25p	BCY34 35p	C106D 65p	OC77 45p	ZTX302 18p	2N3615 75p
AC128 25p	BCY39 1.00	GET111 55p	OC81 25p	ZTX341 20p	2N3702 10p
AC176 25p	BCY42 30p	GET115 55p	OC83 25p	ZTX500 15p	2N3704 10p
AC187 25p	BCY43 25p	GET880 45p	OC140 55p	ZTX503 17p	2N3705 10p
AC188 25p	BCY55 2.50	LM309K	OC170 25p	ZG301 30p	2N3714 1.80
ACY17 30p	BCY70 15p	(T03) 1.87	OC171 30p	2N404 20p	2N3771 1.75
ACY20 20p	BCY71 20p	MAT121 25p	OC200 45p	2N427 35p	2N3773 2.00
ACY21 20p	BCY72 15p	MJE340 50p	OC201 75p	2N496 15p	2N3790 2.25
ACY39 55p	BCY87 2.99	MJE370 75p	OC202 80p	2N497 15p	2N3819 35p
AD140 50p	BD121 50p	MJE520 75p	OC203 50p	2N706 10p	2N3820 50p
AD149 50p	BD124 80p	MJE2935	OCP71 1.25	2N930 20p	2N3866 85p
AD161 35p	BD131 75p	1.10	ORP12 50p	2N987 45p	2N3903 15p
AD162 35p	BD132 80p	MJE3055	ORP60 40p	2N1131 25p	2N3906 12p
AF117 20p	BF115 25p	75p	P346A 20p	2N1132 25p	2N4061 12p
AF118 50p	BF167 25p	MFF105 40p	RA8308AF	2N1132 18p	2N4062 12p
AF124 25p	BF173 25p	NKT214 20p	2N1304 22p	2N1304 22p	2N4196 15p
AF139 30p	BF179 30p	NKT216 40p	RA8508AF	2N1305 22p	2N4871 35p
AF186 40p	BF180 30p	NKT217 40p	55p	2N1307 25p	2N5457 30p
AF239 40p	BF194 15p	NKT403 70p	TAA263 75p	2N1308 25p	2N5777 55p
ASY27 30p	BF195 15p	NKT404 60p	TAL209 39p	2N1613 20p	28001 1.00
ASY29 25p	BF861 25p	OA10 50p	TIP29A 50p	2N1671 1.00	28012 10.00
BA102 30p	BF898 25p	OA10 50p	TIP30A 80p	2N2147 75p	28018 6.25
BA115 7p	BFX13 25p	OA81 10p	TIP31A 60p	2N2160 58p	28026 8.90
BA145 15p	BFX34 75p	OA91 7p	TIP32A 70p	2N2217 25p	28301 50p
BA133 5p	BFX37 30p	OA200 7p	TIP33A	2N2221 20p	28303 65p
BA136 7p	BFX88 20p	OA202 10p	1.00	2N2222A	28324 95p
BC107 10p	BFY50 20p	OC16 78p	TIP34A	25p	40250 50p
BC108 15p	BFY51 20p	OC19 95p	1.50	2N2368A	40300 40p
BC109 10p	BFY52 20p	OC23 85p	TIP35A	1.50	40361 60p
BC109C 12p	BFY64 60p	OC25 40p	2.50	2N2906 20p	40382 50p
BC113 15p	BFY90 80p	OC28 65p	TIP36A	2N2926 (all	40408 50p
BC117 20p	BYL36 5.00	OC35 50p	3.00	cols)	40486 75p
BC143 35p	BXK20 15p	OC36 85p	TIP41A 75p	2N3053 20p	40636 1.10
	BYZ27 15p	OC42 40p	TIP42A 85p	2N3054 50p	40430 1.00

QUANTITY DISCOUNTS

10% 12+ : 15% 25+ : ANY ONE TYPE
20% 100+ : 25% 250+
From above sections except Integrated Circuits and Special Offers where discounts are included.
Minimum order value £1 please.
Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90	59p	2N2926	10p
1000 MC/S		All Colours	
25 + 20p		25 + 9p	
100 + 17p		100 + 8p	
500 + 13p		500 + 6p	
		1000 + 5p	
AF117 Mullard 25p		2N3819 Texas 35p	
25 + 17p		25 + 30p	
100 + 15p		100 + 25p	
500 + 12p		500 + 20p	
		1000 + 15p	
OC170 Mullard 25p		BC107, BC108, BC109 10p each	
25 + 20p		All Makes	
100 + 18p		25 + 8p	
500 + 13p		100 + 7p	
1000 + 13p		500 + 6p	
		1000 + 5p	
BY127 Mullard 15p		ADI61, AD162 35p each	
25 + 12p		25 + 32p	
100 + 10p		100 + 28p	
500 + 9p		500 + 25p	
1000 + 8p		1000 + 22p	
OA202 10p		2N3053 20p	
100 + 8p		25 + 18p	
500 + 7p		100 + 15p	
1000 + 5p		500 + 12p	
		1000 + 10p	
OC35 Mullard 50p		2N3055 55p	
25 + 45p		25 + 50p	
100 + 40p		100 + 45p	
500 + 35p		500 + 38p	
1000 + 30p		1000 + 33p	

ZENER DIODES

400 M/W 5%
Miniature
BZY 88 Range
All voltages
3-3-33 Volt
10p each.
25 + 9p
100 + 8p
500 + 8.5p
1000 + 6p
Any one type.

1 1/2 Watt 5%
Wire Ends
Metal Case
All voltages
6-8-10 Volt
20p each
25 + 18p
100 + 16p
500 + 12p
1000 + 10p
Any one type.

3 Watt Plastic
Wire Ends 5%
3EZ Range
All voltages
6-8-10 Volt
30p each.

SILICON RECTIFIERS WIRE ENDED PLASTIC

Type P.I.V. 1-11
1 amp miniature
IN4001 50 6
IN4002 100 7
IN4003 200 8
IN4004 400 8
IN4005 600 10
IN4006 800 12
IN4007 1000 15
1-5 amp miniature
PL4001 50 8
PL4002 100 9
PL4003 200 10
PL4004 400 10
PL4005 600 12
PL4006 800 15
PL4007 1000 16

LINEAR (O/P AMPS)

702C T05 75p
709C T09 35p
709C D.I.L. 85p
723C T099 £1.00
723C D.I.L. 95p
725C T099 £4.50
741C T099 55p
741C D.I.L. 55p
747C T099 £1.10
747C D.I.L. £1.10
72741P D.I.L. 60p
72748P D.I.L. 60p
SINCLAIR IC12 £1.80
TOSHIBA TH9013P
20 WATT AMP
£4.47 POST PAID
TH9014P Pre Amp
£1.50

DATA AND CIRCUITS REF. 42 10p
FREE WITH PURCHASES

TRANSISTORS, IC's, TRIACS, BRIDGES, SCR's, LDR's

ALL VOLTAGES
6-8-10 Volt
30p each.

PLESSEY INTEGRATED CIRCUIT
3 Watt Amplifier BL403 D
Complete with 8-page booklet, circuits and data
£1.50 each


TRIACS
STUD WITH ACCESSORIES

Type	Volts	Price
P.I.V.		1-11
3 AMP RANGE		
BC35A	100	75p
BC35B	200	79p
BC35D	400	85p
6 AMP RANGE (T048)		
SC		



"Where can I get exclusive units at lowest prices?..."

ROC ELECTRONICS!

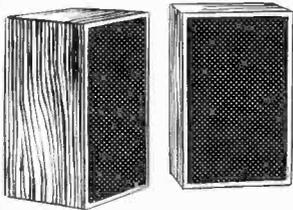

R.088 MATCHED STEREO LOUD SPEAKERS. Here's real value in stereo speakers! Each unit comes complete with 10-foot lead and phono plug, and look really smart. Power handling per speaker: 4 watts rms, 8 watts peak. Frequency range: 40-16,000 Hz. Flux density: 8,500 gauss. Impedance: 8 ohms. Dimensions: 9" high, 5 1/2" wide, 4 1/2" deep. Finish: oiled walnut. **ROC PRICE £9.50 pair.** Normal Price £10.75

REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500

A superb hi-fi amplifier with all the features you've ever wanted - for under £46.00. Saving over £10.00 on the normal retail value. Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push-button input controls - magnetic phono (high/low) tuner, aux. mono, monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz \pm 1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA, tuner/aux 250mV. Hum and noise: phono - 50db, tuner/aux - 65db. How's that for a specification! Size 14 1/2" wide, 3 1/2" high, 10 1/2" deep.



As reviewed in "POPULAR HI-FI" February 1972

ROC PRICE £35.20
Normal Price £55.50



OLSON RA-310 AM/FM/MPX STEREO TUNER

This ROC Tuner is especially designed to match the Olson AM-395 Stereo Amplifier. In price and value, as well as its good looking design! But of course it's also the RA-310 costs £10.00 less than the normal retail value, and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM: 87-108 MHz, AM: 525-1605 kHz. FM Sensitivity: FM: 3µV, AM: 250µV. Stereo separation 30dB at 1kHz, image rejection 60dB. Size: 11 1/2" wide, 4" high, 7 1/2" deep.

ROC PRICE £31.20
Normal Price £50.00




REALISTIC SA-100B 6-WATT STEREO AMPLIFIER

Here's fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide, 3" high, 5 1/2" deep. And yet it has separate ganged volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/tuner and power on/off slide switches. The ends are oiled walnut, with matching enamelled metal top. The front panel is satin aluminium and walnut-brown. Frequency response is 50 to 10,000 Hz \pm 3dB. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.

ROC PRICE £12.45
Normal Price £21.00

SPECIAL OFFER!

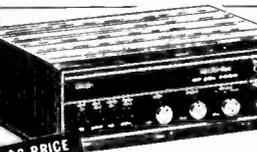TEC HI-IMP HEADPHONE RADIO
When you want to listen to the radio all by yourself then this will solve the problem. Separate volume and tuning controls with easy-to-use knobs. Frequency range is 535 to 1605 kHz medium wave band. Maximum output is 300 mW. **Normal Price £7.65 ROC PRICE £5.00**



EAGLE LC.07 STEREO MOVING-MAGNET CARTRIDGE

Here's your opportunity to own a transcription cartridge for the price of a ceramic! It is specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance \pm 1dB. Channel separation: 28dB. Compliance: 12 x 10⁻⁶ cm/dyne. **ROC PRICE £8.37**



OLSON AM-395 40-WATT STEREO AMPLIFIER

An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the AM-395 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for taping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble tones when listening at low output levels. Frequency response: 20-20,000 Hz \pm 3dB. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3.0mV RIAA, crystal phono 100mV, tape 160mV, tuner: 180mV. Size 11 1/2" wide, 4" high, 7 1/2" deep. The specification reads well - sounds even better!

ROC PRICE £24.10
Normal Price £39.50



A-3000 36-WATT SOLID STATE STEREO AMPLIFIER
The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front - all the controls you're ever likely to need plus a headphone socket. On the rear - signal inputs, speaker outputs and a line fuse for circuit protection. Specifications: 18 watts rms per channel into 8 ohms. Frequency response 20-35,000 Hz (\pm 2db) Inputs: Magnetic, Ceramic, Tuner, Tape, Aux. Tape Play. Size: 345mm x 300mm x 130mm.

ROC PRICE £28.00
Normal Price £45.70



OLSON AM400 4-WATT STEREO AMPLIFIER
Here's marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for turntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz \pm 3dB. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV, tuner/aux 80mV. Size 8" wide, 2 1/2" high, 4 1/2" wide.

ROC PRICE £10.50
Normal Price £15.70



25-WATT 3-WAY CHRYSLER 'LIVING AUDIO' SPEAKER CE-50
This high quality speaker has its own built-in 3-way sound response switch, giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units on 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s. into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10 1/2" x 7 1/2" x 8 1/2". Exactly right for matching the most modern decor.

ROC PRICE £27.25
Normal Price £39.95 each.



PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-10
This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received - that's the time to switch to 'Stereo'! The SSA-10 has all the facilities you'd expect to find on tuners costing twice as much - separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz, AM 535-1605 kHz. Frequency response: 50-10,000 Hz \pm 3dB. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4 1/2" high, 8" deep.

ROC PRICE £27.55
Normal Price £42.00


CONSTRUCTORS' KITS

TWO TRANSISTOR RADIO KIT
Complete with solar cell **£2.50**

10 PROJECT INTEGRATED CIRCUIT KIT
Build a radio, Morse key, etc. **£3.50**

SOLAR ELECTRONIC KIT
20 ways of harnessing the sun's energy **£4.50**

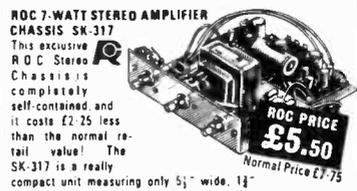TWO OCTAVE ELECTRONIC ORGAN KIT
Make your own music. Complete with speaker **£4.50**




ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317
This exclusive ROC Stereo Chassis is completely self-contained, and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5 1/2" wide, 1 1/2" high and 8 1/2" deep. It contains its own mains power supply, and has a ganged volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz \pm 3dB, output 3.5 watts music power per channel into 8 ohms. Input, phono, 600mV, signal-to-noise ratio better than 45dB.

ROC PRICE £5.50
Normal Price £7.75



R.446 3-WAY MATCHED SPEAKERS
These will do justice to your amplifier - and to your pocket. At only £20.00 a pair, they are real value-for-money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a 6 1/2" base unit plus tweeter. Frequency range: 40 to 18,000 Hz. Size 14" high, 9" wide, 6 1/2" deep.

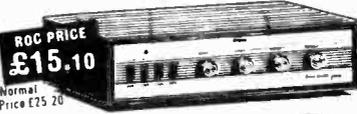ROC PRICE £20.00
Normal Price £27.00 per pair.



OLSON AM-372 16-WATT STEREO AMPLIFIER
Here's a really good amplifier at a really down-to-earth price - nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you - reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones, and tape recorders. Frequency response is 30 to 20,000 Hz \pm 3dB. Output 16 watts r.m.s. per channel music power into 8 ohm speakers. P-ono input 200mV. Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.

ROC PRICE £15.10
Normal Price £25.20

ROC ELECTRONICS LTD
N. JORY Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211
CALLERS WELCOME 9-6 MON. TO SAT.
ALSO AT 87 TOTTENHAM COURT RD, LONDON W1
TEL: 01-580 3739 OPEN 9-6 MON.-FRI. SAT. 9-1



Return-of-post mail order service from Edgware Road. Orders over £10 post free (UK only). Add 25p for p & p to orders under £10. HP terms available for callers.

counters are reset simultaneously because the reset lines are common.

SN7475N QUADRUPLE BISTABLE LATCH

The SN7475N is a bistable latch which is used as a temporary store for binary information, Fig. 7.2. Information which is present at a data input (D)

is transferred to the Q output while the clock is high. The Q output follows the data for as long as the clock is high but the last information is retained at the data output when the clock goes low.

SN74141N DECODER-DRIVER

The SN74141N is one of several decoder-drivers available in the TTL range and is designed to drive

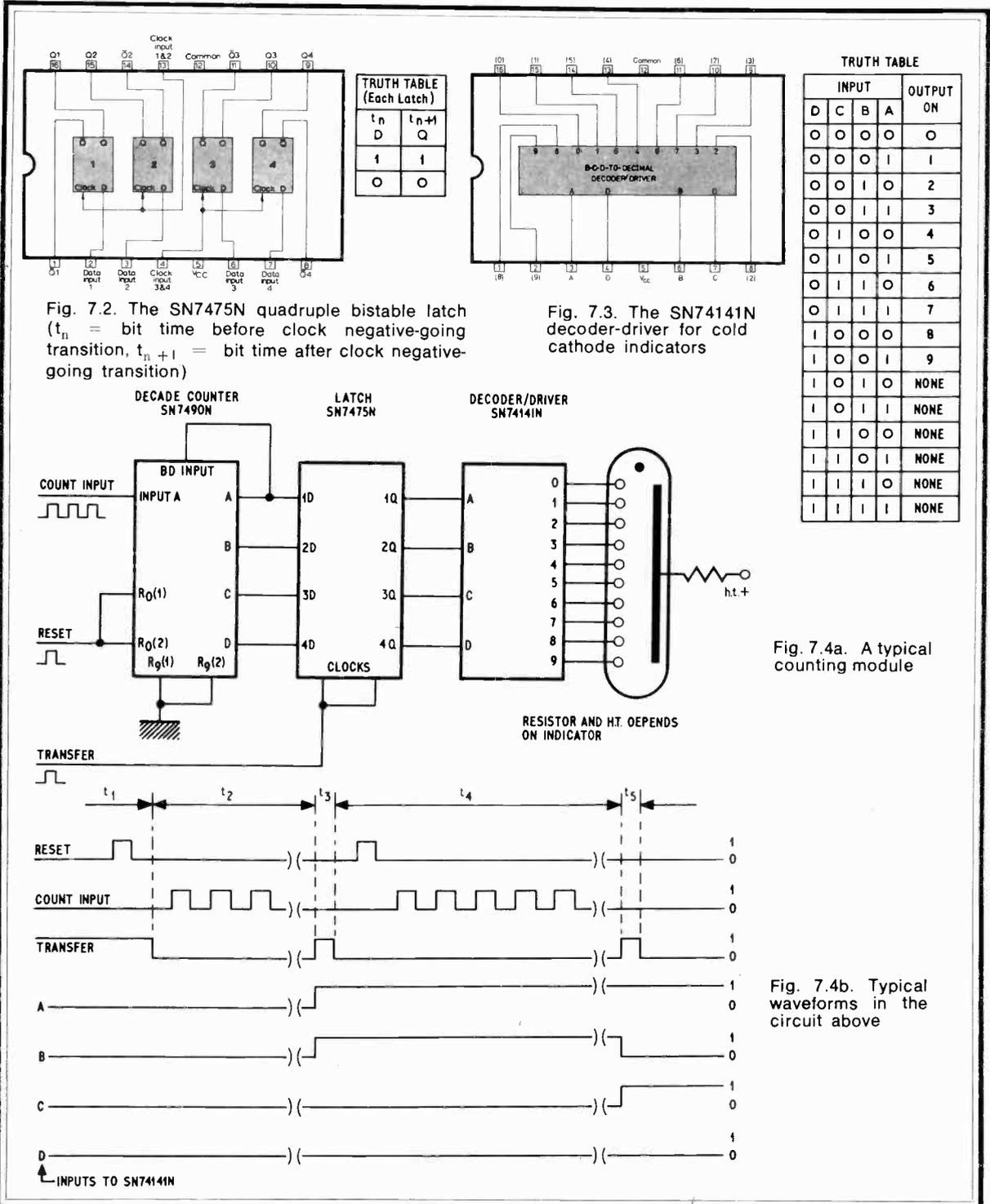


Fig. 7.4a. A typical counting module

Fig. 7.4b. Typical waveforms in the circuit above

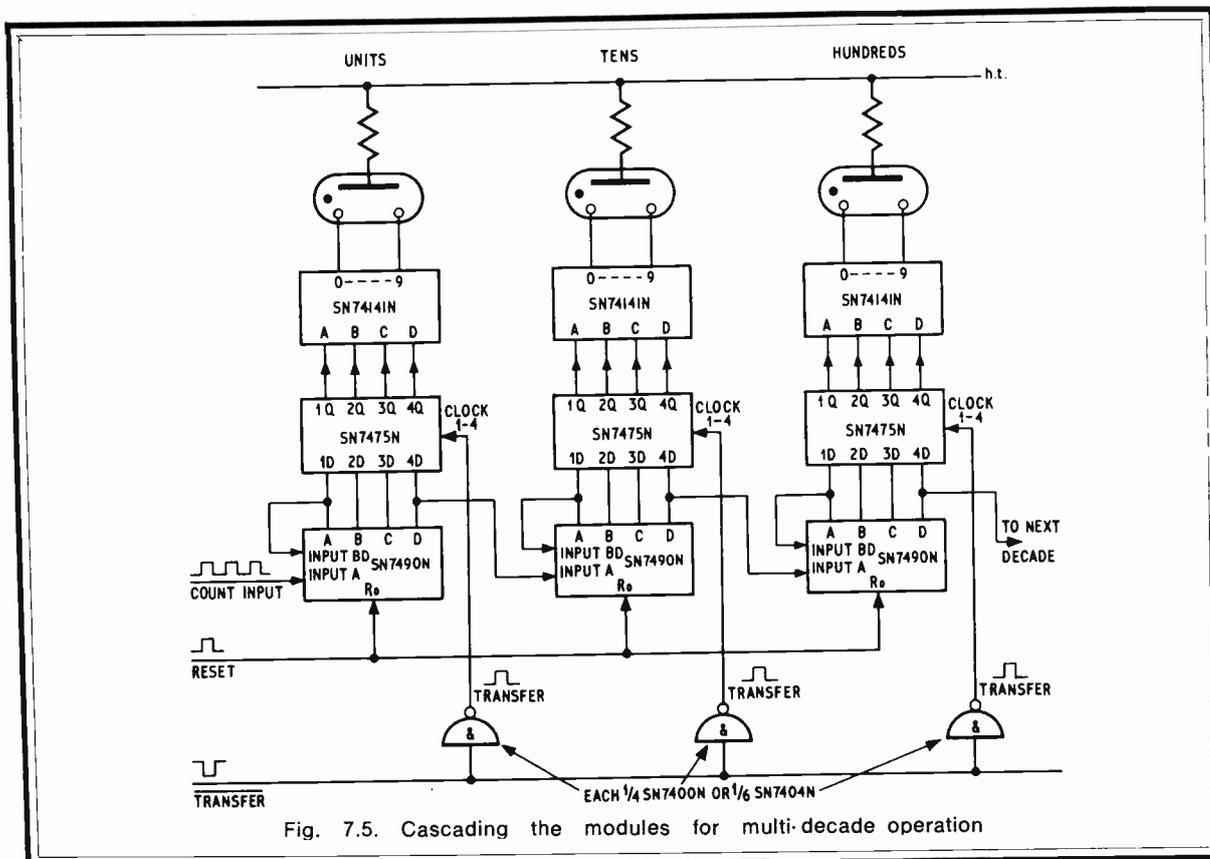


Fig. 7.5. Cascading the modules for multi-decade operation

cold cathode indicator tubes. It accepts a BCD input which it decodes to drive the cathodes of an indicator tube without the need for external components, as in Fig. 7.3.

SINGLE COUNTER MODULE

A typical application for a single counting module is shown in Figs. 7.4a, b, with the counting sequence.

- (a) During t_1 the decade counter is reset to 0.
- (b) During t_2 a BCD count of three is available at the output of the SN7490N, but the indicator still displays 0.
- (c) At the start of t_3 the indicator will display 3, and at the end of t_3 the BCD count of three is committed to the memory of the SN7475N. The decade counter is free to count again.
- (d) During t_4 the decade counter is reset to 0 and will then repeat the cycle to display five.

For multi-decade operations the modules may be cascaded as shown in Fig. 7.5.

PRACTICAL DETAILS

For those constructors who wish to experiment with these applications, R.S. Components produce the three integrated circuits, a printed circuit board, and the indicator tube.

The 5V logic supply and the h.t. can be derived from a transformer which gives 6.3 volts and 250 volts.

For testing purposes the reset and transfer lines may be derived from switches, and the input signal derived from a Schmitt trigger SN7413N oscillator.

FAN-IN PROBLEMS

(a) RESET (SN7490)

The reset line of the SN7490 can have a fan-in of one if the other reset input is returned to V_{CC} , so that an SN7400 (fan-out of 10) can drive an adequate number of decades.

(b) COUNT INPUTS (SN7490)

The A or BD inputs of the SN7490 can be driven from an SN7400.

(c) TRANSFER CLOCK (SN7475)

The transfer line of each SN7475 has a fan-in of eight (two per latch). The solution is to use one quarter of an SN7400 for each SN7475 package or to use a buffer (such as the SN7437 or SN7440) which has a fan-out of 30.

CONCLUSION

This article has shown how three integrated circuits can be used to interface with cold cathode indicator tubes. Where the intermediate outputs are not required the new SN74142N combines these three circuits into one 16 pin dual-in-line package, with a considerable space saving.

For driving displays other than cold cathode indicators the SN74141N would be replaced by one of the other drivers in the range. Although seven segment indicators (for example) are popular because they only need a 5V rail, cold cathode indicator tubes are still preferred by many people, since the required h.t. is not difficult to provide.

ZN414 £1.25 POST FREE
 The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.

I.C. Sockets
 Dual in-line or Zig Zag (Quil) 14 and 16 pin
 Our Price 1p per pin

VDR's & Thermistors

A15B	75p	GL23	£1.00	VA1005	15p
C21	15p	R53	£1.32	VA1026	13p
C24	13p	R54	£1.46	VA1033	13p
C213A	13p			VA1040	10p
E298 ED/A258	10p			VA1053	10p
E298 ZZ/06	10p			VA1055S	10p
GL16	£1			VA1034	10p

Potentiometers

5KΩ 50KΩ 500KΩ
 10KΩ 100KΩ 1MΩ
 25KΩ 250KΩ 2MΩ

log or lin less switch (& 1KΩ lin) 12p
 log or lin with switch 24p
 dual less switch 40p
 dual with switch 10K, 100K & 1M log only 52p
 10K log - 10K antilog less switch 40p

Capacitors

dise ceramic	low voltage		
01μF 18v	5p	0.1μF 30v	5p
0.22μF 18v	5p	0.22μF 6v	5p
0.47μF 12v	5p	0.47μF 3v	5p
ceramic plate	30V		
1000pf	10p	4700pf	10p
2200pf	10p	10,000pf	10p

Slider Pots

Single	Dual	log
10K	10 + 10K	or
25K	25 + 25K	lin
50K	50 + 50K	
100K	100 + 100K	Knobs
30p	50p	10p

Resistors

1/2 watt 5% Carbon Film - low noise Hi-Stabs

All E24 values 1p each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct 33% for 100 of one type or 25% for mixed orders over £1 in value.

1 W 10% Carbon Composition 3p each
 2 W 10% Carbon Composition 6p each
 2 1/2 W 5% Wire wound 9p each
 5 W Wire wound 9p each
 10 W Wire wound 10p each
 plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25.

Eliminators

9 volt @ 20mA (PP3) £1.25
 6 volt @ 50mA £1.50
 9 volt @ 50mA £1.50
 6 - 6 volt, 50mA £2.50
 9 - 9 volt, 50mA £2.50
 7 1/2 volt for cassette recorders £3.00
 6 7/8 or 9 volt £3.00
 3, 4 1/2, 6, 7 1/2, 9, 12 or 500mA (illus.) £3.99
 Car Battery Converter fully stabilised to provide 6, 7 1/2 or 9 volts (p. & p. 15p on all types) £4.99

Ceramic - plate 63V (C333)

1 8pf	33pf	120pf
2 2pf	10pf	39pf
3 3pf	1 1/2pf	47pf
3 9pf	15pf	56pf
4 7pf	18pf	68pf
5 6pf	22pf	82pf
6 8pf	27pf	100pf

all 5p. each

NEW LISTS

LOUDSPEAKERS No. 4
COILS AND INDUCTORS No. 5
TRANSFORMERS No. 6
 (postage 5p)

SGS

EA1000

3 Watt Audio Amplifier

Our Price Inc. handbook £2.49

Presets

Vertical or Horizontal

0.1 watt 5p	0.25 watt 7p		
1 1K 1/2	10K 1/2	100K 1/2	1M 1/2
250	2.5K 1/2	25K 1/2	250K 1/2
500	5K 1/2	50K 1/2	500K 1/2

mylar film 100V

1000pf 2p	0.1μF 3p	0.68μF 4p
2000pf 2p	0.2μF 3p	1μF 5p
5000pf 2p	0.4μF 3p	2μF 5p
	0.5μF 3p	

Diodes & Rectifiers

AA119 9p	BA156 15p	BY176 £1.50
AA120 9p	BA243 56p	BY182 £1.50
AA129 9p	OA47 10p	BY250 23p
BA102 25p	OA79 9p	IN4001 8p
BA115 17p	OA90 7p	IN4002 7p
BA130 10p	OA91 7p	IN4003 8p
BA145 20p	OA200 10p	IN4004 8p
BA148 20p	BY100 15p	IN4005 10p
BA154 13p	BY126 15p	IN4006 12p
BA155 14p	BY127 15p	IN4007 15p

SGS

EA1000

3 Watt Audio Amplifier

Our Price Inc. handbook £2.49

Eliminators

9 volt @ 20mA (PP3) £1.25
 6 volt @ 50mA £1.50
 9 volt @ 50mA £1.50
 6 - 6 volt, 50mA £2.50
 9 - 9 volt, 50mA £2.50
 7 1/2 volt for cassette recorders £3.00
 6 7/8 or 9 volt £3.00
 3, 4 1/2, 6, 7 1/2, 9, 12 or 500mA (illus.) £3.99
 Car Battery Converter fully stabilised to provide 6, 7 1/2 or 9 volts (p. & p. 15p on all types) £4.99

polystyrene 160V

10pf to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. 3p each

metallised polyester 250V (C280)

0.1μF 3p	0.68μF 3p	47μF 8p
0.15μF 3p	1μF 4p	68μF 11p
0.22μF 3p	1.5μF 4p	1μF 13p
0.33μF 3p	2.2μF 5p	1.5μF 20p
0.47μF 3p	3.3μF 6p	2.2μF 24p

FM TUNER chassis fully transistorised 9 volt operation. OUR PRICE £6.25

Matching stereo decoder £4.97 Ask for model list No. 11

SGS

EA1000

3 Watt Audio Amplifier

Our Price Inc. handbook £2.49

Presets

Vertical or Horizontal

0.1 watt 5p	0.25 watt 7p		
1 1K 1/2	10K 1/2	100K 1/2	1M 1/2
250	2.5K 1/2	25K 1/2	250K 1/2
500	5K 1/2	50K 1/2	500K 1/2

metallised polyester 400V (C281)

0.1μF 4 1/2p	0.47μF 6p	2.2μF 10p
0.15μF 4 1/2p	0.68μF 6p	3.3μF 14p
0.22μF 4 1/2p	1μF 7p	4.7μF 15p
0.33μF 5 1/2p	1.5μF 8p	

silvered mica 1% (-50pf) 500V

2.2pf-820pf 7p	4.7nF-5600pf 19p
1nF-2nF 9p	6800pf-0.1μF 29p
2.7nF-3nF 16p	

mixed dielectric 600V

0.1μF 7p	0.47μF 7p	2.2μF 16p
0.22μF 7p	0.68μF 8p	4.7μF 24p
0.33μF 7p	1μF 8p	1μF 33p

CHROMASONIC electronics

MAIL ORDERS: Where no p. & p. charge is shown a minimum of 7p applies, p. & p. on overseas orders is charged at cost.
 ADDRESS: T. O. Dept. 56, Farley Green Road, London N10 3HN. Telephone: 01-883 3705.

Heat Sinks

TOS TO18 5p
 TO66 TO3 15p
 Power Tab 13p

DIPI10/2 for SL403D 15p

10D 50p

Transistors & Integrated Circuits

AC107 25p	BC147 10p	BF196 15p	OC81 19p	2N1304 22p	2N5172 15p
AC126 11p	BC148 10p	BF197 15p	OC140 20p	2N1711 25p	BZ788 10p
AC127 15p	BC149 10p	BF272 53p	OC170 23p	2N1893 30p	ZENERS SERIES ea.
AC128 15p	BC157 12p	BF550 24p	OC171 30p	2N2926 all 16p	
AC176 15p	BC158 10p	BF751 21p	ZTX107 15p	2N3053 23p	LO05T1 £1.50
AC187 25p	BC159 12p	BR730 36p	ZTX108 12p	2N3054 50p	LO37T1 £1.50
AC187K 25p	BC169 15p	BSX21 28p	ZTX109 15p	2N3055 49p	MC1303 £1.75
AC188 25p	BC268 15p	BSY95A 14p	ZTX300 12p	2N3702 12p	MC1330 70p
AC188K 25p	BD115 67p	BU105/02 £1.75	ZTX301 15p	2N3703 12p	MC1380 75p
AC220 20p	BD131 70p	MJE340 67p	ZTX302 20p	2N3704 10p	MC1351 £1.00
AD140 40p	BD132 70p	MPF192 40p	ZTX303 20p	2N3705 10p	MC1359 £1.00
AD149 40p	BD131/2M P	MPF103 37p	ZTX304 25p	2N3706 10p	MFC4000B 49p
AD161 40p	BF160 21p	MPF104 37p	ZTX341 20p	2N3707 15p	MFC4010A 55p
AD162 60p	BF167 20p	MPF106 45p	ZTX500 15p	2N3708 12p	LM380 £1.45
AF114 18p	BF173 20p	OC28 40p	ZTX501 15p	2N3709 12p	SL403D £1.50
AF115 18p	BF179 25p	OC28 40p	ZTX502 20p	2N3710 12p	TAD100 £1.50
AF116 18p	BF180 25p	OC35 40p	ZTX503 17p	2N3711 12p	FILTER LP1175 £1.50
AF117 18p	BF181 30p	OC44 15p	ZTX504 50p	2N3819 35p	
AF139 28p	BF184 25p	OC45 15p	ZTX531 25p	2N3903 15p	μA709C 45p
BC107 10p	BF185 25p	OC71 11p	2N697 18p	2N3904 17p	μA710 45p
BC108 10p	BF194 15p	OC72 17p	2N708 12p	2N3905 21p	μA723C £1.05
BC109 10p	BF195 15p	OC76 15p	2N708 15p	2N3906 12p	μA741C 50p

mixed dielectric 1000V

1000pf 6p	6800pf 9p	1μF 12p
2200pf 6p	0.1μF 9p	2.2μF 22p
3300pf 6p	0.22μF 6p	2000pf 5p
4700pf 6p	0.47μF 12p	

Ceramic 12KV.d.c. 8KV.d.c. HI-K 750V.

10pf 9p	200pf 9p	1000pf 5p
15pf 9p	220pf 9p	1500pf 5p
22pf 9p	250pf 9p	2000pf 5p
68pf 9p	270pf 9p	3000pf 5p
82pf 9p	300pf 9p	5000pf 5p
100pf 9p	750V DISC	10,000pf 5p
120pf 9p	470pf 5p	feed-
140pf 9p	1000pf 5p	through
1500pf 9p	5000pf 5p	
180pf 9p	10,000pf 5p	1000pf 5p

Veroboard

Copperclad Plain

0.1" x 0.15"	1p
2 1/2" x 1"	6p
2 1/2" x 3 1/2"	20p
2 1/2" x 5"	24p
3 1/2" x 3 1/2"	24p
3 1/2" x 5"	27p
17" x 2 1/2"	67p
17" x 3 1/2"	90p
17" x 5"	75p

Spot-face Cutter 36p
 Pin Insertion Tool 47p
 Terminal Pins 18p per pack of 36

ADCOLA INVADER

Rotary MAINS 25p

SINGLE WAFER ROTARY 25p

SLIDE D.P.D.T. 17p

TOGGLE S.P.S.T. 250V. 1A 18p

TOGGLE D.P.D.T. 250V. 1A 26p

Phono Socket 4p
 Coax (Flash) 1706 4p
 Socket L646 7p
 Coax (Surface Solder) 8p
 D.in Socket A, B or C 8p
 Phono Plug 5p
 Insulated TERMINALS 13p each
 10kΩ 4mm plug 13p each
 Loudspeaker Plug 8p each
 Loudspeaker Socket 10p

Available in Red, Black, Green, White, Yellow, Blue and Grey.

4mm PLUG. Stackable same colours (except Grey) as terminals.

Mullard B Siemens Electrolytics

CAP μF	VOLTAGE							
	4	6.3	10	16	25	40	63	80
1.5	-	-	-	-	-	-	-	6p
2.2	-	-	-	-	-	-	-	6p
3.3	-	-	-	-	-	-	-	6p
4.7	-	-	-	-	-	-	-	6p
6.8	-	-	-	-	-	-	-	6p
10	-	-	-	-	-	-	-	6p
15	-	-	-	-	-	-	-	6p
22	-	-	-	-	-	-	-	6p
33	-	-	-	-	-	-	-	6p
47	6p	-	-	-	-	-	-	6p
68	-	6p	-	-	-	-	-	6p
100	-	6p	-	-	-	-	-	6p
150	-	6p	-	-	-	-	-	6p
220	-	6p	-	-	-	-	-	6p
330	-	6p	-	-	-	-	-	6p
470	-	6p	-	-	-	-	-	6p
680	-	10p	-	-	-	-	-	6p
1000	-	10p	-	-	-	-	-	6p
1500	-	12p	-	-	-	-	-	6p
2200	-	18p	-	-	-	-	-	6p
3300	-	21p	-	-	-	-	-	6p
4700	-	21p	-	-	-	-	-	6p

Quantity Prices on application.

Aluminium Boxes

Including baseplate and screws


No.	L.	W.	D.	Price	p. & p.
(7)	2 3/4"	x 5 1/2"	x 1 1/2"	35p	8p
(8)	4"	x 4"	x 1 1/2"	35p	8p
(9)	4"	x 2 3/4"	x 1 1/2"	35p	8p
(10)	4"	x 5 1/2"	x 1 1/2"	40p	8p
11	4"	x 2 1/2"	x 2"	35p	8p
12	3"	x 2"	x 1"	32p	8p
13	6"	x 4"	x 2"	50p	10p
14	7"	x 5"	x 2 1/2"	58p	12p
15	8"	x 6"	x 3"	75p	18p
16	10"	x 7"	x 3"	85p	20p

Hi-Volt Electrolytics

1.2	4	8μF 450V	14p	32μF 450V	20p
1.6μF	450V	15p	50μF 350V	20p	
8	8μF 450 V W	18p	32 - 32μF 450 V W	25p	
8	16μF 450 V W	20p	32 32μF 450 V W	33p	
16	16μF 450 V W	25p	50 50μF 350 V W	45p	

BSR LATEST SUPERSLIM STEREO & MONO

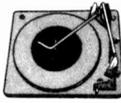Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 18 months' guarantee. AC 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 3 1/2 in. below motor board 8 1/2 in.



With STEREO and MONO XTAL £8.75 Post 25p

RCS BARGAIN 4 TRANSISTOR MONO AMPLIFIER

Powerful 3 watts output, 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make, size 8" wide x 4" deep x 3" high.

PRICE £5.50 Post 25p

RCS DE-LUXE 3 WATT AMPLIFIER. Ready made, tested. Printed circuit. 3 watts output. Tone and volume controls. Complete with output valve and rectifier, two knobs, and high performance loudspeaker. Double wound fully isolated mains transformer. A.C. mains 200/250V. Response 50-12,000 cps. Sensitivity 300mV. £4 Post 25p

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with separate pick-up arm fitted LF/78 turnover motor £4.50 cartridge Post 25p



HI-FI PICK UP CARTRIDGES

Stereo/Mono 9TA £2.50; GP94 £2.50; GP93 £2. Sapphire Mono GP91 £1.50; Powerpoint LP/78 60p.

GARRARD DECCA DISCO DECK

Single play Stereo/Mono Demar transcription head and arm. Four speeds. 10 1/2 in. turntable. Anti-rumble filter. Bias compensation. Laboratory motor.



SPECIAL PRICE £18.50 Post 25p

METAL PLINTH AND PLASTIC COVER

Cut out for most Garrard or B.S.R. Most will play with cover in position. Latest Design. Covered in black leatherette. Antimagnetic. 12 1/2 x 14 1/2 x 7 1/2 in. high. Post 35p

£4.50

ALSO AVAILABLE IN SOLID NATURAL MAHOGANY WAX POLISHED FINISH—AT SAME PRICE

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 80 minutes or 0 to 8 hours. Fully insulated. Makers list price £4-50. Brand new and fully guaranteed. OUR PRICE £1.50 P. & P. 15p or £3 pair Post Free. (Please state type when ordering)



BLANK ALUMINIUM CHASSIS

18 s.w.g. 2 1/2 in. sides 6 x 4 in. 45p; 8 x 6 in. 55p; 10 x 7 in. 65p; 12 x 8 in. 85p; 14 x 9 in. 90p; 16 x 10 in. 90p; 18 x 10 in. 21. ALUMINIUM PANELS 18 s.w.g. 6 x 4 in. 9p; 8 x 6 in. 15p; 10 x 8 in. 16p; 12 x 10 in. 18p; 14 x 12 in. 20p; 16 x 10 in. 25p; 18 x 12 in. 34p; 12 x 12 in. 40p; 16 x 10 in. 50p

RADIO BOOKS (Post 3p)

Handbook of transistor equivalents	40p
Radio valve guide, Book 1, 2, 3, 4, 5 (each)	15p
Master colour code folder	30p
Boys' book of crystal sets and simple circuits	15p
Universal gram motor speed indicator	8p
High fidelity loudspeaker enclosures	40p
Practical Stereo handbook	30p
Sound and Loudspeaker Manual	50p
Coil design and code calculator	20p
Radio, TV and electronics data book	35p
Transistor circuits manual, No. 4	15p
Practical transistor audio amplifier Book 1	40p
Transistor subminiature receivers	35p
Practical Transistor Novelty Circuits	40p
Resistor colour code calculator	10p
Engineers' and Machinists' reference tables	20p
TV fault finding	50p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less PLEASE STATE VOLTAGE REQUIRED. £2 Post Free Details S.A.E. Size 3 1/2 x 1 1/2 in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size 1 1/2 x 1 1/2 x 1". Response 25 c.p.s. to 25 Kc/s, 20 db gain. For use with valve or transistor equipment. 90p Post Full instructions supplied. Details S.A.E.

MAINS TRANSFORMERS

	All post 25p each
250-0-250 80 mA. 6.3 v. 4 amp.	£1.50
250-0-250 80 mA. 6.3 v. 5 amp.	£2.25
350-0-350 80 mA. 6.3 v. 3.5 a. 6.3 v. 1 a. or 5 v. 2 a.	£2.25
300-0-300 v. 120 mA. 6.3 v. 4 a. C.T. 1.2 v. 2 a.	£3.25
MINIATURE 200 v. 20 mA. 6.3 v. 1 a. 2 1/2 x 2 1/2 in.	75p
MIDGET 220 v. 45 mA. 6.3 v. 2 a. 2 1/2 x 2 1/2 in.	90p
HEATER TRANS. 6.3 v. 3 a.	80p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs	
2 amp. 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v.	£2.25
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2.25	
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £2.25	
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60, £3.75	
3 amp. 5, 8 and 13V	£1.00
5 amp. 5, 8 and 13V	£1.20
3 amp. 3, 5, 8, 10, 13 and 5-0-5V	£1.30
5 amp. 3, 5, 8, 10, 13 and 5-0-5V	£1.50
AUTO TRANSFORMERS. 115v to 230v or 230v to 115v. 150w. £2.25; 500w. £6.25; 750w. £10; 1000w. £15.	
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12v. 1 1/2 amp. £1.50; 2 amp. £1.80; 4 amp. £2.50	
BATTERY CHARGERS—Ready built with leads and clips	
1 1/2 amp. £2.40; 4 amp. £4.50; 6 amp. £6.50	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 1/2 amp. 40p; 2 amp. 55p; 4 amp. 85p.	
LUCAS 2DS500 Full wave Bridge 70v. 5 amp 95p.	

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3 amps. 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. £10 Carr. 50p Can be used as 800 watt auto transformer 240-110V.

NEW TUBULAR ELECTROLYTICS	CAN TYPES
2/350V 14p	250/25V 14p
4/350V 14p	500/25V 20p
8/450V 14p	1000/25V 35p
15/450V 20p	1000/50V 47p
32/450V 20p	800/450V 20p
25/25V 10p	8+18/450V 20p
50/50V 10p	18+18/450V 25p
100/25V 10p	32+32/350V 25p
	100+50+50/350V 45p

LOW VOLTAGE ELECTROLYTICS. 1, 2, 4, 5, 8, 10, 15, 20, 30, 50, 100, 200mF 15V 10p. 600mF 12V 15p; 25V 20p; 50V 30p. 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p. 2000mF 6V 25p; 25V 42p; 50V 57p. 2500mF 50V 82p; 3000mF 25V 47p; 50V 65p. 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

CERAMIC, 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1µ, 0.5µ, 1µ; 1µ; 2µ; 5µ; 2mF 150V 15p. 500V-0.001 to 0.05µ; 0.1µ; 0.2µ; 0.5µ; 1µ; 2µ. 250V MICA. Close tolerance 1%. 25-500pF; 500-2.2µF 10p; 2.7-5.6µF 20p; 6.8-50µF 0.01, mid 30p each. TWIN GANG. "0-0" 20pF+170pF, 65p; Slow motion drive 365pF+365pF with 25pF+25pF, 50p; 500pF standard 45p; single gang 500pF 75p; small 3-gang 500 pF £1.80. SHORT WAVE SINGLE. 10p, 30p, 20pF, 55p, 50pF, 55p.

SHORT WAVE SINGLE GANG. Precision Silver Plated Gangable Tuning Condensers. 50p each. Values up to 100pF. Section Couplers supplied FREE with two or more gangs.

NEON PANEL INDICATORS 250V AC/DC Amber 20p. RESISTORS. 1/4 w. 1 w. 2 w. 10%; 1/2 w. 5p. 10Ω to 10M. HIGH STABILITY. 1/4 w. 10Ω to 10 meg. 4p. Ditto 5% Preferred values 10 ohms to 10 meg. 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 2 watt, 1 ohm to 8.2 ohms 10p. TAPE OSCILLATOR COIL. Valve type, 35p.

WEYRAD P50—TRANSISTOR COILS

RA2W Ferrite Aerial	72p	Spare Cores	3p
Osc. P50/1AC	33p	Driver Trans. LFDT4	58p
1.F. P50/2CC ke/s	36p	Printed Circuit, PCA1	58p
3rd I.F. P50/3CC	36p	J.B. Tuning Gang	65p
P51/1 or P51/2	36p	Weyrad Booklet	58p
P50/3V	36p	OPT1	58p
Mullard Ferrite Rod 8 x 1/2 in.	20p	6 x 1/2 in. 20p.	

VOLUME CONTROLS

80ohm Coax 4p yd. BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £1.40; 60 yd. £2. PRINGLE LOW LOSS 10p yd. IDEAL 825 and colour

1 1/2 inch DIAMETER WAVELENGTH SWITCHES. 25p. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 25p each. 1 p. 1 2-way, or 4 p. 2-way, or 4 p. 3-way 25p. TOGGLE SWITCHES. 1p. 4p. 2p. 6p. dt. 22p. Sub-miniature, sp. 80p; dp. 37p; dp. dt. 45p.

ALL PRICES INCLUDE ANY V.A.T.

E.M.I. 13 1/2 x 8 in. SPEAKER SALE!



With twin tweeters. £3.95 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 25p
With flared tweeter cone and ceramic magnet. 10 watt. £2.25 Bass res. 45-80 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p

TEAK CABINET 18 x 10 x 8 in. £5 Post 25p

GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 cps. Ideal F.A. Column. Hi-Fi Enclosure Systems, etc. Suitable cabinet 12 x 8 x 6 1/2. £4



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 18,000 cps. Size 3 1/2 x 3 1/2 in. deep. Rating 10 watt, 3 ohm or 15 ohm models. £1.90 Post 10p Crossover 95p.

GOODMANS 8 in WOOFER

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass resonance 35 cps. Frequency response 30-8,000 cps. £4.50



LOUDSPEAKERS P.M. 3 OHMS. 7 1/2 in. £1.25; 6 1/2 in. £1.50; 8 x 5 in. £1.80; 8 in. £1.75; 10 x 8 in. £1.90; 10 in. £2.

SPECIAL OFFER! 8 ohm 2 1/2 in. £1.30; 5 ohm 2 1/2 in. 3 in. 5 in. 25 ohm 2 1/2 in. dia.; 3 in. dia.; 3 ohm 2 1/2 in. dia.; 6 in. 8 x 4 in.; 7 x 4 in.; 8 x 5 in. TYPE 18 ohm, 2 1/2 in. 3 1/2 in. 5 in. dia. (6 x 4 in. 8 ohm, 11-50).

RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8 in. diameter 4 watt; 10 in. diameter 5 watt; 12 in. diameter 6 watt, 3 or 8 or 15 ohm models £2-20 each. Post 15p. SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-16Kc/s, 10W 8 ohm or 15 ohm £1.95. De Luxe Horn Tweeters 2-18 Kc/s, 15W, 15 ohm £3. TWO-WAY 3,000 c.p.s. CROSSOVERS 3 or 8 or 15 ohm 95p.

TWO-WAY CROSSOVER NETWORK 3,000 c/s

With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5 1/2 x 4 in. with control knob, tweeter and woofer leads and input. £1.90 Post terminals. Suitable for 3 to 8 ohm impedance.

VALVE OUTPUT TRANS. 25p. MIKE TRANS. mu metal 100-1 £1.25; 5 WATT MULTI RATIO 3, 8 and 15 ohms 80p. PUSH-PULL VALVE OUTPUT TRANSFORMERS. £12-50 50 watt. £29-50 100 watt

STEREO/MONO HEADPHONES

New model with new type slider volume controls. Stereo/Mono switch. 8 ohms. £10. High Quality with tweeters and volume controls. 8 ohm. £7. Budget Model. 8 ohm. £3.25. HEADPHONE JUNCTION BOX with switch £1.75. Mono Stethoscope 8 ohms. 65p. EAR PIECES. Crystal 25p. Magnetic 5 ohms. 13p. Magnetic 25 ohms. 23p. ACS 1000 ohms. 53p.

BRITISH MADE STEREO MULTIPLEX DECODER

Brand New. 7 transistors plus integrated circuit. Fibre glass printed circuit board. Size 2 1/2 x 8 1/2 x 2 in. Pre-Aligned. Complete with stereo beacon indicator. 12V d.c. operation. 400mV output for 100V input. Full instructions for any FM Tuner. Some technical experience essential. DIPLOE LOFT AERIAL £1.50. Post 15p CABLE 4p yard. £6.50



COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET BOXES SURFACE OR PLUG 25p. BALANCED TWIN RIBBON FEEDER 300 ohms. 5p yd. JACK SOCKET Sid. open-circuit 14p, closed circuit 23p; Chrome Lead Socket 45p. Phono Plugs 5p. Phono Socket 5p. JACK PLUGS Sid. Chrome 15p; 3-5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 15p; 5-pin 15p. DIN PLUGS 3-pin 15p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 8p; CANS 5p.

MINIMUM POST AND PACKING 15p.

RADIO COMPONENT

Illustrated Catalogue, Radio Books & Component Lists 10p. Written guarantee.

E.M.I. WOOFER AND TWEETER KIT £5.75

THE PAIR Post 25p.
(Available separately.
Woofer £4.25; Tweeter
£1.90).

Comprising a fine example of a Woofer 10½ x 6in. with a massive Ceramic Magnet, 44oz, Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps

SUITEABLE ENCLOSURE 20 x 13 x 9in.
MODERN DESIGN. TEAK WOOD FINISH

£9 Post 25p



8in. or 10in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8in. 10 watts, 10in. 12 watts music power.

£3.75 Post 25p



TEAK VENEER SPEAKER CABINET Fluted Wood Front

MODEL "A". 20 x 13 x 9in.
For 12in. dia. or 10in. speaker. £9 Post 25p

MODEL "B". 16 x 10 x 9in.
For 13 x 8in. or 8in. speaker. £5 Post 25p


MODEL "C". 16 x 8 x 6in.
For 10 x 6in. or 6in. speaker. £4 Post 25p

LOUDSPEAKER CABINET
WADDING 18in. wide, 15p ft

BARGAIN AM TUNER.
Medium Wave.
Transistor Superhet
Ferrite aerial. 9 volt. £4.95



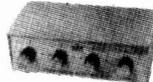BARGAIN 4 CHANNEL
TRANSISTOR MONO
MIXER. Add musical
highlights and sound effects
to recordings. Will mix
Microphone, records, tape
and tuner with separate
controls into single output.
9 volt. battery
operated. £3.95



STEREO VERSION OF ABOVE 25.95

BARGAIN FM TUNER
88-108 Mc/s Six Transistor.
9 volt. Printed
circuit. Calibrated slide
dial tuning.
Walnut Cabinet.
Size 7 x 5 x 4in. £14.85



BARGAIN FM TUNER £9.85

as above less cabinet
BARGAIN 3 WATT AMPLIFIER. 4 Transistor
Push-Pull Ready built, with volume control.
9 volt battery operated. £4.50

£4.50

THE "INSTANT" BULK TAPE
ERASER & HEAD DEMAGNETISER.
Suitable for cassettes, and all
sizes of tape reels. A.C. mains 200/250V.
Leaflet S.A.E. £2.50 Post 15p




WAFER THIN HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10½ x 8½ x ½in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment.

Ideal for home handyman and experimenters. Suitable for Heating Pads, Food Warmers, Convector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in the greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1.50)
ALL POST PAID—Discounts for quantity.

BAKER 12in MAJOR £9

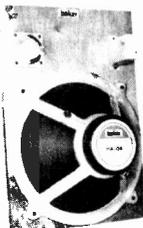

30-14,500 c.p.s., 12in.
double cone, woofer and
tweeter cone together
with a BAKER ceramic
magnet assembly having
a flux density of 14,000
gauss and a total flux of
145,000 Maxwells. Bass
resonance 40 c.p.s. Rated
20 watts. State 3 or 8 or
15 ohm. Post Free.

Module kit, 30-17,000 c.p.s.
with tweeter, crossover,
baffle and instructions. £11.50
Post 25p

BAKER "BIG-SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25"
12in. 25 watt £8
3, 8 or 15 ohms. Post 25p

GROUP "35"
12in. 35 watt £9
3, 8 or 15 ohms. Post 25p

GROUP "50"
15in. 50 watt £20
8 or 15 ohms. Post 25p



MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music. 4-way Mixing. Response 10-30,000 cps. Matches all loudspeakers. 8/15 ohm A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £49 Post Free




CALLERS ONLY! DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version, 4 inputs, 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. 4, 8 and 15 ohm matching. £55

Q MAX CHASSIS CUTTERS

A die, punch and Allen Screw

1in. Round . . . 88p	1½in. Round . . . 88p	Key "B" for above . . . 8p
1½in. Round . . . 75p	2in. Round . . . 88p	2in. Round . . . £2-05
Key "T" for above . . . 5p	1½in. Round . . . 88p	2½in. Round . . . £2-30
1in. Round . . . 83p	1½in. Round . . . £1-05	Key "C" for above . . . 12p
1½in. Round . . . 83p	1½in. Round . . . £1-05	2in. Round . . . £4-10
1in. Round . . . 88p	1½in. Round . . . £1-10	2in. Round . . . £5-25
1½in. Round . . . 88p	1in. Round . . . £1-10	3in. Round . . . £8-10
1in. Round . . . 90p	1in. Round . . . £1-25	Key "E" for above . . . 18p
1in. Round . . . 90p	1in. Round . . . £1-43	1in. Square with key . . . £1-93
Key "A" for above . . . 5p	1½in. Round . . . £1-50	

SLIDER VOLUME CONTROLS

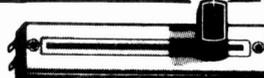

MONO LOG or LINEAR.
Size 3¼ x 1½ x ½in. with knobs.
5K, 10K, 25K, 50K, 100K.
250K, 500K, 1 MEG, 2 MEG. 65p EACH

E.M.I. TAPE MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 138mA. Spindle 0.187 x 0.75in. Size 3½ x 2½ x 2in. (illustrated). Post 15p. £1-25

BALFOUR GRAM MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA. Spindle 1 x 3/20. Size. 2½ x 2½ x 1½in. Post 15p. 85p

E.M.I. GRAM MOTORS. 120v or 240v a.c. 2,400 rpm. 2-pole 70mA. Post 15p. 75p



BAKER HI-FI SPEAKERS HIGH QUALITY — BRITISH MADE

REGENT 12in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps
Flux Density 12,000gauss
Useful response 45-13,000cps
3 or 8 or 15 ohm models

£8 Post 25p

DE-LUXE Mk II 12in. 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance 30cps
Flux Density 14,000gauss
Useful response 25-16,000cps
8 or 15 ohms models

£10 Post 25p

SUPERB 12in. 20 watts

A high quality loudspeaker. Its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 16,500gauss
Useful response 20-17,000cps
8 or 15 ohms models

£15 Post 25p

AUDITORIUM 12in. 25 watts

A full range reproducer for high power Electric Guitars, public address, multi-speaker systems, electronic organs. Ideal for Hi-Fi and Discotheques.

Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 25-16,000cps
8 or 15 ohms models

£14 Post 25p


AUDITORIUM 15in. 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 20-14,000cps
8 or 15 ohms models

£20 Post 25p

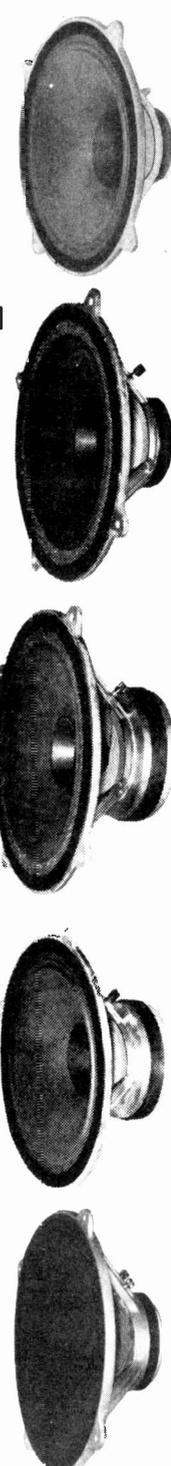Hi-Fi Enclosure Manual containing 20 plans designs, crossover data and cubic tables. 42p. Post Free.



ALL PRICES INCLUDE ANY V.A.T. OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m. (Closes for Lunch 1.15-2.30)

SPECIALISTS 337 WHITEHORSE ROAD · GROYDON

(Export: Remit cash and extra postage.)

Buses 50, 68, 159. Rail Sethurst

Telephone 01-684-1665



3W STEREO AMPLIFIER
£3.90;
10W AMPLIFIER,
£3.75.



R.F. FIELD INDICATOR
Model FL-30HA
Frequency Range
(5 ranges) 1M/cs to
250M/cs, £3.



TAPE RECORDER
LEVEL METER
500µA, 50p.

MINIATURE INDICATOR LAMPS (5 colours), 11p; 6.3V or 12V Bulbs for above, 4p.
MAINS NEONS with long leads, 6p; Panel mounting (red, green, clear), 15p. **CARTRIDGES:** Compatible to ACOS GP91-3SC, 90p; Stereo GP93-1, £1.15. **HEADPHONES:** High Impedance (2,000 ohm), 90p; Stereo 8 ohm, £1.95; Stereo/Mono 8/16 ohm, £2.10. **MICROPHONES:** Lapel, 28p; ACOS Mic 60, £1; Cardioid Dynamic Microphone Dual Impedance 600 ohm and 50K, £4.50. **CONDENSER Microphone,** £8.62. **JUNCTION BOXES** JB3, £1.20. Please note there will be 10% V.A.T. charge as from April 1.

Large S.A.E. for list No. 5. Special Prices for quantity quoted on request. Please add 10p for P. & P. on orders under £5.

M. DZIUBAS

158 Bradshawgate, Bolton, Lancs. BL2 1BA

GUNTON ELECTRONIC IGNITION KIT £9.35 INC. VAT

READY BUILT UNIT GUARANTEED 5 YEARS £11.55 INC. VAT

Patents Pending. 12 volt only—state pos. or neg. earth. Capacitive discharge ignition is recognised as being the most efficient system and will give you:

- ★ Continual Peak-Tuned Performance
- ★ Up to 20% reduced fuel consumption
- ★ Easier All-weather Starting
- ★ Increased Acceleration and Top Speed
- ★ Longer Spark Plug Life
- ★ Increased Battery Life
- ★ Elimination of Contact Breaker Burn
- ★ Purer Exhaust Gas Emission

Kit includes absolutely everything for assembly: Ready drilled Case and Hardware Printed Circuit Board, Cables, Coil Connectors, Silicon Grease Nuts and Bolts, etc. 8 page illustrated instructions cover fitting of all types of tachometers. Call in for a workshop demonstration. S.A.E. all enquiries please, or Phone 33652. (Many letters from satisfied customers.)

SCORPIO: Transformer £2.42. Printed Circuit Board 83p

All prices include carriage and V.A.T.



ALUMINIUM BOXES

Complete with baseplate and screws

AT DIRECT FROM MANUFACTURERS' PRICES WITH RETURN OF POST SERVICE

Type No	L	W	D	Price
7*	5½	2½	1½	44p
8*	4	4	1½	44p
9*	4	2½	1½	44p
10*	5½	4	1½	53p
11	4	2½	2	44p
12	3	2	1	39p
13	6	4	2	59p
14	7	5	2½	68p
15	8	6	3	88p
16	10	7	3	96p

* These sizes accept standard veroboard range.

All prices include carriage and V.A.T. 20% discount on 10 or more boxes. 30% discount on orders over £10.

Dept. PE4, ELECTRONICS DESIGN ASSOCIATES
82 BATH STREET, WALSALL WS1 3DE

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD

C.W.O. Please. P. & P. please add 10p to order under £2.

RESISTORS

High stability, low noise, carbon film resistors. Tubular miniature high power resistors.

Power Watts	Tolerance	Range	Values Available	Price
½	5%	2.2-2.2MΩ	E12	1-99 100+ 1p 0.8p
1	5%	2.2-10MΩ	E12	1p 0.8p
1	5%	2.2-10MΩ	E12	2p 1.5p
4	10%	1-10 ohm	E12	6p —

Quantity prices available for any selection. Ignore fractions on total order.

CAPACITORS

Electrolytics, general purpose, miniature, axial lead. Mullard O15, O16, O17 series.

Value	Voltage	Price	Value	Voltage	Price
1µF	63V	6p	22µF	63V	6p
1.5µF	63V	6p	47µF	63V	6p
2.2µF	63V	6p	100µF	40V	6p
3.3µF	63V	6p	150µF	25V	6p
4.7µF	63V	6p	220µF	25V	11p
6.8µF	63V	6p	470µF	25V	13p
10µF	63V	6p	680µF	25V	20p
15µF	63V	6p	1,000µF	25V	25p

POLYESTER FILM CAPACITORS

Mullard C296 series
400V d.c.; µF: 0.001, 0.0015, 0.0022, 0.0033, 0.0047, 0.0068, 0.01, 0.015, 0.022, 23p each. µF: 0.033, 0.047, 0.068, 0.1, 4p each. µF: 0.15, 6p. µF: 0.22, 7p. µF: 0.33, 10p. µF: 0.47, 13p. 160V d.c.; µF: 0.1, 0.15, 4p. 0.22, 5p. 0.33, 6p. 0.47, 7p. 0.68, 10p. 1.0, 13p.

Mullard C280 series. P.C. mounting
400V d.c.; µF: 0.01, 0.015, 0.022, 3p each. 0.033, 0.047, 4p each. 250V d.c.; µF: 0.068, 0.1, 0.15, 4p each. µF: 0.22, 0.33, 5p each. µF: 0.47, 7p. µF: 0.68, 10p. µF: 1.0, 11p.

CERAMIC DISC CAPACITORS

Working voltage 50V d.c., Plaquette body with 25mm leads. Range: 22µF-10,000µF. 2p each.

SLIDER POTENTIOMETERS

Single, 10kΩ, 25kΩ, 50kΩ, 100kΩ, log or linear, 35p.
Dual gang, 10kΩ + 10kΩ, etc., above values, log or linear, 50p.
Knobs for above, 10p.

PRESET POTENTIOMETERS SKELETON

Horizontal or vertical mounting. 0.25W Miniature, 53p each.

SEMICONDUCTORS

TRANSISTORS

AC126	10p	BC148	10p	OC42	11p
AC127	10p	BC149	10p	OC44	11p
AC128	10p	BD131	70p	OC45	11p
AD161	30p	BD132	70p	2N2926R	9p
AD162	30p	BFY50	22p	2N2926O	9p
AF117	10p	BFY51	22p	2N2926V	9p
BC107	7p	BFY52	22p	2N2926G	10p
BC108	7p	OC26	40p	2N3054	55p
BC109	7p	OC27	40p	2N3055	55p
BC147	10p	OC35	40p		

LINEAR INTEGRATED CIRCUITS

709 35p; 741 40p; 723 80p; DIL sockets 14 and 16 pin, 20p
All IC's are in DIL package.

ZENER DIODES

BYZ88 series. Power rating: 400mW. 5% tolerance. Values available: 3.3V-30V, 12p.

DIODES

OA85	7p	OA91	5p	IN4004	7p
OA90	5p	IN4001	6p	IN4007	7p

SILICON BRIDGE RECTIFIER WO1 30p (1 amp-100V)

POTENTIOMETERS

Carbon track, 1kΩ-2MΩ, log or linear, single Gang, 12p. 5kΩ-2MΩ log or linear, dual gang, 37p. 5kΩ-2MΩ, log or linear, single gang with switch, 24p. Knobs for above: 10p each.

VEROBOARD

	0.1 matrix	0.2 matrix	0.1 matrix	0.2 matrix
24in × 32in	22p	16p	17in × 24in	75p
24in × 5in	24p	24p	17in × 5in (plain)	—
32in × 32in	24p	24p	17in × 32in (plain)	—
32in × 5in	27p	27p	17in × 24in (plain)	—
				42p

Pin insertion tool, 52p. Spot face cutter, 42p. Packet of 50 pins, both sizes, 20p.

JACK PLUGS AND SOCKETS

Standard screened	12p	2.5mm screened	8p
Stereo screened	10p	3.5mm screened	10p
Standard socket	12p	2.5mm sockets	7p
Stereo sockets	15p	3.5mm sockets	7p

DIN PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin (180 or 240), Plugs, 12p. Sockets, 8p.

Post this Coupon for Catalogue

Please enclose 10p postage stamps for a copy of the catalogue which gives details of listed items listed in this advert, and more.

NAME.....
(BLOCK CAPITALS PLEASE)
ADDRESS.....

AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. **£5-75** plus 25p post and insurance.



TAPE HEADS

We are gradually obtaining more information about the Trivox tape heads we have, we are told that these have been wound in a very ingenious way so that winding may be coupled either in parallel or in series depending whether high or low impedance is required. We also have matching erase heads and now offer these in pairs. 1 record and 1 erase head. Price of the 2 track 45p per pair, 4 track 75p per pair. Pair mounted on plate 45p extra.

MAINS OPERATED CONTACTOR

230/240V 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10A. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2in. **£1-50** each.




TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. **88p**. KNUCKLED MODEL FOR F.M. 50p.

MAINS CLOCK & TIME SWITCH

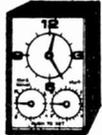Smith's main's driven clock with 15A programmable switch also notes showing how you can use this to wake up with music playing, kettle boiling or come home to a warm house, warn-off burglars, keeps pets warm, halves your heating bills etc., etc. **£1-75** +20p p. & p.



WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 50p post free.

IMMERSION HEATERS BY REMPLOY

Standard fitting for domestic water tanks, made by the famous Remploy Company. Complete with sealing washers suitable for 200-240V a.c. Depth into tank 11in. 2kW or 3kW. **£1-50** plus 40p each post and insurance.



NEED A SPECIAL SWITCH?

Double Leaf Contact. Very slight pressure closes both contacts. 6p each, 60p doz. Plastic pushrod suitable for operating, 5p each, 45p doz.



THERMOSTAT

Continuously variable 30°-90°C. Has sensor bulb connected by 33in of flexible tubing. On operation a 15A 250V switch is opened and in addition a plunger moves through approx. 1in. This could be used to open valve on ventilator, etc. **£1-50** plus 23p p. & ins.



HIGH ACCURACY THERMOSTAT

Uses differential comparator I.C. with thermistor as probe. Designer claims temperature control to within 1/7th of a degree. Complete kit with power pack **£5-50**.

For digital instruments, counters, timers, clocks, etc. Hi-vac. XN. 3. Price **£1-45** each. 10 for **£18**.

12-WAY SUB-MINIATURE MULTI-CORE CABLE

7-0076 copper cores each core. P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16in thick. Price 20p per yard.

VAT From April 1st VAT must be added to total orders.

STANDARD WAFER SWITCHES

No. of Poles	Standard size 1 1/2" wafer—silver-plated 5-amp contact, standard 1 1/2" spindle 2" long—with locking washer and nut.											
	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way	40p	40p	40p
1 pole	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
2 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
3 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
4 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
5 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
6 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
7 poles	70p	70p	70p	95p	£1-20	£1-20	£1-20	£1-20	£1-20	£1-20	£1-20	£1-20
8 poles	70p	70p	70p	95p	£1-20	£1-20	£1-20	£1-20	£1-20	£1-20	£1-20	£1-20
9 poles	70p	70p	70p	95p	£1-45	£1-45	£1-45	£1-45	£1-45	£1-45	£1-45	£1-45
10 poles	70p	70p	70p	95p	£1-20	£1-45	£1-45	£1-45	£1-45	£1-45	£1-45	£1-45
11 poles	70p	70p	70p	95p	£1-20	£1-70	£1-70	£1-70	£1-70	£1-70	£1-70	£1-70
12 poles	70p	70p	70p	95p	£1-20	£1-70	£1-70	£1-70	£1-70	£1-70	£1-70	£1-70

THYRISTOR LIGHT DIMMER

For any lamp up to 250W. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price **£2-95** plus 20p post and insurance. Industrial model 3A with control knob but not mounted on switch plate **£3**.



HORSTMANN "TIME AND SET" SWITCH

(A 30A Switch). Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around **£5**. Special snip price **£1-50**, p. & ins. 23p.



13 AMP TWIN GANG SOCKETS

Offered at less than wholesale price your opportunity to replace those dangerous adaptors—brown bakelite flush mounting—standard fitting. Unswitched **20p** each, separately switched **30p** each. Less 10% ten or more +20p postage if order under **£4**.




4 WATT AUDIO AMPLIFIER £1-45



Works off dry batteries, car battery or mains power pack. Only **£1-45**. This low price possible only because the make is over-produced. Unrepeatable once stocks are cleared. Made by the famous Mullard company and carries their full guarantee. Complete in dustproof case, amplifier may be used for Mono or Stereo, music or speech. Hundreds of applications. Frequency response 50Hz-16KHz. Supplied complete with connection diagram and operating notes. Postage & Ins. 20p. **FREE** All purchasers receive Mullard booklet "Do It Yourself Stereo" tells all you need to know to build your own stereo system. Write today to avoid missing this terrific offer.

HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10A type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from makers display over **£10** each. Special snip price **£5-75** plus 25p post and insurance. Don't miss this terrific bargain.

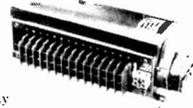

MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, January 73. All electronic parts **£2** post paid.




DIGITAL COUNTER TIMER

Very stable and reliable crystal controlled circuit. Capable of working in excess of 15MHz. Construction simplified by use of 15 integrated circuits. Complete kit with case **£29-50** or construction data and price list 50p.

INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over **£5**. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices **25p** upwards with circuits and technical data of each. Complete parcel only **£1** Post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**

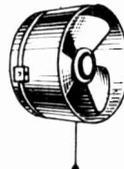TERMS—10% discount if ten of an item ordered, send postage where quoted—other terms post free if order for these over **£6** otherwise add 20p.



EXTRACTOR FAN

Cleans the air at the rate of 10 times each hour. Suitable for kitchens, bath-rooms, factories, changing rooms, etc., it's so quiet it can hardly be heard. Compact 5 1/2in casing with 5 1/2in fan blades. Kit comprises motor, fan blades, steel casing, pull switch, mains connector, and fixing brackets. **£2-50** plus 30p post and ins.

QUICK CUPPA

Mini Immersion Heater, 350W 200/240V. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. **£1-25**, post and insurance 14p. 12V car model also available same price. Jug heater **£1-50** plus p. & p. 14p.



MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12V for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer, rectifier, smoothing and load resistor condensers and instructions. Real snip at only **£1** plus 20p postage.



TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless, August issue. **£2-95** plus 20p post and insurance.

WINDSCREEN WIPER CONTROL

Beat dirty roads, drizzle, fog, etc. Kit of parts to make this useful accessory with circuit details. **£2-25**.



12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mH/d smoothing. Price **£2** plus post & packing.

ONE CHIP RADIO

Ferranti's latest device ZN414—gives results better than superhet. Supplied complete with technical notes and circuits. **£1-25** each. 10 for **£11**.

HI-Q TUNER COMPONENTS

For experimenting with the ZN414
Kit No. 1—Plessey Miniature Tuning Condenser with built in LW switch and 3in Ferrit slab and litz wound MW coil, **85p**.
Kit No. 2—Air spaced tuning condenser 6in ferrite rod, litz wound MW and LW coils, **85p**.
Kit No. 3—Air spaced TC with slow motion drive 3in ferrite rod, with Litz wound LW and MW coils, **£1**.
Kit No. 4—Permeability tuner with fast and slow motion drive and LW loading coils, **45p**.

6 VOLT CLOCK MOTOR

Works from 50 cycle mains through condenser, resistor or step-down transformer. This is a synchronous motor made by Smiths, so it is an extremely accurate speed controller. Very small in size (2W) and with a polythene cover. Price **30p** each. 10 for **£2-70**.

SOLDER GUN

A must for every busy man, gives almost instant heat also illuminated gun. 100W **£2-25** plus post and ins. 20p. BIG JOB 250W model **£4-75** plus post and ins. 40p.

MAINS OPERATED SOLENOIDS

Model 772—small but powerful 1 1/2in x 1 1/2in approx. size 1 1/2in x 1 1/2in x 1 1/2in **60p**.
 Model 400/1 1 1/2in pull, size 2 1/2in x 2 1/2in x 1 1/2in **75p**.
 Model TT10 1 1/2in pull, size 3 x 2 1/2 x 2 1/2in **£1-80** plus 20p post and insurance.

3 STATE PERMEABILITY TUNER

Made originally for Radiomobile car radios. This is a medium wave tuner with a frequency coverage 16kc-525kc. Aerial, RF and oscillator sections (long wave coil available) small size, only 2 1/2 x 2 x 1 1/2in. Can be used with our 1F module and AF modules and a few inter connection components to make a complete compact receiver. Circuit supplied. Price **65p** less 10% for 10.



J. BULL (ELECTRICAL) LTD.

(Dept. P.E.), 7 Park Street, Croydon CRO 1YD
 Callers to 102/3 Tamworth Road, Croydon

Don't miss

SOUND 73 international

BLOOMSBURY CENTRE HOTEL

Coram Street, Russell Square
London W.C.1

13-15 MARCH 1973
Tues/Wed 10.00-18.00 hrs.
Thurs 10.00-17.00 hrs.

**THE ONLY EXHIBITION IN
EUROPE EXCLUSIVELY
FEATURING**

PUBLIC ADDRESS & ALLIED EQUIPMENT

There will also be Lectures and
Demonstrations

Tickets and information from
the organisers

**THE ASSOCIATION OF
PUBLIC ADDRESS ENGINEERS**
6 Conduit Street, London
W1R 9TG ENGLAND
TEL. 01-493 5256

PRACTICAL ELECTRONICS "SCORPIO" ELECTRONIC IGNITION SYSTEM



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, capacitor fitted in the vehicle are used. No extra or special components are required.

Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision.

Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7 1/2 in x 4 1/2 in x 2 in. approx.

Complete assembly and wiring manual 25p, refundable on purchase of kit. Price: £10.50 plus 50p P. & P.

PSYCHEDELIC LIGHTING UNIT Mk. 3



This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size 9 in x 7 in x 3 in. Price £25 carr. paid.

PLEASE NOTE ALL THE ABOVE PRICES ARE SUBJECT TO V.A.T. ADJUSTMENT

DABAR ELECTRONIC PRODUCTS

98a Lichfield Street, Walsall, Staffs. WS1 1UZ

TELEPHONE: WALSALL 34365

TELEGRAMS: DABELEC Walsall Staffs.

ERSIN

Multicore
5 CORE SOLDER

for fast, easy
reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

EASY-TO-USE DISPENSERS



Size 5
Savbit alloy
18 swg, 18p
(illustrated).
Size 19A
60/40 alloy
18 swg, 18p
Size 15
60/40 alloy
22 swg, 22p

IDEAL FOR HOME CONSTRUCTORS

Size 1 cartons in 40/60, 60/40
and Savbit alloys
in 7 gauges 25p




Size 12
for Service
Engineers and
Electricians.

75ft of 18 swg
Savbit alloy, 75p



NEW! BIB WIRE STRIPPER AND CUTTER

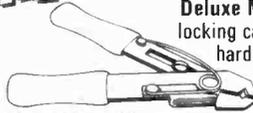

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T.
From Electrical and Hardware Shops. If unobtainable, send 10p p&p direct to:
Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

OPEN ALL DAY SATURDAYS

RESISTORS

1W Iskra high stability carbon film—very low noise—capless construction.
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm.
1W 2% ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price
1	5%	4.7Ω-2.2MΩ	E24	100+
1	10%	3.3MΩ-10MΩ	E12	1p
1	2%	10Ω-1MΩ	E24	3.5p
1	10%	1Ω-3.9Ω	E12	1p
1	5%	4.7Ω-1MΩ	E12	1p
4	10%	1Ω-10Ω	E12	6p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/2W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 10Ω, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0.1 inch max).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 6p each.

TRANSISTORS

AC107	15p	AF125	20p	BD132	75p	OC28	50p	2N3702	13p
AC126	12p	AF126	20p	BD133	75p	OC35	50p	2N3703	12p
AC127	12p	AF127	20p	BF115	25p	OC42	12p	2N3704	13p
AC128	12p	AF128	32p	BF173	20p	OC44	12p	2N3705	12p
AC131	12p	AF178	32p	BF177	28p	OC45	12p	2N3706	11p
AC132	12p	AF180	40p	BF178	32p	OC70	12p	2N3707	12p
AC176	12p	AF181	40p	BF179	32p	OC71	12p	2N3708	10p
AC187	22p	BC107	9p	BF180	32p	OC72	12p	2N3709	11p
AC188	22p	BC108	9p	BF181	32p	OC81	12p	2N3710	11p
AD140	50p	BC109	9p	BF194	15p	OC82D	12p	2N3711	11p
AD149	45p	BC147	13p	BF195	15p	2N2904	20p	2N4062	12p
AD161	36p	BC148	13p	BF197	15p	2N2926R	9p	40360	35p
AD162	36p	BC149	13p	BF200	32p	2N2926G	9p	40361	35p
AF114	20p	BC157	14p	BFY50	20p	2N2926V	9p	40362	40p
AF115	20p	BC158	14p	BFY51	20p	2N2926G	9p	40408	40p
AF116	20p	BC159	14p	BFY52	20p	2N2926G	9p	ZTX302	15p
AF117	30p	BC187	22p	BU105	225p	2N3054	58p	ZTX500	15p
AF124	22p	BD131	75p	OC26	45p	2N3055	60p	ZTX502	20p

ZENER DIODES

400mW 5% 3.3V to 30V, 12p. | WIRE WOUND POTS, 3W, 10, 25, 50Ω and decades to 100KΩ, 35p.

DIODES

RECTIFIER	Signal	Price
BY127	1250V 1A	12p
BZ107	800V 6A	25p
BZ113	200V 6A	20p
IN4001	50V 1A	7p
IN4004	400V 1A	8p
IN4007	1000V 1A	10p

SIGNAL

OA85	7p
OA90	5p
OA91	5p
OA202	7p
IN4148	5p
BA114	8p

BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2 1/2in = 10p; 9in x 2in = 7p

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.
SINGLE 10K, 25K, 100K log. or lin. 40p.
DUAL GANG, 10K + 10K etc. log. or lin. 60p.
KNOB FOR ABOVE 12p.
FRONT PANEL 65p.
18 Gauge panel 12in x 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THERMISTORS

VA10555	15p
VA10665	15p
VA1077	15p
R53	£1.35

COMPACT CASES—IN PLASTIC LIBRARY

BOX C90	65p
C120	85p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 21p. 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p. 0.047μF, 0.068μF, 0.1μF, 4p. 0.15μF, 6p. 0.22μF, 71p. 0.33μF, 11p. 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF 3 1/2p. 0.15μF 4 1/2p. 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 7 1/2p. 0.68μF, 11p. 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p. 0.033μF, 0.047μF, 0.068μF, 3 1/2p. 0.1μF, 4p. 0.15μF, 0.22μF, 5p. 0.33μF, 6 1/2p. 0.47μF, 8 1/2p. 0.68μF, 11p. 1.0μF, 13p. 1.5μF, 20p. 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 21p. 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3 1/2p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD O15/6/7 RANGE REPLACES C426, C457 RANGES.

(μF/V): 10/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/63, 33/40, 47/40, 47/25, 47/40, 47/63, 68/63, 68/16, 100/4, 100/10, 100/25, 100/40, 150/63, 150/16, 150/25, 220/4, 220/10, 220/16, 330/4, 330/10, 470/63, 5p each. 68/63, 150/40, 220/25, 330/16, 470/10, 680/63, 1,000/4, 9p, 100/63, 150/63, 220/40, 470/25, 680/16, 1,000/10, 1,500/63, 12p. 220/63, 470/40, 680/25, 1,000/16, 1,500/10, 2,200/63, 15p. 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10, 3,300/63, 4,700/4, 18p.

SOLID TANTALUM BEAD CAPACITORS 12p

0.1μF	35V	2.2μF	35V	22μF	16V
0.22μF	35V	4.7μF	35V	33μF	10V
0.47μF	35V	6.8μF	25V	47μF	6.3V
1.0μF	35V	10μF	25V	100μF	3V

ELECTROLYTIC CAPACITORS Miniature P.C. mounting 5p each.

(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

VEROBOARD

2 1/2 x 3 1/2	22p	0.15	16p
2 1/2 x 4	24p	0.15	16p
3 1/2 x 3 1/2	24p	0.15	16p
3 1/2 x 5	27p	0.15	16p
17 x 2 1/2	75p	0.15	16p
17 x 3 1/2	100p	0.15	16p
17 x 5 (plain)	—	0.15	16p
17 x 3 1/2 (plain)	—	0.15	16p
17 x 2 1/2 (plain)	—	0.15	16p
2 1/2 x 5 (plain)	—	0.15	16p
2 1/2 x 3 1/2 (plain)	—	0.15	16p
Pin insertion tool	52p		
Spot face cutter	42p		
Pkt. 50 pins	20p		

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin Plug 12p. Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable 22p/metre.

BATTERY ELIMINATOR £1.50

9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF 64V	74p	2500μF 64V	80p	4500μF 16V	50p
2500μF 40V	74p	2800μF 100V	£2.60	4500μF 25V	£1.68
2500μF 50V	58p	3200μF 16V	50p	5000μF 50V	£1.10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF	10p	0.047μF	13p	0.22μF	20p
0.022μF	12p	0.1μF	13p	0.47μF	22p

POLYSTYRENE CAPACITORS 160V 2 1/2%

10pF to 1,000pF E12 Series Values 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI £2

The GDI is the worlds first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.

PRINTED BOARD MARKER 97p

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

LARGE RANGE ITT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX
INTRODUCTORY OFFER: 15% DISCOUNT ON THE PRICES OF IC's ON ALL ORDERS RECEIVED BEFORE THE END OF MARCH, 1973


1-11	12-24	25-99	100+	7448	185	175	170	165	74118	100	82	73	64
7400	18	16	14	13	7450	18	16	14	74121	43	40	38	36
7401	18	16	14	13	7451	18	16	14	74141	100	95	90	85
7402	18	16	14	13	7453	18	16	14	74145	150	140	135	130
7403	18	16	14	13	7454	18	16	14	74150	330	280	250	220
7404	20	18	16	14	7460	18	16	14	74151	110	100	95	89
7405	20	18	16	14	7470	30	28	25	74153	200	110	105	95
7406	50	45	40	35	7472	30	28	27	74154	120	180	170	160
7407	56	50	44	38	7473	40	38	36	74155	150	120	100	86
7408	36	30	27	23	7474	40	36	32	74156	130	120	100	96
7409	36	30	27	23	7475	55	52	50	74180	155	136	112	105
7410	18	16	14	13	7476	40	36	32	74190	155	190	185	180
7411	23	21	20	18	7480	100	95	90	74191	195	190	185	180
7412	36	30	27	23	7481	125	115	110	74192	200	190	180	164
7413	34	28	26	22	7482	100	96	90	74193	200	180	170	150
7416	45	43	39	34	7483	100	97	95	74196	200	190	180	170
7420	18	16	14	13	7484	120	115	110	74197	200	195	180	170
7421	36	30	27	23	7485	250	245	240					
7426	32	29	23	20	7486	45	42	37					
7430	20	18	16	14	7487	75	67	60					
7432	40	36	32	28	7488	100	92	85	709	14 pin DIL			32p
7440	20	18	16	14	7491	100	70	65	741	8 pin DIL			34p
7441	80	75	70	65	7492	75	68	60	723	14 pin DIL			28p
7442	80	75	70	65	7493</								

Sinclair Project 60

Now—the Z.50 Mk.2


with built-in automatic transient overload protection

When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use, is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symmetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50; circuitry has been re-designed, making this versatile high performance amplifier better than ever.

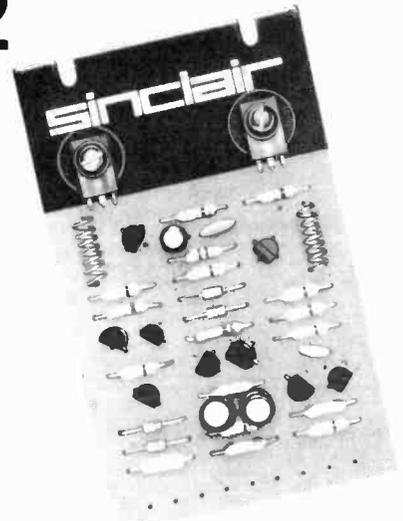

with free manual
£5.48

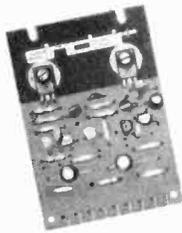Z.30 the power amplifier for quality and economy




with free manual
£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm (3 1/4 x 2 1/4 x 1/2). Z.30, Z.50 and Z.50 MK.2 modules are compatible and interchangeable.

Brilliant new technical specifications

Input impedance 100 K Ω
Input (for 30w into 8 Ω) 400mV
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better
Distortion 0.02% up to 20W at 8 Ω . See curve
Frequency response 10Hz to more than 200 KHz \pm 1dB
Max. supply voltage 45v (4 Ω to 8 Ω speakers) (50v 15 Ω speakers only)
Min. supply voltage 9v
Load impedance — minimum: 4 Ω at 45v HT
Load impedance — maximum: safe on open circuit

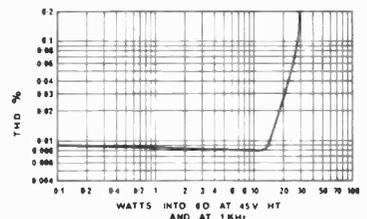

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave deluxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

Guarantee


If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

sinclair

the world's most advanced high fidelity modules

Stereo 60 Pre-amp/control unit

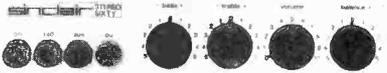

Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio – up to 3mV, Mag. p.u. 3mV, correct to R.I.A.A. curve ± 1 dB. 20 to 25,000 Hz. Ceramic p.u. – up to 3mV. Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +12 to –12dB at 10KHz. BASS +12 to –12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed. **£9.98**

Project 60 Stereo F.M. Tuner




The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7 μ V for lock-in over full deviation. **Squelch level:** Typically 20 μ V. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10Hz – 15KHz (± 1 dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 μ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25–30VDC. **Indicators:** Stereo on; tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**

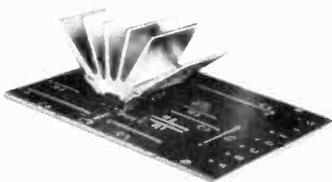Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC. make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS


Output power: 6 watts RMS continuous (12 watts peak) 6–8 Ω . **Frequency Response:** 5Hz to 100KHz ± 1 dB. **Total Harmonic Distortion:** Less than 1% (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.

£2.98 Post free

Power Supply Units The new PZ.8 Mk.3

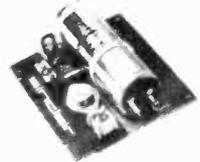

The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK.2 amplifiers are used. Nominal working voltage – 45

PZ.8 Mk.3—£7.98

(Mains transformer, if required) £5.98

PZ.5 30v. un stabilised

(not suitable for Project 60 tuner) £4.98

PZ.6 35v. stabilised

(not suitable for IC. 12) £7.98

Project 605



the easy way to
buy and build
Project 60
without
soldering

Project 605 in one pack contains: one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free
All you need for a superb 30 watt high fidelity stereo amplifier

£29.95

Order form

Please send

I enclose cash/cheque/money order

Name _____

Address _____

PE/4/73

SINCLAIR RADIONICS, Business Reg. No. 699483:
London Rd, St. Ives, Hunts. PE17 4HJ

sinclair

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206


MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N.9 803 1685

LOW VOLTAGE AMPLIFIER

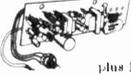5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output.
With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.



£1.75

plus 13p P. & P.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7, or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Our Price £2.75 plus 10p P. & P. Same model suitably wired for the Philips Cassette £3 plus 10p P. & P.




DIGITAL CLOCK KIT

24-hr. Nixie dig. clock kit. We supply: a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. £22.50 + 50p P. & P. Please send S.A.E. if you require more information.

V.A.T.
From 1st April, 1973, you will please include on your Total (Goods plus Postage and Packing) Value Added Tax at the Standard Rate.

EA1000 3 WATT AUDIO AMPLIFIER

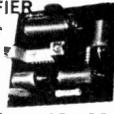An Audio Amplifier designed around the TAA621 Linear I.C.—
Supply Voltage 9-24V
Speaker Imp. 8-16 ohm
Frequency 50Hz-25kHz
Overall Size 2in x 3in x 2 1/2in
Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at + 5p P. & P.



£2.63

S.G. BROWN "DIPLOMAT" MONO/STEREO HEADSET

Finest quality British made Light weight Headphones. Incorporate ceramic piezo electric Transducers. Specifications:—Frequency 20-17,500 CPS. Impedance Predominantly capacitive, at 001MFD per earpiece can be regarded as 150K at 1Kcs. Weight—3.5oz. (98 grams). Please include 10p per set P.P. A Bargain at £1.50 each set.



TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2 1/2in. x 3 1/2in. x 3 1/2in. This converter supplies 6, 7, or 9 volts and is transistor regulated. A real money saving device for £2.50 plus 10p P. & P.

MINIATURE RELAY

6 volt 70 ohm. Single Pole Changeover 40p plus 5p P. & P. Approx. size = 1 1/2in. x 1in. x 2 1/2in.

ADD LUXURY TO YOUR CAR

WITH A MOTOR DRIVEN CAR AERIAL

Spec: 3 Section
Aerial Length 100cm
Length under Fender 40cm
Cable Length 120cm
Supplied complete with Fixing Bracket and plus 25p
Control Switch. £5.75 P. & P.




MAINS TRANSFORMER

Fused Primary 240V. Secondary 220V or 50mA. 6.5V or 1A. This transformer is made to a very high standard and is a small size: 2 1/2in x 2 1/2in x 2 1/2in. 68p plus 10p P. & P.



EMI LOUSPEAKER 450

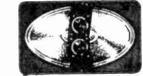10W 13in x 8in ± two 2 1/2in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp. £3.75 plus 38p P. & P. each.



CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60 28p, C90 38p, C120 48p plus 5p P. & P.

PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass Middle-Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500V lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) £18.50 plus 38p P. & P.



If you require more information please send S.A.E.

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U.BUILD IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

- ★ THE POWER AMP MODULE TP100W 170W r.m.s. 40 wave 300W instantaneous peak into 8 ohm (60W into 16 ohm). £14.28 carr. 45p
- ★ THE PRE-AMP MODULE Four control pre-amp. Vol, Bass, Treble, Middle controls. Designed to drive most amplifiers using F.E.T. first stage. £23.96 carr. 25p
- ★ THE POWER SUPPLY MODULE PS100 Is supplied complete with mains transformer. £9.68 carr. 50p Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. If you purchase all three modules. £25 carr. 75p Send S.A.E. for further details on this or our ready built amplifiers.


BRIGHTNESS CONTROL

Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a M.K. Box. Enjoy the pleasure of having the precise amount of light you require at any time. Our Price £2.75 plus 8p P. & P. each.



PHOTOELECTRIC KIT

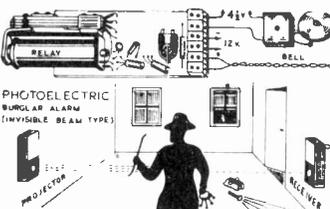CONTENTS: P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for motived-light operation with a few additional components.



PHOTOELECTRIC KIT £2.85

Postage and Pack. 16p (U.K.)
Commonwealth
SURFACE MAIL 25p
AIR MAIL £1.40
Australia, New Zealand, S. Africa, Canada and U.S.A.
Also Essential Data Circuits and Plans for Building 10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.
CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks. Infra-red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price £1.45. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £2.10. Postage 15p (U.K.). Commonwealth: Surface 20p, Air Mail £1.15.

BIOFEEDBACK AMPLIFIER KIT

Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brainwaves, learn to relax, meditate, etc.
CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C., Electrodes, Leads, Chassis, Case, Batteries, Plans and Instructions. Price £4.75 postage and pack. 25p (U.K.). Commonwealth: Surface 30p. Air Mail £1.

ALPHA-BETHA-THETA BRAINWAVE MONITOR KIT

Aural Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.
CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis, Case, Earphone, Battery, Plans and Instructions. Price £3.25. postage and pack. 15p (U.K.). Commonwealth: Surface 25p. Air Mail 75p.

YORK ELECTRICS Mail Order Dept.
335 BATTERSEA PARK ROAD, LONDON, S.W.11
Send S.A.E. for full details, a brief description of all Kits and Projects

COMPARE OUR PRICES

Speaker Bargains	£p	ACOS GP91/28C or GP91/38C stereo compatible	1.05
E.M.I. 13in x 8in 3, 8 & 15 ohms plain	2.00	ACOS GP94 stereo ceramic	1.75
with tweeter	2.25	ACOS GP95 stereo crystal	1.85
1W tweeter	3.50	ACOS GP96 stereo ceramic	1.75
Type 350 -30 watt with tweeter 8 ohms, P.P. 37p.	7.25	9THAC Sonotone stereo ceramic (diamond)	1.95
8in x 5in 3, 8 & 15 ohms	1.30	9THAC Sonotone stereo ceramic (diamond) Shilind	1.95
7in x 4in 3 & 8 ohms	1.05	ACOS GP67/20 mono crystal	65
FANE 8in 8 ohms, dual cone	2.30	ACOS GP101 stereo crystal	75
CELESTION 8in 15 ohm	1.50	19-TI Sonotone stereo crystal	80
BAKER GROUP 25 12in 25W 8 or 15 ohm	5-75	Postage up per cartridge	
Postage 25p per speaker			
2 1/2in 8 or 64 ohm P.P. 10p	50		

Kil-torm cabinets, leak	£p	Battery Eliminators	£p
(17in x 10in x 6in)	2.75	240v input 6 or 9s d.c. output at 160 mA	1.99
with a 130ml 8in or 8in cut out		240v input 6, 7, or 8v output at 300 mA	2.99
(12in x 12in x 6in) with a 8in 6in or 8in cut out.	2.25	12v d.c. input (for cars) 6, 7, or 9v d.c. output at 300 mA	2.99
(please specify cut out)		P. & P. 10p	
8 or 15 ohm			
Postage 25p per speaker			
2 1/2in 8 or 64 ohm P.P. 10p	50		

Microphone Bargains	£p	Tapes "MYLAR" base finest quality British made.	£p
MIC45 "ACOS" metal case, crystal hand	95	5in 600ft 35p	5in 1800ft 85p
CM 20 Crystal Hand	45	5in 900ft 45p	7in 1200ft 55p
DX143 Dynamic, cassette-type stick	1.00	5in 1200ft 60p	7in 1800ft 80p
MIC60 "ACOS" stick crystal	1.00	5 1/2in 900ft 45p	7in 1200ft 55p
CM70 ELANET stick metal, switch crystal	1.45	5 1/2in 1200ft 55p	7in 2400ft 95p
DM160 Dynamic uni-dir, ball metal	3-75	Postage 9p each	
UD130 50K/600 ohm uni-dir, ball metal	4-50		
TW209 Leason dual imp ball metal uni-dir	5-75		
Condenser Mike uni-dir 600 ohm	7-95		
Guitar mike	45		
Lapel type, crystal	40		
Postage 17p each			

Cartridges—with standard fittings & styli
GOLDRING G850 3.25
GOLDRING G800 4.95

THIS MONTH'S SPECIAL OFFER
Amrad Stereo Headphones
Model HPS 5A with v.c. controls. Recommended retail price £6.95. Our price £3.95. P. & P. 25p

Slight price alterations due to V.A.T. will effect certain of our items after April 1st.

RIVERSDALE ELECTRONICS
ALL OUR MERCHANDISE IS FULLY GUARANTEED

Mail Order Dept. E4/73,
P.O. Box 470,
Manchester M60 4BU
SEND 25p FOR COMPLETE CATALOGUE

BRITAIN'S FASTEST SERVICE!



A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	6p	BCY58	18p	CA3043	£1.73	OA81	8p	1N4007	19p	2N6027(D13T1)
AC107	40p	BCY70	15p	CA3044	£1.42	OA90	8p	1N4148	4p	
AC126	20p	BCY71	30p	CA3046	86p	OA91	5p	1N5400	18p	3N84
AC127	25p	BCY72	15p	CA3048	£2.34	OA95	5p	1N5404	80p	3N128
AC128	24p	BD124	75p	CA3052	£1.80	OA200	6p	1N5408	25p	3N140
AC128/AC176		BD131	75p	CA3065	£1.80	OA202	7p	1S44	4p	3N152
		BD132	75p	CA3088E	£1.38	OC20	97p	1S920	7p	3015F
AC151	12p	BD131/132	£1.50	CA3090Q	£4.70	OC25	37p	1S940	6p	3015G
AC152	15p	BDY20	92p	CD4001AE	72p	OC28	70p	1S5009	80p	7400
AC153	19p	BF115	23p	CD4009AE	£1.56	OC29	70p	1S5012	80p	7401
AC176	16p	BF163	35p	CD4011AE	72p	OC35	60p	1S5015	75p	7402
AC153/176K	32p	BF167	18p	CD4012AE	£1.16	OC36	63p	1S5018	75p	7403
AC187	17p	BF173	19p	CD4013AE	£1.48	OC41	40p	1S5024	75p	7404
AC188	23p	BF177	25p	CD4015AE	£3.90	OC42	40p	1S5047	75p	7405
AC187/188K	23p	BF178	31p	CD4017AE	£3.90	OC44	20p	1N4004	23p	7408
ACY17	27p	BF180	35p	CD4018AE	£3.90	OC45	20p	1N6996	15p	7409
ACY18	20p	BF194	15p	CD4020AE	£4.34	OC71	20p	2N697	17p	7410
ACY19	20p	BF195	15p	CD4024AE	£2.78	OC72	20p	2N698	30p	7413
ACY20	20p	BF196	15p	CR1/051C	45p	OC75	25p	1N706	10p	7420
ACY21	19p	BF200	35p	CR1/401C	60p	OC76	25p	2N706A	12p	7425
ACY22	10p	BF254	14p	CRS3/05AF	£1.08	OC77	40p	2N708	16p	7430
AD140	55p	BF255	15p	CRS3/40AF	£1.53	OC81	20p	2N911	50p	7440
AD149	50p	BFX13	25p	CZ6	15p	OC81D	20p	2N914	20p	7442
AD161	35p	BFX29	25p	D10 (NTGD10)	40p	OC83	23p	2N918	42p	7443
AD162	38p	BFX84	25p	IRT84	£2.90	OC89	25p	2N929	25p	7444
AD161/162	70p	BFX85	34p	LIC709C/5	42p	OC139	25p	2N930	25p	7445
AF106	24p	BFX86	25p	LIC723C/14	£1.00	OC140	40p	2N1131	24p	7446
AF114	25p	BFX87	24p	LIC741C/8	45p	OC170	25p	2N1132	24p	7447
AF115	25p	BFX88	24p	LIC741C/8	45p	OC171	30p	2N1302	17p	7450
AF116	25p	BFY50	15p	LIC741C/8	45p	OC172	42p	2N1303	17p	7451
AF117	25p	BFY51	15p	LIC741C/8	45p	OC173	42p	2N1304	17p	7452
AF118	44p	BFY52	15p	LIC741C/8	45p	OC174	42p	2N1305	24p	7454
AF124	25p	BFY53	17p	LIC741C/8	45p	OC175	42p	2N1306	30p	7455
AF125	24p	BFY90	£1.05	LIC741C/8	45p	OC176	42p	2N1307	30p	7470
AF126	17p	BP101	75p	MC1303P	£1.75	OC177	9p	2N1308	34p	7472
AF139	30p	BPX66	£1.35	MC1305P	£2.20	OC178	9p	2N1309	34p	7473
AF186	40p	BRY39	40p	MC1307P	£1.65	OC179	7p	2N1559 (CR1)	60p	7474
AF239	36p	BSX19	16p	MC1310P	£2.95	OC180	7p	401C	80p	7475
AF279	47p	BSX20	16p	MC1312P	£2.75	OC181	7p	401C	15p	7476
ASV26	25p	BSX21	20p	MC1330P	£2.00	OC182	7p	401C	15p	7477
ASV27	30p	BSY27	20p	MC1352P	£2.00	OC183	20p	2N1711	54p	7480
ASV28	22p	BSY29	25p	MC4024P	£2.20	OC184	20p	2N1893	54p	7482
ASV29	30p	BSY95A	12p	MC4044P	£2.20	OC185	28p	2N2218	33p	7483
BA138	15p	BY100	20p	MFC6030	£1.63	OC186	44p	2N2218A	44p	7486
BA136	8p	BY127	22p	MFC6040	£1.15	OC187	20p	2N2219	53p	7490
BB103	16p	BTY79/400R	92p	MFC8010	£1.38	OC188	60p	2N2219A	53p	7491A
BB104	28p	BT106	£1.20	MFC8040	£1.24	OC189	80p	2N2219A	17p	7492
BB105	32p	BZY88C/3V	13p	MFC9020	£1.24	OC190	17p	2N2369	17p	7493
BC107	10p	BZY88C/3V6	13p	MJE371	68p	OC191	17p	2N2369A	17p	7494
BC107/BC177		BZY88C/4V3	13p	MJE520	62p	OC192	42p	2N2484	42p	7495
BC108	24p	BZY88C/4V3	13p	MJE521	62p	OC193	42p	2N2646	45p	7496
BC108/BC178		BZY88C/4V7	13p	MJE2955	£1.06	OC194	44p	2N2904	44p	74100
BC109	10p	BZY88C/5V1	13p	MJE3055	66p	OC195	49p	2N2904A	49p	74107
BC109/BC179		BZY88C/5V6	13p	MJ480	97p	OC196	65p	2N2905	65p	74121
BC109	10p	BZY88C/6V2	13p	MJ481	97p	OC197	75p	2N2905A	75p	74141
BC109/BC179		BZY88C/6V8	13p	MJ491	£1.25	OC198	18p	2N2924	18p	74150
BC109C	24p	BZY88C/7V5	13p	MJ802	£4.12	OC199	20p	2N2925	20p	74151
BC140	11p	BZY88C/8V2	13p	MJ802/MJ4502	£1.20	OC200	10p	2N2926	10p	74153
BC147	30p	BZY88C/10V	13p	MJE56	£8.56	OC201	60p	2N3053	27p	74154
BC148	9p	BZY88C/11V	13p	MJ900	£1.80	OC202	70p	2N3054	50p	74155
BC149	10p	BZY88C/12V	13p	MJ1000	£1.50	OC203	80p	2N3055	50p	74156
BC157	12p	BZY88C/13V	13p	MJ4502	£4.44	OC204	£1.00	2N3391A	25p	74190
BC158	11p	BZY88C/15V	13p	MPF102	£7.50	OC205	30p	2N3525	£1.04	74191
BC159	12p	BZY88C/16V	13p	MPF103(2N5457)	VA10665	OC206	15p	2N3702	9p	74192
BC147/157		BZY88C/18V	13p	MPF104(2N5458)	VA1039	OC207	15p	2N3703	9p	74193
BC148/158		BZY88C/21V	13p	MPF105(2N5459)	VA1077	OC208	15p	2N3704	9p	74196
BC149/159		BZY88C/22V	13p	MPF105(2N5459)	W005	OC209	15p	2N3705	9p	74198
BC167	11p	BZY88C/24V	13p	NKT0033	46p	OC210	30p	2N3706	9p	40250
BC168	10p	BZY88C/27V	13p	NKT0033	46p	OC211	30p	2N3707	9p	40309
BC169	11p	BZY88C/30V	13p	NKT0033	46p	OC212	30p	2N3708	9p	40310
BC169C	11p	BZY88C/31V	13p	NKT0033	46p	OC213	30p	2N3709	9p	40311
BC177	14p	BZ X61C/8V2	23p	NKT0212	25p	OC214	35p	2N3710	9p	40312
BC178	13p	BZ X61C/9V1	23p	NKT0213	25p	OC215	44p	2N3711	9p	40320
BC179	14p	BZ X61C/10V	23p	NKT0216	26p	OC216	25p	2N3819	25p	40360
BC182	10p	BZ X61C/11V	23p	NKT0217	25p	OC217	11p	2N3823E	20p	40362
BC182L	10p	BZ X61C/12V	23p	NKT0218	25p	OC218	18p	2N3826	20p	40366
BC183L	10p	BZ X61C/15V	23p	NKT0223	27p	OC219	15p	2N3866	£1.10	40407
BC184	13p	BZ X61C/16V	23p	NKT0274	18p	OC220	23p	2N3904	28p	40408
BC184L	12p	BZ X61C/18V	23p	NKT0275	20p	OC221	28p	2N4058	28p	40409
BC212	12p	BZ X61C/20V	23p	NKT279A	12p	OC222	13p	2N4058	13p	40410
BC212L	12p	BZ X61C/22V	23p	NKT281	29p	OC223	30p	2N4061	11p	40432
BC238	10p	BZ X61C/24V	23p	NKT282	29p	OC224	11p	2N4062	11p	40468A
BC238/308		BZ X61C/27V	23p	NKT401	71p	OC225	18p	2N4444	£2.20	40512
BC257	9p	BZ X61C/30V	23p	NKT402	77p	OC226	17p	2N4871	40p	40576
BC258	8p	CA3004	£2.25	NKT403	65p	OC227	45p	2N5245	45p	40600
BC259	9p	CA3005	£1.50	NKT404	60p	OC228	20p	2N5457(MPF103)	40p	40601
BC307	12p	CA3011	92p	NKT405	79p	OC229	4p	2N5458(MPF104)	49p	40602
BC308	10p	CA3013	£1.30	NKT406	62p	OC230	7p	2N5458(MPF104)	49p	40603
BCY30	25p	CA3014	£1.52	NKT407	29p	OC231	10p	2N5459(MPF105)	46p	40673
BCY31	48p	CA3018	88p	NKT773	25p	OC232	15p	2N5777	45p	40739
BCY32	50p	CA3018A	£1.19	NKT781	29p	OC233	10p			
BCY33	20p	CA3020	£1.55	NTGD10	40p	OC234	10p			
BCY34	25p	CA3028A	88p	OA47	8p	OC235	12p			
BCY38	30p	CA3035	£1.52	OA79	8p	OC236	15p			

ELECTROLYTIC AXIAL LEADS

Mfd.	Working Voltage	Price	Mfd.	Working Voltage	Price
1.0	40v	7p	100	16v	6p
2.2	100v	5p	100	25v	6p
2.2	25v	7p	100	40v	7p
2.2	63v	5p	100	63v	10p
4.7	40v	5p	220	25v	8p
10	25v	5p	220	40v	9p
16	63v	6p	470	25v	12p
22	25v	6p	1000	25v	16p
20	40v	6p	2200	25v	30p
47	25v	6p	4700	16v	33p
25	40v	6p			

CAPACITORS—METALLISED POLYESTER

Stock values: MFD Price each

0.01, 0.015, 0.022, 0.033	3p
0.047, 0.068, 0.10	4p
0.150, 0.220	5p
0.33	7p

TRANSFORMERS

MAINS ISOLATING SERIES
Primary 200-250 Volts Secondary 240 Volts Centre
Tapped (120V) and Earth Shielded
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ d
07	20	1 11	7.0 x 6.0 x 6.5	1.61 30
100	60	3 8	8.9 x 8.0 x 7.7	2.39 36
61	100	5 12	10.2 x 8.9 x 8.3	2.62 52
30	200	9 8	12.0 x 10.3 x 10.0	4.39 52
62	250	12 4	9.5 x 12.7 x 11.4	5.80 67
55	350	15 0	14.0 x 10.8 x 12.4	7.77 82
63	500	27 0	17.1 x 11.4 x 15.9	11.20 ..
92	1000	40 0	17.8 x 17.1 x 21.6	20.63 ..
128	2000	63 0	24.1 x 21.6 x 15.2	34.10 ..

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ d
113	20	1 11	7.3 x 4.3 x 4.4	0-115-210-240	0.85 22
64	75	1 14	7.0 x 6.4 x 6.0	0-115-210-240	1.66 30
4	150	3 0	8.9 x 6.4 x 7.6	0-115-200-220-240	2.00 36
66	300	6 0	10.2 x 10.2 x 9.5	..	3.89 52
67	500	12 8	14.0 x 10.2 x 11.4	..	5.78 67
84	1000	16 0	11.4 x 14.0 x 14.0	..	10.49 82
93	1500	28 9	13.5 x 14.9 x 16.5	..	15.20 ..
95	2000	40 0	17.8 x 16.5 x 21.6	..	19.84 ..
73	3000	45 8	17.4 x 18.1 x 21.3	..	26.99 ..

TOTALLY ENCLOSED 115V AUTO TRANSFORMERS
115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets. £7.87. P & P 67p.
Also available a 20 Watt version. £1.67. P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)

Ref. No.	12V	24V	Amps.	Weight lb oz	Size cm.	Secondary Windings	P & P £ d
111	0.5	0.25	12	7.6	5.7 x 4.4	0-12V at 0.25A x 2	0.85 22
213	1.0	0.5	1	8.3	5.1 x 5.1	0-12V at 0.5A x 2	1.01 22
71	2	1	1	7.0	6.4 x 5.7	0-12V at 1A x 2	1.33 22
18	4	2	1	8.3	7.0 x 7.0	0-12V at 2A x 2	1.86 36
70	6	3	12	10.2	7.6 x 8.6	0-12V at 3A x 2	2.24 42
108	8	4	5	10.0	8.3 x 8.2	0-12V at 4A x 2	2.48 52
72	10	5	6	7.9	10.8 x 10.2	0-12V at 5A x 2	2.94 52
17	16	8	7	12.1	9.5 x 10.2	0-12V at 8A x 2	4.54 52
115	20	10	11	12.1	11.4 x 10.2	0-12V at 10A x 2	5.78 67
187	30	15	16	12.1	13.3 x 12.1	0-12V at 15A x 2	10.67 82
226	60	30	34	17.0	14.5 x 12.5	0-12V at 30A x 2	19.61 ..

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ d
112	0.5	1 4	8.3 x 3.7 x 4.9	0-12-15-20-24-30V	1.01 22
79	1.0	2 0	7.0 x 6.4 x 6.0	..	1.35 36
3	2.0	3 2	8.9 x 7.0 x 7.6	..	2.01 36
20	3.0	4 6	10.2 x 8.9 x 8.6	..	2.48 42
21	4.0	6 0	10.2 x 10.0 x 9.6	..	2.94 52
51	5.0	6 8	12.1 x 10.0 x 8.6	..	3.66 52
117	6.0	7 8	12.1 x 10.0 x 10.2	..	4.36 52
88	8.0	10 0	14.0 x 11.7 x 10.0	..	5.64 67
89	10.0	12 2	14.0 x 10.2 x 11.4	..	7.14 67

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ d
102	0.5	1 11	7.0 x 7.0 x 5.7	0-19-25-33-40-50V	1.33 30
103	1.0	2 10	8.3 x 7.3 x 7.0	..	1.94 36
104	2.0	5 0	10.2 x 8.9 x 8.6	..	2.69 42
105	3.0	6 0	10.2 x 10.2 x 8.3	..	3.65 52
106	4.0	9 4	12.1 x 11.4 x 10.2	..	4.83 52
107	6.0	12 4	12.1 x 11.1 x 13.3	..	7.14 67
118	8.0	18 9	13.3 x 13.3 x 12.1	..	9.32 97
119	10.0	19 12	16.5 x 11.4 x 15.9	..	11.68 97

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P £ d
124	0.5	2 4	8.3 x 9.5 x 6.7	0-24-30-40-48-60V	1.35 36
126	1.0	3 0	8.9 x 7.6 x 7.6	..	1.88 36
127	2.0	5 6	10.2 x 8.9 x 8.6	..	2.94 42
125	3.0	8 0	11.9 x 9.5 x 10.0	..	4.48 52
123	4.0	10 6	11.4 x 9.5 x 11.4	..	5.78 67
120	6.0	16 12	13.3 x 12.1 x 12.1	..	8.37 82
122	10.0	23 2	16.5 x 12.7 x 16.5	..	13.85 ..

Ref. No.	Amps.	Weight lb oz	Size cm.	P & P £ d
45	1.5	1 9	7.0 x 6.0 x 6.0	1.34 30
5	4.0	3 11	10.2 x 7.0 x 8.3	2.03 42
86	6.0	5 12	10.2 x 8.9 x 8.3	3.07 52
146	8.0	6 12	8.9 x 10.2 x 10.2	3.49 52
50	12.5	11 14	13.3 x 10.8 x 12.1	5.20 67

All ratings are continuous. Standard construction: open with solder tags and wax impregnation. Enclosed styles to order.

FULL SPEC. TRANSISTORS
BC107/108/109 9-0p each 2N 3055 68p each AD 161/162 60p pair
25 + 7p + mica and bushes + mica and bushes
100 + 65p 25 + 55p 25 + 55p
500 + 6p 100 + 45p 100 + 50p
Minimum order 10 pieces this range. 500 + 40p 1000 + 45p

AVOMETERS • MAINS KEYNECTOR
ELECTROSIL RESISTORS

*CARRIAGE VIA BRB

BARRIE electronics

11 MOSCOW ROAD, QUEENSWAY
LONDON W2 4AH. Tel: 01-229 6681/2
NEAREST TUBE STATIONS: BAYSWATER, QUEENSWAY

B.H. COMPONENT FACTORS LIMITED

SPECIAL RESISTOR KITS (±W 5% or ±W 5% CARBON FILM)
10E12 Kit: 10 of each E12 value, 10 ohms—1M, a total of 610, £2.80 net
25E12 Kit: 25 of each E12 value, 10 ohms—1M, a total of 1,525, £6.50 net

POLYESTER CAPACITORS MULLARD C280 250V
µF: 0.01, 0.015, 0.022, 0.033, 0.047, 3p each; 0.068, 0.1, 0.15, 4p each; 0.22, 5p; 0.33, 7p; 0.47, 8p; 0.68, 10p; 1.0, 13p; 1.5, 20p; 2.2, 23p

MULLARD POLYESTER CAPACITORS C296 SERIES
160V: (µF) 0.01, 0.015, 0.022, 2p; 0.047, 0.068, 3p; 0.15, 0.22, 4p; 0.33, 5p; 0.47, 6p; 0.68, 1.0, 10p.
400V: (µF) 0.001, 0.0015, 0.0022, 0.0033, 0.01, 2p; 0.015, 0.033, 3p; 0.068, 4p.

MINIATURE ELECTROLYTIC MULLARD C426 SERIES (3p each)
(µF/V) 1/63, 4/40, 8/40, 10/40, 10/64, 16/40, 20/64, 25/25, 32/10, 40/16, 64/10, 80/16, 80/25, 100/6, 4, 125/16, 200/6, 4, 200/10, 320/6, 4, 125/10.
MULLARD C437: (µF/V) 64/64, 9p; 160/25, 9p; 160/40, 11p; 640/6, 4, 9p; 1600/6, 4, 14p.

ELECTROLYTIC CAPACITORS. Tubular and large can
(µF/V) 2.5/50, 3p; 4/10, 10/25, 16/15, 20/25, 25/15, 25/25, 40/6, 64/10, 200/6, 250/10, 4p; 10/6, 10/50, 25/50, 32/50, 50/10, 64/25, 100/25, 5p; 50/50, 64/40, 250/15, 1.000/3, 6p; 100/50, 250/25, 400/10, 500/10, 500/12, 640/10, 1.000/6, 8p; 500/25, 10p; 500/50, 12p; 1.000/12, 10p; 1.000/25, 2.000/12, 2.500/12, 15p; 1.000/50, 35p; 2.000/25, 25p; 2.500/25, 30p; 2500/50, 55p; 3.000/50, 65p; 5.000/50, 85p; 1.000/100, 60p; 8/350, 12p; 16/350, 17p; 32/350, 22p.

MINIATURE CERAMIC PLATE CAPACITORS
50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8. (µF) 0.01, 0.015, 0.022, 0.033, 2p, 0.047, 30V, 3p, 0.1, 1.00V, 5p.

CARBON FILM RESISTORS ±W 5%, 10 ohms—2.2M, ±W 5%, 22 ohms—1M. 1p each or 100 for 55p; 1.000 for £4.

METAL FILM RESISTORS ±W 5%, 22 ohms—10M, 1p each or 100 for £1.

VEROBOARD	0.1	0.15	IN4001	6p	QUANTITY DISCOUNT SPECIAL BULK BUY PRICES ARE AVAILABLE BY QUOTATION FOR LARGE PROJECTS VAT. Please add VAT at the standard rate after 1st April
24 x 5in	25p	25p	IN4002	7p	
24 x 3in	23p	17p	IN4003	7p	
32 x 5in	29p	30p	IN4004	9p	
32 x 3in	25p	25p	IN914	6p	
24 x 5in lin 2 for 12p	12p	12p	µL914	30p	
24 x 5in (plain)	—	12p	OC71	12p	
24 x 3in (plain)	—	11p	OC75	15p	
5 x 3in (plain)	—	20p	OC83	18p	
Insertion tool	54p	54p			
Track cutter	40p	40p			
Pins, pkt. 25	8p	8p			

2 pin DIN Plug, 12p; Skt., 10p; 3 pin DIN Plug, 13p; 3 core circ. mains cable White, 3 yds., 24p; Skt., 10p; 5 pin DIN Plug, 18p; 180V, 15p; 5kt., 12p. Transistor Equip. Book, 40p; Carbon pots 5K-2M log, & lin, single 15p, single with switch 24p, dual 42p.

Dept. P.E. 61, CHEDDINGTON ROAD, PITSTONE
Near LEIGHTON BUZZARD, BEDS, LU7 9AQ
Tel.: Cheddington 668446 STD. (0296)
Inquiries—S.A.E. Catalogue FREE Callers please phone first.

AUTOMATIC EMERGENCY SUPPLY

250v 50 Hz—150 watt Inverter. Full kit of parts excluding meter. Circuit as appeared in December P.W. Complete kit—£16.95 + 80p. P. & P.

OTHER INVERTERS AVAILABLE IN KIT FORM

150 Watt—£13.50 + 60p P. & P. 75 Watt—£7.80 + 60p P. & P.
300 Watt—£17.90 + 85p P. & P. 40 Watt—£5.20 + 40p P. & P.
25 Watt—£2.60 + 20p P. & P.

All above operate from 12v. battery and give 250v.—50Hz. Output. 24 volt types are also available, alternative outputs or taps can be supplied. Transformers and/or Transistors can be supplied separately.

SPECIAL OFFER

12v. Fluorescent lights, suitable for tents, caravans, houses or secondary lighting for factories, hotels, etc. 12 inch—8 watt—£3.40 post paid, 21 inch—13 watt—£4.20 post paid. Large discounts available for quantities.

TEXAN AMPLIFIER

Fibre glass P.C. board—£2.00 + 10p P. & P.
Transformer—£4.00 + 30p P. & P.
Other components including Teak Cabinet—£24.00 + Postage.

ASTRO ELECTRONICS

6 BARNES ROAD, CHESTERFIELD, DERBYSHIRE

A.M.C. ELECTRONICS LTD.

SCORPIO ELECTRONIC IGNITION UNIT

COMPLETE KIT WITH ALL PARTS AND COMPREHENSIVE CONSTRUCTION AND FAULT FINDING DATA

COMPLETE KIT £11.00 + V.A.T. ... post paid.
DATA 10p → V.A.T. ... S.A.E. (Footscap please).
TRANSFORMER £2.30 + V.A.T. ... post paid.
P.C.B. GLASS FIBRE 65p + V.A.T. ... post paid.
LATEST NEWS — P.E. TRIFFID. P.C.B. 65p post free.
Please add 15p to orders under £1.50. Send S.A.E. for other itemised prices.

AMCEL, MAIL ORDER 160 DRAKE STREET, ROCHDALE, LANCASHIRE OL16 1RY

SINE to SQUARE CONVERTOR
5Hz to 250kHz
9V operation. Sine input 1-15V—output 0-7V. Completely assembled with amplitude control and mark space preset, £2.25 ea. P. & P. 15p.

MODERN TELEPHONES type 706.
Two tone grey, £3.75 ea. The same but black, £2.75 ea. P. & P. 25p ea.
AS NEW type 706 **BLUE**, £5 ea. P. & P. 25p.
Also **TOPAZ YELLOW** £4.50 ea. P. & P. 25p.
STANDARD GPO DIAL TELEPHONE (black) with internal bell, 87p ea. P. & P. 50p. Two for £1.50. P. & P. 75p. All telephones complete with bell and dial.

MULLARD ELECTROLYTICS
2200MFD 100V
10A (50°C)
70p each
BRAND NEW BOXED
10 off—60p each
100 off—45p each
47000 MFD 25V 28A
60p each
P. & P. 10p

LARGER REDUCTION FOR QUANTITY

POTENTIOMETERS

COLVERN 3 watt. Brand new, 5; 10; 25; 500 ohms; 1; 2.5; 5; 10; 25; 50K all at 13p ea.
MORGANITE Special Brand new, 2.5; 10; 100; 250; 500K; 2.5 meg. 1in sealed, 17p ea.
BERCO 2½ Watt. Brand new, 5; 10; 50; 250; 500 ohms; 1; 2.5; 5; 10; 25; 50K at 15p ea.
STANDARD 2 meg. log pots. Current type 15p ea.
INSTRUMENT 3in Colvern. 5 ohm 35p ea.; 50K and 100K 50p ea.
BOURNS TRIMPOT POTENTIOMETERS. 10; 20; 50; 100; 200; 500 ohms; 1; 2; 2.5; 5; 10; 25K at 35p ea. ALL BRAND NEW.
RELIANCE P.C.B. mounting: 270; 470; 500 ohms; 10K at 35p ea. ALL BRAND NEW.

20Hz to 200kHz WB SINE AND SQUARE GENERATOR

Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £6.85 each. P. & P. 25p. (Not cased, not calibrated.)

WOBBULATOR

Sweeps 8 to 45MHz ready to use. 6.3V a.c. required. £9 each. P. & P. 25p. (Not cased, not calibrated.)

HARTLEY TYPE 13A

ONLY £18.00

DOUBLE BEAM OSCILLOSCOPE

TB2Hz-750kHz. Band width 5.5MHz. Sensitivity 33Mv/cm. Calibration markers 100kHz and 1MHz. A completely reliable general purpose oscilloscope. Supplied with CIRCUIT DIAGRAM and Mains lead. Carr. £1.50.
As above. Complete with all accessories. £25.00. Carr. £1.50.
Many other oscilloscopes available.

GRATICULES. 12cm x 14cm in High Quality plastic. 30p ea. P. & P. 5p.

MOTOR—miniature synchronous, size 1½in x 2in x ¾in. 240V operation, 1 rpm. 25p ea. P. & P. 5p.

SAVE THOSE EXPENSIVE IC's with an AP Test Clip. £1 ea. P. & P. 10p.

P.C.B. pack S & D. Quantity 2 sq ft—no tiny pieces. 50p plus P. & P. 20p.
FIBRE GLASS as above £1 plus P. & P. 20p.

DELIVERED TO YOUR DOOR
1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.

LOOSE LEAF BINDERS. Blue plastic cover. 4 ring. Standard size. 4 for £1. P. & P. 35p. 25 for £5. Carr. £1.

Panel switches DPDT ex eq. 10p ea.; DPST Brand new, 17p ea.; DPST twice, brand new 25p ea.
HEAVY DUTY 6 amp 2 pole c/o—20p ea.

FIRST TIME EVER at £42.50

Solartron CD711S2 Double Beam Oscilloscope d.c.—9MHz; 3mV/cm; trigger delay; crystal calibrator; 4in flat faced tube. In good working condition. Carriage £1.50.

ELECTRONIC TIMER UNITS—wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only £2.50 incl. carriage.

CAPACITOR PACK—50 Brand new components only 50p. P. & P. 17p.

POTS—10 different values. Brand new—50p. P. & P. 17p.

COMPONENT PACK consisting of 2.2 pole 2 amp push on/off switches; 4 pots, various, brand new; 250 resistors ¼ and ½ watt, many high stabs, etc. Fine value at 50p per pack. P. & P. 17p.

5 CRYSTALS 70 to 90kHz. Our choice, 50p. P. & P. 15p.
Matched pairs, 50p per pair. P. & P. 15p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, 25p the lot. P. & P. 10p.

5 GOOD QUALITY MOVING COIL METERS, £3. P. & P. 37p.

MANUALS AVAILABLE


Cossor	Solartron	Advance	Telequipment
339	D300	DA	S31
1035	CT436	D2	S32A
1049	CD523S2	J	D43
E.M.I.	AD557	Furzehill	Hartley 13A
WM2	CD711S2	0160	CT38
WM8		1684	

This is only a small example of the manuals we have in stock, S.A.E. with your enquiries—we may be able to help.

CHILTMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College) Tel.: Reading 582605/65916

SUPERSOUND 13 HI-FI MONO AMPLIFIER

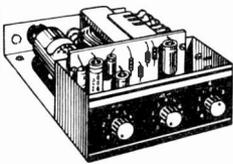


A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with

separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 5in high x 6in wide x 7 1/2in deep. A.C. 200/250V.

PRICE £10.50 P. & P. 25p.

DE LUXE STEREO AMPLIFIER

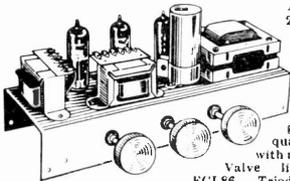

A.C. mains 200-240 volts. Using heavy duty fully isolated main transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up - 2 ECL86 Triode - Pentodes.

1. E780 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. x 4 1/2in. x 4in. Overall height including valves 5in. Ready built and tested to a high standard. **Price £8.92.** P. & P. 45p.

NEW! POWER SUPPLY UNIT

200/240V A.C. Input. Four switched fully smoothed D.C. outputs giving 6V and 7 1/2V and 9V and 12V at 1 amp continuous (1 1/2 amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6" x 3 1/2" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

PRICE £4.50 P. & P. 35p.

BLACK ANODISED 18g. ALUMINIUM HEAT SINKS. For T03, complete with mica's and bushes. Size 2 1/2in x 3in approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS. 8" x 6", 5 for 50p. P. & P. 13p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL x 3 1/2inW x 3inD. **Price £1.85.** P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V, Sec. 9-0-9 at 500mA. **85p.** P. & P. 13p. Pri. 200/240V, Sec. 12-0-12 at 1 amp. **95p.** P. & P. 13p. Pri. 200/240V, Sec. 10-0-10 at 2 amp. **£1.45.** P. & P. 30p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-20KHz. Gain 26dB. Solid encapsulation size 1 1/2 x 1 1/2 x 1/2in. Brand new - complete with instructions. **Price 85p.** P. & P. 13p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. **ONLY 40p.** Post 5p.

V.A.T.

Prices in this advertisement (incl. P. & P.) will be subject to V.A.T. as from 1st April, 1973.

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

4-SPEED RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing. **LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge £8.97. Carr. 50p. With stereo cartridge £7.97. Carr. 50p. **Garrard SP25 Mk. III** with heavy precision machined die cast turntable. **£10.95.** Carr. 60p.

SPECIAL BARGAIN OFFER! PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT60, etc., or B.S.R. C109, C129, A21, etc. Black leatherette finish. Size 12 1/2in x 14 1/2in x 3 1/2in high (approx. 1 1/2in high, including rigid smoked acrylic cover). **NOW ONLY £4.50** P. & P. 35p.

LATEST ACOS GP91/180 Mono Compatible Cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. **£1.50.** P. & P. 8p.

SONOTONE STAIN COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond SLP and Sapphire 78. **ONLY £2.50.** P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. **£3.** P. & P. 10p. **LATEST RONETTE T/O Stereo Compatible Cartridge** for EP/LP/Stereo/78. **£1.63.** P. & P. 10p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. **£1.50.** P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer, matched for 3 ohm speaker. **Size 7in. w. x 3d. x 6h.** Ready built and tested. **PRICE £3.95.** P. & P. 40p. **ALSO AVAILABLE** mounted on board with output transformer and speaker ready to fit cabinet below. **PRICE £5.25.** P. & P. 50p. **DE LUXE QUALITY PORTABLE R/P CABINET MK II** Complete motor board size 14 1/2 x 12in., clearance 2in. below, 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 5 x 8in. **PRICE £4.75.** P. & P. 50p.

SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2in high x 10 1/2in wide x 5 1/2in deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £8.40 Carr. 60p.

CABINET AVAILABLE SEPARATELY **£4.50.** Carr. 60p.

Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. **£6.50.** Carr. 65p.

LOUDSPEAKER BARGAINS

5in 3 ohm **£1.05.** P. & P. 15p. 7 x 4in 3 ohm **£1.15.** P. & P. 20p. 10 x 6in 3 or 15 ohm **£1.90.** P. & P. 30p. E.M.I. 8 x 5in 3 ohm with high flux magnet **£1.62.** P. & P. 20p. E.M.I. 13 1/2 x 8in with high flux ceramic magnet with parasitic tweeter 3, 8, or 15 ohm **£3.20.** P. & P. 30p. E.M.I. 13 x 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network **£4.20.** P. & P. 30p. **BRAND NEW** 12in 15W H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with HiFlux ceramic ferrohar magnet assembly **£6.75.** Guitar models: 20w **£6.75.** 35w **£8.50.** P. & P. 38p each.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS. With large ceramic magnet and plasticised cone surround. 8 ohm impedance. **£2.75.** P. & P. 25p.

12in "RA" TWIN CONE LOUDSPEAKER 10 watts peak handling, 3, 8 or 15 ohm, **£2.20.** P. & P. 30p. 35 ohm SPEAKERS 3" ONLY 65p. P. & P. 13p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER
Size - 1 1/2in x 1 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. **Only £5.95 each.** P. & P. 25p.
VYNAIR & REKINE SPEAKERS & CABINET FABRICS
app. 5 1/2in. wide. Usually £1.75 yd., our price 75p yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3 1/2in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. **PRICE £2.95.** P. & P. 10p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR **PRICE £1.05.** P. & P. 8p.

CENTRE ZERO MINATURE MOVING COIL METER. 100uA for balance or tuning. Approx. size 1in x 1in 1/2in. Limited number 75p. P. & P. 10p.

HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—Instructions included). Output stage for any speakers from 5 to 16 ohms Compact design, all parts supplied including drilled metal work, high quality ready drilled fibre glass printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to meet his own specifications. Power output 14W 12-30,000Hz. Sensitivity better than 80mV into 1MΩ. Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1.0 amp. Overall size—12" wide x 8" deep x 2 1/2" high.

Full detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES AMPLIFIER KIT, £10.50 P. & P. 15p.


(Magnetic input components 30p extra)

POWER PACK KIT, £3 P. & P. 30p.

CABINET, £2.75 P. & P. 30p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, **£20.50.** Post Free.

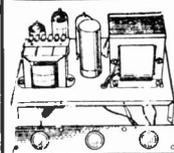Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discograph use, etc.



3-VALVE AUDIO AMPLIFIER H434 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in w. x 4in. d. x 4 1/2in. h. Incorporates ECC83, EL84, E270 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 41 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£4.95.** P. & P. 35p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to H434 above but employs entirely different and advanced circuitry. Complete set of parts, etc. **£4.10.** P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 5in. high overall. A.C. mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. **OUR ROCK BOTTOM BARGAIN PRICE £2.95** P. & P. 35p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL34s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL34s, ECC83, EF86 and E270 rectifier. Simple instruction booklet 15p (Free with parts). All parts sold separately. **ONLY £7.97.** P. & P. 55p. Also available ready built and tested **£10.97.** P. & P. 60p.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

Dept. PE, 170 High St., Merton, London, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

BRAND NEW GUARANTEED

SEMICONDUCTORS & COMPONENTS

RETURN OF POST SERVICE

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS IN THIS MAGAZINE

TRANSISTORS

2N109	0-40	2N3055	0-60	2N3458	0-30	AF200	0-35	BCY31	0-40	BFX30	0-25
2N174	1-40	2N3390	0-20	2N3459	0-40	AF239	0-41	BCY32	0-60	BFX37	0-33
2N176	0-75	2N3391	0-20	3N128	0-83	AF240	0-72	BCY33	0-25	BFX44	0-33
2N274	0-75	2N3391A	0-22	3N138	1-65	AF279	0-54	BCY34	0-35	BFX63	2-48
2N335	0-75	2N3392	0-13	3N140	0-82	AF280	0-49	BCY35	0-45	BFX68	0-30
2N351	0-95	2N3393	0-12	3N141	0-81	AF211	0-55	BCY40	0-50	BFX85	0-30
2N376	1-00	2N3394	0-12	3N142	0-58	AL102	0-75	BCY42	0-15	BFX86	0-25
2N384	0-93	2N3402	0-17	3N143	0-75	AL103	0-70	BCY43	0-15	BFX87	0-27
2N385A	0-20	2N3403	0-19	3N152	0-92	AY226	0-30	BCY58	0-21	BFX88	0-25
2N404	0-83	2N3404	0-24	3N153	0-81	ASY27	0-36	BCY59	0-21	BFX89	0-45
2N456	0-75	2N3405	0-27	3N154	0-64	ASY28	0-28	BCY66	0-84	BFY41	0-45
2N456A	0-75	2N3414	0-10	3N155	0-17	ASY29	0-30	BCY70	0-17	BFY17	0-85
2N457A	0-80	2N3415	0-10	3N209	2-49	ASY50	0-20	BCY71	0-20	BFY18	0-35
2N491	3-25	2N3416	0-15			ASY55	0-35	BCY72	0-13	BFY19	0-35
2N494	0-26	2N3417	0-21	LM741CN	(4.1.1)	ASZ21	0-55	BCY77	3-47	BFY20	0-50
2N501	0-94	2N3370	1-25	L741C	(4.1.1)	AU103	1-25	BCY87	3-47	BFY20	0-50
2N506	0-16	2N3371	1-25	(TO5)	0-40	BC107	0-14	BCY88	2-40	BFY29	0-40
2N597	0-15	2N3372	0-87			BC108	0-14	BCY89	0-80	BFY30	0-20
2N598	0-25	2N3702	0-10	40550	0-55	BC113	0-16	BCZ11	0-50	BFY43	0-65
2N599	0-28	2N3703	0-10	40309	0-81	BC114	0-12	BD115	0-75	BFY50	0-19
2N706	0-10	2N3704	0-10	40310	0-50	BC115	0-15	BD116	0-75	BFY51	0-18
2N706A	0-12	2N3705	0-10	40313	0-92	BC116	0-15	BD121	0-75	BFY52	0-18
2N708	0-15	2N3706	0-09	40316	0-50	BC116A	0-18	BD123	0-82	BFY53	0-15
2N709	0-10	2N3707	0-10	40318	0-07	BC117	0-21	BD124	0-80	BFY56	0-34
2N711	0-60	2N3708	0-07	40318	0-92	BC118	0-24	BD129	0-35	BFY60	0-41
2N718	0-21	2N3709	0-09	40322	0-92	BC119	0-27	BD131	0-40	BFY75	0-40
2N718A	0-30	2N3710	0-09	40380	0-40	BC121	0-23	BD132	0-50	BFY76	0-22
2N720	0-50	2N3711	0-09	40382	0-50	BC123	0-29	BD135	0-43	BFY77	0-24
2N721	0-55	2N3712	0-95	40383	0-88	BC125	0-15	BD136	0-49	BFY78	0-36
2N814	0-22	2N3713	1-08	40389	0-46	BC126	0-20	BD137	0-55	BFY90	0-55
2N816	0-20	2N3714	1-15	40394	0-56	BC132	0-30	BD138	0-63	BFY39	0-29
2N910	0-50	2N3715	1-22	40406	0-40	BC133	0-11	BD140	0-23	BSX20	0-13
2N929	0-20	2N3716	1-30	40408	0-50	BC136	0-15	BDY10	1-25	BSX21	0-20
2N930	0-20	2N3717	2-40	40409	0-50	BC137	0-15	BDY11	1-50	BSX26	0-34
		2N3781	3-67	40410	0-53	BC138	0-24	BDY17	1-50	BSX27	0-34
		2N3782	3-37	40411	2-25	BC140	0-34	BDY18	1-75	BSX28	0-25
		2N3789	1-76	40411	2-25	BC141	0-39	BDY19	1-87	BSX29	0-47
		2N3790	2-20	40414	3-55	BC142	0-30	BDY20	0-80	BSX30	0-68
		2N3791	2-06	40438	1-44	BC143	0-21	BDY28	0-55	BSX35	0-78
		2N3792	2-12	40474	0-69	BC144	0-24	BDY60	0-65	BSX60	0-64
2N1090	0-30	2N3794	0-20	40488A	0-44	BC145	0-21	BDY61	0-57	BSX61	0-42
2N1091	0-32	2N3819	0-35	40601	0-87	BC147	0-11	BDY62	0-52	BSX76	0-15
2N1131	0-25	2N3820	0-48	40601	0-46	BC148	0-11	BP115	0-23	BSX77	0-20
2N1132	0-25	2N3823	0-62	40602	0-42	BC149	0-13	BP117	0-43	BSX78	0-25
2N1184	1-50	2N3824	0-75	40603	0-56	BC150	0-18	BP119	0-58	BSX79	0-28
2N1302	0-16	2N3826	0-23	40604	0-56	BC154	0-18	BP121	0-25	BSX80	0-15
2N1303	0-16	2N3854	0-18	40636	1-10	BC157	0-14	BP123	0-27	BSX25	0-15
2N1304	0-20	2N3854A	0-18	40673	0-70	BC158	0-13	BP125	0-25	BSX26	0-20
2N1305	0-25	2N3855	0-16	40707	0-16	BC159	0-14	BP127	0-27	BSX27	0-15
2N1306	0-22	2N3855A	0-16	AC113	0-18	BC159	0-37	BP122	0-20	BSX28	0-15
2N1307	0-22	2N3856	0-16	AC115	0-18	BC159	0-13	BP123	0-20	BSX28	0-15
2N1308	0-22	2N3856A	0-16	AC117	0-20	BC159	0-13	BP123	0-20	BSX28	0-15
2N1309	0-25	2N3857	0-16	AC118	0-18	BC160	0-11	BP124	0-16	BSX29	0-15
2N1493	0-90	2N3858	0-16	AC121	0-13	BC160	0-11	BP128	0-23	BSX31	0-15
2N1507	0-24	2N3859	0-16	AC126	0-25	BC169C	0-13	BF159	0-27	BSY22	0-25
2N1613	0-19	2N3859A	0-16	AC127	0-25	BC169C	0-13	BF160	0-23	BSY23	0-25
2N1631	0-38	2N3860	0-16	AC128	0-20	BC170	0-11	BF161	0-41	BSY54	0-30
2N1637	0-38	2N3866	0-85	AC142K	0-15	BC171	0-13	BF163	0-20	BSY56	0-79
2N1638	0-32	2N3877	0-25	AC151V	0-24	BC172	0-11	BF166	0-31	BSY65	0-15
2N1671	1-25	2N3877	0-28	AC152V	0-17	BC172	0-10	BF167	0-21	BSY78	0-40
2N1701	1-46	2N3878	1-46	AC153	0-22	BC172	0-10	BF173	0-22	BSY79	0-20
2N1702	2-61	2N3879	1-00	AC153K	0-25	BC173	0-09	BF173	0-22	BSY79	0-20
2N1711	0-23	2N3900	0-20	AC154	0-20	BC183L	0-09	BF178	0-35	BSY95A	0-49
2N1893	0-37	2N3900A	0-21	AC176	0-25	BC184	0-11	BF179	0-43	BT104	1-42
2N2102	0-30	2N3901	0-32	AC176K	0-20	BC184L	0-11	BF180	0-35	BT105	2-25
2N2147	0-75	2N3903	0-32	AC187K	0-20	BC187	0-25	BF181	0-34	CT11	0-53
2N2148	0-60	2N3904	0-22	AC188K	0-26	BC204	0-11	BF183	0-40	C24	0-13
2N2192	0-40	2N3905	0-21	ACY17	0-30	BC205	0-10	BF184	0-17	C425	0-36
2N2194	0-40	2N3906	0-22	ACY18	0-25	BC206	0-11	BF185	0-25	C426	0-25
2N2193	0-40	2N4036	0-40	ACY19	0-20	BC207	0-10	BF194	0-14	C428	0-25
2N2193A	0-42	2N4037	0-35	ACY20	0-20	BC208	0-09	BF195	0-16	C444	0-26
2N2194	0-27	2N4038	0-19	ACY21	0-20	BC208	0-09	BF196	0-15	040N3	0-62
2N2194A	0-20	2N4039	0-12	ACY22	0-13	BC212K	0-10	BF197	0-10	GET11	0-45
2N2195	0-37	2N4060	0-11	ACY28	0-25	BC212L	0-12	BF198	0-18	GET113	0-25
2N2195A	0-18	2N4061	0-11	ACY30	0-42	BC214L	0-14	BF199	0-18	GET114	0-20
2N2218A	0-18	2N4062	0-11	ACY39	0-55	BC236	0-16	BF200	0-40	GET115	0-50
2N2219	0-20	2N4302	0-25	ACY40	0-20	BC237	0-08	BF224J	0-14	GET119	0-35
2N2219A	0-20	2N4303	0-32	ACY41	0-20	BC237	0-08	BF225J	0-19	GET120	0-40
2N2220	0-20	2N4313	0-80	ACY44	0-31	BC238	0-09	BF239	0-09	GET35	0-20
2N2221	0-20	2N4314	0-87	AD136V	0-96	BC251	0-22	BF237	0-22	GET36	0-20
2N2221A	0-22	2N4315	0-95	AD140	0-50	BC252	0-18	BF244	0-16	GET38	0-20
2N2222	0-20	2N4316	0-20	AD141	0-50	BC253	0-23	BF245	0-33	GET873	0-15
2N2222A	0-32	2N4317	0-17	AD142	0-50	BC255	0-09	BF246	0-43	GET880	0-30
2N2368	0-11	2N4318	0-53	AD143	0-45	BC257	0-09	BF247	0-49	GET883	0-20
2N2369	0-05	2N4319	0-50	AD149V	0-66	BC258	0-09	BF247	0-49	GET883	0-20
2N2369A	0-15	2N4320	0-50	AD149V	1-28	BC259	0-13	BF254	0-16	GET887	0-20
2N2646	0-50	2N4321	0-50	AD150	0-63	BC262	0-18	BF257	0-47	GET890	0-22
2N2647	1-20	2N4322	0-65	AD150	0-63	BC262	0-18	BF257	0-47	GET890	0-22
2N2711	0-12	2N4323	0-30	ADZ11	1-50	BC263	0-23	BF258	0-53	GET895	0-25
2N2712	0-12	2N4326	0-60	ADZ12	1-75	BC300	0-42	BF259	0-55	MA8001	0-18
2N2713	0-17	2N4327	1-00	AF106F	0-40	BC301	0-34	BF261	0-23	MA8002	0-47
2N2714	0-17	2N4328	1-80	AF114	0-25	BC302	0-27	BF264	1-45	MA8003	0-47
2N2904	0-18	2N4329	2-23	AF115	0-25	BC303	0-54	BF270	0-21		
2N2904A	0-25	2N4330	0-69	AF116	0-25	BC304	0-43	BF271	0-21		
2N2905	0-28	2N4331	2-70	AF117	0-20	BC307	0-10	BF272	0-40		
2N2905A	0-28	2N4332	1-24	AF118	0-20	BC307A	0-10	BF273	0-15		
2N2906	0-13	2N4333	0-22	AF119	0-20	BC307A	0-10	BF274	0-17		
2N2906A	0-23	2N4334	0-26	AF121	0-22	BC308	0-09	BF457	0-63		
2N2907	0-23	2N4335	0-32	AF122	0-22	BC308A	0-09	BF458	0-65		
2N2907A	0-26	2N4336	0-43	AF126	0-20	BC308B	0-09	BF459	0-65		
2N2913	0-75	2N4337	0-82	AF127	0-20	BC309	0-10	BF521	1-75		
2N2923	0-12	2N4338	1-24	AF139	0-38	BC309A	0-10	BF522A	2-30		
2N29											

Would you spend an hour a day to earn more money in Electronics- Television-Radio?

If you're willing to give up one hour or more a day we can help you get into the lucrative growth industries of electronics, television, radio.

And if you're already in, we can help you get on!

With our know-how and wide experience in teaching, plus your determination to study, we can turn your interest into the technical knowledge you need for success. Once you've got the qualifications you need, you'll be in a good position to take full advantage of the opportunities which exist today in all fields of electronics—in television (colour and black/white) and in radio. (We teach you the theory and practice of valve and transistor portable circuits while you build your own 5 valve receiver, transistor portable and high grade test instruments.)

With ICS you study at home—at your own pace, when you choose, in the time you've got available. Your ICS tutors will give you all the help and encouragement you need to pass any exams you want to take.

Don't waste another day. Take your first step now towards a better paid, more assured future. Send for your FREE Careers Guide today.

ICS your key to the door of opportunity

Tick or state subject of interest and post to:
International Correspondence Schools
Dept. 230E Intertext House, Stewarts Road
London SW8 4UJ

Subject of interest


- Society of Engineers Graduateship (Electrical Engineering)
- C & G Telecommunications Technicians Certificates
- C & G Electrical Installation Work
- C & G Certificate in Technical Communication Techniques
- MPT General Certificate in Radio Telegraphy
- Audio, Radio & TV Engineering & Servicing
- Electronic Engineering, Maintenance, Engineering systems, Instrumentation & Control systems
- Computer Engineering and Technology
- Electrical Engineering, Installations, Contracting, Appliances
- Self-build radio courses

Name

Address

Occupation Age

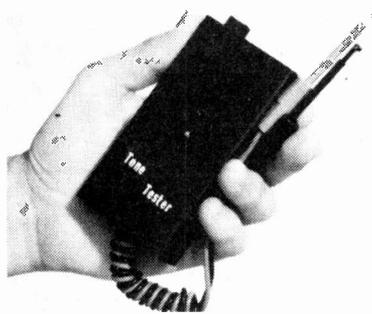Accredited by the Council for the Accreditation of Correspondence Colleges



TOPE TESTER

The Tone Tester is a solid-state dual impedance continuity tester with tone injection.

Applications: Wiring. Cable installation. Production line testing. Damage free testing of solid-state assemblies.

Power supply: integral 1.5v battery.
Continuity test: impedance—low 0—10 ohms high 0—50k ohms.
Tone injection: 1-4 Vp—p up to 300 ohms
O.C. loop. *Tone injection on HTD only.*

HTD dual impedance with tone injection
£5.80. HTL low impedance only £4.84.
HTH high impedance only £4.96.

Highams Electronic Communications Ltd
Dept E 58-60 Redchurch St London E2

ELECTRONIC BARGAINS

COMPAKS

Manufacturers' fall-outs which include functional and part-functional units. Ideal for learning and experimenting.

PAK 1	13 mixed 7400 series	66p
PAK 2	10 unijunction T1543	55p
PAK 3	6 S.C.R.'s	55p
PAK 4	50 silicon and germanium NPN and PNP transistors	55p

Valve Equivalent Book	40p
Transistor Equivalent Book	40p
List over 3,000 equivalents	

ACOUSTIC WADDING

Bonded Acrylic Fibre 1in thick. Per square yard 50p

VYNAR SPEAKER CLOTH

Black—Black and Silver—Black and Gold

	Sizes:	60p
18in x 25in		£1.10
36in x 25in		£2.20
36in x 50in		
Send S.A.E. for samples		

SOLDERING IRONS

	Retail Price	Our Price
Antex CN240	£1.98	£1.58
Antex CN240	£1.87	£1.49
Antex X25	£1.92	£1.54

FERRANTI RADIO CHIP

ZN414 £1.23

AMPLIFIER MODULE

5 watt, 9 volt supply, 4, 8 or 16 Ω speaker, £3.30

Fully Guaranteed. Mail order only. P. & P. 13p. Cheque or P/O to:

T. F. J. ELECTRONICS
25 EASTBURY COURT
LEMSFORD ROAD
ST. ALBANS, HERTS.

U.H.F. TV AERIALS

SUITABLE FOR COLOUR & MONO-CHROME RECEPTION



All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS

7 element £2.25. 11 element £2.75. 14 element £3.25. 18 element £3.75.

WALL MOUNTING c/w WALL ARM AND BRACKET. 7 element £3.25. 11 element £3.75. 14 element £4.25. 18 element £4.75.

CHIMNEY MOUNTING ARRAYS c/w MAST AND LASHING KIT. 7 element £4. 11 element £4.50. 14 element £4.75. 18 element £5.25.

MAST MOUNTING arrays only 7 element £2.25. 11 element £2.75. 14 element £3.25. 18 element £3.75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9p yd.

KING TELEBOOSTERS from £3.75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps £7.50. State clearly channel number required on all orders. P. & P. on all aerials 50p accs. 15p. C.W.O. min. C.O.D. charge 25p.

BBC-ITV-FM AERIALS

BBC (band 1) Wall S/D £2. LOFT inverted 'T' £1.25. EXTERNAL 'H' array only £3. ITV (band 3) 5 element loft array £2.50. 7 element £3. COMBINED BBC-ITV etc: 1+5 £2.75. 1+7 £3.50. WALL AND CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from £3.75.

COMBINED U.H.F.—V.H.F. aerials 1+5+9 £4. 1+5+14 £4.50. 1+7+14 £5. F.M. RADIO loft S/D £1. 3 element £3.25. 4 element £3.50. Standard coaxial plugs 9p. Coaxial cable 5p yd. Outlet box 30p. P. & P. all aerials 50p, accs. 30p. C.W.O. min. C.O.D. charge 25p. Send Sp for fully illustrated lists.

CALLERS WELCOMED
OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS

40-41 Monarch Parade, London Rd.
Mitcham, Surrey
Telephone 01-648 4884

TRANSISTOR AUDIO AND RADIO CIRCUITS

by MULLARD

£1.80. Postage 12p.

TRANSISTORIZED RADIO CONTROL FOR MODELS by D. W. Aldridge. £2.50. Postage 12p.

HI FI YEAR BOOK 1973. £1.50. Postage 20p.

BEGINNER'S GUIDE TO TELEVISION by Gordon J. King. £1.60. Postage 10p.

RADIO TECHNICIAN'S BENCH MANUAL by H. W. Hellyer. £3. Postage 15p.

INTEGRATED CIRCUIT POCKET BOOK by R. G. Hibberd. £2.50. Postage 12p.

FIELD EFFECT TRANSISTORS by MULLARD. £1.80. Postage 12p.

HAM RADIO: A BEGINNER'S GUIDE by R. H. Warring. £1.60. Postage 12p.

110 THYRISTOR PROJECTS USING SCRs AND TRIACS by R. M. Marston. £1.40. Postage 8p.

50 PHOTOELECTRIC CIRCUITS AND SYSTEMS by P. S. Smith. £1.30. Postage 8p.

FOUNDATIONS OF WIRELESS AND ELECTRONICS by M. G. Scroggie. £1.80. Postage 25p.

RADIO VALVE & TRANSISTOR DATA by A. M. Ball. 75p. Postage 12p.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185
Closed Saturday 1 p.m.

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V

All Types from 1 to 50 amp from stock.

SHROUDED TYPE

1 amp, £7-00
2.5 amp, £8-05
5 amp, £11-75
10 amp, £22-50
15 amp, £25-00

20 amp, £49-00
25 amp, £58-00
37.5 amp, £82-00
50 amp, £98-00



2.5 amp OPEN TYPE

(Panel Mounting) 1/2 amp, £4-75.
1 amp, £7-00. 2 1/2 amp, £8-05. All carriage paid.

DOUBLE ENDED MOTOR UNIT

Powerful, continuously rated, 2-speed. Either 6 or 12 volt D.C. operation. PRICE £2 incl. P. & P.



12 VOLT D.C. MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 r.p.m. complete with external gear train (removable) giving approx. final speed of either 125 r.p.m. or 240 r.p.m. Size: 4 1/2 in x 2 1/2 in dia. Either type price 95p incl. P. & P.




REVERSIBLE SPLIT PHASE MOTOR

250 r.p.m., 100-115/210-240V A.C., 2 in. x 1 in. Ideal for rim-drive models, display, etc. Extremely powerful for size (including small capacitor). 75p incl. P. & P.

PARVALUX TYPE SD19 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS

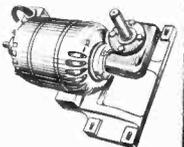30 r.p.m., 40 lb. ins. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Excellent equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of the maker's price. £6-80. Incl. P. & P.




PARVALUX Type: SD1.S/8586/OJ A.C. 50 r.p.m.

7 lb. in. Continuously rated. Less base. £6-30. Post Paid.

TYPE: SD1.S/8940/OM

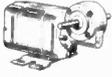230/250V A.C. 50 r.p.m. 22 lb. in. Continuously rated. Incl. base. £7-30. Incl. P. & P.



The above motors are new and unused.

PARVALUX TYPE SD2. 200/250 VOLT A.C./D.C. HIGH SPEED MOTOR

Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built-in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated below. PRICE £2. Incl. P. & P.



600 WATT DIMMER SWITCH.

Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £3 incl. P. & P.



VENNER ELECTRIC TIME SWITCH

200/250V Ex. GPO.

Tested. Manually set 2 on, 2 off every 24 hrs. Override switch: 15A, £3.45, 20A, £3.95. Incl. P. & P. Also available with solar dial ON dusk, OFF dawn. Price as above.



24-HOUR TIMER

Can be adjusted to give a switching delay of between 2 hrs. to 24 hrs. Driven by 200/250V A.C. synchronous motor. 15 amp c/o contacts. Mfg. Crater Controls Ltd. Supplied with scale calibrated 0-10 (2 hrs. per division). Brand New. £2. Incl. P. & P.



HONEYWELL PROGRAMME TIMERS

240V. A.C. 5 r.p.m. motor. Each cam operating a c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. 15 cam model £6. Incl. P. & P. 10 cam model £5. Incl. P. & P. 2 cam model with 15 r.p.m. motor £2. Incl. P. & P.



SIMPLE 12 CAM PROGRAMMER 240V A.C. 15 RPM MOTOR with 4 adjustable cams and 8 that may be profiled to individual requirements, £3-75. Incl. P. & P.

36V 30 AMP. A.C. or D.C. VARIABLE I.T. SUPPLY UNIT

INPUT 220/240V a.c. OUTPUT CONTINUOUSLY VARIABLE 0-36V



Fully isolated. Fitted in robust metal case with Voltmeter, Ammeter, Panel Indicator and handles. Input and output fully fused. Ideally suited for Lab. or Industrial use. £70. Incl. P. & P.

MOTOROLA MAC II/6 PLASTIC TRIAC 400 PIV. 10 AMP

Now available EX STOCK. Supplied with full data and applications sheet. Price £1-12. Incl. P. & P. Suitable DIAC (RCA 40583) 30p each.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT Speed adjustable 1 to 30 flash per sec. All electronic components including Veroboard S.C.R. Unit, Xenon Tube and instructions £6-55. Incl. P. & P.

NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. approx. 1 output of Hy-Lyght. Price £11. Incl. P. & P.

HY-LYGHY STROBE MK III

Designed and produced for use in large rooms, halls and the photographic field and utilises a silica tube, printed circuit, also a special trigger coil. Speed adjustable 0-20 f.p.s. Light output approx. greater than many (so called 4 Joule) strobes. £12-50. Incl. P. & P.

THE 'SUPER' HY-LYGHY KIT

Approx. four times the light output of our well proven Hy-Lyght strobe. Incorporating:
● Heavy duty power supply.
● Variable speed from 1-13 flash per sec.
● Reactor control circuit producing an intense white light.

Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20-75. Incl. P. & P.

ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE, SUPER HY-LYGHY KIT including reflector. £7-45. Incl. P. & P. For Hy-Lyght Kit including reflector. £4-45.

7-INCH POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 66p. Incl. P. & P.

FROM APRIL 1st V.A.T. (at the standard rate) MUST BE ADDED TO ALL PRICES

RAINBOW STROBE FOUR LIGHT CONTROL MODULE

Will operate four of our Hy-Lyght or Super Hy-Lyght Strobes in either 1, 2, 3, 4 sequence; 2 + 2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: £18-75. Incl. P. & P. Send S.A.E. for details.

COLOUR WHEEL PROJECTOR

Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £18-50 + 35p. P. & P. 6 INCH COLOUR WHEEL As used for Disco lighting effects, etc. Price £5-75 incl. p. & p.



BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Outer bulb designed to absorb visible light and transmit u.v. rays. Extremely compact and powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16-50. Incl. P. & P. Spare bulb £7-30. Incl. P. & P.



BLACK LIGHT FLUORESCENT U.V. TUBES

4ft. 40 watt. Price £5-80 incl. P. & P. (For use in standard bi-pin fluorescent fittings). MINI 9 in. 6 watt black light U.V. tube. £1-45. Incl. P. & P. Complete ballast unit and holders for 9 in. tube. £1-85.

Superior Quality Precision Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230mA; 2.5 kΩ, 2A; 3.5kΩ, 5 kΩ, 140mA. Diameter 3 1/2 in. Shaft length 1 in. dia. 1/2 in. All at £1-73. Incl. P. & P.
50 WATT. 1/5/10/25/50/100/250/500/111/5/2/5/5kΩ. All at £1-23. Incl. P. & P.
25 WATT. 10/25/50/100/250/300/500/111/5/2/5/3/5/5kΩ. All at 98p. Incl. P. & P.
Black Silver Skirted knob calibrated in Nos. 1-9. 1/2 in. dia brass bush. Ideal for above Rheostats. 18p ea.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1)	1	2	3	4
Col. ohms	52	4-6	6M	63p*
Col. (2)	52	4-6	4 c/o	78p*
Working d.c. volts	150	6-12	4 c/o	78p*
	185	8-12	6M	63p*
Col. 3	230	6-12	2 c/o	63p*
Contracts	410	10-18	4 c/o	73p*
	600	12-24	4 c/o	63p*
Col. (4)	600	9-18	2 c/o	63p*
Price	700	16-24	4M 2B	63p*
	700	16-24	4 c/o	78p*
HD =	700	15-35	2 c/o HD	73p*
Heavy duty	700	16-24	6M	65p*
	700	6-12	1 c/o HD	75p*
Incl. Base	700	20-30	6 c/o	75p
	1,250	24-36	4 c/o	63p*
All prices	2,500	36-45	6M	63p*
incl. P. & P.	2,400	30-48	4 c/o	50p
	9,000	40-70	2 c/o	50p*
	15k	85-110	6M	50p*

12 VOLT D.C. RELAY 140 ohm coil

Type 1: Three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below.)
Type 2: One set of c/o contacts, 60p incl. P. & P.
Type 3: 4-8 volt, 3 c/o HD, 67 ohm coil. 78p.

SPECIAL OFFER

700 ohm 4 c/o. Ex. new equipment. £50 per 100 incl. bases (minimum 100).

'DIAMOND H' 230 VOLT A.C. RELAYS (Unused)

Three sets c/o contacts rated at 5 amps. PRICE: 60p. Incl. P. & P. (100 lots £40 including P. & P.)



MINIATURE LATCHING RELAY

Manufactured by Clare-Elliott Ltd. Type F. 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size 1/2" high, 1/2" wide, 1/2" thick. Complete with 3" leads. New 73p. incl. P. & P.

UNISELECTOR SWITCHES

NEW 4 Bank 25 Watt

24V d.c. operation. £5-88. P. & P. 25p. 6 Bank 25 Watt 24V d.c. £6-75. Post Paid. 8 Bank 25 Watt, 24V d.c. operation. £7-88. Incl. P. & P.



'HONEYWELL' PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises a c/o rated at 10 amps 240V. A.C. Black knob 1 in. Fixing hole 1/2 in. ONE bank 30p; TWO bank 40p; THREE bank 55p; incl. P. & P. Quot. for quantity.



'HONEYWELL' LEVER OPERATED MICRO SWITCH

15 amps 250 volt A.C. c/o contacts. Types N39, N95, N100, N101 NEW in maker's carton. PRICE: 10 for £1-90 incl. P. & P.



Very special offer

MICRO SWITCH

5 amp c/o contacts. Fitted with removable metal panel assembly. Ex. P.O. 20 for £1 incl. post. (Min. order 20.)

METER BARGAIN

BALANCE/LEVEL METERS 100-0-100 Micro Amp. Size 1 1/2 in x 1 1/2 in. Price only 75p including P. & P.



AMMETERS NEW! 2 1/2 in. Flush round. Available in D.C. Amps 1, 5, 15, 20 or A.C. Amps 1, 5, 10, 15, 20, both types £1-75 incl. P. & P. 0-300V. A.C. £1-90 incl. P. & P.



INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L 8 in, W 4 in, H 6 in, weight 6 lb. 1,000V, 1,000 megohms, £34-00 incl. P. & C. 500V, 500 megohms, £28 incl. P. & C.



Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

SERVICE TRADING CO

All Mail Orders—Callers—Ample Parking
Dept. PE4, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

BOOKS AND PUBLICATIONS

KILRIMONT BOOKS

110 I.C. Projects (1971), £1.20 + 5p post; 110 Semiconductor projects (1969), £1.20 + 5p post; Understanding Electronic Components (1972), £2.50; Transistor Circuit Design Tables (1971), £2.80; Digital Logic (1971), £1.50; Audio Technicians Bench Manual (1971), £2.50; T.V. Technicians Bench Manual (1971), £2.50; Introduction to Semiconductor Devices (1972), £1.90 + 5p post. Many others. Please send for lists. Post free unless indicated.
KILRIMONT BOOKS (D), Kilrिमont House, London Road, Braintree, Essex

THOSE 1,000 BANBURY UFO'S! Details of our Prediction (and list) S.A.E. Numerous Charts, Map, Detectors. R. & E. PUBLICATIONS, Highlands, Needham Market, Suffolk.

COURSES

London Borough of Enfield Trent Park College of Education Cockfosters, Barnet, Herts. TECHNOLOGY TEACHING 3-YEAR COURSE FOR MEN AND WOMEN

VACANCIES exist on the Course starting in September, 1973 for Mature Students (over 24 years) wishing to become teachers of Technology, for whom there is an increasing demand in Schools. Learning through problem solving situations forms an essential part of the Certificate Main subject "TECHNOLOGICAL STUDIES", involving techniques and methods of craft, Science and Mathematics, and offering a wide range of practical experience.

Applications will be considered from students with various qualifications and types of experience, together with an interest in the development of practical solutions to a wide range of problems.

Grants are available.

Prospectus, information and application forms from:
 The Academic Registrar, Trent Park College of Education, Cockfosters, Barnet, Herts.
 D. B. Denny, Chief Education Officer.

EDUCATIONAL

ENGINEERS. Get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Buildings, etc., FREE book from: BIET (Dept. ZC BPE 25), Aldermaston Court, Reading, RG7 4PF. Accredited by CACC.

A SUCCESSFUL CAREER IN RADIO

Get the success you deserve—take an ICS home study course. Pass C&G, M.P.T. exams FIRST TIME! Free books. Low cost. Personal tuition. Send TODAY for FREE Guide on Radio, TV, Electronics, Electrical Engineering.

Name _____

Address _____

ICS Dept. 730HI
Stewarts Road,
London SW8 4UJ

SITUATIONS VACANT

MEN! £50 p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500 + p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators
Training Centre
M84, Oxford House
9-15 Oxford Street, W.1
Telephone 01-734 2874

127 The Piazza, Dept. M84
Piccadilly Plaza, Manchester 1
Telephone 061-236 2935

SERVICE SHEETS

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/inquiries. Catalogue 15p. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 15p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

WANTED

TOP PRICES PAID

for new valves and components

Popular T.V. and Radio types
KENSINGTON SUPPLIES
 (B) 367 Kensington Street
 Bradford 8, Yorks.

WANTED URGENTLY. Back issues of P.E. June, July and August 1968. KIRK, Wash. fold Farm, Leyburn, Yorks. Leyburn 2193.

FOR SALE

MORSE MADE EASY!!
FACT NOT FICTION. If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognize the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18W.P.M. in 4 weeks guaranteed. Beginner's Section only 23-30, complete course 24-50 (Overseas £1 extra) details only, 4p stamp. 01-660 2896 G3HC (Box 19), 45 GREEN LANE, PURLEY, SURREY

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

P.E. No. 1 to CURRENT ISSUE. Missing April 66, August 70, September 71, December 65. X Model 8 Avo. Ring Whitley Bay 27325.

ALL ISSUES P.E. with binders and indexes. 8 Volumes. Offers. Box No. 47.

TV LINE OUT-PUT TRANSFORMERS

Tidman Mail Order Ltd., 236 Sandycroft
 Road, Richmond, Surrey TW9 2EQ
 01-948 3702

FIBRE OPTICS

Flexible Light Pipe for conveying light to inaccessible positions. Fibroflex Type 1, Glass 1.14mm effective dia. PVC sheathed. 44p per metre. (VAT inc.), P. & P. 10p. Any quantity.

Polariser Sheet up to 1 sq. ft. max. size. 161p per sq. in. (VAT inc.), P. & P. up to 6 in. square 10p; over 6 in. square 30p

- ★ Cut down glare
- ★ See those nixie tubes
- ★ Cross them for light control
- ★ Make your own strain gauge for plastics and glass

Circuit Board Etching Kits. Full instructions. £1.37½ (VAT inc.), P. & P. 14p

Photographic CDS Light Cells—used (with part of original circuit free), 33p (VAT inc.), Post free.

All items are strictly C.V.O.

From: **ARVIN SERVICE COMPANY**
 12 CAMBRIDGE ROAD
 ST. ALBANS

8L0-8YN STEPPING MOTORS. Type S850-1001, 14V d.c. Torque 50 oz in. £23. A few magnetic chucks for same, £6-50 (all new). MICHAELS, 36 Orchard Way, Stanbridge, Nr. Leighton Buzzard, Beds.

COLLARO STUDIO DECK, 89. Motek deck in recorder, £11. 5-10 amplifier and f.m. £12 (o.n.o.). 01-634 4290.

LADDERS

LADDERS, 24ft £9-80, carr. 80p. Leaflet (Dept. PEE), HOME SALES LADDER CENTRE, Baldwin Road, Stourport, Worcs. Tel. 029-93 2574.

AERIALS

DIRECT FROM MANUFACTURER—a comprehensive catalogue of UHF and VHF/FM aerials, fixing brackets, chimney lashings, clamps, masts, amplifiers, cable, etc., for the D.T.V. enthusiast. Complete with useful installation hints. Send 3p stamp to CLAYDEW ENTERPRISES (PE), 261 Hardess Street, London, S.E.24.

RECEIVERS AND COMPONENTS

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"), Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 62p per doz., £3.75 per 100; £7.50 per 1,000; £350 per 10,000. All carriage paid.
G.W.M. RADIO LTD.
 40/42 Portland Road, Worthing, Sussex 0903 34897

BRAND NEW COMPONENTS BY RETURN, Electrolytics, 16V, 25V, 50V, 1, 2-2, 4-7, 10 mfd.s., 3½p; 22, 47, 4p (50V, 5p); 100, 5p (50V, 6p). Subminiature bead-type tantalums 0-1/35V, 0-22/35V, 0-47/35V, 1/35V, 2-2/35V, 4-7/35V, 10/16V, 8p. Mylar Film 100V, .001, .002, .005, .01, .02, 2p; .04, .05, 2½p; .068, .1, 3p. Polystyrene 63V, E12 series 10 pf., -10,000 pf., 2p. Miniature Highstab Resistors E.12 series 5% Third Watt Carbon Film 1Ω-10MΩ (10% over 1M) and 1W Metal Film 27Ω-10MΩ, 8 for 5p. Insured postage 8p. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

RESISTORS

CARBON FILM

20-1-1-1-1-2 WATT MOST VALUES
STD 5%, 60p/100, £5/1,000
STD 2%, 65p/100, £5-50/1,000
HI-STAB 2%, 70p/100, £6/1,000
VALUES YOUR CHOICE IN FIVES
POSTAGE FREE—C.W.O.

WRAP RESISTORS

9 ELLEN CLOSE, NORTH PETHERTON, SOMERSET
TELEPHONE: NORTH PETHERTON 662501

Trampus electronics

All Brand New. No Rejects or
Remarks. Money Back
Assurance.

DIGITAL INDICATORS: 5V
0-9DP with socket and red
filter, £1.39. Nixie type, 97p.
1/2 LED 7SEG + DP DIL type,
£2-50.

LIGHT EMIT DIODES: Red.
Visible red/panel clip/data 36p.
209 type, 33p. Infra red type,
£1.

IG GAS DETECTOR: Smoke, Butane Vapour, etc.,
£1-87.

ULTRASONIC: Transducer/remote control, £2.

IC digital clock

28 pin DIL 12/24 hr. 4/8 digit, £11-50, data 9p.
Kit £21. Indicators £1-29 ea. PCH £1-69. Case 35p.
PW ELECTRONIC CAR IGNITION KIT, £6-67.

STEREO.

QUAD AUDIO from stereo, matrix IC, £3-67.
MAGNETIC CARTRIDGE, diamond 20-20KHz.
£4-19. DUAL IC PREAMP £1-67. FM HI-FIT TUNER
£2. MC1310P MPX FM decoder, £2-69. KIT £3-45.

INTEGRATED CIRCUITS: with data, 709 705, 21p;
DIL, 28p; 710 and 748, 33p; 723, 55p.
741 OP AMP DIL, 28p. Photodetector/amp, 33p.
Voltage regulator 1A, 5 to 20V 3 lead, £1-49.

RECEIVER ZN414 Ferranti 3 lead, £1-10. AF
amps: 2W, £1-19; 3-5W, £1-33; 8L403, £1-45.
555 Timer/mono/as table osc. clock, 95p.

BRANDED TEXAS/TIT etc. FULL RANGE

Gates, 7400/1/2/3/4/5/10/30/30/40/50, etc., 15p;
7413, 28p; 7470/72, 28p; 7473/74/76, 37p; 7447,
£1-27; 7490, 59p; 7492, 67p; 74121, 40p; 74141, 89p;
DIL PLUG or IC case, 16 pin, 10mm high, 35p.

SEMICONDUCATORS:
BC107, 8p. BC108, 8p. BC109, 8p. 2N3055, 40p.
AC125/6/7/8, AC127/8, AC187/8, AF117, 15p;
AD161/2, 35p ea.; BC147/8/9, 9p; BC167/8/9, 17p;
BC177/8/9, 15p; BC182/3/4, 9p; BC212/3/4, 9p;
BCY70, 16p; BD131/2, 65p; BFY50/51/52, 17p;
OC92/85, 49p; OCT1, 27p; T1843 U.T. 29p; 2N700,
12p; 2N2369, 21p; 2N2646, 49p; 2N3033, 17p;
2N3055, 40p; 2N3614, 55p; 2N3702/3/4/5/6/7, 10p;
2N3708/9/10/11, 9p.

FETs: 2N3819, 28p; 2N3923, 29p; 2N3866 UHF,
59p.

ME 0411/2, 18p; ME 4001, 12p; ME 4102, 11p.

DIODES:
IN914, 3p; OA91, 5p. **ZENERS:** BZY88 400mW,
10p.

IN4001, 4p; **IN4004**, 8p; 50V 1A Bridge, 23p.
TRANSFORMERS: JA mini12/24V, £1; 6/12V, £1.
SCR 400V: 1A, 28p; 3A, 49p; 4A, 55p; 6A Triac,
60p.

CAPACITORS: 25/30V Electrolytic,
10/50/100µF, 5p; 200/500µF, 8p; 1,000µF, 15p.
DISC: 22pf to 0.047µF, 4p; up to 0.1µF, 6p.
PRESSETS: 0.25W, 5p. **RESISTORS** 1/2W 5%, 14p.
CARBON POTS, 12p ea. Switch + 12p. Dual,
60p.

All DIN plugs, 13p; sockets, 9p. Vero stocked.
Copper Board 12" x 6"; S.R.B.P., 40p. FeC 1lb,
20p.

Antex irons at R.R.P. Desolder Braid, 16p.
WEATHER STATION barometer, temp., humid.,
£3.

FREE CATALOGUE S.A.E. Discount 20 + 10%.
C.W.O. P. & P. UK & Europe 7p. Overseas 35p.

P.O. BOX 29, BRACKNELL, BERKS.

5-N-Channel FETs 3819E—£1

Full specification devices complete with circuit
details for building voltmeter, timer, ohm-
meter, etc.
Send 10p for full list of field effect transistors and
other top quality transistors available at bar-
gain prices.

REDHAWK SALES LTD.
45 Station Road, Gerrards Cross, Bucks.
MAIL ORDER ONLY

PRECISION

POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.
0.47µF: ±5% 30p; ±2% 40p; ±1% 50p
1.0µF: ±5% 40p; ±2% 50p; ±1% 60p
2.2µF: ±5% 50p; ±2% 60p; ±1% 75p
4.7µF: ±5% 70p; ±2% 80p; ±1% £1-15
6.8µF: ±5% 85p; ±2% £1-15; ±1% £1-60
10µF: ±5% £1-10; ±2% £1-40; ±1% £1-80
15µF: ±5% £1-80; ±2% £2-10; ±1% £2-70

TANTALUM BEAD CAPACITORS: Values
available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at
35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V,
47µF 6V, 100µF 3V—all at 9p each; 6 for 50p;
14 for £1. Special pack 6 off each value (78
capacitors) £5.

NEW 1-TRANSISTORS: BC107, BC108,
BC109. All at 9p each; 6 for 50p; 14 for £1. All
brand new and marked. Full spec. devices. May
be mixed to qualify for quantity prices. AF178
—40p each; 3 for £1.

POPULAR DIODES: IN914, 7p each; 8 for
50p; 18 for £1. IN916, 9p each; 6 for 50p; 14 for
£1. 1S44, 5p each; 11 for 50p; 24 for £1. All
brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values
available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11,
12, 13.5, 15V. Tol. ±5% at 5mA. All new and
marked. Price 10p each; 6 for 50p; 14 for £1.
Special offer 6 off each voltage (66 zeners) £4-50.

RESISTORS: Carbon film 5%, 1/4W at 40°C, 1W
at 70°C. Range from 2.2Ω to 2.2MΩ in E12 series,
i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and
their decades. High stability, low noise. All at
1p each; 8p for 10 of any one value; 70p for
100 of any one value. Special pack—10 off each
value 2.2Ω to 2.2MΩ (730 resistors) £5.

440V A.C. CAPACITORS: 0.1µF, size 1 1/2in x
1/2in, 25p; 0.25µF, size 1 1/2in x 1/2in, 30p; 0.47 and
0.5µF, size 1 1/2in x 1/2in, 35p; 1.0µF, size 2in x 1in,
45p; 2.0µF, size 2in x 1in 75p.

SILICON PLASTIC RECTIFIERS 1-5A—
Brand new wire-ended DO27, 100PIV at 8p
each or 4 for 30p; 400PIV at 9p each or 4 for
34p; 800PIV at 14p each or 4 for 50p.
5p post and packing on all orders below £5.

MARCO TRADING
(Formerly W. & T. WOOD)
Dept. E2, The Maltings, Station Road
Wem, Shropshire

COMPUTER PANELS: 9in x 7 1/2in long lead
Trans. and Comps., AF13, 8 Trans., 25p (10p); E43,
16 Trans., 40p (10p); E47, 10 Trans., 30p (10p).

AMERICAN PANELS: 4 for 80p (12p) with data.

M.C. METERS: 2-3in, three assorted, £1-05 (25p).

WIRE ENDED NEONS: 10 for 45p (8p); 20 for
75p (8p). Bank of five with 5 C407 Driver Trans., 46p.
Bank of 30 with 5 C407 Driver Trans., £2 (10p).

22 WAY STEPPING SWITCH with Reset, Mains
Operation, 80p (10p).

NEW 46 WAY AS ABOVE, £1-25 (25p).

CROUZET GEARED MOTOR. Mains, 15 r.p.m.,
a.c./w., 75p (15p).

5 FIGURE RESETTABLE COUNTER. 18/22V, will
work on 12V, £2 (15p).

SILICON DIODES 650V 1 1/4in. 10 on Tagboard, 30p
(5p).

I.C. 7400 SERIES ON PANEL(S). 10 for 75p (10p).

COPPER CLAD PAX. PANELS. 5 1/2in x 5 1/2in
6 for 30p (10p).

POLYSTYRENE CAPACITORS. 125V, 100pF to
0.012, 20p dozen; 0.015 to 0.068, 30p dozen (if
ordered alone 10p).

MIXED POLYSTYRENE/S. MICA CAPS. 100 for
45p.

71b ASSORTED COMPONENTS, £1-50.
21b ASSORTED COMPUTER PANELS, £1-50.
S.A.E. 9in x 4in FOR LISTS.

J.W.B. RADIO
75 HAYFIELD ROAD, SALFORD 6, LANCs
Postage in brackets Mail order only
FROM 1st APRIL ADD 10% FOR V.A.T.

100 WATT AMPLIFIER

Fully protected, transformerless, 9 transis-
tor circuit. Input 500 mV. Output into
8 ohms. 0.1% distortion.
Printed circuit board and full instructions.
£1-45p + 10p P. & P. S.a.e. for list of
component bargains.

**EDMUNDS COMPONENTS, 134 NORTH END
ROAD, LONDON, W14.** (Mail order only)

VISIT AUTO TRACTION. Thousands of
bargains in surplus radio equipment. Meters,
motors, relays, TR/TX, telephone equipment,
aircraft equipment. S.A.E. enquiries, 27a
Arragon Road, Twickenham, Middx.
01-892 0489.

Bridge of 4 Z574 diodes, 800 p.i.v., 750MA on
panel. New, 50p, p.p.

Transformer, 9-0-9V 100mA. New 65p, p.p.

Transformer, 24V-14V 500mA. New, £1-15,
p.p.

Transformer, 20-0-24V 1A. New, £1, p.p.

P/C Board 5/5 5 1/2in x 5 1/2in. 10 for 50p + 15p
P. & P.

Transformers, 7.5 + 7.5V app. 1A, 60p,
p.p. 18-0-18V 200mA + 24V 40mA 70p, p.p.

F.M. Tuner, with RF stage with AGC. 3 plug
in transistors neg. earth. Size 2 1/2in x 2in x
1 1/2in. With circuit, £1-25, p.p.

Crouzet Geared Motors, 240 volt 10, 15, 30
or 60 rpm, new, £1-40, p.p.

Transformers, 52-0-52V 1A + 22-0-22V
0.2A, £2, p.p. 34-0-34V 2A + 22-0-22V-2A,
£2, p.p.

Veeder root 7 digit counter. 115V 2-5VA.
75p, p.p.

UHF Tuners, transistorised, £1-50, p.p.

Vero board 0.1 4in x 2 1/2in. 10 for £1 +
15p p.p.

3BP1 Scope Tube with base and screen
(ex equipt.), £2-50, p.p.

Mullard I.F. Module, A.M./F.M. to suit
our tuner, transistorised, £1-25, p.p.

All goods subject to 10% V.A.T. from April
1st.

R.T. SERVICES (Mail order only)

77 Hayfield Road, Salford 6

ADD V.A.T. AT THE STANDARD RATE AFTER APRIL 1st.

MICROCIRCUITS: 709 28p; 710 36p; 723 57p;
741 28p; 748 37p; PA230 70p; SL702C 50p; FET
Op Amp £1-62.

TRANSISTORS: 2N696 14p; 2N697 14p;
2N706A 11p; 2N1613 16p; 2N1711 16p; 2N2218
19p; 2N2219 19p; 2N2219A 19p; 2N2904 17p;
2N2926 RED 6p; ORANGE 7p; YELLOW 8p;
GREEN 9p; 2N3053 15p; 2N3054 40p; 2N3055
35p; 2N3702 10p; 2N3703 10p; 2N3704 10p;
2N3705 9p; 2N3706 9p; 2N3709 8p; 2N3710 9p;
2N3711 9p; 2N4058 12p; 2N4059 9p; 2N4061 11p;
2N4062 11p; 2N5172 10p; 2N5550 39p; AC107
28p; AC126 12p; AC127 12p; AC128 12p; AC176
15p; AC177 23p; ACY21 17p; AF114 14p; AF115
14p; AF116 14p; AF117 5p; AF124 22p; AC107A
15p; BC107B 7p; BC108A 5p; BC108B 7p; BC108C
7p; BC109B 6p; BC109C 7p; BC125 14p; BC147A
9p; BC167A 10p; BC168B 9p; BC169B 10p;
BC177 13p; BC178 12p; BC179 16p; BCY70 13p;
BCY71 22p; BD142 35p; BF115 20p; BF194 13p;
BFX29 24p; BFX84 20p; BFX86 15p; BFX87 24p;
BFX88 18p; BFX50 15p; BFY51 15p; BFY52 15p;
BLY47A 40p; BSX20 12p; OC4 12p; OC45 12p;
OC71 12p; OC72 12p; OC81 18p; OC83 24p.

M.E. SERIES AVAILABLE.

RECTIFIERS: 1A: 50V 3p; 100V 4p; 200V 4p;
400V 5p; 800V 6p; 1,000V 7p; 3A: 400V 12p.

ZENERS BZY88 SERIES: 2.7V to 33V 8p each.

DIODES: IN914 3p; OA90 5p; OA200 5p;
OA202 8p. SCR IR122D (400V 5A) £1-14. BTX30-
600 75p.

LED Panel Lamp with Bush and Data 40p.
Soldercon DIY IC Pin Sockets 1p per Pin.

IC Sockets HI or LO: 14 pin 12p; 16 pin 15p.
Carbon Film 1/4W 5%. Resistors E12 Values 22 to
2.2M 1p each or 7p per 10 of one value.

DALO ETC RESIST FILLED FIBRE TIP PEN 80p.
MINIATURE METAL GLAZE RESISTORS 1/4W 5%
41p each.

ITT POCKET MULTIMETER 27 ranges £17.

JEF ELECTRONICS (P.E.4)
York House, York Drive, Grappenhall,
Warrington, WA4 2EJ. Mail Order Only.
C.W.O. P. & P. 10p per order minimum. Price
List Free.

BEDFORD ELECTRONICS

2 Grove Place Bedford
Bedford SI96L

YOUR LOCAL COMPONENTS SUPPLIER

FREE CATALOGUE ON REQUEST

RADIO & TELEVISION AERIAL BOOSTERS

£2-95, five television valves 45p. 50p bargain
transistor packs, bargain £1 resistor and cap-
acitor packs. UHF-VHF televisions £7-50.
Carr. £1-50. S.A.E. for 3 leaflets. VELCO
ELECTRONICS, Bridge St., Ramsbottom,
Bury, Lancs.

SPECIAL OFFER. 100 mixed resistors.

Preferred Values 1W and 1/4W £1-25, including
postage. 2.2mF 260V WKG 10p each, including
P.P. ALEXANDERS, 16 Inverness Street,
London, N.W.1. Tel. 465 5322.

CASED AMPLIFIERS

2 x ECC83, EL84, EZ80. 20 μ V I/P sensitivity 2W O/P into 7in x 4in 3 Ω speaker. All contained in polished cabinet with non-standard single motor deck. Tested with circuit, £3 (£1).

COMPUTER PANELS

Lots of transistors inc. power types, diodes, R's, C's, pot cores, etc. Some boards broken, but good value at 3lb for £1 (25p), 7lb for £2 (40p).

60p COMPONENT PACKS

Resistors: 350 carbon, 60p (15p); 200 5% hi-stab, 60p (12p); 100 1 and 2%, 60p (8p). Capacitors: 150 mica, poly, ceramic, 60p (8p); 75 electrolytic, 60p (15p); 150 paper, foil, polyester, 60p (15p). Any 5 packs, £2.50 (25p).

FERRIC CHLORIDE

Anhydrous technical quality in sealed 1lb packs, 40p (15p); 10lb, £3.50 (50p).

Components: BC107-8-9, 8p ea., 14 for £1; 709C, 25p; 741C, 25p; 723C, 40p; 2N3055, 35p; 1N4006, 7p; 1N4006, 11p; Crofon 1610 Light Guide, 64 filament, £1 per metre, 5+80p; 10+70p. Surplus capacitors MFD/V: 0.47/350, 6p; 2/150, 2p; 8/350, 8p; 8/450, 10p; 25/25, 5p; 500/50, 12p; 550/6, 3p; 1000+500/18, 12p—lots of others. Lots of odd units, scopes, meggers, avo's, sig. gens, etc., at shop for callers. S.A.E. list. Post in brackets, small parts 3p.

GREENWELD (PE7)

24 Goodhart Way, West Wickham, Kent. Tel. 01-777 2001. Shop at 21 Deptford Broadway, S.E.8. Tel. 01-692 2009.

COMPONENTS—Integrated Circuits, Digital Displays, Diodes, Resistors, Capacitors, Switches. List 3p. CAVERN ELECTRONICS, 29 Clarendon Road, Leicester, LE3 6FB.

MINIATURE CARBON FILM RESISTORS. 5%, $\frac{1}{4}$ W, $\frac{1}{2}$ W, $\frac{3}{4}$ W, E12 Series. 22ohm to 1M Ω . 10 for 7p. 50 for 30p. Mixed values and wattages to your choice. ELECTRONIC COMPONENTS, Lake Bargain Centre, 113 Park Road, Didscot. (Mail order only.)

MISCELLANEOUS

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	$\frac{1}{2}$ lb Reel
10-14	£1-15	65p
15-19	£1-15	65p
20-24	£1-18	68p
25-29	£1-25	75p
30-34	£1-30	80p
35-40	£1-40	85p

The above prices cover P. & P. in U.K. Supplied by

INDUSTRIAL SUPPLIES

102 Parrwood Rd., Wingham, Manchester 20
Telephone No. 061-224 3553

AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS

because this Ministry approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5 50 NOW (S.A.E. for details) TO: 'BOFFIN PROJECTS'

DEPT. KE2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

METER REPAIRS. Ammeters, voltmeters, multi-range meters, etc. Send to METER REPAIRS, 39 Chesholm Road, London, N16 0DS.

RUN YOUR TAPE RECORDER OFF A.C. MAINS

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, model and plug required.) P. & P. 15p. Also available for single outputs 6V, 9V, 12V, 18V, £2 P. & P. 15p.

R.C.S PRODUCTS (RADIO) LTD.
(Dept. P.E.), 31 Oliver Road, London, E.17



ASTOUNDING new MARK 7 AC POWER UNIT with TWO OUTPUTS and LOW BATTERY DRAIN gives the MOST BRILLIANT and BEST EVER INTERNATIONAL PERFORMANCE of all time from 12 volt CAR BATTERY. Fantastic for a VAST RANGE of HUNDREDS of makes and types of 200-240 volt AC and UNIVERSAL AC/DC ELECTRICAL APPLIANCES and EQUIPMENT within its scope. Wonderful for FLUORESCENT TUBES up to the GIANT 8ft. 125 watt size. RECHARGES YOUR BATTERY from any other battery by using any motorist's AC MAINS battery charger. Should be £14 + £1 delivery. OUR PRICE (UNUSED but case marked) ONLY £6.90 + £1 delivery. 8 day's approx. against cash. C.O.D. with pleasure. (Send SAE for details)

Dept PE, BROADWAY DISTRIBUTORS, The Generator Centre, House of Time, 273 Broadway, Rossall, Fleetwood, Lancs.

DIMMIT

range of light dimmers

- ★ professional modules for industrial use on heaters, lamps, motors, etc.
- ★ commercial modules for studio, stage, disco and clubs, etc.
- ★ attractive standard wall mounting models for home and office, etc.

Rotary and slider control versions. Ratings available: 400W, 1,000W, 2,000W.

Send 10p for complete catalogue and price list. Discount for quantities.

YOUNG ELECTRONICS

54 Lawford Road, London NW5 2LN
01-267 0201

Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 65p.)

SEND 5'X7' S.A.E. FOR DETAILS TO:

CROFTON ELECTRONICS
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

CONSTRUCTION AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

MUSIC

If your interest is in SYNTHESISERS and other ELECTRONIC MUSIC projects, you need our 1973 catalogue of circuit assemblies and units. Detailed and informative, complete with project layouts. Send 20p P.O. to: TAYLOR ELECTRONIC MUSIC DEVICES
P.O. Box 42, Chester CH1 2PW

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, MC relays, components, etc. Lower Beeding 236.

PSYCHEDELIC MINI-STROBE

A very POWERFUL, POCKET-SIZED STROBE-LIGHT that is SELF-CONTAINED and you can take anywhere. Go to parties and really BRAIN-FREEZE them with DAZZLING PSYCHEDELIC EFFECTS and STOP-MOTION FLASHES. Boffin's new MINI-STROBE kit constitutes a fully solid-state electronic device which is COMPLETE with FUTURISTIC case/reflector unit, printed-circuit board, electronics, and source-lamp—the only extra is a battery which you can buy locally. The whole thing can be easily built in a few hours.

A veritable FLICKERING FASCINATOR! Adjustable flash-rate. GET ONE (or two) NOW and BEGIN STEALING THE THUNDER at DISCOS and PARTIES with your own POCKET-LIGHTNING!

SEND £1.95 for YOUR MINI-STROBE, to:

Boffin Projects

4 Cunliffe Rd., Stoneleigh, Ewell, Surrey

P.E. SYNTHESISER KNOB KIT

Complete kit, colour coded as per the front cover of February 1973 issue (43 knobs including 7 with calibrated skirts). Made in good quality plastic with £3.56 Post substantial brass inserts Free and grub screws.

DE LUXE KIT

As above but all knobs having calibrated skirts for easy recording £5.36 Post of settings and reprogramming. Free

RE-AN PRODUCTS LTD. BURNHAM RD., DARTFORD, KENT Tel.: DARTFORD 20785

NYLON/A.B.S. EQUIPMENT BOXES, 4-2in x 2-1in x 1-65in inside, take up to 14 blade terminals, 50p. Terminals 1p each. Useful 4-way terminal blocks, spring connectors, 15p. P. & P. 8p per order. MODEC, Curbridge Road, Witney, Oxon.

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

ANALOGUE COMPUTER

Reduced to £150

Shots General Purpose Analogue Computer, complete with stabilised power supplies and double beam oscilloscope for display of results. 18 Function Units (integrators/summers), etc. Details and parts list on request. Demonstration by appointment. Instruction Manual and some spares available. Offers considered.

J. Gray, Oakhill, Bath BA3 5HU
Phone: Oakhill 255

Versatile
10 in
ONE



MINI-LAB Comprising:
• AC and DC Voltmeter • Audio Generator • Ohm Meter • Resistance Substitution • Capacitance Substitution • DC Ammeter • Battery Supply • RF Signal Generator • RF Field Strength Indicator.

This new, unique instrument combines all you need for testing. Money plus 25p.p.&p. back if not satisfied. £11.25

Cash with order or send S.A.E. for illustrated data sheet to:

J. H. ASSOCIATES LTD. (Dept. PE)
Cricketfield Lane, Bishop's Stortford, Herts

ELECTRONICS FANATICS

whether beginner or advanced — we offer a range of over 35 SUPER projects.

Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's just GOT TO BE LOADS TO INTEREST YOU in the science-fiction-world of BOFFIN.

GET YOUR CATALOGUE — SEND JUST 15p NOW!

TO: BOFFIN PROJECTS
4 CUNLIFFE ROAD
STONELEIGH, EWELL
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

FIBRE OPTIC SUPPLIERS

P.O. BOX 702, LONDON W10 6SL

FLEXIBLE LIGHT CONDUIT used to convey light to inaccessible positions for inspection, panel indicators, photo-electric and other applications.

FIBROFLEX Type 1 glass fibre flexible light conduit, 1.14mm active dia., bundle sheathed in P.V.C. Prices per metre (U.K. post free): 1-4, 70p; 5-9, 55p; 10+, 40p; 25m, 66p per reel. Epoxy resin plus ferrules inc. with orders over 10m.

CROFON Type 1610 plastic flexible light conduit, 64 filaments. Active dia. 1.80mm. Prices per metre: 1-4, 1.20; 5-9, 1.10; 10+ 80p. 25m, 161p per reel.

PLASTIC MONOFILAMENT Type FP20, 0.5mm dia. unsheathed. 100m, 13.50; 200m, 16.

Send 5 A.E. for full range of products, price list and literature. Overseas orders add 50p please.

GLASS FIBRE P.C. BOARD—large supplies available. $\frac{1}{8}$ in single sided one ounce copper, 2p per sq ft (under 1ft); 75p per sq ft (over 1ft). $\frac{1}{4}$ in double sided one ounce copper, 1p per sq ft (under 1ft); 21p per sq ft (over 1ft). Please add 10p per sq ft postage and packing. We can cut to your size at 1p per cut. **SOLID STATE LIGHTING**, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP (as in 'W.W.' July '72) **MOTOROLA MC1310P**

EX STOCK DELIVERY

Specn. Separation: 40dB 50Hz—15kHz. Distortion: 0.3%. I/P level: 560mV rms. O/P level: 485mV rms per channel. Input impedance: 50k. Power requirements: 8-12V (at 16mA). Will drive up to 75mA stereo 'on' lamp or LED.

KIT COMPRISES FIBREGLASS PCB (Printed and tinned), Resistors, I.C.s., Capacitors, Preset Potm. and Instructions. Only 13.50 post free.

LIGHT EMITTING DIODE (Red) Suitable as stereo 'on' indicator. For above with panel mounting clip and instructions. Only 35p + p.p.

MC1310P only 12.77 + p.p. 6p
14 PIN DIL SOCKETS, 16p each.

SPECIAL OFFER
IN4002 100V 1A RECT. DIODES. Full Specification Devices. **ONLY 6p each.**

Fi-Comp Electronics
BURTON ROAD
EGGINTON, DERBY DE6 6GY



LOUDSPEAKER BARGAINS

Fane Pop 100 Watt 18" 8 15 ohm	£19.50
Fane Pop 60 Watt 15" 8 15 ohm	£11.15
Fane Pop 50 Watt 12" 8 15 ohm	£9.25
Fane Pop 25 2 12" 25 watts 8 15 ohm	£5.40
Fane Pop 15 12" 10 watts 8 15 ohm	£4.00
Baker Group 25 12" 3, 8 or 15 ohm	£6.60
Baker Group 15 12" 3, 8 or 15 ohm	£8.00
Celestion P58 for Unisys	£2.25
EMI 13 x 8, 3, 8 or 15 ohms	£2.25
EMI 13 x 8, 3, 8 or 15 ohms	£2.60
EMI 13 x 8 twin tweeter 3, 8 or 15 ohms	£3.80
EMI 13 x 8 type 350 15 watt 8 ohm	£8.00
Richard Allen 8" 3, 8 or 15 ohm	£2.25
Richard Allen 12" dual cone 3 or 15 ohm	£2.50
Fane 8" dual cone 8087 8 or 15 ohm	£2.85
Fane 8" J cone roll surround 8077 8 or 15 ohm	£3.50
Elac 59RM109 9" x 5" 15 ohm	£2.70
Elac 59RM114 9" x 5" 8 ohm	£2.70
Elac 6" d cone 8 ohm	£2.25
Elac 6" d cone roll surround 8 ohm	£3.50
Elac 4" tweeter 8 ohm	£1.50
Cross over for above (p & p free)	£1.50
Goodmans 8 P, 8 or 15 ohm	£4.75
Goodmans 10 P, 8 or 15 ohm	£5.25
Goodmans 12 P, 8 or 15 ohm	£10.50
Goodmans 15 P, 8 or 15 ohm	£17.00
Goodmans 18 P, 8 or 15 ohms	£27.50
2", 2" or 3" 80 ohm	£1.65
Philips 5.8 ohm	£1.95
7" x 4" or 8" x 5" 3 or 8 ohm	£1.95
10" x 6" 3, 8 or 15 ohm	£2.00

FREE with orders over £6—Hi-Fi Loudspeaker Enclosures* book.


All units guaranteed new and perfect. Prompt despatch p & p. 25p per speaker.

WILMSLOW AUDIO, Dept. PE

10 Swan St., Wilmslow,
Cheshire, SK9 1HF

SINCLAIR EQUIPMENT—

IC12	£2.00
Z50	£4.25
PZ5	£3.97
Z30	£3.50
Project 60 tuner	£16.80
AFU	£4.50
Stereo 60	£7.80

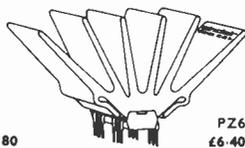


KITS OF PARTS FOR THE IC12
Includes all parts for the printed circuit and volume bass and treble controls needed to complete the mono version £1.30. Stereo version with balance control £3.00.

POWER UNITS FOR THE IC12
A set of components to construct a 30V, 0.5 Amp power supply £2.27. Also suitable Sinclair PZ5 fully constructed £3.97.


PROJECT 60 KIT £2.50
Our extremely popular kit contains the extra capacitors, DIN plugs and sockets, cables and fuse holder needed to complete Project 60.

S-DECS AND T-DECS

S-DECS	£1.44
T-DECS	£2.88
M-DEC A	£3.00
16 diil IC carriers	£1.25

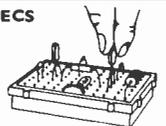

SINCLAIR EXECUTIVE CALCULATOR

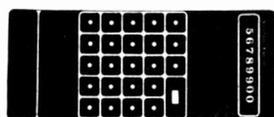

OUR PRICE ONLY £69 (List Price £79)

SWANLEY ELECTRONICS
32 Goldsel Road, Swanley, Kent

Mail order only. Postage 10p per item. Lists 10p. After April 1st please add 10% extra for V.A.T.

BELLING LEE INSULATED TERMINALS. Red or Black, 5 amp max. 10p pair, p.p. 34p

BERCOSTAT WIREWOUND RHEOSTAT. 50 volt, 800 Ω , 25 watts, 2in dia. 25p, p.p. 71p.

FINNED ALUMINIUM HEATSINK. 9in x 1 1/2in. Ready drilled. 20p, p.p. 61p.

SUB-MIN. CROC CLIPS. Red or Black, insulated 4p. Min. quantity, 6, p.p. 34p.

GARRARD MAG. TAPE DECKS: 141 p.p., 50V, solenoid operated brakes, etc. Mains voltage motors 27-50 each, p.p. 11-23.

4 1/2in PLAINAIR FANS. Complete, capacitor, ex equip. 2,800 r.p.m. 23-50, p.p. 40p.

ELECTRIC MOTORS, HOOVER OR CROMPTON PARKINSON. 250V. Single phase a.c.
1 h.p., 1,440 r.p.m., 23-75, p.p. 41.
1/2 h.p., 1,425 r.p.m. or 2,800 r.p.m., 26-75, p.p. 41-25.

1 h.p., 1,440 r.p.m., 22-25, p.p. 75p.

AUDIO CONNECTORS

3 pin Din Plug 13p each.
5 pin Din Plug A type, B type 13p ..
2 pin Din Speaker Plug/Socket 10p ..

3 pin Din Line Socket 18p ..
3 1/2mm Jack Plug Screened 10p ..
Standard Jack Plug 10p ..

Screened Standard Jack Plugs 15p ..
Stereo Jack Plug 18p ..
Screened Stereo Jack Plug 18p ..

Phono Plugs: Red or Black 3p each.
P.p. on above items 34p.

MAINS GREENS. Size: 4in x 1 1/2in. 15p, p.p. 34p.
Red or Green.

LEVER ACTION P.O.1000 TYPE SWITCHES
Lock 4-pole changeover, 15p, p.p. 34p. Ex equip.
Lock 2-pole changeover, 10p, p.p. 34p. Ex equip.

AUDIO LEADS
Screened Phono Leads 46in long, 15p.
3 1/2mm JACK/3 1/2mm JACK 7ft 6in long, 40p.
6-Pin Din A Type, 3-PIN A TYPE. Approx. 5ft long, 70p.

P.p. on above items 54p.

MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,500pF 64V, 7,100pF 40V, 50p each. 20,000 30V, 25,000 25V, 35,000 15V, 30p each, p.p. 10p.

MULLARD FULLWAVE RECTIFIERS
6-48V, 15 amp, 75p, p.p. 84p.

BELLING LEE 1 1/2 amp in-line rubber covered interference suppressor, 25p, p.p. 8p.

RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 54p.

SOLENOIDS 12 VOLT PULL ACTION
2in x 1in x 1 1/2in, 40p, p.p. 8p.

SIMENS MINIATURE RELAY. Double pole changeover dust cover/base 48V, 2500, 50p, p.p. 5p new.

OMRON MK2 MIDGET POWER RELAY. 12V d.c. Double pole changeover. New, 70p, p.p. 5p.

STC MINIATURE RELAY 280 Ω , perspex cover, 6-15V new, 35p, p.p. 5p.

GARDNER'S POTTED TRANSFORMER, 0-250V. Input: 18V 300mA, 50V 150mA, 6V 250mA output. Size: 3in x 2 1/2in x 2 1/2in. 21, p.p. 20p. Ex equip. tested.

TELESCOPIC AERIALS
Chromed 7in closed, 28in extended, 6 section ball jointed base, 23p, p.p. 8p new.

MULLARD 4 DM 160 INDICATORS in plastic holder/cover, ex equip., size approx. 1 1/2in x 1 1/2in x 1 1/2in, 30p, p.p. 8p.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200 Diodes: 1 rect relay: 1 AZ 229 zener ass. capacitor/resistor. Power supply 22V, 250 mA d.c. Output 240V a.c. 21, p.p. 20p. Ex equip.

WIRING CABLE
Size: 1020. Various colours. 350yd, 60p, p.p. 20p.

TOGGLE SWITCHES. Double throw. Ex equip. new condition, 75p doz., p.p. 13p.

TOGGLE SWITCHES. Single pole, double throw. Ex equip., new condition, 50p doz., p.p. 13p.

PAINTON PLUG SOCKETS. Type 159 series. Working voltage 350V a.c./d.c. current, max. 3 amp a.c./d.c. 7 pin plug and socket, 50p, p.p. 6p. 15 pin plug and socket, 21, p.p. 6p. 31 WAY PLUG AND SOCKET. 21-50, p.p. 6p.

CASH WITH ORDER PLEASE

FIELD ELECTRIC LIMITED

3 Shenley Road
Borehamwood, Herts.

Adjacent Elstree Mainline Station
Tel.: 01-953 6009

BUILD A PROFESSIONAL SYNTHESISER



You too can build a professional synthesiser like the one illustrated using the professionally-proven range of Dewtron modules. **NEW MODUMATRIX** modular matrix system replaces clumsy patching. 3 and 4 octave keyboards and contacts.

VCO-2 STABLE, PRECISION V/C OSCILLATOR gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. £22 each or £25 each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch-sensitive playing when used with VCO-2 signals. £15.

Modules (except VCO-1), guaranteed two years.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to a leading group. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I. Send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES
CASH SAVINGS

by buying modules and parts in bulk!

All modules are available separately:

Ring Modulator RM2, £8. Voltage-controlled Oscillator VCO1, £10.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £12. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £9. etc., etc. **ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE.** Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £4.50. REVERB Module and spring unit £15.

NEW COMPONENTS

Post and packaging free for orders over £1.50, include 10p P&P for each single pack under £1.50.

200 Mixed Resistors all types, 50p. 100 Mixed Modern and Miniature Resistors, 50p. 10mF 64V Electrolytic Caps, 5 for 25p; 12 for 50p. 640mF 16V Electrolytic Caps, 3 for 30p; 7 for 60p. 10mF 63V WIMA non-electrolytic, 15p each. 3200mF 10V, 15p; 3 for 38p; 5 for 60p.

SEMICONDUCTORS

Any 6 of the following, 50p, or 10p each. OC71, BFY50, 2N3702, CV8615, BSY95A, NTG885, 2N930, OA81, 2 x 1N914. (OR P60 50p).

CONSTRUCTORS' ITEMS

Subminiature Omron 12V d.c. relays mounted on CCT board, 3 for 60p, P&P 9p; mounted on CCT board with components, 2 for 60p, P&P 7p. GPO Relays, various 200Ω-7000Ω, 30p each. Uniselectors, 10 pole, 25 way, £1 each, P&P 25p. Heavy Duty Foot Pedals, 50p, P&P 20p. 6V 5 digit High Speed Counters, £1.50, 15p P&P.

DICTATING MACHINES

£2.50 each—ideal for spares, motor, power pack, record/replay, electronics with mike £3.25.

TRANSFORMERS

Mains—13V 2.5A and 15V 0.75A £1.45, 20p P&P. Mains—13V 1A 12V 0.5A, £1.25, 20p P&P. Mains—13V 5A and 24V 2A, £2, 25p. P&P. Mains—24V 100mA and 6V 100mA, 75p, 10p P&P. Power Pack—suitable to run Transistor Radio or Cassettes Recorder, 5.5V, 100mA, smoothed d.c. output £1.20, 20p P&P.

EX COMPUTER CIRCUIT BOARDS

10 Boards, 50p, 8p P&P; 25 Boards, £1, 18p P&P. 2 Boards with 2 power transistors, 1E 4 x OC28 type, 50p, 7p P&P.

LAWBAK ELECTRONICS

(HI-FI AND COMPONENTS SPECIALISTS)

18 HIGH RD., SWAYTHLING, SOUTHAMPTON

Telephone: Southampton 58479

No Half Day Closing

Discount and Credit Terms Available

BAKER 12in. MAJOR £9



30-14,500 cps. Double cone woofer and tweeter combination. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 c.p.s. 20 watt RMS.

MAJOR MODULE KIT **£11.50**

30-17,000 cps. with tweeter, crossover and baffle.

BAKER LOUDSPEAKERS FULL RANGE

Regent 12 in.	£8	Superb 12 in.	£15	Group 25 12 in.	£8
Major 12 in.	£9	Auditorium 12 in.	£14	Group 35 12 in.	£9
Deluxe 12 in.	£10	Auditorium 15 in.	£20	Group 50 15 in.	£20

BAKER LOUDSPEAKER CO., BENSHAM MANOR PASSAGE
THORNTON HEATH, SURREY Tel. 01-684 1665

MINIATURE PUSH-BUTTON SWITCHES

4 pole changeover, 250V. Switching 0.1A and carrying 5A. 12.7mm pitch. Total depth 64mm. Available in banks of 1, 3 or 5. Actions available: independent, normal interlock, or momentary. Price per switch unit 40p.

Mains switch 250V 5 amp can be fitted separately or on same frame as above: 1 pole changeover, 50p; 2 pole changeover, 80p.

Illumination for above (12V lamp holder, button) 50p. The Main Switch above with 12mm threaded bush and nut for panel mounting: 1 pole changeover, 80p; 2 pole changeover, £1.05.

NEON in amber lens and holder with resistance for 250V operation, 15p.

MINIATURE SLIDER SWITCH 2 pole changeover. Outside sizes 25mm x 8mm switching 0.3A and carrying 1A, 12p.

MINI MOTOR BOOSTER (P.E. July 1972). Complete kit of parts excepting motor, £2.25, or built and tested, £3. Using 2N3054 and OC202.

All components supplied separately.

2N3054	50p	BC107	00p	BC169	12p
2N3055	70p	BC108	10p	OA200	08p
OC202	85p	BC109	10p	1N4001	07p

P. & P. up to £3-10p. Over £3—free—Postal only.

BORDER ELECTRONICS (Supplies and Manufacture)

8 Broompark, KELSO, Roxburghshire TD5 7SN

Tel.: Kelso 2864

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you . . . but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.


"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. BPE03 Aldermaston Court, Reading RG7 4PF.

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Faringdon Street, London, E4 6. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand: Gordon & Gotch (A/S) Ltd.; South Africa: Central News Agency Ltd.; Rhodesia and Zambia: Kingstons Ltd.; East Africa - Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2-65 (€2.13.00). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

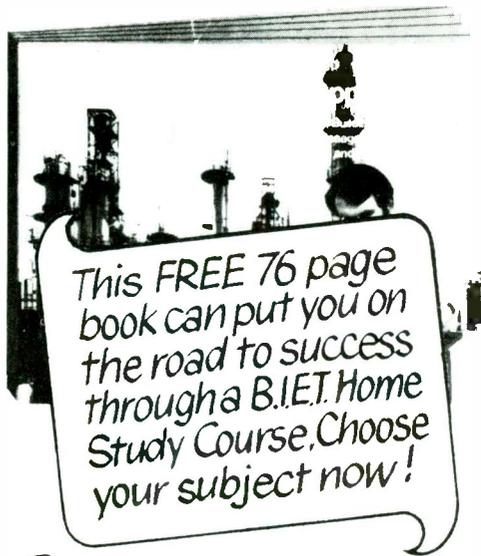

This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

CUT OUT THIS COUPON
Tick or state subject of interest.
Post to address below.

- | | | |
|------------------------------------|---|---|
| MECHANICAL | <input type="checkbox"/> Man. Prod.—cont. | <input type="checkbox"/> Construction-cont. |
| A.M.S.E. (Mech.) | <input type="checkbox"/> Quality Control | <input type="checkbox"/> Building |
| Boiler Inspect. | <input type="checkbox"/> Salesmanship | <input type="checkbox"/> Building Drawing |
| & Operation | <input type="checkbox"/> Storekeeping | <input type="checkbox"/> Build. Foreman |
| C & G Eng. Crafts | <input type="checkbox"/> Work Study | <input type="checkbox"/> Carpentry & Join. |
| C & G Fabricat. | <input type="checkbox"/> Works | <input type="checkbox"/> Civil & Municipal |
| Diesel Engng. | <input type="checkbox"/> Management | <input type="checkbox"/> Engineering |
| Eng. Inspection | <input type="checkbox"/> DRAUGHTSMANSHIP | <input type="checkbox"/> Construction |
| Eng. Metallurgy | A.M.I.E.D. | <input type="checkbox"/> Engineering |
| Inst. Eng. & Tech. | Design of Elec. | <input type="checkbox"/> Construction |
| Inst. Motor Ind. | Machines | <input type="checkbox"/> Surveyors |
| Mainten. Eng. | Die & Press Tool | <input type="checkbox"/> Institute |
| Mechanical Eng. | Design | <input type="checkbox"/> Clerk of Works |
| Sheet Metal Work | Electrical | <input type="checkbox"/> Council Eng. |
| Welding | Draughtsmanship | <input type="checkbox"/> Geology |
| | Gen. Draughtsmanship | <input type="checkbox"/> Health Eng. |
| | Jig & Tool Des. | <input type="checkbox"/> Heat & Vent. |
| | Tech. Drawing | <input type="checkbox"/> Hydraulics |
| ELECTRICAL & ELECTRONIC | <input type="checkbox"/> RADIO & TELE-COMMUNICATIONS | <input type="checkbox"/> Inst. of Builders |
| A.M.S.E. (Elec.) | Colour TV | <input type="checkbox"/> Inst. Works & |
| C & G Elec. Eng. | C & G Radio/TV/ | <input type="checkbox"/> Highway Sup. |
| C & G Elec. Inst. | Electronics | <input type="checkbox"/> Painting & Dec. |
| C & G Elec. Tech. | C & G Telecomm. | <input type="checkbox"/> Public Hygiene |
| Computer Elect. | Tech. | <input type="checkbox"/> Road Engineer. |
| Elec. Maths | Prac. Rad. Elec. | <input type="checkbox"/> Structural Eng. |
| Elec. Science | (with kit) | <input type="checkbox"/> Surveying |
| Electronic Eng. | <input type="checkbox"/> Radio Amateurs | |
| Electrical Eng. | Exam. | GENERAL |
| Install. & Wiring | Radio Servicing | <input type="checkbox"/> Agricultural Eng. |
| Meters | & Repairs | <input type="checkbox"/> Council of Eng. |
| & Measuring | Radio & TV Eng. | <input type="checkbox"/> Inst. |
| Instruments | Trans. Course | <input type="checkbox"/> Farm Science |
| | TV Main. & Serv. | <input type="checkbox"/> General Educat. |
| MANAGEMENT & PRODUCTION | <input type="checkbox"/> AUTO & AERO | <input type="checkbox"/> Gen. Plastics |
| Auto. Control | Aero Eng. | <input type="checkbox"/> Pract. Maths |
| Computer Prog. | A.M.I.M.I. | <input type="checkbox"/> Pract. Slide Rule |
| Electronic Data | A.E.C. Cert. | <input type="checkbox"/> Pure & Applied |
| Processing | Auto Engineer. | <input type="checkbox"/> Maths |
| Estimating | Auto Repair | <input type="checkbox"/> Refrigeration |
| Foremanship | C & G Auto. Eng. | <input type="checkbox"/> Rubber Tech. |
| Inst. Cost & Man | Garage | <input type="checkbox"/> Sales Engineers |
| Accountants | Management | <input type="checkbox"/> Tech. Report |
| Inst. Marketing | Motor Trade Man. | <input type="checkbox"/> Writing |
| Management | Network Plan. | <input type="checkbox"/> Timber Trade |
| Metrication | Numerical Plan. | <input type="checkbox"/> University Ent. |
| Motor Trade Man. | Operational | |
| Network Plan. | Research | |
| Numerical Plan. | Personnel Man. | <input type="checkbox"/> G.C.E. |
| Operational | Planning Eng. | <input type="checkbox"/> 58 'O' & 'A' |
| Research | Production Eng. | <input type="checkbox"/> LEVELS SUBJECTS |
| Personnel Man. | | <input type="checkbox"/> Over 10,000 |
| Planning Eng. | | <input type="checkbox"/> group passes |
| Production Eng. | | |

Coaching for many major exams including ONC, C & G, etc.

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE03 QN
Aldermaston Court, Reading RG7 4PF BPE03

NAME
Block Capitals Please
ADDRESS
.....
.....
OTHER SUBJECTS AGE

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Henry's

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

BUILD THE TEXAN

★ FREE TEAK CASE with complete kits!

FEATURES: New slim design with 6 ICs, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardners low field slim line transformer. Fibre glass PC panel. Complete chassis work.


HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES—DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES: On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector: Mag, P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape head etc. (Parts list Ref. 20 on request). Constructional Details Ref. No. 21. 30p.

SPECIAL KIT PRICE **£28.50** P. & P. 45p
COMPLETE WITH FREE TEAK CABINET

20 + 20 WATT INTEGRATED. I.C. STEREO AMPLIFIER

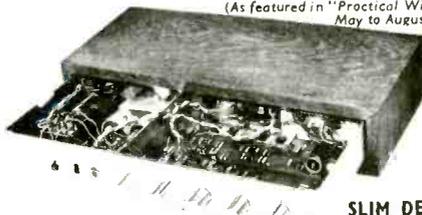(As featured in "Practical Wireless" May to August 1972)



SLIM DESIGN WITH SILVER TRIM

Overall chassis size 14½ in. x 6 in. x 2 in. high

Designer approved kits distributed by Henry's!

ELECTRONIC KITS

Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

IC RECEIVER

ZN414 Radio integrated circuit as featured in Practical Wire, less, January, 1973; Practical Electronics, February, 1973. Price £1.20.

BATTERY TAPE DECK

Garrard 9V tape deck with heads, etc. As previously advertised. Limited quantity. £9.50. Post 30p.

LEARN A LANGUAGE

Recorded Cassettes with step by step phrase books. French, German, Spanish, Italian. £1.49 per cassette. £5.50 per set of four.

DISCO SPOTBANK

As illustrated on the front cover of Practical Wireless, April, 1973. £12.75. P. & P. 35p.

HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES.

FREE 24-page detailed brochure (Ref. No. 17).

★ You can see the savings! ★

EMI HIGH QUALITY CASSETTES

The best U.K. low noise tapes but at a special price. "Living Sound" cassettes meet the highest international standard (IEC94A). Fantastic price savings.

	C60	C90	C120
3 for	£1.10	£1.47	£1.80
6 for	£2.00	£2.85	£3.50
10 for	£3.10	£4.65	£5.60
RRP each	71p	98p	£1.48

Full guarantee. Post paid. See earlier page of this magazine for transistors and semiconductor devices.

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits. PRICE PER PAIR £5.90. Post 10p.

MARRIOTT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO
 "17" High Impedance £2.00
 "18" Med. Impedance £2.00
 "36" Med.-Low Imp. £3.50
 Erase Heads for above 75p
 "63" 2 track mono — High Impedance £1.75
 "43" Erase Head for above 75p

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)
 XN3, XN13, GN6 0-9 side view with data, 85p.
 GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.
 3015F 7 seg. £2 each, £7 per 4 with data.
 12 and 24 hour clock circuits. Ref. No. 31 15p.

MINIATURE AMPLIFIER

5 transistor. 300mW o/p. Fitted volume and sensitivity control 9 volt operated. £1.75 each, p.p. 15p.

QUALITY SLIDER CONTROLS

60mm stroke singles and ganged. Complete with knobs. 5kΩ, 10kΩ, 25kΩ, 100kΩ, 250kΩ, 500kΩ, 1 meg. Log and Lin. 40p each, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ. Log and Lin. ganged. 60p each.

LOW COST HI-FI SPEAKERS



E.M.I. Size 13½ in x 8½ in and Ceramic Magnet
TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.
TYPE 150TC Twin cone version £2.75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85. Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70. Post 28p.



POLISHED CABINETS 150, 150TC, 450 £4.60. Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 OHM)
SERIES 6 (Assembled 150TC) per pair £16.50. Post 70p.
SERIES 8 (Assembled 450) per pair £18.95. Post 70p.




ML3 MW/LW TUNER TO BUILD

Uses Mullard Module. Slow motion tuning. Built-in battery. Ferrite aerial. Overall size 7 in x 2½ in x 3½ in. **TOTAL COST TO BUILD** £4.85. Post 15p. All parts sold separately—Leaflet No. 6.

"BANDSPREAD" PORTABLE TO BUILD

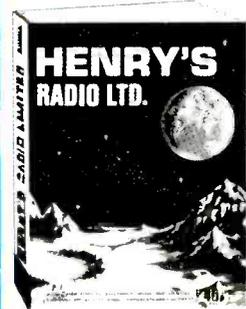Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandspread for extra selectivity. 600mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. **TOTAL COST TO BUILD** £7.98, p.p. 32p (Batt. 22p). All parts sold separately—Leaflet No. 2.



CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.


PRICE 55p Post paid (40p FOR CALLERS)
PLUS! FIVE 10p VOUCHERS

Send to this address—Henry's Radio Ltd. (Dept. PE), 3 Alberman Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303", see above.

TEST EQUIPMENT

Just a selection

SE250B Pocket Pencil Signal Injector, £1.90
 SE500 Pocket Pencil Signal Tracer, £1.50
 THL33D Robust 2 K/Volt, £4.55; with case £4.95
 TE15 Dip Meter 440 KHz—280 MHz, £13.45
 500 30 K/Volt Multimeter, £9.25; with leather case, £10.50
 200 H20 K/Volt Multimeter, £4.20; with case £4.95
 AF105 50K/V Multimeter, £8.50; with case, £9.50
 U4341 AC/DC Multimeter with transistor tester with steel case, £10.50
 TE20D RF Generator 120KHz—500MHz, £15.95. Carr. 35p
 TE22D Audio Generator 20Hz—200KHz, £17.50. Carr. 35p
 CI-5 3in Pulse Scope 10Hz—10MHz, £39.00. Carr. 50p
 TE65 Valve Voltmeter 28 ranges, £17.50. Carr. 40p
ALL NOMBREX MODELS IN STOCK

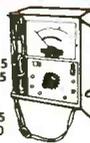

BUILD THIS VHF FM TUNER

5 TRANSISTORS 300kc/s BANDWIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. **TOTAL** £6.97, p.p. 20p. Decoder Kit £5.97. Tuning meter unit £1.75. Mains unit (optional) Model P5900 £2.47. Post 20p. Mains unit for Tuner and Decoder P5612 £3.25. Post 20p.



PA-DISCO-LIGHTING

UK's Largest Range—Write phone or call in. Details and demonstrations on request.
DJ30L 3 Channel sound to light unit, 3kW, £29.50
DJ40L 3 Channel Mic (Built-in) to light, 3kW, £38.75
DJ705 70 watt Disco amp/mixer, £49.75
DISCOAMP 100 watt Disco amp/mixer, £65.85
DJ1055 30 watt Disco amp/mixer, £32.25
 Anti-Feedback Quality Mic, £11.50
DJ1500 50 watt PA amplifier, £43.95
DJ700 70 watt £52.75
 Group 300 150 watt rms Group Valve amplifier, £86.00
 ● Portable discos—details on request
 ● Credit terms for callers



FIBRE OPTICS LIGHTING MICS EFFECTS PROJECTORS SPOTS DIMMERS STANDS MIXERS SPEAKERS Everything for PA — Disco — Lighting. FREE Stock List Ref. No. 18.

SINCLAIR PROJECT 60 MODULES —SAVE POUNDS

Z30 £3.57 Z50 £4.37
 STEREO 60 £7.97 PZ5 £3.97
 PZ6 £6.37 PZ8 £4.77.
 Transformer for PZ8 £2.95.
 Active Filter Unit £4.45.
 Stereo FM Tuner £16.95.
 IC12 £1.80 Q16's £15 pair.
 Post, etc. 20p per item.



PACKAGE DEALS Post 25p
 2 x Z30, Stereo 60, PZ5 £15.95
 2 x Z30, Stereo 60, PZ6 £18.00
 2 x Z50, Stereo 60, PZ8 £20.25
 Transformer for PZ8 £2.95
 PROJECT 605 KIT £19.95

VAT Prices DO NOT include Value Added Tax. From 1st April, 1973, 10% must be added and shown separately to your total order (inclusive of post/packing). Help us to help you receive your order without delay.

Henry's RADIO LIMITED
 EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
 354-356 High Fidelity and Tape Equipment 01-402 5854/4736
 309 PA-Disco-Lighting High Power Sound 01-723 6963
 303 Special offers and bargains store
 All mail to 303 Edgware Road, London W2 1BW

Open—9 am-6 pm
 6 days a week
 (309 closed Thursday)
 All stores open all day Saturday