

PRACTICAL

# ELECTRONICS

AUGUST 1973

20p



## BATTLE CHESS

AUDIO COMPRESSOR

550 v MEGOHMMETER

P.E. Sound Synthesiser...

REVERBERATION AMPLIFIER

# Antex X25



## The Japanese have a Yen for it.

*in case you are not familiar with Japanese:*

Our distributors in Japan are telling their their customers about the importance (when soldering I.C.'s and transistors) of the low leakage of our Model X.25 soldering irons.

**Model X.25** - 25 watt sells at £1.75 + P & P 8p VAT 18p

**Model G** - 18 watt £1.95 + P & P 5p V.A.T. 20p

**Model CCN** - 15 watt miniature iron £1.95 + P & P 5p VAT 20p

Ask your usual wholesaler or retailer for Antex irons or if you have any difficulty, send the coupon to us direct.

**ANTEX** From radio or electrical dealers, car accessory shops or in case of difficulty direct from:  
**ANTEX LTD. FREEPOST PLYMOUTH PL1 1BR**  
 (no stamp required) Tel 0752 67377.

Please send the following:  Please send the ANTEX colour catalogue.

I enclose cheque/P.O./Cash (Giro No. 258 1000) .....

NAME .....

ADDRESS ..... P.E.8

# PRACTICAL ELECTRONICS

VOLUME 9 No. 8 AUGUST 1973

---

## CONSTRUCTIONAL PROJECTS

- BATTLE CHESS** *by D. Coles*  
Bring the battlefield to the game of chess 664
- AUDIO COMPRESSOR** *by R. A. Penfold*  
Provides an almost constant output from widely varying inputs 669
- P.E. SOUND SYNTHESISER—7** *by G. D. Shaw*  
Reverberation amplifier for springline, ring modulator and peak level meter 678
- 550V MEGOHMMETER** *by B. V. Lamb*  
A high voltage generator for checking mains insulation 696
- SIMPLE FLASHER** *by J. B. Dance*  
Using the 555 timer chip to control the operation of flashing lights 702

## GENERAL FEATURES

- INGENUITY UNLIMITED**  
Light-Operated Power Controller—Reed Relay Current Trip—Reversing Light Warning 672
- 25 YEARS OF SEMICONDUCTORS—2** *by M. J. Rose*  
Power devices, photo devices and integrated circuits 692
- LOGIC TUTOR EXPERIMENTS—4** *by M. J. Hughes*  
De Morgan's Theorem 704
- NEW DEVICES . . . APPLICATIONS**  
The latest in circuit ideas for the experimenter 705

## NEWS AND COMMENT

- EDITORIAL—Two-Way Link** 663
- SPACEWATCH** *by Frank W. Hyde*  
Sun jolts the earth—Chinook winds—Asteroids 674
- STRICTLY INSTRUMENTAL** *by K. Lenton-Smith*  
Comments on contemporary sounds 677
- COMPONENT SHOW '73**  
Report from the recent London RECMF Show held at Olympia 689
- INDUSTRY NOTEBOOK** *by Nexus*  
What's happening inside industry 698
- ELECTRONORAMA**  
Looking at the latest developments in electronic watches 700
- READOUT**  
Author of the Synthesiser answers back 710
- IMPORTANT ANNOUNCEMENT**  
Quadraphonics comes to P.E. 691

Our September issue will be published on Friday, August 10, 1973

---

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2-65.



## "I MADE IT MYSELF"

Imagine the thrill you'll feel! Imagine how impressed people will be when they're hearing a programme on a modern radio you made yourself.

# Now! Learn the secrets of radio and electronics by building your own modern transistor radio!

Practical lessons teach you sooner than you would dream possible.

What a wonderful way to learn - and help qualify yourself for a new, better-paid career! No dreary ploughing through page after page of dull facts and figures. With this fascinating Technatron Course, you learn by building!

You build a modern Transistor Radio... a Burglar Alarm. You learn Radio and Electronics by doing actual projects you enjoy - making things with your own hands that you'll be proud to own! No wonder it's so fast and easy to learn this way. Because learning becomes a hobby! And what a profitable hobby. Because opportunities in the field of Radio and Electronics are growing faster than they can find people to fill the jobs!

**No mathematics, no soldering - yet you learn faster than you ever dreamed possible.**

Yes! Faster than you can imagine, you pick up the technical know how you need. Specially prepared step-by-step lessons show you how to: read circuits - assemble components - build things - experiment. You enjoy every minute of it!

You get everything you need. Tools. Components. Even a versatile Multimeter that we teach you how to use. All included in the course AT NO EXTRA CHARGE! And this is a course anyone can afford. You can even pay for it in easy payments - in fact you could make extra cash from spare-time work when you've turned yourself into a qualified man through B.I.E.T. training.

**So fast, so easy, this personalised course will teach you even if you don't know a thing today!**

No matter how little you know now, no matter what your background or education, we'll teach you. Step by step, in simple easy-to-understand language, you pick up the secrets of radio and electronics.

You become a man who makes things, not just another of the millions who don't understand. And you could pave the way to a great new career, to add to the thrill and pride you receive when you look at what you have achieved. Within weeks you could hold in your hand your own powerful radio. And after the course you can go on to acquire high-powered technical qualifications, because B.I.E.T.'s famous courses go right up to City & Guilds levels.

**Send now for FREE 76 page book - see how easy it is - read what others say!**

Find out more now! This is the gateway to a thrilling new career, or a wonderful hobby you'll enjoy for years. Send the coupon now. There's no obligation.

**POST TODAY FOR FREE BOOK**

To: BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY QH BPE18  
Aldermaston Court, Reading RG7 4PF

Yes, I'd like to know more about your course. Please send me free details - plus your big, 76-page book that tells about all your courses.


NAME

ADDRESS



BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

# P.E. SOUND SYNTHESISER

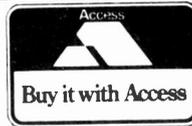

SIMPLY SEND EXACT DETAILS OF NAME AND NUMBER COPIED FROM THE FACE OF YOUR ACCESS CARD AND LEAVE THE REST TO US.

## DESIGNER APPROVED KITS

The 'RING MODULATOR' I.C.  
**SG 3402N**

£1.74 each

ELECTRONIC ATTENUATOR  
**MFC 6040**

£1.00 each

**Z1J NOISE DIODE**  
43.5p each

mini D.I.L.  
741's 32p each  
while stocks last

4p stamp brings latest lists


Attractive discounts on quantity purchases.

We stock a full range of professional quality components as specified for this exciting project and many prices are down.

2% M.O. resistors now 3.2p ea. 5% low noise carbon film 1.8p ea. Cermet presets now 37.5p ea. Full range of capacitors - Ceramic, Electrolytic, Polyester, Styrene, Carbonate, Silver Mica, etc. Modular hardware kits; Dual-Rail Regulated Power Supplies; Individual component/module kits from date of publication. P.C.B. for the exciting 'Hutchinson' Tone Control Module.

**EATON AUDIO** P.O. Box No. 3, ST. NEOTS HUNTINGDON PE19 3JB

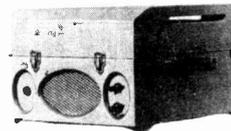TERMS: MAIL ORDER ONLY. C.W.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2. Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P. All prices subject to V.A.T.



## CASED AMPLIFIERS

Polished wooden cabinet 14 x 13 x 9in with hinged lid containing a sensitive (20μV) 4-valve amplifier with tone and volume controls, giving about 3 watts output to the 7 x 4in 3Ω speaker. Also a

non-standard single motor tape deck. Easily converted to record player, guitar practice amp., baby alarm, etc. Supplied in good working condition with circuit diagram. Mains operated. Only £3 (£1 up to 200 miles, £1.20 over). Special cassettes £1 (25p). Spare heads 40p. Damaged machines from £1.50 to callers only. Amplifier chassis, 2 ECC83, EL84, EZ80 £1.65 (35p).

## COMPUTER PANELS

Type A: 4 OC35, 4 GET103, etc., 50p; Type C: 2 OC35, 2 OC76, 6 OC42, etc., 30p; Type D: 4 OC36, 8 GET103, etc., 60p (5p each). Type E: 4 OC29, 4 trim pots, 4 ACY19, 8 other transistors, 35 diodes, etc. £1 (10p).

Parcel of 12 top quality boards £2 (25p). 7lb of lower quality including some broken £2 (40p), 56lb £12 (c.p.). Boards from 5p to callers. Pack of boards containing at least 500 components, including 50 transistors 60p (15p)

## 71B BARGAIN PARCELS

Hundreds of new components - capacitors, resistors, switches, crystals, pots, PC boards, etc. Outstanding value £1.65 (35p). 500 assorted resistors, good selection £1 (15p); 40 asstd. pots £1 (25p); 300 asstd. capacitors, all types £1 (25p). Heavy duty heat sinks 6 x 5 x 3in, weight 3lb with 2 power transistors, OC36 or 2N1146A £1 (25p). Large selection of panel meters for callers. Audio oscillator 50Hz-20kHz, BFO No. 8 £10; RF Signal generator, Marconi TF144G, 85kHz-25MHz from £12. 741C TO99 or 8 pin DIL 28p; BC107/9 14 for £1; 2N3055 35p. Veroboard in stock. Post in brackets, small parts 3p. VAT NOT INCLUDED. S.A.E. list, details.

## GREENWELD ELECTRONICS (PE3)

24 Goodhart Way, West Wickham, Kent. SHOP at 21 Deptford Broadway, SE8 (next to old cinema). Callers most welcome. Tel. 01-692 2009.

# SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT. NEW & SECONDHAND MUSICAL INSTRUMENTS. DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES

Announcing our improved range of constructor modules

FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A "Plastic Power" Driver Transistors now available.

To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.



**SA35** 35W RMS uses 7 transistors and 7 diodes. Carr. paid. **£4.45**

A NEW ADDITION IS THE **SA50 at £5.65**

Carr. paid. A rugged, well built unit, capable of 50W RMS out, with all the advantages of Saxon Amplifier design and quality. Ready now.

**SA100** makes an ideal unit in disco assemblies

A real glutton for work. Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid. **£10.90**

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000Hz ± 1dB	All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in its SA100
Distortion	0.2% at 1kHz	
Loads	4 to 16 ohms	
Quiescent current	15mA	
Noise	Better than -75dB	
Supply voltage	SA35-45V SA50 45/65V SA100 40-70V	
Size	4 1/2in x 4in x 1in (SA100) 4in x 3in x 1in (SA35/SA50)	

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilised supply for 2 SA25/35's	£4.90
PU70	Unstabilised supply for one or two SA100	£7.75 carr. 40p
PS45	Stabilised module for 2 SA25's or two SA35's	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted	£3.50 carr. 20p
PS70	Stabilised supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

## TWO NEW PA/MIXER CONTROL UNITS

Built for hard work!

In extra slimline easy-fit case.

Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master controls. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos, etc. Standard jack sockets, compact design. In strong metal cases. All Units guaranteed for 3 years.

- HIGH AND LOW IMPEDANCE INPUTS
- BASS/TREBLE/VOLUME ON EACH PAIR
- MASTER CONTROL ON OUTPUT

**M4H**  
4 high Z, 4 low Z inputs, 4 sets of controls. Case 10" x 8" and only 2 1/2in deep. Carr. paid. **£18.50 + V.A.T.**

**M6HL**  
12 inputs (6 high Z, 6 low Z). Carr. paid 18" x 8" 2 1/2". **£27.50 + V.A.T.**

Channel section modules, for building your own: gain—16 x (24dB). Tone controls—18dB swing. Carr. paid.

**£3.50 + V.A.T.**


### CONTROL UNITS

Mono (as shown). **£6.50**

Carr. 20p.

Stereo. **£15.80**

Carr. 30p.

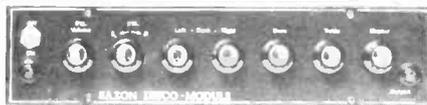

Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2in x 3in x 4in deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume. Microphone volume, bass treble, mains on/off. **COMPARABLE TO UNITS AT OVER TWICE THE PRICE.** (N.B.—Stereo only has mic. Input.)

PLEASE ADD 10% FOR V.A.T. TO TOTAL VALUE OF YOUR ORDER

S.A.E. brings Saxon equipment and bargains list

● 160 watts version with power supply (Carr. 50p) **£27.90**

### 120 WATT HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.

SPECIFICATION

Power output, 120W into 8 ohms	Module only (Carr. 20p)	<b>£13.90</b>
Freq. response, 20-20,000Hz ± 2dB		
Input sensitivity, 200mV into 10K		
Construction, Fibreglass board		
Size, 8in x 4in x 4in (5in with supply)	Module and power supply (Carr. 40p)	<b>£18.95</b>
Low distortion parallel push-pull output stage.		



### 3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls, 2 amplifier sockets eliminate need for split leads. Up to 3kW lighting load. Smartly finished steel case. Carr. 30p. **£19.75**

### SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3kW (3,000W) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.

### SINGLE CHANNEL UNIT

Operates from 5-100W amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range, at a cost of about 5p. Carr. pd. **£8.90**

### COMPLETE AMPLIFIERS

CSE 100 **£34.90** carr. free

This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100W RMS and continuous signal outputs of 70W. Two individually controlled inputs with wide range bass and treble controls.

SAXON 100 **£48.50** carr. free



With an RMS output of 120W speech and music, 100W continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

### LOUDSPEAKERS British made bargains!!

12in 25W 8/15 ohms **£5.95** carr. 30p. 15in 50W 8/15 ohm **£14.50** carr. 30p. 12in 40W 15,000 gauss magnet system 8/15 ohm **£11.50** carr. 40p. 600 Watt 3 colour Light Boxes Smart Rexine finish **£15** carr. free.

### A.K.G. MICROPHONES

D11 DHL IDEAL DISCO MIKE ONLY **£9.45** (rrp **£11.00**). S.A.E. for special price list.

Order and personal shoppers to:

**SAXON ENTERTAINMENTS LTD., 329 Whitehorse Road, W. Croydon, Surrey CR0 2HS**

Telephone 01-684 6385

From 9.30 a.m.-5.30 p.m.

TRADE AND EXPORT ENQUIRIES INVITED.

Prices quoted do not include V.A.T. 10% must be added on to total value of order for V.A.T.

### TERMS OF BUSINESS

Cash with order (C.W.O.). For C.O.D. please add 35p extra, cash by regd. letter please.

# You'll hardly be able to believe your ears!

Can you  
really get  
sound quality  
like this for  
less than £18?  
Yes you can!  
with the new  
**STEREO 21**



Until now, richly satisfying sound has always cost a richly satisfying price. *But not any more!* For an almost unbelievable £17.95, you can have Stereo 21—audio for the connoisseur.

Whatever your taste in music, you can hear it on STEREO 21 the way its composers heard it in their dreams! Beethoven or Mahler . . . Ellington or Jellyroll Morton . . . Das Nibelung or Jesus Christ Superstar . . . Carols from King's College Chapel or the return of a Beatle . . . everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!

And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience!

Top-quality amplifier, BSR turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit, no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins, all parts supplied including full instructions—all for £17.95 (plus the cost of post and packing if you buy by mail), and—round it all off—a money-back Guarantee if your pleasure in STEREO 21 is not complete!

**Just think—In only a few days  
you could be giving your ears  
the treat of a lifetime—AND introducing  
your envious friends to  
STEREO 21!**

Personal shoppers and mail order price

**£17.95**

Plus £1.50 P&P.

Diamond styli, if required, £1.37 extra



**RADIO AND TV COMPONENTS (ACTON) LTD.**

21d High Street, Acton, London W3 6NG

323 Edgware Road, London W2

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

Practical Electronics August 1973

# VISCOUNT III— a boost in the output

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as *value for money!* And that's something you get in abundance with VISCOUNT III. We design it... we make it... we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back. And the teak finish will harmonise and enhance virtually any style of interior decor!

The heart-stopping timbre of Tom Jones at his most virile... the last lingering harmonics of a solo performance by Heifetz or Menuhin... the pathos and the panache of Liza Minelli... the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have *never* experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

**SPEAKERS:** Duo Type II Size approx. 17in x 10½in x 6½in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. £14.00 a pair. £2.20 p. & p. Duo Type III Size approx. 23in x 11½in x 9½in. Drive unit 13½in x 8½in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20KHz. Teak veneer cabinet. £32.00 a pair - £3.30 p. & p.

#### PRICES: SYSTEM 1

Viscount III R 102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP25 Mk III with	
MAG cartridge plinth & cover	£18.00 + £1.75 p & p
<b>total</b>	<b>£56.20</b>

STILL ONLY **£49** COMPLETE

Available complete for only £49.00 + £3.50 p. & p.

#### PRICES: SYSTEM 2

Viscount R 102 amplifier	£24.20 + £1 p & p
2 Duo Type III speakers	£32.00 + £3.30 p & p
Garrard SP25 Mk III with	
MAG cartridge plinth & cover	£18.00 + £1.75 p & p
<b>total</b>	<b>£74.20</b>

Available complete for £85.00 + £4 p. & p.



## THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles it covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is 7in wide, 2in high and 4½in deep.  
 \* Circuit diagram and comprehensive instructions 55p free with parts.  
 \* Fully retractable and lockable car aerial £1.37 post paid.

#### CAR RADIO KIT £6.60 p. & p. 55p


Speaker with baffle and fixing strips £1.65. 23p p. & p., post free if bought with the kit. Send stamped addressed envelope for leaflet.

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

**SOUND 50 45 WATT MONO AMPLIFIER.** Ideal for Disco. Output Power: 45 watts R.M.S. (Sine Wave) Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control 2 inputs at 200mV into 470K. Size: 19½ x 10½ x 8ins. Amplifier £31.35 plus £1.65 p. and p. Output for 3, 8 and 15 ohm speakers.



**£31.35** + £1.65 p. & p.

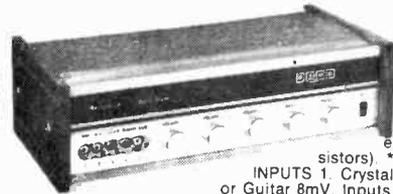

## RELIANT Mk IV £13.50


\*5 Electrically Mixed Inputs. \*3 Individual Mixing controls. \*Separate bass and treble controls common to all 5 inputs. \*Mixer employing F.E.T. (Field Effect Transistors). \*Solid State Circuitry. \*Attractive Styling.

INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner. Monitor. Organ, etc.). All 250mV sensitivity. Output 20 watts into 8 ohms (suitable for 15 ohms). Size approx. 12½ x 6 x 3½ ins. £13.50 p. & p. 60p.
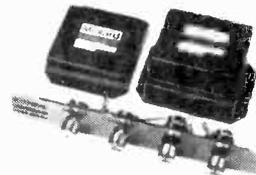
## UNISOUND MODULES

ONLY £7.64 + 55p p. & p.

For the man who wants to design his own stereo—here's your chance to start with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.




## IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. Mains operated.

**£9.90** p. & p. 80p

The Viscount III, the fabulous Stereo 21 and the Unisound Modules will all accept this unit, simply connect up.

ALL PRICES INC. VAT

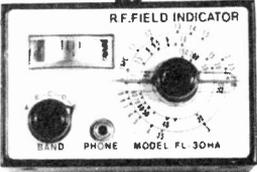

**R.F. FIELD INDICATOR**  
Model FL-30HA. Frequency Range: 5 ranges 1Mc/s to 250Mc/s. £3.



4 1/2 in. x 3 1/2 in. **METER.** 30µA, 50µA or 100µA. £2-50.



**TAPE RECORDER LEVEL METER**  
500µA. 50p



**MULTI-METER**  
Model 200H  
20,000 ohm/volt. £4-80.




**CARDIOID DYNAMIC MICROPHONE**  
Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms. £4-50.



**MULTI-METER**  
Model C-7081GN  
Range Doubler 50,000 ohm/volt, 15µA High Sensitivity Meter. £11-25.

All items advertised in previous numbers of this magazine still available. There is 10% V.A.T. charge on all items. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 5. Special prices for quantity quoted on request.

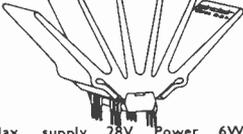**M. DZIUBAS**  
158 Bradshawgate • Bolton • Lancs. BL2 1BA



**SINCLAIR IC12** £2-00  
Max. supply 28V. Power 6W RMS. Complete with free printed circuit board and 44-page instruction booklet.

**KITS FOR IC12 AND IC TOMORROW**  
Except for the power kits and speakers all items suit both integrated circuits.

**DELUXE KIT**  
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1-45. Stereo version with balance control £3-30.

**POWER KIT FOR IC12**  
A set of components to construct a 28V 0.5A power supply £2-27. Also suitable Sinclair PZ5 £3-97.

**POWER KIT FOR IC TOMORROW**  
A set of components to construct a 35V 1A power supply £2-97.

**LOUDSPEAKERS FOR IC12**  
8 ohm types. 5" £1-00. 5" x 8" £1-45.

**PREAMPLIFIER KITS.**  
Type 1 for magnetic pickups, mics. and tuners with 3 position equalisation switch. Mono model £1-20. Stereo model £2-20. Type 2 for ceramic or crystal pickups. Mono 60p. Stereo £1-20.  
SEND S.A.E. FOR FREE LEAFLET ON KITS AND TBA651.

**S-DECS AND T-DECS**

S-Decc	£1-44
T-Decc	£2-88
µ-Decc A	£3-00
16 di IC carriers	£1-20

**IC RADIO CHIP TBA651** £2-10  
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabiliser. With data £2-10. Send S.A.E. for free leaflet. Kit of resistors, capacitors and IF filters £1-75 extra.

**SWANLEY IC TOMORROW** £2-50  
The World's most powerful IC amplifier. Similar to the above but operates at 35V max. supply and gives 12W RMS output. Manufactured for us by a leading semiconductor company. Supplied with our instructions and a 6-month guarantee, but no printed circuit.

**SINCLAIR EQUIPMENT**

Z30	£3-50	Stereo 60	£7-80
PZ5	£3-97	Z50	£4-25
PZ8	£6-60	PZ6	£6-40
AFU	£4-50		

Transformer for PZ8 £2-95.  
Project 60 tuner £16-80.  
Project 605 £19-90.

**EXECUTIVE CALCULATOR** £50

**PROJECT 60 KIT** £2-50  
Our extremely popular kit contains the extra capacitors, din plugs and sockets, cables and fuseholder needed to complete Project 60.

**SWANLEY ELECTRONICS**  
32 Goldsel Road • Swanley • Kent BR8 8EZ  
Postage 10p per item. Please add 10% extra to total cost of order for VAT. Official credit orders from schools, etc., welcome. Full lists 10p post free. Send S.A.E. for free 8-page book on IC TOMORROW, IC12 kits and TBA651.

# Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.

Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a

mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Training Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

Ring  
**01-637 2171**

between 9 a.m. and 9 p.m. and ask for Mr PLATT

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.

Please give me further information.

Name \_\_\_\_\_

Address \_\_\_\_\_

Age \_\_\_\_\_ Phone \_\_\_\_\_ PE8

**CONTROL DATA**  
INSTITUTE **CONTROL DATA**  
LIMITED

The Training Division of one of the world's largest Computer manufacturers.

# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

## COMPLETE TELEPHONES



EX G.P.O. NORMAL HOUSEHOLD TYPE

**ONLY £1.05**

POST & PACKING 45p EACH



## TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

**ONLY 27½p**

POST & PACKING 16½p

## TESTED AND GUARANTEED PAKS

- B79 4 IN4007 Sil. Rec. diodes, 1,000 PIV 1 amp. plastic **55p**
- B81 10 Reed Switches, 1" long 1" dia. Highspeed P.O. type **55p**
- B99 200 Mixed Capacitors. Approx. quantity, counted by weight **55p**
- H4 250 Mixed Resistors. Approx. quantity counted by weight **55p**
- H7 4 Wirewound Resistors. Mixed types and values **55p**
- H9 2 OCP71 Light Sensitive Photo Transistor **55p**
- H28 20 OC200/1/2/3 PNP Silicon uncodded TO-5 can **55p**
- H30 20 1 Watt Zener Diodes, Mixed Voltages 6.8-43V **55p**
- H35 100 Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked **55p**
- H38 30 Short lead Transistors, NPN Silicon Planar types **55p**
- H39 10 Integrated circuits 6 gates BMC 962, 4 flip flops BMC 945 **55p**
- H40 20 BFY 50/2, 2N696, 2N1613, NPN Silicon uncodded TO-5 **55p**
- H41 2 BD131/BD132 Complementary Plastic Transistors **55p**

## UNMARKED UNTESTED PAKS

- B1 50 Germanium Transistors PNP, AF and RF **55p**
- B66 150 Germanium Diodes Min. glass type **55p**
- B83 200 Trans. manufacturers' rejects all types NPN; PNP, Sil. and Germ. **55p**
- B84 100 Silicon Diodes DO-7 glass equiv. to OA200, OA202 **55p**
- B86 100 Sil. Diodes sub. min. IN914 and IN916 types **55p**
- B88 50 Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc. **55p**
- H6 40 250mW. Zener Diodes DO-7 Min. Glass Type **55p**
- H15 30 Top Hat Silicon Rectifiers, 750mA. Mixed volts **55p**
- H16 15 Experimenters' Pak of Integrated Circuits. Data supplied **55p**
- H17 20 3 amp. Silicon Stud Rectifiers, mixed volts **55p**
- H20 20 BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts **55p**
- H34 15 Power Transistors, PNP Germ. NPN Silicon TO-3 Can **55p**

## MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1.10 each**



OVER  
**1,000,000**

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

**600,000** Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc.

Audio NPN, similar to ZTX300, 2N3708/9 BC107/8/9, BC168/9, etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 500 for £3.30, 1,000 for £5.50, 10,000 for £44.

P & P 11p per 1,000

## OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon Alloy, TO-5 can.  
TYPE "B" PNP Silicon, plastic encapsulation.  
TYPE "E" PNP Germanium AF or RF.  
TYPE "F" NPN Silicon plastic encapsulation.  
TYPE "G" NPN Silicon, similar ZTX300 range.  
TYPE "H" PNP Silicon, similar ZTX500 range.

**8 RELAYS FOR 8 VARIOUS TYPES P & P 27½p £1.10**

## Our famous PI Pak is still leading in value for money

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.I. Only 55p. 11p P & P on this Pak.



## A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Television.

**This complete kit of parts costs £3.85, post paid.**

A MUST for Colour T.V. Alignment.

## STEREO DECODER £4.95

A ready built unit, ready for connection to the I.F. stages of your existing FM Radio or Tuner Unit. A tell tale light can be connected to show the presence of a Stereo transmission and correct operation of the Unit.

The Unit is in the form of a small printed circuit, and no further alignment is necessary, as all preset adjustments have already been carried out at the factory.

It is recommended that a L.E.D. is used as the indicating light and a suitable device is available from us at 36½p.

Supplied with necessary instructions and written guarantee.

## FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

**100,000** Plastic Power Transistors

in stock, more on way!

## NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min.	15	HFE Min.	15
40 watt	1-12	22p	13-25	26-50
90 watt	1-12	26p	20p	18p
		24p	24p	22p
Range 2	VCE Min.	40	HFE Min.	40
40 watt	1-12	33p	13-25	26-50
90 watt		38p	31p	29p
		36p	36p	33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

**INTEGRATED CIRCUITS.** We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

**METRICATION CHARTS** now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

## LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16½p each } Now new low  
16 pin type at 18p each } profile type

## BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines: **B.P.I. Transistor Equivalents and Substitutes:** 40p

This includes many thousands of British, U.S.A., European and C.V. equivalents.

**The I1116 Radio Valve & Transistor Data Book 9th Edition: P & P 23½p** 75p

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of publications.

N.B.—Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME.....

ADDRESS.....

ALL PRICES INCLUDE 10% V.A.T.

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

# BI-PRE-PAK LTD

Co. Reg No. 820919

DEPT. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX

TELEPHONE: SOUTHEND (0702) 46344

# A DEXTER DIMMASWITCH

ALLOWS COMPLETE



LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression. 600 watt £3.52 Kit form £2.97 300 watt £2.97 Kit form £2.42

All plus 12p post and packing

Prices include VAT. Please send c.w.o. to:

## DEXTER & COMPANY

1 ULVER HOUSE  
19 KING STREET  
CHESTER CH1 2AH  
Tel: 0244-25883

AS SUPPLIED  
TO H.M. GOVERNMENT  
DEPARTMENTS, HOSPITALS,  
LOCAL AUTHORITIES,  
ETC.

### EX COMPUTER PC PANELS

2 x 4in packed with semiconductors and top quality resistors, capacitors, diodes, etc. Guaranteed min. 35 transistors plus data. 10 boards 50p (9p).

### SPECIAL BARGAIN PACK

25 boards £1 (25p). Panels with 4 power transistors sim OC28 50p (9p).

### ELECTROLYTICS

68,000µ 16V, 4½ x 2in dia. 25,000µ 25V, 20,000µ 30V, 5,000µ 90V, 35,000µ 15V, 8,000µ 55V, 4½ x 3in dia. 50p (15p). 15,000µ 15V, 10,000µ 35V, 4½ x 2in dia. 30p (10p). 2,000µ 25V wire ends 15p (5p), 12 for £1-50 (15p).

### 20A DIODES

4 for £1 (7p)

### 3A DIODES

4 for 50p (5p)

### 8 BLACK TOGGLES dpst 50p (8p).

### 250 MIXED CAPACITORS

60p (8p)

### 250 MIXED RESISTORS

60p (8p)

### 150 HI-STAB RESISTORS

60p (8p)

### 200 SI PLANAR DIODES

50p (5p)

### UNTESTED

### SUB-MIN. CO-AX. PLUGS

4 pairs 50p (5p)

### & SKTS.

10 for 50p (5p)

### REED RELAYS, MIXED

8 for 50p (8p)

### MICRO SWITCHES

8 for £1 (12p)

### ASSORTED RELAYS

12 for 50p (5p)

### MIN. GLASS NEONS

10 for 55p (5p)

### 10 WAY TERMINAL BLOCKS

50p (5p)

### QH BULBS 12V 55W

100 cfm 4½ x 2in. £3-50 (28p)

### PAPST EXTRACTOR/BLOWER FANS

Postage and package shown in brackets. Please add 10% VAT to prices.

## KEYTRONICS


(Mail Order only)

44 EARLS COURT ROAD  
LONDON W8

01-478 8499

## INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!  
HANDY!  
TIDY!

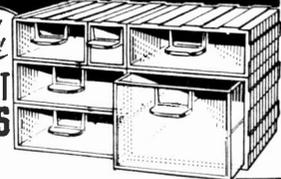

DISCOUNT PRICES

Newest, neatest system ever

designed for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

### BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins). £1-25 DOZEN.

DOUBLE UNITS (2D) (5ins 4½ins x 2½ins). £2-10 DOZEN.

TREBLE (3D) £2-20 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £3-25 for 8, EXTRA LARGE SIZE (6D1) £3-10 for 8.

### PLUS QUANTITY DISCOUNTS!

Orders £6 and over DEDUCT 5% in the £. Orders £10 and over DEDUCT 7½% in the £. Orders £20 and over DEDUCT 10% in the £.

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES

Please add 10% V.A.T. to total remittance

**IVORYET LIMITED**

(Dept. PE8) 124 Cricklewood  
Broadway, London, N.W.2  
Tel. 01-450 4844

# Collect Wireless World Circards. And build a valuable dossier on circuit design.



Circards is a new and comprehensive system, launched by Wireless World, to provide professional engineers and enthusiasts with valuable up-to-the-minute data on circuit design. Data not available from any other single source.

Circard sets come in wallets and cost £1 (£1.15 overseas) per set. A subscription to Nos. 6-15 costs £9 (£10.50 overseas) - sets published monthly.

Start your personal dossier on circuit design by completing and returning the coupon below.

Subjects already covered by Circard.

1. Basic Active Filters.
2. Switching circuits: Comparators and Schmitts.
3. Waveform Generators.
4. AV Measurements.
5. Audio Circuits: preamplifiers, mixers, filters and tone controls.

Subjects to be published during the year.

6. Power Amplifiers.
7. Constant Current circuits.
8. Opto-electronics.
9. Basic Logic Gate circuits.
10. Astables.
11. Micropower circuits.
12. Wideband Amplifiers.
13. Alarm circuits.
14. Pulse Modulators.
15. Digital counters.

To: J. Rider, Wireless World, IPC Business Press Limited, Sundry Sales Dept, 33 Bowling Green Lane, London, EC1R 0NE.

Please send me set no(s) ..... @ £1 (£1.15 o/s) each  \*

I wish to subscribe to set Nos. 6-15 @ £9 (£10.50 o/s)  \*

I enclose cheque/money order for £.....  \*

\*Tick as required


Name .....

Address .....

Company registered in England. Registered office: Dorset House, Stamford Street, London SE1 9LU. Registered No: 677128
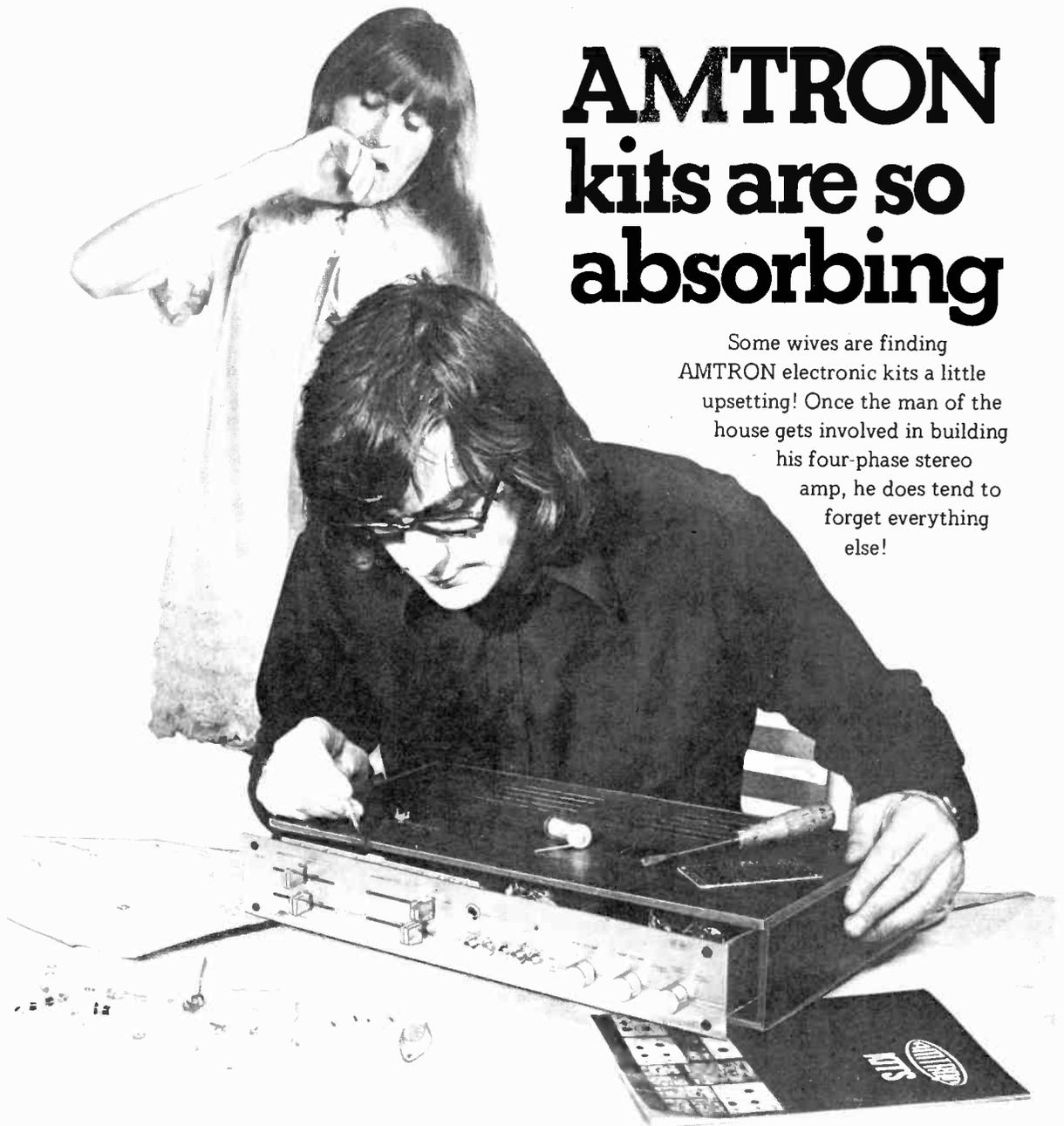
# AMTRON kits are so absorbing

Some wives are finding AMTRON electronic kits a little upsetting! Once the man of the house gets involved in building his four-phase stereo amp, he does tend to forget everything else!



AMTRON produce a varied range of 200 electronic kits which include Power supplies; L.F. instruments; tuners; receivers and I.C. digital equipment.

Kits are sold in attractive blister packs which contain solder and full instructions.

Prices range from £1.10 to £80.

Next time the "little lady" starts to complain, try buying her a kit, and before you know it she'll be an AMTRON enthusiast too.

Contact your local stockist



Trade & Education enquiries welcome

AMTRON U.K. LTD. 4 & 7 CASTLE STREET, HASTINGS, SUSSEX. TEL: HASTINGS 2875

# TO SPARK YOUR IMAGINATION!

Kit comprises **EVERYTHING** Case, cables, coil connectors, Silicon grease, 8-page instruction leaflet.



## the SPARKRITE

### Electronic Ignition Kit only £9.35

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance. • Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed. • Suitable for all engines up to 8 cyls. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gunton Ignition. Price: £9.35 inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth) Ready built unit also available £11.55 inc. V.A.T. and postage. GUARANTEED 5 YEARS.

**ORDER NOW** To: ELECTRONICS DESIGN ASSOCIATES,  
82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £9.35. Or for ready built unit £11.55.

NAME

ADDRESS

(Live near Walsall? Call in for an actual workshop demo. It really is convincing)

PE8

# SPA RADIO

335-337 HIGH STREET, CHELTENHAM  
GLOUCESTER. Tel 54303

Please Note: Add 10% V.A.T. to order total including post, packing and insurance. All goods new and manufacturer guaranteed. Post, packing and insurance in brackets

- Spatronic PB8C Mains 8 Track Cartridge Playback Unit. B.S.R. chassis, encased and wired to feed existing stereo system. £11 (45p).
- B.S.R. T145 Unit. As above but chassis only (wired). £8-55 (40p).
- B.S.R. C114 Mini-changer fitted X54 Comp. Cartridge. Unit fitted with 18V overwind on motor for mono amplifier. £3-90 (30p).
- B.S.R. Model MP60 Single Play Turntable Unit (chassis). £8-50 (70p).
- B.S.R. Model MP60. As above but fitted G800 Mag. Cartridge. £11-50 (75p).
- Many bargain B.S.R. Auto Units for callers only at £5 to £8 plus V.A.T.
- Garrard SP25 Mk 3 Single Play Turntable Unit (chassis). £10-25 (75p).
- Garrard SP25 Mk 3 fitted plinth and cover. wired ready to play. £18-75 (55p).
- Garrard 2025 T/C fitted KS40A Cer. Stereo Cartridge (chassis). £7-65 (75p).
- Spatronic P1 Plinth/Base. Solid Alformosa for above decks. £2-10 (30p).
- Spatronic C1 Cover to fit above plinth (most are fitted). £1 (30p).
- Garrard AP76 Single Play Trans. Turntable (chassis). £19-50 (95p).
- Garrard Zero 100S Single Play Trans. Turntable (chassis). £34-50 (£1 20).
- Spatronic P2 Plinth/Base. Solid Alformosa for above decks. £3 (35p).
- Spatronic C2 Cover to fit above plinth (most are clear). £1-90 (35p).
- Spatronic E2 Equipment Cabinet designed for the B.S.R. C114 Mini-player. To house either a Mono Player or the Mullard Unix. Ask for leaflet. Systems on permanent demonstration here.
- Mullard Unix Stereo Modules and Control Panel (complete). £11-30 (75p).
- Acos GP93.1 Stereo Crystal Cartridge. Exc. many amplifiers. £1-30 (50p).
- B.S.R. SC5 high quality Ceramic Cart. Perfect for Unix. Dulci and many other ceramic input amplifiers. £1-75 (6p).
- Goldring G800 Magnetic Cartridge (very special offer). £3-90 (75p).
- Jap NM55 Sin Cer. Magnet Speaker. Perfect for cassette ext. 8 ohm. £1-10 (10p).
- Electro-Acoustic 8RM 8in Cer. Magnet Speaker. State 8 or 15 ohm. Also Single or Dual Cone. Single. £1-90; Dual. £2-15 (25p).
- Electro-Acoustic 10RM Cer. Magnet Speaker. State 8 or 15 ohm. Also Single or Dual Cone. Single. £2-25; Dual. £2-55 (28p).
- Celestion PS127/C 12in Dual Cone 20W Unit for hi-fi or good quality P.A. or Discotheque. Many cabinets for callers. £8 (85p).
- Goodmans 12F Disco/P.A. Speaker. 8 and 15 ohm heavy duty. £10-50 (65p).
- Dulci Model 207.7 + 7W R.M.S. Stereo Amplifier. £15-90 (60p).
- Kyoto Model S2000 10 + 10W R.M.S. Stereo Amplifier. £23-90 (75p).
- Keletron KSA700 7 + 7W R.M.S. Stereo Amplifier. £22 (70p).
- Keletron KSA1500 15 + 15W R.M.S. Stereo Amplifier. £29 (90p).
- Keletron KS4 Two Speaker System. 4W R.M.S. 8W music. Size H. 11in. W. 6in. D. 6in. Freq. response 70-15,000Hz. Each £7-30 (75p).
- Keletron KS6 Three Speaker System. 6W R.M.S. 12W music. Size H. 15in. W. 8in. D. 7in. Freq. Response 60-19,000Hz. £9 (65p).
- Keletron KS8 Three-Speaker System. 8W R.M.S. 16W music. Size H. 19in. W. 10in. D. 9in. Freq. response 40-19,000Hz. £11-75 (95p).

## WINDSCREEN WIPER DELAY KIT

Complete kit of parts including drilled and tinned fibreglass printed circuit board.

The unit provides intermittent wiper operation with a delay up to approximately 60 seconds which can be varied to optimise visibility in conditions of light rain, spray, etc. The original wiper switch overrides when normal operation is required.

Suitable for most British cars

£2.86 inc. V.A.T. and P.&P.

ESSEX X-RAY CO. LTD.

Cash with order

57 THEYDON PARK RD.

THEYDON BOIS, EPPING, ESSEX CM16 7LR

## LIQUID WHEEL AND CASSETTE PROJECTORS



Specially designed for discotheque lighting this machine uses a 300 watt power cooled bulb that has a two-position intensity switch combined with a long lamp life protection circuit. An image up to 20ft across can be projected in a darkened room at a distance of 35ft. Cassette machine (illustrated) will take a range of cassettes including moire patterns. The liquid wheel machine will only accept liquid or crystal wheels but gives a more vivid effect.

Price (cash with order) liquid wheel projector £33.95; cassette projector £36.95. Supplied complete with one effect post free.

**M.V. AMPLIFICATIONS**  
ORCHARD MEADOW, UFFINGTON ROAD, STAMFORD, Lincs.

# THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

## BRAND NEW FULLY GUARANTEED DEVICES

AC107	0-82	AD162	0-37	BC148	0-11	BD137	0-50	BF188	0-44	OC19	0-39	2G371	0-18	2N2219	0-22	2N3054	0-51	2N4059	0-11
AC113	0-22	AD161	0-37	BC149	0-13	BD138	0-55	BF194	0-13	OC20	0-70	2G371B	0-13	2N2220	0-24	2N3055	0-55	2N4060	0-13
AC115	0-28	AD162(AMP)	0-81	BC150	0-22	BD139	0-61	BF195	0-13	OC22	0-42	2G373	0-18	2N2221	0-22	2N3056	0-16	2N4061	0-13
AC122	0-13	ADT140	0-55	BC152	0-19	BD155	0-88	BF197	0-16	OC24	0-82	2G377	0-18	2N2222	0-22	2N3059A	0-18	2N4062	0-13
AC125	0-19	AF114	0-27	BC153	0-31	BD175	0-66	BF200	0-50	OC25	0-42	2G378	0-13	2N2269	0-16	2N3393	0-16	2N4285	0-19
AC126	0-19	AF115	0-27	BC154	0-33	BD176	0-66	BF222	1-05	OC26	0-28	2G381	0-18	2N2369A	0-16	2N3394	0-16	2N4286	0-19
AC127	0-19	AF116	0-27	BC157	0-20	BD177	0-72	BF257	0-50	OC28	0-55	2G382	0-18	2N2411	0-27	2N3395	0-19	2N4287	0-19
AC128	0-19	AF117	0-27	BC158	0-13	BD178	0-72	BF258	0-66	OC29	0-55	2G401	0-33	2N2412	0-27	2N3402	0-23	2N4288	0-19
AC132	0-16	AF118	0-27	BC159	0-13	BD179	0-77	BF259	0-84	OC36	0-46	2G414	0-33	2N2646	0-52	2N3403	0-23	2N4289	0-19
AC134	0-16	AF124	0-33	BC160	0-50	BD180	0-77	BF262	0-23	OC37	0-14	2G417	0-23	2N2711	0-23	2N3404	0-31	2N4290	0-19
AC137	0-16	AF125	0-28	BC161	0-55	BD185	0-72	BF263	0-61	OC41	0-22	2N389	0-39	2N2712	0-23	2N3405	0-46	2N4291	0-19
AC141	0-16	AF126	0-31	BC167	0-13	BD186	0-72	BF270	0-39	OC42	0-27	2N388A	0-61	2N2714	0-23	2N3414	0-17	2N4292	0-19
AC141K	0-19	AF127	0-31	BC168	0-13	BD187	0-77	BF271	0-33	OC44	0-17	2N404	0-22	2N2904	0-19	2N3415	0-17	2N4293	0-19
AC142	0-16	AF139	0-33	BC169	0-13	BD188	0-77	BF272	0-88	OC45	0-14	2N404A	0-31	2N2904A	0-23	2N3416	0-31	2N5172	0-13
AC142K	0-19	AF178	0-33	BC170	0-13	BD189	0-88	BF273	0-39	OC70	0-11	2N524	0-44	2N2905	0-23	2N3417	0-31	2N5457	0-35
AC151	0-17	AF179	0-55	BC171	0-16	BD190	0-83	BF274	0-39	OC71	0-11	2N527	0-44	2N2905A	0-23	2N3425	0-83	2N5458	0-35
AC154	0-22	AF180	0-55	BC172	0-16	BD195	0-94	BF286	0-42	OC72	0-14	2N598	0-48	2N2906	0-17	2N3646	0-10	2N5459	0-44
AC155	0-22	AF181	0-50	BC173	0-16	BD196	0-94	BF289	0-30	OC74	0-18	2N599	0-50	2N2906A	0-23	2N3647	0-11	2N5460	0-44
AC156	0-22	AF186	0-50	BC174	0-16	BD197	0-99	BF284	0-24	OC75	0-17	2N606	0-14	2N2907	0-22	2N3703	0-11	2N5461	0-46
AC157	0-27	AF129	0-41	BC175	0-24	BD198	0-99	BF285	0-33	OC76	0-17	2N607	0-15	2N2907A	0-24	2N3704	0-12	2N5462	0-46
AC165	0-22	AF192	0-72	BC177	0-21	BD199	1-05	BF286	0-24	OC77	0-28	2N608	0-27	2N2923	0-16	2N3705	0-11	2N5463	0-61
AC166	0-22	AF193	0-72	BC178	0-21	BD200	1-05	BF287	0-27	OC81	0-17	2N609	0-39	2N2924	0-16	2N3706	0-10	2N5464	0-77
AC167	0-22	AF226	0-28	BC179	0-21	BD205	0-88	BF288	0-24	OC81D	0-17	2N609	0-39	2N2925	0-16	2N3707	0-12	2N5465	0-83
AC168	0-27	AF227	0-33	BC180	0-27	BD206	0-88	BF290	0-22	OC82	0-17	2N706A	0-10	2N2926	(G)	2N3708	0-08	2N5466	0-83
AC169	0-16	AF228	0-28	BC181	0-27	BD207	1-05	BF291	0-22	OC82D	0-17	2N708	0-13	2N2926	(Y)	2N3709	0-14	2N5467	0-83
AC176	0-22	AF229	0-28	BC182	0-11	BD208	1-05	BF292	0-22	OC83	0-22	2N711	0-33	2N2926	(Y)	2N3710	0-10	2N5468	0-82
AC177	0-27	AF230	0-28	BC182L	0-11	BDY20	1-10	BF293	0-19	OC84	0-22	2N717	0-39	2N2926	(Y)	2N3711	0-10	2N5469	0-82
AC178	0-31	AF231	0-28	BC183	0-11	BDY15	0-22	BF294	0-54	OC89	0-22	2N718	0-27	2N2926	(O)	2N3819	0-31	2N5470	0-46
AC179	0-31	AF232	0-28	BC183L	0-11	BDY17	0-50	BF295	0-17	OC140	0-22	2N718A	0-55	2N2926	(O)	2N3820	0-55	2N5471	0-62
AC180	0-19	AF233	0-28	BC184	0-13	BDY18	0-77	BF296	0-17	OC169	0-28	2N726	0-31	2N2926	(R)	2N3821	0-39	2N5472	0-77
AC180K	0-22	AF234	0-28	BC184L	0-13	BDY19	0-77	BF297	0-17	OC170	0-28	2N727	0-31	2N2926	(R)	2N3822	0-31	2N5473	0-77
AC181	0-16	AF235	0-28	BC185	0-13	BDY21	0-50	BF298	0-17	OC171	0-28	2N744	0-22	2N2926	(H)	2N3823	0-33	2N5474	0-77
AC181K	0-22	AF236	0-28	BC187	0-31	BDY22	0-50	BF299	0-17	OC200	0-28	2N744	0-22	2N2926	(H)	2N3824	0-33	2N5475	0-77
AC187	0-24	AF237	0-28	BC207	0-12	BDY23	0-50	BF300	0-17	OC201	0-31	2N914	0-18	2N3010	0-77	2N3905	0-31	2N5476	0-46
AC187K	0-22	AF238	0-24	BC208	0-12	BDY24	0-55	BF301	0-17	OC202	0-31	2N918	0-33	2N3011	0-16	2N3906	0-30	2N5477	0-46
AC188	0-24	AF239	0-10	BC209	0-13	BDY25	0-61	BF302	0-20	OC203	0-28	2N929	0-23	2N3053	0-19	2N4058	0-13	2N5478	0-50
AC188K	0-22	AF240	0-10	BC212L	0-12	BDY26	0-50	BF303	0-20	OC204	0-28	2N930	0-23						
AC197	0-22	AF241	0-11	BC213L	0-12	BDY27	0-77	BF304	0-20	OC205	0-39	2N1131	0-22						
AC198	0-22	AF242	0-11	BC214L	0-12	BDY28	0-77	BF305	0-20	OC206	0-39	2N1132	0-24						
AC198K	0-22	AF243	0-11	BC215L	0-12	BDY29	0-77	BF306	0-20	OC207	0-39	2N1133	0-24						
AC199	0-39	AF244	0-13	BC216L	0-12	BDY30	0-77	BF307	0-20	OC208	0-39	2N1134	0-24						
AC200	0-39	AF245	0-13	BC217L	0-12	BDY31	0-77	BF308	0-20	OC209	0-39	2N1135	0-24						
AC201	0-39	AF246	0-13	BC218L	0-12	BDY32	0-77	BF309	0-20	OC210	0-39	2N1136	0-24						
AC202	0-39	AF247	0-13	BC219L	0-12	BDY33	0-77	BF310	0-20	OC211	0-39	2N1137	0-24						
AC203	0-39	AF248	0-13	BC220L	0-12	BDY34	0-77	BF311	0-20	OC212	0-39	2N1138	0-24						
AC204	0-39	AF249	0-13	BC221L	0-12	BDY35	0-77	BF312	0-20	OC213	0-39	2N1139	0-24						
AD130	0-42	BC140	0-33	BD124	0-66	BF180	0-33	MP101	0-41	2G345	0-18	2N2218	0-22	AA119	0-09	BY133	0-23	OA10	0-39
AD140	0-53	BC141	0-33	BD131	0-55	BF181	0-33	MP102	0-46	2G346	0-18	2N2218	0-22	AA120	0-09	BY164	0-55	OA47	0-08
AD142	0-53	BC142	0-33	BD132	0-66	BF182	0-44	MP103	0-41	2G347	0-18	2N2218	0-22	AA129	0-09	BYX38/30	0-70	OA70	0-08
AD143	0-42	BC143	0-33	BD133	0-72	BF183	0-44	MP104	0-41	2G348	0-18	2N2218	0-22	AA130	0-10	BYX38/30	0-70	OA70	0-08
AD149	0-53	BC145	0-50	BD135	0-44	BF184	0-28	MP105	0-41	2G349	0-18	2N2218	0-22	AA131	0-10	BYX38/30	0-70	OA70	0-08
AD161	0-37	BC147	0-11	BD136	0-44	BF185	0-33	MP106	0-41	2G350	0-18	2N2218	0-22	AA132	0-10	BYX38/30	0-70	OA70	0-08

### DIODES AND RECTIFIERS

AA119	0-09	BY133	0-23	OA10	0-39
AA120	0-09	BY164	0-55	OA47	0-08
AA129	0-09	BYX38/30	0-70	OA70	0-08
AA130	0-10	BYX38/30	0-70	OA70	0-08
AA131	0-10	BYZ10	0-39	OA81	0-08
AA132	0-11	BYZ11	0-33	OA85	0-10
AA133	0-11	BYZ12	0-33	OA90	0-07
AA134	0-11	BYZ13	0-28	OA91	0-07
AA135	0-11	BYZ14	0-44	OA95	0-08
AA136	0-11	BYZ15	0-39	OA200	0-07
AA137	0-11	BYZ16	0-39	OA202	0-08
AA138	0-11	BYZ17	0-39	OA207	0-07
AA139	0-11	BYZ18	0-39	OA210	0-08
AA140	0-11	BYZ19	0-31	OA219	0-06
AA141	0-11	BYZ20	0-31	OA219	0-06
AA142	0-11	BYZ21	0-31	OA219	0-06
AA143	0-11	BYZ22	0-31	OA219	0-06
AA144	0-11	BYZ23	0-31	OA219	0-06
AA145	0-11	BYZ24	0-31	OA219	0-06
AA146	0-11	BYZ25	0-31	OA219	0-06
AA147	0-11	BYZ26	0-31	OA219	0-06
AA148	0-11	BYZ27	0-31	OA219	0-06
AA149	0-11	BYZ28	0-31	OA219	0-06
AA150	0-11	BYZ29	0-31	OA219	0-06
AA151	0-11	BYZ30	0-31	OA219	0-06
AA152	0-11	BYZ31	0-31	OA219	0-06
AA153	0-11	BYZ32	0-31	OA219	0-06
AA154	0-11	BYZ33	0-31	OA219	0-06
AA155	0-11	BYZ34	0-31	OA219	0-06
AA156	0-11	BYZ35	0-31	OA219	0-06
AA157	0-11	BYZ36	0-31	OA219	0-06
AA158	0-11	BYZ37	0-31	OA219	0-06
AA159	0-11	BYZ38	0-31	OA219	0-06
AA160	0-11	BYZ39	0-31	OA219	0-06
AA161	0-11	BYZ40	0-31	OA219	0-06
AA162	0-11	BYZ41	0-31	OA219	0-06
AA163	0-11	BYZ42	0-31	OA219	0-06
AA164	0-11	BYZ43	0-31	OA219	0-06
AA165	0-11	BYZ44	0-31	OA219	0-06

# The largest selection

## NEW LOW PRICED TESTED S.C.R.'S

	PIV				
	50	100	200	400	800
1A TO5	2p	2p	2p	2p	2p
3A TO66	0-28	0-28	0-34	0-48	0-50
5A TO66	0-34	0-52	0-54	0-62	0-75
5A TO64	0-34	0-52	0-54	0-62	0-75
7A TO48	0-52	0-55	0-63	0-74	0-85
10A TO48	0-56	0-64	0-87	0-83	1-07
16A TO48	0-59	0-70	0-83	1-03	1-38
30A TO48	1-27	1-54	1-76	1-83	4-40

## SIL. RECTS. TESTED

PIV	300mA		1.5A		3A		10A		30A	
	DO7	8016	1A1C	RO16	SO10	SO10	SO32A	8032A	8032A	8032A
50	0-04	0-06	0-08	0-08	0-16	0-23	0-66			
100	0-04	0-07	0-06	0-15	0-18	0-28	0-85			
200	0-06	0-10	0-07	0-16	0-22	0-27	1-10			
400	0-07	0-15	0-08	0-22	0-30	0-41	1-38			
600	0-08	0-18	0-11	0-26	0-38	0-50	2-05			
800	0-11	0-19	0-12	0-28	0-41	0-61	2-20			
1000	0-12	0-30	0-16	0-33	0-51	0-70	2-75			
1200		0-37		0-42	0-63	0-83				

V.BOM.	2A		10A	
	TO-18	TO-18	TO-18	TO-18
100V	33	55	85	
200V	55	85	99	
400V	77	83	1-21	

FOR TRIACS	DIACS		WITTH	
	BR100	(D32)	41p	each

## FREE

One 50p Pak of your own choice free with orders valued \$4 or over.

**BRAND NEW TEXAS GERM. TRANSISTORS**  
Coded and Guaranteed

Pak No.	QNT
T1	8 2G3713 OC71
T2	8 1D1374 OC75
T3	8 1D1216 OC81D
T4	8 2G381T OC81
T5	8 2G382T OC82
T6	8 2G344B OC44
T7	8 2G345B OC45
T8	8 2G378 OC78
T9	8 2G399A 2N1302
T10	8 2G417 AF117

All 55p each pak

**2N2060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS.** Our price 28p each.

**120 VCB NIXIE DRIVER TRANSISTOR.** 2N1893 FULLY TESTED AND CODED N.D. 1-24 18p each. TO-5 N.P.N. 25 up 17p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18. Eqt. ZTX300 8p each. Any QTY.

## POWER TRANS BONANZA!

**GENERAL PURPOSE GERM. PNP**  
Coded G.P100. BRAND NEW TO-3 CASE. POSS. REPLACE—OC25-28-29-30-35-36. NKT 401-403-404-405-406-430-451-452-453. T13027-3028, 2N260A, 2N466A-457A-458A, 2N811 A & B. 2P-220-222, ETC. V.CBO 80V V.CEO 50V IC 10A PT. 30 WATTS Hie 30-170.  
PRICE 1-24 47p each 25-99 44p each 100 up 40p each

**SILICON High Voltage 260V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded R 2400 V.CBO 250V V.CEO 100IC 6A/30 Watts. HFE type 20/T 5MHZ. OUR PRICE EACH: 1-24 55p 25-99 50p 100 up 44p**

**ADI61/162 PNP M.P. COMP GERM TRANS. OUR LOWEST PRICE OF 80p PER PAIR**

## KING OF THE PAKS Unequalled Value and Quality

### SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-55
U 2	60 Mixed Germanium Transistors AF/PF	0-55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-55
U 4	40 Germanium Transistors like OC81, AC128	0-55
U 5	60 200mA Sub-Min. Silicon Diodes	0-55
U 6	30 Sil. Planar Trans. NPN like BSY95A, 2N706	0-55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0-55
U 8	50 Sil. Planar Diodes DO-7 Glass 230mA like OA200/202	0-55
U 9	26 Mixed Voltages, 1 Watt Zener Diodes	0-55
U 10	20 BA Y <sup>2</sup> 0 charge storage Diodes DO-7 Glass	0-55
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0-55
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0-55
U13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0-55
U14	150 Mixed Silicon and Germanium Diodes	0-55
U15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0-55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-55
U18	8 6 Amp Silicon Rectifiers BYZ13 Type up to 600 PIV	0-55
U19	25 Silicon NPN Transistors like IC108	0-55
U20	12 1/2 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-55
U21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0-55
U22	30 MDT's like M1Z Series PNP Transistors	0-55
U23	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	0-55
U24	25 300MHz NPN Silicon Transistors 2N708, HSY27	0-55
U25	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-55
U26	12 NPN Germanium AF Transistors TO-1 like AC127	0-50
U29	10 1 Amp SCR's TO-5 can, up to 600 PIV CR81/25-600	1-15
U30	13 Plastic Silicon Planar Trans. NPN 2N2926	0-55
U31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3207	0-55
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0-55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-55
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 28302/4	0-55
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-55
U36	25 Silicon Alloy NPN Transistors TO-5 BFY50/51/52	0-55
U37	30 Silicon Alloy Transistors 80-2 PNP OC200, 28322	0-55
U38	20 Fast Switching Silicon Trans. NPN 400MHz 2N3011	0-55
U39	30 R.F. Germ. PNP Transistors 2N1303/5 TO-5	0-55
U40	10 Dual Transistors 6 lead TO-5 2N2060	0-55
U41	25 RF Germanium Transistors TO-5, OC45, NKT72	0-55
U42	10 VHF Germanium PNP Transistors 2N1302/5 AF117	0-55
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0-55
U44	20 Sil. Trans. Plastic TO-5 BC115/NPN	0-55
U45	7 3A SCR. TO-6 up to 600PIV	1-10

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

**SILICON PHOTO TRANSISTOR.** TO-18 Lens end NPN Sim. to BP x 25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 80p 44p 38p

## F.E.T.'S

2N3810	31p	2N5458	35p
2N3820	55p	2N5459	44p
2N3821	34p	BFW10	66p
2N3823	31p	MFP105	41p

## NEW 6TH EDITION

**TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 99p each.

**A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.**

**SILICON 50 WATTS MATCHED NPN/PNP BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new. V.CBO 100V V.CEO 50IC 10A. HFE type 100/T 3mHZ. OUR PRICE PER PAIR: 1-24 pra: 86p 25-99 pra: 61p 100 pra: 55p**

## QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q 1	20 Red spot transistors pnp	0-55
Q 2	16 White spot R.F. transistors pnp	0-55
Q 3	4 OC71 type transistors	0-55
Q 4	6 Matched transistors OC44/45/81/81D	0-55
Q 5	4 OC75 transistors	0-55
Q 6	5 OC72 transistors	0-55
Q 7	4 AC128 transistors pnp high gain	0-55
Q 8	4 AC126 transistors pnp	0-55
Q 9	7 OC81 type transistors	0-55
Q 10	7 OC71 type transistors	0-55
Q11	2 AC127/128 Complementary pairs	0-55
Q12	3 AF116 type transistors	0-55
Q13	3 AF117 type transistors	0-55
Q14	3 OC171 H.F. type transistors	0-55
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0-55
Q16	2 GE7880 low noise Germanium transistors	0-55
Q17	5 npn 2 x ST.141 & 3 x ST.140	0-55
Q18	4 MADT*82 x MAT 100 & 2 x MAT 120	0-55
Q19	3 MADT*82 x MAT 101 & 1 x MAT 121	0-55
Q20	4 OC4 (Germanium transistors A.F.)	0-55
Q21	4 AC127 npn Germanium transistors	0-55
Q22	20 NKT transistors A.F. R.F. coded	0-55
Q23	10 OA202 Silicon diodes sub-min.	0-55
Q24	8 OA81 diodes	0-55
Q25	15 IN914 Silicon diodes 75PIV 75mA	0-55
Q26	8 OA85 Germanium diodes sub-min IN89	0-55
Q27	2 10A 600 PIV Silicon rectifiers 18425R	0-55
Q28	2 Silicon power rectifiers BYZ13	0-55
Q29	4 Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0-55
Q30	7 Silicon switch transistors 2N706 npn	0-55
Q31	6 Silicon switch transistors 2N708, npn	0-55
Q32	3 pnp Silicon transistors 2 x 2N1131, 1 x 2N1132	0-55
Q33	3 Silicon npn transistors 2N1711	0-55
Q34	7 Silicon npn transistors 2N2369, 300MHz code (P397)	0-55
Q35	3 Silicon pnp TO-5, 2 x 2N2904 & 1 x 2N2905	0-55
Q36	7 2N3646 TO-18 plastic 300MHz npn	0-55
Q37	3 2N3053 npn Silicon transistors	0-55
Q38	7 pnp transistors 4 x 2N3703, 3 x 2N3702	0-55

## ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify electronic calculations features the following scales:— Conversion of Frequency and Wavelength. Calculation of L, C and f of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and "e" Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 2cm x 4cm. Complete with case and instructions. Price each: £3-69

## INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	= 12 x 7400	0-55	UIC44	= 5 x 7446	0-55	UIC86	= 5 x 7485	0-55
UIC01	= 12 x 7401	0-55	UIC45	= 5 x 7447	0-55	UIC90	= 5 x 7490	0-55
UIC02	= 12 x 7402	0-55	UIC46	= 5 x 7448	0-55	UIC91	= 5 x 7491	0-55
UIC03	= 12 x 7403	0-55	UIC47	= 12 x 7450	0-55	UIC92	= 5 x 7492	0-55
UIC04	= 12 x 7404	0-55	UIC51	= 12 x 7451	0-55	UIC93	= 5 x 7493	0-55
UIC05	= 12 x 7405	0-55	UIC53	= 12 x 7453	0-55	UIC94	= 5 x 7494	0-55
UIC06	= 8 x 7406	0-55	UIC54	= 12 x 7454	0-55	UIC95	= 5 x 7495	0-55
UIC07	= 8 x 7407	0-55	UIC60	= 12 x 7460	0-55	UIC96	= 5 x 7496	0-55
UIC08	= 12 x 7410	0-55	UIC70	= 8 x 7470	0-55	UIC100	= 5 x 74100	0-55
UIC13	= 8 x 7413	0-55	UIC72	= 8 x 7472	0-55	UIC121	= 5 x 74121	0-55
UIC20	= 12 x 7420	0-55	UIC73	= 8 x 7473	0-55	UIC141	= 5 x 74141	0-55
UIC30	= 12 x 7430	0-55	UIC74	= 8 x 7474	0-55	UIC151	= 5 x 74151	0-55
UIC40	= 12 x 7440	0-55	UIC75	= 8 x 7475	0-55	UIC154	= 5 x 74154	0-55
UIC41	= 5 x 7441	0-55	UIC76	= 8 x 7476	0-55	UIC183	= 5 x 74183	0-55
UIC42	= 5 x 7442	0-55	UIC80	= 5 x 7480	0-55	UIC199	= 5 x 74199	0-55
UIC43	= 5 x 7443	0-55	UIC81	= 5 x 7481	0-55			
UIC44	= 5 x 7444	0-55	UIC82	= 5 x 7482	0-55			
UIC45	= 5 x 7445	0-55	UIC83	= 5 x 7483	0-55			

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

**BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES— 18 BALDOCK STREET (A10), WARE, HERTS. TEL. (STD 0920) 61593**

open MON.-SAT. 9.15 a.m. to 6 p.m., FRIDAY until 8 p.m.

All mail orders please add 10p post and packing. Send all orders to BI-PAK, P.O. BOX 6, WARE, HERTS.

# -the lowest prices!

## 74 Series T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS




1			25			100+		
SN7400	0-17	0-18	0-13	SN7486	0-35	0-34	100+	0-33
SN7401	0-17	0-18	0-13	SN7489	6-05	5-78	5-50	5-50
SN7402	0-17	0-18	0-13	SN7490	0-74	0-71	0-64	0-64
SN7403	0-17	0-18	0-13	SN7491	1-10	1-05	0-99	0-99
SN7404	0-17	0-18	0-13	SN7492	0-74	0-71	0-64	0-64
SN7405	0-17	0-18	0-13	SN7493	0-74	0-71	0-64	0-64
SN7406	0-38	0-34	0-31	SN7494	0-85	0-82	0-75	0-75
SN7407	0-39	0-35	0-31	SN7495	0-35	0-32	0-25	0-25
SN7408	0-20	0-14	0-18	SN7496	0-98	0-93	0-86	0-86
SN7409	0-20	0-19	0-18	SN74100	1-82	1-76	1-71	1-71
SN7410	0-17	0-18	0-13	SN74104	1-07	1-04	0-97	0-97
SN7411	0-28	0-24	0-28	SN74105	1-07	1-04	0-97	0-97
SN7412	0-39	0-34	0-31	SN74107	0-44	0-42	0-40	0-40
SN7413	0-32	0-29	0-27	SN74110	0-51	0-50	0-55	0-55
SN7414	0-48	0-45	0-42	SN74111	1-38	1-27	1-21	1-21
SN7417	0-48	0-44	0-42	SN74112	1-10	1-05	0-99	0-99
SN7420	0-17	0-18	0-13	SN74119	1-40	1-38	1-21	1-21
SN7422	0-55	0-53	0-50	SN74121	0-44	0-41	0-38	0-38
SN7423	0-55	0-53	0-50	SN74122	1-54	1-43	1-21	1-21
SN7425	0-55	0-53	0-50	SN74123	3-08	2-97	2-80	2-80
SN7426	0-50	0-46	0-44	SN74141	0-74	0-71	0-64	0-64
SN7427	0-50	0-46	0-44	SN74145	1-65	1-54	1-43	1-43
SN7428	0-77	0-72	0-68	SN74150	3-40	3-27	3-10	3-10
SN7430	0-17	0-18	0-13	SN74151	1-10	1-05	0-99	0-99
SN7432	0-50	0-46	0-44	SN74153	1-32	1-21	1-05	1-05
SN7433	0-88	0-83	0-77	SN74164	1-98	1-87	1-76	1-76
SN7437	0-71	0-68	0-66	SN74155	1-54	1-43	1-32	1-32
SN7438	0-71	0-68	0-66	SN74156	1-54	1-43	1-32	1-32
SN7440	0-17	0-18	0-13	SN74157	2-09	1-98	1-87	1-87
SN7441	0-74	0-71	0-68	SN74159	1-98	1-87	1-76	1-76
SN7442	0-74	0-71	0-68	SN74161	1-98	1-87	1-76	1-76
SN7443	1-43	1-38	1-32	SN74162	4-40	4-13	3-85	3-85
SN7444	1-43	1-38	1-32	SN74163	4-40	4-13	3-85	3-85
SN7445	1-98	1-95	1-93	SN74164	2-42	2-37	2-31	2-31
SN7446	1-07	1-04	0-97	SN74165	2-48	2-42	2-37	2-37
SN7447	1-10	1-07	1-05	SN74166	3-85	3-58	3-30	3-30
SN7448	1-10	1-07	1-05	SN74174	2-53	2-42	2-31	2-31
SN7450	0-17	0-18	0-13	SN74175	1-78	1-65	1-54	1-54
SN7451	0-17	0-18	0-13	SN74176	2-75	2-64	2-53	2-53
SN7453	0-17	0-18	0-13	SN74177	2-75	2-64	2-53	2-53
SN7454	0-17	0-18	0-13	SN74180	2-20	1-78	1-54	1-54
SN7460	0-17	0-18	0-13	SN74181	6-05	5-50	5-23	5-23
SN7470	0-32	0-29	0-27	SN74182	2-20	1-98	1-76	1-76
SN7472	0-32	0-29	0-27	SN74184	3-85	3-58	3-30	3-30
SN7473	0-41	0-39	0-35	SN74190	2-15	2-09	2-04	2-04
SN7474	0-41	0-39	0-35	SN74191	2-09	2-04	1-98	1-98
SN7475	0-50	0-48	0-46	SN74192	2-15	2-09	2-04	2-04
SN7476	0-44	0-43	0-43	SN74193	2-20	1-88	1-83	1-83
SN7480	0-74	0-71	0-64	SN74194	2-97	2-86	2-76	2-76
SN7481	1-32	1-27	1-21	SN74195	2-20	2-09	1-98	1-98
SN7482	0-98	0-95	0-94	SN74196	1-98	1-87	1-76	1-76
SN7483	1-21	1-18	1-05	SN74197	1-98	1-87	1-76	1-76
SN7484	1-10	1-05	0-99	SN74198	6-05	5-50	4-95	4-95
SN7485	3-98	3-85	3-74	SN74199	6-05	5-50	4-95	4-95

## BI-PAK DO IT AGAIN!

### 50W pk 25w (RMS)

0.1% DISTORTION!  
HI-FI AUDIO AMPLIFIER

### THE AL50

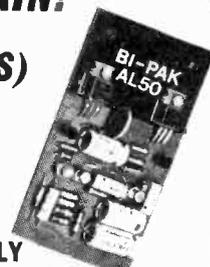

- \* Frequency Response 15Hz to 100,000—1dB. **ONLY £3.58 each**
- \* Load—3, 4, 8 or 16 ohms.
- \* Distortion—better than 0.1% at 1KHz.
- \* Signal to noise ratio 80dB.
- \* Supply voltage 10-35 Volts.
- \* Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT—TESTED—GUARANTEED.

### STABILISED POWER MODULE SPM80



AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 15 amps at 35 volts. Size: 68mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disc Systems, Public Address, Intercom Units, etc. Handbook available, 10p. **PRICE £3.25**

TRANSFORMER BMT80 £2.15 p. & p. 28p

### STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise PNP devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

#### SPECIFICATION

Frequency Response 20Hz - 20kHz ± 1dB  
 Harmonic Distortion better than 0.1%  
 Inputs: 1. Tape Head 1.25mV into 60KΩ  
 2. Radio, Tuner 35mV into 50KΩ  
 3. Magnetic P.U. 1.5mV into 50KΩ  
 All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB from 20Hz to 20kHz.  
 Base Control ± 15dB at 20Hz  
 Treble Control ± 15dB at 20kHz  
 Filters: Rumble (High Pass) 100Hz  
 Scratch (Low Pass) 8kHz  
 Signal/Noise Ratio better than -65dB  
 Input overload + 25dB  
 Supply + 35 volts at 20mA  
 Dimensions 292mm x 82mm x 35mm



**ONLY £13.15**

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE, HERTS

Postage and packing add 10p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

### LINEAR I.C.'s—FULL SPEC.

Type No.	Price	1-24	25-99	100+
BP201C—8L201C	0-70	0-59	0-50	
BP710C—8L701C	0-70	0-55	0-50	
BP702C—8L702C	0-70	0-65	0-50	
BP702—72702	0-59	0-60	0-44	
BP709—72709	0-40	0-39	0-33	
BP709P—μA709C	0-40	0-38	0-33	
BP710—72710	0-40	0-46	0-44	
BP711—μA711	0-40	0-48	0-44	
BP741—72741	0-55	0-50	0-45	
μA709C	0-31	0-29	0-27	
TAA263	0-77	0-68	0-61	
TAA293	0-99	0-83	0-77	
TAA350	1-87	1-74	1-65	
EA1000	2-80			

### ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C.'s

Type	Price	1-24	25-99	100 up
BP930	0-13	0-12	0-11	
BP932	0-14	0-13	0-12	
BP933	0-14	0-13	0-12	
BP935	0-14	0-13	0-12	
BP936	0-14	0-13	0-12	
BP944	0-14	0-13	0-12	
BP945	0-28	0-27	0-24	
BP946	0-13	0-12	0-11	
BP948	0-28	0-27	0-24	
BP951	0-72	0-66	0-61	
BP962	0-13	0-12	0-11	
BP9093	0-44	0-42	0-39	
BP9094	0-44	0-42	0-39	
BP9097	0-44	0-42	0-39	
BP9099	0-44	0-42	0-39	

### NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015P Minitron	All indicators 0-9 + Decimal point. All side viewing. Full data for all types available on request.
Anode Voltage (Vdc)	170min	175min	5	
Cathode Current (mA)	2-3	14	8	
Numerical Height (mm)	16	13	9	
Tube Height (mm)	47	32	22	
Tube Diameter (mm)	19	13	12 wide	
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47	
PRICE EACH	£1.87	£1.70	£1.50	

### RTL MICROLOGIC CIRCUITS

	Price each	1-24	25-99	100 up
Epoxy TO-5 case				
μL900 Buffer	38p	38p	29p	
μL914 Dual 21/p gate	38p	38p	29p	
μL923 J-K flip-flop	55p	51p	49p	
Date and Circuits Booklet for IC's	Price 8p.			

### DUAL IN LINE SOCKETS

	1-24	25-99	100+
(14 & 16 Lead)			
TS014	0-33	0-30	0-28
TS016 16 pin type	0-34	0-35	0-33
BP814 14 pin type (low cost)	0-17	0-15	0-12
BP816 16 pin type (low cost)	0-18	0-16	0-13

# CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT.  
No. 11  
MAYES RD.  
LONDON  
N22  
6TL

**COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR**  
OUR SHOPS ARE OPEN ALL DAY  
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY  
(WE CLOSE ALL DAY THURSDAY)  
13 SOUTH MALL, EDMONTON, N.9 803 1685

### "CRESCENT" BUBBLE LIGHT SHOW

A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour makes the music you produce more interesting and will appeal to the visual as well as the audio senses. This budget system compares very favourably with the more sophisticated and much higher priced models.

Specification: Projector: 150W, convection cooled, at 30ft the projected image = 18ft. Motor: 1 rev per 2 min. Liquid Wheel: 6in diameter multicolour. The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use, £15; 6in Liquid Wheel, £5 = £20 + 75p cart.

### TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2½in x 2½in x 3½in. Our Price £2.75 plus 10p P. & P. Same model suitably wired for the Philips Cassette £3 plus 10p P. & P.

### TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2½in. x 3½in. x 1½in. This converter supplies 6, 7½ or 9 volts and is transistor regulated. A real money saving device for £2.50 plus 10p P. & P.

### MINI LOUSPEAKERS

2½in 80 ohm, 50p; 2½in 40 ohm, 50p. Please include 5p P. & P. on each L.S.

### CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C90 28p, C90 38p, C120 48p plus 5p P. & P.

### PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) £18.50 plus 38p P. & P.

If you require more information please send S.A.E.

### DIGITAL CLOCK KIT

24-hr. Nixie dig. clock kit. We supply: a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. £22.50 + 50p P. & P. Please send S.A.E. if you require more information.

### AL20 5 WATT AUDIO AMPLIFIER

A low cost high quality 5 watt audio amplifier designed for use in stereo systems, record players and other audio equipment. Supply Voltage = 9 to 30 volts. Frequency = 50 to 25 kHz. Overall Size = 3in x 2½in x 1½in approx. Full technical data and diagrams with each module. All guaranteed and a bargain at £2.63 plus 5p P. & P.

V.A.T. From 1st April, 1973, will you please include on your Total (Goods plus Postage and Packing) Value Added Tax at the Standard Stated Rate.

### 200/250V MAINS RELAY

Heavy duty contacts. 2,500V coil. All new and unused D.P.D.T. mains relays 50p + V.A.T. Carr. Free. Special quantity price: £40 per 100 relays.

### MAINS TRANSFORMER

Fused Primary 240V. Secondary 220V @ 50mA. 6.3V @ 1A. This transformer is made to a very high standard and is a small size: 2in x 2½in x 2½in. 63p plus 15p P. & P.

### ADD

### LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL

Spec.: 5 Section Extended Length 100cm. Length under Fender 40cm. Cable Length 120cm. Supplied complete with Fixing Bracket and Control Switch. £6.75 plus 25p P. & P.

### LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high I.M.P. input this amplifier will work as a record player, baby alarm, etc., amplifier.

£1.75

plus 13p P. & P.

### EMI LOUSPEAKER 450

10W 13in x 8in ± two 2-2½in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp. £3.75 plus 38p P. & P. each.

### 7in x 4in LOUSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1.60. Free postage on this item.

New VAT EDITION

## Lasky's Audio-Tronics '73

# Lasky's Audio-Tronics Catalogue 1973

The new 1973 VAT edition of Lasky's famous Audio-Tronics Catalogue will be available in early April—FREE on request. The 48 tabloid size pages—many in full colour—have been reprinted with VAT price changes for your convenience, together with many new items. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape Recording and Audio Accessories. Send for your copy now and see for yourself that VAT can mean a saving on many of the 1000's of items we offer.

# FREE

Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME .....

ADDRESS .....

PE14

LASKY'S RADIO LIMITED, 3-15 CAVELL STREET, LONDON E.1.

## D.I.Y. TECHNICAL BOOKS

PAL RECEIVER SERVICING (280pp)	£3.50
MAKING AND REPAIRING TRANSISTOR RADIOS	£1.00
HOW TO REPAIR SMALL APPLIANCES	£1.20
TRANSISTOR RADIO SERVICING MADE EASY	£1.70
CAR RADIO SERVICING MADE EASY	£1.30
HI-FI PROJECTS FOR THE HOBBYIST	£1.00
TAPE RECORDING FOR THE HOBBYIST	£1.30
RADIO HANDBOOK (896 pp)	£6.00
ELECTRONIC EXPERIMENTS AND PROJECTS	£2.25
TRANSISTOR-TV SERVICING GUIDE	£1.25
99 WAYS TO IMPROVE YOUR HI-FI	£1.50
99 WAYS TO IMPROVE YOUR ELECT-PROJ.	£1.50
101 EASY HAM RADIO PROJECTS	£1.50
ELECTRONIC GAMES, TOYS YOU CAN BUILD	£1.40
HOW TO BUILD SPEAKER ENCLOSURES	£1.50
1-2-3-4 SERVICING STEREO AMPS.	£2.50
99 ELECTRONIC PROJECTS	£1.50
HANDBOOK OF BASIC ELECTRONIC EQUIPMENT	£1.75

Add 10% FOR POSTAGE AND PACKING

WHEEL (PE), 41A ADELAIDE GROVE, LONDON W12

## GET BETTER ALL-ROUND PERFORMANCE WITH DEXTER CAPACITOR DISCHARGE IGNITION



The Dexter Capacitor Discharge Ignition Unit can improve performance in many ways —

- ★ EASIER STARTING
- ★ REDUCED FUEL CONSUMPTION ★ BETTER ACCELERATION ★ HIGHER TOP SPEED ★ EXTENDED LIFE FOR BATTERY AND SPARK PLUGS
- ★ NO MORE CONTACT BREAKER POINT BURN ★ IMPROVED COMBUSTION ★

The Dexter Capacitor Discharge Ignition Unit is fully suppressed to prevent radio interference. It can be fitted easily and simply to your car, and costs only £9.80 plus 25p post and packing. 12 Volt neg. earth only. Fully guaranteed for 12 months


DEXTER & CO. 1 Ulver House  
19 King Street, Chester CH1 2AH. Tel. 0244 25883





**I.L.P.** (Electronics) Ltd

# 100 WATTS!

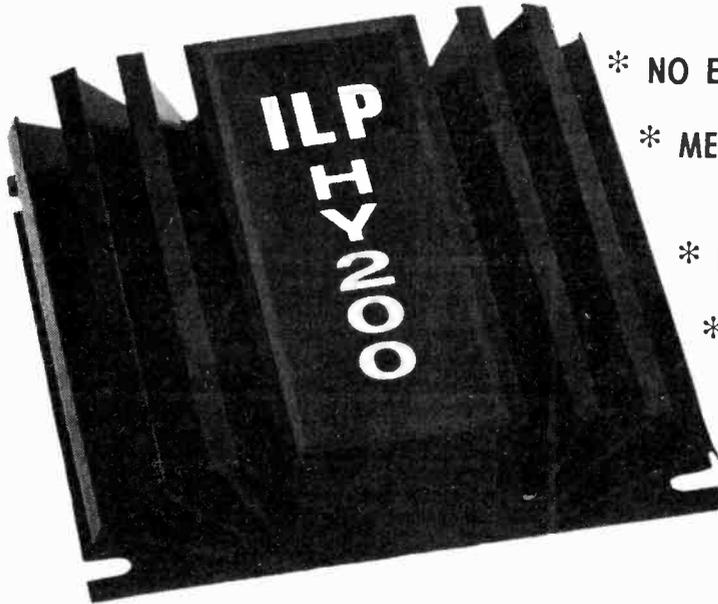

- \* NO EXTERNAL COMPONENTS
- \* MECHANICALLY & ELECTRICALLY ROBUST
- \* INTEGRAL HEATSINK
- \* HERMETICALLY SEALED UNIT
- \* ATTRACTIVE APPEARANCE
- \* LOW COST
- \* BRITISH BUILT

With the development of the HY200, ILP bring you the first **COMPLETE** Hybrid Power Amplifier.

**COMPLETE**: because the HY200 uses no external components!

**COMPLETE**: because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.

**OUTPUT POWER**: 100 watts RMS; 200 watts peak music power. **INPUT IMPEDANCE**: 10k $\Omega$ . **INPUT SENSITIVITY**: 0Dbm (0.775volt RMS). **LOAD IMPEDANCE**: 4-16 $\Omega$ . **TOTAL HARMONIC DISTORTION**: less than 0.1% at 100 watts, typically 0.05%. **SIGNAL : NOISE**: better than 75Db relative to 100 watts. **FREQUENCY RESPONSE**: 10Hz-50KHz  $\pm$ 1Db. **SUPPLY VOLTAGE**:  $\pm$ 45volts. **APPLICATIONS**: P.A., Disco, Groups, Hi-Fi, Industrial. **PRICE**: £14.90 inc. VAT & P&P. Trade applications welcomed.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

TRANSISTORS	
Output Transistors	
BD 112	25p
OC 36	50p
BD 145	25p
Small Signal N.P.N.	
BC 108	10p
BC 109	10p
BF 194	10p
Transmitting Types	
BFR 64	£1
BKY 93A	£5
BLY 93A	£9
Microwave Varactor Diodes	
BXY 27/28/32/35/36/37/38/39/40/41	£1
Microwave Detector	
CAY 10	£5
Microwave Mixer	
CL 7331	£20
Microwave Gunn Effect Oscillator	
CL 8370	£10
CL 8380	£10
CL 8390	£10
CL 8470	£40
Microwave Tunnel Diodes	
AEY 13	£5
AEY 16	£10
R.F. Transistors	
BF 180	20p
BF 194	10p
AF 124	20p

Field Effect Transistors	
BFW 12/13/14	25p
Micro-miniature N.P.N.	
BFS 18R	10p
LDA 400/403/450/452	10p
Infra-red Transmitters	
COY 11A	£4
COY 12A	£10
Light-sensitive Trans	
OCP 70	20p
Complementary Drivers, 2 watts (per matched pair)	
INTEGRATED CIRCUITS	
TBA 500 Luminance I.C.	£1
TBA 510 Chrominance I.C.	£1
FEQ 101 64bit Memory	12p
7400	12p
7401	12p
7410	12p
7420	12p
7440	12p
7453	12p
7470	24p
7472	24p
7473	32p
7474	32p
7482	88p
7483	95p
7490	58p
7491	78p
7492	58p
7493	58p
7495	68p
5400	10p
6404	10p

**NEW! NEW! NEW! NEW!**  
An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.  
Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light (No need to use ultra-violet) Spray with developer. Rinse and etch in normal manner.  
Light sensitive aerosol spray £1.00 plus postage  
Developer and Etchant 50p

NEWER THAN NEW! !	
Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes	
75mm x 100mm	33p
150mm x 100mm	66p
150mm x 200mm	£1.32
Epoxy-Resin	
75mm x 100mm	22p
100mm x 150mm	44p
150mm x 200mm	88p
Copper-clad Fibre Board	
12in x 6in	45p
Copper-clad Epoxy Resin Board	
12in x 6in	25p

VEROBOARD	
2 1/2in x 1in x 0.15in	8p
3 1/2in x 2 1/2in x 0.15in	16p
3 1/2in x 3 1/2in x 0.15in	20p
5in x 2 1/2in x 0.15in	20p
5in x 3 1/2in x 0.15in	28p
17in x 2 1/2in x 0.15in	55p
17in x 3 1/2in x 0.15in	74p
3 1/2in x 2 1/2in x 0.1in	21p
3 1/2in x 3 1/2in x 0.1in	24p
5in x 2 1/2in x 0.1in	23p
5in x 3 1/2in x 0.1in	28p
Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0-1 or 0-15) 36 for 18p. Special Offer Pack consisting of 5 2 1/2in x 1in boards and a Spot Face Cutter—50p. *ODDS & ENDS —1p sq in	

MULLARD POLYESTER CAPACITORS	
500,000 in STOCK!!!	
0-001µF	0-0018µF
0-0012µF	0-0022µF
0-0015µF	0-0027µF
0-0018µF	0-0033µF
0-0022µF	0-0039µF
0-0027µF	0-0047µF
0-0033µF	0-0056µF
0-0039µF	0-0068µF
0-0047µF	0-0082µF
0-0056µF	0-01µF
0-0068µF	0-012µF
0-0082µF	0-015µF
0-01µF	0-018µF
0-012µF	0-022µF
0-015µF	0-027µF
0-018µF	0-033µF
0-022µF	0-039µF
0-027µF	0-047µF
0-033µF	0-056µF
0-039µF	0-068µF
0-047µF	0-082µF
0-056µF	0-1µF
0-068µF	0-12µF
0-082µF	0-15µF
0-1µF	0-18µF
0-12µF	0-22µF
0-15µF	0-27µF
0-18µF	0-33µF
0-22µF	0-39µF
0-27µF	0-47µF
0-33µF	0-56µF
0-39µF	0-68µF
0-47µF	0-82µF
0-56µF	1µF
0-68µF	1.2µF
0-82µF	1.5µF
1µF	1.8µF
1.2µF	2.2µF
1.5µF	2.7µF
1.8µF	3.3µF
2.2µF	3.9µF
2.7µF	4.7µF
3.3µF	5.6µF
3.9µF	6.8µF
4.7µF	8.2µF
5.6µF	10µF
6.8µF	12µF
8.2µF	15µF
10µF	18µF
12µF	22µF
15µF	27µF
18µF	33µF
22µF	39µF
27µF	47µF
33µF	56µF
39µF	68µF
47µF	82µF
56µF	100µF
68µF	120µF
82µF	150µF
100µF	180µF
120µF	220µF
150µF	270µF
180µF	330µF
220µF	390µF
270µF	470µF
330µF	560µF
390µF	680µF
470µF	820µF
560µF	1000µF
680µF	1200µF
820µF	1500µF
1000µF	1800µF
1200µF	2200µF
1500µF	2700µF
1800µF	3300µF
2200µF	3900µF
2700µF	4700µF
3300µF	5600µF
3900µF	6800µF
4700µF	8200µF
5600µF	10000µF
6800µF	12000µF
8200µF	15000µF
10000µF	18000µF
12000µF	22000µF
15000µF	27000µF
18000µF	33000µF
22000µF	39000µF
27000µF	47000µF
33000µF	56000µF
39000µF	68000µF
47000µF	82000µF
56000µF	100000µF
68000µF	120000µF
82000µF	150000µF
100000µF	180000µF
120000µF	220000µF
150000µF	270000µF
180000µF	330000µF
220000µF	390000µF
270000µF	470000µF
330000µF	560000µF
390000µF	680000µF
470000µF	820000µF
560000µF	1000000µF
680000µF	1200000µF
820000µF	1500000µF
1000000µF	1800000µF
1200000µF	2200000µF
1500000µF	2700000µF
1800000µF	3300000µF
2200000µF	3900000µF
2700000µF	4700000µF
3300000µF	5600000µF
3900000µF	6800000µF
4700000µF	8200000µF
5600000µF	10000000µF
6800000µF	12000000µF
8200000µF	15000000µF
10000000µF	18000000µF
12000000µF	22000000µF
15000000µF	27000000µF
18000000µF	33000000µF
22000000µF	39000000µF
27000000µF	47000000µF
33000000µF	56000000µF
39000000µF	68000000µF
47000000µF	82000000µF
56000000µF	100000000µF
68000000µF	120000000µF
82000000µF	150000000µF
100000000µF	180000000µF
120000000µF	220000000µF
150000000µF	270000000µF
180000000µF	330000000µF
220000000µF	390000000µF
270000000µF	470000000µF
330000000µF	560000000µF
390000000µF	680000000µF
470000000µF	820000000µF
560000000µF	1000000000µF
680000000µF	1200000000µF
820000000µF	1500000000µF
1000000000µF	1800000000µF
1200000000µF	2200000000µF
1500000000µF	2700000000µF
1800000000µF	3300000000µF
2200000000µF	3900000000µF
2700000000µF	4700000000µF
3300000000µF	5600000000µF
3900000000µF	6800000000µF
4700000000µF	8200000000µF
5600000000µF	10000000000µF
6800000000µF	12000000000µF
8200000000µF	15000000000µF
10000000000µF	18000000000µF
12000000000µF	22000000000µF
15000000000µF	27000000000µF
18000000000µF	33000000000µF
22000000000µF	39000000000µF
27000000000µF	47000000000µF
33000000000µF	56000000000µF
39000000000µF	68000000000µF
47000000000µF	82000000000µF
56000000000µF	100000000000µF
68000000000µF	120000000000µF
82000000000µF	150000000000µF
100000000000µF	180000000000µF
120000000000µF	220000000000µF
150000000000µF	270000000000µF
180000000000µF	330000000000µF
220000000000µF	390000000000µF
270000000000µF	470000000000µF
330000000000µF	560000000000µF
390000000000µF	680000000000µF
470000000000µF	820000000000µF
560000000000µF	1000000000000µF
680000000000µF	1200000000000µF
820000000000µF	1500000000000µF
1000000000000µF	1800000000000µF
1200000000000µF	2200000000000µF
1500000000000µF	2700000000000µF
1800000000000µF	3300000000000µF
2200000000000µF	3900000000000µF
2700000000000µF	4700000000000µF
3300000000000µF	5600000000000µF
3900000000000µF	6800000000000µF
4700000000000µF	8200000000000µF
5600000000000µF	10000000000000µF
6800000000000µF	12000000000000µF
8200000000000µF	15000000000000µF
10000000000000µF	18000000000000µF
12000000000000µF	22000000000000µF
15000000000000µF	27000000000000µF
18000000000000µF	33000000000000µF
22000000000000µF	39000000000000µF
27000000000000µF	47000000000000µF
33000000000000µF	56000000000000µF
39000000000000µF	68000000000000µF
47000000000000µF	82000000000000µF
56000000000000µF	100000000000000µF
68000000000000µF	120000000000000µF
82000000000000µF	150000000000000µF
100000000000000µF	180000000000000µF
120000000000000µF	220000000000000µF
150000000000000µF	270000000000000µF
180000000000000µF	330000000000000µF
220000000000000µF	390000000000000µF
270000000000000µF	470000000000000µF
330000000000000µF	560000000000000µF
390000000000000µF	680000000000000µF
470000000000000µF	820000000000000µF
560000000000000µF	1000000000000000µF
680000000000000µF	1200000000000000µF
820000000000000µF	1500000000000000µF
1000000000000000µF	1800000000000000µF
1200000000000000µF	2200000000000000µF
1500000000000000µF	2700000000000000µF
1800000000000000µF	3300000000000000µF
2200000000000000µF	3900000000000000µF
2700000000000000µF	4700000000000000µF
3300000000000000µF	5600000000000000µF
3900000000000000µF	6800000000000000µF
4700000000000000µF	8200000000000000µF
5600000000000000µF	10000000000000000µF
6800000000000000µF	12000000000000000µF
8200000000000000µF	15000000000000000µF
10000000000000000µF	18000000000000000µF
12000000000000000µF	22000000000000000µF
15000000000000000µF	27000000000000000µF
18000000000000000µF	330000000

# Build yourself a TRANSISTOR RADIO

WITH AFTER SALES SERVICE

## ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND.

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Fine tone moving coil speaker. (Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

TOTAL BUILDING COSTS


**£9.35**

P.P. & INS. 52p

(OVERSEAS P. & P. £1.05)



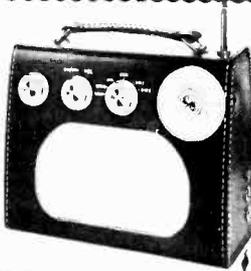
## ROAMER EIGHT Mk. I NOW WITH VARIABLE TONE CONTROL



7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£7.68** P.P. & INS. 47p (OVERSEAS P. & P. £1.05)


## ROAMER SEVEN Mk. IV

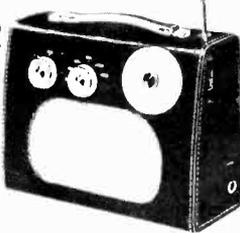

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6.58** P.P. & INS. 47p (OVERSEAS P. & P. £1.05)


## ROAMER SIX

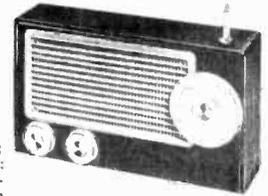

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages - 6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Easy build plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS **£4.38** P.P. & INS. 31p (OVERSEAS P. & P. £1.05)


## POCKET FIVE

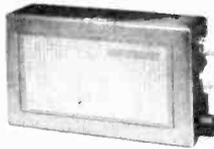

3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages - 5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 6 1/2in x 4 1/4in x 3 1/4in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2.50** P.P. & INS. 24p (OVERSEAS P. & P. 65p)

## TRANSONA FIVE

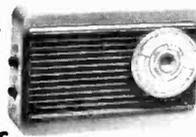


### 5 TRANSISTORS AND 2 DIODES

3 TUNABLE WAVE BANDS: MW, LW AND TRAWLER BAND. 7 stage - 5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2in x 4 1/4in x 1 1/4in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2.75** P.P. & INS. 25p (OVERSEAS P. & P. 65p)

## TRANS EIGHT

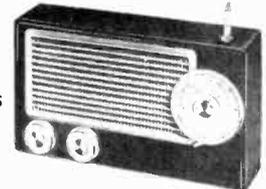

### 8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery recharger switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£4.95** P.P. & INS. 33p (OVERSEAS P. & P. £1.05)



## "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and easy build plans 25p (FREE with parts).

ALL PARTS INCLUDING CASE AND PLANS **£6.05** P.P. & INS. 33p (OVERSEAS P. & P. £1.05)

## RADIO EXCHANGE LTD

61a HIGH ST., BEDFORD MK40 1SA. Tel. 0234 52367  
Reg. no. 788372

I enclose £ \_\_\_\_\_ please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

P.E. 55

# Sinclair Project 60

## Now—the Z.50 Mk.2


with built-in automatic transient overload protection

When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symmetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50. Circuitry has been re-designed, making this versatile high performance amplifier better than ever.



with free manual  
£5.48
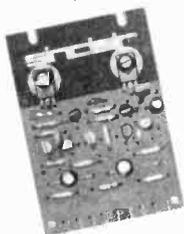
### Z.30 the power amplifier for quality and economy




with free manual  
£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm (3 1/8 x 2 1/4 x 1/2). Z.30, Z.50 and Z.50 MK.2 modules are compatible and interchangeable.
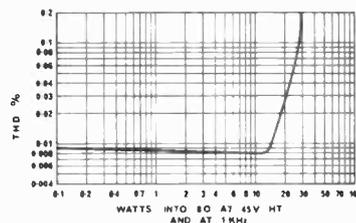
### Brilliant new technical specifications

Input impedance 100 K $\Omega$   
Input (for 30w into 8 $\Omega$ ) 400mV  
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better  
Distortion 0.02% up to 20W at 8 $\Omega$ . See curve  
Frequency response 10Hz to more than 200 KHz  $\pm$  1dB  
Max. supply voltage 45v (4 $\Omega$  to 8 $\Omega$  speakers) (50v 15 $\Omega$  speakers only)  
Min. supply voltage 9v  
Load impedance – minimum : 4 $\Omega$  at 45v HT  
Load impedance – maximum : safe on open circuit



## Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	<b>Z.30</b>	Crystal P.U., 12V battery volume control, etc.	<b>£4.48</b>
Mains powered record player	<b>Z.30, PZ.5</b>	Crystal or ceramic P.U. volume control, etc.	<b>£9.45</b>
12W. RMS continuous sine wave stereo amp. for average needs	<b>2 x Z.30s, Stereo 60; PZ.5</b>	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	<b>£23.90</b>
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	<b>2 x Z.30s, Stereo 60; PZ.6</b>	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	<b>£26.90</b>
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier (60W. RMS into 8 ohms)	<b>2 x Z.50s, Stereo 60; PZ.8, mains transformer</b>	As above	<b>£34.88</b>
Indoor P.A.	<b>Z.50, PZ.8, mains transformer</b>	Mic., guitar, speakers, etc., controls	<b>£19.43</b>

F.M. Stereo Tuner (£26) & A.F.U. (£6.98) may be added as required.

### Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

# sinclair

# the world's most advanced high fidelity modules

## Stereo 60 Pre-amp/control unit



Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

**SPECIFICATIONS**—**Input sensitivities:** Radio — up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A. curve  $\pm 1$ dB. 20 to 25,000 Hz. Ceramic p.u. — up to 3mV. Aux — up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +12 to -12dB at 10KHz. BASS +12 to -12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed. **£9.98**

## Project 60 Stereo F.M. Tuner




The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

**SPECIFICATIONS**—**Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7 $\mu$ V for lock-in over full deviation. **Squelch level:** Typically 20 $\mu$ V. **Signal to noise ratio:** >65dB. **Audio frequency response:** 10Hz — 15KHz ( $\pm 1$ dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 $\mu$ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25—30VDC. **Indicators:** Stereo on, tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**
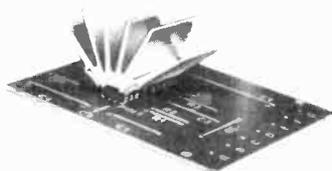
## Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC. make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

### SPECIFICATIONS

**Output power:** 6 watts RMS continuous (12 watts peak) 6—8 $\Omega$ . **Frequency Response:** 5Hz to 100KHz  $\pm 1$ dB. **Total Harmonic Distortion:** Less than 1% (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual

**£2.98** Post free

## Power Supply Units The new PZ.8 Mk.3



The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK.2 amplifiers are used. Nominal working voltage — 45.

PZ.8 Mk.3—£7.98

(Mains transformer, if required) £5.98

PZ.5 30v un stabilised

(not suitable for Project 60 tuner) £4.98

PZ.6 35v stabilised

(not suitable for IC.12) £7.98

## Project 605



the easy way to  
buy and build  
Project 60  
without  
soldering

Project 605 in one pack contains one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering.

Complete with comprehensive manual, post free

**£29.95**

All you need for a superb 30 watt high fidelity stereo amplifier

## Order form

Please send

enclose cash/cheque/money order.

Name \_\_\_\_\_

Address \_\_\_\_\_

PE/7/73

SINCLAIR RADIONICS LTD., LONDON ROAD  
ST. IVES, HUNTINGDONSHIRE PE17 4HJ

# sinclair

Add 10% V.A.T. to all prices quoted on page opposite and above

Practical Electronics August 1973

659

# parts for PRACTICAL ELECTRONICS projects

After many requests, Electro Spares are now supplying lists of components for all the projects featured in "Practical Electronics", commencing with May 1973 issue. Just forward an S.A.E. (preferably 9" x 4" minimum), and state which project is of interest to you—we will forward an individually priced list of the components required.

No need to buy a full kit—you need only purchase the parts you require at any one time.

All Electro Spares supplied components are new, branded products of reputable manufacturers, and carry full makers' guarantees.

We regret we cannot supply lists for projects published before May 1973 issue.

**"ONE SOURCE" BUYING MAKES SENSE—  
IT CAN SAVE YOU TIME, MONEY AND POSTAGE**

## "p.e." f.m. varicap stereo tuner

Electro Spares offer a kit of high quality parts to the published specification for this remarkable tuner, featured in "Practical Electronics", May 1973.

Features include pushbutton "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy, "no problem" construction, requiring only a few simple setting up adjustments with a D.C. Voltmeter. Uses **NEW** pre-set modules for R.F. and I.F. circuits—no circuit alignment. High efficiency integrated circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator.

Fibre Glass P.C. Board, neat slim line cabinet, with brushed aluminium front panel, push buttons, etc., etc.

**IDEAL FOR USE WITH THE "TEXAN", "P.E. GEMINI" AND ANY GOOD QUALITY STEREO AMPLIFIER.**

Please send S.A.E. for full details.

## "p.e. gemini" stereo amplifier

**QUALITY HI-FI FOR THE HOME CONSTRUCTOR**

30 Watts (R.M.S.) per Channel into 8 ohms!

Total Harmonic Distortion 0.02%!

Frequency Response (-3 dB) 20Hz — 100kHz!

We are still continuing to supply components for this fabulous amplifier, which is now recognised as practically the ultimate in High Fidelity. We know of no better unit for the home constructor, and can supply a booklet, containing full specification, complete constructional information, wiring diagrams, fault finding guide, etc., etc., price 55p plus 4p postage.

Our **new, low comprehensive price list** is supplied with each booklet, or supplied separately on receipt of large S.A.E.

**FOR PEOPLE WHO REQUIRE THE BEST—  
IT HAS TO BE THE "p.e. gemini"**

NOTE OUR NEW ADDRESS—WITH NEW MAIL ORDER DEPARTMENT FOR QUICK EFFICIENT SERVICE.

PLEASE PAY US A CALL—VISITORS WELCOME—EASY PARKING.

## Electro-Spares

**288 Ecclesall Road  
Sheffield S11 8PE**

**Tel.: Sheffield 668888**

**"THE COMPONENT CENTRE  
OF THE NORTH"**

## COMPARE OUR PRICES

Speaker Bargains	£p
E.M.L. 131n x 8in 3, 8 & 15 ohms	
plain	2-00
with tweeter	2-25
twin tweeter	3-50
Type 350 -20 watt with tweeter 8 ohms. P.P. 37p.	7-25
8in x 5in 3, 8 & 15 ohms	1-10
6½" (93550) 8 ohm	2-20
8" (14A/1000) 8 ohm 10 watt	4-00
EM1 3" Tweeter C/Magnet 8 ohm	1-00
FANE 7in x 4in 3 & 8 ohms	2-10
8in 8 ohm, dual cone	9-00
CELESTION 8in 15 ohm	1-40
BAKER GROUP 25 12in 25W 8 or 15 ohm	6-00
Postage 25p per speaker	
5" 8 ohm c/magnet P.P. 10p	80
2½in 8 or 64 ohm P.P. 10p	45
<b>Kit-form cabinets, teak</b>	
(17in x 10in x 6in) with a 15in x 8in or 8in cut out	2-95
18in x 11in x 9in with 13in x 8in cut out for EM1 350	23-95
(12in x 12in x 6in) with a 8in x 5in or 8in cut out. (please specify cut out)	2-25
Add 35p per Cabinet for post & packing	
<b>Microphone Bargains</b>	
CM 20 Crystal Hand	45
DX143 Dynamic, cassette-type stick	1-00
CM70 PLANET stick metal, switch crystal	1-45
DM160 Dynamic uni-dir, ball metal	3-75
UD130 50K/600 ohm uni-dir, ball metal	4-50
TW209 Leeson dual imp ball metal uni-dir	5-75
Condenser Mike uni-dir 600 ohm	7-95
Guitar mike	45
Lapel type, crystal	40
Postage 17p each	
<b>Cartridges—with standard fittings &amp; styli</b>	
	5p

ACOS GP91/28C or GP91/38C stereo compatible	90
ACOS GP94 stereo ceramic	1-60
ACOS GP95 stereo crystal	1-15
ACOS GP96 stereo ceramic	1-50
9THAC Sonotone stereo ceramic (diamond)	1-70
9THAC/G Sonotone stereo ceramic (diamond) slimline	1-70
ACOS GP67/2C mono crystal	65
ACOS GP101 compatible crystal	65
19-TI Sonotone stereo crystal	80
Postage 5p per cartridge	

Battery Eliminators	
240v input 6 or 9v d.c. output at 150 mA	1-99
12v d.c. input (for cars, fits in lighter socket) 6, 7, 4 or 9v d.c. output at 300 mA	2-50
P. & P. 10p	

Tapes—"MYLAR" base finest quality British made.	
5in 600ft 36p	5½in 1800ft 85p
5in 900ft 45p	7in 1200ft 55p
5in 1200ft 60p	7in 1800ft 80p
5½in 900ft 45p	7in 2400ft 95p
Postage 9p each	

Plastic Library Cases for	
5in Reels 16p	7in Reels 21p
5½in Reels 19p	P. & P. 5p each

### THIS MONTH'S SPECIAL OFFER

EMI Loudspeaker Enclosure Kit (LEK 450/8). Comprising 2 EMI 450 Speakers (8 ohm 10 watt, T/Tweeter plus cross-over) and 2 EMI Cabinet Kits 18" x 10" x 11". Plus acoustic wadding, glue, screws, instructions, etc. Recon. Retail price £29.20. Bargain at £18.00 inc. VAT, plus 50p P. & P.

Add 10% V.A.T. on prices incl. P. & P.

**RIVERSDALE  
ELECTRONICS**  
ALL OUR MERCHANDISE IS FULLY GUARANTEED

Mail Order Dept. E8/73,  
P.O. Box 470,  
Manchester M60 4BU  
SEND 25p FOR  
COMPLETE CATALOGUE

## A.M.C. ELECTRONICS LTD.


### SCORPIO ELECTRONIC IGNITION UNIT

COMPLETE KIT WITH  
ALL PARTS AND  
COMPREHENSIVE CONSTRUCTION  
AND FAULT FINDING DATA

COMPLETE KIT	£10.95 including V.A.T. and postage.
DATA	10p including V.A.T. and postage.
TRANSFORMER	£2.53 including V.A.T. and postage.
P.C.B. GLASS FIBRE	70p including V.A.T. and postage.
LATEST NEWS — P.E. TRIFFID.	P.C.B. 70p including post and V.A.T.
	Please add 15p to orders under £1.50. Send S.A.E. for other itemised prices.

**AMCEL, MAIL ORDER** 160 DRAKE STREET, ROCHDALE  
LANCASHIRE OL16 1PY
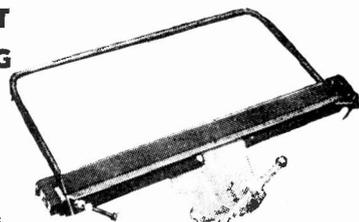
### PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS



With Bevelled Former Bars

No. 1. Capacity 18 gauge mild steel x 36in. wide	£17 carr. 50p
No. 2. Capacity 18 gauge mild steel x 24in. wide	£12 carr. 38p
No. 3. Capacity 16 gauge mild steel x 18in. wide	£12 carr. 38p
Also new bench models. Capacities 36in. x 18 gauge £35. 24in. x 16 gauge £32. Carriage 75p. Add 10% VAT to total price of machine and carriage.	
End folding attachments for radio chassis. Tray and Box making for 36in. model, 27½p per ft. Other models 17½p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.	

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997

# Henry's

## YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

### INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. BRANDED FROM TEXAS I.T.T. FAIRCHILD



Type	1/11	12/24	26/99	Type	1/11	12/24	26/99	Type	1/11	12/24	26/99
SN7400	0-20	0-18	0-18	SN7450	0-20	0-18	0-18	SN74145	1-50	1-40	1-30
SN7401	0-20	0-18	0-18	SN7451	0-20	0-18	0-18	SN74150	3-85	2-85	2-15
SN7402	0-20	0-18	0-18	SN7453	0-20	0-18	0-18	SN74151	1-10	0-85	0-90
SN7403	0-20	0-18	0-18	SN7454	0-20	0-18	0-18	SN74153	1-25	1-27	1-20
SN7404	0-20	0-18	0-18	SN7460	0-20	0-18	0-18	SN74154	2-00	1-75	1-65
SN7405	0-20	0-18	0-18	SN7470	0-30	0-27	0-25	SN74155	1-55	1-47	1-35
SN7406	0-30	0-27	0-25	SN7472	0-30	0-27	0-25	SN74156	1-55	1-47	1-35
SN7407	0-30	0-27	0-25	SN7473	0-40	0-37	0-35	SN74157	1-80	1-70	1-50
SN7408	0-20	0-18	0-18	SN7474	0-40	0-37	0-35	SN74160	2-60	2-40	2-25
SN7409	0-45	0-42	0-35	SN7475	0-55	0-52	0-50	SN74161	2-60	2-40	2-25
SN7410	0-20	0-18	0-18	SN7476	0-75	0-72	0-65	SN74162	3-40	3-25	2-70
SN7411	0-23	0-22	0-20	SN7480	0-80	0-75	0-67	SN74163	3-40	3-25	2-70
SN7412	0-42	0-40	0-35	SN7481	1-25	1-15	1-10	SN74164	2-75	2-50	2-10
SN7413	0-30	0-27	0-25	SN7482	0-87	0-80	0-70	SN74165	4-00	3-50	3-00
SN7416	0-30	0-27	0-25	SN7483	1-00	0-90	0-85	SN74166	4-00	3-50	3-00
SN7417	0-30	0-27	0-25	SN7484	0-90	0-85	0-80	SN74167	6-25	5-80	5-10
SN7420	0-20	0-18	0-18	SN7486	0-45	0-41	0-38	SN74170	4-10	3-55	3-05
SN7422	0-70	0-64	0-60	SN7490	0-75	0-70	0-65	SN74174	1-35	1-27	1-15
SN7423	0-48	0-44	0-40	SN7491AN	1-00	0-95	0-90	SN74176	1-60	1-35	1-20
SN7425	0-48	0-44	0-40	SN7492	0-75	0-70	0-65	SN74177	1-60	1-35	1-20
SN7427	0-42	0-39	0-35	SN7493	0-75	0-70	0-65	SN74180	1-55	1-30	1-20
SN7428	0-50	0-45	0-42	SN7494	0-80	0-75	0-70	SN74181	7-00	6-00	5-50
SN7430	0-20	0-18	0-18	SN7495	0-80	0-75	0-70	SN74182	2-00	1-80	1-60
SN7432	0-42	0-39	0-35	SN7496	1-00	0-97	0-95	SN74184	2-40	2-00	1-80
SN7433	0-70	0-64	0-60	SN7497	0-25	0-25	0-20	SN74185	2-40	2-00	1-80
SN7437	0-65	0-60	0-50	SN74100	2-50	2-50	2-00	SN74186A	2-40	2-00	1-80
SN7438	0-65	0-60	0-50	SN74104	1-45	1-35	1-20	SN74190	1-95	1-85	1-75
SN7440	0-20	0-18	0-18	SN74105	1-45	1-35	1-20	SN74191	1-95	1-85	1-75
SN7441AN	0-75	0-72	0-70	SN74107	0-50	0-45	0-40	SN74192	2-00	1-80	1-80
SN7442	0-75	0-72	0-70	SN74110	0-80	0-70	0-60	SN74193	2-00	1-80	1-80
SN7443	1-00	0-95	0-90	SN74118	1-00	0-95	0-90	SN74194	2-50	2-25	1-90
SN7445	2-00	1-75	1-60	SN74119	1-80	1-75	1-65	SN74195	1-85	1-70	1-60
SN7446	2-00	1-75	1-60	SN74121	0-80	0-75	0-65	SN74197	1-50	1-40	1-30
SN7447	1-75	1-60	1-45	SN74122	1-35	1-25	1-10	SN74198	4-60	3-70	3-35
SN7448	1-75	1-60	1-45	SN74141	1-00	0-95	0-90	SN74199	4-60	3-70	3-35

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX  
LARGER QUANTITY PRICES PHONE (01) 402 4891  
HIGH POWER SM 74 HOO } Now in stock - send for list No. 36  
LOW POWER SM 74 LHO }

### A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AA300	10p	BC147	12p	BU105	2.25	OC44	15p	T1843	35p	2N8055	55p
AA342	15p	BC169G	12p	BY100	15p	OC45	15p	V405A	25p	2N3440	75p
AAZ13	10p	BC182	10p	BY126	15p	OC57	50p	ZTX108	12p	2N3442	1.25
AC107	35p	BC214	15p	BY127	15p	OC71	15p	ZTX300	12p	2N3625	75p
AC126	25p	BCY32	75p	BYZ13	35p	OC72	25p	ZTX301	15p	2N3614	50p
AC127	25p	BCY34	35p	C106D	85p	OC77	45p	ZTX302	18p	2N3615	75p
AC128	25p	BCY39	1.00	GET111	55p	OC81	25p	ZTX341	20p	2N3702	10p
AC176	25p	BCY62	1.00	GET115	55p	OC83	25p	ZTX342	10p	2N3704	10p
AC187	25p	BCY43	2.50	GET880	45p	OC140	55p	ZTX503	17p	2N3705	10p
AC188	25p	BCY55	2.50	LM309K		OC170	25p	2G301	30p	2N3714	1.80
ACY17	30p	BCY70	15p	(T03)	1.87	OC171	30p	2N404	20p	2N3771	1.75
ACY20	20p	BCY71	20p	MAT121	25p	OC200	45p	2N527	25p	2N3772	2.00
ACY21	20p	BCY72	15p	MJE340	50p	OC201	75p	2N696	15p	2N3790	2.25
ACY39	55p	BCY87	2.80	MJE370	70p	OC202	60p	2N697	15p	2N3819	35p
AD140	50p	BCZ11	50p	MJE520	70p	OC203	50p	2N706	10p	2N3820	50p
AD149	50p	BD124	80p	MJE2955		OCPT1	1.25	2N930	20p	2N3866	85p
AD161	35p	BD131	75p		1.10	ORP12	50p	2N987	45p	2N3903	15p
AD162	35p	BD132	80p	MJE3055		ORP60	40p	2N1131	25p	2N3906	12p
AF117	10p	BF115	25p		75p	P346A	20p	2N1132	25p	2N4061	12p
AF118	10p	BF167	25p	MFF105	40p	RA8310AF		2N1302	18p	2N4062	12p
AF124	25p	BF173	25p	NK7214	20p	RAS508AF	45p	2N1304	22p	2N4125	15p
AF139	30p	BF179	30p	NK7216	40p	TAA2063	75p	2N1305	22p	2N4781	35p
AF186	40p	BF180	30p	NKT217	40p	TIL209	38p	2N1307	25p	2N5457	30p
AF239	40p	BF194	15p	NKT403	70p	TIP29A	50p	2N1308	25p	2N5777	55p
AS272	30p	BF195	15p	NKT404	50p	TIP29B	38p	2N1613	20p	28001	1.00
AS298	25p	BF861	25p	OA5	50p	TIP30A	60p	2N1671	1.00	28012	10.00
BA102	30p	BF898	25p	OA19	35p	TIP30A	60p	2N2147	75p	28018	6.25
BA115	7p	BF113	25p	OA91	10p	TIP31A	60p	2N2160	50p	28026	8.90
BA145	15p	BFX34	75p	OA91	7p	TIP32A	70p	2N2217	25p	28301	50p
BAX13	5p	BFX37	30p	OA200	7p	TIP33A		2N2221	20p	28303	65p
BAX16	7p	BFX88	20p	OA202	10p		1.00	2N2222A		28324	95p
BC107	10p	BFY50	20p	OC16	75p	TIP34A		2N2369A	25p	40250	50p
BC108	10p	BFY51	20p	OC20	85p		1.50	40361	15p	40360	40p
BC109	10p	BFY52	20p	OC23	85p	TIP35A		2N2906	20p	40362	50p
BC109C	12p	BFY50	50p	OC25	40p		2.50	2N2926	(all cols)	40408	50p
BC113	15p	BLY36	8.00	OC35	50p		3.00			40486	75p
BC117	20p	B8X20	15p	OC36	65p	TIP41A	75p	2N3053	20p	40636	1-10
BC143	35p	B8Y27	15p	OC42	40p	TIP42A	85p	2N3054	50p	40430	1-00

### VAT

Prices DO NOT include Value Added Tax. From 1st April 10% must be added and shown separately to your total order (inclusive post/packing). Help us help you receive your order without delay.

### QUANTITY DISCOUNTS

10% 10+; 15% 25+; 20% 100+; 25% 250+ ANY ONE TYPE

From above sections except Integrated Circuits and Special Offers where discounts are included. Minimum order value £1 please. Postage 7p on all orders.

### SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90	59p	2N2926	10p
1000 MC/S		All Colours	
25 + 50p		25 + 9p	
100 + 45p		100 + 8p	
500 + 40p		500 + 6p	
		1000 + 5p	

AF117 Mullard	25p	2N3819 Texas	35p
25 + 17p		25 + 30p	
100 + 15p		100 + 25p	
500 + 12p		500 + 20p	
		1000 + 15p	

OC170 Mullard	25p	BC107, BC108, BC109 10p each	
25 + 20p		All Makes	
100 + 15p		25 + 8p	
500 + 13p		100 + 7p	
1000 + 13p		500 + 6p	
		1000 + 5p	

BY127 Mullard	15p	ADI61, AD162	35p each
25 + 12p		25 + 32p	
100 + 10p		100 + 28p	
500 + 9p		500 + 25p	
1000 + 8p		1000 + 22p	

OA202	10p	2N3053	20p
25 + 8p		25 + 18p	
100 + 7p		100 + 15p	
500 + 6p		500 + 12p	
1000 + 5p		1000 + 10p	

OC35 Mullard	50p	2N3055	55p
25 + 45p		25 + 50p	
100 + 40p		100 + 45p	
500 + 38p		500 + 38p	
1000 + 30p		1000 + 33p	

### ZENER DIODES

400 M/W 5% Miniature  
BZY 88 Range  
All voltages 3-3 Volt 10p each.  
25 + 9p  
100 + 8p  
500 + 6.5p  
1000 + 5p  
Any one type.

### LINEAR (O/P AMPS)

702C TO5 75p  
709C TO9 35p  
709C D.I.L. 35p  
723C TO99 £1.00  
723C D.I.L. 95p  
725C TO99 £4.50  
741C TO99 55p  
741C D.I.L. 55p  
747




# NEW FROM DENMARK

## Already Established As One Of The Best Selling Kits in Europe

**JOSTY KIT today**

is counted among the leading manufacturers of electronic kits in Europe. Constantly the experienced engineers at the **JOSTY** laboratories work on improvement of existing kits and on new developments. Only the best materials and components have been used. The circuit-boards are manufactured according to the newest developments in this field and are supplied with all holes drilled and printed showing the exact placing of the components. Our long standing experience enables us to guarantee every **JOSTY KIT** for **ONE YEAR** for all parts as well as the correct function of the assembled kit. **JOSTY KIT'S** are a quality produce of DENMARK.

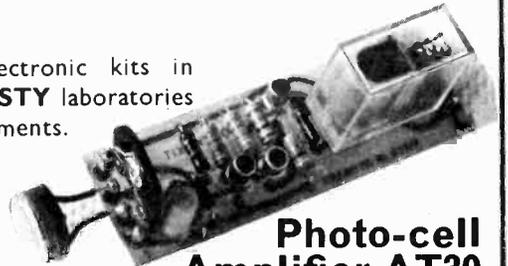

**Photo-cell  
Amplifier AT30**

NO more searching for Components, it's all in the bag the Josty way.

# ELECTRONIC CONSTRUCTION KITS

We are sorry, you may have a little difficulty obtaining these kits at present. We at Josty are doing everything we can to produce more kits but in the meantime they are only available from

### APPOINTED JOSTY KIT STOCKISTS

T. Pattison,  
5 Maritime Terrace,  
Blandford Street,  
Sunderland,  
Co. Durham.

Red Radio Shop,  
31 Crowtree Rd.,  
Sunderland,  
Co. Durham.

J. R. Gough,  
27 East Smithy St.,  
South Shields,  
Co. Durham.

Payne & Hornsby Ltd.,  
3 Andrews House,  
Gallowgate,  
Newcastle-on-Tyne.

Richley & Freeman Ltd.,  
100 Percy St.,  
Newcastle-on-Tyne.

Aitken Bros. Ltd.,  
35 High Bridge,  
Newcastle-on-Tyne.

Hamilton Music Store,  
Corporation Rd.,  
Middlesbrough,  
Teesside.

B. Williams,  
16 Borough Rd.,  
Middlesbrough,  
Teesside.

McKenna & Brown Ltd.,  
135 High St.,  
Redcar,  
Teesside.

Jaytron Ltd.,  
178-9 Phibsborough Rd.,  
Dublin 7,  
Ireland.

Bond & Mason,  
94 Church Rd.,  
Stockton,  
Teesside.

T. Jaques,  
Waterdale Rd.,  
Doncaster,  
Yorks.

Modern Electronics,  
5 Sunny Bar,  
Doncaster,  
York.

Misons,  
Citadel Row,  
Carlisle,  
Cumberland.

Televue Rentals,  
414 Catcote Rd.,  
Hartlepool,  
Co. Durham.

### JOSTY KIT RETAIL PRICE LIST (APRIL, 1973)

Model No.	Description	RRP Excluding V.A.T.	V.A.T.	Total RRP incl'd. V.A.T.
AF20	Mono Transistor Amplifier	4.80	0.48	5.28
AF30	Mono Transistor Pre-Amplifier	2.61	0.26	2.87
AF310	Mono Amplifier (for Stereo use two)	5.91	0.59	6.50
AT5	Automatic Light Control	2.58	0.26	2.84
AT30	Photo Cell Switching Unit	5.70	0.57	6.27
AT50	400W Triac Light Dimmer Speed Control	4.80	0.48	5.28
AT55	1,300W Triac Light Dimmer Speed Control	5.70	0.57	6.27
AT56	2,200W Triac Light Dimmer Speed Control	6.90	0.69	7.59
AT60	Psychedelic Light Control, Single Channel	7.80	0.78	8.58
AT65	Psychedelic Light Control, 3 Channel	14.55	1.45	16.00
HF61	Medium Wave Transistor Radio	3.33	0.33	3.66
HF65	F.M. Transistor Transmitter	2.70	0.27	2.97
HF75	F.M. Transistor Receiver	2.88	0.28	3.16
HF310	F.M. Tuner Unit	15.81	1.58	17.39
HF325	De-Luxe F.M. Tuner Unit	24.12	2.41	26.53
HF330	Stereo Decoder for use with HF310 or HF325	9.96	0.99	10.95
HF395	Aerial Amplifier for AM/FM Bands I, II and III	1.77	0.17	1.94
GP310	Stereo Pre-Amp to use with 2, AF310	21.27	2.12	23.39
GU330	Tremelo Unit for guitars, etc.	7.50	0.75	8.25
NT10	Power Supply 100mA 9V Stabilised, 12V Unstabilised	6.15	0.61	6.76
NT300	Professional Stabilised Power Supply 2 - 30V, 2-2A	12.51	1.25	13.76
NT305	Transistor Converter 12/15V, a.c./d.c. to 6V, 7.5V, or 9V d.c.	4.50	0.45	4.95
NT310	Power Supply 240V a.c. to 2 x 18V d.c. at 2A	4.80	0.48	5.28
NT315	Power Supply 240V a.c. to 4.5-15V d.c. 500mA	9.57	0.95	10.52

**Sole UK Distributors**

# RADIO SUPPLIES

(Components) Ltd.

P.O. BOX 27 • 39 WHITBY STREET • HARTLEPOOL TS24 7BR  
TELEPHONE 0429-5750 or 68002

## TWO-WAY LINK

**C**OMMUNICATION is a fundamental function of electronics. It is particularly appropriate therefore to discuss certain aspects of communication relating to this magazine and its readers. First, one unquestionable fact: the link forged between a magazine and its readers is of inestimable value and significance. To this it can be confidently added that a magazine devoted to a creative hobby is especially favoured in that feedback from its readers is often likely to be in the form of examples of readers' own personal efforts and experiences. Such direct positive evidence of a live and actively committed readership is perhaps the best and most encouraging reward the editorial staff of such a publication could wish for.

PRACTICAL ELECTRONICS is proud of the two-way link established between individual readers and the magazine. We believe this is mutually stimulating. The existence of this link has long been evident, and has been demonstrated most effectively in our pages through the medium of *Ingenuity Unlimited*. Reference to the popularity and importance of this feature is not out of place. It has often been commented upon that the circuit ideas published constitute a most valuable source of reference to designers and constructors alike. We agree, and feel sure that many a reader must have saved time and effort through studying the ideas in *Ingenuity Unlimited*.

The varied nature of these miscellaneous circuits is, in itself, quite instructive. It indicates a wide catholic range of interests and shows that the inventive spirit is as much alive as ever; a refreshing and reassuring antidote to the drab uniformity of thought and action which characterises many aspects of modern life.

The circuits published in *I.U.* are generally of modest proportions, but that is no true measure of their actual or potential worth. They represent the new outlook and approach to electronics which has emerged in the course of the last few years. The dramatic scaling down in physical size of components over the last decade has given electronics greater—almost total—freedom in the environmental sense, and in many instances it is released entirely from the shackles of the mains umbilical cord. One result of all this has been the creation of an enormous variety of small circuits, many owing their origination to the enterprising efforts of private individuals to solve some problem or meet some particular need through the agency of electronics, the very thought of which would have been preposterous a few years ago. Many of these are worth recording for the benefit of others.

We are glad to be able to present some of the fruits of this kind of private enterprise in *Ingenuity Unlimited*. And never let it be forgotten that such relatively simple circuits as these may sometimes prove to be the seeds from which bigger and grander concepts grow.—I.E.B.

**Editor**  
F. E. BENNETT

**Editorial**  
R. D. RAILTON *Assistant Editor*  
D. BARRINGTON *Production Editor*  
G. GODBOLD  
S. R. LEWIS B.Sc.

**Art Dept.**  
J. D. POUNTNEY *Art Editor*  
J. A. HADLEY  
R. J. GOODMAN

**Advertisement Manager**  
D. W. B. TILLEARD  
Phone: 01-634 4202

P. J. MEW  
Phone: 01-634 4210

C. R. BROWN, *Classified*  
Phone: 01-634 4301

*Editorial & Advertising Offices:*  
Fleetway House, Farringdon St.,  
London EC4A 4AD  
Phone: *Editorial* 01-634 4452  
*Advertisements* 01-634 4202

# BATTLE CHESS

By D. COLES



THE GAME of chess is more Machiavellian than military in its tactics and strategy and the circuit described here provides a version which is much more like the action of a military battle than court intrigue. Thus: Battle Chess.

No claim to originality is made by the author since Edgar Rice Burroughs—of Tarzan fame—once wrote a book called the "Chessmen of Mars" in which the idea was developed fully. The trouble with the Martian game was the requirement for real people, expected to fight to the death. The finding of 32 people willing to play chess in this way would undoubtedly prove difficult but the Battle Chess circuit is designed to simulate the duels which occur.

## THE GAME

In basic concept Battle Chess uses the moves of its namesake but introduces a variety of programmable factors which come into play each time there is a confrontation. Thus one piece does not merely "take" its opponent—they have to fight the situation out in an electronic simulation.

## PROGRAMMING

A number of factors have been programmed into the simulation circuit which parallel those found in real life military situations:

1. The strength of the various chessmen.
2. The addition of arms which increase the fighting strength of a chessman.
3. The reduction in fighting power due to supply problems (i.e. distance between duelling chessmen and their respective King's squares).
4. The proximity of supporting chessmen.
5. The effects of morale.

Combinations of resistors are used to determine factors 1 to 4. Resistance values interact with each other to affect the frequency of multivibrators (see Fig. 1).

Morale, on the other hand, is time dependent, being at its highest immediately after a successfully completed duel. The charge remaining in a capacitor simulates the effects of morale; the charge leaks away to nothing and the probability of winning the next duel drops from exceptionally high for the previously winning player to the normal value over a period of about ten minutes.

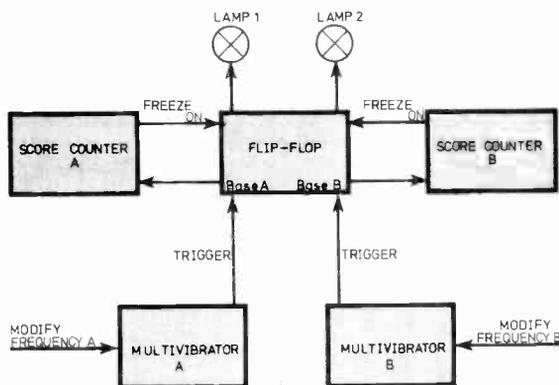


Fig. 1. Block schematic of the Battle circuit showing how the basic units are interconnected

The factors which combine in the game of Battle Chess make it virtually impossible to predict the outcome of a simulated duel. Thus the tactics and strategy which have to be developed by the player are more dynamic, more subject to caprice, than those used in conventional chess and are designed to approximate the real life strategy of a series of military engagements.

### THE SIMULATION CIRCUIT

The circuit is shown in block form in Fig. 1 and in detail in Fig. 2.

Two conventional multivibrators A and B have their frequencies determined by external resistances connected between points 1 and 2 and the negative rail. The pulses of each multivibrator simulate the thrusts and parries of a duel and the resistances which combine to set the frequency of oscillation

freeze with the winning side indicated by the light which remains lit.

The opposing capacitor's charge is neutralised through diodes D1 or D2 so that the other Darlington remains unswitched. The charge in the winning capacitor remains at the switching voltage as long as the lamp remains lit and leaks away once the circuit is switched off. This slowly leaking charge represents the player-army's morale and if a fight is started before the charge has gone, it takes less time to build up to its switching value.

### CONSTRUCTION

The simulation circuit layout is not critical and the Veroboard method of construction is ideal.

The multivibrators may be constructed first and checked by temporarily connecting 3.3kΩ resistors

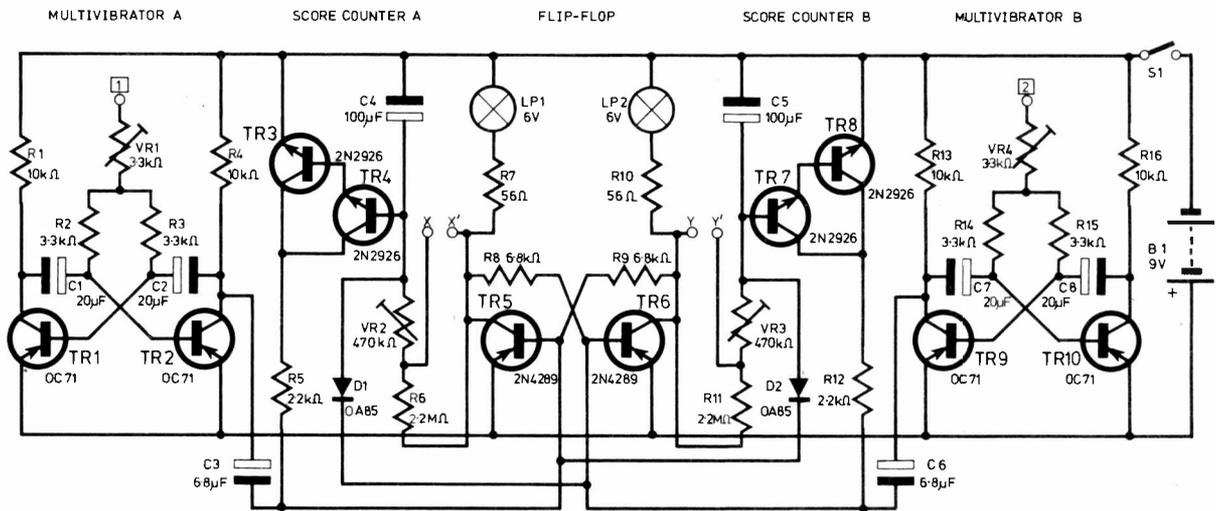


Fig. 2. Detailed circuit diagram of the equipment. When setting the timing of the various sections it may be necessary to select the electrolytic capacitors C1 to C8 if the variable resistors VR1 to VR4 are unable to provide sufficient adjustment to "pull" the periods into agreement

represent the value of the chessman, its distance from its King's square—representing G.H.Q.—and the number of friendly chessmen and their relative positions.

Pulses from each multivibrator are fed to a central flip-flop via capacitors C3 and C6. These pulses switch the flip-flop so that lamps LP1 and LP2 are switched on alternately with a continuously varying mark/space ratio. The lamps, as well as providing a visual analogue of the duel, eventually indicate which side has won.

Depending on which flip-flop transistor is ON, a current flows in R7 or R10 providing a potential difference which charges capacitors C4 and C5 through resistors R6 and R11. Additional resistors may be inserted at points XX' and YY' to reduce the overall resistance and allow C4 or C5 to charge faster.

These additional resistances simulate weapons used by the battling chessmen. When either C4 or C5 reaches a voltage of about 0.7 volts, the associated score counter, a Darlington pair, switches on, causing two things to happen. The Darlington pair output biases the flip-flop via R5 or R12, causing it to

between points 1 and 2 and the negative rail. Connect the 9 volt battery and check oscillation with a voltmeter across R4 and R13.

The flip-flop should be built on next, together with its trigger pulse feeds, C3 and C6. Connecting the battery should now cause the lamps to flash alternately in response to the multivibrators and clearly show the variation in mark/space ratio.

When constructing the score counters remember that diodes D1 and D2 must be good ones. A reverse leak on one or both of these, even if only four to five micro-amps, will upset the impartiality of the circuit. Pliers used as a heat shunt when connecting them will reduce the risk of damaging their characteristics.

To test the score counters, connect the battery once more and briefly touch a 10kΩ resistor, connected to the positive rail, to the positive lead of C3. The lights should cease to flash, LP1 should stay lit and LP2 extinguish.

Leave the circuit in this state to check that it is a stable condition; if the situation changes it will almost certainly be one of the diodes at fault. Repeat the test with C5.

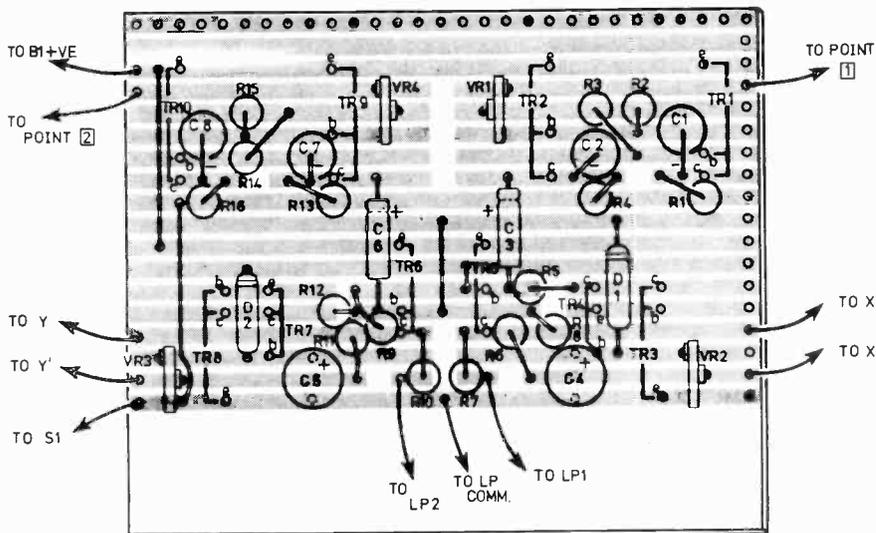



Fig. 3. Veroboard layout of the components on 0.1 inch pitch board. In the present case this was cut from a sheet edge to give a blank area which can be drilled for fixing as required

Finally, test that the flip-flop is charging the score capacitors properly. Temporarily connect a  $1M\Omega$  resistor across the points XX'. Discharge the score capacitors by shorting their positive leads to the negative rail before switching on. The lamps should flash for 10 to 15 seconds and then LP1 will remain on and LP2 off. Repeat with the  $1M\Omega$  resistor across the points YY' and the opposite situation should occur. Failure at this stage could be due to poor solder joints, leaky diodes or slight tracking between the Veroboard copper strips.
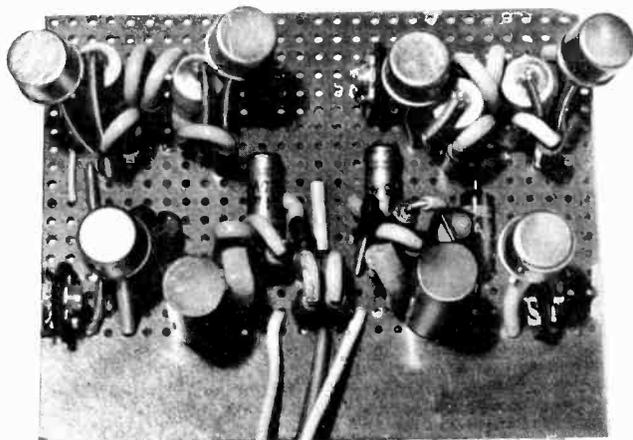
### THE PLAYING BOARD

The playing board consists of a matrix of 64 4-way sockets. Each side utilises two of the pin sockets and the connections to each side are similar and may be considered separately.

One of the pin sockets acts as a power feed and is connected to the negative line through a series resistor and a switch contact as in Fig. 4. Current is transferred to the other pin socket through the resistance of the chessman as shown in Fig. 5 and to the multivibrator through a second series resistor and switch contact. The two switches (1-pole, 8-way) act as Rank and File co-ordinates and locate the



Completed circuit board for Battle Chess

## COMPONENTS . . .

### BATTLE CIRCUIT

#### Resistors

R1, R4, R13, R16	10k $\Omega$	R6, R11	2.2M $\Omega$
R2, R3, R14, R15	3.3k $\Omega$	R7, R10	56 $\Omega$
R5, R12	2.2k $\Omega$	R8, R9	6.8k $\Omega$

#### Capacitors

C1, C2, C7, C8	20 $\mu$ F	
C3, C6	6.8 $\mu$ F	All 12V working
C4, C5	100 $\mu$ F	

#### Potentiometers

VR1, VR4	3.3k $\Omega$	
VR2, VR3	470k $\Omega$	All Skeleton Preset

#### Transistors and Diodes

TR1, TR2, TR9, TR10	OC71, OC72 or similar
TR3, TR4, TR7, TR8	2N2926 or similar
TR5, TR6	2N4289 or similar
D1, D2	OA85

#### Miscellaneous

LP1, LP2	6V, 60mA
S1	Single pole ON/OFF (pushbutton type)
B1	PP7, PP9 or similar Veroboard

### PLAYING BOARD

#### Resistors

R101, R115	4.4k $\Omega$
R102, R116	3.3k $\Omega$
R103, R117	2.7k $\Omega$
R104, R108, R118, R128	2.2k $\Omega$
R105, R109, R114	} 1.7k $\Omega$
R119, R122, R127	
R106, R110, R113, R120,	} 1.2k $\Omega$
R123, R126	
R107, R111, R112, R121,	} 1.0k $\Omega$
R124, R125	
RX (28 off)	10k $\Omega$

#### Miscellaneous

Four Phono sockets  
64 four-way sockets  
4 single-pole 8-way wafer switches  
Wire, hardboard, 2in  $\times$   $\frac{1}{2}$ in section wood, glue, screws, panel pins.

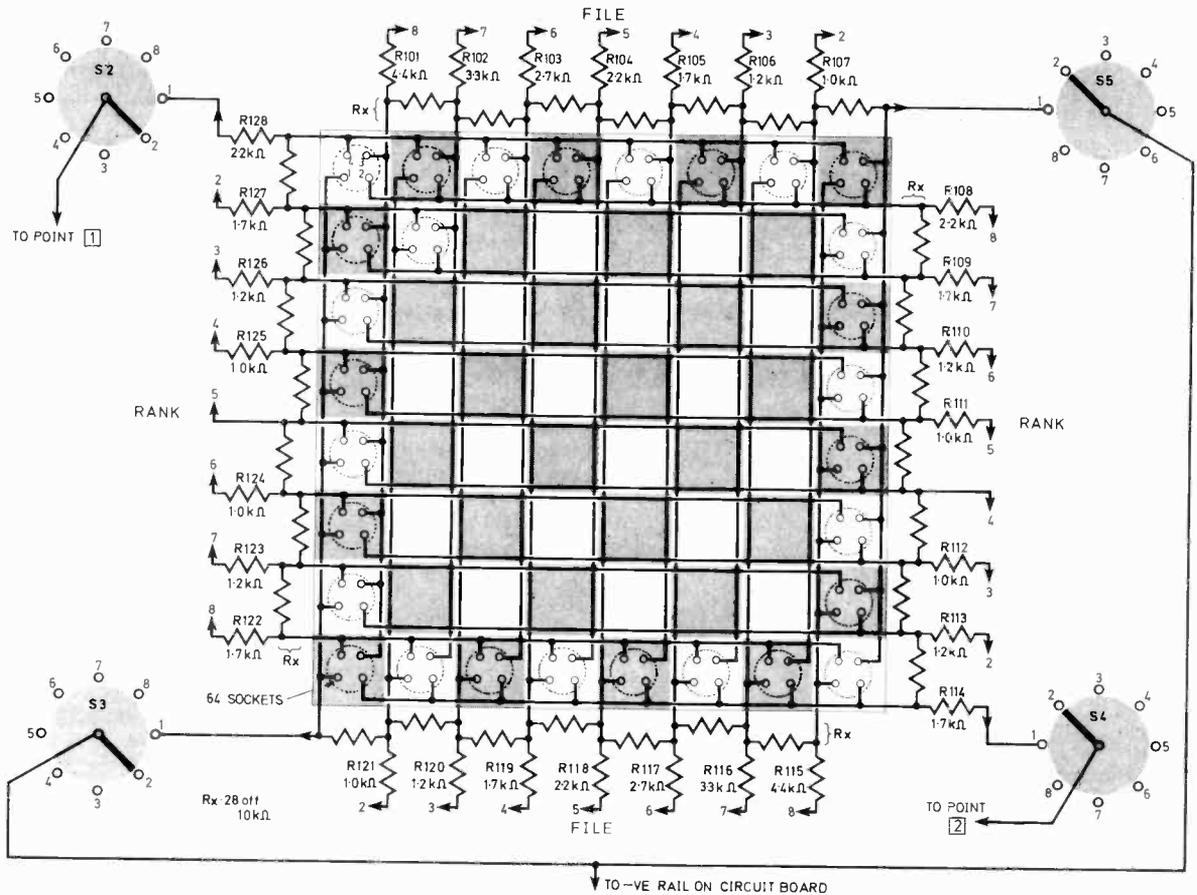


Fig. 4. Wiring of the playing board and Rank & File selection switches. Only the sockets at the periphery have been shown but, of course, there is a socket in each square, wired in a similar manner to all the others

chessmen which are to take part in the duel. The combined resistance of the two series resistors reduces the base biasing current in proportion to the chessman's distance from its King's square.

In addition to the series resistance and the chessman, each Rank and File is connected to its neighbouring Rank or File by a  $10k\Omega$  resistor so that a parallel path exists through every other friendly chessman. Thus the number and closeness of the other chessmen modify the final value of the biasing resistance; in effect, they lend their support.

## BALANCING

Variations in the chessmen, the weapons, and the playing board resistors are quite in order and may be interpreted as the usual random variations to be found in any army. However, the battle simulator must be balanced so that should an identical situation occur, neither side has a better chance of winning. The four variable resistors VR1 to VR4 are used to balance the circuit.


Starting with the multivibrators temporarily solder a  $4.7k\Omega$  resistor to each biasing network at 1 and 2 in turn, using 1 per cent or 5 per cent resistor if possible. Using a voltmeter across R4 or R13, count the number of oscillations in a ten second interval. Using the variable resistors, VR1 or VR4 alter the frequencies until they are, as nearly as possible, equal.

To balance the score counters, temporarily solder two  $2.2M\Omega$  resistors across points XX' and YY'. Switch on the simulator and note which lamp goes out permanently first. Alter VR2 and VR3 until only a small change in each preset changes the lamp which goes out. In between each try, it will be necessary to switch off and discharge C4 and C5.
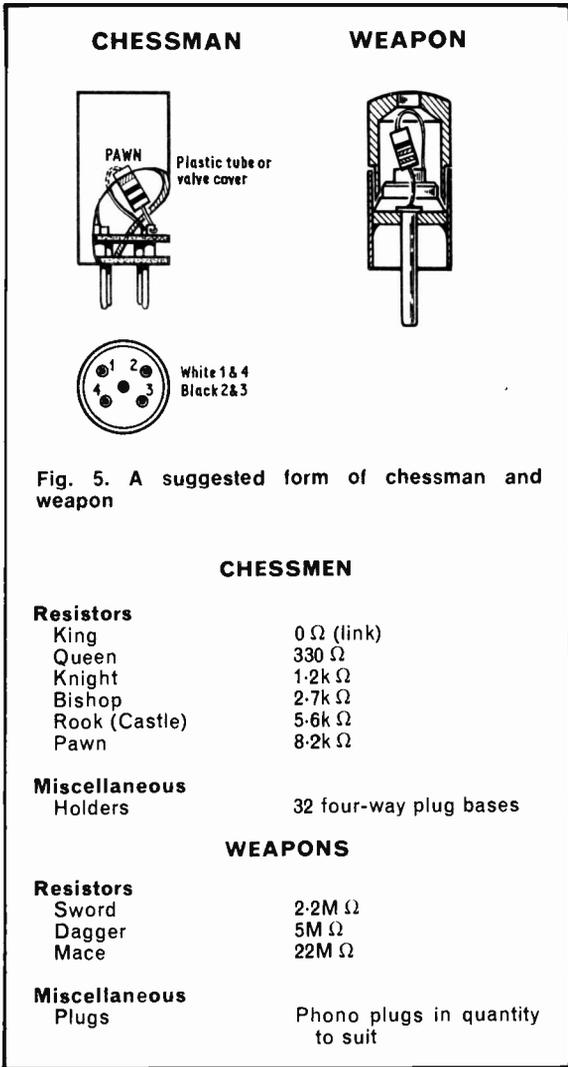
## THE PLAYING BOARD

The playing board circuit is shown in Fig. 4 together with details of switch connections. The 64 sockets are arranged in an  $8 \times 8$  array on a hardboard mounting which forms the top of the circuit cabinet and the playing board. The four single-pole, eight-way switches are mounted two at each end, the press on, press off mains switch, the lamps and phono sockets can be mounted in any convenient position. The line and interconnecting resistors are suspended in the wiring. The wiring can be tied into looms and attached to the inside of the wooden sides with wiring clips. The sockets can be attached with Araldite.

The sides and ends of the cabinet are fastened to the hardboard top with glue and panel pins. The bottom, another piece of hardboard, is secured to the sides with a few screws so that it can be removed for servicing. Dimensions have not been given since size and proportions will vary with the constructor.



## CHESSMEN AND WEAPONS

In the present example the chessmen are constructed on the four-way plug bases by soldering the correct resistors between the requisite pins as in Fig. 5 and Aralditing a length of plastic tube onto the base. The tube length may be varied to indicate the power of the piece; say three inches for a King reducing to one inch for a pawn. The name of the chessmen should be marked on the outside of the tube. The weapons are constructed similarly, using the phono plugs. Remember the Queening rule for pawns which successfully reach the opposite side of the board and make two Queens for each side.

The more ambitious might wish to mount genuine chessmen on the bases or perhaps even make pieces of their own devising. There are plenty of techniques available today to do this.

## FINAL TESTING

When all the wiring is complete and the circuit board secured inside with small brackets, the complete unit may be tested. Switch both sets of co-ordinate switches to Rank 1, File 8 and place a pawn

from each side at this position. Switch on the simulator and observe the rate at which the lights flash. Switch off and move the pawns to square: Rank 8, File 1 and switch on; the lights should now flash more slowly. Try the same tests with Kings; the same thing should happen except that the rate of flashing will be higher in both cases. Sometime during these tests a win will be indicated; when this happens, switch off and wait for the score capacitors to discharge, or alternatively discharge by shorting while switched off.

Try adding other pieces to the board in different positions and note the different flashing frequencies of each combination. In some cases the difference will be hard to distinguish since the alteration will be small.

## RULES OF PLAY

The chessmen move as for conventional chess and for the same distances.

When one player wishes to take an opposing piece and gain the occupied square, the attacking player must verbally challenge the other. Attacking and defending chessmen should be indicated and the defender cannot retreat from the challenge.

Rank and File co-ordinates are set on the switches to indicate the squares holding each piece. Weapons may be selected at any time and plugged into the phono sockets. The battle simulator is now switched on and the two lamps will flash alternately for, typically, 20 or 30 seconds. The light which remains on after the flashing has ceased indicates the winner who can now occupy the disputed square. The loser is removed from the game and the winner confiscates the loser's weapons for his own arsenal.

## TACTICS

The interaction of Player/Chessman/Position/Weapons/Morale alters the probability of any particular piece winning and if two roughly equal chessmen are opposed it is virtually impossible to predict a duel's outcome. The tactics used in Battle Chess can be effective in placing a player in a stronger position.

For example, wherever possible arrange to do battle as near as possible to your own King's square or try to arrange that your own combatant is close to a number of friendly pieces—the more powerful, the better.

Force battles to take place within 5 or 10 minutes of a previously successful battle or fight a delaying action for a similar time if a battle has just been lost. This avoids or uses the morale charge on the capacitor.

Of course there are the obvious comments like "don't throw pieces away in needless battles, they may be useful for support if not for combat" and finally always remember, you may win a battle but lose the war.

## NOTES

Although the rules of play suggested follow the rules of conventional chess, the equipment can be used to simulate modern battle conditions quite successfully. The playing board may be marked out with a map, and infantry, tanks, missiles can be substituted for pawns, knights, rooks, etc. In this case, the constructor is left to formulate his own rules. ★

# audio



# compressor

By R. A. Penfold

**A**N AUDIO compressor is an audio amplifier which is designed to provide a constant output level, from a wide variety of input levels. Thus it is sometimes referred to as a constant volume amplifier. It merely consists of an audio amplifier which is fitted with some form of automatic gain control.

## AUDIO COMPRESSION

Reasons for using audio compression vary, as it can be used in several applications. It is often used in tape recording when something such as a debate is to be recorded, and only one microphone is to be used.

The use of compression obviates the need to re-adjust the recording level each time a different person speaks, as, once the level is set for one speaker, the correct modulation depth will be obtained for all the others. This is of course providing that all the speakers are close enough to the microphone, to provide a sufficient output to operate the compressor. This technique also removes the possibility of overmodulation at unexpectedly high volume levels.

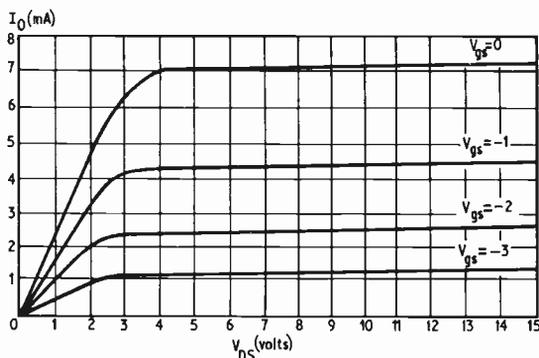


Fig. 1. Drain current plotted against drain to source voltage for a typical *n*-channel f.e.t.

Speech compression is used in some amateur transmitters in order to maintain a high average modulation level, without running the risk of overmodulating an a.m. transmitter, or exceeding the maximum power rating of the power amplifier of an S.S.B. transmitter.

Simple peak clipping circuits are sometimes used instead, but these introduce a comparatively high degree of distortion, and are not as effective.

## USING AN F.E.T.

When subject to a low voltage between the drain, and source terminals, an f.e.t. exhibits the characteristic of an ordinary resistor. This is illustrated in Fig. 1, which shows typical transfer characteristics of an *n*-channel f.e.t., at various gate voltages.

It will be seen that the value of the resistor formed by the f.e.t. can be varied by altering the gate bias voltage. It can be varied from a few hundred ohms to many megohms.

## THE CIRCUIT

A circuit diagram of an audio compressor utilising an f.e.t. in a voltage controlled attenuator is shown in Fig. 2. The input impedance to the unit is high (typically 2.5 megohm), and is suitable for use with a crystal microphone. The output is at a low impedance, and will drive virtually any amplifier. For low level inputs (i.e. below the level at which compression begins) a voltage gain of about 275 is available with the gain control at maximum.

In order to obtain the required high input impedance, the input transistor, TR1, is operated in the emitter follower mode. This is direct coupled to TR2, which is a common emitter amplifier.

For TR1 to produce a very high input impedance it must have a fairly high impedance in its emitter circuit. R4 is therefore used to raise the input impedance to TR2, in order to achieve this.

The bootstrapping technique has been employed in order to virtually eliminate the shunting effect the biasing resistors, R1, R2, and R3 would otherwise have on the input impedance. C3 is the bootstrapping capacitor.

Transistors TR1 and TR2 are used mainly as a buffer amplifier, and provide only a small voltage gain.

### VOLTAGE CONTROLLED ATTENUATOR

The output from TR2 is fed via C4 to the voltage controlled attenuator. R7 and R8 form a tap on the main supply rail, and produce a suitably low supply voltage for the f.e.t. TR3. The drain to source impedance of TR3, and R9 form an attenuator.

With no negative bias at TR3 gate, the drain to source impedance is very low, and the attenuation factor of the circuit is very low. By giving a negative bias at TR3 gate, the drain to source impedance can be greatly increased, and the attenuation factor of the circuit thus also greatly increased. A voltage controlled attenuator is thus formed.

The output from the attenuator is fed via C5 to the input of a very high gain common emitter amplifier, TR4, which is followed by an emitter follower stage,

tens of ohms. This will have a negligible effect upon the attenuation factor of the circuit.

Raising the input level slightly will increase the bias voltage, and due to the logarithmic relationship between bias voltage, and drain to source resistance, this will cause a much larger increase in this resistance, say a few hundred ohms. This will result in a noticeable, although still only small increase in the attenuation factor of TR3 and R9.

### INPUT LEVEL

It is at this point that raising the input level will begin to have a very noticeable effect on the voltage controlled attenuator, as only a very small change in bias is required to cause an increase of several kilohms in the drain to source resistance of TR3. Thus an increase in the input level causes the gain of the amplifier to drop considerably, and so reduce the output level. The output level will therefore tend to remain almost constant, even though the input level may vary considerably, providing the

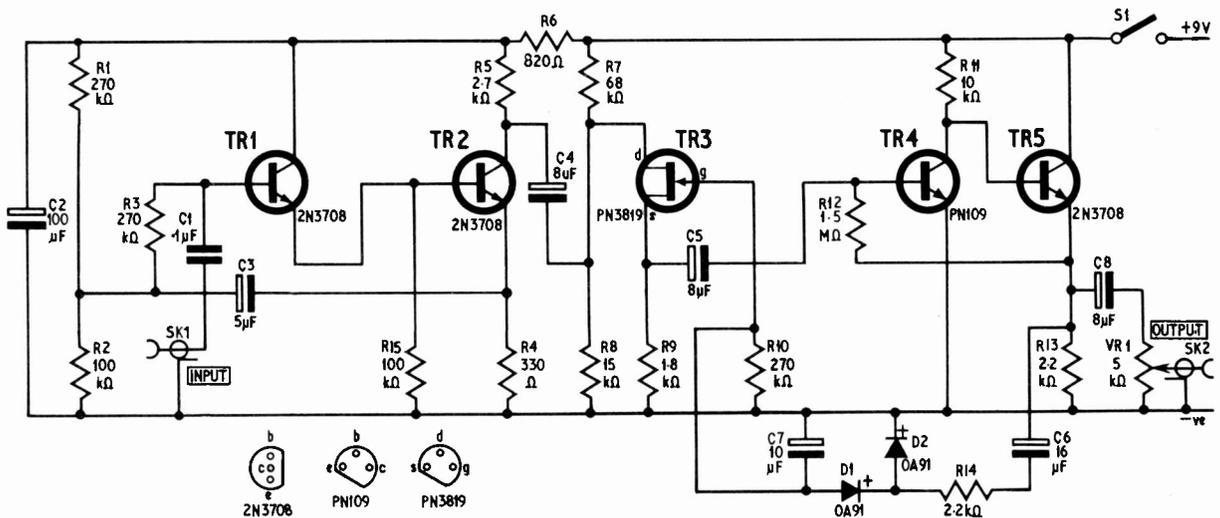


Fig. 2. Circuit diagram of the complete Audio Compressor

TR5. From the emitter of TR5, some of the signal is fed via C8 to the volume control, VR1, and then to the output socket. The remainder of the signal is used to produce the biasing voltage for the attenuator.

### RECTIFYING CIRCUIT

It is fed via C6, and R14 to a rectifying circuit, consisting of D1 and D2. This arrangement is used as it provides a fast attack speed, but with a long decay. C7 smoothes the a.f. half cycles to a d.c. negative bias, which is then fed to the gate terminal of the f.e.t.

There is not a linear relationship between the gate bias voltage, and the drain to source resistance of the f.e.t. With a low level input, only a small bias voltage will be produced, and this will only alter the value of the resistor formed by TR3 by a few


input is above the level at which compression commences.

Even with quite high input levels (up to about 0.25V r.m.s.) there will be only a small degree of distortion in the circuit. The use of modern silicon transistors in the input stage ensures a low noise level.
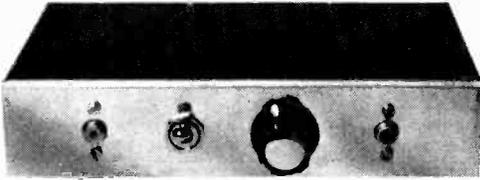
### TIME CONSTANT

The attack of the a.g.c. circuit is very fast, being virtually instantaneous, but the time constant capacitor, C7, produces a fairly long decay time (about two seconds). For most applications this is very desirable, as it prevents the gain from rising during brief pauses in the signal, and the noise which would subsequently accompany this.

However, the decay time can be altered to suit individual requirements by altering the value of C7, the larger its value, the longer the decay time.



# audio compressor

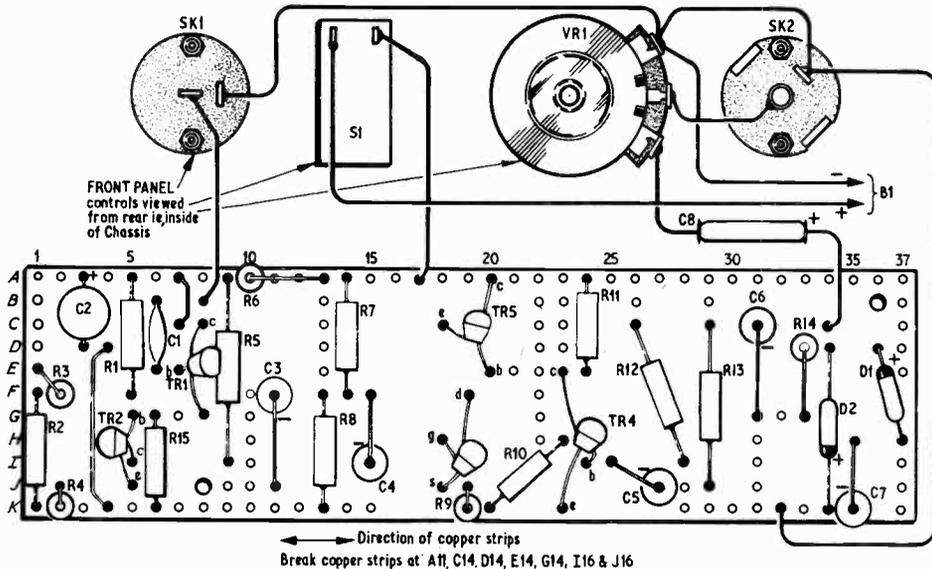


Fig. 3. Layout of the components on the Veroboard panel and interconnections to the other components. Note breaks in copper strips

## COMPONENTS . . .

### Resistors

R1 270k $\Omega$	R8 15k $\Omega$
R2 100k $\Omega$	R9 1.8k $\Omega$
R3 270k $\Omega$	R10 270k $\Omega$
R4 330 $\Omega$	R11 10k $\Omega$
R5 2.7k $\Omega$	R12 1.5M $\Omega$
R6 820 $\Omega$	R13 2.2k $\Omega$
R7 68k $\Omega$	R14 2.2k $\Omega$
	R15 100k $\Omega$

Miniature  $\frac{1}{4}$ W,  $\pm 10\%$

### Potentiometer

VR1 5k  $\Omega$  logarithmic

### Semiconductors


TR1, TR2, TR5 2N3708 (3 off)  
 TR3 PN3819  
 TR4 PN109 } (Arrow Electronics Ltd.)  
 D1, D2 OA91 or similar (2 off)

### Capacitors

C1 0.1  $\mu$ F disc ceramic  
 C2 100  $\mu$ F  
 C3 5  $\mu$ F  
 C4 8  $\mu$ F  
 C5 8  $\mu$ F  
 C6 16  $\mu$ F  
 C7 10  $\mu$ F  
 C8 8  $\mu$ F  
 All 10V electrolytic except C1
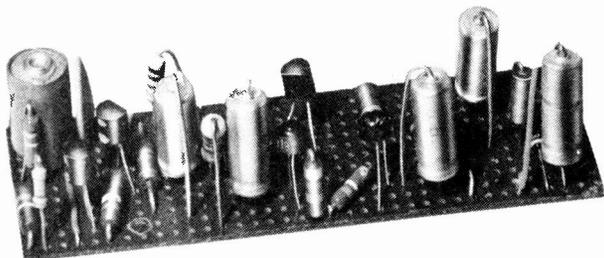
### Miscellaneous

S1 S.P.S.T. toggle switch.  
 Veroboard panel, 0.1in. matrix  
 7in  $\times$  4in  $\times$  1  $\frac{1}{2}$ in  
 Aluminium chassis with base plate (H. L. Smith and Co.)  
 SK1, SK2 phono sockets (2 off)  
 Control knob, 9V PP6 battery and clips to suit, hardware




## CONSTRUCTION

Constructional requirements will vary widely, as some constructors may wish to build the unit as an integral part of some piece of equipment, while others may wish to build it as a self-contained unit, as was the prototype. In either case the Veroboard layout shown in Fig. 3 can be used. 0.1in matrix board is used, and the copper strips run lengthwise. These are cut at a number of points as detailed in the diagram.

A 7in x 4in x 1.5in aluminium chassis fitted with a base plate is used as a case for the prototype. The Veroboard panel is mounted on stand-off insulators in order to hold it a little way clear of the metal case. A PP6 battery is used to power the unit, this particular type being a good fit in the case, and has virtually its shelf life with normal use.

Phono sockets were used for SK1, and SK2 on the prototype, but almost any type of two way socket is of course suitable. Due to the high input impedance of the unit it is essential that the input lead is screened, in order to avoid unwanted noise pick up.

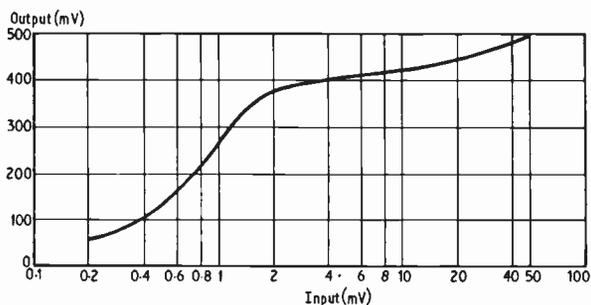

**Fig. 4.** Graph showing the relationship between the input and output voltages of the Audio Compressor. It can be seen that while the input changes from 2 to 50 millivolts the output only changes by 25 per cent

## RESULTS

A graph of the results obtained on the prototype compressor is shown in Fig. 4. This shows input voltage versus output voltage. With an input of 1mV or less the gain is fairly constant at about 275, or a little less. Above this the gain decreases slightly as the input voltage is raised, until it reaches about 2.6mV, and increasing the input voltage above this level has very little effect upon the output. ★

# INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

This is YOUR page and any idea published will be awarded payment according to its merits.

## LIGHT-OPERATED POWER CONTROLLER

THE circuit shown in Fig. 1 will control the a.c. power delivered to a mains load according to the level of light incident on a light-dependent resistor PCC1. An advantage of this circuit is its extreme simplicity and consequent ease of construction.

As the mains voltage rises the capacitor C1 is charged via the potentiometer formed by R1 and PCC1. When the voltage across C1 rises sufficiently, the bi-directional trigger diode D1 breaks down and C1 is discharged into the gate of the triac CSR1, switching it into its low resistance state. The combination of a 0.1μF capacitor and the breakover voltage of the diac of around ±30V gives a sufficient pulse to ensure the triggering of most commonly available triacs. The diac also ensures that the maximum voltage rating of the LDR is not exceeded. Since the triac and the diac are bi-directional this situation occurs on both positive and negative-going half-cycles of the mains supply, the triac returning to its high resistance state at each zero point in the cycle.

The point in each half-cycle at which the triac is fired is determined by the incident light on PCC1, full power being delivered to the load when this point occurs very early in the cycle—i.e. with the LDR in

## REED RELAY CURRENT TRIP

A SIMPLE over current protection device for a series regulated power supply can be made using a thyristor and a reed relay. The circuit diagram is shown in Fig. 1.

When a fault current appears across VR1 and R1, R2, diode D1 conducts a positive going signal to the gate of the thyristor CSR1 which triggers it on. The reed relay then closes applying a negative voltage to the base of TR1 cutting it off and reducing the output voltage to zero.

The action of this cutout is much faster than a fuse thus protecting the sensitive semiconductor in the circuit being supplied. The lamp LPI will show a fault condition until the SCR is shorted by S1. If the fault is still present the thyristor will fire cutting off the supply again.

The trip current is set by VR1. The reed relay is a miniature type about an inch long with 250 turns of 32 s.w.g. enamelled copper wire wound onto the reed relay body.

G. Daddy,  
Hull.


darkness. The power that can be controlled by the circuit depends only on the ratings of the triac and on the adequacy of its heat sink.

Components L1, L2, C2, R2 provide suppression of the radio interference generated by the switching of the triac and also protect the triac against mains-borne transients to which these devices are highly susceptible. Note that R2 is necessary to limit the discharge current of C2 which might otherwise exceed the peak surge current of the triac when it fires, and destroy it.


Owing to the triac's low tolerance to over-voltage transients, this circuit can not be recommended for use with motor loads without the incorporation of additional protection. If circuit values are altered, to change the light threshold or the operating range of the unit for example, care should be taken not to exceed the current/power ratings of the LDR, the diac and the triac gate.

Circuit values are such that incident daylight will result in no power being applied to the load, while the level of light around dusk will give full power.

I. Page,  
London, S.W.13.

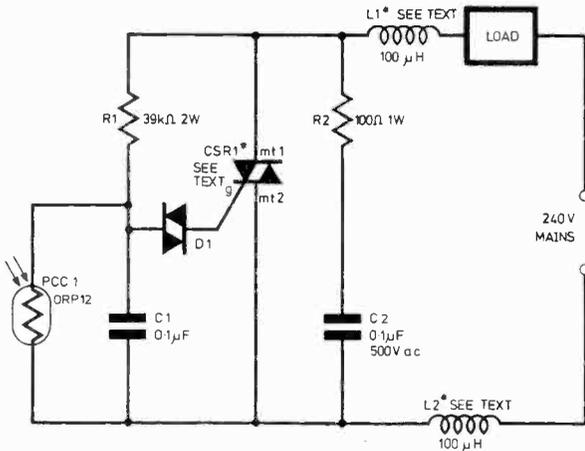

## REVERSING LIGHT WARNING

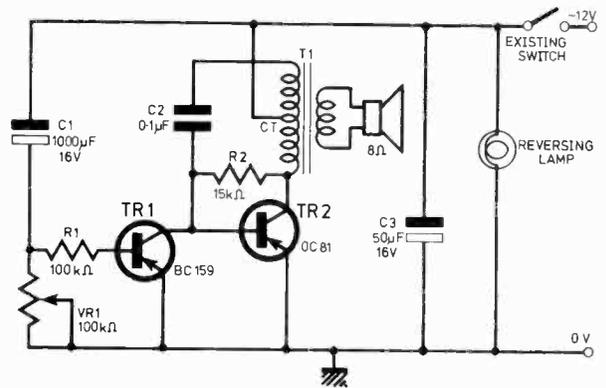


**M**ANY cars have reversing lights fitted which are operated by a switch on the dash; this must by law be illuminated, but I have found it quite easy to leave the switch on accidentally for periods during the daytime.

I therefore devised the circuit shown in Fig. 1. This is wired in parallel with the reversing light(s), and sounds a warning if left on for more than about a minute. When power is applied, C1 slowly charges up through VR1 and TR1, the latter remaining switched on until C1 is almost fully charged. TR2 is a conventional oscillator, but cannot operate until TR1 turns off, when it produces a fairly loud tone in the speaker.

Components are not critical. TR1 can be any silicon *pnp* transistor, and any of the OC72/75/81/82 range will work as TR2. Transformer T1 is a small audio output transformer out of an old transistor radio.

The circuit was made up on a small piece of tag-board, and mounted behind the dashboard.

D. L. Atkin,  
Sheffield.

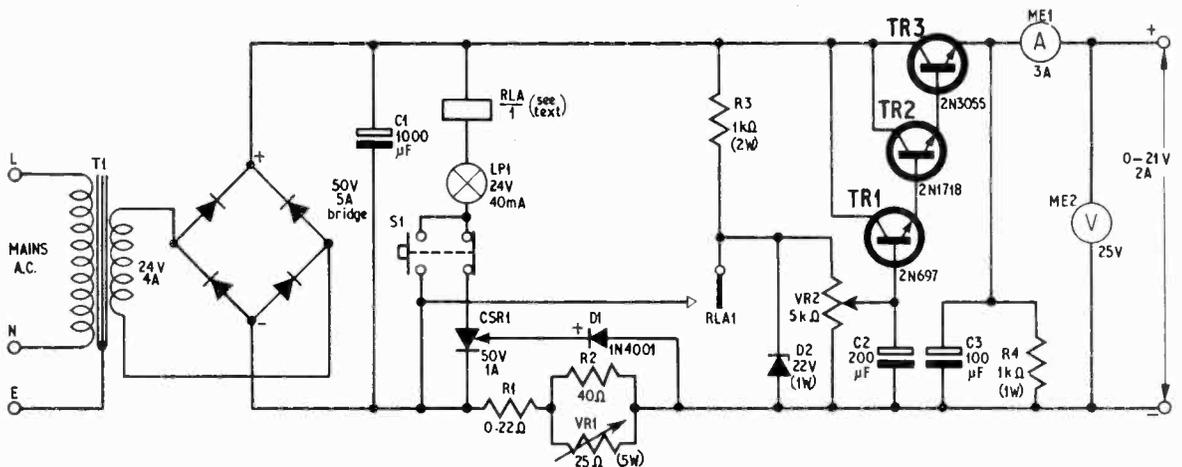

## SUN JOLTS THE EARTH

Solar storms release an enormous amount of energy which can affect the spin of the earth on its axis. Some ten years ago the French astronomer, A. Danjon, announced that the very large solar flare of 1959, significantly affected the length of the day. At that time he was not very well supported by colleagues.

However, the very energetic solar storm which occurred in August 1972 showed an even greater effect on the earth. A change of more than 10 milliseconds was recorded. This particular solar storm is the greatest that has been recorded during the 470 years that observations have been made.

The storm, which began on August 2, started with very pronounced sun spot activity and continued for a week. At that time there were probes orbiting the earth and sun and the Pioneer 10 spacecraft was on its way towards Jupiter. It was thus a time when an enormous amount of data was to hand to record the solar activity.

The recorded cosmic rays and the ejected plasma measurements have enabled an estimate to be made of the manner in which the magnetosphere is affected. The storm also gave a clue to the mechanism involved. There is always a short interval between the time of storm and the jolt that the earth receives. The theory is that the particles and the plasma disturb the atmospheric circulation, thereby affecting the earth's spin.

## CHANDLER WOBBLE

That the length of day is increasing has been known for a long time since it can be determined by observation. The main effect is from the tidal action between the sun-earth-moon system. Another condition that affects the length of day is the Chandler wobble.

Named after its discoverer, the poles of the earth wobble against the star background in a regular way over a period of fourteen months. The effect is by no means well understood but it is thought to be due to the fluidic centre core of the earth. The wobble effect on the slowing down of the earth's rotation is superimposed on the main tidal variation.

In addition to the Chandler wobble there is still another effect and that is the seasonal variation of the large scale atmospheric movements. Here again the actual mechanism is not fully understood though it is noted that this effect is on the same scale as that of the solar activity.



BY FRANK W. HYDE

## CHINOOK WINDS

The strong winds which blow on the eastern slopes of the Rocky Mountains are known as the Chinook winds and in some areas do much damage as there has been no way in which to predict when these winds will come. It is thought that the winds are related to the temperature inversion layer of the atmosphere on the windward side of the Continental Divide.

It is now thought that the Chinook wind of the Northern Plains is produced because the weight of the air causes a compression which in turn raises the temperature. While this is helpfully welcomed in some places it is not in others.

## EARLY WARNING

To provide some means of prediction, audio methods are being tried out and powerful audio pulses are being directed at the atmosphere. These pulses transmitted vertically upwards every twenty seconds, at a frequency of 1,000 Hz, are reflected by the inversion layers. High power is required because some of the temperature inversion layers are as high as 7,000 ft.

By using a doppler sounder it is hoped to measure the profiles of the winds. The very obvious advantage of this, in addition to warning, is the possible effects of pollution carried by air. Siting factories and other process plants could be predetermined and a possible reduction of pollution effects controlled.

## ASTERIODS

The earth seems to have a wider influence in the solar system than was first thought. There are from time to time reports that certain asteroids come close to the earth and but for the grace of cosmic law the home planet would be exposed to a catastrophe. It has now been established that certain of the asteroids are specifically involved.

The asteroids which have been the subject of special study are the Apollo group consisting of Toro and Geographos, which cross the earth's orbit, and three of the Amor group, Eros, Amor and Ivar, which cross Mars' orbit. These asteroids all have orbits round the sun but are perturbed in these orbits by the influence of the planets.

Of the five asteroids named Geographos is perturbed only at random. The others have regular periodical perturbations in respect of the earth's orbital period. The way in which this occurs is rather complex for there is libration in the sense that the whole pattern of the orbit rocks about the earth-sun line. Libration or rocking implies a periodic variation in the orbital period but the period can oscillate without libration.

## ORBITAL PERIODS

The periods that emerge are in the ratio five earth periods to eight Toro which would result in a period of 150 years were it not complicated by a relation with Venus. This ratio of 5 Venus periods to 13 Toro gives a 180 year period. The Toro orbit is therefore an unstable one and it is expected that this may change after 2200 A.D.

The complicated nature of these variations of one body relative to another is further indicated by the fact that the earth perturbs Eros once every seven years and also the asteroid Amor is involved. In the case of Ivar two perturbations take place in each 28 years. This has a libration of 300 years and is the most stable of the orbits.

## TAILPIECE

It seems that there is to be a further revival of the Velkovsky theories. Claims are being made as to confirmation of such events as the Jupiter radiations and the magnetic remanence in the older moon rocks with a suggestion that the main craters and valleys are no more than 300 years old.

At any rate no one can say that the astronomical world and that of space is dull.

# LARGE STOCKS, ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new and to makers' specifications.

# ELECTROVALUE

## Electronic Component Specialists

### TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power	60p
AC153K pnp germanium low power	32p
AC176K npn germanium low power	32p
AD161 npn germanium medium power	42p
AD162 pnp germanium medium power	40p
AF139 pnp germanium UHF	49p
NPN: BC107 13p, BC108 12p, BC109 13p, BC167 11p, BC168 10p, BC169 11p.	
PNP: BC177 21p, BC178 19p, BC179 21p, BC257 12p, BC258 11p, BC259 13p.	

Standard groupings available.

BD135 npn medium power	37p
BD136 pnp medium power	38p

### DIODES

OA90, OA91, OA95, 6p each; OA200, 9p; OA202, 10p.  
Other semiconductors: AC128, 17p; AF117, 32p; BFY51, 19p. Full lists and technical data will be found in Catalogue No. 6. See also amendments list.


### SIEMENS THYRISTORS

0.8A 400V 56p, 600V 70p.  
3A 400V 60p, 600V 88p.

**ZENER DIODES** full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

### DIN PLUGS AND SOCKETS

by Hirshmann, 4A rating

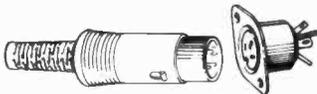


2 way LS —socket 10p, plug 12p  
3 way scr.—socket 10p, plug 12p  
5 way scr.—socket 11p, plug 15p

### TRANSISTOR ACCESSORIES

TO3 cover, 7p; Heat sinks 1°C/W, type 6W1, undrilled, 60p.
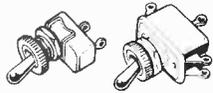
### SWITCHES

1011 SPST toggle, 20p; 409 DPDT toggle, 29p (these are chrome plated, 2.5A rating); 7201 sub-miniature DPDT 250V a.c./2A, 48p.




### ROTARY SWITCHES

Radiospares Miniature Maka-switch (in assembly kit form). Shaft, 48p. Wafers, MBB-2P5W, 1P11W; BBM1P12W, 2P6W, 3P4W, 4P3W, 6P2W, 32p each.

### WAVECHANGE SWITCHES

IP12W, 2P6W, 3P4W, 413W, 24p each.

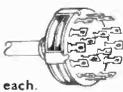

### ELECTROLYTIC CAPACITORS

Rated voltage:	3V	6.3V	10V	16V	25V	40V	63V	100V
Capacity $\mu$ F	0.47	—	—	—	—	—	10p	7p
	1.0	—	—	—	—	10p	10p	7p
	2.2	—	—	—	—	7p	7p	8p
	4.7	—	—	—	—	7p	8p	7p
	10	—	—	10p	—	7p	8p	7p
	22	—	—	7p	7p	7p	7p	9p
	47	7p	—	8p	8p	8p	7p	9p
	100	8p	7p	7p	7p	9p	11p	19p
	220	7p	8p	8p	8p	9p	10p	27p
	470	8p	9p	9p	10p	12p	17p	24p
	1,000	10p	12p	12p	17p	20p	24p	40p
	2,200	14p	17p	22p	25p	36p	40p	—
	4,700	25p	28p	37p	41p	54p	—	—
	10,000	40p	43p	—	—	—	—	—

Prices subject to amendment by the manufacturer.

### RESISTORS - 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99 (see note below)	100 up
C	1/20W	5%	82 $\Omega$ - 220K $\Omega$	E12	9	8	7.5
C	1/8W	5%	4.7 $\Omega$ - 470K $\Omega$	E24	1	0.9	0.75 nett
C	1/4W	5%	4.7 $\Omega$ - 10M $\Omega$	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7 $\Omega$ - 10M $\Omega$	E24	1.2	1	0.95 nett
C	1W	5%	4.7 $\Omega$ - 10M $\Omega$	E12	2.5	2	1.6 nett
MO	1/2W	2%	10 $\Omega$ - 1M $\Omega$	E24	4	3	2 nett
WW	1W	10%	0.22 $\Omega$ - 3.9 $\Omega$	E12	7	7	6
WW	3W	5%	1 $\Omega$ - 10K $\Omega$	E12	7	7	6
WW	7W	5%	1 $\Omega$ - 10K $\Omega$	E12	9	9	8

Codes: C = carbon film, high stability, low noise.  
MO = metal oxide, Electrofl TR5, ultra low noise.  
WW = wire wound, Plessey.


Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.)

Send S.A.E. for latest supplement of additional lines and price amendments to our No. 6 Catalogue
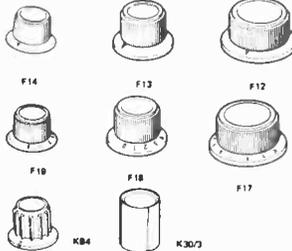
### KNOBS

All grub screw fitting for jin shafts. Black. For other types — see Catalogue No. 6, p. 54.  
F.14 (20mm) pack of 2, 32p; F.13 (26mm) pack of 2, 38p; F.12 (33mm) pack of 2, 40p; F.19 (20mm) pack of 2, 32p; F.18 (26mm) pack of 2, 38p; F.17 (33mm) pack of 2, 40p; K8.4 (20mm) pack of 4, 40p; K30/3 (17mm) aluminium, 24p each.




### POTENTIOMETERS

Rotary, carbon track, double wiper  
SINGLE P20 lin. 100  $\Omega$  to 2.2M  $\Omega$ , 12p; P20 log. 4.7K  $\Omega$  to 2.2 Meg. 12p; P20 log. 4.7K  $\Omega$  to 2.2M  $\Omega$ , 12p; Dual gang lin. 4.7K  $\Omega$  to 2.2M  $\Omega$ , 42p; Dual log. 4.7K  $\Omega$  to 2.2M  $\Omega$ , 42p; Log/antilog, 10K, 22K, 47K, 1M  $\Omega$  only, 42p; Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.  
Only decades of 10, 22 and 47 available in ranges quoted.

DUAL CENTRIC DP20 in any combination of 20 values, 60p; with switch, 72p. SLIDER  
Lin. or log. 10K to 1 meg. in all popular values, each 26p.  
Control knobs blk./white/red/yel./gr./blue/dk. grey/lt. grey, 5p each.

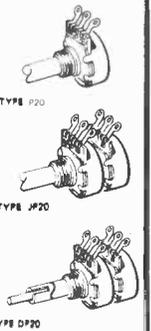CARBON SKELETON PRESETS  
Small high quality, PR lin. 100  $\Omega$ , 220  $\Omega$ , 470  $\Omega$ , 1K, 2K, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M  $\Omega$ . Vertical or horizontal mounting, 5p each.



### TRANSFORMERS—MAINS

MT3 30V/2A plus 4 taps	£2.85
MT103 50V/1A plus 4 taps	£2.55
MT104 50V/2A plus 4 taps	£3.50
MT127 60V/2A plus 4 taps	£3.80
13T05 13V/1A, CT	£1.25
28T05 12 + 12V, 2.0-2V.	£1.65

### IT'S ALL IN THE LATEST ELECTROVALUE CATALOGUE

No. 6 (4th printing) contains details of 100's of semiconductors; ICs with circuit diagrams, R's and C's of practically every kind, accessories, components, tools, materials, etc., information and equivalent tables, etc. Well illustrated (96 pages, 5 1/2" x 8 1/2") 25p post free with refund voucher for 25p allowable on orders over £5 or more.

with  
25p  
refund  
voucher

### DISCOUNTS


All items offered for sale in accordance with our stated terms of business, copy of which available on request.  
Not allowed on nett price items. 10% on orders for £5 or more. 15% on orders of £15 or more. Prices subject to alteration without prior notice. Prices quoted D.O. NOT include V.A.T. Orders received from U.K. customers must be accompanied by an additional 10% of the nett value for V.A.T.  
Overseas orders are exempt.  
POSTAGE AND PACKING FREE  
SURCHARGE 10p on small mail orders under £2.  
Overseas orders carriage and insurance charged at cost.

# ELECTROVALUE

(Dept. PE8), 28 ST. JUDE'S ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB  
Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 3603 Telex 264475  
Eng. Reg. No. 1047768 Registered Office: 28 St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB
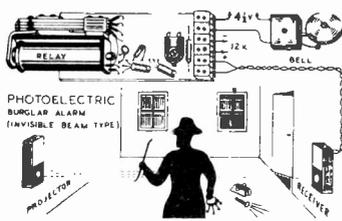
# PHOTOELECTRIC KIT

CONTENTS: P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation with a few additional components.



**PHOTOELECTRIC KIT**  
**£2.85**

Postage and Pack. 15p (U.K.)  
Commonwealth  
SURFACE MAIL 25p  
AIR MAIL £1.40  
Australia, New Zealand,  
S. Africa, Canada and U.S.A.  
Also Essential Data Circuits  
and Plans for Building  
10 Advanced Designs

## INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photocell Receiver (as illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks. Infra-red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price £1.45. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

## LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £2.10. Postage 15p (U.K.). Commonwealth: Surface 20p, Air Mail £1.15.

## BIOFEEDBACK AMPLIFIER KIT

Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brainwaves, learn to relax, meditate, etc.

CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C., Electrodes, Leads, Chassis, Case, Batteries, Plans and Instructions. Price £4.75 postage and pack. 25p (U.K.). Commonwealth: Surface 30p. Air Mail £1.

## ALPHA-BETHA-THETA BRAINWAVE MONITOR KIT

Aural Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.

CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis, Case, Earphone, Battery, Plans and Instructions. Price £3.25, postage and pack. 15p (U.K.). Commonwealth: Surface 25p. Air Mail 75p.

**YORK ELECTRICS** Mail Order Dept.

335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects

# FERRANTI

## ZN414 Radio i.c.

only **£1.32** WITH DATA

WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS

BFS59	15p	ZTX310	9p	ZTX504	43p	ZS170	10p
BFS60	20p	ZTX311	10p	ZTX510	17p	ZS171	13p
BFS61	20p	ZTX312	10p	ZTX530	21p	ZS172	16p
BFS96	15p	ZTX313	11p	ZTX531	22p	ZS174	17p
BFS97	23p	ZTX314	13p	ZTX550	17p	ZS176	23p
BFS98	20p	ZTX320	31p	ZTX551	17p	ZS178	38p
ZTX107	9p	ZTX330	15p	2N3055	72p	ZS270	11p
ZTX108	8p	ZTX331	16p	* DIODES *		ZS271	16p
ZTX109	11p	ZTX382	13p	ZS120	8p	ZS272	18p
ZTX212	14p	ZTX383	15p	ZS121	10p	ZS274	19p
ZTX213	14p	ZTX384	18p	ZS122	13p	ZS276	26p
ZTX214	15p	ZTX450	17p	ZS123	16p	ZS278	37p
ZTX300	12p	ZTX451	17p	ZS124	18p	* ZENERS *	
ZTX301	13p	ZTX500	12p	ZS140	25p	KS030A to	
ZTX302	17p	ZTX501	13p	ZS141	43p	KS180A—	
ZTX303	14p	ZTX502	17p	ZS142	33p	all types 19p	
ZTX304	21p	ZTX503	14p	ALL DEVICES TOP GRADE, BRAND NEW, AND FULLY GUARANTEED			

WE CAN SUPPLY ANY FERRANTI DEVICE. Send S.A.E. for quotation

PRICES SLASHED! RCA CA3090Q £3.25; CA3075 99p. Limited quantity only.


P. E. Triffid. ZT1711 24p; 2N1132 25p.  
POSTAGE AND PACKING 10p—Free over £2. Send S.A.E. for our full price list and data sheet.

ALL PRICES INCLUDE V.A.T.

**DAVIAN ELECTRONICS**

PO BOX 38 OLDHAM, LANCS. OL2 8XJ

# HOME RADIO COMPONENTS

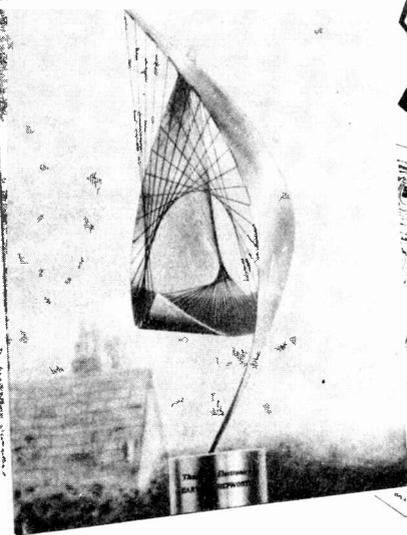

250 pages 11 1/4" x 8 1/2"

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

# The Catalogue you MUST have!

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Only 55p.

plus 22p POST AND PACKING

**POST THIS COUPON**  
with cheque or P.O. for 77p.

Name \_\_\_\_\_

Address \_\_\_\_\_

HOME RADID (Components) LTD. Regd. No. 912966 London  
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

# Strictly

by K. Lenton-Smith

THE piano, without which no home was complete several decades ago, is now becoming a rarity because of lack of living room space and other home entertainment attractions. This could be one of the reasons that the guitar is often the choice of younger members of the household.

For those wishing to take up a keyboard instrument, the Electric Piano is ideal as it occupies very little room.

## ELECTRIC PIANO

The majority of these instruments suffer from only one disadvantage musically in that the keyboard is usually a standard five octave (organ) manual, against the seven octaves of a conventional piano. Nevertheless, five octaves are probably sufficient for performing many piano pieces. The cost of a compact electric piano may be well under £200 and, with pre-amplified output, it is small enough to be easily carried in one hand.

The percussive attack of a conventional piano will readily penetrate a semi-detached house's party wall; the volume of its electronic counterpart may be closely controlled. Ear-phones may be used for practising late in the evening. The electric piano allows changes of timbre, such as harpsicord, honky-tonk, etc.

Like the majority of commercial electronic organs, the generated waveform is square. The usual arrangement is a Hartley (sine wave) oscillator, followed by a series of Eccles-Jordan frequency dividers (square wave) for each of the 12 chromatic notes of the scale. The dividers are invariably integrated circuits as these are cheaper and smaller than discrete components and there is a saving in labour costs.

Piano tuners introduce small frequency variations to give an ordinary piano added brilliance: from middle "C", notes above are progressively sharpened slightly, those below flattened. A system of electronic frequency division—where tuning must be mathematically accurate—would thus not appear to be ideal. In practice, however, this discrepancy is not noticeable and, given a good amplification system (which could well be the domestic hi-fi), a most realistic piano results.

## KEYING METHODS

Diode-keying is normally used in electric pianos as this keying method can produce the attack/decay characteristics of a piano fairly closely. Keying transients are practically eliminated by diode-keying and precious metal keyswitches are not vital.

Some instruments employ a changeover keyswitch where a capacitor is kept charged while the key is at rest, depression of the key connecting the charged capacitor to the gating circuit. Filtering is required to round up the square waveform somewhat, usually in the form of a passive low pass filter for "piano" tone.

The keyboard may be split by a special control so that a "walking bass" may be played without drowning the melody line. The Italian-made "Instapiano" is an attractive example, retailing at about £160 before VAT. It measures approximately 48in × 10in × 4in.

## PLAYING TECHNIQUE

The electric piano has a number of advantages, not least that there is plenty of published piano music available. Though it may take a little getting used to, pianists have no difficulty in accustoming themselves to the electric piano.

Where two manuals and a pedal clavier are concerned, printed music is not so readily available—unless the player particularly likes Bach and Handel.

The pianist who turns to the organ has some formidable problems: as long as a note is held it will sound,

unlike the automatic decay of the piano/electric piano. Thus, attempting to play piano scores on an organ results in disaster—and what does one do with the pedals except "double" the left hand part?

Any constructional project is a challenge to get the beast working! Those who build musical instruments have a further challenge: they have to master the keyboard, and organists who like lighter music will find three-stave scores few and far between.

## CHORD SYMBOL BASIS

A number of readers will have built the P.E. Organ, or have access to an organ, and may have experienced difficulty buying music. The usual light music score includes the piano part, guitar symbols, vocal line and chord symbols; the last two are the important items for the organist. With practice, it is possible to play both manuals and pedals using this information only, on sight.

Memorising what each chord symbol involves might, at first, appear to be a mammoth task. Relatively few key signatures are used in popular music as the publishers have to bear in mind the transposing instruments (normally B flat and E flat) which may be involved. The same chords appear frequently and can be memorised as easily as the resistor colour code! But it must be admitted that the "bridge" often moves into a strange key and demands quick thinking.

The right hand part (melody) should be registered in a way that makes the tune fairly incisive; single notes are often sufficient and, where chords are used, the melody should still stand out.

The left hand part is the problem and should be considered along with the pedals; accompaniment registration should be quieter and less clear cut than the upper manual. The root of the chord symbol can be used for the pedal on the downbeats, at least for a start, alternating with the fifth (i.e., C—G) except where a diminished chord is indicated. The left hand plays the notes indicated by the chord symbol, according to the time signature and rhythm, using an "anchor note" if possible.



## THE GOOD COMPANIONS

Two magazines designed to complement each other in every way—together satisfying the needs of everyone involved in electronics.

# PE

*Everyday Electronics* caters especially for the newcomer to this field, and shows, in full detail, how to build many simple and useful items; it also offers advice and facts on constructional methods and component purchase, and explains circuit operation in straightforward terms.

This month *EE* features the construction of a Waa-Waa Pedal, a Slave Flash for photographers, and an Electronic Doorbell.

It's all quite simple with *Everyday Electronics*. August issue on sale Friday, July 20. 15p.

# PE Sound Synthesiser 7

## REVERBERATION AMPLIFIER

## RING MODULATOR

## PEAK LEVEL METER

By G.D. SHAW



**T**HIS month the Ring Modulator, Peak Level Meter circuit and Reverberation Amplifier will be described.

### THE RING MODULATOR

With the ring modulator the combination of tones follows a complex inter-relationship in which each frequency is continuously compared with and modified by the other. The resultant output provides a tone which consists of the sum and difference of the two constituent frequencies appearing at the same time and irrespective of the phase angle relationship. A typical output waveform is illustrated in Fig. 7.1.

A simplified version of a transistorised ring modulator manufactured in integrated circuit form by Silicon General, the SG3402N, is shown in Fig. 7.2 and it will be seen that the device consists essentially of a pair of cross-coupled differential pairs jointly controlled by a third. Two inputs—carrier and modulator—are required and it is important to differentiate between them since the input characteristics are dissimilar. Application of equal amplitude signals to both inputs will provide an output showing about 3dB voltage gain over either input. Removal of the modulator with the carrier still applied will result in attenuation of the output signal by about 50dB but if the input situation is reversed the output attenuation is only about 35dB.

Although designed primarily for communications work the SG3402N is capable of working satisfactorily at quite low audio frequencies by the simple expedient of increasing the value of the input and decoupling capacitors.

The frequency response of the prototype Ring Modulator is shown in Fig. 7.3 and will be seen to be effectively flat over most of the audio frequency spectrum. The theoretical circuit is shown in Fig. 7.4.

The maximum input signal to the SG3402N should not normally exceed 50mV and thus resistive attenuators are employed to raise the signal level, at the input sockets, to one more compatible with the signal level normally routed around the Synthesiser. With the value of resistors employed in the attenuators the maximum input signal at the sockets is thus 500mV.

IC2 serves to amplify the output to about 1.5V at the rated input levels and measured at an input frequency to both channels of 1kHz. The ring modulator shares a circuit board with the peak level meter and the board layout is shown in Fig. 7.5.

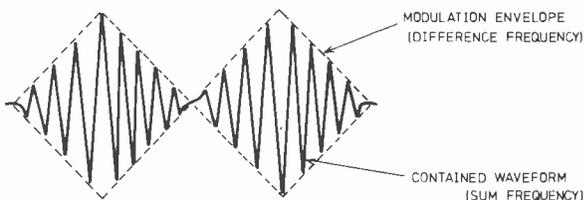


Fig. 7.1. Typical output waveform of the Ring Modulator

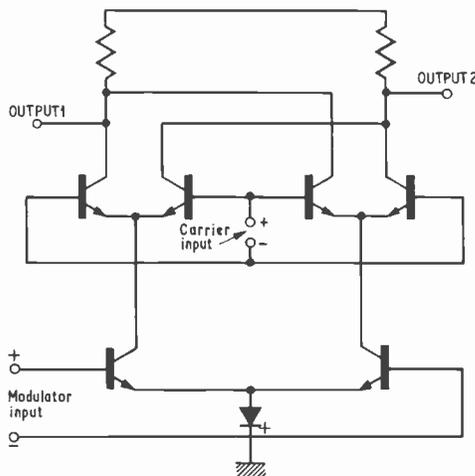


Fig. 7.2. Schematic of a transistorised Ring Modulator

## RANGE OF SOUNDS PRODUCED

The type of modulation produced by the ring modulator is wholly unique and thus also is the range of sounds which can be achieved. If two pure tones are modulated together and one of them is reduced in frequency the resultant output would follow the pattern shown in the table below which relates the sum and difference output frequencies with the carrier and modulator input frequencies.

	Frequency (Hz)						
<b>Carrier</b>	700	600	500	400	300	200	100
<b>Modulator</b>	400	400	400	400	400	400	400
<b>Sum</b>	1100	1000	900	800	700	600	500
<b>Difference</b>	300	200	100	0	100	200	300

It can be seen that, whereas the resultant sum reduces in frequency at the same rate as the carrier, the frequency reduces until it reaches zero (carrier and modulator frequencies equal) and then, as the carrier continues to fall to a frequency lower than that of the modulator, the difference frequency begins to increase at a proportional rate.

When the inputs to the Ring Modulator carry harmonics in addition to the pure tones then further series of frequency relationships are established for each of the component harmonics relative to one another and to the respective fundamentals.

When the inputs to the Ring Modulator are of symmetrical triangular waveform, such as those generated by the v.c.o., an extremely complex set of frequency relationships is established due to the fact that, in common with the square wave, the triangular waveform consists of a long series of odd harmonics.

## SOUNDS PRODUCED

The Ring Modulator may be used in many fascinating ways from the creation of truly "out of this world" sounds, the transposition of tones, bell-like sounds, Dalek voices and so on.

In the transposition of tones the only stipulation is that the modulating frequency should be higher than the carrier (this latter input consisting of the signal for treatment). For any range of carrier frequencies the modulator frequency has to be calculated or determined empirically, to provide the best overall effect.

An interesting experiment can be carried out by cascading two Ring Modulators. The first uses the v.c.o. output to drive carrier and modulator inputs so that the output is the octave, or second harmonic, of the v.c.o. frequency. The output of the first Ring Modulator is used to drive the modulator input of the second whilst the carrier input is derived direct from the v.c.o. Thus the difference frequency of the second Ring Modulator will follow, exactly, the performance of the v.c.o. while the sum frequency will approximate to a quarter-tone accompaniment about  $1\frac{1}{2}$  octaves higher. There are very wide possibilities for further experiment in this kind of mode.

A true bell tone is very complex and is difficult to imitate with exactitude. A fairly close approximation may be achieved by adjusting two v.c.o.s to a mid-range frequency, say 4kHz, such that there is a slow beat between them. One v.c.o. then drives the carrier and the other v.c.o. the modulator input of the Ring Modulator. A very important characteristic of the bell-like sound lies in its envelope presentation and this will be dealt with in detail in next month's article.

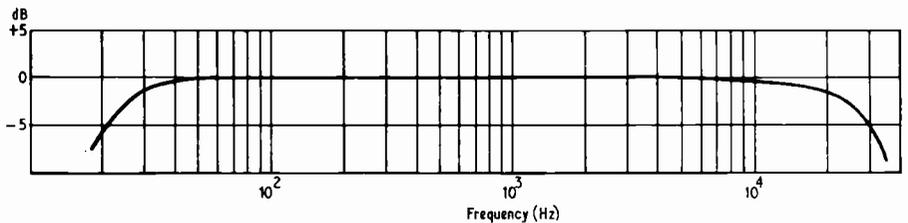


Fig. 7.3. Frequency response of prototype Ring Modulator

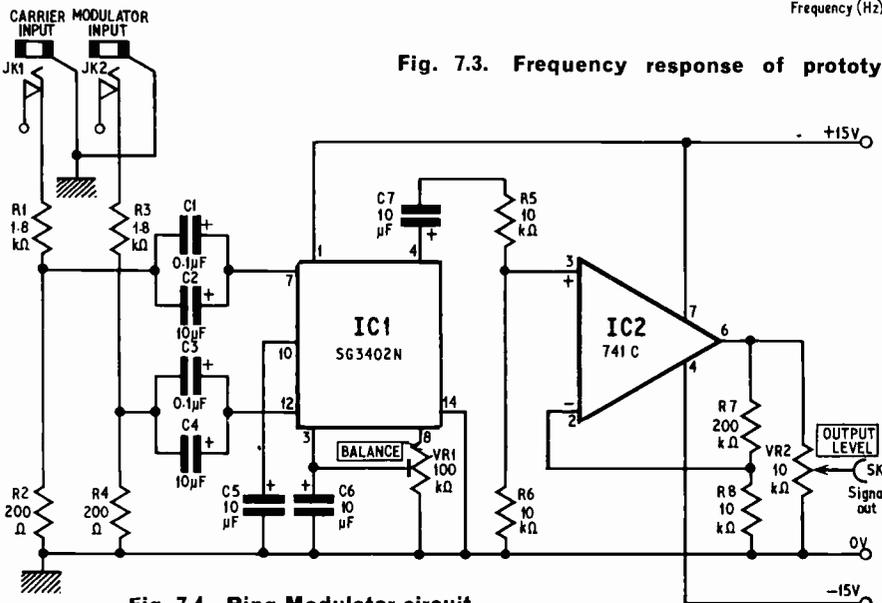


Fig. 7.4. Ring Modulator circuit

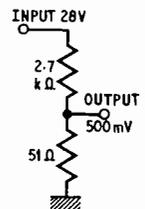


Fig. 7.5. Simple resistive attenuator for use with the Ring Modulator

# PEAK LEVEL METER

# RING MODULATOR

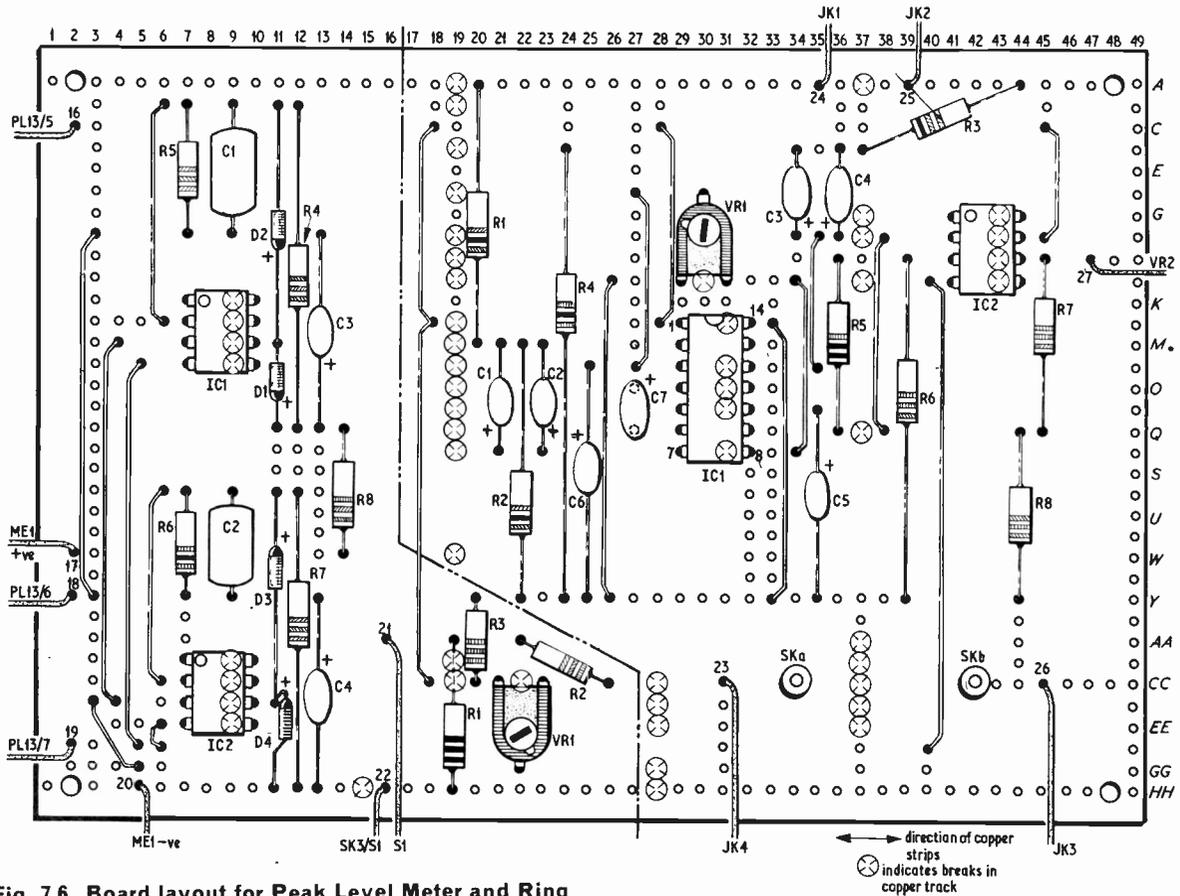


Fig. 7.6. Board layout for Peak Level Meter and Ring Modulator

## COMPONENTS . . .

### PEAK LEVEL METER CIRCUIT

#### Resistors

- R1 91k  $\Omega$
- R2-R3 20k  $\Omega$  (2 off)
- R4 91k  $\Omega$
- R5-R6 3.3k  $\Omega$  (2 off)
- R7 91k  $\Omega$
- R8 110k  $\Omega$
- All 5%  $\frac{1}{2}$  watt carbon

#### Capacitors

- C1-C2 1,500pF (2 off)
- C3-C4 22 $\mu$ F 16V tantalum

#### Potentiometers

- VR1 50k  $\Omega$  carbon preset

#### Diodes

- D1-D4 IN914 (4 off)

#### Integrated Circuits

- IC1-IC2 741C (2 off)

#### Miscellaneous

- ME1 MR38P SEW panel meter (G. W. Smith Ltd.)
- SK3 2mm miniature socket

### RING MODULATOR

#### Resistors

- R1 1.8k  $\Omega$
- R2 200  $\Omega$
- R3 1.8k  $\Omega$
- R4 200  $\Omega$
- R5 10k  $\Omega$
- R6 10k  $\Omega$
- R7 200k  $\Omega$
- R8 10k  $\Omega$

All 5%  $\frac{1}{2}$  watt carbon

#### Capacitors

- C1 0.1 $\mu$ F 35V
- C2 10 $\mu$ F 16V
- C3 0.1 $\mu$ F 35V
- C4-C7 10 $\mu$ F 16V (4 off)

All tantalum

#### Potentiometers

- VR1 100k  $\Omega$  carbon preset
- VR2 10k  $\Omega$  miniature moulded carbon

#### Integrated Circuits

- IC1 SG3402N
- IC2 741C

#### Miscellaneous

- JK1, JK2 3.5mm miniature jack sockets (2 off),
- SK1 2mm miniature socket, Veroboard as required

### 2N414 £1.25 POST FREE

The I.C. Radio in a TO18 can. Supplied complete with data sheet No. 10 which contains specification, circuit and details and prices of components such as ferrite rods, compression trimmers etc.

#### I.C. Sockets

Dual-in-line or Zig Zag (Quilt). 14 and 16 pin  
Our Price 1p per pin

### VDR's & Thermistors

A15B 75p	GL23 £1 00	VA1005 15p
CZ1 15p	R53 £1 32	VA1026 13p
CZ4 13p	R54 £1 46	VA1033 13p
CZ13A 13p		VA1040 10p
E298 ED/A258 10p		VA1053 10p
E298 ZZ/06 10p		VA1055S 10p
GL16 £1		VA1034 10p

### Potentiometers



5KΩ	50KΩ	500KΩ	
10KΩ	100KΩ	1MΩ	
25KΩ	250KΩ	2MΩ	

log or lin less switch (& 1KΩ lin) 12p  
log or lin with switch 24p  
dual less switch 40p  
log only 52p  
10K log 10K antilog less switch 40p

### Capacitors

disc ceramic		low voltage	
01μF 18v	5p	0.1μF 30v	5p
022μF 18v	5p	0.22μF 6v	5p
047μF 12v	5p	0.47μF 3v	5p
ceramic plate		30V	
1000pf	10p	4700pf	10p
2200pf	10p	10,000pf	10p

### Slider Pots

Single	Dial	log	or
10K	10 + 10K		lin
25K	25 + 25K		
50K	50 + 50K		
100K	100 + 100K		
30p	50p	10p.	

Knobs

### Resistors

1/2 watt 5% Carbon Film low noise Hi Stabs

All E24 values 1p each plus p. & p. 7p for up to 50 Resistors and a further 2p for each additional 50. Deduct 33% for 100 of one type or 25% for mixed orders over £1 in value

1 W 10% Carbon Composition 3p each  
2 W 10% Carbon Composition 6p each  
2 W 5% Wire wound 9p each  
5 W Wire wound 9p each  
10 W Wire wound 10p each  
plus p. & p. 7p for up to 25 resistors plus 1p for each additional 25

### Eliminators



6 volt → 50mA £1 50  
9 volt → 50mA £1 50  
6 volt 50mA £2 50  
9 volt 50mA £2 50  
7 1/2 volt for cassette recorders £2 00  
6.75 or 9 volt £3 00  
3.45, 6.75, 9, 12 or 500mA (illus.) £3 99  
Car Battery Converter fully stabilised to provide 6, 7 1/2 or 9 volts (p. & p. 15p on all types) £4 99

**NEW LISTS**  
LOUDSPEAKERS No. 4  
COILS AND INDUCTORS No. 5  
TRANSFORMERS No. 6  
(postage 5p)

### Diodes & Rectifiers

AA119 9p	BA156 15p	BY176 £1 50
AA120 9p	BA243 56p	BY182 £1 50
AA129 9p	DA47 10p	BY250 23p
BA102 25p	OA79 9p	IN4001 6p
BA115 17p	OA90 7p	IN4002 7p
BA130 10p	OA91 7p	IN4003 8p
BA145 20p	OA200 10p	IN4004 8p
BA148 20p	BY100 15p	IN4005 10p
BA154 13p	BY126 15p	IN4006 12p
BA155 14p	BY127 15p	IN4007 15p

### SGS

EA1000

3 Watt Audio Amplifier  
Our Price inc. handbook £2 49

5 Watt Audio Amplifier  
Our Price £3 99  
Less quantity discount



**FM TUNER**  
chassis fully transistorised 9 volt operation. OUR PRICE £4 97  
Ask for model list No. 11

### Presets

Vertical or Horizontal

0.1 watt 5p	0.25 watt 7p		
100 1KΩ	10KΩ	100KΩ	1MΩ
250 2.5KΩ	25KΩ	250KΩ	2.5MΩ
500 5KΩ	50KΩ	500KΩ	5MΩ

Ceramic - plate 63V (C333)

1 8pf	8.2pf	33pf	120pf
2 2pf	10pf	33pf	150pf
3 3pf	11pf	47pf	180pf
3 9pf	15pf	56pf	220pf
4 7pf	18pf	68pf	270pf
5 6pf	22pf	82pf	330pf
6 8pf	27pf	100pf	

mylar film: 100V

10000pf 2p	0.1μF 3p	0.68μF 4p
20000pf 2p	0.2μF 3p	1μF 5p
50000pf 2p	0.4μF 3p	2μF 5p
	0.5μF 3p	

polystyrene 160V

10pf to 10,000pf in multiples of 10, 15, 22, 33, 47 & 68. 3p each

metallised polyester 250V (C280)

0.1μF 3p	0.68μF 3p	47μF 8p
0.15μF 3p	15μF 4p	68μF 11p
0.22μF 3p	15μF 4p	1μF 13p
0.33μF 3p	22μF 5p	1.5μF 20p
0.47μF 3p	33μF 6p	2.2μF 24p

metallised polyester 400V (C281)

0.1μF 4p	0.47μF 6p	22μF 10p
0.15μF 4p	0.68μF 6p	33μF 14p
0.22μF 4p	1μF 7p	47μF 15p
0.33μF 5p	1.5μF 8p	

silvered mica 1% (>50pf) 500V

2 2pf-820pf 7p	4 7nF-5600pf 19p
1nF-2.2nF 9p	6800pf-0.1μF 29p
2 7nF-3.6nF 16p	


mixed dielectric 600V

0.1μF 7p	0.47μF 7p	22μF 16p
0.22μF 7p	0.68μF 8p	47μF 24p
0.33μF 7p	1μF 8p	1μF 33p

# CHROMASONIC electronics

Please add 10% V.A.T. to your total order

### Heat Sinks

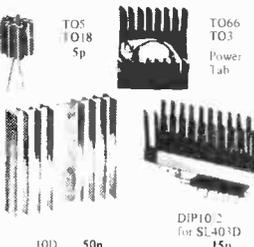

TO5 TO18 5p  
TO66 TO3 14p  
TO18 TO3 15p  
Tah 13p

DIPILO 2 for SL401D 15p

IOD 50p

### Transistors & Integrated Circuits

AC107 25p	BC147 10p	BF196 15p	OC81 19p	2N1304 22p	2N5172 15p
AC126 17p	BC148 10p	BF197 15p	OC140 20p	2N1711 25p	BZV88 10p
AC127 15p	BC149 10p	BF272 53p	OC170 23p	2N1983 30p	ZENERS SERIES / ea.
AC128 15p	BC157 12p	BFY50 24p	OC171 30p	2N2926 10p	LO8T1 £1.50
AC176 15p	BC158 10p	BFY51 21p	TX107 15p	2N3053 23p	LO8T1 £1.50
AC187 25p	BC159 12p	BRV39 36p	TX108 15p	2N3054 50p	LO3T1 £1.50
AC187K 25p	BC169 15p	BSX21 26p	TX209 15p	2N3055 49p	MC1303 £1.75
AC188 25p	BC268 15p	BSY95A 14p	TX200 12p	2N3102 12p	MC1330 8p
AC188K 25p	CD155 87p	BU105/02 £1.75	TX201 15p	2N3103 12p	MC1351 £1.00
ACV20 25p	BD131 70p	MJ340 67p	TX202 20p	2N3104 10p	MC1351 £1.00
AD140 40p	BD132 70p	MPE192 40p	TX203 20p	2N3105 10p	MC1352 £1.00
AD149 40p	BD133/2M.P.	MPE193 37p	TX204 25p	2N3106 10p	MFC000B 49p
AD181 40p		MPE194 37p	TX2341 20p	2N3107 15p	MFC010A 35p
AD182 60p		MPE195 40p	TX2500 15p	2N3108 12p	LM880 £1.45
AF114 15p	BF167 20p	MPE196 45p	TX2501 15p	2N3109 12p	SL401D £1.50
AF115 18p	BF173 20p	OC28 40p	TX2502 20p	2N3110 12p	SL401G £1.50
AF116 18p	BF180 25p	OC35 40p	TX2503 12p	2N3111 12p	SL401H £1.50
AF117 18p	BF181 30p	OC44 15p	TX2504 50p	2N3819 35p	SL401I £1.50
AF139 28p	BF184 25p	OC45 15p	TX2531 25p	2N3903 15p	UA709C 34p
BC107 10p	BF185 25p	OC71 11p	2N697 18p	2N3904 17p	UA710 45p
BC108 10p	BF194 15p	OC72 11p	2N706 12p	2N3905 21p	UA722C 95p
BC109 10p	BF195 15p	OC76 15p	2N708 15p	2N3906 12p	UA741C 47p

### Mixed dielectric 1000V

10000pf 6p	6800pf 9p	1μF 12p
22000pf 6p	0.1μF 9p	22μF 22p
33000pf 6p	0.22μF 9p	47μF 30p
47000pf 6p	0.47μF 12p	

Ceramic

12KV d.c.	8KV d.c.	HI-K 750V
10pf 9p	200pf 9p	1000pf 5p
15pf 9p	220pf 9p	1500pf 5p
22pf 9p	250pf 9p	2000pf 5p
68pf 9p	270pf 9p	3000pf 5p
82pf 9p	30pf 9p	5000pf 5p
100pf 9p	750V DISC	10,000pf 5p
120pf 9p	470pf 5p	feed
140pf 9p	1000pf 5p	through
150pf 9p	5000pf 5p	
180pf 9p	10,000pf 5p	1000pf 5p

### Veroboard

Copperclad Plain

0.1"	0.15"	0.15"
------	-------	-------

2 1/2" x 1"	6p	6p
2 1/2" x 3 1/2"	20p	16p (9)
2 1/2" x 5"	24p	21p (7)
3 1/2" x 3 1/2"	24p	21p (8)
3 1/2" x 5"	27p	27p (10)
1 7/8" x 2 1/2"	67p	50p
1 7/8" x 3 1/2"	90p	70p
1 7/8" x 5"		75p

Spot-face Cutter 36p  
Pin Insertion Tool 47p  
Terminal Pins 18p per pack of 36

**NEW LISTS**  
BOXES, CHASSIS, etc. No. 7  
TRANSISTORS, I.C.'s, etc. (soon)  
(postage 5p)

### Aluminium Boxes

Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2 1/2"	5 1/4"	1 1/2"	35p	8p
(8)	4"	4"	1 1/2"	35p	8p
(9)	4"	2 1/4"	1 1/2"	35p	8p
(10)	4"	5 1/4"	1 1/2"	40p	8p
(11)	4"	2 1/4"	2 1/2"	35p	8p
(12)	3"	2"	1 1/2"	32p	9p
(13)	6"	4"	2"	50p	10p
(14)	7"	5"	2 1/2"	58p	12p
(15)	8"	6"	3"	75p	16p
(16)	10"	7"	3 1/2"	85p	20p

### ADCOLA INVADER



Coax Plug 8p  
Coax (Flush) Socket 8p  
Coax (Surface) Socket 8p  
Phono Socket 4p  
Din Plug 15p  
Din Socket A, B, C 8p  
Phono Plug 5p  
Insulated TERMINALS 13p each  
Loudspeaker Plug 10p  
Loudspeaker Socket 10p

Available in Red, Black, Green, White, Yellow, Blue and Grey

4mm PLUG Stackable same colours (except Grey) as terminals

ROTARY MAINS 25p  
SINGLE WAFER ROTARY 25p  
SLIDE D.P.D.T. 17p  
TOGGLE 5 P.S.T. 250V 1A 18p  
TOGGLE D.P.D.T. 250V 1A 20p

Sovbit Solder Dispenser Contains 12 ft. of colled 18 l.w.g. Enzin Multi-core Sovbit Alloy 18p each


### Mullard B Siemens Electrolytics

CAP μF	VOLTAGE			
	4	6.3	10	15 25 40 63
1.5	—	—	—	6p
2.2	—	—	—	6p
3.3	—	—	—	6p
4.7	—	—	—	6p
6.8	—	—	—	6p
10	—	—	—	6p
15	—	—	—	6p
22	—	—	—	6p
33	—	—	—	6p
47	6p	—	—	6p
68	—	—	—	10p
100	6p	—	—	6p
150	—	—	—	6p
220	6p	—	—	6p
330	6p	—	—	6p
470	—	—	—	12p
680	—	—	—	12p
1000	10p	—	—	12p
1500	—	—	—	15p
2200	—	—	—	15p
3300	—	—	—	15p
4700	21p	—	—	15p

Quantity Prices on application

### Hi-Volt Electrolytics

1 2.4 8μF 450V	14p	32μF 450V	20p
16μF 450V	5p	50μF 350V	20p
8 8μF 450 V	18p	32 32μF 350 V	25p
8 16μF 450 V	20p	32 32μF 450 V	43p
16 16μF 450 V	25p	50 50μF 350 V	35p

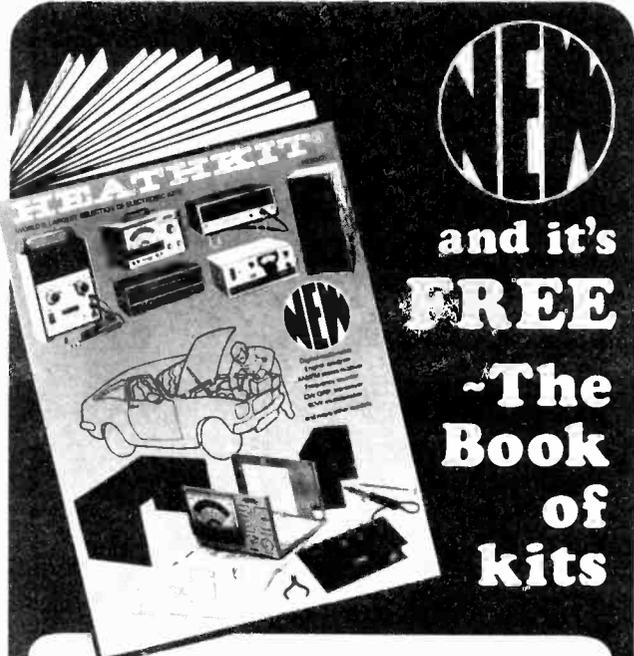

**NEW**  
and it's  
**FREE**  
-The  
**Book**  
of  
**kits**

See for yourself the range of wonderful new kits that Heath have presented in the latest catalogue. We now offer something for everyone, including stereo hi-fi equipment, radios, intercoms, calculators, automotive testers, shortwave and amateur radio, testers and instruments for technicians and hobbyists . . . all at money-saving prices. And payment is so easy—choose cash or our low deposit terms (starting at £2 per month for up to £40 credit).

You can build a Heathkit model using only a soldering iron and a few simple hand tools. Foolproof assembly is guaranteed using the step-by-step construction manual included with every kit.

Add to this a technical consultant service both before and after purchase and you will see why kit building the Heathkit way is so popular all over the world.

Send now for your free copy of the Heathkit electronic kit catalogue—and if your friend is likely to borrow it, fill his name and address in below and we'll send him a copy too!

Please send a FREE Heathkit Catalogue to my friend

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

**HEATH**  
Schlumberger **HEATH (GLOUCESTER) LTD., DEPT. PE/08/73**  
BRISTOL ROAD, GLOUCESTER GL2 6EE.

Please send me a FREE Heathkit Catalogue

I want to know more about your Cash and Low Deposit Terms, without obligation.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

**HEATH**  
Schlumberger **HEATH (GLOUCESTER) LTD., DEPT. PE/08/73**  
BRISTOL ROAD, GLOUCESTER GL2 6EE.

**FIRST TIME EVER at £42.50.** Solartron CD711S2 Double Beam Oscilloscope d.c.—9MHz; 3mV/cm; trigger delay; crystal calibrator; 4in flat faced tube. In good working condition. Carriage £1.50.  
**SOLARTRON CT 316** (D300 range). DC to 6 mcs. 3" tube. TB up to 0.75 micro secs per centimetre. Built in calibrator. Size 8½" x 11" x 20". Price £22.50. Carr. £1.25.  
**MARCONI VALVE VOLT-METER** type TF 958(CT208) DC to 100 mcs. 5" mirror backed meter complete with probe, leads etc. £12.50. Carr. £1.25.

**GRATICULES.** 12cm x 14cm in High Quality plastic. 30p each. P. & P. 5p.

**MODERN TELEPHONES** type 705. Two tone grey, £3.75 each. The same but black, £2.75 each. P. & P. 25p each.

Also **TOPAZ YELLOW** £4.50 each. P. & P. 25p.

**STANDARD GPO DIAL TELEPHONE** (black) with internal bell, £7.00 each. P. & P. 50p.  
Also **TOPAZ YELLOW** £4.50 each. P. & P. 25p.

**20Hz to 200kHz WB SINE AND SQUARE GENERATOR.** Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £6.85 each. P. & P. 25p. (Not cased, not calibrated.)

**WOBBULATOR.** Sweeps 8 to 45Hz ready to use. 6.3V a.c. required. £9 each. P. & P. 25p. (Not cased, not calibrated.)

**CAPACITOR PACK.** 50 Brand new components only 50p. P. & P. 17p.

**5 MOVING COIL METERS** various. £2. P. & P. 37p.

**POTS**—10 different values. Brand new—50p. P. & P. 17p.

**COMPONENT PACK** consisting of 2.2 pole 2 amp push on/off switches; 4 pots, various, brand new; 250 resistors ½ and ¼ watt, many high stabs, etc. Fine value at 50p per pack. P. & P. 17p.

**P.C.B. PACKS & D. Quantity 25sft**—no tiny pieces. 50p plus P. & P. 20p.

**FIBRE GLASS** as above £1 plus P. & P. 20p.

**5 CRYSTALS** 70 to 90kHz. Our choice, 50p. P. & P. 15p. Matched pairs, 50p per pair. P. & P. 15p.

**TRIMMER PACK.** 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, 25p the lot. P. & P. 10p.

**ELECTRONIC TIMER UNITS**—wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only £2.50 incl. carriage.

**LIGHT EMITTING DIODES** (Red) from Hewlett-Packard. Brand New 38p each. Holder 1p each. Information 5p.

**PHOTOCELL** equ. OCP71, 13p each.

**PHOTO-RESIST** type Clare 703. Two for 50p.

**AMERICAN OSCILLOSCOPE** type USM24. A 10 meg scope—all min. valves complete with circuit diagram. Mains input 115 volt 50 cycles therefore £20. With step-down transformer £22.50. Carr. £1.50.

**MOTOR MIN. SYNCHRONOUS.** Size 1½" x 2" x 1", 240V operation, 3.6 RPM, 25p each. P. & P. 5p.

**DELIVERED TO YOUR DOOR** 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.

PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 7.30 p.m. ANY DAY

**CHILTEAD LTD**

7/9 ARTHUR ROAD, READING, BERKS.  
(rear Tech. College) Tel.: Reading 582605/65916

**PRACTICAL ELECTRONICS**  
"SCORPIO" ELECTRONIC  
IGNITION SYSTEM



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required.

Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision.

Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7½in x 4½in x 2in. approx.

Complete assembly and wiring manual 25p, refundable on purchase of kit. Price: £10.50 plus 50p P. & P.

**PSYCHEDELIC LIGHTING**  
UNIT Mk. 3



This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c.  
Complete assembly built and tested. Size 9in x 7in x 3in. Price £25 carr. paid.

PLEASE NOTE ALL THE ABOVE PRICES ARE SUBJECT TO V.A.T. ADJUSTMENT

**DABAR ELECTRONIC PRODUCTS**

98a Lichfield Street, Walsall, Staffs. WS1 1UZ

TELEPHONE: WALSALL 34365

TELEGRAMS: DABELEC Walsall Staffs.

Dalek voices are produced by modulating a modified speech waveform at about 15-20Hz. Speech, and certain types of music waveforms, can present a very peaky characteristic. The peaks are multiplied and added to in the Ring Modulator and thus, if the signal is remodulated several times, or if the initial frequency is high enough, the final output contains a large proportion of sound which bears a remarkable resemblance to white noise. The cure for this problem is to limit the dynamic range of the signal.

Although exact details for such a procedure lie outside the scope of this series a passable method is to feed the offending signal to one of the input amplifiers and, observing the output on the oscilloscope, adjust the gain of the amplifier so that a large proportion of the peaks are suitably clipped. If insufficient gain is available to allow an adequate degree of clipping the input amplifiers may be cascaded. The achievement of clipping means, of course, that the amplifier output signals are swinging between the positive and negative saturation levels and it will be necessary to attenuate the signal quite considerably. Fig. 7.5 shows a simple resistive attenuator which will give a signal of about 500mV from a 28V source.

## CONSTRUCTION

Construction of the Ring Modulator is quite straightforward and the only critical requirement lies with the observation of polarity of the tantalum capacitors. Reversal of any of the capacitors will result in noisy operation and, in the case of the output capacitor, no operation at all. Tantalum capacitors have been specified in order to conserve space and there is no reason why 10V electrolytics should not be used with an alternative layout.

## SETTING UP

Setting up the Ring Modulator consists only of providing a modulation balance. Set VR1 to its mid position and apply a common sine wave signal to both inputs. The output of the ring modulator will be a sine wave which is twice the frequency of the applied signal. If the modulation is out of balance alternate peaks of the output signal will be at different amplitudes. VR1 should be adjusted to bring the peaks into line at which point the modulation is balanced.


It is a wise precaution to repeat this measurement from time to time to adjust for settling down changes in the circuit.

## THE PEAK LEVEL METER

In the prototype Synthesiser the meter circuit was based on a precision rectifier built around a pair of operational amplifiers arranged in such a way as to eliminate the effect of the diode forward voltage drop. Although the circuit proved to be very responsive it was found, in practice, to present a number of disadvantages. In the case of a.c. signals the meter would read only the r.m.s. value and although it was possible to determine the actual peak-to-peak value by application of a form factor for known wave shapes the determination of peak-to-peak values for complex waveforms proved to be a very hit and miss affair.

In a similar manner, when endeavouring to set up reasonably accurate programming voltage levels, the rapid response of the meter frequently made it difficult to establish the peak value with any certainty.

Fig. 7.7. Circuit diagram of Peak Level Meter

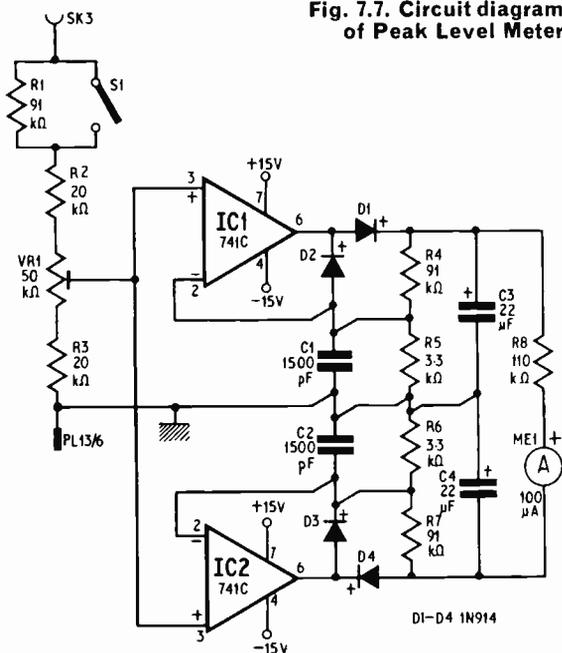

In consequence it was decided to redesign the meter circuit to provide a peak reading facility which would be independent of waveform configuration and which would have a reasonably long decay time to ease the establishment of transient level readings. The final circuit is shown in Fig. 7.7. IC1 and its associated circuitry is used to read the positive going peaks while IC2 deals with the negative side of the signal. The operation of the circuit is as follows.

## CIRCUIT OPERATION

The input sensitivity of the circuit at the i.c. is about 200mV for full scale deflection of the meter. A positive going peak of this value appearing at the input of IC1 will swing the output positive to a level determined by the values of R4 and R5, about 6.2V with the values shown, and capacitor C3 will charge at a rate determined essentially by the effective current output of the i.c. The charging time for C3 is thus rather less than 2ms.

If, after the capacitor is charged, the 200mV peak is replaced by a lower amplitude peak the tendency would be for the i.c. to swing hard negative due to the effect of the positive voltage from the capacitor appearing at the inverting input via R4. This tendency is prevented by D2 which limits the negative excursion of the output to about 700mV.

Capacitor C3 discharges through R4 + R5 in parallel with R8 + R (meter) and with the values shown takes about 1 second. C1 serves to decouple a.c. from the feedback loop and thus effectively extends the accurate range of the meter to about 15kHz.

The negative reading side of the circuit around IC2 operates in the same way. The circuit is adjusted to give full scale deflection with inputs of 1.0V and 0.5V by means of the attenuator with inputs of 1, 2, 3 and VR1.

In using the meter it should be borne in mind that the peak values recorded represent only half the total peak to peak value of the signal being measured

and this applies whether the signal is symmetrical or assymmetrical about zero. When measuring low frequency programming signals of greater than 1Hz the minimum reading of the meter between peaks does not represent the lowest level of programming signal.

This particular meter circuit can be used to measure the peak level of single transients of not less than 2mS duration.

### ADVANTAGES

In tape recording the peak level meter scores heavily over the more conventionally employed v.u. meter. This latter meter will record what is essentially the mean value of signal presented to the recording amplifier and if, as is generally the practice, the mean level is kept to about -3dB transient peaks are likely to be clipped or otherwise distorted. The use of a peak level meter, on the other hand, enables the peaks to be kept within the limits imposed by the recording amplifier and thus enhances the overall quality of the recording.

### THE REVERBERATION AMPLIFIER

Reverberation, or re-echo, in varying degrees is a characteristic observed in the majority of large halls, public buildings, cathedrals and so on. In a properly designed and proportioned hall the inherent reverberation characteristic can provide a high degree of enhancement to the sounds occurring therein.

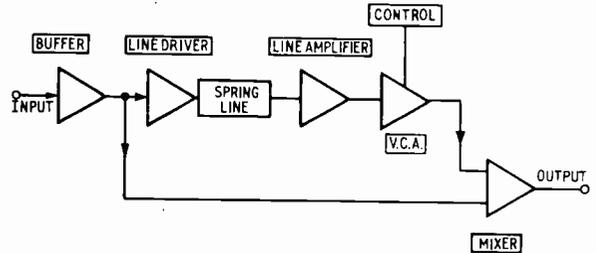


Fig. 7.8. Block diagram of Reverberation Amplifier

### COMPONENTS . . .

#### REVERBERATION AMPLIFIER

##### Resistors

R1	10k $\Omega$	R15	3.9k $\Omega$
R2	270k $\Omega$	R16	110k $\Omega$
R3	39k $\Omega$	R17	13k $\Omega$
R4-R5	10k $\Omega$	R18	13k $\Omega$
R6	47k $\Omega$	R19	0.5 $\Omega$
R7	10k $\Omega$	R20	0.5 $\Omega$
R8	6.8k $\Omega$	R21	56 $\Omega$
R9	390 $\Omega$	R22	10k $\Omega$
R10	10k $\Omega$	R23	10k $\Omega$
R11	20k $\Omega$	R24	120k $\Omega$
R12	10k $\Omega$	R25	10k $\Omega$
R13	10k $\Omega$	R26	See text
R14	10k $\Omega$		All 5% $\frac{1}{2}$ watt carbon unless otherwise stated

##### Capacitors

C1, C2	0.1 $\mu$ F ceramic
C3	620pF silver mica
C4	4 $\mu$ F 15V elect.
C5	0.1 $\mu$ F ceramic
C6	0.1 $\mu$ F ceramic
C7, C8	10 $\mu$ F 16V tantalum
C9	0.003 $\mu$ F ceramic
C10	See text
C11, C12	100 $\mu$ F elect. 22V

##### Transistors and Diodes

TR1	2N2905	TR3	BC209C
TR2	2N2219	D1, D2	1N914

##### Potentiometers

VR1	5k $\Omega$ lin.
VR2a/b	10k $\Omega$ lin. (two ganged)
VR3	10k $\Omega$ lin.



##### Integrated Circuits

IC1, IC2	741C
IC3	MFC6040
IC4, IC5, IC6	741C

##### Miscellaneous

Spring line type HR42 (Henry's Radio), JK3, JK4 3.5mm jack sockets (2 off), SK2 2mm miniature socket

#### BUFFER AMPLIFIER

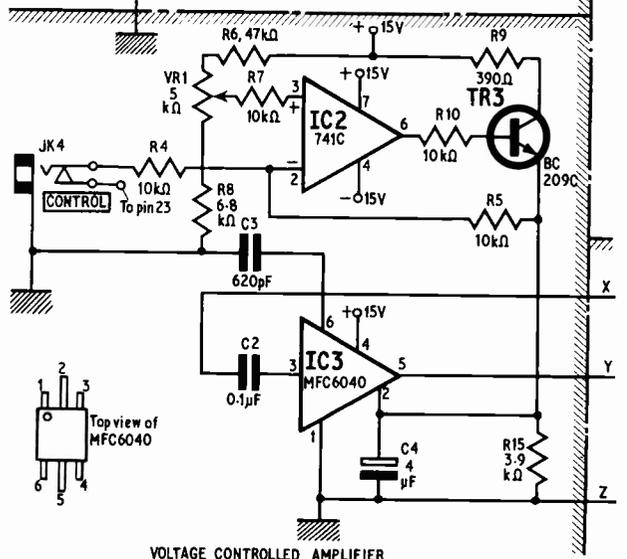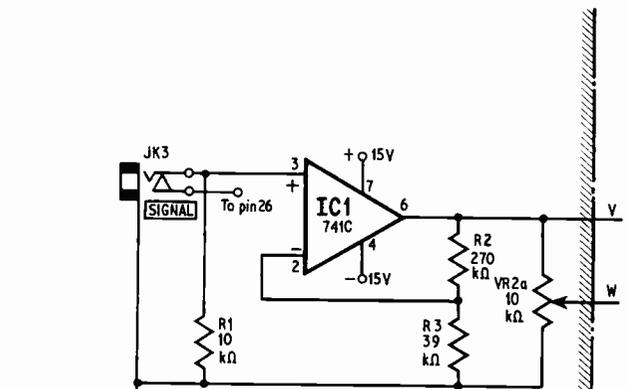

There are a number of ways in which a reverberation characteristic may be simulated and for the Synthesiser the spring line has been adopted. The spring line consists essentially of a coiled wire, usually steel, which is supported at each end in a compliant mounting. At the supported ends of the wire are fitted electro-magnetic transducers. The line driving transducer is excited by an electrical signal and the varying field produced causes mechanical wave motion to be set up in the spring line. When the wave motion reaches the far end of the line it sets up an electrical disturbance in the line output transducer which is, in turn, amplified and added to the original signal.

Part of the original mechanical wave motion is reflected back down the spring line where it serves to modify further on-coming waves.

Because a mechanical wave motion travels much more slowly than its electrical counterpart the signals received by the line output transducer are delayed in relation to their source, such delay being a function of the length of wire used in the spring line. Thus

the mixing of the mechanically routed signal with the source signal constitutes the addition of an echo. However, since the wave motion, once initiated, travels back and forth along the line until its amplitude becomes negligible, multiple echoes are received and added to the original signal.

The spring provides a further useful feature having its origin in the fundamental resonance of the system. When the driving signal passes through the frequency at which the system resonates the output is characterised by a sudden increase in amplitude which can be as much as three times the value of the normal mean signal. Similarly when the input signal passes through any of the harmonics of the resonant frequency there is an increase in output signal amplitude, and this despite the fact that the useful range of the HR42 spring line, specified for this project, is limited at its upper end to about 4kHz. In the prototype unit quite high resonant peaks were occurring at up to 25kHz.

The combination of multiple echoes and varying amplitude imparts a very useful "singing" quality to an otherwise uninteresting sound.

LINE DRIVER AND OUTPUT AMPLIFIERS


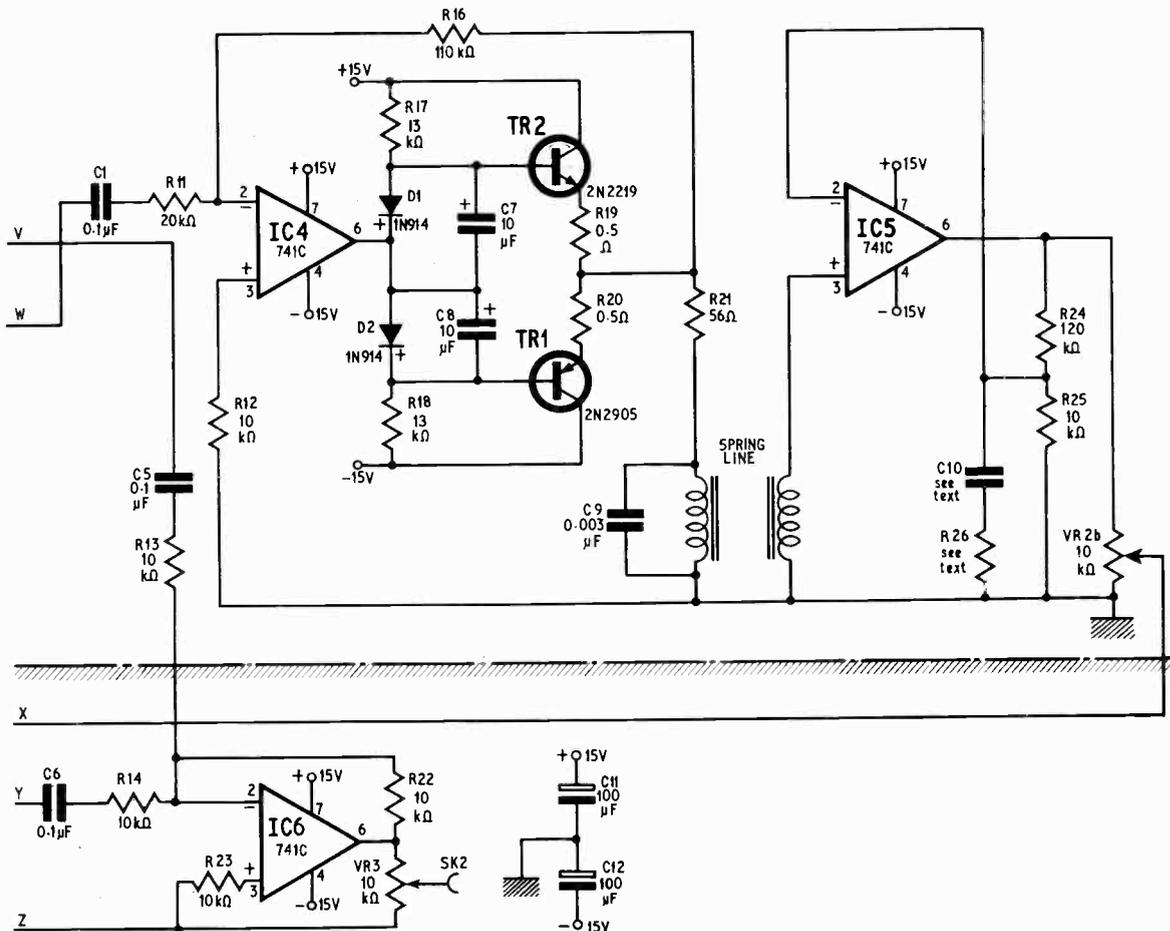


Fig. 7.9. Circuit diagram of Reverberation Amplifier

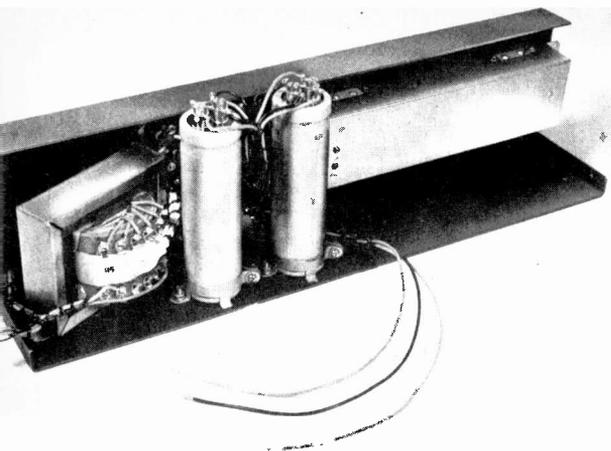

The spring line unit is attached to the p.s.u. sub-frame

### DESIGN CONSIDERATIONS

In the prototype the line driving amplifier employed a single transistor operating in what was effectively Class A. The current consumption was thus quite high even in the quiescent state and small variations in the power supply rails gave rise to noise in the system which was apparent when the line was not being driven hard. For the modular version of the Synthesiser therefore the Reverberation Amplifier was redesigned to reduce current consumption, reduce hum and noise to negligible proportions and to enable a complete divorcing of the voltage controlled part of the system so that the amplifier may be built as a separate unit outside the Synthesiser project altogether.

A fortuitous advantage of the re-design provides sufficient power capability to drive two HR42 or one HR42 and one HR162 spring lines in series. It is also theoretically possible to drive up to four of the above spring lines in any combination although this latter method has not been tested.

The advantage in using more than one spring line in the system lies in the fact that it is rare for two units to have identical resonances and delays and thus two or more units can only improve the overall reverberation characteristic.

### CIRCUIT ACTION

The Reverberation Amplifier is shown in block form in Fig. 7.8 and the circuit diagram in Fig. 7.9. The input signal is led to a buffer stage, which has a gain of about six, and the output is divided to drive the line amplifier and output mixer. The line driving amplifier consists of a pre-amplifier built around a 741 and having a gain of about five which, in turn, provides drive to a complementary pair of output transistors having a current gain of about a hundred and arranged in what may be described as a modified form of Class B. The output from this latter stage provides drive direct to the spring line through a current limiting resistor.


The output from the spring line is amplified by another 741 having a gain of about nine and then led to the input of the voltage controlled amplifier based on the Motorola MFC6040. This latter device has a maximum gain of 13dB and a maximum attenuation of about 77dB relative to the input signal which should not normally exceed 500mV r.m.s. The overall gain of the spring line route is thus arranged so that when the line is being driven hard at a non-resonant frequency, and with the v.c.a. at maximum gain, the output of the v.c.a. is equal to the output of the buffer stage and thus the mixer is receiving equal components of reverberated and non-reverberated signal.

The choice of component values for C10 and R26 may be arrived at by experiment on the basis of the measured response of individual spring lines. To limit the gain to 6dB a value of 2.5 kilohms for R26 will suffice.

The value of C10 is calculated on the basis of the frequency at which the 6dB gain is required. For a frequency of 15kHz the value of C10 is 1nF.

The v.c.a. is controlled by a separate 741 arranged in the differential mode. The non-inverting

Photograph of the assembled module

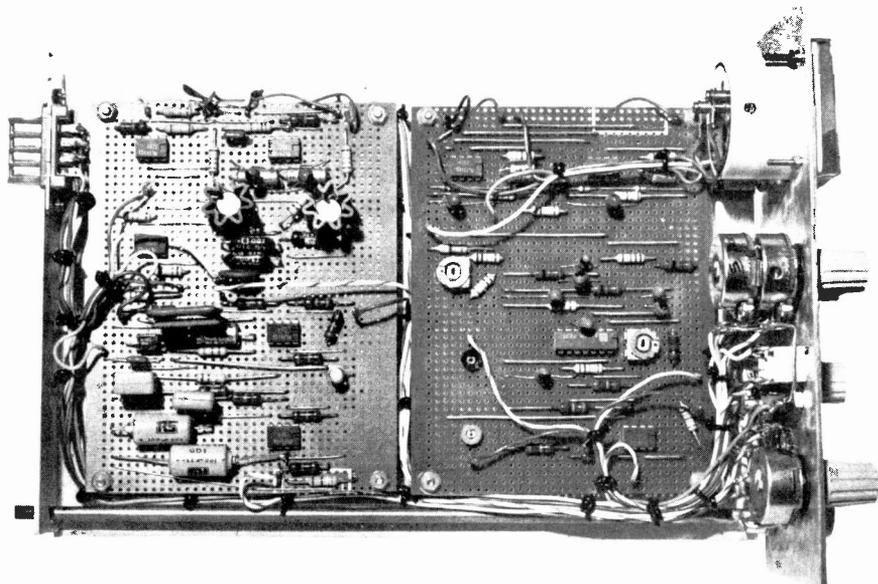

# REVERBERATION AMPLIFIER

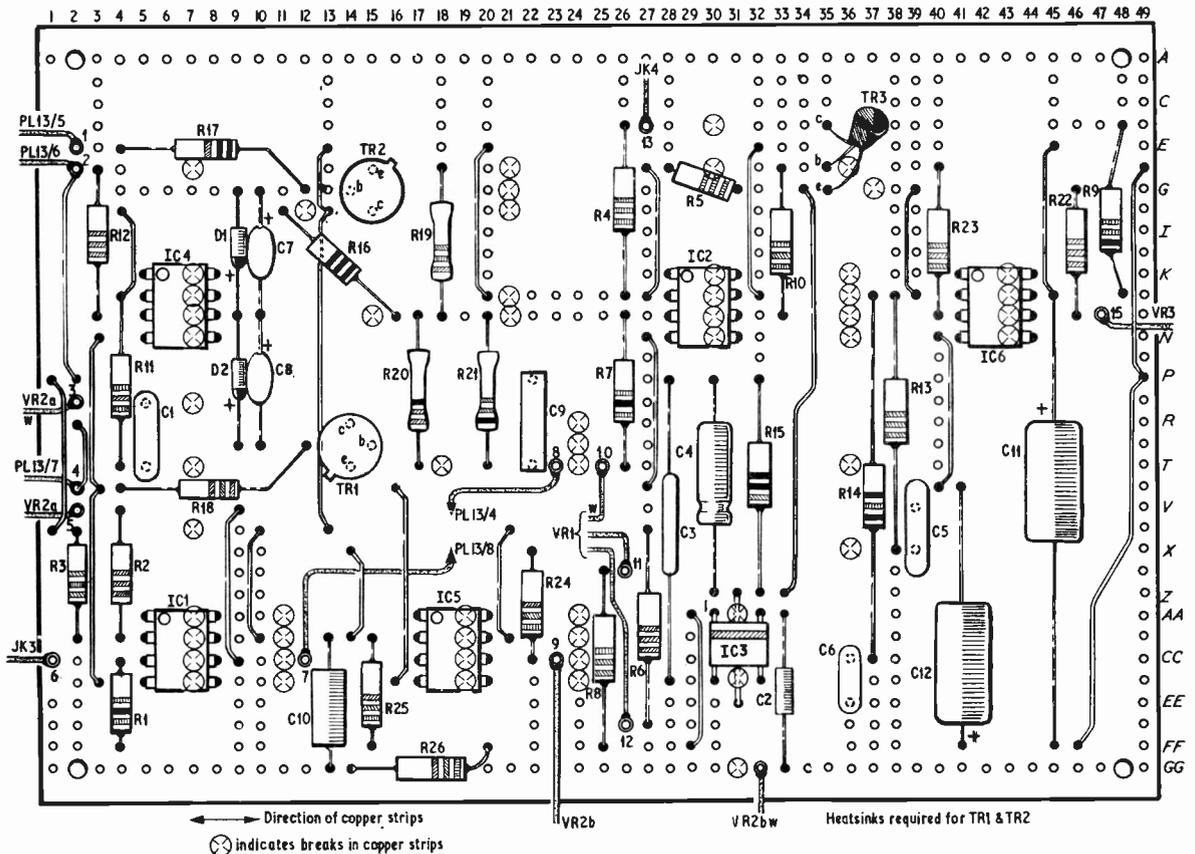


Fig. 7.10. Board assembly of Reverberation Amplifier

input is driven by a positive voltage derived from the divider R6, R8, and VR1. The high and low ends of VR1 are thus at 3.0V and 1.75V respectively. The inverting input of the 741 is driven by a control voltage which should have a swing of 2.5V maximum.

With VR1 at its minimum setting a control voltage swinging from zero to -2.5V will have the effect of attenuating the output of the MFC6040. With VR1 at its maximum setting a control voltage swinging from zero to +2.5V will have the effect of amplifying the output of the MFC6040 from -77dB to +13dB relative to its input signal. The inverting input of the 741 acting as control amplifier is prewired to a ramp generator which will, of course, provide the first mode of v.c.a. operation described due to its negative going output.

If external automatic control of reverberation is not required it is essential that a grounded jack plug be inserted into the control socket otherwise the output of the control amplifier will be insufficient to swing the MFC6040 through its full range.

The current sink at the control input of the MFC6040 is specified as being 2mA but on several


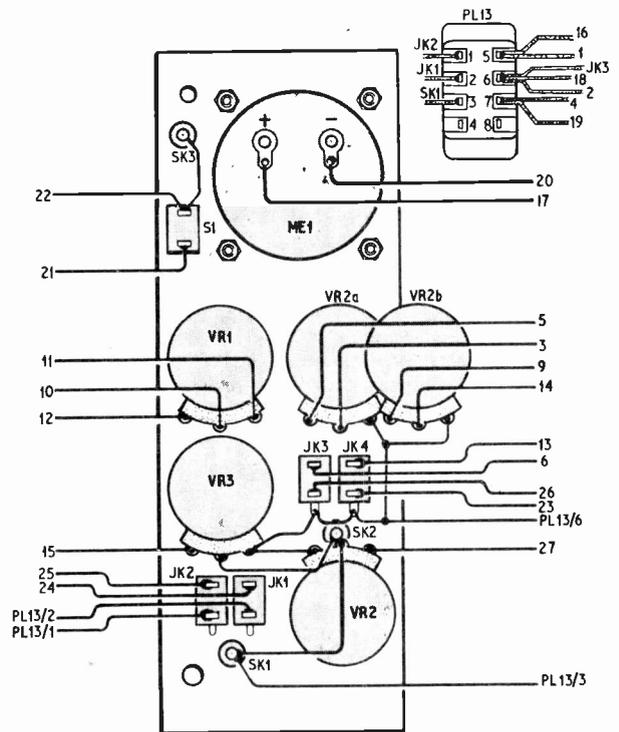


Fig. 7.11. Front Panel Wiring

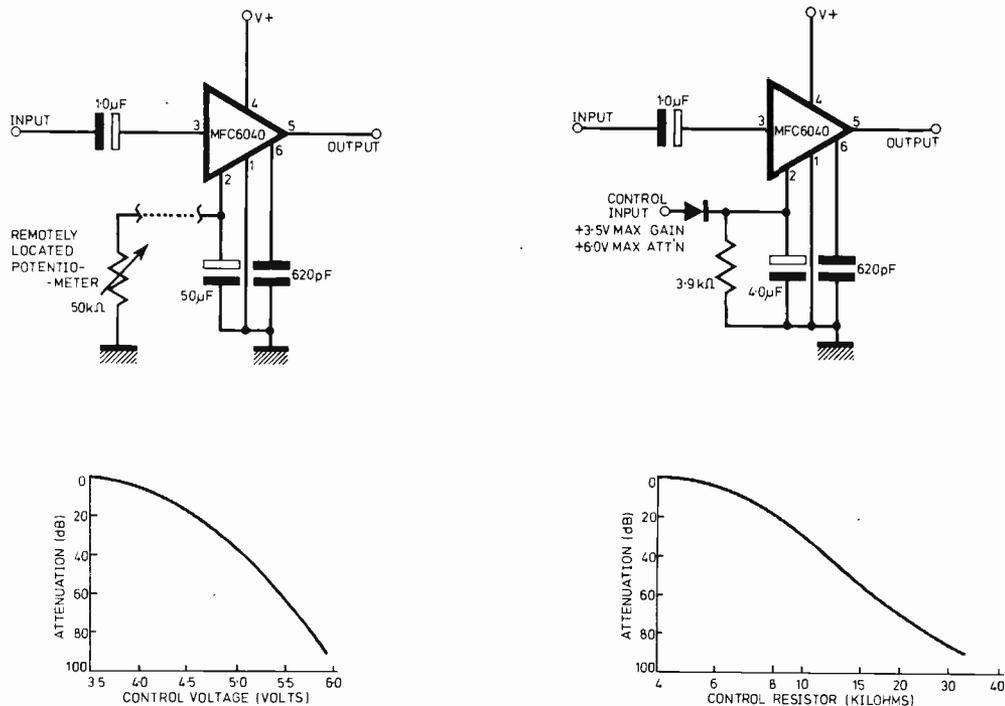

**Fig.7.12. Two methods of providing external control using a potentiometer and voltage control input. The relevant response curves are located below each circuit. Here the 0dB reference equals a 13dB gain**

tested in this mode of operation quite a wide variation in current sink was noted, the highest being 25mA. Consequently it is prudent to provide a series transistor on the output of the control amplifier, with overall feedback, in order that the 741 is not overloaded. The effect of overload will not necessarily damage the 741 but it could result in a reduction of the output voltage swing which would, in turn, affect the operation of the 6040.

### OMITTING THE V.C.A.

For some possible applications the use of voltage control will not be required and, in these instances, the MFC6040 and associated control amplifier may be omitted from the circuit entirely. In these circumstances the gain of the line output amplifier, IC5, will have to be increased by a factor of 0.33 if equal reverberated and non-reverberated components are required at the mixer. The output of IC5 is, of course, led direct to C6 on the mixer in these latter circumstances.

### CONSTRUCTION

Fig. 7.10 illustrates the recommended circuit board layout. Construction is quite straightforward and the only setting up required lies in checking the signal levels at the outputs of the buffer, line driver and line output amplifiers to ensure that equal signal components from both sources are presented at the mixer when the line is being driven hard at a suitable non-resonant frequency.

Adjustment of the gain of the line output amplifier may be necessary and is dependent upon the mechanical attenuation of the line which may differ unit to unit.

Overall construction of the module should generally follow the pattern previously described and the wiring of the components on the front panel and McMurdo plug are shown in Fig. 7.11.

In this module the McMurdo plug has insufficient ways to carry all the necessary signals and two extra leads are required to carry the control and audio signals to the reverberation amplifier. Reference to the block diagram in the first part of the series will show that the control signal is derived from RG2 while the audio signal is derived from the right channel of the output amplifiers yet to be described. Suitable leads should be run from the respective McMurdo sockets on these latter modules to a point immediately adjacent the left hand Vero endplate and secured to the connector mounting rail by a tie of lacing cord. From this point they should run along the end plate and be trimmed so that they protrude about three inches beyond the front face of the mainframe. Terminated in 1mm miniature plugs, they can be mated with their respective sockets on the Ring Modulator circuit board when the finished module is being inserted into the mainframe.

A fully comprehensive revision of all module interconnections will appear in part nine of the current series.

For the benefit of constructors who may wish to explore the possibilities of the MFC6040, Fig. 7.12 shows two possible methods of providing external control with the resistance attenuation curve and the control voltage attenuation curve of this very versatile device.

*In Part 3, VRZ is 100Ω.*

**Next month: The Envelope Shaper will be described.**



# Components

# Show '73

**D**ESPITE the recent adoption of the title International London Electronic Components Show, the RECMF of old seems still to be so called both on the official catalogue and by many of the exhibitors and visitors. However, this year it bears little resemblance to the Radio Show of old. Perhaps the word "subdued" would describe the feeling best.

In size the 1973 event was not much more than half its previous size, a factor with very mixed blessings. Obviously less to see but, to the footsore visitor, the possibility of seeing most of what was there without total self destruction. And, with less stands, the opportunity to see around, particularly from the gallery which of recent years has tended to become rather crowded.

The last three years have left their mark on the industry very clearly, as the drop in the number of exhibitors showed and it is a shame that some of the more famous semiconductor manufacturers chose not to attend. In fact the usual bustle, not just of visitors, but of new products looking for markets seemed to be muted almost out of existence.

Generally the atmosphere was one of trading rather than of displaying goods, many of the stands were totally bereft of components or equipment and, in this sense were a sad disappointment to the engineer looking for new "toys". However, the current world shortage situation in many component areas probably goes a long way to explaining this.

## RADIO RECEIVER I.C.s

Perhaps one thing which stands out from the show is the advances being made in integrated circuits. It is almost possible to build anything using i.c. techniques these days and several of the manufacturers are trying to prove just that.

Fairchild displayed a set of interesting chips which can make up an a.m. or f.m. radio with stereo facilities. These included their 720 single chip a.m. receiver, the 753 f.m. gain block, the 758 phase-

lock loop stereo decoder, the 3075 f.m. i.f. amplifier and limiter, detector and audio pre-amplifier, and the 706 audio power amplifier with a 5W capacity.

Both mono and stereo were demonstrated using either one or two of the power amplifier chips and considering the nature of the halls at Olympia, reception was very impressive.

To an extent of course, this type of display is really more of an application demonstration than a display of new concepts since the basics of such systems have been around for some time. However, it does illustrate the way in which we can expect developments to go as more and more roles are taken over by the chip.

## FILTERS USING I.C.s

Take the case of Siliconix of Swansea, well known in the semiconductor market. They are investigating the ability of multi-amplifier chips to provide variable filters, of great value in audio control and generation applications.

They have already developed some prototype circuits using their L114 triple operational amplifier and have established that it is possible to obtain a tuning range from 0 to 10kHz, that high  $Q$ s up to 400 can be obtained, that high and low bandpass is simultaneously possible and that both gain and  $Q$  are easily programmable.

Indeed, they have even developed a digitally programmed filter using one of their own DG 507 chips to do the logic control.

With all this compression of componentry on to chips one almost wonders where the discrete component went. But one only has to look at any circuit board to see the still tremendous need for power rail droppers, couplers and so on.

## MULTI-PURPOSE INSTRUMENT

On the more constructional side there were a number of interesting items. For the portable instrument constructor there was the Pakit kit multi-purpose instrument. An analogue display and movement is available to fit a moulded plastic

case which has ample room for circuitry and components. Available from Elcometer Instruments Ltd., the Pakit can be bought complete with a rechargeable power supply, self-designed front panel, leather carrying case and printed circuit.

The basic unit with case will probably market for something under £20.

## CASES AND PACKAGING

For the inveterate casemaker there was a display of coated aluminium panel material from Bakelite Xylonite Ltd., which provides both strong covering, attractive colours and, as an added bonus fairly high electrical insulation by virtue of the plastic coating material.

For the man who is always losing components on the bench there was an interesting adaption of the plastic packaging market. Dunlavin Converters have developed their Ducon Carripallet system for packaging delicate materials to the point where it can be used for other applications.

Thus the Carripallet is a multi-cavity foam plastic pad measuring  $400 \times 400 \times 50$ mm and with 25 cells. Laid on its back, which is a cardboard support layer, it can be used as a multi-compartment tray. As the material is flexible foam plastic it will not damage delicate parts and indeed components can be stuck upright in it if required.

Normally items of this type are sold in large quantity only, but we understand that single sheets are available and will probably cost about £1 each.

Weller were at the show with their latest low voltage temperature-controlled soldering pencils (no longer irons we see), the W-MCP available with a variety of tip shapes.

## PANEL METERS

On the meter front several so-called panel meters were on display including the Dinline 50, the first such product to come from the Avo stable. The name is based on the rectangular styling which follows the DIN (IEC 51) specification.

A digital panel meter is something that, only a short while ago, would have been regarded as an instrument rather than a component. By miniaturisation and recent price reductions in digital i.c.s, Analogue are able to offer a versatile 3-digit digital panel meter at only £25 in quantity. Designated the 2530, this unit can measure, display and transmit voltages and currents of either polarity. The 2530 has fully floating inputs just like any analogue meter so that measurements with respect to any arbitrary level in a circuit can be made.

A filament readout is used for good readability and low cost. This meter can be incorporated in many types of instrument giving a really competitive alternative to analogue measuring instruments.

West Hyde displayed their Contil digital panel meter card with three digit display in Atron tubes and costing less than £25.

Integrated Photomatrix showed their digital panel meter kit using a MOS LSI chip and i.e.d. display which is available for £36.75. Of course the IPL unit is considerably smaller than many other displays on show.

### LARGE SCALE INTEGRATION

One of the fastest-growing areas of semiconductor technology must be the MOS large scale integration (LSI) field. All the major companies appear to be competing to see who can cram the most MOSTS into a single 24-pin package.

One of the latest contenders in this competition is the Motorola MCM6571L character general i.c. It contains a read only memory of 8,192 bits which can produce 128 different characters, including upper and lower case and Greek symbols, each character being formed by a matrix of seven horizontal and nine vertical dots. As well as the stored characters themselves there are 128 bits which are used to automatically control each character position so that the "tails" of letters such as p, q, and j come below the base line as in normal typewritten material.

Another piece of news in the MOS LSI field comes from General Instrument Microelectronics who announced that slashing price reductions have been made on their C500 calculator i.c. Its new price of £13.70 (1 off) represents an £18 drop from its previous value. G.I. hope that this new low price will encourage designers to regard the calculator i.c. as just another component for use in many types of instrument where arithmetic operations are to be carried out. For instance, they could be used in a weighing scales which automatically displays the price of the goods after the price per pound is typed in.

### NEW LOW-PRICE FOR I.E.D. DISPLAYS

While MOS manufacturers are aiming at miniaturisation, the display device manufacturers are aiming at bigger and brighter components. One of the innovators of i.e.d. displays, Monsanto, announced new low prices for their displays.

Single i.e.d.s can now be bought for 5p in large quantities making it possible for manufacturers to use them in such applications as diagnostic lamps on printed circuit boards, panel lamps, and battery "low" indicators.

On the numeric display side the MAN5, a green seven-segment device is down to £3.99 from £9 (1 off) and the MAN64A, a 0.4in numeric display down to £4.27 from £7.85.

### NEW TIMER INTEGRATED CIRCUIT

Another example of large scale integration, but this time combining digital and analogue functions was on show at the Elremco stand. Designated the LR171E, this i.c. has an enormous range of applications because of its inherent flexibility.

It uses a digital counter so that timing ranges of seconds, hours or even weeks can easily be obtained. A digital-to-analogue converter is used to give a current output which means that a cheap meter can be used to give an indication of time elapsed.

It has eight operational modes, delayed on, delay interval etc., and has three digital outputs which give indications at  $\frac{1}{2}$ ,  $\frac{1}{4}$  and  $\frac{1}{8}$  of a preset time period.

The i.c. is TTL compatible and has integral output drivers for a triac or SCR. Price is £12 for one off.

### RUSSIAN COMPONENTS

Many manufacturers are finding difficulty obtaining such ubiquitous components as resistors and capacitors and so it is not really surprising to see more and more imported components creeping into instruments such as calculators.

Z & I Aero Services are importers of Russian resistors and capacitors and supply both to industry and non-professional users. The components are cheap, clearly marked with their values (not colour coded) and readily obtainable.

### NOVEL BREADBOARDING AID

A novel breadboarding system which has great potential in the amateur field was shown by Critchley Bros. Ltd. Manufactured by the German firm of Christel Wainwright, the system is called "Mini-Mounts." Each Mini-Mount is a

small rigid board with a copper pattern on one side and adhesive on the other. Components are soldered onto the boards which are then positioned anywhere on a convenient baseboard (which could be copper-plated to give a good ground plane), and stuck in place.

This system has many advantages over other similar systems: no holes need be drilled; the adhesive holds the Mini-Mounts firmly in place yet they can be moved if the circuit requires; components and Mini-Mounts can be re-used if care is taken.

Mini-Mounts to take DIL i.c.s, and other such components are available so the system gives great scope to the designer.

### NEW SHAPE FOR LAMINATIONS

Though by no means a spectacular breakthrough, the new design for transformer laminations by Kent Insulations shows how old and tested designs can be improved with a little ingenuity. Instead of the usual "E" shape the new type has a tapered centre arm so that excellent mechanical and magnetic contact is made when the two halves are fitted together.

### MULTI-MEMORY MACHINE

On the Advance Electronics stand and in fact using the same case as the Advance calculators was a new accounting aid from Phytron. Called the Analysis 14 this calculator incorporates 13 accumulating memories each of which can be debited or credited at any time simply by selecting the required store with one of thirteen keys. Only credit and debit (i.e. addition and subtraction) are available, the manufacturers suggesting that this instrument is to complement, rather than replace, the normal desk calculator which can multiply and divide.

At £210 this calculator cannot really be termed inexpensive by modern standards and one wonders whether a machine without a print-out is really useful in accounting, where mistakes cost money.

### CONCLUSIONS

One wonders why a star attraction like the actual *Apollo* capsule "Charlie Brown" which circled the moon four years ago, which was on show on the Livinstone Hire stand together with a piece of moonrock, received so little publicity. This could have attracted great crowds, was this what the organisers were afraid of?

At a time when electronics is developing so fast, the show was not up to expectations and one can only hope that the companies will stop hiding their lights under bushels and give us some really interesting shows in the future. ★

**STARTING NEXT MONTH!**  
**PRACTICAL ELECTRONICS Proudly Presents the**

**PE RONDO..**

# **QUADRAPHONIC SOUND SYSTEM**

- 4 x 20 watt (continuous in 8 ohms) high quality power amplifier**
- High quality preamplifier and control unit with wide dynamic range**
- A.M./F.M. receiver of advanced design**
- CBS SQ quadraphonic decoder**

The PE RONDO is a total system incorporating the very latest technology and it will be described in full with all constructional details in a series of articles starting next month.


The receiver incorporates a varicap f.m. tuner with integrated circuit i.f. amplifier, quadrature detector and phase-locked-loop stereo decoder; and a unique i.c. phase-locked-loop synchrodyne a.m. medium-wave mono tuner. Optional i.c. matrix decoders: CBS SQ quadraphonic decoder or CBS SQ logic-enhanced quadraphonic decoder. Additional decoders will be presented as further systems become viable.

Modular construction techniques give flexibility, whilst the use of state-of-the-art i.c. technology allows all electronics to be housed in one compact unit. The system is completed by four shelf-mounting speakers, construction of which will also be fully described in this series of articles.

**Also:** PHASING UNIT • PHOTOGRAPHIC THERMOMETER & EXPOSURE METER

**PRACTICAL  
ELECTRONICS**

SEPTEMBER ISSUE ON SALE AUGUST 10, 1973

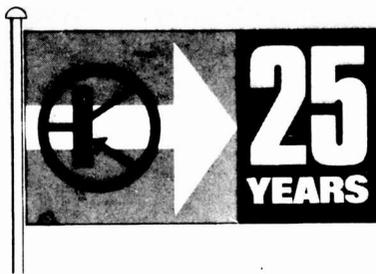

# 25 YEARS OF SEMICONDUCTORS

## PART 2

By M. J. Rose (MULLARD LTD.)

### POWER DEVICES, PHOTO DEVICES AND INTEGRATED CIRCUITS

THE first article described the types of transistor and small-signal diode available. This article considers power devices, photo devices using, or emitting light, and the most revolutionary semiconductor device of all—the integrated circuit.

#### POWER DIODES

The amount of power that can be handled by a semiconductor diode is limited by the junction temperature. Provided the heat dissipated within the device can be conducted away so that the maximum permissible junction temperature is not exceeded, the diode will operate satisfactorily. Therefore a power diode should have as large a junction area as possible, and a low thermal resistance to the case. The cooling area can be increased by mounting the diode on a suitably shaped heatsink.

Germanium power diodes were developed using these techniques, and could carry currents of approximately 10A and withstand peak inverse voltages of up to 600V. The introduction of silicon, however, led to their replacement during the 1960's by silicon diodes with junctions alloyed or diffused with aluminium.

#### AVALANCHE DIODES

As the reverse voltage across a junction diode is increased, a voltage is reached where avalanche breakdown occurs, marked by a sudden increase of current. Provided the diode can withstand the current at breakdown, it will recover when the reverse voltage is decreased below the breakdown value. Avalanche diodes are designed to withstand such breakdown currents, and so can be used safely in applications where voltage transients are likely to be encountered.

By the end of the 1960's other protection devices such as high-speed fuses had been developed so that semiconductor-diode rectifier systems were firmly established in such applications as battery chargers, electroplating and electrolysis processes,

and electric furnace supplies. These semiconductor systems occupied less space than the existing systems, had a higher rectifier efficiency, and for the first time presented power engineers with a device that had no wear-out effects.

A high-voltage rectifier stack is shown in the photograph of Fig. 8. Diodes are mounted on heatsinks around a central fixing stud. Such stacks can be cooled by natural convection, or for higher currents by forced-air cooling or immersion in an oil bath.

Fig. 8 High-voltage rectifier stack operating at 12kV and 5A with natural convection cooling (length approximately 10in)

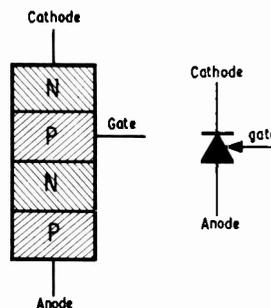
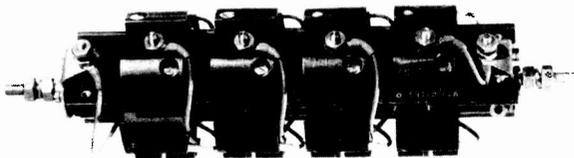


Fig. 9 Structure and circuit symbol of thyristor

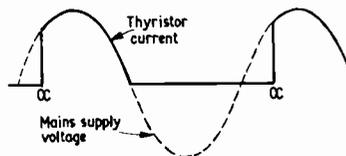


Fig. 10 Phase control using thyristor

#### THYRISTORS

The thyristor or controlled silicon rectifier was developed for power control in parallel with the silicon rectifier diode. The rectifier action of the thyristor allows a current to flow in one direction only, but in addition current can only flow when the thyristor has been triggered.

In form, the thyristor is a four-layer *pnpn* device, as shown in Fig. 9. The circuit symbol is also shown in this figure. If the anode is positive with respect to the cathode, and a positive voltage is applied to the gate, the thyristor conducts. Once conduction has been established, the gate voltage can be removed.

Therefore the thyristor can be triggered by a pulse provided the duration is sufficient to allow the current to be established. The thyristor is made non-conducting by reducing the current to below a holding value.

The method of power control with thyristors is shown by the waveforms in Fig. 10. By varying the trigger angle within the half-cycle ( $\alpha$ ), the amplitude of the current pulses passed by the thyristor, and hence the power delivered to the load, can be varied. This control technique is called phase control.

A second method of control is burst triggering, used for loads with a high thermal inertia such as furnaces. In this method, complete half-cycles of the mains supply are passed by the thyristor, the ratio of half-cycles passed to those blocked determining the power to the load.

### TRIACS

Another device for power control similar to the thyristor is the triac or bidirectional thyristor. This device is equivalent to two thyristors connected in inverse-parallel with a common gate connection. The circuit symbol for a triac is shown in Fig. 11. A current will flow through the device when the gate is sufficiently positive or negative with respect to

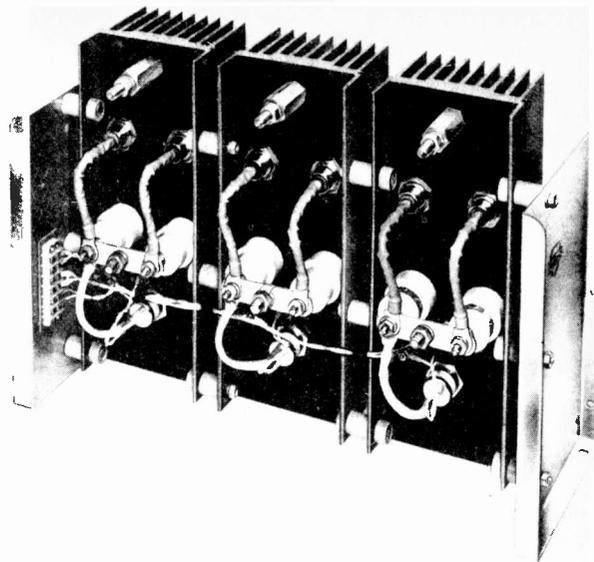


Fig. 12 Thyristor stack for operation on 440V three-phase mains to control 110A per phase

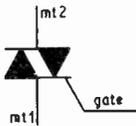


Fig. 11 Circuit symbol for triac

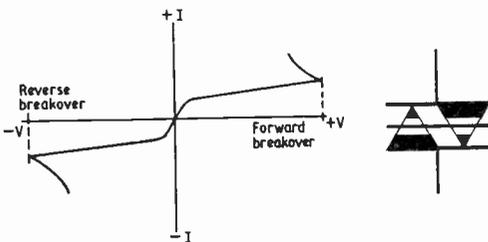


Fig. 13 Breakdown characteristic and circuit symbol for diac

terminal mt1, the direction of current flow depending on the relative polarities of mt1 and mt2.

The currents that could be handled by thyristors, and the inverse voltages they could withstand, increased during the 1960's as the manufacturing techniques were improved. Present-day thyristors can handle currents up to 1000A and withstand inverse voltages of over 2kV. Protection devices have been developed as with rectifier diodes to ensure reliable operation under practical conditions.

A typical thyristor stack with thyristors connected in a bridge configuration for the control of power to a load is shown in Fig. 12. The thyristors are mounted on heatsinks.

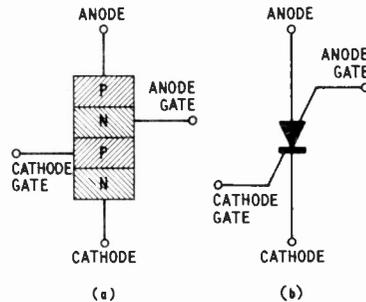


Fig. 14 Structure and circuit symbol for silicon controlled switch

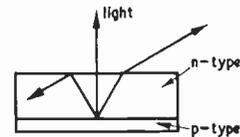


Fig. 15 Diagram showing construction of a typical light emitting diode

### THE DIAC

The diac, or bidirectional diode thyristor, is a useful trigger device for thyristors and triacs. It uses avalanche breakdown, but as the characteristic in Fig. 13 shows, the voltage decreases after breakdown so that the gate circuit is not overloaded on triggering.

### SILICON CONTROLLED SWITCH

Another four-layer *pnpn* device is the silicon controlled switch or SCS. Unlike the thyristor and triac, both intermediate layers of the SCS are accessible making it a four-terminal device. The structure and circuit symbol are shown in Fig. 14.

The SCS (like the thyristor) has two stable states: conducting and non-conducting. The SCS can be used in two circuit configurations. In one, the load is connected in the anode gate circuit so that the SCS operates as a four-terminal device. In the other, the load is in the anode circuit and the anode gate is not connected. The SCS then acts as a low-power thyristor or three-terminal device.

## PHOTOTRANSISTORS AND PHOTODIODES

Light falling on a junction in a semiconductor diode or transistor affects the current through the device. The energy of the light dislodges electrons and so increases the number of carriers available at the junction.

Constructive use of this effect is made in photodiodes and phototransistors where the change in current with light can be used in such applications as light meters and alarm systems.

Other semiconductor materials exhibit a change of resistance with light, and this effect is used in photoconductive cells (or light-dependent resistors). The choice of semiconductor material determines which part of the spectrum the device responds to, for example cadmium sulphide responds to visible light while lead sulphide is used for infrared detectors.

## LIGHT EMITTING DIODES

Another type of photodevice is the electroluminescent or light-emitting diode (Fig. 15). This device is made from gallium arsenide or gallium arsenide phosphide, and when a sufficiently high current (a few milliamperes) is passed through, light is emitted. Such diodes can be used as indicator lights directly coupled into, for example, computing systems.

## INTEGRATED CIRCUITS

Of all the semiconductor devices that followed the invention of the transistor, the most revolutionary both in reducing the size of equipment and improving reliability is the integrated circuit.

The problems of manufacturing different circuit elements on the same silicon chip were overcome so that integrated circuits that were both practicable and economic became available by the mid-1960's.

Today two types of integrated circuit (i.c.) are available, the bipolar and MOS, each with their advantages and disadvantages for particular applications.

## BIPOLAR I.C.

The bipolar i.c., as the name implies, uses bipolar transistors manufactured by the planar process. Diodes are formed by a single diffusion, capacitors by using a reverse-biased diode junction, and resistors by a single diffusion like a stretched-out diode with connections at both ends. The main problem with the manufacture of bipolar i.c.s is isolation between components.

## MOS INTEGRATED CIRCUITS

The transistor used in MOS i.c.s is a field-effect transistor, the MOSFET or MOST. Because MOS i.c.s are almost exclusively used in digital applications, an MOST can form the load for another MOST, the transistors are directly coupled, and the capacitances on which information is stored are formed by the gate capacitances of the MOSTs

themselves. Thus only transistors and connections need to be formed on the chip.

One advantage of MOS i.c.s over the bipolar type already mentioned, is the fact that no isolating diffusion is needed on the chip. In addition, an MOST is smaller than the equivalent bipolar transistor. Both these reasons lead to a higher packing density being achieved with MOS i.c.s. On the other hand, bipolar i.c.s have a higher operating speed, and can drive higher current and capacitive loads which MOS i.c.s cannot do without interface circuits.

Thus the choice of MOS or bipolar i.c. may well depend on the requirements of the application rather than any clear-cut advantage of a particular type.

In general, it can be said that small scale integration (SSI) is rarely economical with MOS i.c.s so that gate packs and flip-flops will use bipolar i.c.s.

Large scale integration (LSI) for such devices as random-access memories (RAMs) and read-only memories (ROMs) will use MOS i.c.s. The choice for medium scale integration (MSI) will depend on the application.

## COMPLEMENTARY MOS

A limitation on the use of MOS i.c.s occurs through the use of field-effect transistors. The current-carrying channel for the transistor is formed in the substrate, and so normally only *p*-channel or *n*-channel devices but not both can be formed on any one i.c.

To overcome this, a technique called complementary symmetry MOS or CMOS has been developed. Areas of *p*-material are diffused into an *n*-type substrate so that both *n*-channel and *p*-channel MOSTs can be formed.

More diffusions are required for CMOS than with normal MOS i.c.s, and a lower packing density results. On the other hand, there are considerable advantages for the user, particularly higher operating speeds and lower dissipation.


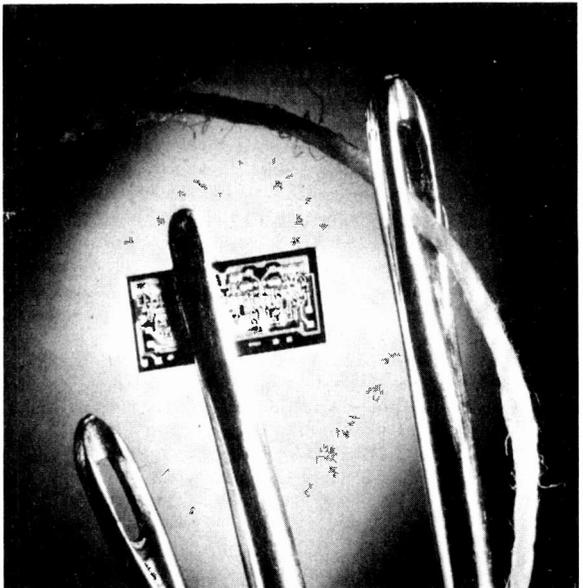


Fig. 16 Integrated circuit chip compared with ordinary sewing needle, the chip being 1.5 × 3mm

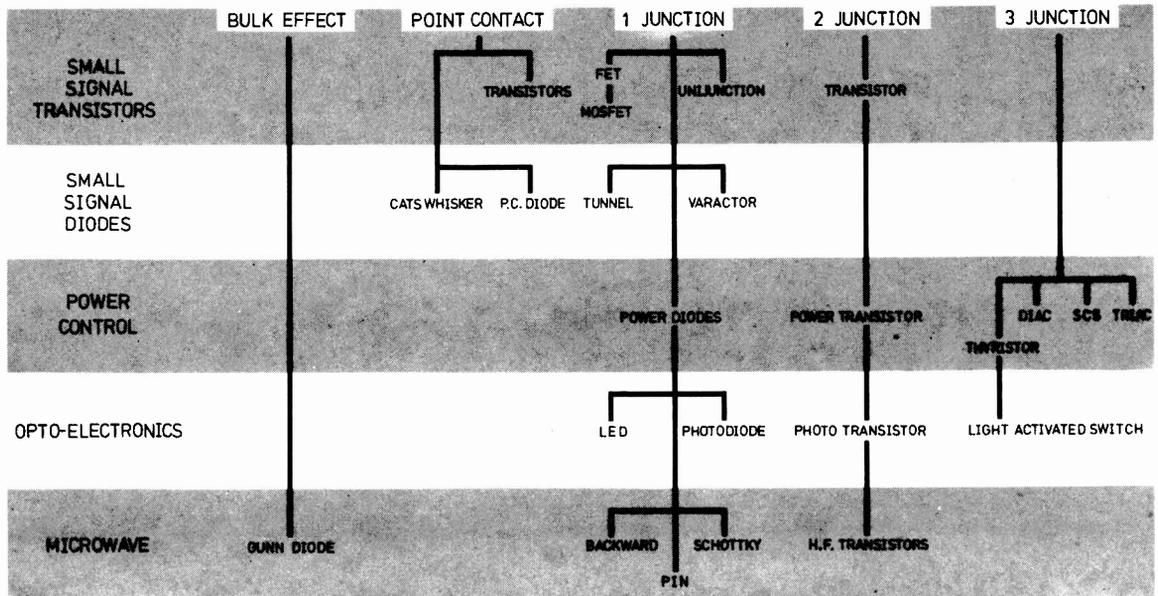

### FAMILY TREE OF SEMICONDUCTOR DEVICES

#### LINEAR I.C.s

The i.c.s described above are digital circuits. Later in the 1960's linear i.c.s were developed. In terms of the number of devices contained, these i.c.s are more complex than the equivalent discrete stages they replace, although cheaper and with better performance. Today a wide range of linear i.c.s is available covering r.f. and i.f. amplifiers, operational amplifiers, TV signal-processing circuits and audio amplifiers with output powers up to several watts.

The reduction in size possible with an i.c. is impressive, typified by such photographs as that in Fig. 16 showing a silicon chip containing over 120 devices passing through the eye of an ordinary sewing needle.

#### COLLECTOR DIFFUSION ISOLATION

Another process which overcomes many of the disadvantages of conventional bipolar i.c.s has been developed by Ferranti from an American idea. Known as the collector diffusion isolation (CDI) process, it makes use of thin epitaxial layers but needs only five masking processes making it comparable to MOS technology in simplicity.

Fig. 17 shows the structure of a CDI transistor. The process uses a *p*-type substrate into which buried low resistivity *n*+ areas are diffused where each resistor, transistor or diode is to be formed. A thin epitaxial *p*-type layer is then diffused. The collector diffusion is then made producing low resistivity *n*+ channels round each component. This diffusion serves three purposes: to make contact with the buried *n*+ area which forms the collector; to provide isolation between components; and to define base and resistor areas.

A shallow *p*-type layer is diffused over the whole slice to define resistor values. A shallow emitter diffusion then follows.

The CDI process reduces transistor areas by up to a third and also enables digital and linear circuits to be combined on one slice. The main disadvantage is that there is no *pnp* transistor available, though

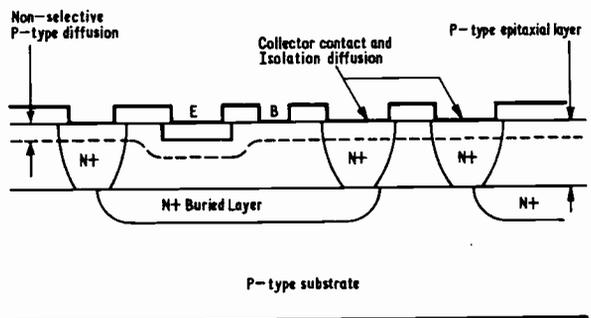


Fig. 17 Structure of a CDI transistor (Ferranti)


a *p*-channel f.e.t. under development should overcome this difficulty.

#### CONCLUSIONS

From the original low-power low-frequency transistor have developed transistors capable of operating high in the radio frequencies, transistors handling powers of over 100W, transistors capable of switching wave-forms with rise times of 1ns. Signal diodes operating in the microwave frequencies have been developed, and diodes and thyristors capable of operating on high-voltage supplies controlling powers measured in megawatts. Devices reacting to and producing light are available, and devices containing a complete computer processing system on a chip only 3.5mm square.

Although the transistor was the fore-runner, the most revolutionary device may well be the integrated circuit which has brought a new concept into electronic circuit design. The thermionic valve (apart from its more specialised forms such as klystrons and magnetrons) had a commercial life of about 35 years. It may well be that the discrete transistor apart from more specialised forms like photodevices will have a shorter life. ★

# 550 VOLT MEGOHMMETER

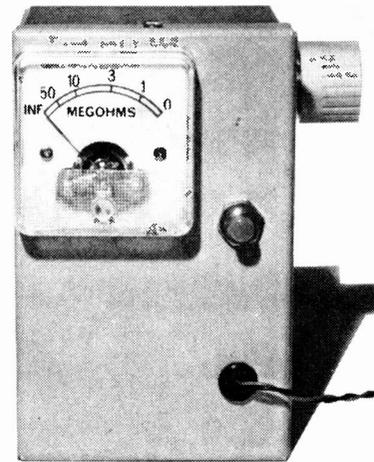

by B. V. Lamb

THE PAST few years have seen more and more householders tackling home wiring installation work. When the work is completed and before the mains can be permanently connected certain safety checks have to be made. This article and project deal with a very useful instrument that will measure the insulation resistance of the wiring.

Poor insulation causes current to flow between the line and earth or neutral. This current in turn will generate heat in the wiring, which if of sufficient temperature could cause fuse blowing or, more seriously, a fire.

Unfortunately, most do-it-yourself wiring enthusiasts do not possess the means for measuring leakage currents at high voltage. Commercially available instruments are expensive and secondhand units are not cheap either. The traditional instrument consists of a hand driven generator that causes a high voltage to appear across a lead terminating in a couple of croc clips, a meter registers the insulation resistance. More recently, electronic testers have tended to replace the hand driven types.

## DESIGN CONSIDERATIONS

The a.c. voltage in the United Kingdom is 240 volts r.m.s.. Since we are interested in peak voltage, and  $V_{\text{peak}} = V_{\text{r.m.s.}} \times 1.414$  the test voltage generator will need to be at least 340 volts. In practice, however, regulations require that a minimum of 500 volts be used.

The 550 volt megohmmeter here described satisfies the twin requirements of the home electrician; it is easy to build and the price is low compared to commercially available units. Push button operation is employed as this prevents inadvertent battery run down due to a switch being left on. All of the components are readily available.

As to the choice of a suitable transistor high voltage generator; the demands made by the Megohmmeter dictate that a sine wave oscillator type d.c. convertor be used. There are three broad types of d.c. convertor that could be used, namely: ringing choke, multivibrator and sine wave.

Each of these circuits produce an oscillating voltage that is stepped up to a higher voltage by means of a transformer and then rectified to give a d.c. voltage at the required level.

Although the least efficient of the three, the sine wave oscillator is the first choice in favour of the ringing choke method when it comes to ease of starting. In economy of components it beats the multivibrator circuit. Since the Megohmmeter does not need to produce more than about 170 microamps under short circuit conditions, a low efficiency high voltage generator does not matter in the least.

## CIRCUIT OPERATION

Transformer T1, TR1 and the associated circuitry form a sine wave oscillator whose period of oscillation is determined by the inductance and self capacitance of T1 (Fig. 1).

The feedback winding of T1 sustains the oscillation and is connected to the junction of R1 and R2 which together with R3 and VR1 set the d.c. bias for TR1. C1 prevents a.c. degeneration. VR1 allows for variation in voltage developed across the collector winding of T1.

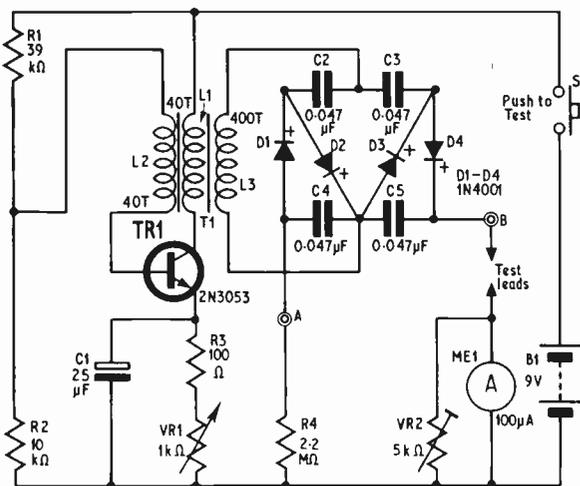


Fig. 1. Circuit diagram of the Megohmmeter

The diodes, D1, D2, D3 and D4 plus the capacitors, C2, C3, C4 and C5 comprise a voltage quadrupler circuit. This circuit rectifies the a.c. voltage appearing across L3 and multiplies by four its equivalent d.c. value.

By varying VR1 over its whole range the open circuit output at the test leads can be varied from approximately 300 to 650 volts. In practice however, the voltage will be set at 550 for normal use. The wide range does allow for increased versatility and the constructor will be able to make use of this from time to time.

## CONSTRUCTION

Dismantle the Ferroxcube core and carefully mount the bobbin on a suitable arbor — the author used a wheelbrace which had a gear ratio of 3.75 : 1 clamped in a bench vice and a 2BA screw as the arbor.

Strip a 2in length of thin pliable plastic sleeve from some spare wire and thread this onto some 41 s.w.g. enamelled copper wire (L3).


Carefully wind 400 turns and finish off L3 by insulating with one turn of Scotch Tape.

Next wind 40 turns of 41 s.w.g. for L2 and similarly insulate. Finally wind 40 turns of 28 s.w.g. for L1 and complete the transformer with a layer of tape.

The rest of the construction is quite straightforward (Fig. 2). The only caution is that building the circuit on inferior leaky tagboard is bound to cause difficulty in getting an infinity reading since leakage current will cause a standing error. The ideal case is plastic although metal can be used if care is taken with insulation.

## SETTING UP

Once the circuit has been built, it is first of all necessary to establish the working of the oscillator.

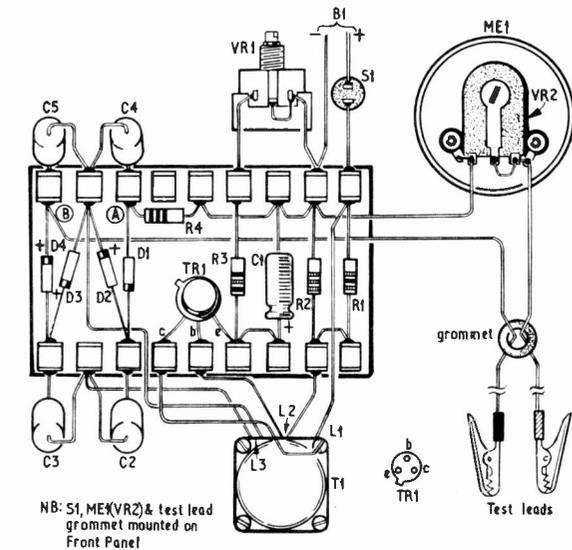

**Fig. 2. Layout of the components on the tagboard and interconnections to the transformer, potentiometer, pushbutton and meter.**

## COMPONENTS . . .

### Resistors

- R1 39k  $\Omega$
- R2 10k  $\Omega$
- R3 100  $\Omega$
- R4 2.2M  $\Omega$
- All  $\frac{1}{4}$ W 10% carbon

### Potentiometers

- VR1 1k  $\Omega$
- VR2 5k  $\Omega$  preset

### Capacitors

- C1 25 $\mu$ F 6.4V electrolytic
- C2, 3, 4, 5 0.047 $\mu$ F 400V polyester (4 off)

### Semiconductors

- TR1 2N3053
- D1, 2, 3, 4 1N4004 or any 400 p.i.v. low current diode (4 off)

### Miscellaneous

- S1 Miniature pushbutton
- ME1 100 $\mu$ A f.s.d.
- T1 Ferroxcube core type LA1 or equivalent
- 9 way Tagboard
- Crocodile Clips (2 off)
- 9V Battery, PP7 or similar
- Metal case 4in  $\times$  2 $\frac{1}{2}$ in  $\times$  2in
- 41 and 28 s.w.g. enamelled copper wire

Short the test clips together and the meter should indicate some value. If no movement is seen the oscillator feedback winding (L2) has to be reversed. Once the circuit is working, the output should be set to 550 volts.

Connect a high resistance voltmeter between points A and B then adjust VR1 for 550 volts. During this operation the test clips must of course be open circuited. The meter can now be calibrated in terms of megohms.

Remove the meter from its case and place it on the working surface having previously cleaned up and dusted down. Carefully remove the scaleplate and paint the reverse side matt white with emulsion paint.


When dry place the scaleplate — with its original markings uppermost — on a piece of cardboard. With a compass find the radius of the scale line and the maximum and minimum positions. Transfer these lines to the blank side. Screw the scaleplate back on the meter.

Short out the test clips and mark the scale with a soft pencil at this point. Now connect 1, 3, 10 and 50 megohm resistors and mark these equivalent points in. A professional job can be done by using plastic film ink for the scale lines and Letraset for the letters and numbers.
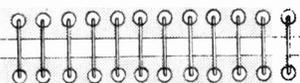
## CONCLUSION


The 550 volt insulation tester that has been described should prove to be a valuable addition to the electricians tool kit. There are of course other uses to which it can be put, insulation tests for the electronic engineer being one example.

By making a simple twin pointed probe, relative dampness in wood and plaster can be measured. ★



# INDUSTRY NOTEBOOK

*By Nexua*

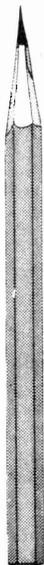

## UPTURN

Yesteryear's sobs and groans from industry salesmen were conspicuously absent at the London Electronic Components Show. Nobody seemed to care that the show was smaller than before and, from first reports, less well attended. Those who came were buyers and that was the important thing.

But it wasn't all smiles and sunshine. The spectre of empty order books may have retreated but only to make way for another spectre to give top management some sleepless nights. What is haunting the industry to-day is how to get components made fast enough to meet the demand. Those major companies which had spare capacity have none today. An even worse fear looming up is a shortage of raw materials.

But, on the whole, things look pretty good. Quipped one exhibitor, "If you can't make a few bucks in these conditions you never will."

This year's Chairman of RECMF, Ronald Bulgin, wore one of the biggest smiles at the show. His publicly quoted family business is still a profit leader in the industry and he will preside as the component industry Chairman in a boom period. What could be better?

Wearing his chairman's hat rather than his company's, he put out a public plea for rationalisation of the exhibition calendar. And he was quite right to do so. In the past six months we have had Electronica in Munich, the Paris Salon and the British show at Olympia. What the industry needs is one big international show a year in Europe with London, Paris and Munich in rotation so that each of the three electronics "capitals" puts on a show every three years.

A sensible idea but unlikely to be accepted by exhibition organisers while they still make huge profits from the present spate of shows. The only hope is that the economic forces of the market place will do what exhortation won't. If enough would-be exhibitors opted out, the exhibition organisers would have to adjust their ideas.

## ROYAL SPOKESMAN

His Royal Highness The Duke of Kent is tipped to succeed Admiral of the Fleet Earl Mountbatten of Burma as an important independent commentator on electronic industry affairs.

As yet, The Duke admits to being "a complete amateur, hardly knowing the difference between R and C." But having heard him speak on the subject I find him well-informed. Naturally, he is briefed in advance of public utterances but I am reliably told that his interest in electronics borders on the enthusiastic and that he is eager to expand his knowledge of the industry not only in its technology but also in its commercial and social impact.

If knowledge is born of experience he should be learning fast. He is a member of the National Electronics Council and opened the London Electronic Components Show and, more recently, Microwave '73 at Brighton.

## THE OLD AND THE NEW

This is a good year for anniversaries. Sperry Gyroscope has just celebrated 60 years in the U.K. with an exhibition opened by Prince Philip, Duke of Edinburgh, at the company's Bracknell HQ. Then there's AVO Ltd., celebrating fifty years in coil winding equipment and instruments (the millionth Avometer left the works as long ago as 1965!).

But what about companies yet unborn? There are plenty on the way to swell the ranks of industry. Expect announcements soon that Jim Griffith, boss of Plastronics, is setting up a manufacturing plant in Germany and that Maurice Hatter, a co-founder of Keyswitch Relays (subsequently sold to Thorn), is moving back into relay manufacture in a plant in Italy. Two new British Euro-babies for the Common Market.

## HI-FI

Cosmocord is looking to hi-fi as a logical expansion based on its long history in pick-up cartridges, audio instruments and, more recently,

head sets and ear protectors. For a start, the company has won the sole U.K. franchise for quality speakers built by Martin in the USA. There is a complete range from about £30 per pair up to £200 for a single 100W multiple speaker unit.

Cosmocord tell me that there is a possibility of making some of the Martin range in the U.K. but following the recent introduction of the ACOS "Lustre" pick-up arm (reported to be doing well), it is more likely that manufacture will be concentrated on tuners and amplifiers to complete the audio chain. Cosmocord marketing men are scanning the market with a keen eye before committing themselves, but if the Martin speakers are to come as part of a Cosmocord hi-fi package my guess is that they are looking at the top end of the market.

The company has now absorbed the Birch-Stolec thumbwheel switch business — renamed Cosmocord-Stolec—which has a turnover of some £250,000 a year. In all Cosmocord is targeted for £1.85 million turnover in the fiscal year just started.

## NOT ALL HONEY

Although the electronics capital goods sector has a more healthy looking order book than last year, things are still sluggish according to the Electronic Engineering Association. Sales at £684.5 million, although marginally higher in total than in the previous year, were in real terms, showing a decline said retiring President Dr B. J. O'Kane in his "state of the industry" address at the EEA annual luncheon. Best areas in the year under review were communications and marine radar, both of which showed gains of better than 20 per cent.


Disturbing and perhaps an uncomfortable experience for Rank-Xerox, brightest and most profitable jewel in the Rank crown, is the impending Monopolies Commission probe. The British inquiry follows the threat to the U.S. parent company of anti-trust action by the U.S. Trade Commission. Curtailing of Rank-Xerox activities could have quite an effect on many of the smaller electronic companies who are engaged in sub-contract work for the company.

Even prosperous Mullard has its black spots. Forecast losses on integrated circuit manufacture this year is £700,000, following losses of nearly £3 million in the past two years. Break-even is forecast by the end of the year and profit by the end of '74, or perhaps a little earlier. Meantime, the really hot lines like colour TV tubes more than make up for the deficiency.
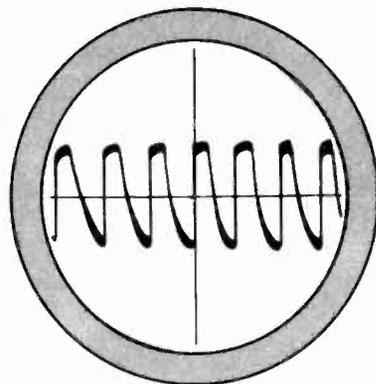
# look! electronics really mastered

... practical  
... visual  
... exciting!

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
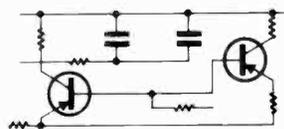
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments, amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW for BROCHURE

or write if you prefer not to cut page

To **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY.** Please send your free brochure, without obligation, to: we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EL83

**special free gift also to all our students**

# ELECTRONORAMA

## STEPS FORWARD IN TIME . . . .

UNTIL 1970 electronic watches seemed to make very little impact on the market, probably because the manufacturers themselves seemed mostly reluctant to invest in this new technology. However three years ago the major Swiss manufacturers unveiled new electronic models incorporating quartz oscillators and it became clear that the whole industry was actively concerned with "the watch of the future".

### THREE TYPES

Since that time electronics have become the major topic of interest and excitement throughout the watch world. Today there are three types of electronic watches driven by batteries. These are tuning fork, quartz and solid state.

Tuning fork watches employ an acoustic resonator (tuning fork) as a timing device and a motor driven by a transistor circuit. Because of this they do not tick but emit a slight hum. The accuracy of these watches is about one minute a month.

Quartz systems with mechanical display use a quartz crystal which oscillates under the effect of an alternating electric field. These oscillations, through a system of circuits and a motor, control the hands of the watch and provide accuracy within 5 seconds a month.

Solid state electronic models show the time in figures with a digital display instead of hands and have no moving parts. They use a quartz crystal oscillator as a timekeeper and activate a liquid crystal or diode display on the face of the watch. Again these have an accuracy of around 5 seconds a month. In addition to these, there are watches which are better described as electric rather than electronic. They employ a conventional hair spring and a balance wheel as the timing mechanism, but are powered by a battery as opposed to a main spring. Their accuracy is no more than that of a comparable conventional watch.

### SIMPLE SERVICING

The advent of electronic watches offers considerable benefits as substantial improvements in accuracy and reliability can be achieved. In addition, problems of after-sales service will be reduced at a time when servicing is increasing in cost and there are fewer skilled watchmakers, because the regular cleaning and maintenance necessary for conventional watches is either considerably reduced or eliminated for electronic models.

### NEW DESIGN CONCEPTS

Omega, part of SSIH (Société Suisse pour l'Industrie Horlogère SA)—the world's third largest watch manufacturer—have announced new design concepts for electronic watches, which made their international debut last month at the Swiss Industries Fair in Basle.

The three new watches are the Megaquartz 2400, the Time Computer and the Megasonic 720. The Megaquartz is a quartz watch with a mechanical display. It has a precision reaching  $\pm$  one second a month in normal wear—the world's most accurate watch.

The Time Computer is a solid state electronic watch with no moving parts, which shows the time digitally. This model has an accuracy within five seconds a month.

The third new model, the Megasonic 720, is an original and entirely new development of the basic tuning fork watch, and has an accuracy reaching 10 seconds a month in normal wear.

### THE MEGAQUARTZ 2400


The Megaquartz 2400 heralds a new generation of quartz watches. Announced as the world's most accurate watch it only varies within one second a month. This remarkable increase in precision over earlier quartz watches (about 1 minute a year) is achieved with a crystal vibration of 2,359,296 times a second.

The first generation of quartz watches used frequencies of up to 65,536Hz. In order to achieve any further technical progress beyond this point it was necessary to increase frequency up to at least 1,000,000Hz, but microelectronic technology was not available to make this practical.

Now with the Megaquartz 2400 Omega have developed a unique electronic microcircuit. This has been achieved by using an analogue circuit dividing the quartz frequency, and by the most advanced CMOS technology in the area of integrated circuits of micropower.

One characteristic of the watch would be important to the "Jet Set", who travel between time zones. In order to maintain the accuracy of the minute and second hands the watch can be immediately adjusted by moving the hour hand alone.

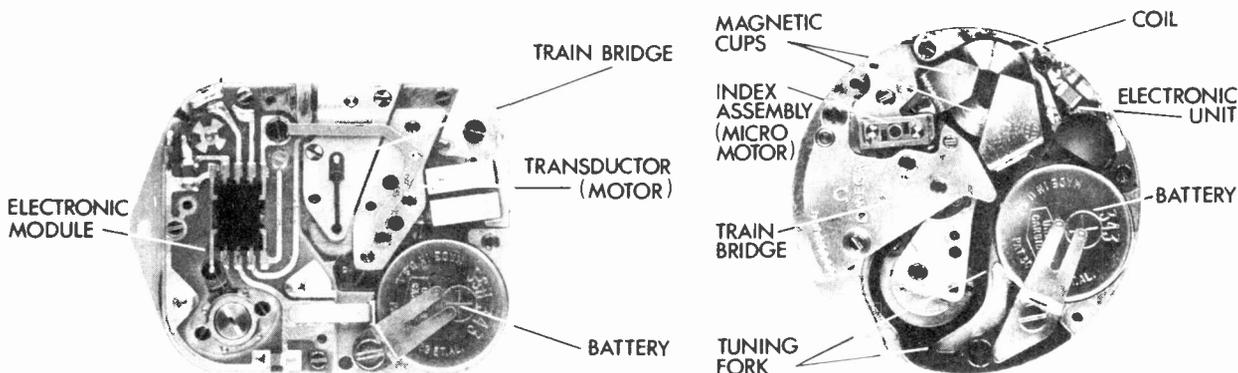Megaquartz 2400 is now in production, and it is expected that it will be available in the U.K. in 1974, at prices starting from £425.



Photograph showing the movement of the Megaquartz 2400, claimed to be the world's most accurate watch

Movement of the Megasonic 720 — the first original development on the basic tuning fork watch



The Time Computer. A solid state digital watch with no moving parts

### THE TIME COMPUTER

The Time Computer is a completely solid state digital watch with no moving parts. The display is by red light emitting diodes arranged for four digits.

Time is shown "on demand" by pushing a command button which illuminates the light emitting diodes covered by a synthetic ruby face, chosen for its hardness and filtering qualities. When the command button is pressed the time in hours and minutes is shown for 1.25 seconds and is then replaced by the seconds for as long as the button remains depressed.

Another advance in this timepiece is its unique system for resetting time that allows hours or minutes to be changed independently. This is an obvious advantage for international travellers constantly flying from one time zone to another. Time is changed by inserting a tiny magnetic key into one of the two timeset recesses in the back of the watch, one linked to the minute digits, the other to the hours. To change the hour only, the magnet is placed into the hour recess, when the face lights up to show the hour digits moving forward.

The Time Computer has the equivalent of 1,238 transistors in a surface area of only  $3.8 \times 3.8$ mm. Its brain is an electronically operated quartz crystal vibrating 32,768 times a second.

The vibrations are counted and the results are fed to the driver decoder circuit, which activates the time display on demand. The watch is powered by two tiny batteries.

Because the watch has no moving parts there is no need for the oiling and cleaning advised for conventional movements.

The Omega Time Computer will be available in the shops within a few months at around £300.

### MEGASONIC 720

Electronic tuning fork (acoustic resonator) watches are well established and proven on the market. Almost all the major manufacturers offer models which are basically derived from the original invention in the 1950's by Max Hetzel.

The Megasonic 720 has distinct advantages over earlier tuning fork watches. It gives a considerable improvement in accuracy to within  $\pm 10$  seconds a month in normal wear, compared with 60 seconds in similar watches. This is achieved by increasing the frequency at which the resonator vibrates to 720 hertz compared to 300/360.

The acoustic resonator is stimulated by an integrated circuit. The movement is transmitted to the train by an original micromotor. The train is driven by magnetic gear, and conventional display shows seconds, minutes, hours, day and date. A mercury battery powers the movement and guarantees it for one year's running.

Its launch is scheduled for 1974 in a new range of models styled Omega Megasonic 720. Retail prices have not yet been finalised, but are expected to be only slightly above existing models.

# TRANSFORMERS

**MAINS ISOLATING SERIES**  
Primary 200-250 Volts Secondary 240 Volts Centre Tapped (120V) and Earth Shielded  
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £	P & P D
07	20	1 11	7.0 x 6.0 x 6.5	1 77	30
100	60	3 8	8.9 x 8.0 x 7.7	2 62	36
61	100	5 12	10.2 x 8.9 x 8.3	2 88	52
30	200	9 8	12.0 x 10.3 x 10.0	4 83	52
62	250	12 4	9.5 x 12.7 x 11.4	6 38	67
55	350	15 0	14.0 x 10.8 x 12.4	8 55	82
63	500	27 0	17.1 x 11.4 x 15.9	12 32	*
92	1000	40 0	17.8 x 17.1 x 21.6	22 70	*
128	2000	63 0	24.1 x 21.6 x 15.2	37 50	*

PLEASE NOTE  
NEW ADDRESS  
AS BELOW

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Tops	P & P £	P & P D
113	20	1 11	7.3 x 4.3 x 4.4	0-115-210-240	0 93	22
64	75	1 14	7.0 x 6.4 x 6.0	0-115-210-240	1 82	30
4	150	3 0	8.9 x 6.4 x 7.6	0-115-200-220-240	2 20	36
66	300	6 0	10.2 x 10.2 x 9.5	...	4 28	52
67	500	12 8	14.0 x 10.2 x 11.4	...	6 35	67
84	1000	16 0	11.4 x 14.0 x 14.0	...	11 54	82
93	1500	28 9	13.5 x 14.9 x 16.5	...	16 72	*
95	2000	40 0	17.8 x 16.5 x 21.6	...	21 82	*
73	3000	45 8	17.4 x 18.1 x 21.3	...	29 70	*

**TOTALLY ENCLOSED 115V AUTO TRANSFORMERS**  
115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets, £8 63, P & P 67p.  
Also available a 20 Watt version, £1 84, P & P 22p.

### LOW VOLTAGE SERIES (ISOLATED)

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Windings	P & P £	P & P D	
111	0.5	0 25	12	7.6 x 5.7 x 4.4	0-12V at 0.25A x 2	0 93	22
213	1.0	0 5	1	8.3 x 5.1 x 5.1	0-12V at 0.5A x 2	1 11	22
71	2	1	1	7.0 x 6.4 x 5.7	0-12V at 1A x 2	1 46	22
18	4	2	2	8.3 x 7.0 x 7.0	0-12V at 2A x 2	2 04	36
79	6	3	12	10.2 x 7.6 x 8.6	0-12V at 3A x 2	2 46	42
108	8	4	5	10.0 x 8.3 x 8.2	0-12V at 4A x 2	2 73	52
72	10	5	6	3 7.9 x 10.8 x 10.2	0-12V at 5A x 2	3 23	52
17	16	8	7	8 12.1 x 9.5 x 10.2	0-12V at 8A x 2	4 99	52
115	20	10	11	13 12.1 x 11.4 x 10.2	0-12V at 10A x 2	6 35	67
187	30	15	16	12 13.3 x 12.1 x 12.1	0-12V at 15A x 2	11 73	82
226	60	30	34	0 17.0 x 14.5 x 12.5	0-12V at 30A x 2	21 57	*

### 30 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Tops	P & P £	P & P D	
112	0.5	1 4	1	8.3 x 3.7 x 4.9	0-12-15-20-24-30V	1 11	22
79	1.0	2 0	7.0	6.4 x 6.0	...	1 48	36
3	2.0	3 2	8.9	7.0 x 7.6	...	2 21	36
20	3.0	4 6	10.2	8.9 x 8.6	...	2 72	42
21	4.0	6 0	10.2	10.0 x 8.6	...	3 23	52
51	5.0	6 8	12.1	10.0 x 8.6	...	4 02	52
117	6.0	7 8	12.1	10.0 x 10.2	...	4 89	52
88	8.0	10 0	14.0	11.7 x 10.0	...	6 20	67
89	10.0	12 2	14.0	10.2 x 11.4	...	7 85	67

### 50 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Tops	P & P £	P & P D
102	0.5	1 11	7.0 x 7.0 x 5.7	0-19-25-33-40-50V	1 46	30
103	1.0	2 10	8.3 x 7.3 x 7.0	...	2 13	36
104	2.0	5 0	10.2 x 8.9 x 8.6	...	2 96	42
105	3.0	6 0	10.2 x 10.2 x 8.3	...	4 01	52
106	4.0	9 4	12.1 x 11.4 x 10.3	...	5 31	52
107	6.0	12 4	12.1 x 11.1 x 13.3	...	7 85	67
118	8.0	18 9	13.3 x 13.3 x 12.1	...	10 25	97
119	10.0	19 12	16.5 x 11.4 x 15.9	...	12 85	97

### 60 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Tops	P & P £	P & P D
124	0.5	2 4	8.3 x 9.5 x 6.7	0-24-30-40-48-60V	1 48	36
126	1.0	3 0	8.9 x 7.6 x 7.6	...	2 06	36
127	2.0	5 6	10.2 x 8.9 x 8.6	...	3 23	42
125	3.0	8 8	11.9 x 9.5 x 10.0	...	4 92	52
123	4.0	10 6	11.4 x 9.5 x 11.4	...	6 35	67
120	6.0	16 12	13.3 x 12.1 x 12.1	...	9 20	82
122	10.0	23 2	16.5 x 12.7 x 16.5	...	15 23	*

### LEAD ACID BATTERY CHARGER TYPES

Ref. No.	Amps	Weight lb oz	Size cm.	P & P £	P & P D
45	1.5	1 9	7.0 x 6.0 x 6.0	1 47	30
5	4.0	3 11	10.2 x 7.0 x 8.3	2 23	42
86	6.0	5 12	10.2 x 8.9 x 8.3	3 37	52
146	8.0	6 4	8.9 x 10.2 x 10.2	3 84	52
50	12.5	11 14	13.3 x 10.8 x 12.1	5 72	67

All ratings are continuous. Standard construction: open with solder tags and wax impregnation. Enclosed styles to order.

**FULL SPEC. TRANSISTORS (E.G.)**  
BC107/108/109 10p each. | 2N 3055 60p each | AD161 162 60p pair  
+ mica and bushes | + mica and bushes

Carriage via B.R.S.

★ Quantity prices on application

**ELECTROSIL RESISTORS • ALCOMETERS**  
**PLEASE ADD 10% FOR V.A.T.**  
INC. P. & P.


**BARRIE electronics**

3, THE MINORIES, LONDON EC3N 1BJ


TELEPHONE: 01-488 3316/8

NEAREST TUBE STATIONS: ALDGATE & ALDGATE EAST

# SIMPLE

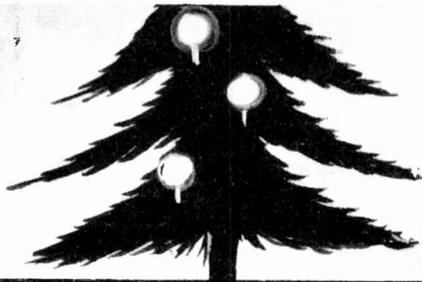

# FLASHER

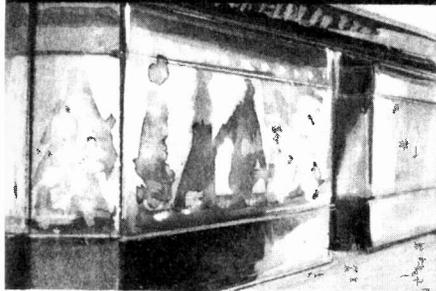

By J. B. DANCE, M.Sc.



IN THE June issue of PRACTICAL ELECTRONICS the introduction of a new integrated circuit, the 555, was discussed in detail from both the theoretical and practical point of view. Only one application as a timer suitable for photography or event control was considered as a constructional project.

Thus we now consider the application of this i.c. to the control of such items as the lights on the Christmas tree or in a window display so as to provide a flashing effect. At the instant the one set of lights is switched off, another set can be switched on if this is desired. The two sets are then illuminated alternately.

## THE CIRCUIT

The type NE555V i.c. which has a dual-in-line encapsulation was used by the writer, but the NE555T in the circular TO-99 encapsulation is equally suitable. Both types have eight connecting leads and contain the equivalent of 23 transistors, two diodes and 16 resistors in a small package.

The 555 is used in the astable mode in this application. In the circuit shown in Fig. 1, the capacitor C1 alternately charges and discharges so that the potential across it varies between  $V_{cc}/3$  and  $2V_{cc}/3$ . Each time the voltage across C1 falls to  $V_{cc}/3$ , the 555 is automatically re-triggered by means of the connection to the trigger pin 2; the capacitor then commences to charge again.

## TIMING

The charging current flows through both R1 and R2. It can be shown that the time for charging from  $V_{cc}/3$  to  $2V_{cc}/3$  is  $0.693(R_1 + R_2)C_1$  seconds where  $R_1$  and  $R_2$  are expressed in ohms and  $C_1$  is expressed in farads. During discharge the current from C1 flows through R2 only; thus discharging takes the shorter time  $0.693R_2C_1$ . The frequency of oscillation is  $1.44/(R_1 + 2R_2)C_1$ . The charging time cannot be made shorter than the discharging time.

If one uses the values for R1, R2 and C1 shown in the circuit, one can calculate that the charging time is 4.8 seconds and the discharging time 3.3

seconds. This should be suitable for the automatic switching of lights in a shop window or on a Christmas tree.

In practice the times will not be exactly equal to the calculated values since the values of the three components will differ somewhat from their marked values. In particular, electrolytic capacitors have very wide tolerances.

The component values can be altered to obtain the desired switching times. However, for applications of this type one does not need to adjust the values critically. One may require shorter times for use in a flashing toy; for example, C1 may be reduced to  $2\mu\text{F}$  or  $1\mu\text{F}$ . The value of the power supply voltage,  $V_{cc}$ , does not affect the switching times appreciably.

## THE RELAY

The relay remains open whilst the capacitor is charging, but closes during the discharging time. A diode must be placed in parallel with the relay in order to suppress the transient back e.m.f.; the latter is generated across the inductive relay coil when the current ceases to flow through it. If the transient voltage is not suppressed with a diode, it could damage the integrated circuit.

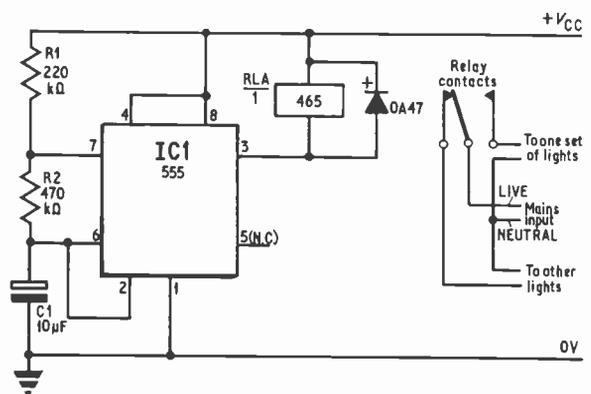


Fig. 1. Circuit diagram for the simple i.c. flasher

The writer used an economical microswitch relay type MS1B designed for printed circuit board mounting. It is readily available (through retailers) from Keyswitch Relays Ltd. The value of the power supply voltage,  $V_{cc}$ , used must match the recommended relay operating voltage to within about 20 per cent. If  $V_{cc}$  is between five and seven volts, an MS1B with a 6V, 50mA coil rating should be employed. Alternatively  $V_{cc}$  may be between 9.5 and 15.5V, in which case the MS1B employed should have a 12V, 26mA coil rating.

The MS1B relay has a single group of change-over contacts which can switch 250V at up to 5A in a.c. circuits. This maximum power of 1.25kW is more than is likely to be required in any shop window of moderate size.

Nevertheless, a larger relay can be used in this circuit if necessary provided that it does not require a current of over 200mA to operate it. Another type of microswitch relay, the Keyswitch Relay type MS2B, has two pairs of change-over contacts each of which can control a current of up to 2A in a 250V a.c. circuit. In d.c. circuits the current ratings of relay contacts are lower (0.2A at 250V and 0.25A at 100V for both the MS1B and MS2B).

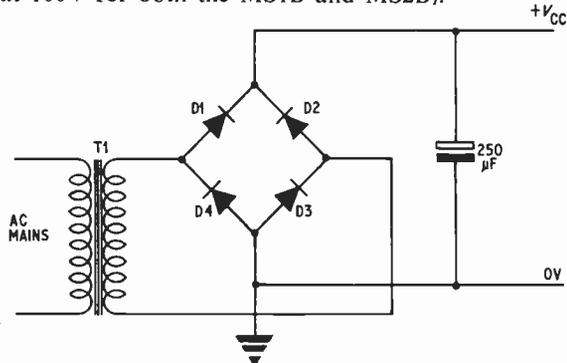


Fig. 2. Circuit diagram for a suitable power supply

## POWER SUPPLY

The circuit of Fig. 1 can be operated from a small battery. Indeed, this is the most sensible source of power to use in a toy for children. The integrated circuit itself requires a current of about 3mA (maximum 6mA) when  $V_{cc}$  is 5V, but the current rises to about 10mA (maximum 15mA) when  $V_{cc}$  is 15V. The relay coil current is additional to these values.

When the circuit is used to switch 250V lamps on and off, it is normally more convenient to employ a small power pack which operates from the mains.

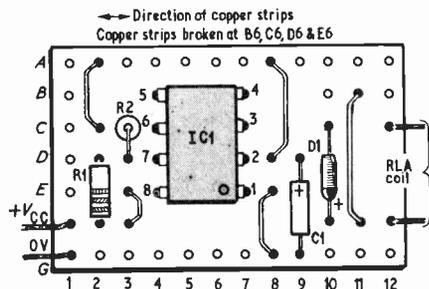


Fig. 3. Board layout for the flasher circuit

## Components

### Resistors

- R1\* 220k  $\Omega$ , 1/10W, 10%
- R2\* 470k  $\Omega$ , 1/10W, 10%

### Capacitors

- C1\* 10 $\mu$ F, 15V electrolytic

### Miscellaneous

- NE555V (or NE555T) Signetics integrated circuit
- OA47 gold bonded germanium diode.
- MS1B relay, 6V or 12V coil (see text).
- Mains three-way input plug if needed.
- One or two two-way output connectors (depending on whether one or two sets of lights are to be switched).
- Eight pin dual-in-line socket (if NE555V used).
- \* Values may be altered to obtain desired switching times.

### POWER PACK

- T1 Small mains transformer with an output of either about 5V or about 10V r.m.s., depending on the relay used (see text).
- D1-4 1N4001 or similar or alternatively one bridge rectifier such as REC 41A (RS Components Ltd.).
- 250 $\mu$ F capacitor, 15V, electrolytic.

The whole system can then be operated from a supply which is switched off at a preset time at night by the normal type of time switch used for controlling the lighting in many shop windows.

A suitable power supply circuit is shown in Fig. 2. The output of the secondary winding of the transformer T1 should be chosen so that it is suitable for the coil operating voltage of the relay used. A 5V r.m.s. transformer winding is suitable for a relay with a 6V coil rating, whilst a 10V r.m.s. winding may be used with a 12V relay. However, these voltages are not very critical.

The output voltage of the transformer may be rectified by four separate diodes (D1 to D4), such as type 1N4001. Alternatively a single bridge rectifier (such as the RS Components type REC 41A) may be used instead of the four diodes.

## CONSTRUCTION


The whole unit, including the mains power pack, may be placed in a small die-cast metal box. One suitable box of approximate external dimensions 114  $\times$  89  $\times$  55mm is available from RS Components Ltd., whilst another type of approximate dimensions 119  $\times$  93  $\times$  52mm is available from Eddystone Radio Ltd.

The metal box should be connected to the mains earth when used with mains equipment for safety reasons. The small mains transformer can be mounted directly on the box, but the remaining components are conveniently mounted on a small circuit board. One can solder directly to the contacts of the 555 integrated circuit, but it is generally more convenient to employ an eight-pin dual-in-line socket if the NE555V is used.

In view of the simplicity of the circuitry and mechanics involved it is deemed unnecessary to discuss construction in greater depth on this project.



# LOGIC TUTOR EXPERIMENTS..

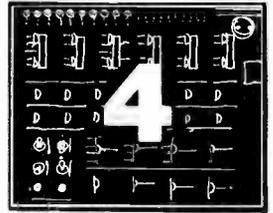

## DE MORGAN'S THEOREM

FIRSTLY the answer to last month's question. There are various ways of getting the six input AND but they all use the same principle. There is an Associative rule in Boolean algebra which says that if you have a number of variables coupled by the same logical functions then the variables can be grouped together in sub-groups and combined by their function independently; the independent groups can then be coupled together with like functions to produce the final desired effect.

Thus if we want to AND together inputs A, B, C, D, E and F we can carry out the operation in three stages; firstly we AND A with B and C (as a sub-group) then D with E and F as a separate sub-group. Finally we take the outputs of each of the sub-groups and AND them together in a two input gate to give the total effect.

One form of six input AND gate using NANDS is shown in Fig. 4.1. Notice that it is necessary to use a lot of gates to carry out what is basically a very simple function. It would be much more economical—in space and cost—to use a six input NAND followed by an inverter or alternatively convert a four input NAND into a six input version using an expander before inverting.

### DE MORGAN'S THEOREM

Referring to the truth table for the NAND we could say that the output is 1 when A is 0 OR B is 0. Remember we are describing the same function as last month but are using a different point of view. Using the Boolean nomenclature that  $\bar{A}$  represents "when A is nought" we can say that the output Q is given by  $\bar{A}$  or  $\bar{B}$

$$Q = \bar{A} + \bar{B}$$

But from a different view point—last month we saw that

$$Q = \overline{A \cdot B}$$

Therefore by normal algebraic argument we can say that

$$\bar{A} + \bar{B} = \overline{A \cdot B}$$

This proves the first of De Morgan's Theorems which—in very simple terms—says that an inverted AND is identical to a sort of inverted OR.

There is a second theorem which is very similar (it is worth you thinking how to argue it out) which says:—

$$\overline{A \cdot B} = \bar{A} + \bar{B}$$

Again in simple terms an inverted OR is the same as a sort of inverted AND.

Before moving on, take note of a catch that beginners sometimes fall into.  $\overline{A \cdot B}$  is not the same as saying  $\bar{A} \cdot \bar{B}$ . This means that when writing Boolean expressions you have to be careful with the length and breaks of the negate bar over the top of the alphabetical characters. Sometimes brackets are used to make the distinction clear in complex expressions.

### OR FROM NAND

De Morgan's Theorem is one of the most used in Boolean algebra because it gives a NAND gate a duality of purpose. Depending on how we want to think we can say that the output is either  $\bar{A} \cdot \bar{B}$  or  $\bar{A} + \bar{B}$ . We have already utilised the former to give us AND from NAND. Now we can use the latter to give us basic OR.

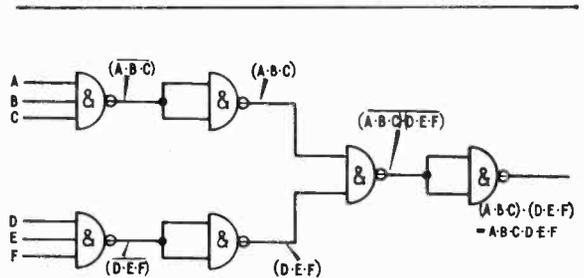


Fig. 4.1. A solution to last month's problem.

Fig. 4.2 shows the way of producing a fundamental two input OR function. The inputs A with B become  $\bar{A}$  with  $\bar{B}$  at the outputs of their respective inverters. The output of the final NAND can be considered to be an OR function coupling the inverted form of its inputs. Therefore the output in this case is  $\bar{\bar{A}} + \bar{\bar{B}}$ . The double negates over each variable cancel and we are left with  $A + B$ .

Use the toggle switches on the Logic Tutor to provide inputs to this circuit and monitor the logic levels at the various nodes on the lamps and check these against the truth table for the circuit shown in Fig. 4.2.

As an exercise try and use the knowledge you now have of the Associative rule and the gates available on Logic Tutor to produce a six input OR. (One answer to be given next month).

by M. Hughes

Next month we shall deal with the EXCLUSIVE OR function.

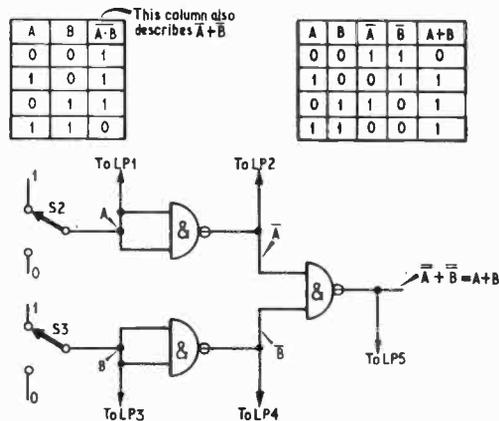


Fig. 4.2. OR from NAND logic.

# NEW DEVICES ...APPLICATIONS

## I.C. TRIAC CONTROL

In this section we present a selection of both new devices and applications, with news of applications developed for existing devices.

Generally only basic circuit details will be given sufficient for the experimenter to create his own equipment.

THE TRIAC is, without a doubt, one of the most convenient forms of a.c. power control yet devised. Provided one supplies it with correctly timed trigger pulses, it will control large amounts of power reliably without taking up too much space.

A variety of methods of supplying the trigger pulse have been developed but thus far these have involved discrete components. Now a new integrated circuit has been developed by Plessey specifically for triac control circuitry. Of necessity it is internally fairly complex as can be seen from the block schematic of Fig. 1.

It includes an amplifier, capacitor charge and discharge control circuitry, a comparator, a voltage stabiliser, a zero crossing detector and a triac firing circuit.

The basic function performed by this SL440 as the device is identified is in phase control circuits in which the power in the load depends on the phase angle or point on the a.c. cycle, at which the triac is fired. The extra facilities offered by the SL440 enable various circuits to be implemented with the bare minimum of external discrete components.

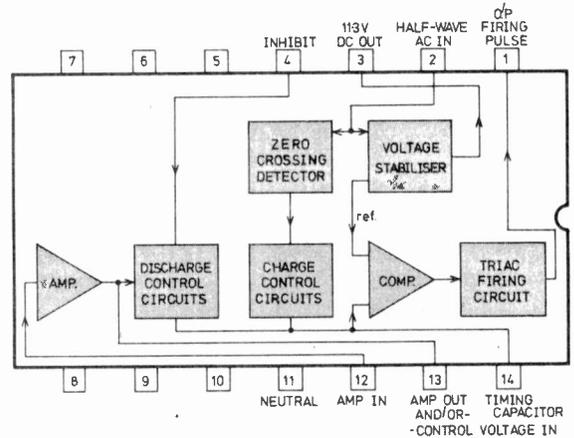


Fig. 1 Block schematic diagram of the SL440

### TIMING CIRCUIT

The SL440 contains a timing circuit with a period determined by external control voltages. It is the timing circuit's period which determines exactly when in each half cycle of the mains power supply the triac is fired.

This is illustrated diagrammatically in Fig. 2. Whenever the mains power supply crosses through zero volts,

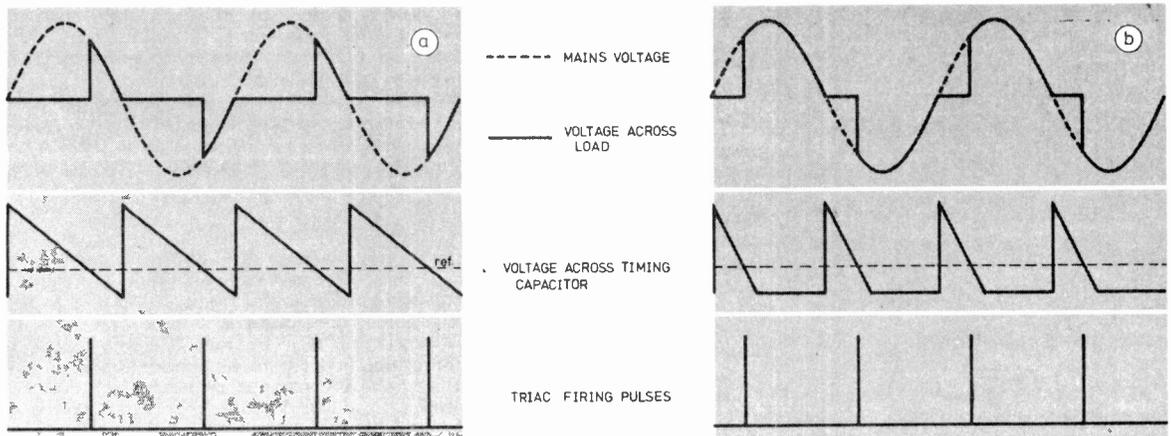


Fig. 2 (a) When the voltage across the timing capacitor falls below the on-chip reference voltage a triac firing pulse is generated. (b) When the capacitor is discharged more quickly, more power is applied to the load

either in the positive or negative direction, a capacitor external to the i.c., but connected to it, is rapidly charged.

During the following half cycle the capacitor discharges at a rate determined by an external control voltage until the voltage across the capacitor falls to a level set within the i.c. When this occurs a pulse is generated which fires the triac.

In Fig. 2a the effect of quite a long timing period is illustrated. As the mains power supply crosses through zero the timing capacitor connected to pin 14 is charged. During each half cycle the capacitor discharges at a constant rate until the voltage across it reaches the same value as the reference when a triac firing pulse is generated.

In the illustration the dotted sinewave represents the mains supply while the solid line indicates the voltage across the load.

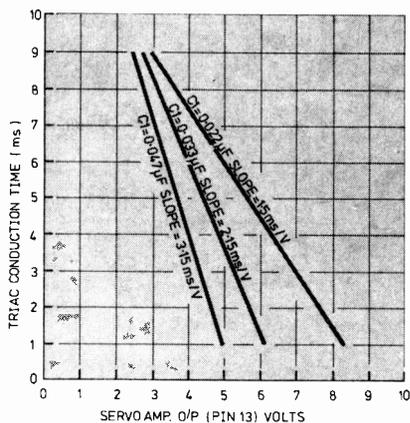


Fig. 3 Showing triac conduction time for different values of timing capacitor and different voltages at pin 13

### DISCHARGE RATE

The external control voltage setting the discharge rate would normally range from 3 to 8 V, this being sufficient to alter the power in the load from zero to full power. An inverse law applies in that the lower the control voltage the higher the power in the load. The actual power in the load for a given control voltage is also dependent on the value chosen for the timing capacitor.

The larger the capacitor's value the greater the power applied to the load for a given control voltage. These relationships can be seen in Fig. 3, which plots the control voltage against triac conduction time for three different values of timing capacitors.

### ON-CHIP AMPLIFIER

The SL440 integrated circuit incorporates an amplifier, called a servo amplifier by Plessey, which can be used to produce the control voltage. It can really be looked at as a grounded emitter amplifier with a beta of about 2,000 and a 2 kΩ resistor in the emitter. It is necessary to connect a suitable external load resistor.

The amplifier is useful in motor speed control as an error voltage amplifier or it can be connected as an

integrator in automatic lamp dimmer circuits and the like.

### VOLTAGE STABILIZER

The SL440 contains a voltage stabilizer which performs three main functions. Firstly, it provides a stabilized 11.3 V supply for the rest of the chip; it also provides the reference voltage against which the voltage across the timing capacitor is compared and, finally, it provides a stabilized 11.3 V supply for circuitry external to the chip. However, the current available for off-chip circuits is extremely limited and must not be allowed to exceed 3 mA.

### MAINS INPUT

The SL440 does not require a d.c. power supply in the conventional sense. Power input is obtained directly from the mains via a diode and series dropping resistor. With

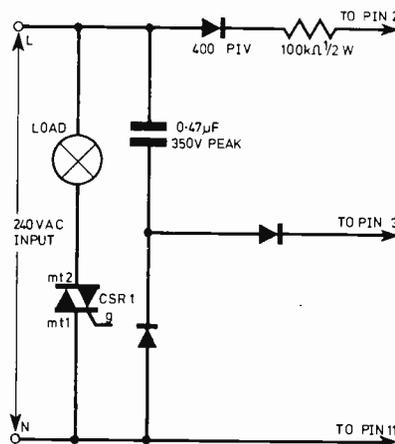


Fig. 4 A circuit to replace the heat dissipating mains dropper resistor

the values recommended by Plessey, the half-wave rectified input has a peak value of about 60 or 70 V. The series resistor (6.8 kΩ, 5 W) can be eliminated with the circuit shown in Fig. 4.

The half-wave rectified input, as well as supplying power, also allows the chip to detect the zero crossings of the mains. Each time a zero crossing is detected the circuitry on the chip charges the external timing capacitor.

### OUTPUT AND INHIBIT

When the voltage across the timing capacitor falls below that of the reference voltage supplied to the comparator from the voltage stabilizer, an output triac firing pulse is generated. This pulse is 50 µs wide and must not be allowed to exceed 60 mA. However, this will be more than sufficient for most applications.

An inhibit input is provided which, when connected to the common line (or less than 5 V), prevents any firing pulses from being generated. This input could be used in conjunction with current sensing circuits for protection purposes.

APPLICATIONS

# ALL OUR PRICES INCLUDE V.A.T.

## BSR LATEST SUPERSLIM STEREO & MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. AC 200/250V Size 13 1/2 x 11 1/2 in. Above motor board 3 in. below motor board 2 1/2 in.



with STEREO and MONO XTAL £8.25 Post 25p.

## PORTABLE PLAYER CABINET

Modern design. Black resin covered. Silver front grille. Chrome fittings.

Motor board cut for BSR deck £4.50 Post 25p

## E.M.I. WOOFER AND TWEETER KIT £5.75

Available separately Post 25p.  
Wooler £4.25 Tweeter £1.90  
Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in. with a massive Ceramic Magnet, 440z. Gauss, 13,000 lines. Aluminium cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 in. square has a special light-weight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.



Impedance Standard 8 ohms  
Maximum Power 12 watts  
Useful Response 35 to 18,000 c/s  
Base Resonance 45 c/s  
SUITABLE ENCLOSURE 20 x 13 x 9 in.  
MODERN GROOVED FRONT DESIGN.  
TEAK FINISH £9.90 Post 25p

## SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch. Light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 60 minutes Type A or 0 to 6 hours Type B. Makers last list price £4.50. Brand new and fully guaranteed. Fully insulated. OUR PRICE £1.65. P & P 15p or £3 pair. (PLEASE STATE TYPE A OR B WHEN ORDERING)



## WEYRAD P50 — TRANSISTOR COILS

RA2W Ferrite Aerial 72p	Spare Cores 3p
Osc. P50/1AC 35p	Driver Trans. LFDT4 58p
L.F. P50/CC 470 kc/s 36p	Printed Circuit, PCA1 58p
8rd L.F. P50/CC 36p	J.B. Tuning Gang 65p
P51/1 or P51/2 38p	Weyrad Booklet 10p
P50/3V 36p	OPT1 58p

Mullard Ferrite Rod 8 x 1/2 in. 20p. 6 x 1/2 in. 20p.

## VOLUME CONTROLS 80 Ohm Coax 4p yd.

5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. EDGE 5K.S.P. Transistor 25p.

BRITISH AERIALITE AERIAL-AIR SPACED 40 yd. £1.40; 60 yd. £2. FRINGE LOW LOSS 10p yd. Ideal 625 and colour

## 8 in. or 10 in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 c/s. Bass resonance 55 c/s. 8 ohm impedance. 8 in 10 watts, 10 in 12 watts music power. £3.75 Post 25p



## E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With twin tweeters. £4.50  
Basic res. 45-60 c/s. Flux 10,000 gauss. Size 3 or 8 or 15 ohm. As illustrated. Post 25p



With flared tweeter cone and ceramic magnet. 10 watt. Basic res. 45-60 c/s. Flux 10,000 gauss. Size 3 or 8 or 15 ohm. Post 25p

## Bookshelf Cabinet 16 x 10 x 9 in. £5.50

## BRITISH MADE STEREO MULTIPLEX DECODER £6.95

Brand New. 7 transistors Plus integrated circuit. Fibre-Glass printed circuit board. Size 21 x 8 1/2 x 1. Pre-Aligned. Complete with stereo beacon detector. 12V d.c. operation. 400mV Output for 100mV Input. Full instructions for any FM Tuner. Some technical experience essential.

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in sides 6 x 4 in 45p; 6 x 6 in 53p; 10 x 7 in 65p; 12 x 8 in 85p; 14 x 9 in 90p; 16 x 6 in 90p; 12 x 3 in 50p; 16 x 10 in £1. ALUMINIUM BOX 8 x 4 x 4 in 80p. ALUMINIUM PANELS 18 s.w.g. 6 x 4 in 9p; 8 x 4 in 25p; 14 x 3 in 15p; 10 x 7 in 19p; 12 x 5 in 20p; 12 x 6 in 25p; 16 x 6 in 28p; 14 x 9 in 34p; 12 x 12 in 40p; 16 x 10 in 50p. PAXOLIN PANEL 10 x 8 in 15p.

## ANOTHER R.C.S. BARGAIN! 4 TRANSISTOR MONO AMPLIFIER

Powerful 3 watt output, 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make. £5.95 25p  
Suitable 7" x 4" speaker, £1.

## R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 8 or 12 or 15 or 18 or 20V d.c. at 100mA or less. £2.20 15p  
PLEASE STATE VOLTAGE REQUIRED. Post Details S.A.E. Size 3 1/2 x 1 1/2 in.

## R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1 1/2 x 1 1/2 in. Response 25 c/s to 25 kc/s, 26 dB gain. For use with valve or transistor equipment. 99p Post 10p  
Full instructions supplied. Details S.A.E.

## COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2 x 10 x 8 1/2 in. 3 watts per channel, plays all records 33 1/3 rpm 45 rpm. Separate volume and tone controls. 240V AC mains. Attractive £25 Plus 85p carriage.

## BRITISH FM/VHF TUNING HEART

88 to 108 M/CS British made. 2 Transistors ready aligned requires 10-7 M/CS I.F. Complete with tuning gang. Connections supplied but some technical experience essential. Our price £3.95 Post 20p

## MAINS TRANSFORMERS

Eagle MT12 12-0-12V 50mA	All post 25p each	90p
250-0-250 80mA 6-3V 3-5A, 6-3V 1A, or 5V 2A		£2-50
350-0-350 80mA, 6-3V 3-5A, 6-3V 1A, or 5V 2A		£3
300-0-300V 120mA, 6-3V 4A C.T., 6-3V 2A		£3-25
MINIATURE 200V, 20mA, 6-3V 1A, 2 1/2 x 2 1/2 x 2 in		75p
MIDGET 220V 45mA, 6-3V 2A, 2 1/2 x 2 1/2 x 2 in		90p
HEATER TRANS. 6-3V 3A		60p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 1A, 2A, 3A, 4A, 5A, 6A, 8A, 9A, 10A, 12A, 15A, 18A, 24A and 30V		£2-25
1A, 6A, 8A, 10A, 12A, 18A, 20A, 30A, 36A, 40A, 48A, 60V		£2-25
2A, 6A, 8A, 10A, 12A, 18A, 20A, 24A, 30A, 36A, 40A, 48A, 60V		£2-25
3A, 6A, 8A, 10A, 12A, 18A, 20A, 24A, 30A, 36A, 40A, 48A, 60V		£2-75
5A, 5A, 8A, 13V 11-0, Dito 5A		£1-20
3A, 5A, 8A, 10A, 13V, 5-0-5V £1-30, Dito 5A		£1-50
6-0-6 500 mA		90p
9V 1 amp		95p
12V 300 mA		75p
12V 500 mA		85p
12V 750 mA		95p
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V. 150W £2-25; 500W £6-25; 750W £10; 1000W £15.		
CHARGER TRANSFORMERS. Input 200/250V for 6 or 12V. 1A £1-50; 2A, £1-80; 4A, £2-50.		
BATTERY CHARGERS. 1 1/2A £2; 3A £3; 4A £4; 6A £4-50.		

## MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. OUR PRICE £10 Carr. Famous make. (Value £18)  
Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V.

## NEW ELECTROLYTIC CONDENSERS

2/350V 14p	250/25V 14p	50+50/350V 35p
4/350V 14p	500/25V 20p	60+100/350V 58p
8/450V 14p	1000/25V 35p	32+32/250V 18p
16/450V 15p	1000/50V 47p	32+32/450V 33p
32/450V 20p	8+8/450V 18p	350+50/325V 50p
25/25V 10p	8+16/450V 20p	32+32+32/350V 43p
50/50V 10p	16+16/450V 25p	100+50+50/350V 48p
100/25V 10p	32+32/350V 25p	

## LOW VOLTAGE ELECTROLYTICS

1.2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
500mF 12V 15p; 25V 30p; 50V 50p.  
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.  
2000mF 6V 25p; 25V 42p; 50V 57p.  
2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.  
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 86p; 50V 95p.

CERAMIC, 1pF to 0.01mF 4p. Silver Mica 2 to 5000pF 4p. PAPER 350V-0.1 4p, 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1"m. 2-2-500F 8p; 580-2-200F 10p; 2-700-5-800F 20p; 6-800F 0-01, mid 30p each. TWIN GANG. "0-0" 208pF +176pF 8p; 500pF standard 45p. 365pF +365pF with 25pF +25pF. Slow motion drive 50p. SHORT WAVE SINGLE 10pF 30p, 25p, 50p, 50pF 55p. NEON PANEL INDICATORS 250V AC/DC. Amber 20p. RESISTORS. 1/4W, 1/2W, 1W, 2W, 5W, 10W, 100W, 1000W. HIGH STABILITY. 1/4W 2%, 10 ohms to 6 meg., 100p. Dito 5%. Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 1000 ohm each. 0.5 ohm to 50 ohms 10p. TAPE OSCILLATOR COIL Valve type 35p.

## ALL MODELS "BAKER SPEAKERS" IN STOCK Hi Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p Post Free

## BAKER MAJOR 12" £9.90

Post 25p  
30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 ohms must be stated.  
Module kit, 30-17,000 c/s with tweeter, crossover, 800 ohm and 15 ohm instructions. £12.50  
Please state 3 or 8 or 15 ohms. Post 25p

## BAKER "BIG-SOUND" SPEAKERS Post 25p

'Group 25' 12in. 25W 3 or 8 or 15 ohm	'Group 35' 12in. 35W 3 or 8 or 15 ohm	'Group 50' 15in. 50W 8 or 15 ohm
£8.80	£9.90	£22

TEAK VENEERED HI-FI SPEAKER CABINETS. For 12in or 10in dia. speaker 20 x 13 x 9 in. £9.90. Post 25p. For 13 x 8 in or 8in speaker 16 x 10 x 9 in. £5.50. Post 25p. For 8 x 5 in speaker 16 x 8 x 8 in. £4.40. Post 25p. For 6in and Tweeter 12 x 8 x 6 in. £4.00. Post 25p. LOUDSPEAKER CABINET WADDING 18in wide, 15p ft.

## GOODMANS 6 1/2 in. HI-FI WOOFER

8 ohm, 10W. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. Suitable Cabinet 12 x 8 x 6 1/2 Suitable Tweeter £2



## ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 2 1/2 in deep. Rating 10W, 3 ohm or 15 ohm models. £1.90 Post 10p. Crossover 85p

## SPEAKER COVERING MATERIALS. Samples Large S.A.E.

Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £1-95. De Luxe Horn Tweeters 2-18kc/s, 15W, 15 ohm £3. CROSSOVERS, TWO-WAY 3,000 c/s 3 or 8 or 15 ohm 95p. LOUDSPEAKERS P.M. 3 OHMS. 7in dia., £1-25; 6in, £1-50; 8 x 5in, £1-60; 10in, £2-00; 8in, £1-75; 10 x 6in, £1-90. SPECIAL OFFER: 82 ohm, 2 1/2 in, 2 1/2 in; 35 ohm, 2 1/2 in, 3 in, 2 1/2 in; 3 1/2 in dia., 3 in dia., 5 in dia. £1 EACH TYPE 15 ohm, 3 1/2 in dia., 8 x 4 in, 7 x 4 in, 8 x 5 in. 3 ohm, 2 1/2 in, 2 1/2 in, 5 in dia., 6 x 4 in, 5 ohms 11-50. RICHARD ALLAN TWIN COIL LOUDSPEAKERS. 8in. diameter 4W; 10in diameter 5W £2-20; 12in diameter, 6W, £2-50; 3 or 8 or 15 ohm models, £2-20 each. Post 15p. VALVE OUTPUT TRANS. 25p; MIKE TRANS. 50:1 25p. 5 WATT MULTI-RATIO, 3, 8 and 15 ohms 80p. Mike trans. mu metal 100:1 £1-25.

## MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 input speech and music. 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E. £49 Carr. £100



## BARGAIN AM TUNER. Medium Wave. Transistor Superhet, Ferrite aerial. 9 volt. £4.95

## BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. STEREO VERSION OF ABOVE £5.95

## BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control and on/off switch, 18 volt. £4.50

## COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET BOXES, SURFACE OR FLUSH 25p.

BALANCED TWIN RIBBON FEEDER 300 ohms. 5p yd. JACK SOCKET Std. open-circuit 14p, closed circuit 23p; Chrome Lead-Socket 45p; Phone Plugs 5p; Phone Socket 5p. JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 6-pin 10. DIN SOCKETS Lead 3-pin 10p; 5-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS. 5p; CERAMIC 8p; CANS 5p.

## DELUXE 4 POLE MOTOR

1,400 r.p.m. 42 Watt, spindle 1 1/2" x 3/8", size 3 1/2" x 4". As illustrated. Post 25p. £19.95

## TWO RPM GEARED MOTORS 95p Post 25p.

240V A.C. mains. Ideal for displays/disc light wheels. E.M.I. GRAM. MOTOR. 120V or 240V a.c. £1 2,400 r.p.m. 2 pole 70mA. Size 2 1/2 x 2 1/2 in. Post 25p.

337 WHITEHORSE ROAD, CROYDON  
Open 9-6, Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30)  
Buses 50, 68, 157. Rail Selhurst. Tel. 01-684-1665

# YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT  
KEMPSTON HARDWICK  
BEDFORD

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the  
components listed will be sent free on request.  
10p stamp appreciated.

OPEN ALL DAY SATURDAYS

ALL PRICES SUBJECT TO V.A.T.

## RESISTORS

1/4W Iskra high stability carbon film—very low noise—capless construction.  
1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm.  
1/2W 2% ELECTROSIL TRS

Power watts	Tolerance	Range	Values available	Price
1/4	5%	4.7Ω-2.2MΩ	E24	1p
1/4	10%	3.3MΩ-10MΩ	E12	1p
1/4	2%	10Ω-1MΩ	E24	3.5p
1/4	10%	1Ω-3.9Ω	E12	1p
1/2	5%	4.7Ω-1MΩ	E12	1p
1/2	10%	1Ω-10Ω	E12	6p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.  
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ±W, lin ±W).  
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

## SKELTON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.  
mounting (0.1 matrix).  
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 6p each.

## TRANSISTORS

AC107	15p	AF125	20p	BD132	75p	OC28	50p	2N3702	13p
AC126	12p	AF126	20p	BD133	75p	OC35	50p	2N3703	12p
AC127	12p	AF127	20p	BF115	25p	OC42	12p	2N3704	13p
AC128	12p	AF139	32p	BF173	20p	OC44	12p	2N3705	12p
AC131	12p	AF178	32p	BF177	28p	OC45	12p	2N3706	11p
AC132	12p	AF180	40p	BF178	32p	OC70	12p	2N3707	12p
AC176	12p	AF181	40p	BF179	32p	OC71	12p	2N3708	10p
AC187	22p	BC107	9p	BF180	32p	OC72	12p	2N3709	11p
AC188	22p	BC108	9p	BF181	32p	OC81	12p	2N3710	11p
AD140	50p	BC109	9p	BF194	15p	OC82D	12p	2N3711	11p
AD149	50p	BC147	13p	BF195	15p	2N2904	20p	2N4062	12p
AD161	33p	BC148	13p	BF197	15p	2N2926R	9p	40360	35p
AD162	36p	BC149	13p	BF200	32p	2N2926O	9p	40361	40p
AF114	20p	BC157	14p	BFY50	20p	2N2926Y	9p	40362	40p
AF115	20p	BC158	14p	BFY51	20p	2N2926G	9p	40408	40p
AF116	20p	BC159	14p	BFY52	20p	10p	ZTX302	15p	
AF117	20p	BC187	22p	BU105	225p	2N3054	58p	ZTX500	15p
AF124	22p	BD131	75p	OC26	45p	2N3055	60p	ZTX502	20p

## ZENER DIODES

400mW 5% 3.3V to 30V, 12p. | WIRE WOUND POTS, 3W, 10, 25,  
50Ω and decades to 100kΩ, 35p.

## DIODES

### RECTIFIER

BY127	1250V	1A	12p
BZ710	800V	6A	25p
BZ713	200V	6A	20p
IN4001	50V	1A	7p
IN4004	400V	1A	8p
IN4007	1000V	1A	8p

### SIGNAL

OA85	7p
OA90	5p
OA91	7p
OA202	7p
IN4148	8p
BA114	5p

## BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2in = 10p; 9in x 2in = 7p

## SLIDER POTENTIOMETERS

8mm x 9mm x 16mm, length of track 59mm.  
SINGLE 10k, 25k, 100k etc. or lin, 40p.  
DUAL GANG 10k + 10k etc. or lin, 60p.  
KNOB FOR ABOVE 12p.  
FRONT PANEL 65p.  
18 Gauge panel 12in x 4in with slots cut for use  
with slider pots. Grey or matt black finish complete  
with fixings for 4 pots.

## THERMISTORS

VA10555	15p
VA10665	15p
VA1077	15p
RS3	£1.35

## THYRISTORS

2N5060 50V 0.8A 30p.
2N5064 200V 0.8A 47p.
CRS1/40 400V 1A 25p.
106F 50V 4A 40p, 106D 400V 4A 55p.

## MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 21p, 0.0068μF, 0.01μF,  
0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7.5p,  
0.33μF, 11p, 0.47μF, 13p.  
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF 3.5p, 0.15μF 4.5p,  
0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7.5p, 0.68μF, 11p, 1.0μF, 13p.

## MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF,  
3p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6p, 0.47μF, 8p, 0.68μF, 11p, 1.0μF, 13p,  
1.5μF, 20p, 2.2μF, 24p.

## MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF,  
2.2p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3.5p.

## CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

## ELECTROLYTIC CAPACITORS—MULLARD O15/6/7 RANGE REPLACES C426, C457 RANGES.

(μF/V) 1/0/63, 1/5/63, 2/2/63, 3/3/63, 4/7/63, 6/8/40, 10/25, 10/63, 15/16, 15/40, 15/63,  
22/10, 22/25, 22/63, 33/63, 33/40, 47/4, 47/10, 47/25, 47/40, 47/63, 68/63, 68/16, 100/4,  
100/10, 100/25, 100/40, 150/63, 150/16, 150/25, 220/4, 220/10, 220/16, 330/4, 330/10,  
470/63, 5p each. 68/63, 150/40, 220/25, 330/16, 470/10, 680/63, 1,000/4, 9p, 100/63,  
150/63, 220/40, 470/25, 680/16, 1,000/10, 1,500/63, 12p, 220/63, 470/40, 680/25,  
1,000/16, 1,500/10, 2,200/63, 15p, 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10,  
3,300/63, 4,700/4, 18p.

## SOLID TANTALUM BEAD CAPACITORS

0.1μF	35V	2.2μF	35V	22μF	16V	13p
0.22μF	35V	3.3μF	35V	33μF	10V	10p
0.47μF	35V	6.8μF	25V	47μF	6.3V	3p
1.0μF	35V	10μF	25V	100μF	3V	12p

## VEROBOARD

2 1/2 x 3 1/2	0.1	0.15
2 1/2 x 5	22p	16p
2 1/2 x 7 1/2	24p	24p
3 1/2 x 5	24p	24p
3 1/2 x 7 1/2	27p	27p
17 x 2 1/2	75p	57.5p
17 x 3 1/2	100p	78p
17 x 5 (plain)	—	82p
17 x 7 1/2 (plain)	—	60p
17 x 2 1/2 (plain)	—	42p
2 1/2 x 5 (plain)	—	12p
2 1/2 x 3 1/2 (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

## JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

## D.I.N. PLUGS AND SOCKETS

2 pin 3 pin, 5 pin 180°, 5 pin 240°, 6 pin  
Plug 12p. Socket 8p.  
4 way screened cable, 15p/metre.  
6 way screened cable 22p/metre.

## BATTERY ELIMINATOR

£1.50  
9V mains power supply. Same size as PP9 battery.

## LARGE (CAN) ELECTROLYTICS

1600μF 64V 74p	2500μF 64V 80p	4500μF 16V 50p
2500μF 40V 74p	2800μF 100V £2.60	4500μF 25V £1.68
2500μF 50V 58p	3200μF 16V 50p	5000μF 50V £1.10

## HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF 10p	0.047μF 13p	0.22μF 20p
0.022μF 12p	0.1μF 13p	0.47μF 22p

## POLYSTYRENE CAPACITORS 160V 2 1/2%

10pF to 1,000pF E12 Series Values 4p each.

## SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.  
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector £5.20. 12 or 24V battery operated audible alarm £7.30. As above for PP9 battery, £6.40.

## PRINTED BOARD MARKER

97p  
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

# LARGE RANGE IIT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

7400	1-11	12-24	25-99	100+	7448	185	175	170	165	74118	100	82	73	64
7401	18	16	14	13	7450	18	16	14	13	74121	43	40	38	36
7402	18	16	14	13	7451	18	16	14	13	74141	100	95	90	85
7403	18	16	14	13	7453	18	16	14	13	74150	150	140	135	130
7404	20	18	16	14	7454	18	16	14	13	74155	330	280	250	220
7405	20	18	16	14	7460	18	16	14	13	74151	110	100	95	89
7406	30	18	16	14	7470	30	28	25	24	74153	120	110	105	95
7407	50	45	40	35	7472	30	28	27	23	74154	200	180	170	160
7408	36	30	27	23	7473	40	38	36	30	74155	150	120	100	86
7409	36	30	27	23	7474	40	36	32	28	74156	130	120	100	96
7410	18	16	14	13	7475	55	52	50	49	74180	155	136	112	105
7411	23	21	20	18	7476	40	36	32	30	74190	195	190	185	180
7412	36	30	27	23	7480	100	95	90	85	74191	195	190	185	180
7413	34	28	22	22	7481	125	115	110	105	74192	200	190	180	164
7416	45	39	34	34	7482	100	96	90	85	74193	200	180	170	150
7420	18	16	14	13	7483	100	97	90	85	74196	200	190	180	170
7421	36	30	27	23	7484	120	115	110	105	74197	200	195	180	170
7426	32	29	23	20	7485	250	245	240	230					
7430	20	18	16	14	7486	45	42	37	33					
7432	40	36	32	28	7490	75	67	60	52					
7440	20	18	16	14	7491A	100	92	85	79					
7441	80	75	70	65	7492	75	70	65	60					
7442	80	75	70	65	7493	75	68	60	52			</		

# Typical APPLICATIONS

## LIGHT DIMMER

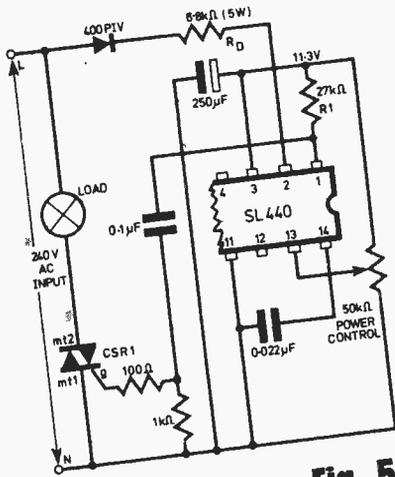


Fig. 5.

## AUTO LIGHT


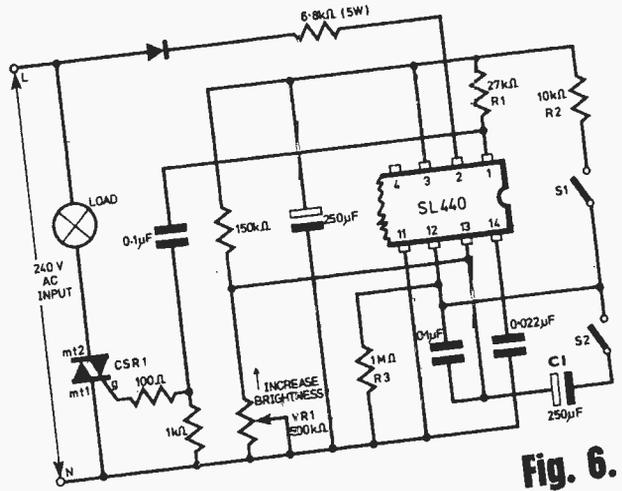


Fig. 6.

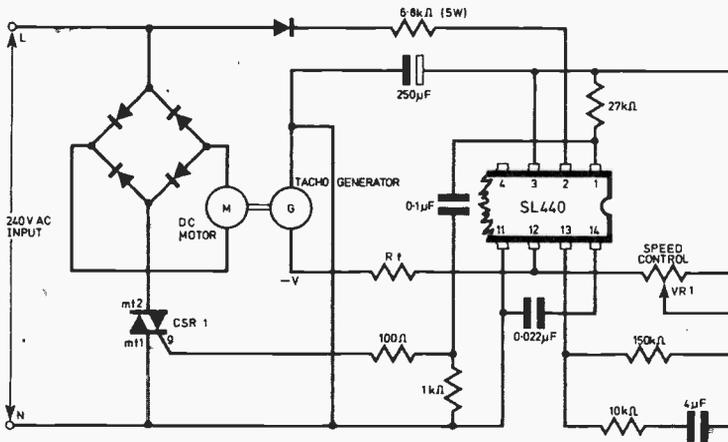

## SPEED CONTROL

Fig. 7.

### APPLICATIONS

Numerous applications for the device will have probably already suggested themselves to the reader. Plessey have developed several circuits.

Fig. 5 shows the SL440 used in a basic lamp dimmer circuit with the minimum of external components. Resistor R1 provides the triac firing circuit with its load.

The potentiometer forms a potential divider across the 11.3 V supply and varies the light output by varying the voltage at pin 13. The input impedance at this point is very high and current flow can be measured in nA. The internal amplifier is not employed in this circuit.

The automatic lamp fader circuit of Fig. 6 is a variation on the same theme, the main difference being that the internal amplifier can be switched to perform an integration of the control voltage.

When S1 is open, the brilliance of the lamp is set by RV1. When S1 is closed, the positive potential derived from the divider R2, R3 is presented to the input causing the lamp to give full output.

If now S2 is closed and S1 is opened, the lamp will gradually reduce in brightness until it reaches the brightness level corresponding to the setting of RV1. The time taken for the fade to occur will depend on the value of the integration capacitor C1. With the value shown, this will be between 20 and 30 minutes.

A motor speed control circuit is shown in Fig. 7. This is basically similar to the previous circuits except that one leg of the potential divider is formed by a tachometer generator driven by the motor.

The device is available from SDS Components Ltd., Hilsa Trading Estate, Portsmouth, Hants, at £2.08p for one-off, £1.82 for 25 off.



D. TROTMAN (SDS COMPONENTS)

# Readout—

## A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

### THE TOPICAL SYNTHESISER

Sir—In answer to Mr. Baily's letter (last month)—he admits that the building of a stable, accurate log law circuit is difficult. I would tend to go further and say that for the average amateur constructor the task is almost impossible. This statement is in no way intended as a slight to the amateur but serves to highlight a situation which seems to be occurring all too often these days. Although there are many more avenues for the amateur to explore than there were a few years ago it is frequently found that exploitation of a particular circuit or function requires the possession of a bewildering array of test equipment and the technical expertise to interpret their respective readings.

This situation is very much in evidence in the case of designing and building a log law v.c.o. as Mr. Baily has testified. There is little point in publishing designs for such circuits since the problems arise, not so much in the building, but in the final setting-up and matching. Thus, from this point of view alone, there is considerable justification in the presentation of a linear v.c.o. which can be built with a minimum of test equipment and which behaves, with few limitations, in an exactly determinable manner. I would like to underline the fact that the P.E. Synthesiser is very much an experimental project which has been designed, as far as possible, to allow the widest possible licence to the individual constructor for the incorporation of modifications and/or additions to the system. In the case of the v.c.o. the overall response is determined by the response of the "front-end" as it is in most commercially available units. Thus by changing the response of the front end only the circuit can be made to obey a variety of laws to suit the whim of the constructor and this without disturbing the settings of the oscillator section at all.

With regard to Mr. Baily's specific criticisms of the linear v.c.o. the following observations apply:

1. No chording facility. This is a perfectly valid criticism and without doubt is the major disadvantage of the linear v.c.o. Octave chords can be played however and the keyboard incorporates a harmony switch for this purpose. If the Synthesiser is to be used for *musique concrete* purposes the lack of chording facility is no disadvantage since a full range of four note chords may be set up and recorded as discrete sounds.

2. No variable keyboard pitch. Not strictly true since the keyboard oscillators have their own manual frequency control with which it is possible to vary the "spread" by about an octave either way. Since the keyboard oscillators are tuned an octave apart this effectively gives a register of seven octaves although the upper and lower ends are not tightly in tune due to the "non-logarity" of the oscillators.

3. Difficulties in tuning . . . Again not entirely valid. The variation in programming voltage from end of the keyboard to the other is only about 65 millivolts (see Fig. 3.4.) consequently there are only two values of fixed resistor and one value of preset per key. The

values of fixed resistor are chosen such that the majority of presets are operating within the middle 60 per cent of their rotation. There is thus not such a vast range of adjustment as Mr. Baily anticipates. Furthermore, and to the advantage of this particular system, the resistive value set-up during tuning affects only one note whereas in the series chain system used with log v.c.o.s any one resistor going unstable will affect all the others downstream in the chain.

4. Poor frequency stability. Voltage and resistance wander can scarcely be cited as being problematical in this respect since they are relatively easy to correct. The use of a well regulated power supply together with adequate decoupling and the use of high stability resistors in the frequency determining networks will largely dispose of the problem. Mr. Baily correctly pinpoints the problem of thermal drift with the linear v.c.o. circuit as published.

On test at an ambient temperature of 18°C and with the oscillator running at 256Hz rapid cycling between about 0°C (induced with a freezer aerosol) and 25°C (close proximity 100 watt lamp) resulted in a variation in frequency of between 222Hz at 0°C and 312Hz at 25°C. This approximates to -10 per cent, +20 per cent on the basic frequency. On the other hand the oscillator in its case was monitored over a 48 hour period with a digital frequency meter and normal changes in day/night ambient temperatures resulted in frequency changes within  $\pm 2$  per cent. Extreme changes in ambient temperatures are unlikely under what might be termed normal operating conditions and such light changes as do occur can be adequately compensated for by adjustment of the manual frequency bias on the oscillators.

5. Uneven swing in pitch control. There is no real answer to this one since Mr. Baily is correctly citing the characteristic of the linear circuit, i.e. the requirement for a progressively increasing programming voltage in order to maintain the same rate of change of frequency as frequency increases. I feel bound to say, however, that I have never noticed this as a problem.

Two final points are worth mentioning. Mr. Baily cites the increase in power required from the use of integrated circuits as opposed to discrete components. This is undoubtedly true and while there is probably a hard core of amateur constructors who enjoy the challenge of design there is a far larger group who build for the sake of building and whose principal requirement from their hobby is results. To this latter group the integrated circuit, in its many forms, represents a release from many of the problems associated with design and allows them to enjoy their hobby more fully as a result. The increase in power required is thus surely a small price to pay?

Finally, on the subject of price, I would be very interested to have full details of the range of Dewtron modules offering the same specification as the P.E. Sound Synthesiser at under £200.

D. Shaw.

## VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT

VARIABLE 0-260V

All Types

from ½ to 50 amp from stock.

### SHROUDED TYPE

1 amp, £7.70  
2.5 amp, £8.86  
5 amp, £12.98  
10 amp, £24.75  
15 amp, £27.50

20 amp, £53.90  
25 amp, £63.80  
37.5 amp, £90.20  
50 amp, £107.80



(Panel Mounting) ½ amp, £5.28.  
1 amp, £7.70, 2½ amp, £8.80. All carriage paid.

## L.T. TRANSFORMERS

All primaries 220-240V

Type No.	Sec. Taps	Price
1	30, 32, 34, 36V at 5A	£5.50
3	30, 40, 50V at 5A	£7.92
2	10, 17, 18V at 10A	£5.83
4	6, 12V at 20A	£7.70
5	17, 18, 20V at 20A	£8.58
6	6, 12, 20V at 20A	£8.14
7	24A at 10A	£6.16
8	4, 6, 24, 32V at 12A	£8.47
9	6 and 12V at 10A	£4.51

### PARVALUX TYPE SD19 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS

30 r.p.m., 40 lb. in. Position of drive spindle adjustable to 3 different angles. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of makers' price. £7.48.



### PARVALUX TYPE SD2. 200/250 VOLT A.C./D.C. HIGH SPEED MOTOR

Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built-in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated below. PRICE £2.20.



### 600 WATT DIMMER SWITCH.

Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £3.30.

### 240V A.C. SOLENOID FLUID VALVE

Will handle liquids or gases up to 7 p.s.i. Forged brass body, stainless steel core and spring. ½ in. b.s.p. inlet/outlet. Precision made, British mfg. PRICE: £2.09. Special quotation for quantity. (New in makers' carton)



### INSULATION TESTERS

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in. W.4in. H.6in. weight 6lb. 1,000V, 1,000 megohms. £37.40. 500V, 500 megohms, £30.80.



### UNISELECTOR SWITCHES

NEW 4 Bank 25 Way, 24V d.c. operation. £7.04, 6 Bank 25 Way, 24V d.c. £8.14, 8 Bank 25 Way, 24V d.c. operation. £9.46.



### 24-HOUR TIMER

Can be adjusted to give a switching delay of between 2 hrs. to 24 hrs. Driven by 200/250V A.C. synchronous motor. 15 amp c/o contacts. Mfg. Crater Controls Ltd. Supplied with scale calibrated 0-10 (2 hrs. per division). Brand New. £2.20.



### HONEYWELL PROGRAMME TIMERS

240V. A.C. 5 r.p.m. motor. Each cam operating a c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. 15 cam model £6.60, 10 cam model £5.50.



SIMPLE 12 CAM PROGRAMMER 240V A.C. 15 RPM MOTOR with 4 adjustable cams and 8 that may be profiled to individual requirements, £4.18.

## 36V 30 AMP. A.C. or D.C.

VARIABLE L.T. SUPPLY UNIT

INPUT 220/240V a.c. OUTPUT CONTINUOUSLY VARIABLE 0-36V

Fully isolated. Fitted in robust metal case with Voltmeter. Ammeter Panel Indicator and handles. Input and output fully fused. Ideally suited for Lab. or Industrial use. £77.



### MOTOROLA MAC II/6 PLASTIC TRIAC 400 PV 10 AMP

Now available EX STOCK. Supplied with full data and applications sheet. Price £1.21. Suitable DIAC 22p each.

## STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

**EXPERIMENTERS' ECONOMY KIT** Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £7.26.

**NEW INDUSTRIAL KIT** Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s. Approx. ½ output of Hy-Light. Price £12.10.

**HY-LIGHT STROBE MK III** For use in lab. room, halls and utilises a silica tube, printed circuit. Speed adjustable 0.20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £13.75.

### THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.

● Variable speed from 1-3 flash per sec.  
● Reactor control circuit producing an intense white light. ONLY £22.88.


**ROBUST, FULLY VENTILATED METAL CASE** For Hy-Light Kit including reflector £4.95. Super Hy-Light Kit including reflector £8.25. 7-inch POLISHED REFLECTOR Ideally suited for above Strobe kits. Price 66p.

### RAINBOW STROBE FOUR LIGHT CONTROL MODULE

Will operate four of our Hy-Light or Super Hy-Light Strobes in either 2, 3, 4 sequence; 2 + 2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: £20.63. Send S.A.E. for details.
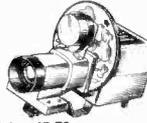
### COLOUR WHEEL PROJECTOR

Complete with oil-filled colour wheel, 100 watt lamp, 200/240V A.C. Features extremely efficient optical system. £20.74.



**6 INCH COLOUR WHEEL** As used for Disco lighting effects, etc. Price £5.72.

### BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £18.15. Spare bulb £8.03.



### BLACK LIGHT FLUORESCENT U.V. TUBES

4ft. 40 watt. Price £6.38. (For use in standard bi-pin fluorescent fittings). MINI 9 in. 6 watt black light U.V. tube. £1.60. Complete ballast unit and holders for 9 in. tube. £2.04.

### ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1½V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3.50.

### FOOT SWITCH

Suitable for Motors, Drills, Sewing Machines, etc., etc. 5 amp. 250 volt. Price £1.



**ALL PRICES INCLUDE V.A.T. POSTAGE AND PACKING** Overseas orders ask for quote

## Superior Quality Precision Made

## NEW POWER RHEOSTATS



New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 1/5/10/25/50/100/250/500/1k/1.5k ohm £1-10.  
50 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/5k ohm £1-54.  
100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k ohm £2-20.

Black Silver Skirted knob calibrated in Nos. 1-9, 1½ in. dia. brass bush. Ideal for above Rheostats, 22p each.

## RELAYS

SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1)	1	2	3	4
Coil ohms	52	4-6	6M	66p*
Col. (2)	52	4-6	4 c/o	88p*
Working d.c. volts	150	6-12	4 c/o	88p*
	185	8-12	6M	66p*
Col. 3	410	10-18	4 c/o	77p*
Contracts	600	9-18	2 c/o	66p*
	700	16-24	4M 2B	66p*
Col. (4)	700	16-24	4 c/o	88p*
Price	700	15-35	2 c/o HD	77p*
	700	16-24	6M	66p*
HD =	700	6-12	1 c/o HD	55p*
Heavy duty	700	20-30	4 c/o	88p*
	1,250	24-36	4 c/o	66p*
	2,500	36-45	6M	55p*
All prices	2,400	30-48	4 c/o	55p*
incl. P. & P.	9,000	40-70	2 c/o	55p*
	15k	85-110	6M	55p*

### 12 VOLT D.C. RELAY 140 ohm coil

Type 1: Three sets c/o contacts rated at 5 amps. 88p (Similar to illustration below.)  
Type 2: 4-8 volt, 3 c/o HD, 67 ohm coil. 88p.

**SPECIAL OFFER** 700 ohm 4 c/o. Ex. new equipment. £55 per 100 incl. bases (minimum 100).

### 230 VOLT A.C. 'DIAMOND H' RELAYS (Unused)

Three sets c/o contacts rated at 5 amps. PRICE: 66p. (100 lots) £44.  
24 volt A.C. 3 c/o 66p. Incl. P. & P.



### MINIATURE LATCHING RELAY

Manufactured by Clare-Elliott Ltd. Type F. 2 c/o permanent latching in either direction. Coil 150 ohm, 15-30 Volt D.C. Size ½" high, ½" wide, ½" thick. Complete with 3" leads. New 77p.



### BLOWER UNIT

200-240 Volt A.C. Precision German built. Dynamically balanced, quiet, continuously rated, reversible motor. Consumption 60mA. Size 120 mm. dia. x 60 mm. deep. Price £3.52.



### 230V FAN ASSEMBLY

Continuously rated, special sealed bearing, removable aluminium blades. Price £1-10.




### 4 BANK 3c/o PUSH BUTTON ASSEMBLY

Black rectangular buttons. 5 units (min. order) £1-10.


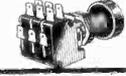
### 'HONEYWELL' PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises a c/o rated at 10 amps 240V A.C. Black knob lin. Fixing hole ½ in. ONE bank 33p; TWO bank 44p; THREE bank 61p. Quot. for quantity.



### 'HONEYWELL' LEVER OPERATED MICRO SWITCH

15 amps 250 volt A.C. c/o contacts. In maker's carton. PRICE: 10 for £2-09.



### Very special offer MICRO SWITCH

5 amp c/o contacts. Fitted with removable metal panel assembly. Ex. P.O. 20 for £1-10 (Min. order 20.)



### METER BARGAIN

BALANCE/LEVEL METERS 100-0-100 Micro Amp. Size 1½ in x 1½ in. Price only 83p.



**AMMETERS NEW!** 2½ in. Flush round. Available in D.C. Amps 1, 5, 15, 20 or A.C. Amps 5, 10, 15, 20, both types \*£1.98. 0-300V. A.C. £2-09.



All Mail Orders—Callers—Ample Parking  
Dept. PE6, 57 BRIDGMAN ROAD  
CHISWICK, LONDON W4 5BB  
Phone 01-995 1560  
Showroom open Mon.-Fri.

# SERVICE TRADING CO.

Personal callers only. Open Sat.  
9 LITTLE NEWPORT STREET  
LONDON WC2H 9JJ  
Phone 01-437 0576



## LOUDSPEAKER BARGAINS

Fane Pop 100W, 18", 8/15 ohm	£21-45
Fane Pop 60W, 15", 8/15 ohm	£12-26
Fane Pop 50W, 12", 8/15 ohm	£10-17
Fane Pop 25/25W, 8/15 ohm	£5-94
Fane Pop 15 12" 15W, 8/15 ohm	£4-40
Fane 122/10a or 122/12	£9-90
Fane Crescendo 15", 8 or 15 ohm	£27-50
Fane Crescendo 12", 8 or 15 ohm	£24-20
Fane 8" d/cone 808T, 8 or 15 ohm	£2-64
Fane 8" d/cone, roll surr. 807T, 8 or 15 ohm	£3-16
Baker Group 25, 3, 8 or 15 ohm	£6-00
Baker Group 35, 3, 8 or 15 ohm	£7-50
Baker De Luxe 12" d/cone	£9-62
Baker Major	£7-50
EMI 13" x 8", 3, 8 or 15 ohm	£2-25
EMI 13" x 8" type 150 d/cone, 3, 8 or 15 ohm	£2-58
EMI 13" x 8" type t/w, 3, 8 or 15 ohm	£3-85
EMI 13" x 8" type 350, 8 ohm	£8-25
EMI 6" x 9.50", 4 or 8 ohm	£2-80
Elac 9" x 5" 59RML09, 15 ohm	£2-53
Elac 9" x 5" 59RMLL4, 8 ohm	£2-53
Elac 6" d/cone 6RM220, 8 ohm	£2-59
Elac 6" d/cone, roll surr. 6RM171, 8 ohm	£3-22
Elac 4" tweeter TW4, 8 or 15 ohm	£1-21
Celestion P38 for 4 ohm	£2-16
Celestion MFL000 25W horn, 8 or 15 ohm	£10-45
Elac 5" 3 ohm	£1-75
Elac 7" x 5", 3, 8 or 15 ohm	£1-52
Elac 8" x 5", 3, 8 or 15 ohm	£1-93
Wharfedale Bronze 8 RS/DD	£3-11
Wharfedale Super 8 RS/DD	£5-50
Wharfedale Super 10 RS/DD	£9-80
Goodmans 8P, 8 or 15 ohm	£3-80
Goodmans 10P, 8 or 15 ohm	£4-49
Goodmans 12P, 8 or 15 ohm	£11-35
Goodmans 15P, 8 or 15 ohm	£17-05
Goodmans 18P, 8 or 15 ohm	£29-70
Goodmans Twinaxiom 8	£6-79
Goodmans Twinaxiom 10	£7-61
Goodmans Axent 100	£6-60
Eagle DT33 dome tweeter, 8 ohm	£4-95
Eagle HT15 tweeter, 8 ohm	£3-46
Eagle CT5 tweeter, 8 ohm	£1-21
Eagle MT10 tweeter	£3-30
Eagle CT10 tweeter	£1-92
Eagle Xovers CN23, 28, 216	£1-10
Kef T27	£4-67
Kef T15	£5-50
Kef B110	£6-16
Kef B200	£7-42
Kef BL39	£10-72
Kefkit 2	£24-75
Richard Allan 12" d/cone, 3 or 15 ohm	£2-20
Richard Allan 8", 3, 8 or 15 ohm	£2-27
8" x 5", 3 or 8 ohm	£1-92
7" x 4", 3 or 8 ohm	£1-38
3", 8 ohm or 80 ohm	65p
2 1/2", 64 ohm	65p
Speaker matching transformer, 3/8/15 ohm	£1-10
Adastra Hiten 10", 10W, 8 or 15 ohm	£2-80
Adastra Top 20 12", 25W, 8 or 15 ohm	£6-32
Stephen speaker kits and cabinets—send for illustrated brochure and list of recommended speakers.	
Car stereo speakers—ask for leaflet.	
PA/Disco amplifiers (carr. and ins. £1):	
Baker 100W	£46-00
Linear 30/40	£25-00
Linear 40/60	£30-00
Linear 80/100	£50-00
FREE with speaker orders over £7—"Hi-Fi Loudspeaker Enclosures" book.	
All units guaranteed new and perfect.	
Prompt despatch.	
Carriage and insurance 25p per speaker.	
(Tweeters and Crossovers 15p each.)	
All prices quoted inclusive of V.A.T.	

**WILMSLOW**  
AUDIO, Dept. PE  
SWAN WORKS, BANK  
SQUARE, WILMSLOW  
CHESHIRE SK9 1HF

## DECADE TTL COUNTER UNIT

COMPLETE OR IN KIT FORM

### COMPLETE UNIT

Decade TTL Unit on fibreglass PCB using 74 series TTL to count up to 18MHz with Nixie tube display. These units may be coupled to provide a multi-digit readout for Frequency Counters, Timers, DVM's, Batch Counters etc. (Application details not available) Requires 200/250V D.C. & 5V D.C. reg.

KIT PRICE: £5.06 plus 10p p&p  
ASSEMBLED AND TESTED  
£5.40 plus 10p p&p

TRANSFORMER, 200/250V to 6V, 1A & 250V for decade power supply, with circuit using 5V Regulator 1/C: £2.20 plus 20p p&p

### COMPONENTS

400V, 8A Triac isolated tab type 1L48, 125A surge 85p  
32V Diac Type D30 suitable for triggering 1L48 23p  
5V Voltage Regulator 1/C. T03 case 600 mA output from 7.5V—15V D.C. input, with instructions £1.98  
Heat Sink, T03, twisted vane, 8" C/W for 5V Regulator 20p  
BC 107, BC 108 6p  
(All plus 6p p&p)

Prices include VAT Please send c.w.o to:

**DEXTER & COMPANY**  
1 ULVERHOUSE 19 KING STREET  
CHESTER CH1 2AH  
Tel: 0244-25883

## P.C.B.: For Mullard Transistor Audio and Radio Circuits Handbook

The following boards are now available: 1st Edition: paper base laminate. 10W H.Q. audio amp, p. 102, 66p. 25W H.Q. audio amp, p. 106, 70p. 10/25W H.Q. audio pre-amp, p. 108, 73p.

2nd Edition: fibreglass laminate. 10W Audio Amp, p. 122, 69p. 15/20W Audio Amp, p. 126, 73p. 25W Audio Amp, p. 128, 73p (incorporates protection circuit, p. 130).


Universal pre-amp, mono, p. 148, 78p. Universal pre-amp, stereo, p. 148, £1-48.

No other circuits are available.

Price includes P. & P. but add VAT. Remittance (not cash or stamps) with order. Allow 14 days for cheque clearance otherwise prompt despatch subject to stocks.

All boards are roller tinned, drilled and have component ident. printed on reverse.

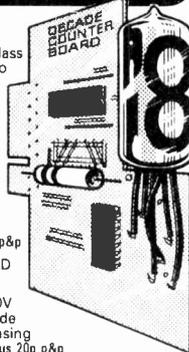**BRIBOND PRINTED CIRCUITS LIMITED**  
Regd. in England 593908  
Terminus Road, Chichester  
Sussex



**PARTRIDGE MAINS ISOLATION TRANSFORMER.** Pri: 105-250V, 3V steps, Sec: 240V, 13 amps. £15, carr. pack. £1.

**PARMEKO MAINS TRANSFORMER** isolated windings. Pri: 200-250V. Sec: 90-120V at 4.5 amp., £4, carr. pack. 50p.

**GARDNER'S POTTED TRANSFORMER, 0-250V.** Pri: 200-250V. Sec. Input: 18V 500mA, 50V 150mA, 6V 250mA output. Size: 3in x 2 1/2in x 2 1/2in, £1, p.p. 20p. Ex equip. tested.

**RIPLEY MAINS TRANSFORMER.** Pri: 110V-240V, Sec: 12.5V: 0.12-5V 750mA 7V:0.7 V1A, £1, p.p. 25p.

**MAINS TRANSFORMER.** Pri: 100-250V, Sec: 22:0-22 200mA, 22:0-22 100mA 0.24V 20mA, £8p, p.p. 25p.

**TRANSISTOR OUTPUT TRANSFORMER, Ratio 8:1, 120mH.** Centre tap 2 watts. output. 20p, p.p. 5p.

**SMOOTHING CHOKE, 11MH, 1 1/2in x 1 1/2in x 1 1/2in, 20p, p.p. 7p.**

**BELLING LEE INSULATED TERMINALS.** Red or Black, 3 amp max. 10p pair, p.p. 4p.

**FINNED ALUMINIUM HEATSINK.** 9in x 1 1/2in. Ready drilled. 20p, p.p. 7p.

**FINNED ALUMINIUM HEATSINK.** 9in x 8in x 1 1/2in. in C.: 4 x 2N3055, £2, p.p. 29p.

**SUB-MIN. CROC. CLIPS.** Red or Black, insulated 4p. Min. quantity, 6, p.p. 4p.

**GARRARD MAG. TAPE DECKS:** 1 1/2 p.p.s., 50V, solenoid operated brakes, etc. Mains voltage motors £7-50 each, p.p. 60p.

**NOTEK 3 speed tape deck (1 1/2in x 3 1/2in x 7 1/2in)** reel to reel 7in mains operated, £7-50, p.p. 60p.

**10 REED SWITCHES** operated by push buttons and magnets, 50p, p.p. 20p.

**COMPONENT PANEL 6 s/crs (200V 4 amps), 6 condensers, 12 resistors, 30p, p.p. 8p.**

**COMPONENT PANEL (9 ICs FJH131) (1-CA300), 1 crystal 7-6kHz ± various other components, £1, p.p. 8p.**

**COMPONENT PANEL, 4 x 500 mfd, 50V d.c. cap. 1 x 2N1218, 1 x 2N1408, 2 x 2N598, plus various other components, 10p, p.p. 9p.**

**NEON PANEL, 24 neon's, wire ended, 90-240V, 20p p.p. 4p.**

**MAINS NEONS** Red or Green. Size: 1/2in x 1/2in x 1 1/2in. 15p, p.p. 4p.

**LEVER ACTION P.O. 1000 TYPE SWITCHES** Lock 4-pole changeover, 15p, p.p. 4p. Ex equip. Lock 2-pole changeover, 10p, p.p. 4p. Ex equip.

**MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,500pF 64V, 7,100pF 40V, 50p each. 50,000 30V, 25,000 25V, 35,000 15V, 80p each, p.p. 10p.**

**MULLARD FULLWAVE RECTIFIERS** 6-38V, 15 amp, 75p, p.p. 9p.

**BELLING LEE 1.5 amp in-line rubber covered interference suppressor, 25p, p.p. 8p.**

**RUBBER 3 PIN 6 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.**

**SOLENOIDS 12V 12V PULL ACTION** 2in x 1in x 1 1/2in, 40p, p.p. 8p.

**SOLENOIDS 12-24V d.c. pull action 1 1/2in x 1 1/2in x 1 1/2in, 40p, p.p. 5p.**

**SOLENOIDS 240V a.c. pull action 2 1/2in x 1 1/2in x 1 1/2in, 50p, p.p. 9p.**

**BANGAMO WESTON TIME LAPPED METAL** Mains operated. 1 1/2in x 1 1/2in x 2in, £1-50 p.p. 7p.

**ARROW RELAY, 240V a.c. coil, double pole change over, 1 make contact's 10A, 240V a.c., 25p, p.p. 8p.**

**OMRON MKE MIDGET POWER RELAY, 12V d.c.** Double pole changeover. New, 70p, p.p. 5p.

**STC MINIATURE RELAY 280Ω, perspex cover, double pole changeover, 6-15V new, 30p, p.p. 5p.**

**STC VARLEY, miniature relays 700Ω, perspex cover, 4 pole changeover, 40p, p.p. 5p.**

**POTTER BRUMFIELD 12V d.c. 3 pole changeover** with base, contacts rated 7A d.c., £1, p.p. 10p.

**TELESCOPIC AERIALS** Chromed 7in closed, 28in extended, 6 section ball jointed base, 28p, p.p. 5p new.

**MULLARD 4 DM 160 INDICATORS** in plastic holder/cover, ex equip., size approx. 1 1/2in x 1 1/2in x 1in, 86p, p.p. 5p.

**PRINTED CIRCUIT BOARD/19 ACV 19's 10 0A200** Diodes: 1 zener relay: 1 AZ 220 zener ass. capacitor/resistors. Power supply 22V, 250 mA d.c. Output 240V a.c., £1, p.p. 20p. Ex equip.

**WIRING CABLE** Size-1-020. Various colours. 350yds, 60p, p.p. 23p.

**TAPE POSITION INDICATOR** Re-settable 3 digits, 30p, p.p. 5p.

All orders add 10% V.A.T.

**FIELD ELECTRIC LIMITED**  
3 Shenley Road  
Borehamwood, Herts.  
Tel.: 01-953 6009

# BRAND NEW SEMICONDUCTORS AND COMPONENTS GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS		40316		0-50		BC125		0-15		BDY20		1-05		BSY26		0-20	
2G301	0-15	2N3414	0-10	40360	0-40	BC126	0-20	BDY38	0-05	BSY27	0-15	SN7400	0-20	SN7401	0-20	SN7402	0-20
2G302	0-15	2N3415	0-10	40361	0-40	BC132	0-20	BDY60	0-00	BSY28	0-15	SN7403	0-20	SN7404	0-22	SN7420	0-20
2G303	0-15	2N3416	0-10	40362	0-40	BC134	0-11	BDY61	1-25	BSY39	0-20	SN7447	1-30	SN7472	0-35	SN7495	0-75
2G306	0-30	2N3417	0-21	40363	0-61	BC136	0-11	BDY92	1-00	BSY39	0-20						
2G309	0-30	2N3418	0-21	40364	0-61	BC137	0-11	BDY92	1-00	BSY39	0-20						
2G346B	0-25	2N3571	1-12	40394	0-65	BC138	0-24	BF119	0-08	BSY53	0-25						
2G371	0-15	2N3572	0-97	40395	0-65	BC140	0-34	BF121	0-25	BSY54	0-30						
2G374	0-15	2N3702	0-11	40406	0-44	BC141	0-39	BF123	0-27	BSY66	0-79						
2N174	1-40	2N3703	0-10	40407	0-38	BC142	0-24	BF125	0-25	BSY65	0-15						
2N404	0-48	2N3704	0-14	40408	0-40	BC143	0-21	BF125	0-20	BSY78	0-40						
2N456	0-75	2N3705	0-10	40409	0-52	BC144	0-24	BF127	0-21	BSY79	0-40						
2N457A	0-80	2N3706	0-09	40410	0-53	BC145	0-21	BF154	0-16	BSY95A	0-09						
2N491	8-25	2N3708	0-07	40414	3-55	BC148	0-10	BF159	0-27	C111	0-53						
2N696	0-15	2N3709	0-09	40467A	0-09	BC149	0-18	BF160	0-23	GET111	0-45						
2N697	0-15	2N3710	0-12	40468A	0-44	BC152	0-18	BF161	0-42	GET114	0-20						
2N698	0-25	2N3711	0-09	40600	0-09	BC156	0-18	BF163	0-20	GET115	0-50						
2N699	0-25	2N3712	0-05	40601	0-07	BC157	0-14	BF166	0-35	GET119	0-35						
2N706A	0-12	2N3713	1-08	40602	0-46	BC158	0-13	BF167	0-21	GET330	0-30						
2N708	0-13	2N3714	1-15	40603	0-53	BC159	0-14	BF173	0-24	GET380	0-20						
2N709	0-38	2N3715	1-23	40604	0-58	BC160	0-37	BF177	0-29	GET880	0-30						
2N711	0-30	2N3716	1-30	40636	1-10	BC167B	0-11	BF178	0-35	GET883	0-20						
2N718	0-21	2N3773	3-05	40673	0-70	BC168B	0-13	BF179	0-43	GET887	0-20						
2N718A	0-25	2N3779	3-10	AC107	0-35	BC169C	0-11	BF180	0-35	TIP29A	0-48						
2N720	0-50	2N3780	2-20	AC113	0-16	BC169B	0-13	BF181	0-32	TIP30A	0-69						
2N721	0-45	2N3780	2-20	AC115	0-16	BC169C	0-13	BF182	0-40	TIP31A	0-72						
2N714	0-22	2N3784	2-06	AC117	0-20	BC170	0-11	BF184	0-17	TIP32A	0-74						
2N916	0-17	2N3789	2-06	AC121	0-13	BC171	0-18	BF185	0-17	TIP33A	1-01						
2N918	0-30	2N3794	1-10	AC127	0-25	BC172	0-10	BF194	0-14	TIP34A	1-51						
2N929	0-14	2N3819	0-37	AC128	0-25	BC182L	0-12	BF195	0-17	TIP36A	3-70						
2N930	0-14	2N3820	0-47	AC141K	0-30	BC183	0-09	BF196	0-15	TIP41A	0-79						
2N1090	0-29	2N3823	0-97	AC142K	0-25	BC183L	0-09	BF197	0-15	TIP42A	0-90						
2N1091	0-24	2N3824	0-75	AC151V	0-14	BC184	0-11	BF198	0-15	TIP2955	0-08						
2N1132	0-20	2N3826	0-23	AC152V	0-17	BC184L	0-11	BF199	0-15	TIP3055	0-08						
2N1392	0-16	2N3854	0-16	AC153K	0-25	BC187	0-05	BF200	0-40	ME0401	0-18						
2N1303	0-18	2N3854A	0-16	AC154	0-20	BC207	0-12	BF225J	0-17	ME0402	0-20						
2N1304	0-20	2N3855	0-16	AC176	0-18	BC208	0-11	BF237	0-22	ME0411	0-17						
2N1305	0-20	2N3855A	0-16	AC187K	0-20	BC212K	0-10	BF238	0-22	ME0412	0-18						
2N1306	0-20	2N3856	0-16	AC188K	0-26	BC212L	0-16	BF244	0-16	ME0413	0-14						
2N1307	0-22	2N3856A	0-16	AC188K	0-26	BC212L	0-16	BF245	0-33	ME1120	0-25						
2N1308	0-25	2N3858	0-16	AC188K	0-26	BC212L	0-16	BF246	0-33	ME1120	0-25						
2N1309	0-25	2N3858A	0-16	AC188K	0-26	BC212L	0-16	BF247	0-49	ME4001	0-09						
2N1483	0-90	2N3859	0-18	AC188K	0-26	BC212L	0-16	BF248	0-49	ME4002	0-09						
2N1507	0-84	2N3859A	0-18	AC188K	0-26	BC212L	0-16	BF249	0-49	ME4003	0-09						
2N1613	0-20	2N3860	0-16	AC188K	0-26	BC212L	0-16	BF250	0-49	ME4004	0-11						
2N1621	0-20	2N3860A	0-16	AC188K	0-26	BC212L	0-16	BF251	0-17	ME4101	0-10						
2N1637	0-36	2N3877	0-25	AC188K	0-26	BC212L	0-16	BF252	0-17	ME4102	0-11						
2N1638	0-32	2N3877A	0-25	AC188K	0-26	BC212L	0-16	BF253	0-38	ME4103	0-10						
2N1701	1-10	2N3900	0-20	AC188K	0-26	BC212L	0-16	BF254	0-45	ME4104	0-11						
2N1702	2-15	2N3900A	0-21	AC188K	0-26	BC212L	0-16	BF255	0-45	ME4104	0-11						
2N1711	0-22	2N3901	0-22	AC188K	0-26	BC212L	0-16	BF256	0-45	ME4104	0-11						
2N1893	0-34	2N3903	0-22	AC188K	0-26	BC212L	0-16	BF257	0-45	ME4104	0-11						
2N2102	0-20	2N3904	0-17	AD136V	0-96	BC300	0-48	BF258	0-45	ME4104	0-11						
2N2147	0-70	2N3905	0-22	AD140	0-55	BC301	0-84	BF259	0-45	ME4104	0-11						
2N2148	0-94	2N3906	0-62	AD142	0-50	BC302	0-87	BF260	0-45	ME4104	0-11						
2N2192	0-40	2N4036	0-62	AD148V	0-48	BC303	0-54	BF261	0-27	ME4104	0-11						
2N2192A	0-40	2N4037	0-42	AD148V	0-48	BC303	0-54	BF262	0-10	ME4104	0-11						
2N2193	0-40	2N4058	0-16	AD150	0-46	BC307	0-10	BF274	0-23	ME8003	0-16						
2N2193A	0-61	2N4059	0-09	AD161	0-49	BC307A	0-10	BF275	0-23	MJ400	0-78						
2N2194	0-20	2N4060	0-11	AD162	0-51	BC308	0-09	BF276	0-23	MJ420	0-86						
2N2194A	0-30	2N4061	0-11	AD161	0-49	BC308A	0-09	BF277	0-23	MJ421	0-88						
2N2195	0-37	2N4062	0-11	AD162	0-51	BC308A	0-09	BF278	0-23	MJ430	0-75						
2N2195A	0-18	2N4302	0-25	AD162	0-51	BC308B	0-09	BF279	0-23	MJ440	0-71						
2N2218A	0-30	2N4303	0-47	AF111	0-25	BC309	0-10	BF280	0-23	MJ440	0-71						
2N2219	0-37	2N4916	0-20	AF115	0-24	BC309B	0-10	BF281	0-23	MJ480	0-75						
2N2219A	0-61	2N4917	0-17	AF116	0-25	BC327	0-22	BF282	0-24	MJ481	0-85						
2N2220	0-38	2N4920	0-71	AF121	0-22	BC328	0-19	BF283	0-24	MJ491	1-94						
2N2221	0-20	2N4918	0-50	AF122	0-22	BC328	0-19	BF284	0-24	MJ802	4-12						
2N2221A	0-38	2N4919	0-63	AF124	0-24	BC330	0-43	BF285	0-24	MJ901	2-15						
2N2222	0-21	2N4921	0-50	AF125	0-25	BC331	0-43	BF286	0-24	MJ1001	2-34						
2N2222A	0-21	2N4922	0-55	AF126	0-25	BC332	0-43	BF287	0-24	MJ1002	2-34						
2N2368	0-11	2N4923	0-60	AF127	0-26	BC333	0-43	BF288	0-24	MJ2500	2-92						
2N2369	0-15	2N5172	0-12	AF127	0-26	BC333	0-43	BF289	0-24	MJ2501	3-25						
2N2369A	0-17	2N5174	0-22	AF128	0-26	BC334	0-43	BF290	0-24	MJ2555	1-00						
2N2369B	0-17	2N5175	0-22	AF129	0-26	BC335	0-43	BF291	0-24	MJ3000	2-79						
2N2847	1-20	2N5176	0-28	AF170	0-25	BC338	0-58	BF292	0-20	MJ3001	2-79						
2N2711	0-12	2N5176	0-28	AF172	0-25	BC339	0-58	BF293	0-20	MJ3002	2-79						
2N2712	0-12	2N5245	0-43	AF173	0-25	BC340	0-58	BF294	0-20	MJ3003	2-79						
2N2713	0-17	2N5180	0-92	AF174	0-25	BC341	0-58	BF295	0-20	MJ3004	2-79						
2N2714	0-17	2N5181	0-92	AF175	0-25	BC342	0-58	BF296	0-20	MJ3005	2-79						
2N2714A	0-17	2N5182	1-24	AF176	0-25	BC343	0-58	BF297	0-20	MJ3006	2-79						
2N2904A	0-25	2N5193	0-11	AF200	0-35	BC349	0-21	BFY31	0-43	MJ3007	2-79						
2N2905	0-33	2N5194	0-10	AF239	0-41	BCY70	0-17	BFY32	0-43	MJ3008	2-79						
2N2905A	0-35	2N5195	1-46	AF240	0-72	BCY71	0-22	BFY33	0-43	MJ3009	2-79						
2N2906	0-24	2N5245	0-43	AF279	0-64	BCY72	0-13	BFY34	0-43	MJ3010	2-79						
2N2906A	0-30	2N5457	0-35	AF280	0-54	BCY73	0-13	BFY35	0-43	MJ3011	2-79						
2N2907	0-32	2N5458	0-33	AF281	0-54	BCY74	0-13	BFY36	0-43	MJ3012	2-79						
2N2907A	0-33	2N5459	0-33	AF211	0-55	BCY89	0-07	BFY37	0-43	MJ3013	2-79						
2N2923	0-12	3N128	0-78	AL102	0-75	HCZ10	0-35	BFY38	0-43	MJ3014	2-79						
2N2924	0-12	3N138	1-65	AL103	0-70	HCZ11	0-50	BFY39	0-43	MJ3015	2-79						
2N2925	0-15	3N139	1-42	ALY26	0-30	BD115	0-75	BFY40	0-43	MJ3016	2-79						
2N2926	0-15	3N140	0-92	ALY27	0-38	BD116	0-75	BFY41	0-43	MJ3017	2-79						
Green	0-12	3N141	0-81	ALY28	0-38	BD121	0-75	BFY42	0-43	MJ3018	2-79						
Yellow	0-10	3N142	0-98	ALY29	0-38	BD122	0-75	BFY43	0-43	MJ3019	2-79						
Orange	0-10	3N143</															

# MAPLIN ELECTRONIC SUPPLIES

★RETURN OF  
POST  
SERVICE



1973 CATALOGUE

**3rd EDITION NOW AVAILABLE**

SEND NOW FOR YOUR COPY OF THIS BEAUTIFULLY PRODUCED FULLY ILLUSTRATED CATALOGUE AND WE WILL FORWARD IT TO YOU BY RETURN OF POST. PLEASE SEND 9p IN STAMPS.

EVERYTHING GUARANTEED BRAND NEW MARKED BY THE MANUFACTURER

MAPLIN: Projected site of London's third airport.

<p><b>RESISTORS</b> Carbon film 5% from 1Ω to 1MΩ, 10% from 1.2MΩ to 10MΩ. E12 series, 1/4W 1p; 1/2W 1.2p. Metal Oxide 2% 10Ω to 1MΩ. E24 series 1/4W 4p. Also 1W, 2 1/2W, 5W, 10W types stocked.</p>	<p><b>POTENTIOMETERS</b> Miniature carbon track with 2in. spindles. 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ. Log or lin (and 1kΩ lin), 12p. Log or lin with switch 23p. Dual gang less switch 38p.</p>	<p><b>P.E. SOUND SYNTHESISER</b></p> <p>If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!</p> <p>We shall be stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboards.</p> <p>Send S.A.E. NOW for our detailed price lists.</p> <p><b>YOU SIMPLY MUST SEE OUR PRICES!</b></p>	<p>8 pin DIL OP AMP 741C 36p. 14 pin 741C 45p.</p> <p>McMURDO Socket, RS8, 52p Plug, RP8, 36p. (As used in P.E. Sound Synthesiser.)</p> <p>Diodes IN914 4p. OA91 6p. BAX 13 5p. IN4001 6p. IN4002 6p. IN4003 7p. IN4004 7p. IN4006 8p. IN4007 9p.</p>	<p><b>SEMI-CONDUCTORS</b></p> <p>We stock a large range of transistors and I.C.s, for details please see our catalogue. LOOK! These popular devices at amazingly low prices. BC107/8/9 10p each. BC169C 12p. BFY51 16p. TIS43 (SS43) 28p. 2N706 10p. 2N2646 45p. 2N3055 49p. 2N 3819 24p.</p>
<p>7 TYPES DISPLAY Minitron 3015F £1.98 each.</p> <p>DIN PLUGS, 3 pin, 9p. 5 pin A (180°), 5 pin B (240°), 10p each.</p> <p>DIN SOCKETS. 3 pin, 5 pin A, 5 pin B, 7p each.</p> <p>DIN LOUDSPEAKER. 2 pin plug, 8p. Socket 6p.</p> <p>JACK PLUGS standard 1/4in plastic barrel, 13p. Stereo, 25p. Bright metal barrel, 17p. Stereo, 29p.</p> <p>JACK SOCKETS standard 1/4in open type, 10p. Moulded 2 break, 13p. Moulded stereo 3 break, 18p.</p>	<p><b>SPECIAL IC</b>, for organ builders. 7 stage frequency divider in one 14 pin DIL package, £2.63 or special price for pack of 12, £25.</p> <p>Why not ask us to slip a data sheet in with your catalogue.</p>	<p><b>NUDES!</b></p> <p>Clothe those naked projects with our superb instrument cases. We are sole distributors of the</p> <p><b>Centurion</b></p> <p>range, designed for the professional market, now available to you at special low prices. S.A.E. please for free illustrated leaflet.</p>	<p><b>HARDWARE</b></p> <p>Wide range of nuts and bolts, plated brass and nylon types plus solder tags, shakeproof washers, etc.</p> <p>SOLDER 10 metres of 22 gauge multicore, 20p.</p> <p>Insulating sleeving 3 sizes, 6 colours.</p>	<p><b>MISCELLANEOUS</b></p> <p>LT700 Eagle sub-miniature O/P transformer 1200/5Ω 200mW max., 35p.</p> <p>Slide switch DPDT, 12p.</p> <p>Miniature push to make non-locking switch 12p.</p> <p>Silicon grease in special dispenser, 20ml, 38p.</p>
<p><b>ROTARY SWITCHES</b></p> <p>Adjustable stop, 1 pole 2-12 way, 2 pole 2-6 way, 3 pole 2-4 way, 4 pole 2-3 way. Only 24p each.</p>	<p>SEE OUR CATALOGUE for details of how you can obtain £1 worth of components.</p> <p><b>ABSOLUTELY FREE</b></p>	<p>V.A.T. Please add 10% V.A.T. to final total. Orders and enquiries for catalogues to <b>MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex SS6 8LR</b></p>	<p><b>Postage and packing FREE in U.K. But we have to ask you to send a 10p handling charge with order under 50p.</b></p>	



## become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

**free!** Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**  
P.O. BOX 156, JERSEY

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

EB83

BLOCK CAPS please

## ELECTROKIT

**12 Lauderdale Road, London, W.9**  
**Telephone 01-286 0011**

**LIGHT DIMMER.** Kit contains all parts including circuit and construction data, 480 watts, fully suppressed. Price **£2-10**

**SCORPIO IGNITION SYSTEMS** (P.E. Nov. 1971), **£9-50**. This kit includes all the parts for the assembly of this popular and reliable system. The hardware and the construction data are included.

Send for details of kits available (please enclose S.A.E.).

All kits sent POST FREE within the limits of the U.K.

Please note, prices shown do not allow for V.A.T. Please add 10% to your order.

## STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP (as in 'W.W.' July '72)  
**MOTOROLA MC1310P**

**EX STOCK DELIVERY**

Specn. Separation: 40dB 50Hz—15kHz. Distortion: 0.3%. 1/P level: 560mV rms. O/P level: 485mV rms per channel. Input impedance: 50k. Power requirements: 8-12V @ 16mA. Will drive up to 75mA stereo 'on' lamp or LED. Simple to build.

**KIT COMPRISES FIBREGLASS PCB** (Printed and tinned), Resistors, I.C., Capacitors, Preset Potm. and Instructions. Only **£3-40** post free + V.A.T.

**LIGHT EMITTING DIODE (Red)**

Suitable as stereo 'on' indicator. For above with panel mounting clip and instructions. Only **29p + p.p. + V.A.T.**


**MC1310P only £2-77 + p.p. 6p + V.A.T.**

**14 PIN DIL SOCKETS. 16p each + V.A.T.**

**NOTE.**—As the supplier of the original decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.

**Fi-Comp Electronics**  
**BURTON ROAD, EGGINTON, DERBY DE6 6GY**
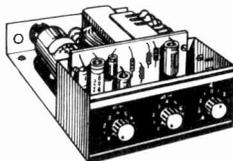
## PRICES NOW INCLUDE VAT SUPERSOUND 13 HI-FI MONO AMPLIFIER




A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz-30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, eucutcheon panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. A.C. 200/250V.

**PRICE £11.60**

P. & P. 25p.

## DE LUXE STEREO AMPLIFIER

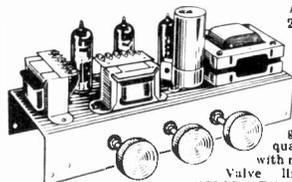

A.C. mains 200-240 volts. Using heavy duty transformer with isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: 2  $\times$  ECL86 Triode Pentodes. Valve line up: 2  $\times$  ECL86 Triode Pentodes. 1  $\times$  EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w  $\times$  4in. x. Overall height including valves 5in. Ready built and tested to a high standard. Price £9.90. P. & P. 45p.

## NEW! POWER SUPPLY UNIT

200/240V A.C. Input, Four switched fully smoothed D.C. outputs giving 6V, 7.5V and 9V and 12V at 1 amp continuous (11 amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6"  $\times$  3"  $\times$  2". Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc. Ready built and tested.

**PRICE £5**

P. & P. 35p.

**BLACK ANODISED 16g. ALUMINIUM HEAT SINKS.** For T03 complete with nuts and bushes. Size 2 1/2in  $\times$  3in approx. 25p pair. P. & P. 5p.

**HIGH GRADE COPPER LAMINATE BOARDS.** 8"  $\times$  6", 5 for 55p. P. & P. 15p.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-50V half wave at 1 amp or 10-10-10, 20-10-20, 30-0-30V, at 2 amps full wave. Size 3inL  $\times$  3inW  $\times$  3inD. Price £2.10. P. & P. 30p.

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240V Sec. 0-9-9a 500mA. £1 P. & P. 13p. Pri. 200/240V Sec. 12-0-12 at 1 amp. £1.10 P. & P. 13p. Pri. 200/240V Sec. 10-0-10 at 2 amp. £1.65 P. & P. 30p.

**GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER.** For P.U., Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2  $\times$  1 1/2  $\times$  1/2 in. Brand new - complete with instructions. Price £2. P. & P. 13p.

**3 REFERENCE ENCYCLOPEDIAS FOR ELECTRONIC ENGINEERS AND DESIGNERS,** covering between them, transistor characteristics, diode and transistor equivalents. Many thousands of up-to-date European types listed.

Diode Equivalents 90p  
Transistor Equivalents 90p  
Transistor Characteristics £1.20  
All three together £2.60

POST FREE

## HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

**CENTRE ZERO MINIATURE MOVING COIL METER.** 100uA for balance or tuning. Approx. size 1in  $\times$  1in  $\times$  1in. Limited number 85p. P. & P. 10p.

Open 9-5.30 Mon. to Fri. 9-5 Sat. Early closing Wed. 1p.m.

A few minutes from South Wimbledon Tube Station.

**RECORD PLAYER BARGAINS**  
Mains models. All brand new in maker's packing. LATEST B.S.R. C109/C189 AUTOCHARGER UNITS. With latest stereo/mono compatible cartridge £7.80 plus 50p P. & P. Garrard EP25 Mk. III with heavy precision machined die cast turntable. £10.66. Carr. 50p

**PRECISION ENGINEERED PLINTHS**  
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025CT, 2500, 3000, 3500, 5100, SP25 II and III, BL66B, AT60, etc., or B.S.R. C109, C129, A21, etc. Black leatherette finish. Size 12 1/2in  $\times$  14 1/2in  $\times$  3 1/2in high (approx. 7 1/2in high, including rigid smoked acrylic cover). P. & P. 35p. Now only £4.95

**LATEST ACOS GP91/18C Mono Compatible Cartridge** with 1/2 stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 8p.  
**SONOTONE STARC COMPATIBLE STEREO CARTRIDGE** T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2.80. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.80. P. & P. 10p.  
**LATEST RONETTE T/O Stereo Compatible Cartridge** for EP/LP/Stereo/78. £1.60. P. & P. 10p.  
**LATEST RONETTE T/O Mono Compatible Cartridge** for EP/LP/78 mono/stereo records on mono equipment £1.50. P. & P. 10p.

**QUALITY RECORD PLAYER AMPLIFIER MK II**  
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w  $\times$  3d.  $\times$  6h. Ready built and tested. PRICE £4.40. P. & P. 40p. AVAILABLE MOUNTED ON BOARD WITH OUTPUT TRANSFORMER AND SPEAKER. PRICE £5.85. P. & P. 50p.

## SPECIAL OFFER!! HI-FI LOUSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16in high  $\times$  10 1/2in wide  $\times$  6in deep. Fitted with E.M.I. Ceramic Magnet 13in  $\times$  8in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

**Our Price £9.25**

Carr. 70p.

CABINET AVAILABLE SEPARATELY £4.95 Carr. 65p.

Also available in 8 ohm with EMI 13in  $\times$  8in, bass speaker with parasitic tweeter. £7.15. Carr. 70p.

**HARVERSON'S SUPER MONO AMPLIFIER**  
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide  $\times$  3in. deep  $\times$  6in. high overall. A.C. mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer.

**OUR ROCK BOTTOM BARGAIN PRICE £3.30**

P. & P. 35p.

## LOUDSPEAKER BARGAINS

5in 3 ohm £1.05. P. & P. 15p. 7  $\times$  4in 3 ohm £1.15. P. & P. 20p. 10  $\times$  6in 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8  $\times$  6in 3 ohm with high flux magnet £1.62. P. & P. 20p. E.M.I. 13  $\times$  8in with high flux ceramic magnet with parasitic tweeter, 3, 8, or 15 ohm £2.50. P. & P. 30p. E.M.I. 13  $\times$  8in, 3 or 8 or 15 ohm with two built in tweeters and crossover network £4.65. P. & P. 30p.

**EMI CERAMIC MAGNET HEAVY DUTY TWEETER.** approx. 3in. Av. 3 or 8 or 15 ohms. £1.25 plus 15p p. & p.

**BRAND NEW.** 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflex ceramic ferrobar magnet assembly £7.50. Guitar models: 25w £7.50. 35w £9.35. P. & P. 40p each.

**SPECIAL OFFER!**  
LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS. With large ceramic magnet and plasticized cone surround. 6ohm impedance. £2.70. P. & P. 25p.

**12in "RA" TWIN CONE LOUSPEAKER**  
10 watts peak handling, 3, 8 or 15 ohm, £2.45. P. & P. 30p. 35 ohm SPEAKERS 3". ONLY 70p. P. & P. 13p.

**"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER**  
Size 11in  $\times$  14in  $\times$  1 1/2in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only 26-55 each. P. & P. 25p.


**VR46 & BEXINE SPEAKERS & CABINET FABRICS**  
app. 5 1/2 in. wide. Our price 85p yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. for samples.

## HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. PRICE £2.30. P. & P. 15p.

**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE £1.15. P. & P. 10p.
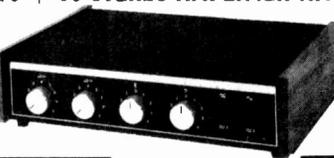
## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



**NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION**

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibre glass printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response  $\pm$  3dB 12-30,000Hz. Sensitivity better than 80mV into 1M  $\Omega$ . Full power bandwidth  $\pm$  3dB 12-15,000Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Test requirements 35V at 1-0 amp. Overall size—12" wide  $\times$  8" deep  $\times$  2 1/2" high. Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

**PRICES AMPLIFIER KIT. £11.55** P. & P. 18p.  
(Magnetic input components 35p extra)

**POWER PACK KIT. £8.80** P. & P. 43p.  
**CABINET. £3.30** P. & P. 35p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £23-10. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosqueue use, etc.

**3-VALVE AUDIO AMPLIFIER EA34 MK II**  
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in w.  $\times$  4in. d.  $\times$  4 1/2in h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 41 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £5.50. P. & P. 35p.

**BRITISH MADE SOLID STATE ALL SILICON STEREO AMPLIFIER.** 15 watts r.m.s. per channel output. Pre. res. 20Hz to 20KHz. Suitable for magnetic or ceramic pickup tape mic, etc., built-in switchable scratch filter, rumble filter and loudness control. 60 in/m slider controls for bass, treble and volume. 10 way push button function, selector switch. This amplifier has specification and performance usually only found in amplifiers costing twice as much. Each amplifier supplied, tested and fully guaranteed. Finished in the most attractive contemporary style teak cabinet. Size 16 1/2in  $\times$  8 1/2in  $\times$  4 1/2in. Makers' recommended price £46.36, incl. V.A.T. Our price (while stocks last) £35.75 incl. V.A.T. plus 75p P. & P. Send S.A.E. for full details of specification.

**10/14 WATT HI-FI AMPLIFIER KIT**  
A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Simple reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL24s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 16p plus S.A.E. (Free with parts). All parts sold separately. ONLY £8.80. P. & P. 50p. Also available ready built and tested £12-10. P. & P. 60p.

**10/14 WATT HI-FI AMPLIFIER KIT**  
A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Simple reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL24s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 16p plus S.A.E. (Free with parts). All parts sold separately. ONLY £8.80. P. & P. 50p. Also available ready built and tested £12-10. P. & P. 60p.

**10/14 WATT HI-FI AMPLIFIER KIT**  
A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Simple reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL24s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 16p plus S.A.E. (Free with parts). All parts sold separately. ONLY £8.80. P. & P. 50p. Also available ready built and tested £12-10. P. & P. 60p.

**10/14 WATT HI-FI AMPLIFIER KIT**  
A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Simple reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15  $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL24s, ECC83, EF86 and EZ80 rectifier. Simple instruction booklet 16p plus S.A.E. (Free with parts). All parts sold separately. ONLY £8.80. P. & P. 50p. Also available ready built and tested £12-10. P. & P. 60p.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

## HARVERSON SURPLUS CO. LTD.

Dept. PE, 170 High St., Merton, London, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES


## "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230v. 50/60 c/s. Variable output 0-260v.



### MODEL S-260 GENERAL PURPOSE BENCH MOUNTING

1 amp.	\$7-00
2-5 amp.	\$8-05
5 amp.	\$11-75
8 amp.	\$15-90
10 amp.	\$22-50
12 amp.	\$23-80
20 amp.	\$49-00
25 amp.	\$58-00
40 amp.	\$82-50

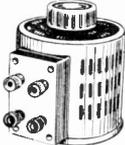

### MODEL S-260B

Panel mounting

1 amp.	\$7-00
2-5 amp.	\$8-05

Carriage and Packing Extra

## AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

80W	\$2-10	P. & P. 18p
150W	\$2-70	P. & P. 18p
300W	\$3-50	P. & P. 23p
600W	\$5-25	P. & P. 33p
1000W	\$7-50	P. & P. 38p
1600W	\$10-20	P. & P. 43p
2250W	\$17-25	P. & P. 50p
5000W	\$36-00	P. & P. 21


## MCA-220 AUTOMATIC VOLTAGE STABILIZER

Input 88-125V a.c. or 176-250V a.c. Output 120V a.c. or 240V a.c. 200VA rating. \$11-97. Post 50p.


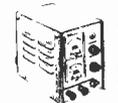
## PS-200 REGULATED P.S.U.

Solid state. Variable output 5-20V d.c. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240V a.c. Size 7 1/2in. x 5 1/2in. \$19-75. Post 50p.




## PS-1000B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12V d.c. up to 3 amps. Meter to monitor current. Input 220/240V a.c. Size 4in. x 8 1/2in. \$11-97. Post 25p.


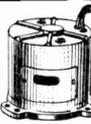
## 230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 RRH CW. 50p each. Post 12p.



## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fitting. 1/4in. dia. shafts. Bulk quantities available.



25 WATT. 10/25/50/100/250/500/1000 ohms. 95p. P. & P. 10p.

60 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. \$1-35. P. & P. 10p.

100 WATT. 1-3/10/25/50/100/250/500/1000 or 2500 ohms. \$1-95. P. & P. 15p.

240° Wide Angle 1mA Meters  
MW1-6 60mm square \$3-97  
MW1-8 80mm square \$4-97  
Post extra



## 230 VOLT A.C. 50 CYCLES RELAYS



Brand new. 3 sets of changeover contacts at 5 amp. rating. 50p each. Post 10p (100 lots 240) Quantities available.

# SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

### TYPE SW.100 100mm x 80mm Fronts

50μA.	\$4-15	5 amp. d.c.	\$3-90
100-0-50μA.	\$3-05	300V a.c.	\$3-70
100μA.	\$3-05	VU Meter	\$4-90
100-0-100μA.	\$3-90		
500μA.	\$3-70		
1mA.	\$3-60		
20V d.c.	\$3-60		
50V d.c.	\$3-60		
300V d.c.	\$3-60		
1 amp. d.c.	\$3-60		



### Type MR.85P. 4 1/2in. x 4 1/2in. Fronts

50μA.	\$3-90	50mA.	\$3-90
100μA.	\$3-90	500mA.	\$3-90
1 amp.	\$3-90	1 amp. a.c.*	\$3-90
5 amp.	\$3-90	5 amp. a.c.*	\$3-90
15 amp.	\$3-90	10 amp. a.c.*	\$3-90
30 amp.	\$3-95	20 amp. a.c.*	\$3-90
20V d.c.	\$3-90	30 amp. a.c.*	\$3-90
50V d.c.	\$3-90		
150V d.c.	\$3-90		
300V d.c.	\$3-90		
15V a.c.	\$3-95		
300V a.c.	\$3-95		
8 Meter 1mA.	\$3-90		
VU Meter	\$4-55		
5000-500μA.	\$3-90		
1mA.	\$3-90		
1-0-1mA.	\$3-90		
5mA.	\$3-90		
10mA.	\$3-90		



### Type MR.88P. 1 21/32in. square Fronts.

200mA.	\$2-95	300mA.	\$2-95
500mA.	\$2-95	750mA.	\$2-95
1 amp.	\$2-95	1 amp.	\$2-95
2 amp.	\$2-95	5 amp.	\$2-95
10 amp.	\$2-95	10 amp.	\$2-95
3V d.c.	\$2-95	10V d.c.	\$2-95
15V d.c.	\$2-95	20V d.c.	\$2-95
50V d.c.	\$2-95	100μA.	\$2-45
100μA.	\$2-45	100-0-100μA.	\$2-40
200μA.	\$2-25	200μA.	\$2-25
500μA.	\$2-25	500μA.	\$2-25
500-0-500μA.	\$2-25	1mA.	\$2-25
1mA.	\$2-25	1-0-1mA.	\$2-25
500V d.c.	\$2-25	2mA.	\$2-25
15V a.c.	\$2-30	5mA.	\$2-25
50V a.c.	\$2-30	10mA.	\$2-25
100V a.c.	\$2-30	20mA.	\$2-25
300V a.c.	\$2-30	50mA.	\$2-25
500V a.c.	\$2-30	100mA.	\$2-25
8 Meter 1mA.	\$2-90	150mA.	\$2-25
8 Meter	\$2-65		




### Type SD.830 82-5mm x 110mm Fronts

10mA.	\$3-10	500mA.	\$2-90
50mA.	\$3-10	1 amp.	\$2-90
100mA.	\$3-10	5 amp.	\$2-90
500mA.	\$3-10	10 amp.	\$2-90
1 amp.	\$3-10	50V d.c.	\$2-90
1 amp.	\$3-10	20V d.c.	\$2-90
5 amp.	\$3-10	300V d.c.	\$2-90
10 amp.	\$3-10	15V a.c.	\$3-10
5 amp. d.c.	\$3-10	30V a.c.	\$3-10
10V d.c.	\$3-10	50V a.c.	\$3-10
20V d.c.	\$3-10	VU Meter	\$3-50
300V d.c.	\$3-10		
15V a.c.	\$3-10		
30V a.c.	\$3-10		
50V a.c.	\$3-10		




### Type MR.52P. 2 1/2in. square Fronts.

50μA.	\$2-60	10V d.c.	\$2-60
100μA.	\$2-60	20V d.c.	\$2-60
500μA.	\$2-60	50V d.c.	\$2-60
1mA.	\$2-60	300V d.c.	\$2-60
5 amp. a.c.*	\$2-60	13V a.c.	\$2-60
10 amp. a.c.*	\$2-60	300V a.c.	\$2-60
20 amp. a.c.*	\$2-60	8 Meter 1mA.	\$2-60
30 amp. a.c.*	\$2-60	VU Meter	\$2-60
		100-0-100μA.	\$2-50
		200μA.	\$2-50
		500μA.	\$2-50
		1 amp. a.c.*	\$2-50
		5 amp. a.c.*	\$2-50
		10 amp. a.c.*	\$2-50
		20 amp. a.c.*	\$2-50
		30 amp. a.c.*	\$2-50

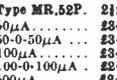


### Type SD.840 63-5mm x 86mm Fronts

50μA.	\$3-05	500mA.	\$2-90
100-0-50μA.	\$3-05	1 amp.	\$2-90
100μA.	\$3-05	5 amp.	\$2-90
100-0-100μA.	\$3-05	10 amp.	\$2-90
200μA.	\$3-05	50V d.c.	\$2-90
500μA.	\$3-05	20V d.c.	\$2-90
1mA.	\$3-05	300V d.c.	\$2-90
5mA.	\$3-05	15V a.c.	\$2-90
10mA.	\$3-05	30V a.c.	\$2-90
50mA.	\$3-05	50V a.c.	\$2-90
100mA.	\$3-05	VU Meter	\$3-15

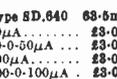


### Type MR.65P. 3 1/2in. x 3 1/2in. Fronts

50μA.	\$3-70	10V d.c.	\$2-60
100-0-50μA.	\$3-15	20V d.c.	\$2-60
100μA.	\$3-15	50V d.c.	\$2-60
100-0-100μA.	\$3-10	150V d.c.	\$2-60
200μA.	\$3-05	300V d.c.	\$2-60
500μA.	\$2-75	15V a.c.	\$2-60
1mA.	\$2-60	50V a.c.	\$2-60
5mA.	\$2-60	150V a.c.	\$2-60
10mA.	\$2-60	300V a.c.	\$2-60
50mA.	\$2-60	8 Meter 1mA.	\$2-60
100mA.	\$2-60	VU Meter	\$3-70
500mA.	\$2-60	50mA a.c.*	\$2-60
1 amp.	\$2-60	100mA a.c.*	\$2-60
5 amp.	\$2-60	200mA a.c.*	\$2-60
10 amp.	\$2-60	500mA a.c.*	\$2-60
15 amp.	\$2-60	1 amp. a.c.*	\$2-60
20 amp.	\$2-60	5 amp. a.c.*	\$2-60
30 amp.	\$2-60	10 amp. a.c.*	\$2-60
50 amp.	\$2-90	20 amp. a.c.*	\$2-60
5V d.c.	\$2-60	30 amp. a.c.*	\$2-60

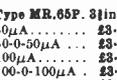

### Type MR.45P. 2in. square Fronts.

50μA.	\$2-70	5 amp.	\$2-40
100μA.	\$2-70	10V d.c.	\$2-40
500μA.	\$2-60	20V d.c.	\$2-40
1mA.	\$2-60	50V d.c.	\$2-40
5 amp. a.c.*	\$2-50	300V d.c.	\$2-40
10 amp. a.c.*	\$2-50	8 Meter 1mA.	\$2-60
20 amp. a.c.*	\$2-50	VU Meter	\$2-70
30 amp. a.c.*	\$2-50	1 amp. a.c.*	\$2-40
		5 amp. a.c.*	\$2-40
		10 amp. a.c.*	\$2-40
		20 amp. a.c.*	\$2-40
		30 amp. a.c.*	\$2-40

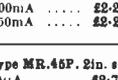

### Type MR.66. 3 1/2in. square Fronts.

1 amp.	\$2-60
5 amp.	\$2-60
15 amp.	\$2-60
30 amp.	\$2-60
50 amp.	\$2-60
5V d.c.	\$2-60
10V d.c.	\$2-60
20V d.c.	\$2-60
50V d.c.	\$2-60
150V d.c.	\$2-60
300V d.c.	\$2-60
500μA.	\$2-60
1mA.	\$2-60
5 amp. a.c.*	\$2-60
10 amp. a.c.*	\$2-60
20 amp. a.c.*	\$2-60
30 amp. a.c.*	\$2-60



## "SEW" BAKELITE PANEL METERS

25μA.	\$4-60	500mA.	\$2-60
50μA.	\$3-65	1 amp.	\$2-60
100μA.	\$3-65	5 amp.	\$2-60
100-0-100μA.	\$3-00	10 amp.	\$2-60
500μA.	\$2-70	50 amp.	\$2-60
500-0-500μA.	\$2-70	10V d.c.	\$2-60
1mA.	\$2-60	20V d.c.	\$2-60
5mA.	\$2-60	50V d.c.	\$2-60
10mA.	\$2-60	150V d.c.	\$2-60
50mA.	\$2-60	300V a.c.*	\$2-65
100mA.	\$2-60	500mA a.c.*	\$2-65
500mA.	\$2-60	1 amp. a.c.*	\$2-65
1 amp.	\$2-60	5 amp. a.c.*	\$2-65
5 amp.	\$2-60	10 amp. a.c.*	\$2-65
10 amp.	\$2-60	20 amp. a.c.*	\$2-65
15 amp.	\$2-60	30 amp. a.c.*	\$2-65
20 amp.	\$2-60		
30 amp.	\$2-60		
50 amp.	\$2-90		
5V d.c.	\$2-60		



## "SEW" EDGEWISE METERS

### Type PE.70. 3 1/2in. x 1 15/32in. x 2 1/2in. deep.

50μA.	\$3-75	500μA.	\$3-20
50-0-50μA.	\$3-60	1mA.	\$3-20
100μA.	\$3-60	300V a.c.	\$3-25
100-0-100μA.	\$3-50	VU Meter	\$3-85
200μA.	\$3-50		

\*MOVING IRON—ALL OTHERS MOVING COIL  
Please add postage

## "SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 105mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3in. mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50μA.	\$5-90	10V d.c.	\$5-95
100μA.	\$5-40	20V d.c.	\$5-95
1mA.	\$5-95	50V d.c.	\$5-95
50-0-50μA.	\$5-40	300V d.c.	\$5-95
10-0-1mA.	\$5-95		
1A d.c.	\$5-95	500mA/5A d.c.	\$7-00
5A d.c.	\$5-95	5V/50V d.c.	\$7-00



- AF20—Mono Amplifier, \$4-90.
- AF30—Mono Pre-Amplifier, \$2-61.
- AF310—Mono Amplifier \$5-91.
- AT5—Automatic Light Control, \$2-58.
- AT30—Photo Cell Switching Unit, \$5-70.
- AT50—400W Triac Light Dimmer Speed Control, \$4-80.
- AT55—1,300W Triac Light Dimmer Speed Control, \$5-70.
- AT56—2,200W Triac Light Dimmer Speed Control, \$6-90.
- AT60—Psychedelic Light Control, Single Channel, \$7-80.
- AT65—Psychedelic Light Control, 3 Channel, \$14-55.
- HF61—Radio, \$3-38.
- HF65—F.M. Transmitter \$2-70.
- HF75—F.M. Receiver, \$2-88.
- HF310—F.M. Tuner Unit, \$15-81.

- HF325—De-Luxe F.M. Tuner Unit, \$24-12.
- HF330—Stereo Decoder for use with HF310 or HF325, \$9-98.
- HF390—Aerial Amplifier for A.M./F.M. bands I, II and III, \$11-77.
- GP310—Stereo Pre-Amp to use with 2 AF310, \$21-27.
- GU330—Tremolo Unit for guitars, etc., \$7-50.
- NT10—Power Supply 100mA 9V Stab., 12V Unstab., \$6-15.
- NT300—Professional Stab. Power Supply 2 x 30V, 2-2A, \$12-51.
- NT305—Transistor Converter 12/15V a.c./d.c. to 6V, 7.5V or 9V d.c., \$4-50.
- NT310—Power Supply 240V a.c. to 2 x 18V d.c. at 2A, \$4-80.
- NT315—Power Supply 240V a.c. to 4-5-15V d.c., 500mA, \$9-57.

Send S.A.E. for new 8-page list of Semiconductor and Valves

ALL PRICES ARE EXCLUSIVE OF 10% V.A.T.



ALSO SEE FOLLOWING PAGES



### UNR 30 RECEIVER



4 Bands covering 550kHz-30MHz. FET. 8 Meter. Variable BFO for 88B. Built-in Speaker. Bandspread. Sensitivity Control. 220/240V a.c. or 12V d.c. 121 x 4 1/2 in. 7 in. Brand new with instructions.

**OUR PRICE £15.75** Carr. 37p


### UR-1A RECEIVER



4 Bands covering 550kHz-30MHz. FET. 8 Meter. Variable BFO for 88B. Built-in Speaker. Bandspread. Sensitivity Control. 220/240V a.c. or 12V d.c. 121 x 4 1/2 in. 7 in. Brand new with instructions.

**OUR PRICE £25.00** Carr. 37p

### SKYWOOD CX203 RECEIVER

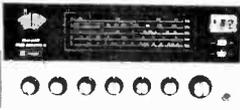

Solid state. 6 bands covering 200-420kHz and 0.55 to 30MHz. Illuminated slide rule dial. Bandspread. Aerial tuning BFO. AVC. ANL. "S" meter. AM/CW/88 B. Integrated speaker and phone socket. 220/240V a.c. or 12V d.c. Size 325 x 266 x 130mm. Complete with instructions and complete.

**OUR PRICE £32.50** Carr. 50p

### LAFAYETTE HA-600 RECEIVER



General coverage 150-400kHz. 550kHz-30MHz. FET front end. 2 mech. filters. Product detector, variable BFO, noise limiter. 8 Meter Bandspread. RF Gain. 15in x 9 1/2 in x 8 1/2 in. 18 lb. 220/240V a.c. or 12V d.c. Brand new with instructions.

**OUR PRICE £50.00** Carr. 50p

### TRIO 9R59DS RECEIVER



4 bands covering 550kHz-30MHz continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. 881-CW. ANL. Variable BFO. 8 meter. Sep. bandspread dial. IF frequency 445kHz audio output 1.5W. Variable RF and AF gain controls 115/250V a.c. Size: 7in x 13in x 10in with instruction manual.

**OUR PRICE £49.50** Carr. Paid

**FULL RANGE OF TRIO STOCKED**



### EMI LOUDSPEAKERS



Model 350. 13in x 8in with single tweeter/crossover. 20-20,000 Hz. 15W RMS. Available 8 or 15 ohms. £7.25 each. P. & P. 37p.

Model 450. 13in x 8in with twin tweeters/crossover. 55-13,000 Hz. 8W RMS.

Available 8 or 15 ohms. £8.62 each. P. & P. 25p.

### SPECIAL OFFER!

#### STEREO SPEAKERS

Matched pair of bookshelf speakers. De luxe teak veneered finish. Size 14 1/2 in x 9 in x 7 1/2 in. 8 ohms. 8W RMS. 18W peak. Complete with DIN lead.

**OUR PRICE £12.95** Carr. 50p

### HA-10 STEREO HEADPHONE AMPLIFIER



All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 5MU/100MU. Output 50mW.

**OUR PRICE £5.97** P. & P. 20p

### MP7 MIXER PREAMPLIFIER



5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2 in x 5 in x 3 in. Inputs: Mics: 3 x 3mV/50K; 2 x 3mV/600 ohm. Phono meg. 4mV/50K. Phono ceramic 100mV. 1 meg. Output 250mV/100K.

**OUR PRICE £8.97** P. & P. 20p

### 1021 STEREO LISTENING STATION



For balancing and gain selection of loudspeakers with additional facility for stereo head-phones switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets 6in x 4in x 2 1/2 in.

**OUR PRICE £2.25** P. & P. 20p

### HAND HELD 2-WAY WALKIE TALKIES

2 channel 300mW. £52.50 Pair. Post 50p.

3 channel 1W. £71.25 Pair. Post 50p.

Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic aerial. Complete carrying case. 100mW £24.95 pair. Post 50p.

(Note: Licence required for operation in U.K.)

## AUDIOTRONIC

### ACR14 BATTERY MAINS CASSETTE RECORDER

Portable twin mono recorder with automatic recording level control. Built in speaker. Ear piece socket. Input or record player. Fast forward and rewind. Output 220/240V a.c. or 6V d.c. operation. Complete with remote control microphone, mains lead, earpiece and batteries.

**GWS PRICE £10.50** P. & P. 50p

### Sportsman AM/FM Portable Radio AR1000

5 wavebands covering 4 M.: 535-1065kHz; F.M. 88-108MHz; A.I.R. 108-135MHz; P.B. 147-174MHz; W.B. 162-5MHz. Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for F.M. and built in ferrite bar for A.M. A.F.C. 3in speaker. Earpiece socket. Green leatherette covered cabinet with metaliside panels. Size 152 x 79 x 219mm. Battery/mains operation.

**OUR PRICE £11.50** P. & P. 35p

### AMR-9000 GLOBAL AM/FM PORTABLE

10 wavebands covering 4 M.: 535-1605kHz. L.W.: 150-380kHz; M.R. 1.6-4.0MHz; S.W.1: 4.0-8.0MHz; S.W.2: 8.0-16MHz; S.W.3: 16-24MHz; P.S.B.1: 30-50MHz; P.S.B.2: 148-174MHz; F.M. 88-108MHz; A.I.R.: 108-135MHz. Features time zone map and tuning dial. Large clear scale. Telescopic aerial and built in aerial. A.F.C. on F.M. 6in x 4in speaker and personal earpiece. Battery/mains operation. Size: 345 x 133 x 305mm.

**OUR PRICE £36.00** P. & P. 50p

### STEREO HEADPHONES

LSH20. Individual volume controls. Stereo mono switch. 8 ohms 40-19,000Hz. £3.50 P. & P. 30p

LSH30. Open back type. Individual tone and volume controls. 8 ohms 30-20,000Hz. £5.50 P. & P. 30p

LSH40. Two way speaker system. Individual volume controls. 8 ohms 20-20,000Hz. £6.95 P. & P. 30p

LSH60. 3in speaker units. 8 ohms 20-20,000Hz. Complete with zipped carrying case. £8.50 P. & P. 30p

LQH400. 4-channel dynamic headphones. Each earpiece has 4 drive units. Two stereo jack plugs fitted to leads. 4-32 ohms. 20-20,000Hz. £9.95 P. & P. 30p

### RANGE OF HIGH QUALITY EQUIPMENT

### ACD660 STEREO CASSETTE DECK



A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter, normal/chrome tape selector, twin VU meter, allier 'record/playback level controls, front panel headphone socket, recording indicator lamp, phono/Din line input sockets, 3.5mm mike input sockets, etc. Frequency response 100-8kHz (100-12kHz CrO2). S/N -45dB. Crosstalk -45dB. Separation -35dB. Noise limiter -6dB at 10kHz. Complete with phone connecting leads.

**GWS £39.50** Carr. & P. 50p

### AHP8D 8 TRACK STEREO TAPE DECK

Can be used with most hi-fi amplifiers. Push button track selector and illuminated track indicators. Attractive cabinet with black and silver trim. Output level 750mV. 220/240V a.c.

**GWS £11.95** P. & P. 50p, plus V.A.T.

### AHP8A 8 TRACK STEREO TAPE PLAYER



Incorporates built in amplifiers giving 41 + 41W r.m.s. output. Pushbutton track selector, illuminated track indicators, slider controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output impedance 8 ohms. 220/240V a.c.

**GWS £17.25** P. & P. 50p, plus V.A.T.

## AUDIOTRONIC DOLBY 'B' NOISE REDUCTION UNITS

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 16 1/2 in x 8 in x 3 1/2 in. a.c. 0/250V.2.

**PROCESS TWO**  
For use with cassette and tape recorders. Freq. res. 30Hz-20kHz-2dB. Off tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. S/N better than 70dB. Supplied with test cassette or tape as required.

**OUR PRICE £34.50** P. & P. 50p

**PROCESS FOUR**  
For use with semi professional tape recorders. Freq. res. 30Hz-20kHz +2dB. S/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

**OUR PRICE £50.00** P. & P. 50p

### LOW NOISE TAPE CASSETTES



TYPE	5	10	25
C90	£1.29	£2.53	£5.99
C90	£1.85	£3.62	£8.59
C120	£2.29	£4.48	£10.63

P. & P. 15p Post Free

CASSETTE TAPE HEAD CLEANER 30p each. P. & P. 6p



Attractive black and silver finish. 12V neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with red pilot lamp. Complete with speakers, mounting brackets and instructions.

**ONLY £12.50** P. & P. 40p



Push button tuning of one LW and five MW stations of your choice. 12V pos. or neg. earth. Complete with speaker, mounting brackets and instructions.

**OUR PRICE £8.95** P. & P. 50p



Manual tuning of Medium and Long waves. 12V pos. or neg. earth. Complete with speaker, mounting brackets and instructions.

**OUR PRICE £6.50** P. & P. 50p



5 section. Fully automatic. 12V d.c. Extends to approx. 40in. Complete with switch, all leads and instructions.

**OUR PRICE £5.95** P. & P. 50p

# SAVE UP TO 33 1/3% OR MORE! GWS

## RECORD DECK PACKAGES



### Carriage and Packing 75p

Complete units with Stereo plinth and carriage ready wired in and cover.

<b>GARRARD</b>	
2025 TC/9TAHCD	£10-65
SP25 111/G800	£15-00
SP25 111/M44E	£16-45
SP25 111/M44-7	£16-10
SP25 111/M55E	£16-80
SP25 111 Module/M75-6	£18-89
AP76/G800	£23-50
AP76/M800E	£25-95
AP76/M44E	£24-95
AP76/M55E	£25-65
AP76/M75ED	£31-70
AP76/M75EJ	£27-85
AP76 Module M75-6	£26-85
AP96 Module M75-6	£30-40
ZERO 1008 Module/M93E	£41-85
<b>B.S.R. McDONALD</b>	
210/SCTM	£6-85
MP60/G800	£15-00
MP60/TPD1/G800	£15-20
MP60/M44-7	£16-60
HT70/TPD1/G800	£18-60

<b>GOLDRING</b>	
GL72/G800	£30-90
GL75/G800	£33-60
GL75/G800E	£36-75
<b>GOODMANS</b>	
TD100/G800 Teak	£46-85
TD100/G800 White	£48-60
<b>LEAK</b>	
Delta/M75-6	£43-95
<b>PHILIPS</b>	
GA105/GP200	£13-80
GA160/GP200 Teak	£19-50
GA212/GP400	£45-25
GA308 (less cartridge)	£23-85
GA308 P/C	£32-75
<b>PIONEER</b>	
PL12D (Less cartridge)	£31-75
PL15C (Less cartridge)	£44-25
PL41D (Less cartridge)	£104-75
PL50 (Less cartridge)	£98-80
PL61 (Less cartridge)	£110-30
PLA35 (Less cartridge)	£61-55
<b>THORENS</b>	
TD160C/Ortofon M15E	
Super	£66-95
TD125 AB/11/Ortofon	
M15ES	£104-25
TD165/Ortofon M15E	
Super	£59-60
<b>WHARFEDALE</b>	
Linton/M44-7 Teak	£23-70
Linton/M44-7 White	£23-80

## SINCLAIR PROJECT 60 PACKAGE DEALS



2 x Z30/Stereo 60/PZ5	£15-95. P. & P. 37p.
2 x Z30/Stereo 69/PZ6	£18-00. P. & P. 37p.
2 x Z50/Stereo 60/PZ8	£20-25. P. & P. 37p.
Transformer for PZ8	£3 extra.
Active Filter Unit	£4-45.
Project 60 FM Tuner	£14-95.
Pair of Q16 Speakers	£10-70.
Sinclair Project 60S	£20-97. P. & P. 37p.
All Sinclair Products in stock:	
3000 Stereo Amplifier	£22-85;
3000 Stereo Amplifier	£28-85;
2000/3000 Stereo Tuner	£28-80.
Q300 Speakers	£23-95 pair. P. & P. 60p extra on above items.

## RECORD DECKS



### Carriage & Packing 50p

<b>B.S.R. McDONALD</b>	
C114 Mini	£3-95
C129 Mono	£5-50
C137	£7-00
510/TPD1	£13-95
610	£9-90
610/TPD1	£14-85
T105	£19-20
810	£24-50
MP60	£7-65
MP60/G800	£10-25
MP60/TPD1	£12-60
MP60/TPD2	£11-25
HT70	£10-97
HT70/G800	£13-60
HT70/TPD1	£15-95
<b>CONNOISSEUR</b>	
B11 Kit	£9-10
B11 Chassis	£11-35
BD1/SAU2/Plinth/Cover	£27-60
BD1S/SAU2/Chassis	£22-70
BD2/SAU2/Plinth/Cover	£28-20

<b>GARRARD</b>	
2025 TC/Stereo	£6-40
SP25 111	£8-50
SP25 111/Acos GP104	£8-50
SP25 111/G800	£10-85
SP25/M75-6	£13-90
A776	£15-55
SL65B	£11-15
SL72B	£17-75
SL95B	£25-25
401	£23-50
ZERO 100A	£30-30
ZERO 1008	£27-85

<b>GOLDRING</b>	
G99	£16-85
G101P/C	£16-85
GL69/2	£15-75
GL72	£17-85
GL72/P	£23-20
GL75	£23-75
GL75P	£29-30
GL78 P/C	£46-55
GL85P/C	£49-50

## SPECIAL GARRARD OFFERS!



### STEREO 1025T

4 speed autochanger unit fitted with stereo ceramic cartridge.

OUR PRICE **£4-95** Carr. & Ins. 50p

### SP25 III WITH ACOS GP 104

4 speed single record player fitted with Acos GP104 stereo ceramic cartridge.

OUR PRICE **£8-50** Carr. & Ins. 50p

## AUDIOTRONIC AMB500 MULTI BAND RADIO

5 wavebands covering MW 535 - 1605KHz and F.M. 88-175MHz. All transistor. Battery or mains operation. Built in aerial and 8 section telescopic aerial. Complete with batteries, shoulder strap and earpiece.

ONLY **£6-95** P. & P. 35p

## FANTASTIC OFFER!



### AKAI CS35 CASSETTE RECORDER

with a pair of CS88 speakers. List £96-10.

OUR PRICE **£56-50** P. & P. 50p

<b>CASSETTE, P. &amp; P. 50p.</b>	
CS35D Deck	£44-45
CS35/CS88 Speakers	£67-85
GX40D Deck	£57-20
GX40 Recorder	£67-20
GX40T Deck/Receiver	£99-05
GX45 Deck	£78-25
GX46D Dolby Deck	£93-55
GX46 Recorder	£99-85
GX60D Deck	£87-65
GX60D Dolby Deck	£92-65

<b>CARTRIDGE (P. &amp; P. 50p)</b>	
CR81 Deck with amp.	£65-40
CR81D Deck	£53-80
CR81T Recorder/Receiver	£92-75
CR808S 4 channel Recorder	£114-25
CR108S 4 chan. Recorder	£93-65

<b>TAPE (P. &amp; P. 75p)</b>	
4000DS Deck	£59-95
4000DS Dust Cover	£3-95
L72L Recorder	£80-35
X5000 Recorder	£82-50
X201D Deck	£108-20
GX20D Deck	£128-95
GX21D	£139-40
GX280D Deck	£196-50
GX370 Deck	£211-50

**TAPE CASSETTE (P. & P. 75p)**

GX190D Deck **£144-50**

**MICROPHONES (P. & P. 50p)**

ADM-11 Dynamic (pair) **£7-50**

**STEREO RECEIVERS (P. & P. 75p)**

AA6300 20+20 watt	£61-95
AA8030 25+25 watt	£92-50
AA8080 40+40 watt	£117-50
AA8100S 2x36 or 4x18 watt	£175-00
AA8500 65+65 watt	£150-50

**STEREO AMPLIFIERS (P. & P. 50p)**

AA5200 20+20 watt	£61-75
AA5500 30+30 watt	£78-50
AA5900 45+45 watt	£117-50

**STEREO TUNERS (P. & P. 50p)**

AT350 AM/FM	£60-50
AT380 AM/FM	£94-50

**4-CHANNEL UNIT (P. & P. 50p)**

SS1 Synthesiser **£33-95**

**SPEAKERS**

SW155 (each) **£51-00**

**STEREO HEADPHONES**

ASE11	£4-75
ASE20	£7-30
ASE22	£8-25

## HOMER INTERCOMS



Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station **£12-97. P. & P. 15p.**

3 Station **£5-25. P. & P. 15p.**

4 Station **£6-82. P. & P. 17p.**

## SH628 STEREO HEADPHONES



Outstanding value. Soft earpads, adjustable headband.

8-16 ohms. 20-20,000 Hz.

Complete with lead and stereo plug.

OUR PRICE **£1-87** P. & P. 30p

## TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive magnetic headset with soft earpads. Impedance 2,000 ohms (d.c. 500 ohms). Frequency response 200-4,000 Hz.

OUR PRICE **£2-25** P. & P. 30p


## LHO25 STEREO HEADPHONES



Lightweight headphones with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6 ft cord and plug.

OUR PRICE **£1-95** P. & P. 30p

## BH001 HEADSET AND BOOM MICROPHONE

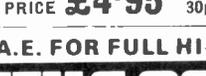

Moving coil. Headphone imp. 16 ohms. M.R. imp. 200 ohms. Ideal for language teaching, communications etc. Complete with leads and plugs.

OUR PRICE **£4-95** P. & P. 30p

## FM TUNER CHASSIS



6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in x 4in x 2 1/2in 3 I.P. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108MHz. Ready built ready for use.

OUR PRICE **£5-95** P. & P. 20p

Stereo Multiplex Adaptor **£4-87.**

## SPECIAL PURCHASE!

### FERGUSON EXPORT MODELS



3408 STEREO TUNER AMP. Covers FM 88-108 MHz. Five push button tuning scales. 8+8 watts rms. Inputs for stereo ceramic cartridge and tape, etc. Separate bass, treble, balance and volume controls.

OUR PRICE **£31-50** Carr. 50p

### 3416 STEREO TAPE DECK



4 track. 7 1/2, 3 1/2, 1 1/2 i.p.s. Stereo/mono record/play. 7in reels. Inputs for dynamic mikes, radio, gram. Complete with cover.

OUR PRICE **£41-95** Carr. 75p

## VAT

All prices are subject to

**10% VAT** (10p in the £)

Order with confidence by post - but remember to add 10% VAT (10p in the £) to total value of goods including carriage/packing and send cash with order.

PLEASE PRINT NAME & ADDRESS CLEARLY.

## SEND LARGE S.A.E. FOR FULL HI-FI DISCOUNT LIST

# G.W.SMITH & CO (RADIO) LTD

ALL MAIL ORDERS TO  
UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ  
TELEPHONE 01-205 3735

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

<b>CENTRAL LONDON</b>			
257/8, Tottenham Court Rd. W.1.	Tel: 01-580 0670	311, Edgware Road, W.2.	Tel: 01-262 0317
10, Tottenham Court Rd. W.1.	Tel: 01-837 2322	382, Edgware Road, W.2.	Tel: 01-723 4194
27, Tottenham Court Rd. W.1.	Tel: 01-436 3715	152/3, Fleet Street, E.C.4.	Tel: 01-353 2833
87, Tottenham Court Rd. W.1.	Tel: 01-580 3739	376, Harrow Road, W.9.	Tel: 01-286 9530
21, Old Compton Street, W.1.	Tel: 01-437 9369		
3, Lisie Street, W.C.2.	Tel: 01-437 8204	<b>ESSEX</b>	
34, Lisie Street, W.C.2.	Tel: 01-437 9155	86, South Street, Romford.	Tel: Romford 20218
119, Edgware Road, W.2.	Tel: 01-723 9789	<b>SURREY</b>	
193, Edgware Road, W.2.	Tel: 01-723 6211	1046, Whitgift Centre, Croydon.	Tel: 01-681 3027
		27 & 21, Eden Street, Kingston.	Tel: 01-546 7885
		32, Hill Street, Richmond.	Tel: 01-948 1481

## ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY

Buy it with Access

BARCLAYCARD

CREDIT TERMS FOR CALLERS (£50 and over)


ALL EQUIPMENT IS BRAND NEW, FULLY GUARANTEED AND OFFERED WITH FULL AFTER SALES SERVICE

All items and prices are correct at 21-673 but subject to change without notice. E & O E.

TERMS Retail mail order subject to £1.00 minimum order. Cash with order only. Trade and educational establishments M/AC on application (minimum £5.00). Postage 10p inland, 25p, Europe. GUARANTEE: All goods carry full manufacturer's warranty. Get in touch today for a complete run-down of devices available from SCS (include SAE) S.C.S. Components Ltd., P.O. Box No. 26, Wembley, Middlesex HA0 1YY Registered in London No. 888454




## Device of the Month NE540L

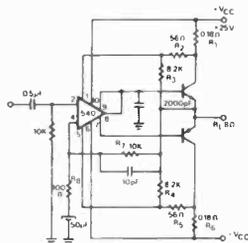
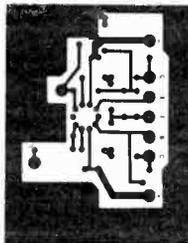
### 35Watt Amplifier

The Signetics 540 is a monolithic, class AB power audio amplifier designed specifically to drive a pair of complementary output transistors.



This device features: internal current limiting; low standby current; high output current capability; wide power bandwidth; low distortion—features which make this device ideal for use as an audio power amplifier.

**Signetics power driver NE540L**  
Yours for just

£1-20  
+  
VAT

including application notes

## Compatible device MCI339P



From Motorola, a monolithic dual stereo preamplifier


for low noise preamplification of stereo audio signals. Just look at some of these features:

- \* Low audio noise
- \* High channel separation
- \* Single power supply
- \* High input impedance
- \* Built-in power supply filter
- \* Emitter follower output

**Motorola monolithic dual stereo preamplifier**

only  
£1-20  
+  
VAT

including applications notes.

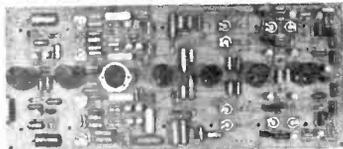

### AURORA

Multichannel Sound Controlled Light (PE Apr./Aug. 71). S/c's (excl. SCR's), Rs, Cs, Pots, Cores—8 ch. £17-75; 4 ch. £10-15. Reg. PSU £3-65. PCB—4 ch. control (4 1/2 in x 10 1/2 in) Mk. 2—also holds rotary or slider pots £2-35. PCB (4 1/2 in x 5 in) Mk. 2—for PSU, Sync Gen. 8 cores, 8 SCR's, £1-35. SCR's—1A, 50p, 3A, 55p.

**A.F. SIGNAL GENERATOR**  
(PE Nov. 72). S/c's, Rs, Cs, Pots, Sw's, PCB (2 1/2 in x 4 in) also holds Sw's, £3-15.

**AUDIO MIXER**  
(PE Jan. 72). Rs, Cs, Pots, PCB (1 1/2 in x 2 in) (i.e. excl.), £1-55.

**DOOR BELL YODELLER**  
(PE Apr. 71). S/c's, Rs, Cs, Pots, PCB (3 in x 3 1/2 in), £5-10. T/fmr £1-30. L/spkr £1-30.

**GEMINI STEREO AMPLIFIER**  
(PE Nov. 70/Mar. 71) Stereo Sets and PCB's. Pre-amp—S/c's £1-85. Rs, Cs, Pots, Mak.—Sw's—with 1/2W MO Rs, £11-60—with 1/2W CF Rs, £9-35—with 1/2W CF Rs, £8-90. PCB (3 1/2 in x 10 1/2 in) for sets with MO and 1/2W Rs, also holds rotary or slider pots and Mak's Sw's, £2-10. Main Amp—Rs, Cs, Pots, £5-40. PCB (3 1/2 in x 5 in), £1-40. PSU—Rs, Cs, Pot, £3-70. PCB (2 in x 4 in), 75p.

**LOGICAL RADIO CONTROL**  
(PE Apr./Jun. 72)—Details in lists


**GEMINI STEREO TUNER**  
(PE Apr./Jun. 72). Rs, Cs, Pot, £3-80. PCB as publ., £1-50.

**MICROPHONE MIXER**  
(PE Apr. 69). S/c's, Rs, Cs, Pots, £2-90. PCB (3 1/2 in x 4 1/2 in) also holds 6 rotary or 4 slider pots, £1-20.

**POST AND PACKING**  
U.K. 10p per order. EXPORT at cost—please allow for this when ordering and also state whether air or surface postage required.
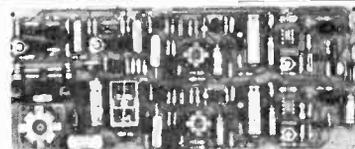
## PHONOSONICS P. C. BOARDS

All PCBs Fibreglass, Drilled, Roller-Tinned. Layout and Circuit Diagrams Free with each PCB. Unless stated "as published". PCBs are designed by Phonosonics. Pots are rotary unless stated as slider.



### HI-FI TAPE LINK

(PE Mar./Apr. 73). S/c's, i.c.'s, Rs, Cs, Relay and pc-base, Pot, Cores and pc-bases, Sw's, Pots, Panel Lamp—Mono, £11-80; Stereo, £18-70. PSU, £2-50. PCB—Main Assy. (3 1/2 in x 9 in) (Stereo) also holds relay and cores, £1-85. PCB—Sub-Assy. (2 1/2 in x 6 1/2 in) (Stereo) holds Sw-assoc. Rs, Cs, Presets and mounts on Sw's, 80p.

**REVERBERATION UNIT**  
(PW Nov./Dec. 72). S/c's, Rs, Cs, Slider Pots, T/fmr, £6-80. PCB (2 in x 1 1/2 in) also holds sliders, £1-20. 9in Spring Unit avail. to order, £3-75.

**VIBRASONIC GUITAR PRE-AMP**  
(PW Sept. 70). Incl. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume. S/c's, Rs, Cs, LDR, Rotary Pots, Lamp, Coupling T/fmr, £7-75. PSU, £2-80. PCB (3 1/2 in x 10 1/2 in) Mk. 2, also holds 7 rotary or slider pots, £2-30.

**ULTRASONIC TRANSMITTER-RECEIVER**  
(PE May 72). S/c's, Rs, Cs, Pot, Relay, Dual PCB (2 in x 5 1/2 in), £3-90. T/fducers avail. to order, £7-30 per pair.

**ALSO**  
PCBs as published (while stocks last) for:  
DIGITAL PSU (PE Aug. 72), 60p  
OSCILLOSCOPE P/A (PE Aug. 72), 40p  
SCORPIO (PE Nov./Dec. 71), 70p  
TRIFFID (PE Feb. 73), 60p

**AND**  
DIGITRONIC (PW Mar. 73). Read-out PCB (1 1/2 in x 3 1/2 in), 60p.

**V.A.T.**  
U.K. Orders only—add 10% to total cost of order.

**TAPE NOISE LIMITER**  
(PE Feb. 72). S/c's, Rs, Cs, Pot, PCB (1 1/2 in x 3 in), £2-20. Reg. PSU and PCB (1 1/2 in x 2 1/2 in), £3-20.

**VERSATILE LIGHT EFFECTS UNIT**  
Single Channel Sound Controlled Light with built-in variable strobe. (PE June 72). S/c's, Rs, Cs, Pots, T/fmrs, Keyswitch, £8-85. PCB (3 1/2 in x 7 1/2 in) Mk. 2, also holds pots, Sw, T/T7 T/fmr, £1-50. SCR's—1A, 50p, 3A, 55p.

**PHOTOPRINT PROCESS CONTROL**  
(PE Jan./Feb. 72). Finds exposures, controls timing, stabs, mains voltage. S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keyswitch, T/fmr, £7-60. PCB (3 1/2 in x 5 1/2 in) also holds pots, Sw, relay, £1-20.

**SOUND SYNTHESIZER (PE Current Series)**  
Details of PCBs and Components in list. Free mailing list service available for further information about PCBs and Sets for this project.

**LIST**  
S.A.E. for free list and with all enquiries please.

PHONOSONICS, DEPT. PE7, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW

MAIL ORDER ONLY


# TRANNIES

**£19.50 ELECTRONIC DIGITAL CLOCK**  
(For complete kit of parts including case.)

I DOCKYARD, STATION ROAD, OLD HARLOW, ESSEX  
Phone Harlow 37739

P/P 10p. Price list S.A.E. (Saturday callers welcome)

ALL PRICES INCLUDE VAT

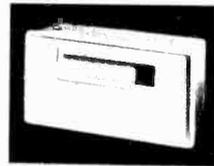

This 4 digit 24 hour clock is available to readers at this special price for 1 month only. Parts would normally cost over £25. Kit of parts includes twelve IC's, indicators, and a smart white plastic case.

## 74 Series TTL

1		25		1		25		1		25		1		25	
SN7400	18p	15p	SN7423	55p	60p	SN7450	16p	15p	SN7489	6.05p	5.85p	SN7400	74p	72p	
SN7401	18p	15p	SN7425	55p	60p	SN7451	18p	15p	SN7490	74p	72p	SN7401	18p	15p	
SN7402	18p	15p	SN7427	49p	48p	SN7453	18p	15p	SN7491	1.10p	1.04p	SN7402	18p	15p	
SN7403	18p	15p	SN7428	77p	72p	SN7454	16p	15p	SN7492	74p	72p	SN7403	18p	15p	
SN7404	18p	15p	SN7430	16p	15p	SN7460	16p	15p	SN7493	74p	72p	SN7404	18p	15p	
SN7405	16p	15p	SN7432	49p	48p	SN7470	33p	29p	SN7494	85p	72p	SN7405	16p	15p	
SN7406	38p	35p	SN7433	94p	82p	SN7472	33p	29p	SN7495	85p	72p	SN7406	38p	35p	
SN7407	38p	35p	SN7437	72p	69p	SN7473	41p	39p	SN7496	85p	72p	SN7407	38p	35p	
SN7408	20p	18p	SN7438	72p	69p	SN7474	41p	39p	SN74100	1.80p	1.75p	SN7408	20p	18p	
SN7409	20p	18p	SN7440	16p	15p	SN7475	50p	47p	SN74104	1.09p	1.06p	SN7409	20p	18p	
SN7410	17p	15p	SN7441	74p	70p	SN7476	44p	43p	SN74105	1.09p	1.06p	SN7410	17p	15p	
SN7411	27p	25p	SN7442	74p	70p	SN7480	73p	70p	SN74107	44p	42p	SN7411	27p	25p	
SN7412	38p	35p	SN7443	1.43p	1.37p	SN7481	1.32p	1.26p	SN74110	81p	59p	SN7412	38p	35p	
SN7413	32p	29p	SN7444	1.43p	1.37p	SN7482	97p	95p	SN74111	1.37p	1.27p	SN7413	32p	29p	
SN7416	47p	43p	SN7445	2.00p	1.92p	SN7403	1.20p	1.15p	SN74118	1.10p	1.05p	SN7416	47p	43p	
SN7417	47p	43p	SN7446	1.07p	1.02p	SN7484	1.10p	1.05p	SN74119	1.47p	1.37p	SN7417	47p	43p	
SN7420	16p	15p	SN7447	1.10p	1.03p	SN7485	3.96p	3.85p	SN74121	44p	41p	SN7420	16p	15p	
SN7422	65p	50p	SN7448	1.10p	1.03p	SN7486	36p	35p	SN74122	1.54p	1.43p	SN7422	65p	50p	

\* Devices may be mixed to qualify for Price Breaks  
\* 100 Plus less 10% off 25 plus break



## Electrolytic Capacitors

4 VOLT		16 VOLT		40 VOLT	
47µF	6½p	15µF	6½p	47µF	6½p
100µF	6½p	33µF	6½p	100µF	9p
220µF	6½p	68µF	6½p	150µF	10p
330µF	6½p	150µF	8p	220µF	11p
1000µF	13p	220µF	9p	470µF	19p
4700µF	29p	680µF	17p	680µF	25p
		1000µF	17p	1000µF	25p
		1500µF	25p	2200µF	44p
		2000µF	43p		
6.3 VOLT		25 VOLT		63 VOLT	
33µF	6½p	10µF	6½p	1µF	6½p
68µF	6½p	22µF	6½p	2.2µF	6½p
150µF	6½p	47µF	6½p	4.7µF	6½p
470µF	11p	100µF	8p	6.8µF	6½p
680µF	13p	150µF	8p	10µF	6½p
1500µF	18p	220µF	8p	22µF	6½p
2200µF	18p	330µF	8p	4.7µF	6½p
3300µF	26p	470µF	10p	6.8µF	6½p
		680µF	13p	10µF	6½p
		1000µF	17p	22µF	6½p
		1500µF	20p	330µF	22p
		2200µF	24p	470µF	26p
				1000µF	44p

## BARGAIN PACKS

- Unmarked Packs
  - Pack of 25 1N4148 55p
  - Pack of 10 BC108 BC107 (Plastic can) 55p
  - Pack of 10 Plastic BC109 55p
  - Pack of 10 BC169 (unmarked) but tested 55p
  - 2N2646 (unmarked) 33p each
  - Pack of 10 2N2926G 55p unbranded but tested

## Linear Integrated Circuits

301 DIL	50p	723c DIL	89p
301 TO99	55p	723c TO99	95p
301 8 PIN DIL	46p	741c 8 PIN DIL	38p
301A DIL	69p	741c 14 PIN DIL	38p
301A TO99	69p	741c TO99	41p
301A 8 PIN DIL	68p	747c DIL	46p
307 DIL	69p	748c DIL	38p
307 TO99	69p	748c TO99	41p
307 8 PIN DIL	69p	748c DIL	1.27p
308 TO99	8.45p	1437 DIL	1.27p
308A TO99	6.40p	1458 TO99	1.27p
709c DIL	75p	3046 DIL	82p
709c TO99	31p	7503 DIL	1.27p



## Transistors

AC107 16p	BC138 36p	BF260 29p	OC44 14p	Diodes & Rectifiers
AC126 14p	BC142 33p	BF259 18p	OC45 14p	
AC127 13p	BC143 33p	BF390 18p	OC70 23p	
AC128 13p	BC144 26p	BF394 37p	OC71 14p	
AC142K 22p	BC145 25p	BFX84 22p	OC72 14p	
AC141K 20p	BC147 9p	BFX85 35p	OC81 14p	1N914 8p
AC176 15p	BC148 9p	BFX86 22p	OC83 22p	1N916 8p
AC187 13p	BC149 9p	BFX87 28p	OC84 28p	1N4148 8p
AC187K 20p	BC153 16p	BFX88 26p	TIP29A 53p	1S44 10p
AC188 13p	BC154 17p	BFY30 21p	TIP30A 84p	1N4007 22p
AC188K 20p	BC157 15p	BFY41 17p	TIP31A 64p	18113 17p
ACY17 24p	BC158 12p	BFY52 17p	TIP32A 73p	18120 17p
ACY18 21p	BC159 14p	BFY64 89p	TIP33 41-05	18121 15p
ACY19 25p	BC167 13p	BFY90 72p	TIP34A	18130 9p
ACY20 22p	BC168 11p	BSX20 18p	21.54	18132 18p
ACY21 23p	BC169 11p	C407 22p	TIP35A	18920 8p
ACY22 15p	BC177 15p	C426 33p	22.53	18922 13p
ACY39 68p	BC179 15p	C428 31p	TIP36A	18940 6p
AD140 40p	BC182L 9p	C450 17p	23.19	AA119 11p
AD142 44p	BC183L 9p	MP8111 36p	TIP41A 79p	AA129 11p
AD143 39p	BC184L 9p	MP8112 42p	TIP42A 91p	AA213 11p
AD149 38p	BC186 33p	MP8113 35p	2N706 13p	AA215 14p
AD150 60p	BC212L 11p	MP8121 33p	2N930 23p	AA217 14p
AD161 29p	BC215L 11p	MP8122 35p	2N131 25p	BA100 10p
AD162 29p	BC216L 11p	MP8123 50p	2N132 28p	BA102 25p
AD M/W 50p	BC258 9p	NKT211 28p	2N1613 22p	BA115 8p
AF114 14p	BC259 9p	NKT212 28p	2N1711 26p	BA144 14p
AF115 14p	BC267 14p	NKT214 25p	2N2904 40p	BA145 22p
AF116 14p	BC268 16p	NKT217 55p	2N2904A	BA154 14p
AF117 14p	BC300 11p	NKT261 29p	44p	BA157 14p
AF118 9p	BC301 32p	NKT271 29p	2N2905 48p	BA116 14p
AF124 27p	BC302 30p	NKT274 20p	2N2924 10p	BA178 19p
AF139 39p	BC303 50p	NKT276 25p	2N2926 10p	BAY31 9p
AF239 41p	BC304 40p	NKT403 71p	2N3053 26p	BY100 19p
AL100 7p	BCY70 17p	NKT405 83p	2N3054 55p	BY126 16p
AL102 66p	BCY71 37p	NKY603	2N3055 52p	BY127 14p
AL103 55p	BCY72 7p	NKT613	2N3405 44p	BYX10 24p
ASY26 31p	BD123 69p	NKT613G	2N3663 57p	BYX10 24p
ASY27 40p	BD130 50p	NKT613G	33p	OA5 19p
AU103 99p	BD131 68p	NKT674 26p	2N3703 9p	OA9 11p
AU110 11.60p	BD132 90p	NKT677G	2N3704 9p	OA10 24p
AU111 77p	BD135 42p	24p	2N3705 9p	OA47 9p
BC107 9p	BD136 50p	NKT713 32p	2N3706 9p	OA70 8p
BC108 9p	BD141 11.7p	NKT713	2N3707 9p	OA73 11p
BC109 9p	BD142 50p	OC19 55p	2N3708 9p	OA79 8p
BC113 15p	BD159 33p	OC20 55p	2N3709 9p	OA81 9p
BC116 16p	BD173 28p	OC23 33p	2N3710 9p	OA85 11p
BC125 16p	BD177 28p	OC25 28p	2N3711 9p	OA90 8p
BC126 23p	BD178 28p	OC28 33p	2N3794 17p	OA91 8p
BC132 18p	BF179 35p	OC29 33p	2N3819 28p	OA92 8p
BC134 16p	BF194 15p	OC35 38p	40361 50p	OA91 8p
BC135 16p	BF196 17p	OC36 38p	40362 50p	OA95 8p
BC137 16p	BF244 27p	OC41 14p	40636 50p	OA200 11p

## MULLARD POLYESTER'S

**MULLARD POLYESTER CAPACITORS C280 SERIES**  
250V P.C. mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 0.22µF, 0.33µF, 0.47µF, 0.68µF, 1.0µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 33µF, 47µF, 68µF, 100µF, 150µF, 220µF, 330µF, 470µF, 680µF, 1000µF, 1500µF, 2200µF, 3300µF, 4700µF, 6800µF, 10000µF, 15000µF, 22000µF, 33000µF, 47000µF, 68000µF, 100000µF, 150000µF, 220000µF, 330000µF, 470000µF, 680000µF, 1000000µF, 1500000µF, 2200000µF, 3300000µF, 4700000µF, 6800000µF, 10000000µF, 15000000µF, 22000000µF, 33000000µF, 47000000µF, 68000000µF, 100000000µF, 150000000µF, 220000000µF, 330000000µF, 470000000µF, 680000000µF, 1000000000µF, 1500000000µF, 2200000000µF, 3300000000µF, 4700000000µF, 6800000000µF, 10000000000µF, 15000000000µF, 22000000000µF, 33000000000µF, 47000000000µF, 68000000000µF, 100000000000µF, 150000000000µF, 220000000000µF, 330000000000µF, 470000000000µF, 680000000000µF, 1000000000000µF, 1500000000000µF, 2200000000000µF, 3300000000000µF, 4700000000000µF, 6800000000000µF, 10000000000000µF, 15000000000000µF, 22000000000000µF, 33000000000000µF, 47000000000000µF, 68000000000000µF, 100000000000000µF, 150000000000000µF, 220000000000000µF, 330000000000000µF, 470000000000000µF, 680000000000000µF, 1000000000000000µF, 1500000000000000µF, 2200000000000000µF, 3300000000000000µF, 4700000000000000µF, 6800000000000000µF, 10000000000000000µF, 15000000000000000µF, 22000000000000000µF, 33000000000000000µF, 47000000000000000µF, 68000000000000000µF, 100000000000000000µF, 150000000000000000µF, 220000000000000000µF, 330000000000000000µF, 470000000000000000µF, 680000000000000000µF, 1000000000000000000µF, 1500000000000000000µF, 2200000000000000000µF, 3300000000000000000µF, 4700000000000000000µF, 6800000000000000000µF, 10000000000000000000µF, 15000000000000000000µF, 22000000000000000000µF, 33000000000000000000µF, 47000000000000000000µF, 68000000000000000000µF, 100000000000000000000µF, 150000000000000000000µF, 220000000000000000000µF, 330000000000000000000µF, 470000000000000000000µF,

# NST

## VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS  
SPECIAL EXPRESS MAIL ORDER SERVICE  
Express postage 1p per transistor, over ten post free  
INTEGRATED CIRCUITS 5p + 1p each added

	sp	sp	sp	sp	sp
1N21	0-17	AFZ12	1-00	BYZ10	0-85
1N23	0-20	ASY26	0-25	BYZ11	0-32
1N85	0-88	ASY27	0-32	BYZ12	0-30
1N283	0-88	ASY28	0-25	BYZ13	0-25
1N266	0-50	ASY29	0-30	BYZ15	1-00
1N645	0-25	ASY36	0-25	BYZ16	0-62
1N725A	0-20	ASY60	0-17	BYZ88CV3	0-15
1N914	0-07	ASY61	0-40	BYZ88CV3	0-15
1N4007	0-20	ASY63	0-20	C111	0-65
18113	0-15	ASY55	0-20	CR8105	0-25
18130	0-18	ASY28	0-25	CR8103	0-45
18131	0-13	ASY86	0-38	CS4B	2-50
18202	0-23	ASZ21	0-42	CS10B	3-18
2G371	0-22	ASZ23	0-75	CS10B	3-18
2G381	0-25	AT Y10	0-98	DD000	0-15
2G414	0-30	AL101	1-50	DD003	0-18
2G417	0-22	BC107	0-10	DD006	0-18
2N404	0-22	BC108	0-10	DD007	0-40
2N697	0-15	BC109	0-10	DD008	0-38
2N698	0-40	BC113	0-15	GD3	0-88
2N706	0-10	BC115	0-20	GD4	0-05
2N706A	0-12	BC116	0-25	GD5	0-88
2N708	0-15	BC116A	0-30	GD8	0-25
2N709	0-63	BC118	0-25	GD12	0-05
2N1091	0-83	BC121	0-20	GET102	0-80
2N1131	0-20	BC123	0-25	CR8103	0-45
2N1132	0-25	BC125	0-68	GET113	0-20
2N1302	0-18	BC126	0-65	GET114	0-15
2N1303	0-18	BC140	0-55	GET115	0-45
2N1304	0-22	BC147	0-15	GET116	0-50
2N1306	0-22	BC148	0-13	GET120	0-25
2N1308	0-25	BC149	0-18	GET872	0-30
2N1307	0-25	BC109	0-10	GET875	0-25
2N1308	0-25	BC158	0-12	GET880	0-37
2N2147	0-75	BC160	0-63	GET881	0-25
2N2148	0-80	BC169	0-13	GET882	0-25
2N2160	0-60	BCY31	0-85	GET885	0-25
2N2218	0-20	BCY32	0-55	GEX44	0-08
2N2219	0-20	BCY33	0-25	GEX491	0-15
2N2369A	0-15	BCY33	0-25	GEX491	0-15
2N2444	1-99	BCY34	0-30	GJ3M	0-25
2N2613	0-28	BCY38	0-40	GJ4M	0-88
2N2646	0-45	BCY39	1-00	GJ5M	0-25
2N2904	0-20	BCY40	0-60	GJ7M	0-87
2N2904A	0-25	BCY42	0-25	HG1005	0-50
2N2906	0-20	BCY70	0-15	H8100A	0-20
2N2907	0-23	BCY71	0-20	MAT100	0-25
2N2924	0-23	BCZ10	0-35	MAT101	0-80
2N2925	0-15	BCZ11	0-50	MAT120	0-25
2N2926	0-10	BD121	0-65	MAT121	0-30
2N3054	0-80	BD123	0-80	MJE620	0-87
2N3055	0-75	BD124	0-75	MJE2955	1-87
2N3702	0-10	BF111	1-82	HS3055	0-20
2N3705	0-10	BF115	0-25	NKT128	0-36
2N3706	0-23	BF117	0-50	NKT129	0-30
2N3707	0-12	BF167	0-25	NKT211	0-25
2N3709	0-10	BF173	0-25	NKT213	0-25
2N3710	0-10	BF181	0-85	NKT214	0-18
2N3711	0-10	BF184	0-20	NKT215	0-37
2N3819	0-85	BF185	0-20	NKT217	0-35
2N6027	0-53	BF194	0-17	NKT218	1-13
2N6088	0-33	BF195	0-15	NKT219	0-33
28901	0-50	BF196	0-15	NKT222	0-20
28904	0-75	BF197	0-15	NKT224	0-22
28901	0-37	BF801	0-88	NKT221	0-24
28902	0-28	BF806	0-28	NKT221	0-24
AA129	0-20	BFX12	0-20	NKT272	0-25
AAZ12	0-80	BFX13	0-25	NKT273	0-18
AAZ13	0-12	BFX29	0-25	NKT274	0-20
AC107	0-37	BFX30	0-25	NKT275	0-25
AC126	0-20	BFX35	0-98	NKT277	0-20
AC127	0-25	BFX36	0-85	NKT278	0-25
AC128	0-20	BFX84	0-25	NKT301	0-40
AC187	0-25	BFX85	0-30	NKT304	0-75
AC188	0-25	BFX86	0-25	NKT403	0-75
ACY17	0-30	BFX87	0-25	NKT404	0-55
ACY18	0-25	BFX88	0-20	NKT678	0-30
ACY19	0-25	BFY10	1-00	NKT713	0-25
ACY20	0-20	BFY11	1-25	NKT717	0-38
ACY21	0-20	BFY17	0-25	NKT777	0-38
ACY22	0-10	BFY18	0-25	OT8B	0-88
ACY27	0-25	BFY19	0-25	SA40	0-25
ACY28	0-17	BFY24	0-45	SFT308	0-88
ACY39	0-80	BFY44	1-00	ST722	0-33
ACY40	0-15	BFY50	0-25	ST723	0-68
ACY41	0-15	BFY61	0-20	ST723	0-68
ACY44	0-25	BFY62	0-92	ST723	0-68
AD140	0-50	BFY63	0-17	ST723	0-68
AD149	0-50	BFY64	0-42	ST723	0-68
AD161	0-37	BFY90	0-85	ST723	0-68
AD162	0-37	BSX27	0-60	ST723	0-68
AF106	0-80	BSX60	0-98	ST723	0-68
AF114	0-25	BSX76	0-15	ST723	0-68
AF115	0-25	BSY26	0-18	ST723	0-68
AF116	0-25	BSY27	0-17	ST723	0-68
AF117	0-25	BSY61	0-60	ST723	0-68
AF118	0-82	BSY95A	0-12	ST723	0-68
AF119	0-20	BSY95	0-12	ST723	0-68
AF124	0-25	BT102/600	0-85	ST723	0-68
AF126	0-20	BTY42	0-75	ST723	0-68
AF127	0-17	BTY79/100R	0-42	ST723	0-68
AF139	0-80	BTY79/400R	0-75	ST723	0-68
AF178	0-85	BTY79/400R	0-75	ST723	0-68
AF180	0-59	BY100	0-15	ST723	0-68
AF181	0-42	BY126	0-15	ST723	0-68
AF186	0-40	BY127	0-17	ST723	0-68
AFY19	1-18	BY182	0-85	ST723	0-68
AFZ11	0-60	BY213	0-25	ST723	0-68

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.  
Valves, Tubes and Transistors - Closed Sat. 1 p.m.-3 p.m.  
Terms C.W.O. only Tel. 01-677 2424-7  
All orders subject to V.A.T. at 10% rate. This must be added to the total order including postage.

## VARIGAP STEREO TUNER F.M.φ

(ACTUAL BEECHING UNITS)

MODULES LPI185/86 £9 pair  
REGULATOR MFC4060 £0.78 each  
DECODER MC1310P £3.15 each  
(100's in stock)  
PRINTED CIRCUIT BOARD—GLASS FIBRE £1.87 each  
READY BUILT AND TESTED BOARDS £23 each  
COMPLETED TUNERS IN TEAK CABINETS £34 each  
(BRUSH ALU. FRONT PANEL with 6 BUTTONS, MAINS + 5 STATIONS)

(ADD 25p POSTAGE TO ABOVE)

### SUPER SPECIAL OFFER WHILE STOCKS LAST

## 25 W. R.M.S. DISCO AMPLIFIERS ONLY £10 each !!

WHAT A LINE UP:

0.2% DISTORTION, 25W RMS INTO 8Ω, FLAT RESPONSE, S/C PROTECTION! AND USING 40361/40362/MJ481/MJ491 TRANSISTORS.

WE ARE MAD! EACH ONE TESTED AND WORKING AND YET ONLY £10 Ready to use.

The catch is you need a 100K log VOLUME CONTROL ONLY!

## B & B ELECTRONICS

64 MANNERS ROAD, BALDERTON, NEWARK NOTTS. Telephone: NEWARK 6895

ALL PRICES INCLUDE V.A.T.



## BAKER 12" MAJOR £9.90

30-14,500 cps. Double cone woofer and tweeter combination. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

## MAJOR MODULE KIT £12.50

30-17,000 cps. response. Tweeter, crossover and baffle as illustrated.

### BAKER LOUSPEAKERS

Regent 12 in. 15W £8.80 Superb 12 in. 20W £16.50  
Major 12 in. 20W £9.90 Group 25 12 in. 25W £8.80  
Deluxe 12 in. 15W £11.00 Group 35 12 in. 35W £9.80

ALL PRICES  
INCLUDE V.A.T.

BAKER LOUSPEAKER CO., BENSHAM MANOR PASSAGE  
THORNTON HEATH, SURREY Tel. 01-684 1665  
LOUSPEAKERS CATALOGUE AND ENCLOSURE PLAN 5p


## NSS

### DO-IT-YOURSELF ELECTRICAL EQUIPMENT

TRANSFORMERS • RECTIFIERS  
INDICATOR LAMPS • RELAYS  
CONTACTS • KEY SWITCHES  
BURGLAR ALARM EQUIPMENT  
SOLDERING IRONS • COMPONENT CASES  
HOLE CUTTERS • TERMINAL BOXES  
plus numerous other electrical components.

Send 10p for full price list and illustrated catalogue to:

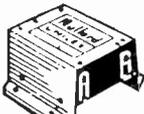NORTHERN SECURITY SUPPLIES (DEPT. PE)  
104 KENT CRESCENT, KENT ROAD, PUDSEY, YORKSHIRE



### MULLARD AMP

Sensational! Once in a lifetime offer! Unrepeatable once stocks are cleared. The amplifier is made by Mullard. Carries maker's Guarantee. In neat case. May be used for Mono or Stereo. Music or speech. Works off dry battery, car batt. or mains power pack. FREE—all who purchase we send copy of Mullard booklet DIY stereo. £1.60



### DRILL CONTROLLER NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.65. Made up model also available. £2.48.

### MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, 4 January 73. All electronic parts £2.20 post paid.



### TIME SWITCH


Smith's mains driven clock with 15 amp switch, also notes showing how you can wake up with music playing kettle boiling or come home to a warm house, warn off burglars, keep pets warm, halve your heating bill. etc. £1.95.

### 1 CHIP RADIO

Ferranti's latest device ZN414—gives results better than superb. Supplies complete with technical notes and circuits. £1.38 each. 10 for £11.11.
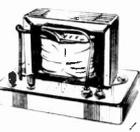
### HI-Q TUNER COMPONENTS

For experimenting with the ZN414. KIT NO. 1. Plessey Miniature Tuning Condenser with built in LW switch and 3" ferrit slab and litz wound MW coil. 72p. KIT NO. 2. Air spaced tuning condenser 6" ferrite rod litz wound MW and LW coils. 94p. KIT NO. 3. Air spaced TC with slow motion drive 8" ferrite rod, with litz wound LW and MW coils. £1.10. KIT NO. 4. Permeability tuner with fast and slow motion drive and LW loading coils. 45p.



### 12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000mF smoothing. Price £2.20, plus 20p post and packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange plug on leads. Silicon rectifiers and smoothing by 3,000mF. Price £6.33 plus 65p post.

### MICRO SWITCH

5 amp changeover contacts. 11p each. 10 for 99p. 15 amp Model 15p Changeover 15p each.



### MAINS RELAY BARGAIN

Special this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V A.C. Good British Make. Unused. Size approx. 1 1/2" x 1". Open construction. Single pole 28p each 10 for £2.48. Treble pole 39p each 10 for £3.57.

### MAINS OPERATED SOLENOIDS

Model 772—small but powerful 1 1/2" pull—approx. size 1 1/2" x 1 1/2" x 1 1/2". 66p. Model 400/1—1" pull. Size 2 1/2" x 2" x 1 1/2". 83p. Model TT10—1 1/2" pull. Size 3 1/2" x 2 1/2" x 2". £1.98 plus 20p post and insurance.

### MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6V, 9V, 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1.10 plus 20p postage.


### DESK TELEPHONES

EX G.P.O. Black standard model with dialing dial but no internal bell. Supplied with connection diagram 94p each—post etc. 40p for single then 65p per pair. Ditto, with bell but without dialing dial 94p each plus 40p post for single then 65p per pair.


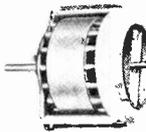
### PAPST MOTORS

Est. 1/40th h.p. Made for 110-120V working, but two of these work ideally together off our standard 240V mains. A really beautiful motor, extremely quiet running and reversible. £1.45 each. Postage one 23p, two 33p. 230V model £3.30.



### 10 AMP DIMMER CONTROL

For the control of lighting on stage or in a studio or for control of portable equipment in workshops, etc. This has two 13 amp socket outlets each is controlled by a 5 amp solid state regulator. The overall length is 17in., width 3 1/2in. and depth 1 1/2in. In the end is fitted a master On/Off switch indicator, lamp and fuse. Price £8.25.

### STANDARD WAFFER SWITCHES

No. of Poles	Standard size 1 1/2" wafer—silver-plated—5 amp contact, standard 1/4" spindle 2" long—with locking washer and nut.										
	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way		
1 pole	44p	44p	44p	44p	44p	44p	44p	44p	44p	44p	44p
2 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p	44p	44p
3 poles	44p	44p	44p	44p	44p	44p	44p	44p	44p	44p	44p
4 poles	44p	44p	44p	77p	77p	77p	77p	77p	1.32	1.32	1.32
5 poles	44p	44p	77p	77p	1.04	1.04	1.04	1.04	1.60	1.60	1.60
6 poles	44p	77p	77p	77p	1.04	1.04	1.04	1.04	1.67	1.67	1.67
7 poles	77p	77p	77p	1.04	1.32	1.32	1.32	1.32	2.15	2.15	2.15
8 poles	77p	77p	77p	1.04	1.32	1.32	1.32	1.32	2.42	2.42	2.42
9 poles	77p	77p	1.04	1.32	1.32	1.32	1.32	1.32	2.70	2.70	2.70
10 poles	77p	1.04	1.04	1.32	1.60	1.60	1.60	1.60	3.00	3.00	3.00
11 poles	77p	1.04	1.04	1.32	1.87	1.87	1.87	1.87	3.25	3.25	3.25
12 poles	77p	1.04	1.04	1.32	2.15	2.15	2.15	2.15	3.52	3.52	3.52

### CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for an improved and even more efficient version (Practical Wireless, June). Price £6.55 plus 20p post. When ordering please state whether for positive or negative systems. De-luxe model including printed circuit board, etc. £7.95.



### MULLARD UNILEX

This D.I.Y. Stereo Amplifier is still available complete at £7.00 for the four Mullard Modules, or Modules can be bought separately as follows:—4 watt amplifier module (2 required) Mullard Ref. No. E.P. 9000—£1.60. Pre amp module Mullard Ref. No. E.P. 9001—£1.98 each. Power Module—Mullard Ref. No. E.P. 9002—£2.53 each. In addition and made to Mullard specification we offer:—Standard Control Unit with escutcheon and knobs—£3.30. Knobs—Set of 4—50p. Special offer the complete Unilex with control panel at Pre VAT price—£10.00 post paid.



### ZPM MODULATION MOTOR

Could also be used to open ventilators, doors, valve, damper, etc. Particularly suitable for remote control. Made by Satchwell. Essentially a reversible geared motor fitted with internal limit switches to stop it at the end of its travel. Size approx. 6in. x 6in. x 5 1/2in. and weighing approx. 10lb. This is extremely powerful and would lift a heavy door or open a long line of ventilators. To operate this motor you put the 50 cycle supply through a changeover switch. For instance a thermostat with changeover contacts could automatically regulate the temperature in a growing house, chicken hatchery, etc. An indicator on the motor graduated 0-10 shows the state of open or close. Also internally fitted is a variable resistor, wires from this to a volt meter would give a remote indication of the open or close position. A very expensive motor if both direct from Satchwell, our price complete with step down Transformer is £16.50.

### CENTRIFUGAL FAN

Mains operated, turbo blower type. Pressed steel housing contains motor and impeller. Motor is 1/10th h.p. giving considerable air flow but virtually no noise. Approx. dimensions 10 1/2in. wide x 1 1/2in. dia. outlet into trunking 10 1/2" x 4in. £6.55 plus 1p post and insurance.



### THIS MONTH'S SNIP


#### TAPE PLAYBACK UNITS

Mains operated. Made by Reditone the famous "music in background people". These are complete units ready to work and we understand that they are in good going order. We have not tested them but would exchange any that do not work properly. These have a superior motor driven fly wheel to control the tape through the capstan and also an even quality useful valve amplifier with EL84 output. In a steel case with carrying handle. Two models offered, good as new £6.50 and somewhat used at £3.50, 75p carriage up to 200 miles then 50p per 100 miles extra. 3-hour cassettes, already recorded light music £1.10 each extra.


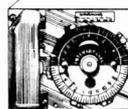
### 24-HOUR TIME SWITCH

Made by Smiths, these are A.C. mains operated. NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5A changeover contacts with switch circuit on or off during these periods. £2.75 post and ins. 25p. Additional time contacts 55p pair.



### MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 500mW power output 72p. Model 1172 750mW power output 94p. Model EP9000 4 watt power output £1.60. EP9001 twin channel or stereo pre amp. £1.99. 10% discount if 10 or more ordered.



## NEW ITEMS THIS MONTH

### MINI SEALED RELAY

American made. Our Ref: REL A1. Measures only 3" wide x 1/2" thick and 3/4" high and it's a double change-over, we don't know the contact rating but estimate this at 3/5 amps. The coil resistance is 600 ohms and 9-12 volt will close it. Ideal for models and miniaturised equipment. It's a plug in relay but we supply complete with base. Price 28p including base.

### SUB-MINIATURE MICROSWITCH

Made by Burgess, their Ref V476—our Ref MS.A1. These measure only 1/2" x 1/2" x 1/2" thick—have change-over contacts and tag connection. Price 16p each or 10 for £1.44.

### 3-CORE MAINS FLEX

Metric size. 5mm which is approx. equivalent to the old 14/36 rating. Suitable therefore for mower or similar portable tools. Cores are colour coded to the new European standard. Brown—live... Blue—neutral... Yellow/Green—earth... Grey... P.V.C. covered overall. 100mm coils £5, 50m coils £3 and 25m coils £1.75. Post 40p on 100m, 25p for 50m coils and 20p for 25m coils.

### PANIC SWITCHES

Tough enough to be foot switches and elegant enough to be panel switches. Bakelite construction with white push rod. Price 40p less quantity discounts. Switch is rated 250V—2 amp.

### 20 WATT CAMPING LIGHT

Also makes good car emergency light. This uses a standard 2 foot 20 watt tube and operates from a 12V car battery drawing approx. 1A. This gives illumination per amp/hour of battery life far in excess to filament lamps and in fact to the miniature 8-13 watt camping lights often offered. Complete unit ready to operate, in strong white enamelled metal frame. These would normally retail at £6 are unused but slightly soiled and we offer these at £3.50 plus 40p post and packing.

### 6 MAINS TRANSFORMERS

Our Ref: MTM1 27 volt at 8 amp. Upright mounting fully shrouded—flying leads—fully tagged primary. Price £3.30.

Our Ref: MTM2 12V at 1 amp. Upright mounting with fixing lugs, tag connection. 240V primary—12V 1 amp secondary. Price 82p.

Our Ref: MTM3 6.3V 2 amp upright mounting with fixing lugs, tag connections. 240V primary—6.3V 2 amp secondary. Price 77p.

Our Ref: MTM4 18V—4 amp with thermal cut-out, upright mounting with fixing lugs—tag connections. Primary 240V—secondary 18V at 4 amp. Price 88p.

Mains Isolation MTM5 350 watts earth shielded—flex leads—upright mounting lugs for fixing. Price £4.40 each.

### 6 VOLT RELAYS

Our Ref: REL M1. Removable clear plastic enclosed two screw fixing. Have a 6 volt D.C. operated coil but two changeover contacts, each rated to make and break 240V A.C. at 15 amps. Price 66p each.

### P.O. TYPE 3000 RELAY

Our Ref: REL M2—100 ohms coil and 2 pair normally open heavy duty contacts. Price 75p each.

### PHOTO-MULTIPLIER TUBE

American R.C.A. type No. 4555. These tubes have a gain of a million or more. Regular Price—over £15. We have a limited quantity and offer these at £4.50.

### TANGENTIAL AIR MOVING UNITS

Work as extractors or blowers especially quiet running, perfectly balanced, plastic impeller—self oiling bearings. Induction motor—outlet size 12" x 2" approx. Ideal to fit in cooker hood. £2.20 plus 30p post and ins.


### 6 DIGIT COUNTER

Resettable. 440 ohm coil up to 25 impulses per second. Ex-equipment—but guaranteed perfect. £2.20 each.


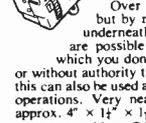
### COMBINATION SWITCH

This comprises of 12 miniature changeover micro switches. Joined in banks of 3 and mounted on frame with four digital numbered thumb wheels and a removable lever for locking the thumb wheel—the thumb wheel operates 3 banks. Over 4,000 combinations are possible but by re-wiring the switch connections underneath then thousands more variations are possible. If you are making equipment which you don't want switched on accidentally or without authority then this is a switch to consider—this can also be used as a coding switch for many other operations. Very neat and compact and measuring approx. 4" x 1 1/2" x 1 1/2" deep. Priced at £3.43.



### PUSH BUTTON SWITCH

Type 14 D.M.G. A very fine switch made by Honeywell. The switch is intended for mounting on panel through oblong hole. No screws required for fixing it's sprung clips secure it quite firmly. The operating button is approx. 1" dia. round and dished for ease of operation. Has 2 sets of 10 amp changeover contacts. Spring loaded, returns to normal when pressure is released. Ideal for instrument or quality gear. Price 50p each, 10 for £4.50, 100 for £40.

TERMS:—10% discount if ten of an item ordered, send postal, where quoted other terms, post free if order for these over £6.00 otherwise add 20p.

## J. BULL (ELECTRICAL) LTD.

(Dept. P.E.), 7 Park Street, Croydon CRO 1YD  
Callers to: 102/3 Tamworth Road, CROYDON.

# Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

## SITUATIONS VACANT



### Brunel Technical College Bristol

Ashley Down, Bristol BS7 9BU

Department of Marine and Aero-Electronics

#### Marine Radio and Electronic Officers

The Department offers the following Courses:  
 (a) For prospective Radio Officers in the Merchant Navy a Course of 2½ years leading to the MPT General Certificate in Radiocommunications and the DoTI Radar Maintenance Certificate. Commences September and January.  
 (b) A 3-year Course for prospective Radio Officers leading to the Marine Radio and Radar Technicians Certificate (CGLI 292) and incorporating the MPT and DoTI Certificates.  
 (c) For qualified Marine Radio or Electronic Officers the MNTB Additional Certificate in Marine Electronics, in two modules of 3 months each.  
 (d) Short advanced technique Courses for serving Radio Officers.  
 (e) MPT R/T Licences.

#### Licensed Aircraft Radio Engineers

The Department provides a 2-year Full-time Course leading to a career in Civil Aviation. The Course is fully approved by the CAA so that successful students may obtain a full Category R Licence at the end of the Course if over 21 years of age. The Department's aircraft, workshops and laboratories cover:  
 12.1 Airborne Communication Systems.  
 12.2 Airborne Navigation Systems.  
 12.3 Airborne Pulse and FM Systems.  
 Courses commence each September.  
 Courses are also provided for Aeronautical Engineering Certificates (AEC 7-12), Aeronautical Engineering Technicians Certificate (CGLI 258), Aeronautical R/T Licences, and Category X Compass Licences.

For further information apply to the Head of Department of Marine and Aero-Electronics, Brunel Technical College, Ashley Down, Bristol BS7 9BU. Telephone (0272) 41241.

## WANTED

**TOP PRICES PAID  
AND TRANSISTORS**  
 Popular T.V. and Radio types  
**KENSINGTON SUPPLIES (B)**  
 367 Kensington Street  
 Bradford 8, Yorks.

## SERVICE SHEETS

**SERVICE SHEETS**, Radio, TV, etc. 8,000 models. Catalogue 15p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**SERVICE SHEETS** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

## MUSICAL INSTRUMENTS

**HALO**—the new gear as supplied to Hawkwind, Solid Gold Cadillac. Tone generators £12-11, ring modulators £12-77, fuzz box £11-34, Wah-wah £11-81, treble boost £8-81. Contact: HALO, Estuary House, Exmouth, Devon.

## EDUCATIONAL

**ENGINEERS.** Get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Buildings, etc., FREE book from: BIET (Dept. ZC BPE 29), Aldermaston Court, Reading, RG7 4PF. Accredited by CACC.

## A SUCCESSFUL CAREER IN RADIO

Get the success you deserve—take an ICS home study course. Pass C&G M.P.T. exams FIRST TIME! Free books. Low cost Personal tuition. Send TODAY for FREE Guide on Radio, TV, Electronics, Electrical Engineering.

Name \_\_\_\_\_

Address \_\_\_\_\_

**ICS**

Dept. 7305  
 Stewarls Road,  
 London SW8 4UJ

## FOR SALE

**SEEN MY CAT?** 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

**TV LINE OUT-PUT TRANSFORMERS**  
 Tidman Mail Order Ltd., 236 Sandycroft  
 Road, Richmond, Surrey TW9 2EQ  
 01-948 3702

**CATALOGUE NO. 18**, Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

## MEN! £50 p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500 + p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators  
 Training Centre  
 M88, Oxford House  
 9-15 Oxford Street, W.1  
 Telephone 01-734 2874

127 The Piazza, Dept. M88  
 Piccadilly Plaza, Manchester 1  
 Telephone 061-236 2935

## LADDERS

**LADDERS**, 241ft \$9-80, carr. 80p. Please add 10% V.A.T. to total order. Leaflet. HOME SALES LADDER CENTRE (PEB2), Haldane, Halesfield (1) North, Telford, Salop. Tel. 0952-580644.

## Electro-Medical Service Department requires

## ENGINEERS

for testing and servicing electronic apparatus. Applicants should be aged 20-30, and should be of O.N.C. standard.

Apply in first instance in writing to:

**SIEREX LIMITED**  
 Electro-Medical Department  
 Heron House, Wembley Hill Road  
 Wembley, Middlesex HA9 8BZ

## BOOKS AND PUBLICATIONS

**THOSE 1,000 BANBURY UFO'S!** Details our prediction. List 10p and S.A.E. Prediction Chart 50p. Flight Pattern 42p. R & E, Highlands, Needham, Suffolk.

**DIGITAL COMPUTER** Logic and Electronics. A four volume Self-instructional course, £2-99 post free. Money back assurance. CAMBRIDGE LEARNING, 8a Rose Crescent, Cambridge.

### FIBRE OPTICS

Flexible Light Pipe for conveying light to inaccessible positions. Fibroflex Type 1, Glass 1.14mm effective dia. PVC sheathed, 44p per metre. (VAT inc.), P. & P. 10p. Any quantity.

**Polariser Sheet** up to 1 sq. ft. max. size. 161p per sq. in. (VAT inc.), P. & P. up to 6 in. square 10p; over 6 in. square 30p

- ★ Cut down glare
- ★ See those nixie tubes
- ★ Cross them for light control
- ★ Make your own strain gauge for plastics and glass

**Circuit Board Etching Kits.** Full instructions. £1-37½ (VAT inc.), P. & P. 14p

**Photographic CDS Light Cells**—used (with part of original circuit free), 33p (VAT inc.), Post free

All items are strictly C.W.O.

From: **ARVIN SERVICE COMPANY**  
12 CAMBRIDGE ROAD  
ST. ALBANS

### MORSE MADE EASY!!

**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tone. 18 W.P.M. in 4 weeks guaranteed.

Beginner's Section only £3.30, complete course £4.50 (Overseas £1 extra) details only, 4p stamp. 01-860 2898 G3HSC (Box 10), 45 GREEN LANE, PURLEY, SURREY

**METER REPAIRS.** Ammeters, Voltmeters, Multi-Range meters, etc., also Linear scale Transistorised Ohmmeters for sale. **METER REPAIRS**, 39 Chesholm Rd., London N16 0DS.

**U.K. DISTRIBUTOR "W2AU"** baluns, antenna hardware, toroid cores also electro-voice microphones plus more. Large S.A.E. T.M.P. (ELECTRONIC SUPPLIES), (Dept. PE), 3 Bryn Clyd, Leeswood, Mold, Flintshire, CH7 4RU.

**LARGE QUANTITY** test equipment, receivers, transceivers, meters, variacs, P.S.U.S. Over 1,000 items for immediate disposal. S.A.E. plus 25p. Refund on purchase over £2. F.J.C., Colne Mill, Alvington, Lydney, Gloucester.

**FOR SALE SPRAGUE HYPASS CAPACITORS.** Axle fitting. Complete with bracket. 1,400 0.5mF 600V d.c. 20 amps, 1,100 0.1mF 250V a.c. 40 amps. SPERRY UNIVAC, Grange Road, Houston Industrial Estate, Livingston, West Lothian.

**FOR SALE TECH. TE200 R.F.** Signal generator £8. Tech. to 0.3 oscilloscope £30. Radio/TV servicing volumes 1969-1971 £20. All in new condition. Phone: Pagham 2187.

**PRACTICAL ELECTRONICS.** Volumes 1-5. Offers. CHASE, 20 Greenside Road, West Croydon, Surrey.

### RECEIVERS AND COMPONENTS

#### 5—N-Channel FETs 3819E—£1

Full specification devices complete with circuit details for building voltmeter, timer, ohmmeter, etc.  
Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

**REDHAWK SALES LTD.**  
45 Station Road, Gerrards Cross, Bucks.  
MAIL ORDER ONLY

**COMPONENTS GALORE.** Pack of 500 mixed components manufacturers surplus plus once used. Pack includes resistors, capacitors, transistors, diodes, I.C., gang, pots, etc. Tremendous value. Send £1 plus 10p P. & P. C.W.O. to CALEDONIAN COMPONENTS, Posterton Firs, Strathore Road, Thornton, Fife.

## PRECISION

### POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.  
0.47µF: ±5% 80p; ±2% 40p; ±1% 80p  
1.0µF: ±5% 40p; ±2% 50p; ±1% 80p  
2.2µF: ±5% 50p; ±2% 80p; ±1% 75p  
4.7µF: ±5% 70p; ±2% 90p; ±1% £1-15  
6.8µF: ±5% 95p; ±2% £1-15; ±1% £1-50  
10µF: ±5% £1-10; ±2% £1-40; ±1% £1-80  
15µF: ±5% £1-60; ±2% £2-10; ±1% £2-70

**TANTALUM BEAD CAPACITORS.** Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (78 capacitors) £5.

**NEW I—TRANSISTORS.** BC107, BC108, BC109. All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178 at 35p each or 3 for 95p.

**POPULAR DIODES.** IN914, 7p each; 8 for 50p; 18 for £1. IN916, 9p each; 6 for 50p; 14 for £1. 1544, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

**NEW LOW PRICE—400 mW Zeners.** Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5mA. All new and marked. Price 9p each; 6 for 50p; 14 for £1. Special offer 6 off each voltage (66 zeners) £4-25.

**RESISTORS.** Carbon film 5%, ¼W at 40°C, 14W at 70°C. Range from 2.2Ω to 2.2MΩ in E12 series; i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decads. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

**400V A.C. CAPACITORS.** 0.1µF, size 1½in X ½in, 25p; 0.25µF, size 1½in X ½in, 30p; 0.47 and 0.5µF, size 1½in X ½in, 35p; 1.0µF, size 2in X ½in, 45p; 2.0µF, size 2in X ½in 75p.

**SILICON PLASTIC RECTIFIERS 1S—** Brand new wire-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each and 4 for 50p.

5p post and packing on all orders below £5.

Please add 10% VAT to all orders

**MARCO TRADING**

Dept. EB, The Maltings, Station Road  
Wem, Shropshire

### DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 69p per doz.; £4-12 per 100; £30-25 per 1,000; £275 per 10,000. All carriage paid.

G.W.M. RADIO LTD.

40/42 Portland Road, Worthing, Sussex 0903 34897

**COMPUTER PANELS.** 9in X 7½in long lead trans. and comp., E4, 8 trans., 27p (10p); E45, 16 trans., 44p (10p); E47, 10 trans., 39p (10p).  
**PANELS** with epoxy and TO18 silicon trans. 4 for 66p (12p).

**MC METERS.** 2in or 3in, three assorted £1-15 (25p).  
**MAINS STEPPING SWITCH.** 22 way with reset 86p (15p).

**RESETTABLE COUNTER.** 5 figure, 18/22V, works on 12V, £2-20 (15p).

**SILICON DIODES.** 650V 1¼A, 10 on tag board, 35p (5p). New 800V 2A, 6 for 25p (5p).

**UNIT WITH 4 x BFY51,** 4 silicon diodes, 4 zeners, caps and resistors, 45p (8p).

**COPPER CLAD PAX PANELS.** 5½in X 5½in, 6 for 83p (10p).

**MIXED POLYSTYRENE'S, MICA CAPS.,** 100 for 50p.

**71b ASSORTED COMPONENTS.** £1-60.

**21b ASSORTED COMPUTER PANELS.** £1-60.

S.A.E. (9in X 4in) for list of computer panels, etc.

### J.W.B. RADIO

75 Hayfield Road, Salford 6, Lancs.  
Postage in brackets Mail order only

**BRAND NEW COMPONENTS** by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10 mF, 4p; 22, 47, 47p (50V, 5p); 100, 51p (50V, 7p); 220, 6p (50V, 9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02, 2p; 0.04, 0.05, 3p; 0.068, 0.1, 3½p. Polystyrene 63V E12 series 10—1,000pF, 2p; 1,200—10,000pF, 3p. Miniature highstab resistors, 5%, E12 series—Carbon Film ¼W, 1Ω—10MΩ (10% over 1 MΩ). Metal Film ¼W, 10Ω—2.2MΩ and 1W, 27Ω—10MΩ all 1p each. Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

## Trampus electronics

Add 10% VAT (to) to all prices. All brand new, no rejects. Money Back Warranty.  
**5V DIGITAL INDICATOR.** 0-9DP socket and Buffer £1-46.  
**LED TYPE 1** 0-9DP DIL £2-25 each; 6 X £2-19 each, 4 digit type £11.  
**LIGHT EMITTING DIODES.** All with data and panel clip. TTL 209 ¼ dia. 20p. Red ¼" dia. type 33p. Green 75p. INFRARED beam LED £1-10.  
**GAS detector** £1-69. Ultrasonic transducer £2.  
**DALO PCB resist marking pen** 60p. (Copper board 12" X 6" SERIP 40p. Pat. chd. PAK 19p.)  
**INTEGRATED CIRCUITS:** with data if required.  
**IC LITE SWITCH:** Photo amp/trig/trigger 40mA/11-20V relay or TTL 87p. Dil relay £1-10.

## IC digital clock

MOS/LSI type, 28 pin, 4 or 6 digit, 12/24hr. Chip with socket £13; PCB £1-69; KIT £21-49. DVM voltmeter £12. Data 30p. 3W AF amp £1-24.

741 D18 pin 28p; 709 19p. D10 28p; 748 28p; mono 710 33p. 555 TIMER/mono/astable osc. clock 88p. REGULATOR: 1¼A 5 to 20V £1-49; 723 57p. RECEIVER ZN414 £1-10. Mini Rf Kit £1-89. 1310 stereo decoder for tuner £2-90. KIT £3-45.

**NEW LOW PRICES**

GATES 7400 1/2/3/4/5/10/20/30/40/50, etc., 14p each. 7413 27p; 7441 73p; 7447 £1-09; 7470, 7472 28p; 7473, 7474 38p; 7475 60p; 7476 32p; 7490 59p; 7492 87p; 7480 69p; 7483 £1-10; 7486 37p; 7493 73p; 7484 85p; 7495 88p; 7496 89p; 74121 45p; 74141 89p; 74190/91/92/93/96 £2-99. DIL Plugs/IC case 10mm high 16 pin 35p.

**DIL SOCKETS:** low or high profile 8/14/16 pin 13p. **SEMICONDUCTORS:**

2N3055 40p; BC107 8p; BC108 8p; BC109 8p; BC147/8/9 10p; BC167/8/9 13p; BC177/8/9 15p; BC182/94 10p; BC212/5/4 11p; BCY70/2 12p; BD131/5 55p; BFY50/1/2/3 13p; TI843 11T 24p; 2N706 11p; 2N369 12p; 2N2926/3 8p; 2N2646 49p; 2N3053 17p; 2N3055 40p; 2N3614 55p; 2N3702/3/4/5/6/7/8/9/10/11 11p 8p each.

2N3819 27p; 2N3823 28p; SCR 400V: 1A 23p; 4A 55p. TRANSFORMER: 1A 6 and 12V £1. CAPACITORS: 18vdc 220pF 0.1µF 4p. 25V electrolytic 10, 50, 100µF 5p; 1,000µF 15p. PRESETS 5p each. RESISTORS ¼W 5%, 11p each. CARBON POTS 12p each. Dual 40p. Switch +12p. All Din Pins 13p; sockets 9p; Vero RRP.

## FLUORESCENT LIGHTS 12VOLT £2.79

13" 8 watt fully built with diffuser. TRIO and CODAR communications and Hi-Fi retailer. ELECTRONIC ORGANS from £67. FW ELECTRONIC CAR IGNITION KIT £6-87. VAP: YOU MUST ADD 20% to all prices. FREE CAT. S.A.E. Data sheets 8p. P. & P. 8p. C.W.O. P.O. BOX 29, BRACKNELL, BERKS.

## R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Veroboard 6: 5 0:1 Matrix, 2 for £1. 4: 4:1 0: Matrix, 4 for £1. 12: 3:1 0:15 Matrix, 75p each.

Mullard A.M. Module. I.F. Strip, LP1166, £1-10 inc. P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2½ X 2 X 1½ in with circuit, £1-37½ inc. P.P.

Crouzet Gearing Motors, 10-30-60 r.p.m. New, £1-54 inc. P.P.

UHF TV Tuners. Transistorised, £1-65 inc. P.P.

3BP1 with Base and Screen, £2-75 inc. P.P. VCR138 CRT. New, boxed, £3-30 inc. P.P.

Brand New Panel Vu Meters, 4½ X 3½ in calibrated, £3-30 inc. P.P.

Transformers. 7.5V + 7.5V ¼A, 66p inc. P.P. 18-0-18V, 200mA + 24V, 77p inc. P.P. 9-0-9V, 100mA, 69p inc. P.P. 12-0-12V, 100mA 69p P.P. 20V, 1A 88p inc. P.P.

Transformers. 52-0-52V, 1A + 22-0-22V, 200mA, £2-20 inc. P.P.

P.C. Board. 5/5, 5½ X 5½in, 10 for 70p inc. P.P.

Panel with 5-200 PIV 1A SCRs + 14 OA200 diodes plus components 70p inc. P.P.

2,500 mfd 100VW capacitor 4½ X 1½". New, 85p inc. P.P.

Panel Meter 50µA. Brand new, 4½ X 3½". £3-30.

**SPECIAL RESISTOR KIT.** ¼W 5% Carbon Film. 10 each E12 value, 22Ω to 2.2M. Total 610 for £3. P. & P. 8p. NEK ELECTRONICS. 28 Carnegie Road, St. Albans, Herts.

**SPECIAL INTRODUCTORY OFFER OF BRAND NEW & MARKED COMPONENTS ALL PRICES INCLUDE V.A.T.**  
**TRANSISTORS:** BC107B, BC108A/B/C, BC109B/Callat 8p; BFY50/51 14p; 2N3055 38p. **DIODES:** IN4148 43p; IN914 41p. **CARBON FILM RESISTORS:** 1/2W 5%, 1/2p each, 30p/50 any mix (220-2.2M) £12.  
**UNMARKED BARGAIN PAKS:** These transistors have been properly tested and are guaranteed to have the specified life spreads. Pak of 5, Plastic BC108A hfe 125-240, 25p; Pak of 5, Plastic BC109B hfe 240-500, 25p; Pak of 5, Plastic BC179A hfe 125-240, 25p; Pak of 4, BFY51 20p; Pak of 4, 2N697 20p. **DIODES:** Pak of 5 OA200 20p; Pak of 12 IN4148 20p.  
 C.W.O. P. & P. 10p, on orders below £4. Overseas at cost. S.A.E. for lists. Mail Order only. Money back if not satisfied.  
**ADFNIC (DEPT. PE), 18 YEW LANE ASHLEY, NEW MILTON, HANTS BH25 3BA**

**BRAND NEW FULL SPEC. DEVICES SATISFACTION OR YOUR MONEY BACK**  
 U.K. ORDERS—Add 10% VAT to Total  
**MICROCIRCUITS:** 709 24p; 710 36p; 723 31p; 741 27p; 748 37p; FET Op. Amp. £1.62.  
**SOLDERCON IC Pin Sockets:** 0.5p per pin.  
**SOCKETS:** 14 pin DIL HI or LO 12p each.  
**RECTIFIERS:** 1A 50V 31p; 100V 4p; 200V 41p; 400V 5p; 800V 6p; 1,000V 7p.  
**ZENERS (BZ Y88):** 2.7V to 33V 8p each.  
**DIODES:** IN914 4p; OA90 6p; IN4148 4p.  
**LED PANEL LAMP** with Bush and Data 28p.  
**DALC PC RESIST PEN** 68p.  
**SUB-MIN. VERTICAL PRESET POTS** (50mV) 100ohms to 220K 4p each.  
**TRANSISTORS:** 2N2926 Brown 6p; 2N3053 15p; 2N3055 35p; 2N3702 10p; 2N3704 10p; 2N3819 26p; BC107A 8p; BC108B 8p; BC109B 8p; BC109C 8p; BC170 15p; BFY50/51/52 15p; AC126/7/8 12p; OC44/45/71/72 12p.  
 Above prices on 30th May. Check our list.  
**JEF ELECTRONICS (P.E.8)**  
 York House, 12 York Drive, Grappenhall, Warrington WA4 2EJ. Mail Order Only. C.W.O. P. & P. at cost. 10p min. List free.

**TOROIDAL MAINS TRANSFORMERS**  
 Slimline and compact, with very low stray hum field, suitable for audio amplifiers up to 60 Watts/channel, etc.  
 Type T1—primary 0-110-120-220-230-240V, 40/60Hz. Secondary 0-45V at 150VA max. Electrostatic screen. Size—only 1 1/2" high x 4 1/2" diameter. Weight 3 1/2lb. Mail order only.  
 Price—only £5.70, post free in U.K.  
 Other types available—send S.A.E.  
**Amplification and Recording**  
 36 Bermuda Terrace, Cambridge

**RADIO & TELEVISION AERIAL BOOSTERS £2.95**, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7.50. Carr. £1.50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.

**TUNBRIDGE WELLS.** Components from TELESERVICE, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

**555 TIMER I.C.** only 90p each inc. VAT. P. & P. 5p. 2 or more post free. C.W.O. to: (HARNWOOD) (D.P.E. 3), Castle Hill, Holmeswood, Sheffield, S18 5WQ. Mail order only.

**BEDFORD ELECTRONICS**  
 2 Grove Place · Bedford  
 Bedford 51961  
**YOUR LOCAL COMPONENTS SUPPLIER**  
 FREE CATALOGUE ON REQUEST

**MISCELLANEOUS**

**CLEARING LABORATORY**, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, MC relays, components, etc. Lower Beeding 236.

**AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS**

because this Ministry approved transmitter/receiver kit does not use R.F.  
 Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.  
**GET YOURS! SEND £5.80 (inc. VAT) NOW S.A.E. for details) MAIL ORDER ONLY TO: 'BOFFIN PROJECTS' DEPT. KE2010 4 CUNLIFE ROAD STONELEIGH, EWELL, SURREY**

A Perfect toast every time. Automatic pop-up toaster has adjustable time control to vary the colour and crispness just the way you like it. Chromium plated with black plastic sides. 220/240V, 800. Comes with 6ft of flex and 3 months' guarantee. Size Bin x 4 1/2in x 7in high.  
 E341 £7.20 Toaster  
 11 Compact go-anywhere cassette tape recorder can be operated by battery or a.c. mains, 220/240V. Automatic recording level. Piano-type keys control play, rewind, wind, stop and record. Sockets for remote control and microphone. Complete with four U2 batteries. Wood grain finish. Size 9in x 5in x 2 1/2in. Weight approx. 6lb.  
 E365 £15.30 Tape recorder

**ACME ELECTRIC CO. (FINSBURY) LTD.**  
 74 Gt. Eastern Street  
 London E.C.2  
 Tel. 01-739 6486-8

**HARDWARE**—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

**NEW FROM ELBON**  
**L.E.D.'s** (Red Emitting) Ideally suited for panel indicators  
 Price only: 33p each or £2.50 for 10  
**Light SENSITIVE SWITCHES**  
 Two types available giving wide operating voltages:  
 LITE-IC2 11V-20V working—£1 each—£8.50 for 10  
 LITE-IC3 20V-30V working—£1 each—£8.50 for 10  
 Applications include: Relay, Triac or Logic Drive automatic light switching and door control, beam break detection—burglar alarm, batch counting and code reading  
**BARGAIN PACK!**  
 2 LITE-IC2, 2 LITE-IC3 and 5 LED's all for £5.00  
 ALL PRICES INCLUDE VAT, PACKING AND CARRIAGE  
 Please send C.W.O. to:  
 LITE-IC, ELBON, SUMMERFIELD,  
 THE CRESCENT, WEST WITTERING, SUSSEX

**Build the Mullard C.C.T.V. Camera**  
 Kits are now available with comprehensive construction manual (also available separately at 76p)  
**SEND 5" 7" S.A.E. FOR DETAILS TO: CROFTON ELECTRONICS 15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG**

**CONSTRUCTION AIDS.** Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

**THERMOCOUPLES**

Acramet and Acrasped thermocouples, from IC are:-  
 Extremely accurate for fluid, gas or metal temperature measurement.  
 Individually calibrated and carry a certificate plus a one year guarantee.  
 Available with immersion or contact, non-earthed, multiples, boss or plug.  
 Details available on request.  
**International Combustion Limited, Sinfen Lane, Derby DE2 9GJ**

**ENAMELLED COPPER WIRE**

S.W.G.	1/b Reel	1/b Reel
10-14	£1.15	65p
15-19	£1.15	65p
20-24	£1.18	68p
25-29	£1.25	75p
30-34	£1.30	80p
35-40	£1.40	85p

Please add 10% to all above prices to cover VAT  
 The above prices cover P. & P. in U.K. Supplied by  
**INDUSTRIAL SUPPLIES**  
 102 Parrswood Rd., Withington, Manchester 20  
 Telephone No. 061-224 3553

**standard german plugs & sockets**  
 With EARTHING CONTACTS

<b>Plug 131</b> 34p inc VAT With cable side entry		<b>Socket 200</b> £1.10 inc VAT Twin socket outlet to fit wall box	
<b>Socket 210</b> 61p inc VAT For bench mounting		<b>Socket 230</b> 55p inc VAT For chassis mounting	

Postage & packing—1 item 3p each additional item 2p over 10 post free TRADE ENQUIRIES WELCOME  
**michael wheeler ltd 01-388 0575**  
 18-19 WARREN STREET LONDON W1P 5DB

**P.E. SYNTHESISER KNOB KIT**  
 Complete kit as Feb. issue £3.91 post free  
 43 knobs, 7 calibrated discs.  
**DE LUXE KIT** as above but £5.89 post free  
 calibrated for programming.  
 Inclusive postage and V.A.T.  
**RE-AN PRODUCTS LTD.**  
 Burnham Road, Dartford, Kent  
 Tel.: Dartford 20785

**PSYCHEDELIC MINI-STROBE**  
 A very FASCINATING, POCKET-SIZED STROBE-LIGHT that is SELF-CONTAINED and you can take anywhere. Go to parties and really BRAIN-FREEZE them with DAZZLING PSYCHEDELIC EFFECTS and STOP-MOTION FLASHES. Boffin's new MINI-STROBE kit constitutes a fully solid-state electronic device which is COMPLETE with FUTURISTIC case/reflector unit, printed-circuit board, electronics, and source-lamp—the only extra is a battery which you can buy locally. The whole thing can be easily built in a few hours.  
 A veritable FLICKERING FASCINATOR! Adjustable flash-rate.  
**GET ONE (or two) NOW and BEGIN STEALING THE THUNDER at DISCOS and PARTIES with your own POCKET-LIGHTNING!**  
 SEND £2.10 (inc. VAT) for YOUR MINI-STROBE. MAIL ORDER ONLY  
**To: Boffin Projects**  
 4 Cunliffe Rd., Stoneleigh, Ewell, Surrey

## ELECTRONICS FANATICS

whether beginner or advanced — we offer a range of over 35 SUPER projects.

Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's SOMETHING GOT TO BE LOADED TO INTEREST YOU in the science-fiction-world of BOFFIN.

GET YOUR CATALOGUE — SEND JUST 15p NOW!

MAIL ORDER ONLY

**TO: BOFFIN PROJECTS**  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL  
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

**GLA88 FIBRE P.C. BOARD**—large supplies available.  $\frac{1}{8}$  in single sided one ounce copper, 2p per 3 sq in (under 1ft); 75p per sq ft (over 1ft).  $\frac{1}{4}$  in double sided one ounce copper, 1p per sq in (under 1ft); 21 per sq ft (over 1ft). Please add 10p per sq ft postage and packing. We can cut to your size at 1p per cut. **SOLID STATE LIGHTING**, The Pirs, Smallworth Lane, Garboldisham, Diss, Norfolk.

**ALUMINIUM SHEET** to individual sizes or in standard packs, 3p stamp for details. **RAMAR CONSTRUCTOR SERVICES**, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

**BURGLAR AND FIRE ALARMS**. Complete Master Control Module now available from our own panels. Ideal for all Alarm/switching circuits with data sheet, etc. **£6-85**. Complete Alarm kits **£49-50**. Magnetic Switches, Sensors, Panels, available. **CANTLE ALARMS**, P.O. Box W06, Windsor, Berks.

## ZIGGY'S 2001 ELECTRONICS Co. Ltd.



**SPECS. MULTIMETER U4324**. Sensitivity 20,000 OPV DC. Usually high current ranges. 3 amp a.c./d.c. Voltages AC3 to 900V d.c. 0.6 to 1200V. Resistance 500 ohms—20-200-2,000k $\Omega$ . Transmission level -10 to +12dB. This high quality instrument has diode protection. Complete with test leads, batteries, etc. **PRICE £8 plus 25p post, etc.**

**MULTIMETER 4313**. Similar to above but special features include 3 amp current range and instrument is housed in metal case with carrying handle. (Illustrated leaflet sent on request.) **ONLY £9.50 plus 25p P. & P.**  
**SANWA JP-5D**. Diode protected. D.C. and A.C. volts 0-500V. D.C. current 0-500 mA. Res. 0-1M  $\Omega$ . **£5-95. P. & P. 20p.**

**EAGLE LT700 TRANS.** LT44 TRANS. Our price 32p each, postage 6p.  
**P. U. HEAD SHELLS AND SLIDES**.  
**GARRARD C2 (SP25 Mk III, etc.)** 45p. M7 (SP25 Mk II and earlier models) 41p.  
**BSR McDonald (310, 510, 610, MP60)** 45p. Postage 6p per shell.

**ARE YOU HUMBLE ABOUT YOUR RUMBLE?** SP25 drive wheels, 65p plus 5p P. & P. MP60 drive wheels, 65p plus 5p P. & P.  
**SUBMINIATURE TOGGLE SWITCHES**—very useful, very small. S/P. 25p. DP/ST. 33p. Postage 5p each, over 10, post free.

**SUBMINIATURE MAINS TRANSFORMERS**. Eagle MT6, 6-0-6, 100 M/A. 80p, postage 10p. MT12, 12-0-12, 50 M/A. 80p, postage 10p.

**MINIATURE TYPE MAINS TRANSFORMERS**. Eagle Type MT280, 6-0-6 280 M/A. £1-20; MT150, 12-0-12, 150M/A. £1-20, MT100, 24-0-24, 100 M/A. £1-20, R/S types, 13V, 0.5 amp. C. Tapped, £1-06, 16.3V, 0.3 amp. C.T., £1-06. Post 15p on min. size.  
**DIAMOND STYLI FOR SONOTONE 9TAHC, LP/78, 65p plus 5p P. & P. LP/LP, 95p plus 5p P. & P.**

**FOR SPEEDY DELIVERY OF THESE MINT CONDITION COMPONENTS PLEASE SEND C.W.O. TO ZIGGY'S 2001 ELECTRONICS CO. LTD., DEPT. P.E.3, 34 MABLEY STREET, LONDON, E.9.**

N.B.—Please add 10% for VAT—Sorry.

## LOW COST LEDs

**MLED 500** in standard TO92 package for P.C. mounting. MV54 is T<sub>1</sub> size, 2 mm, miniature. Both provide visible red light from 1-65V, 20mA. 150() resistors available for 5V d.c. (TTL) operation.

MLED 500	£1-10	£2-20	£3-74	£6-60	£2-65
MV54	£1-10	£2-09	£3-52	£6-05	£2-10
150()	—	—	11p	22p	44p

**MARE'S TAILS**: Spray of several thousand glass fibres, ready to use as part of decorative displays. £11 each including P. & P. and VAT.

**POLARISERS** for light control, glare reduction, modulators, stress analysis, S/N enhancement for displays.

**HN32 Linear Polariser**, for Kerr cells, etc.  
**HRCP7 Red Circular Polariser**, for LED displays.  
**HNCP37 Neutral Circular Polariser**, for c.r.t.s, meters, etc.  
Send 9 x 6in S.A.E. for full details of the above plus our full range of Fibre Optics.

## FIBRE OPTIC SUPPLIERS

P.O. Box 702 LONDON W10 6SL

## SINGLE CHANNEL SOUND-TO-LIGHT CONVERTER



**WITH LIGHT DIMMER**  
Max. Load 2kW at 250V a.c.

Price includes ready built and tested module, edge connector/mounting bracket, dimmer potentiometer, audio sensitivity potentiometer, full connecting data. Price £7-90 inc. VAT + 20p P. & P.  
**EXTRA FACILITIES**. Push-button for Manual Pulsing. 25p extra. Photocell for turning on the lights as the ambient light decreases. 75p extra.

## THREE CHANNEL FILTER UNIT

When used with three single channel modules this unit filters the sound into bass, middle and top frequencies enabling three coloured light displays to be shown. Independent sensitivity controls on each channel. Ready built and tested.

Price £3-40 inc. VAT + 10p P. & P.

## OIL WHEEL PROJECTOR



Build your own using our **MULTI-COLOURED OIL WHEEL AND MOTOR KIT**. Suitable for mounting on virtually all Slide Projectors.

Kit contains:

- \* 6in dia. or 4in dia. OIL WHEEL (please state size required when ordering).
- \* Suitable Miniature mains motor.
- \* Full instructions.
- For Professional Discotheque use or home enjoyment. Price £7-15 inc. VAT + P. & P.

## ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

- Pack No.**
- 1 500 Carbon resistors, 1, 1/2, 1, 2W.
  - 2 100 Electrolytic Condensers.
  - 3 250 Ceramic, Polystyrene, Silver Mica, etc. Condensers.
  - 4 250 Polyester, Polycarbonate, Paper, etc. Condensers.
  - 5 25 Potentiometers, assorted.
  - 6 250 High-stab. 1%, 2%, 5% resistors.
  - 7 50 Assorted Tagstrips.
  - 8 1lb wt. Assorted Nuts, bolts, washers, spacers, etc.
  - 9 25 Assorted switches, rotary, lever, micro, toggle, etc.
  - 10 50 Preset Potentiometers.

**ALL COMPONENTS NEW AND UNUSED**  
£1 + 25p P. & P. per pack £5 for 5 packs post free.

## G.T. ELECTRONICS

267 Acton Lane, London W4 5DG  
01-994 6275

## 4-STATION INTERCOM



£7-99

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 44p.

## MAINS INTERCOM (new model)

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £18-40. P. & P. 60p extra.

## INTERCOM/BABY ALARM



£3-99

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft connecting wire. Complete with battery. P. & P. 30p.

## Transistor TELEPHONE AMPLIFIER



£3-46

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 24p. Full price refunded if not satisfied in 7 days.

**WEST LONDON DIRECT SUPPLIES (PE/7)**  
169 KENSINGTON HIGH STREET, LONDON, W.8

## NEW EDITION TV ENGINEERS' POCKET BOOK

P. J. McGoldrick Price £2-65

**THE RADIO AMATEUR'S HANDBOOK 1973** by A.R.R.L. Price £2-95.

**1-2-3-4 SERVICING CASSETTES** by F. H. Belt. Price £2-30.

**110 THYRISTOR PROJECTS USING SCRs AND TRIACS** by R. M. Marston. Price £1-50.

**VIDEO TAPE PRODUCTION AND COMMUNICATION TECHNIQUES** by J. L. Efrein. Price £1-40.

**INTEGRATED CIRCUIT POCKET BOOK** by R. G. Hibberd. Price £2-60.

**AUDIO SYSTEMS HANDBOOK** by N. H. Crowhurst. Price £1-35.

**BEGINNER'S GUIDE TO PRACTICAL ELECTRONICS** by R. H. Warring. Price £1-40.

**SIMPLE TRANSISTOR PROJECTS FOR HOBBYISTS AND STUDENTS** by L. Steckler. Price £1-35.

**PRINCIPLES OF TRANSISTOR CIRCUITS** by S. W. Amos. Price £1-65.

**NEW IC FET PRINCIPLES AND PROJECTS** by K. W. Sessions. Price £1-20.

**GE TRANSISTOR MANUAL**. Price £1-20. \*ALL PRICES INCLUDE POSTAGE\*

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET  
LONDON W2 1NP

Phone 01-723 4185  
Closed Saturday 1 p.m.

# BUILD A CHORDING PROFESSIONAL SYNTHESISER



The Synthesiser shown above is the Dewtron "Apollo" A.1, which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts.

**VCO-2 STABLE, PRECISION V/C OSCILLATOR** gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control, £22 each or £25 each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. £15. OFT-1 chording module £7.50. Modules (except VCO-1) guaranteed two years.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading group. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I. Approved by the Association of Musical Instrument Industries. Send 15p for full catalogue of our famous musical effects.

## D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)

**PROFESSIONAL MODULES  
CASH SAVINGS**

by buying modules and parts in bulk!  
All modules are available separately:  
Ring Modulator RM2, £8. Voltage-controlled Oscillator VCO1, £10.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £12. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £9. etc., etc. ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £4.50. REVERB Module and spring unit £15. V.A.T. 10% extra. V.A.T. paid orders over £75.

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND

C.W.O. Please. P. & P. please add 10p to orders under £2  
MAIL ORDER, CALLERS SATURDAYS ONLY

### SEMICONDUCTORS

TRANSISTORS				DIODES				LINEAR IC's					
AC125	12p	BC147	12p	OC70	10p	OA85	7p	709C	8 pin	12p	709C	14 pin	32p
AC126	12p	BC148	12p	OC71	10p	OA90	5p	741C	8 pin	36p	741C	8 pin	36p
AC127	12p	BC149	12p	OC72	10p	OA91	5p	741C	14 pin	36p	741C	14 pin	36p
AC128	12p	BD131	49p	2N2218A	13p	OA200	8p	723C	14 pin	80p	723C	14 pin	80p
AC187	12p	BD132	49p	2N2220	10p	OA202	8p						
AC188	12p	BF194	15p	2N2221	10p	IN914	5p						
AD161	30p	BF195	15p	2N2483	10p	IN4001	6p						
AD162	30p	BFY50	22p	2N2484	10p	IN4004	7p						
AF114	12p	BFY51	22p	2N2926R	9p	IN4007	8p						
AF115	12p	OC26	40p	2N2926O	9p	IN4148	5p						
AF116	12p	OC28	40p	2N2926V	9p	BYZ10	20p						
AF117	12p	OC35	40p	2N2926G	10p	BYZ13	16p						
BC107	9p	OC42	10p	2N3014	10p	W01 BRIDGE	400mW						
BC108	9p	OC44	10p	2N3055	55p	RECTIFIER	30V.						
BC109	9p	OC45	10p			1A. Price 30p							

### THYRISTOR

200V 4A 60p

### VEROBOARD

21 x 33in	20p	0.15	18p
21 x 5in	24p	22p	22p
33 x 33in	24p	22p	22p
33 x 5in	27p	30p	30p
21 x 17in	75p	60p	60p
34 x 17in	97p	84p	84p
5 x 17in	128p		
21 x 17in	128p		
33 x 17in	128p		
5 x 17in	128p		
Pkr. 50 pins	20p		
Spot face cutter	42p		
Pin insertion tool	52p		

### JACK PLUGS AND SOCKETS

Standard Screened, 12p	2.5mm Screened, 8p
Stereo Screened, 30p	3.5mm Screened, 10p
Standard Socket, 12p	2.5mm Socket, 7p
Stereo Screened, 15p	3.5mm Socket, 7p

### DIN PLUGS & SOCKETS

Pin: 2, 3, 4, 5 (180° or 240°)  
Plugs, 12p. Socket 8p.

### PHONO PLUGS AND SOCKETS

PLUGS assorted colours 5p.  
Socket: Single 5p  
Double 7p  
Triple 10p

### COMPACT CASSETTES

C60 40p; C90 55p;  
C120 75p.

### SWITCHES

TOGGLE SPST 18p  
DPDT 22p  
SLIDE DP IA 10p  
ROTARY Wafer 12p  
12 Way 25p

### D.C. POWER SUPPLY

Current: 500mA.  
O/P Voltage: 3, 4.5, 6, 7.5, 9, 12.  
PRICE: £3.40 P. & P. 15p.

### STEREO HEADPHONES.

HOSIDEN DH-02V-S.  
8 ohm: Individual vol. control. Soft ear padding. Light wt. PRICE: £2.85. P & P. 15p.

### RESISTORS

Power Watts	Tol.	Range	Miniature wire wound.		PRICE
			Values Available	1-9	
1/4	5%	2.2-3.2M	E12	10-99	100+
1/2	5%	2.2-4.7M	E12	1p	0.7p
1	5%	2.2-10M	E12	1p	0.7p
2	5%	2.2-10M	E12	2p	1.4p
4	10%	1-10 ohm	E12	6p	5p

Do not mix ohmic values to obtain quantity prices. Ignore fraction

### POLYESTER CAPACITORS.

Axial lead type:  
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 2½p; 0.01µF, 0.015µF, 0.022µF, 0.047µF, 3p; 0.068µF, 0.1µF, 0.15µF, 4p; 0.22µF, 7p; 0.33µF, 10p; 0.47µF, 13p.  
160V: 0.1µF, 0.15µF, 4p; 0.22µF, 5p; 0.33, 6p; 0.47µF, 7p; 0.68µF, 10p; 1µF, 13p.  
Radial lead P.C. type:  
250V: 0.01µF, 0.015µF, 0.022µF, 3p; 0.033µF, 0.047µF, 0.068µF, 3½p; 0.1µF, 4p; 0.15µF, 4p; 0.22µF, 0.33µF, 5p; 0.47µF, 7p; 0.68µF, 10p; 1.0µF, 11p.

### ELECTROLYTIC CAPACITORS.

Miniature axial lead type.  
63V: 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 47µF, 68µF, 6p each.  
40V: 100µF, 6p; 150µF 25V, 6p; 25V: 220µF, 11p; 470µF, 13p; 680µF, 20p, 1.000µF, 25p.

### CERAMIC CAPACITORS: 50V d.c. Plaquette body 25mm leads.

Range: 22pF-10,000pF. Price 2p each.

### POTENTIOMETERS: Carbon Track

0.25W, Log and linear values	SLIDER POTENTIOMETERS	
5kΩ - 2MΩ Single Gang	0.25W log and linear values	
5kΩ - 2MΩ s/gang W/switch	10kΩ - 100kΩ Single gang	35p
5kΩ - 2MΩ Dual gang	10kΩ - 100kΩ Dual gang	50p
1K linear single gang	Knobs	10p
Knobs Pointer type		
Small Aluminium		
Black chrome rim		

### PRESET POTENTIOMETERS

0.25W 1kΩ - 1M, Hor. and Vert. 5p  
0.1W Vert. only 3p

## WATFORD ELECTRONICS

35 CARDIFF RD., WATFORD, HERTS, ENGLAND.

Enclose 10p stamps for our comprehensive catalogue.

Name

Address

# FREE!

## Over 150 ways to engineer a better future



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

**HIGHER PAY** **A BETTER JOB**  
**SECURITY**

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course". - Student D.I.B., Yorks.  
 "Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects". - Student J.A.O. Dublin.  
 "My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". - Student C.C.P., Bucks.

#### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to **B.I.E.T. Dept. BPE07 Aldermaston Court, Reading RG7 4PF.**

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.** Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

**CUT OUT THIS COUPON**  
Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL A.M.S.E. (Mech.) Boiler Inspect. & Operation C & G Eng. Crafts C & G Fabricat. Diesel Eng. Eng. Inspection Eng. Metallurgy Inst. Eng. & Tech. Inst. Motor Ind. Mainten. Eng. Mechanical Eng. Sheet Metal Work Welding	<input type="checkbox"/> Man. Prod.—cont. Quality Control Salesmanship Storekeeping Work Study Works Management <b>DRAUGHTSMANSHIP</b> A.M.I.E.D. Design of Elec. Machines Die & Press Tool Design Electrical Draughtsmanship Gen. Draughtsmanship Jig & Tool Des. Tech. Drawing	<input type="checkbox"/> <b>CONSTRUCTIONAL-cont.</b> Building Drawing Inst. Foreman Carpentry & Join. Civil & Municipal Engineering Constructional Engineering Construction Surveyors Institute Clerk of Works Council Eng. Geology Health Eng. Hydraulics Inst. of Builders Inst. Works & Highway Sup. Painting & Dec. Public Hygiene Road Engineer. Structural Eng. Surveying
<input type="checkbox"/> <b>ELECTRICAL &amp; ELECTRONIC</b> A.M.S.E. (Elec.) C & G Elec. Eng. C & G Elec. Inst. C & G Elec. Tech. Computer Elect. Elec. Maths Elec. Science Electronic Eng. Electrical Eng. Install. & Wiring Meters & Measuring Instruments	<input type="checkbox"/> <b>RADIO &amp; TELE-COMMUNICATIONS</b> Colour TV C & G Radio TV/ Electronics C & G Telecomm. Tech. Prac. Rad. Elec. (with kit) Radio Amateurs Exam. Radio Servicing & Repairs Radio & TV Eng. Trans. Course TV Main. & Serv.	<input type="checkbox"/> <b>GENERAL</b> Agricultural Eng. Council of Eng. Inst. Farm Science General Educat. Gen. Plastics Pract. Maths Pract. Slide Rule Pure & Applied Maths Refrigeration Rubber Tech. Sales Engineers Tech. Report Writing Timber Trade University Ent.
<input type="checkbox"/> <b>MANAGEMENT &amp; PRODUCTION</b> Auto. Control Computer Prog. Electronic Data Processing Estimating Foremanship Inst. Cost & Man. Accountants Inst. Marketing Management Metrication Motor Trade Man. Network Plan. Numerical Cont. Operational Research Personnel Man. Planning Eng. Production Eng.	<input type="checkbox"/> <b>AUTO &amp; AERO</b> Aero Eng. A.M.I.M.I. A.E.C. Cert. Auto Engineer. Auto Repair C & G Auto. Eng. Garage Management MAA/IMI Dipl. Motor Vehicle Mechanics <b>CONSTRUCTIONAL</b> A.M.S.E. (Civil) Architecture	<input type="checkbox"/> <b>G.C.E.</b> <b>58 'O' &amp; 'A' LEVELS SUBJECTS</b> Over 10,000 group passes

*Coaching for many major exams including C & G and assistance in O.N.C./H.N.C.*

**POST TODAY FOR A BETTER TOMORROW**

To B.I.E.T., Dept. BPE07 Aldermaston Court, Reading RG7 4PF **ON BPE07**

NAME \_\_\_\_\_  
Block Capitals Please  
ADDRESS \_\_\_\_\_

OTHER SUBJECTS \_\_\_\_\_ AGE \_\_\_\_\_

Accredited by C.A.C.C.

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand: Gordon & Gotch (Asia) Ltd.; South Africa: Central News Agency Ltd.; Rhodesia and Zambia: Kingstons Ltd.; East Africa: Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2.65 (22 E.U.). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or annexed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# Henry's

## YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards—call and see for yourself.

### BUILD THE TEXAN

#### ★ FREE TEAK CASE with complete kits!

**FEATURES:** New slim design with 6 ICs, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardners low field slim line transformer. Fibre glass PC panel. Complete chassis work.


**HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES**—DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

**FACILITIES:** On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector: Mag. P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape head etc. (Parts list Ref. 20 on request). Constructional Details Ref. No. 21. 30p.

**SPECIAL KIT PRICE** **£28.50** P. & P. 45p COMPLETE WITH FREE TEAK CABINET
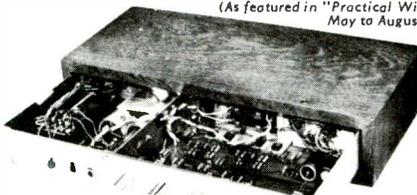
### 20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

(As featured in "Practical Wireless" May to August 1972)



**SLIM DESIGN WITH SILVER TRIM**

Overall chassis size 14½ in. x 6 in. x 2 in. high

Designer approved kits distributed by Henry's!

#### ELECTRONIC KITS

Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

#### IC RECEIVER

ZN414 Radio integrated circuit as featured in Practical Wireless, January, 1973. Article reprint Ref. No. 19. 10p.

#### BATTERY TAPE DECK

Garrard 9V tape deck with heads, etc. As previously advertised. Limited quantity. £9.50. Post 30p.

#### LEARN A LANGUAGE

Recorded Cassettes with step by step phrase books. French, German, Spanish, Italian. £1.36 per course. £5.00 per set of four.

#### DISCO SPOTBANK

As illustrated on the front cover of Practical Wireless, April, 1973. £12.75. P. & P. 35p.

#### HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus demonstrations (for callers) and GUARANTEES.

**FREE** 24-page detailed brochure (Ref. No. 17). ★ You can see the savings ★

#### HIGH QUALITY CASSETTES

The best U.K. low noise tapes but at a special price. "Living Sound" cassettes meet the highest international standard (IEC94A). Fantastic price savings.

	C60	C90	C120
3 for	£1.00	£1.33	£1.62
6 for	£1.80	£2.57	£3.15
10 for	£2.80	£4.20	£5.00

Full guarantee. Post paid. Made by EMI especially for Henry's.

#### ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and new I.C. circuits. PRICE PER PAIR £5.90, Post 10p.

#### MARRIOTT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO  
 "17" High Impedance £2.00  
 "18" Med. Impedance £2.00  
 "36" Med.-Low Imp. £3.50  
 Erase Heads for above 75p  
 "63" 2 track mono — High Impedance £1.75  
 "43" Erase Head for above 75p

#### 7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)  
 XN3, XN13, GN6 0-9 side view with data, 85p.  
 GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.  
 3015F 7 seg. £2 each, £7 per 4 with data.  
 12 and 24 hour clock circuits. Ref. No. 31 15p.

#### MINIATURE AMPLIFIER

5 transistor. 300mW o/p. Fitted volume and sensitivity control 9 volt operated. £1.75 each, p.p. 15p.

#### QUALITY SLIDER CONTROLS

60mm stroke singles and ganged. Complete with knobs. 5kΩ, 10kΩ, 25kΩ, 100kΩ, 250kΩ, 500kΩ, 1 meg. Log and Lin. 40p each, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, Log and Lin. ganged. 60p each.

#### LOW COST HI-FI SPEAKERS



E.M.I. Size 13½in x 8½in and Ceramic Magnet

**TYPE 150** 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.


**TYPE 150TC** Twin cone version £2.75. Post 22p.

**TYPE 450** 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.50. Post 25p.

**TYPE 350** 20 watt with tweeter and crossover, 8 and 15 ohms. £7.50. Post 28p.

POLISHED CABINETS 150, 150TC, 450 £4.60. Post 30p. ASSEMBLED IN POLISHED CABINETS (8 OHM) SERIES 6 (Assembled 150TC) per pair £16.50. Post 70p. SERIES 8 (Assembled 450) per pair £18.95. Post 70p.

#### ML3 MW/LW TUNER TO BUILD

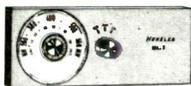

Uses Mullard Module. Slow motion tuning. Built-in

battery. Ferrite aerial. Overall size 7in x 2½in x 3½in. TOTAL COST TO BUILD £4.85. Post 15p. All parts sold separately—Leaflet No. 6.

#### "BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandsread for extra selectivity. 600mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7.98, p.p. 32p (Batt. 22p).

#### CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

**PRICE 55p** Post paid (40p FOR CALLERS)  
**PLUS! FIVE 10p VOUCHERS**

Send to this address—Henry's Radio Ltd. (Dept. PE), 3 Albemarle Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303", see above.

**VAT** All prices are exclusive of 10% VAT which must be added to all orders inc. carr./packing. (Note: Catalogue is not subject to VAT).

#### TEST EQUIPMENT

Just a selection

SE250B Pocket Pencil Signal Injector, £1.90

SE500 Pocket Pencil Signal Tracer, £1.50

THL33D Robust 2 K/Volt, £4.55; with case £4.95

TE15 Grid Dip Meter 440 KHz—280 MHz, £13.45

500 30 K/Volt Multimeter, £9.25; with leather case, £10.50

200H 20K/Volt Multimeter, £4.20; with case £4.95

AF105 50K/V Multimeter, £8.50; with case, £9.50

U4341 AC/DC Multimeter with transistor tester with steel case, £10.50

TE20D RF Generator 120KHz—500MHz, £16.50. Carr. 35p

TE22D Audio Generator 20Hz—200KHz, £17.50. Carr. 35p

CI-5 3in Pulse Scope 10Hz—10MHz, £39.00. Carr. 50p

TE65 Valve Voltmeter 28 ranges, £17.50. Carr. 40p

ALL NOMBREX MODULES IN STOCK



#### BUILD THIS VHF FM TUNER

5 TRANSISTORS 300kc/s BANDWIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. TOTAL £6.97, p.p. 20p. Mk1 Decoder Kit £5.97. Built IC Decoder £6.50. Tuning meter unit £1.75. Mains unit (optional) Model P5900 £2.47. Post 20p. Mains unit for Tuner and/or Decoder P56/12 £3.25. Post 20p.



#### PA-DISCO-LIGHTING

UK's Largest Range—Write phone or call in. Details and demonstrations on request.

DJ30L 3 Channel sound to light unit, 3kW, £29.50

DJ40L 3 Channel Mic (Built-in) to light, 3kW, £38.75

DJ70S 70 watt Disco amp/mixer, £49.75

DISCOAMP 100 watt Disco amp/mixer, £65.85

DJ105S 30 watt Disco amp/mixer, £32.25

Anti-Feedback Quality Mic, £11.50

DJ500 50 watt PA amplifier, £43.95

DJ700 70 watt £52.75

DJ1000 100 watt £63.00

Group 300 150 watt rms Group Valve amplifier, £86.00

● Portable discos—details on request

● Credit terms for callers



FIBRE OPTICS  
 LIGHTING - MICS  
 EFFECTS - PRO-  
 JECTORS - SPOTS  
 DIMMERS -  
 STANDS - MIXERS  
 SPEAKERS  
 Everything for PA - Disco - Lighting. FREE Stock List Ref. No. 18.

#### SINCLAIR PROJECT 60 MODULES

—SAVE POUNDS

Z30 £3.57 Z50 £4.37

STEREO 60 £7.97 PZ5 £3.97

PZ6 £6.37 PZ8 £4.77.

Transformer for PZ8 £2.95.

Active Filter Unit £4.45.

Stereo FM Tuner £16.95.

IC12 £1.80 Q16's £15 pair.

Post, etc. 20p per item.



PACKAGE DEALS Post 25p  
 2 x Z30, Stereo 60, PZ5 £15.95  
 2 x Z30, Stereo 60, PZ6 £18.00  
 2 x Z50, Stereo 60, PZ8 £20.25  
 Transformer for PZ8 £2.95  
 PROJECT 605 KIT £19.95

See earlier page of this magazine for transistors, I.C.'s and Semiconductor prices. Latest List Ref. No. 36 on request

E & OE

**Henry's RADIO LIMITED**  
 EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381  
 354-356 High Fidelity and Tape Equipment 01-402 5854/4736  
 309 PA-DISCO-Lighting High Power Sound 01-723 6963  
 303 Special offers and bargains store  
 All mail to 303 Edgware Road, London W2 1BW

Open—9 am-6 pm  
 6 days a week  
 (309 closed  
 Thursday)  
 All stores open  
 all day Saturday