

PRACTICAL

ELECTRONICS

SEPTEMBER 1973

20p

QUADRAPHONIC

FOUR CHANNEL SOUND

PE **BORDO**

COMPLETE SQ SYSTEM
FOR THE CONSTRUCTOR

Also: Phasing Unit - Photographic Thermometer & Exposure Meter

Why two shafts?

the X25 Soldering Iron

220-240 Volts or 100-120 Volts.


Model X25

The leakage current of the X25 is only a few microamps and cannot harm the most delicate equipment.

Tested at 1500v A.C. 25 watt. Fitted long-life iron-coated bit 1/8"

2 other bits available 3/32" and 3/16"

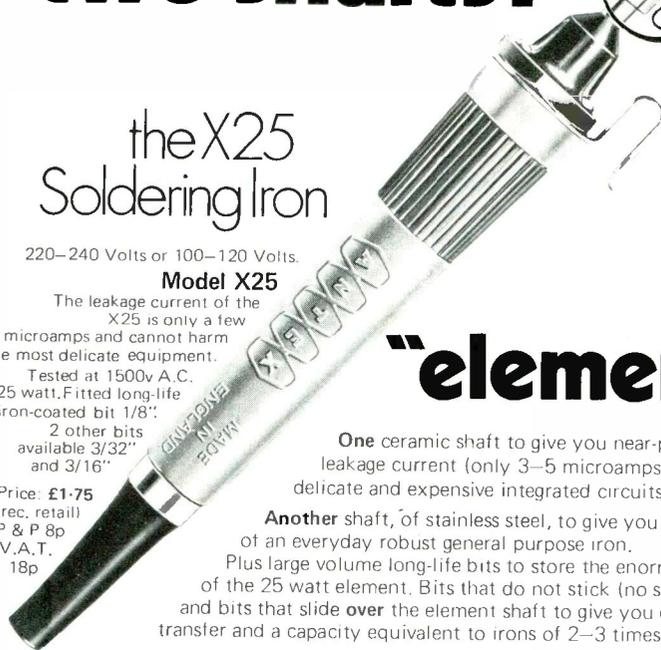Price: **£1-75** (rec. retail) P & P 8p V.A.T. 18p



"elementary"

One ceramic shaft to give you near-perfect insulation and negligible leakage current (only 3-5 microamps) so that you can safely solder delicate and expensive integrated circuits and transistors, even when "live".

Another shaft, of stainless steel, to give you the strength required of an everyday robust general purpose iron.

Plus large volume long-life bits to store the enormous heat-capacity of the 25 watt element. Bits that do not stick (no screws or pins) and bits that slide over the element shaft to give you efficient heat transfer and a capacity equivalent to irons of 2-3 times the wattage.



MODEL CCN

220 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64".

PRICE: **£1-95** (rec. retail) P & P 5p V.A.T. 20p



PRICE: **£2-05** (rec. retail) P & P 12p V.A.T. 22p

MODEL MLX.KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong

plastic wallet with booklet "How to Solder"

MODEL G

18 watt miniature iron, fitted with long life iron-coated bit 3/32".

Voltages 240, 220 or 110. PRICE: **£1-95** (rec. retail) P & P 5p V.A.T. 20p



MODEL SK.1 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE: **£2-95** (rec. retail) P & P 12p V.A.T. 31p

MODEL CN

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64", to 3/16". Voltages 240, 220, 110, 50 or 24. PRICE: **£1-75** (rec. retail) P & P 5p


MODEL CN2

Miniature 15 watt soldering iron fitted with nickel plated bit 3/32". Voltages 240 or 220. PRICE: **£1-75** (rec. retail) P & P 5p

MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, and "How to Solder" booklet.

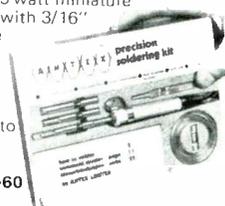PRICE: **£2-60** (rec. retail) P & P 8p. V.A.T. 27p



From radio or electrical dealers, car accessory shops or in case of difficulty direct from:—
ANTEX LTD. FREEPOST
(no stamp required) PLYMOUTH
PL1 1BR. Tel: 0752 67377.

- Please send the ANTEX colour catalogue.
 Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000) Reg. No: 393594

NAME
ADDRESS
P.E.10

PRACTICAL ELECTRONICS

VOLUME 9 No. 9 SEPTEMBER 1973

CONSTRUCTIONAL PROJECTS

- P.E. RONDO QUADRAPHONIC SOUND SYSTEM** *by B. Cole*
The first of a series of articles describing Quadraphonics in theory and practice—
with practical details of a decoder 752
- PHASING UNIT** *by D. Benfield*
A simple sound effects unit 772
- P.E. SOUND SYNTHESIZER—8** *by G. D. Shaw*
Voltage controlled output amplifiers and differential amplifier 775
- AUDIO LOGIC PROBE** *by B. Woodland*
Uses two different tones to indicate logic levels 782
- ENLARGER EXPOSURE METER & THERMOMETER** *by J. M. Bartlett*
An invaluable aid for the photographer who makes his own prints 790

GENERAL FEATURES

- INGENUITY UNLIMITED**
Car windscreen wiper control 768
- LOGIC TUTOR EXPERIMENTS—5** *by M. J. Hughes*
Exclusive OR Function 771
- NEW DEVICES . . . APPLICATIONS**
Describing the TGS (Thermal Gas Sensor) of the PE Electronic Nose 786

NEWS AND COMMENT

- EDITORIAL—A New Dimension in Sound** 751
- SPACEWATCH** *by Frank W. Hyde*
Boulders of Saturn—Gravity Controversy—ESRO and Satellites—Joint Projects 767
- NEWS BRIEFS**
Open University & Electronics—British Technology for USA—Measurements 780
- ELECTRONORAMA**
Cable laying in the Atlantic, from factory to sea floor 788
- MARKET PLACE**
A look at i.c. accessories and audio equipment 797
- INDUSTRY NOTEBOOK**
What's happening inside industry 798
- PATENTS REVIEW**
Cough Monitoring—Wind Direction Indicators 801
- READOUT**
Readers join in the log versus linear controversy 802

Our October issue will be published on Friday, September 14, 1973

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2.65. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

6 volume library '67-'73 is now ready

**the
only work
of its kind
anywhere**

Speedier, more efficient servicing means increased turnover . . .

This library is a gold-mine of technical information. Six hard-bound volumes giving vital data on more than 1500 models of Television (colour and mono), Radios, Car Radios, Stereograms, Record Players and Tape Recorders. More than 4000 pages clearly display thousands of circuits, printed panel diagrams, component layout diagrams, waveform graphs, block diagrams, etc. Over 800 pages, devoted entirely to Colour TV, include installation instructions, new term explanations, purity adjustments, colour balance, static convergence and a wealth of invaluable information. Here, in fact, is all the data you need for efficient and speedy repair work.

Your Guarantee

Sending for these valuable books, even though you also enclose your remittance, commits you to nothing. Unless you are absolutely satisfied you are perfectly free to return the set and if you do so within 10 days of delivery your money will be refunded in full and without question.

How to get your 6-volume set

Detach the Order Form below and send it, with the appropriate remittance to:

Purnell Book Service Ltd.,
Box 20 Abingdon, Berks, OX14 4HE

Makes of Colour TV include:

Alba, Baird, Bang and Olufsen, B.R.C., Bush, Decca, Dynatron, Ecko, Ferguson, Ferranti, G.E.C., Invicta, H.M.V., Marconiphone, I.T.T./K.B., Masteradio, Murphy, Philips, Pye, Sobell, Stella, Ultra, Hitachi, Thorn Consumer Electronics, Korting, R.G.D., Sony, Telefunken.

All these makes of Mono TV, Radios, Car Radios, Stereograms, Record Players, Tape Recorders:

Aiwa, Alba, Baird, Bang and Olufsen, Beogram, Beolit, Blaupunkt, B.R.C., Bush, Cossor, Crown, Dansette, Decca, Defiant, Dulci, Dynatron, Eddystone, Ecko, Elizabethan, Ferguson, Ferranti, Fidelity, G.E.C., Grundig, Hacker, Halcyon, H.M.V., Hitachi, Invicta, I.T.T./K.B., JugoElektra, Klinger, Loewe Opta, Marconiphone, Masteradio, Monogram, Murphy, National, Navico, Perdio, Peto Scott, Philco, Philips, Portadyne, Pye, Radiomobile, Radionette, R.G.D., Roberts' Radio, Robux, Sanyo, Sharp, Sobell, Sony, Standard, S.T.C., Stella, Stereosound, Telefunken, Teletron, Thorn, Sanyo, Ultra, Unitra, Van Der Molen, World Radio, Thorn Consumer Electronics, Elpico, Rigonda (USSR), Waltham.

Plus such developments as:

Mullard Integrated Units, Electronic Video Recording and Reproduction - EVR system, Radio Receivers - Car radios, Stereo Multiplex reception, Capacitance Diode Tuning, Colour Television Test Equipment - Crosshatch Generator, Degaussing Coil, E.H.T. Meter, Colour Bar Generator, Cathode Ray Oscilloscope, Power Supply requirements, Alignment, Circuit design.

To: Purnell Book Services, P.O. Box 20, Abingdon, Berks OX 14 4HE

Please send me the 6-volume set of RADIO & TV SERVICING for which I enclose cheque/P.O. No. _____ crossed and made payable to Purnell Book Services Ltd. for the full cash price of £27.75 tick for £10 deposit to be followed by 4 successive appropriate monthly payments of £4.75 (total £29) box

I understand that unless I am entirely satisfied I may return the volumes in good condition within 10 days and my money will be refunded in full. **BLOCK LETTERS PLEASE**

Name _____

Address _____

TRADE APPLICATION (To be accompanied by Trade Order)

Please supply _____ 6-volume set(s) of RADIO & TV SERVICING at £27.75 per set. (Credit 30 days) **BLOCK LETTERS PLEASE**

Name _____

Company _____


Signature _____

IMPORTANT: Individual volumes are available on application.

Please return entire form. Available U.K. only

027

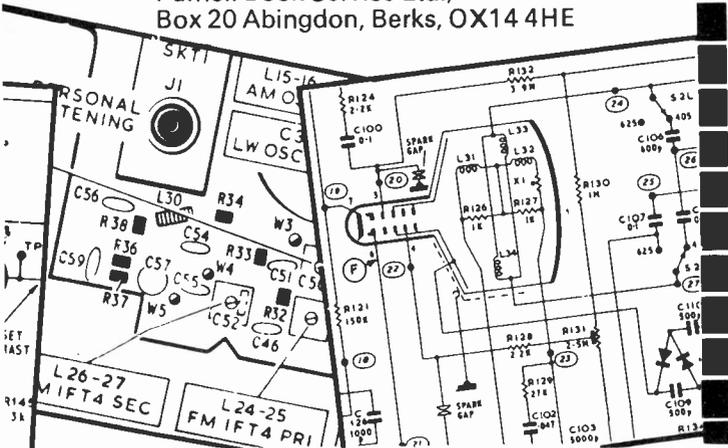Purnell Book Services Ltd Reg London 958963, 49 Poland St., London W1






**SCS COMPONENTS, P.O. Box 26,
Wembley, Middlesex HA0 1YY**
The 'Professional' Amateur Supplier

TERMS Retail mail order subject to £1.00 minimum order.
Cash with order only. Trade and educational establishments
M/AC on application (minimum £5.00).
Postage 10p inland, 25p. Europe.
GUARANTEE: All goods carry full manufacturer's
warranty. Get in touch today for a complete
run-down of devices available from SCS (include SAE).

device of the month ZN414

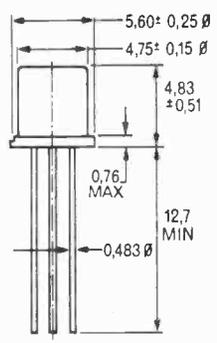


The Ferranti ZN414 is a complete a.m. radio circuit which operates from 1.1 to 1.8 volts and requires only battery, earphones and antenna plus a tuning capacitor and two decoupling capacitors. The ZN414 features: medium and long waveband, good stability on assembly, no setting up of IF coils, plus much more.

a complete a.m radio circuit for just

£1.20
+
VAT

compatible device MFC 4000B

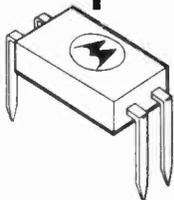

The Motorola 1/4-Watt Audio Amplifier is designed for the output stage of battery powered portable radios.

- * 250 mW of Audio Output Power
- * Low Standby Current—3.5 mA typical
- * Low Harmonic Distortion
- * Reduces Component Count in Portable Radios by Two Transformers and Two Transistors
- * Eliminates Costly Component Matching Requirements

motorola 1/4 watt
audio amplifier
MFC4000

50p
+
VAT



FIBRE OPTIC

High quality glass Fibre Optic cable manufactured by a World famous W. German optical group. Ideal for all light transmission applications and experiments (450-1,300 nm) light monitoring - opto-electronic system - short distance communication systems etc.

Type LKF 450. 450 glass fibres, 40 micron diameter held within a tough, highly flexible P.V.C. sheathing. O.d. 2.3 mm. 17p per metre (39") plus P & P 5p.

Type LKF 800. 800 glass fibres, 70 micron diameter held within a tough, flexible P.V.C. sheathing. O.d. 4.0 mm. £1.75 per metre (39") plus P & P 10p.

End Ferrules. Specially produced brass ferrules for these cables. LKF 450 10p for 10 LKF 800 20p for 10. No P & P when purchased with either type of Fibre Optic cable.

Cheques or Postal Orders to:
H.V. SKAN LIMITED,
425/433 Stratford Road, Shirley,
Solihull, Warwickshire, B90 4AE.
Tel. 021-744 6791.

Video Spray 90 cleans tape heads- in operation



A quick squirt of Video-spray 90 and your tape heads and gaps are rapidly cleaned. And you can use Video-spray 90 whilst the machine is in operation. It dissolves even hardened dirt by simultaneous physical and mechanical action. 99.8% pure. Video-spray 90 can be used safely with any video or sound recording machine. The spray doesn't attack plastics, is electrically non-conductive and is not inflammable. Supplied in 2.5 oz. and 6 oz. cans. Available through your retailer or direct from:

Special Products Distributors Ltd.
81 Piccadilly, London W1V 0HL Tel: 01-629 9556

Choose a Heathkit project.. make your spare time more rewarding



And your first step is absolutely Free—simply send today for the latest Hi-Fi/Electronics catalogue from Heath, the world leaders in electronic kits. Every model is designed with the beginner in mind, and the assembly manuals are famous for their clarity and easy to follow step-by-step instructions. The latest Heathkit catalogue contains many new kit projects that will appeal to you and all our models offer unbeatable value for money. Payment is so easy too—choose cash or low deposit terms (starting at £2 per month for up to £40 credit).

Anyone can build a Heathkit model using only a few simple tools found in most homes and added to this is a technical consultant service both before and after purchase.

These are just a few of the unshakeable reasons why Heathkits are so popular throughout the world. Some samples from our range are shown here.

LOUDSPEAKER KITS feature fully finished cabinets for fast, easy building.

STEREO HI-FI SYSTEMS and **SEPARATES** offer state-of-the-art performance and design.

AUTOMOTIVE TEST AND ANALYSER KITS make car testing and trouble-shooting a pleasure.

LOW PRICED TESTERS AND INSTRUMENTS for hobbyist and technician.

PORTABLE RADIOS AND **HOME/OFFICE INTERCOMS**


DESK AND POCKET ELECTRONIC CALCULATORS

METAL LOCATORS of advanced solid-state design.

AMATEUR RADIO AND SWL RECEIVERS, etc. even a robust **BATTERY CHARGER KIT**

And many more models too numerous to mention here.

FREE Catalogue

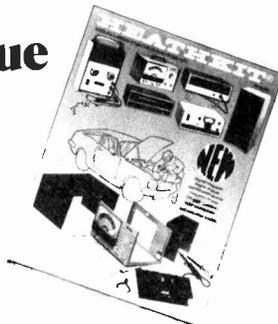

Please send me a FREE Heathkit catalogue and details of your Cash and Low Deposit terms

Name _____

Address _____

HEATH
Schlumberger

Heath (Gloucester) Limited, Dept. PE-09-73
Gloucester GL2 6EE. Telephone 0452 29451

DISCOUNTS UP TO

60%

Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE.

ALL PRICES ARE INCLUSIVE OF V.A.T.

FANTASTIC OFFER

GARRARD SP25 Mk. III

Goldingr G800. Teak finish, plinth and fitted cover with mains lead and DIN plug and screened lead. All fully wired. Please add £1.75 for P. & P. and Ins.

£14-20

TURNTABLES

Please add 95p P. & P. & Ins.

BSR MP60	£8.35
Garrard SP25 Mk. III	£8.70
Garrard SL65B	£12.30
Garrard AP76	£16.45
Garrard 401	£22.45
Garrard Zero 100 single	£30.55
Garrard Zero 100 auto	£33.20
Goldingr G185/P&C	£59.35
Goldingr G101P/P&C	£19.40
Goldingr GL72	£21.95
Goldingr GL72/P	£28.55
Goldingr GL75	£27.40
Goldingr GL75P	£33.95
Goldingr GL75 Lid	£3.85
Leak Delta	£44.20
Pioneer PL12D	£35.10
Thornes TD125	£54.15
Thornes TD125 AB	£81.40
Thornes TD160 AB&C	£44.90
Wharfedale Linton with cart	£25.00

TUNERS

Please add 95p P. & P. & Ins.

Alpha Highgate FT 150	£33.30
Amstrad Multiplex 3000	£24.80
Leak Delta FM (Cased)	£47.45
Leak Delta AM/FM	£56.45
Metrosound FMS 20 Mk. II	£34.85
Rogers R/brook FET4 (Cha)	£29.50
Rogers R/brook FET4 (Cased)	£31.90
Rogers R/bourne FET4 (Cased)	£41.25
Sinclair PRO60 Mod	£14.90
Sinclair cased tuner	£26.15

TUNER AMPLIFIERS

Please add £1.10 P. & P. & Ins.

Alpha FR 3000	£61.35
Goodmans Module 80	£59.90
Goodmans Mod 80 Com	£107.75
Goodmans Mod 90	£74.65
Goodmans One-Ten	£86.65
Leak Delta 75	£107.75
Rogers R/Brook cha.	£62.30
Rotel 150A	£45.90
Rotel 200A	£58.95

AMPLIFIERS

Please add 95p P. & P. & Ins.

Amstrad 8000 Mk. II	£16.45
Amstrad IC2000	£28.80
Amstrad Integra 4000	£23.50
Alpha Highgate FA400	£39.05

All prices correct at time of press. E. & O.E. and are subject to alterations.



GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE9), 174 Pentonville Road, London, N.1. Tel. 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue Ilford, Essex. Tel. 01-550 1086

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS: Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

Global 10 + 10	£19.75
Global 20 + 20	£23.20
Leak Delta 30	£51.05
Leak Delta 70	£63.25
Metrosound ST20E Mk. II	£29.60
Metrosound ST60	£50.85
Rogers R/brook Ch.	£41.15
Rogers R/brook Ca.	£44.50
Rogers R/bourne Ch.	£54.25
Rogers R/bourne Ca.	£56.90
Sinclair 2000	£24.15
Sinclair 3000	£31.00
Sinclair 605	£21.45
Sinclair PRO 60 2 x Z30/PZ5	£16.40

Sinclair PRO 60 2 x Z30/PZ6	£19.45
-----------------------------	--------

Sinclair PRO 60 2 x Z50/PZ8 Trans	£25.25
-----------------------------------	--------

Sinclair AFU (Filter Unit)	£4.95
Sinclair Stereo 60 Pre-amp	£7.35
Sinclair IC 12 (Int. Circ)	£2.20
Sinclair Z30 Amp	£3.85
Sinclair Z50 Amp	£4.50
Sinclair PZ5 Power Supp	£4.20
Sinclair PZ6 Power Supp	£6.15
Sinclair PZ8 Mains Trans	£4.95
Sinclair PZ8 Power Supp	£6.15

SPEAKERS

£1.65 for P. & P. (per pair)

Amstrad Acoustra 1500	£27.95
Amstrad Acoustra 2500	£31.95
Apollo 138	£14.05
B&W DMX 5	£41.65
Celestion Ditton 15	£45.90
Celestion Ditton 44	£74.90
Goodmans D/Maxim	£39.70
Goodmans Mezo 3	£49.70
Goodmans Havant	£34.45
Kelerson LS 100	£20.30
Leak 150	£32.75
Sinclair Q16	£10.95
Sinclair Q30	£30.60
Wharfedale Denton II	£25.70

SPEAKER UNITS

Wharfedale Unit 3	£15.60
Wharfedale Unit 4	£27.25
Wharfedale Unit 5	£39.60

CARTRIDGES

Please add 11p P. & P. & Ins.

Goldingr G850	£2.85
Goldingr G800	£3.70
Goldingr G800E	£6.45
Goldingr G800SE	£12.15
Shure M3D	£3.15
Shure M44E	£4.40
Shure M55E	£5.90
Shure 75ED Type 2	£9.35
Shure V15	£25.95
Shure M75E1 Type 2	£8.10

PLINTH & COVERS

£3.02



For Garrard SP25, 2025TC, 3000, BSR, McDonald MF60 £3.08 P. & P. 71p. For AP76, SL72B, SL95B, etc. £4.51 + 71p P. & P.

Multicore Solder Cream for high quality joints in the Electronics Industry

New Multicore Solder Cream was designed for jobs where second best will just not do. Like manufacturing diodes for instance. Or making a tuner chassis. or soldering thick-film circuits. Multicore Solder Cream, a finely graded solder alloy powder in a thixotropic organic vehicle, is easier, quicker, more economic and more reliable than conventional techniques.

Multicore Solder Cream is different. It doesn't spill or need stirring. It can be applied by syringe, automatic dispensers or screen printing—giving instant soldering with

good spread, strong joints with low contact angles. Suitable as a temporary adhesive during assembly, the clear colour flux residue—without solder globules—makes inspection easier. There are three types of Multicore Solder Cream—one of them may be just what you're looking for.

For full information on this or any other Multicore products, please write on your company's letterhead direct to:



Multicore Solders Ltd., Maylands Avenue, Hemel Hempstead, Herts. HP2 7EP. Tel: Hemel Hempstead 3636. Telex: 82363.

GET BETTER ALL-ROUND PERFORMANCE WITH DEXTER CAPACITOR DISCHARGE IGNITION



- The Dexter Capacitor Discharge Ignition Unit can improve performance in many ways —
- ★ EASIER STARTING
 - ★ REDUCED FUEL CONSUMPTION
 - ★ BETTER ACCELERATION
 - ★ HIGHER TOP SPEED
 - ★ EXTENDED LIFE FOR BATTERY AND SPARK PLUGS
 - ★ NO MORE CONTACT-BREAKER POINT BURN
 - ★ IMPROVED COMBUSTION

The Dexter Capacitor Discharge Ignition Unit is fully suppressed to prevent radio interference. It can be fitted easily and simply to your car, and costs only £9.80 plus 25p post and packing. 12 Volt neg. earth only. Fully guaranteed for 12 months.

DEXTER & CO. 1 Ulver House, 19 King Street, Chester CH1 2AH. Tel. 0244-25883



WINDSCREEN WIPER DELAY KIT

Complete kit of parts including drilled and tinned fibreglass printed circuit board.

The unit provides intermittent wiper operation with a delay up to approximately 60 seconds which can be varied to optimise visibility in conditions of light rain, spray, etc. The original wiper switch overrides when normal operation is required.

Suitable for most British cars

£2.86 inc. V.A.T. and P.&P.

ESSEX X-RAY CO. LTD.

Cash with order

57 THEYDON PARK RD.

THEYDON BOIS, EPPING, ESSEX CM16 7LR

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY £1.05

POST & PACKING 45p EACH



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 27½p

POST & PACKING 16½p

TESTED AND GUARANTEED PAKS

- | | | | |
|-----|-----|---|-----|
| B79 | 4 | IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic | 55p |
| B81 | 10 | Reed Switches, 1" long 1/4" dia. Highspeed P.O. type | 55p |
| B99 | 200 | Mixed Capacitors. Approx. quantity, counted by weight Post & packing 15p. | 55p |
| H4 | 250 | Mixed Resistors. Approx. quantity counted by weight Post & packing 15p. | 55p |
| H7 | 40 | Wirewound Resistors. Mixed types and values | 55p |
| H9 | 2 | OC711 Light Sensitive Photo Transistor | 55p |
| H28 | 20 | OC2001/2/3 PNP Silicon uncoded TO-5 can | 55p |
| H30 | 20 | 1 Watt Zener Diodes. Mixed Voltages 6.8-43V | 55p |
| H35 | 100 | Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked | 55p |
| H38 | 30 | Short lead Transistors, NPN Silicon Planar types | 55p |
| H39 | 6 | Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945 Sil. and Germ. | 55p |
| H40 | 20 | BFY 50/2, 2N696, 2N1613, NPN Silicon uncoded TO-5 | 55p |
| H41 | 2 | BD131/BD132 Complementary Plastic Transistors | 55p |

UNMARKED UNTESTED PAKS

- | | | | |
|-----|-----|--|-----|
| B1 | 50 | Germanium Transistors PNP, AF and RF | 55p |
| B66 | 150 | Germanium Diodes Min. glass type | 55p |
| B83 | 200 | Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ. | 55p |
| B84 | 100 | Silicon Diodes DO-7 glass equiv. to OA200, OA202 | 55p |
| B86 | 100 | Sil. Diodes sub. min. IN914 and IN916 types | 55p |
| H6 | 40 | 250mW Zener Diodes DO-7 Min. Glass Type | 55p |
| H15 | 30 | Top Hat Silicon Rectifiers. 750mA. Mixed volts | 55p |
| H16 | 15 | Experimenters' Pak of Integrated Circuits. Data supplied | 55p |
| H17 | 20 | 3 amp. Silicon Stud Rectifiers, mixed volts | 55p |
| H20 | 20 | BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts | 55p |
| H34 | 15 | Power Transistors. PNP, Germ. NPN Silicon TO-3 Can | 55p |

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.10 each



OVER
1,000,000

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

600,000 Silicon planar plastic transistors. Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc.

Audio NPN, similar to ZTX300, 2N3708/9 BC107/8/9, BC168/9, etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 500 for £3.30, 1,000 for £5.50, 10,000 for £44.

P & P 11p per 1,000

OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR VARIOUS TYPES £1.10
P & P 27½p

Our famous PI Pak is still leading in value for money

Full of Short Lead Semiconductors and Electronic Components, approx. 170.

We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and

a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. Only 55p. 11p P & P on this Pak.



A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This was a project in the September 1972 edition of Television.

This complete kit of parts costs £3.85, post paid.

A MUST for Colour T.V. Alignment.

Electronic Transistor Ignition

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features: Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility. This project is a "star" feature in the September edition of "Electronics Today International" magazine available from August 10th. Our kit is recommended by the ETI magazine.

Complete kit including P. & P. £7.92
Ready built & tested unit £3.02 EXTRA

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

100,000 Plastic Power Transistors

in stock, more on way!

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1 VCE Min. 15 HFE Min. 15

40 watt	1-12	13-25	26-50
90 watt	22p	20p	18p
	261p	241p	22p

Range 2 VCE Min. 40 HFE Min. 40

40 watt	1-12	13-25	26-50
90 watt	33p	31p	29p
	381p	361p	33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16p each | Now new low 16 pin type at 18p each | profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

B.P.I. Transistor Equivalents and Substitutes: 40p

This includes many thousands of British, U.S.A., European and C.V. equivalents.

The Iliffe Radio Valve & Transistor Data Book 9th Edition: P & P 231p. 75p

Characteristics of 3,000 valves and tubes. 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of publications.

N.B.—Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

ALL PRICES INCLUDE 10% V.A.T.

MINIMUM ORDER 55p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. **OVERSEAS ADD EXTRA FOR POSTAGE.**

BI-PRE-PAK LTD

Co. Regr. No. 820919

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX

TELEPHONE: SOUTHEND (0702) 46344

Sinclair Project 60

Now—the Z.50 Mk.2


with built-in automatic transient overload protection

When originally introduced, the Sinclair Z.50 proved how it was possible to design and produce a popularly priced modular power amplifier having characteristics to challenge the world's costliest amplifiers. Many thousands of Z.50's are now giving excellent service day in, day out. But we have also learned that constructors do not always use their Z.50's ideally. That is why we have introduced modifications whereby risk of damage through mis-use is greatly reduced and performance further enhanced. The Z.50 Mk.2 has improved thermal stability, more accurately regulated D.C. limiting to ensure more symmetrical output voltage swing and clipping and still less distortion at lower power. Z.50 Mk.2 is compatible with all other Project 60 modules, and may be incorporated to advantage in existing systems. Eleven silicon epitaxial planar transistors are now used, two more than in the original Z.50; circuitry has been re-designed, making this versatile high performance amplifier better than ever.



with free manual
£5.48

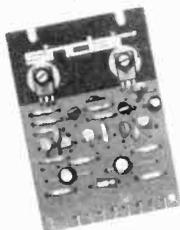Z.30 the power amplifier for quality and economy




with free manual
£4.48

The Z.30 provides excellent facilities for the constructor requiring a high fidelity audio system of less power than that available from Z.50's. Using a power supply of 35 volts, Z.30 will deliver 15 watts RMS into 8 ohms, or 20 watts RMS into 3 ohms using 30 volts. Total harmonic distortion is a fantastically low 0.02% at 15 watts into 8 ohms with signal to noise ratio better than 70 dB unweighted. Input sensitivity 250mV into 100K ohms. Size 80 x 57 x 13 mm (3 1/8 x 2 1/4 x 1/2). Z.30, Z.50 and Z.50 MK 2 modules are compatible and interchangeable.

Brilliant new technical specifications

Input impedance 100 K Ω
Input (for 30w into 8 Ω) 400mV
Signal to noise ratio, referred to full o/p at 30v HT 80dB or better
Distortion 0.02% up to 20W at 8 Ω . See curve
Frequency response 10Hz to more than 200 KHz \pm 1dB
Max. supply voltage 45v (4 Ω to 8 Ω speakers) (50v 15 Ω speakers only)
Min. supply voltage 9v
Load impedance — minimum: 4 Ω at 45v HT
Load impedance — maximum: safe on open circuit

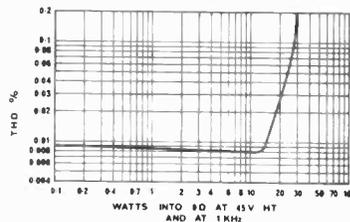

Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.5	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave de luxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (£25) & A.F.U. (£5.98) may be added as required.

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

sinclair

Sinclair Radionics Ltd., R.O. London Rd., St. Ives, Huntingdonshire PE17 4HJ (Phone: St. Ives 64311). Regd. Bus. No. England 699483.

the world's most advanced high fidelity modules

Stereo 60 Pre-amp/control unit



Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio — up to 3mV. Mag. p.u. 3mV. correct to R.I.A.A. curve ± 1 dB 20 to 25,000 Hz. Ceramic p.u. — up to 3mV. Aux — up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +12 to -12dB at 10KHz. BASS +12 to -12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

Built, tested and guaranteed. **£9.98**

Project 60 Stereo F.M. Tuner




The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other advanced features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and switchable squelch circuit for silent tuning between stations. In terms of high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with most other high fidelity systems.

SPECIFICATIONS—Number of transistors: 16 plus 20 in I.C. **Tuning range:** 87.5 to 108MHz. **Sensitivity:** 7 μ V for lock-in over full deviation. **Squelch level:** Typically 20 μ V. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10Hz — 15KHz (± 1 dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 μ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. maximum. **Operating voltage:** 25–30VDC. **Indicators:** Stereo on, tuning. **Size:** 93 x 40 x 207mm.

Built and tested. Post free. **£25**

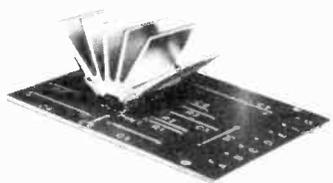Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC. make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak). 6–8 Ω . **Frequency Response:** 5Hz to 100KHz ± 1 dB. **Total Harmonic Distortion:** Less than 1% (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.

£2.98 Post free

Power Supply Units The new PZ.8 Mk.3



The most reliable power supply unit ever made available to constructors. Brilliant circuitry makes failure from over load and even direct shorting of the output impossible. This is due to an ingenious re-entrant current limiting principle which, as far as we know has never before been available in any comparable unit outside the most expensive laboratory equipment. Ripple and residual noise have been reduced to the point of almost total elimination. This is, of course, the perfect unit for Project 60 assemblies, particularly where the new Z.50 MK.2 amplifiers are used. Nominal working voltage — 45

PZ.8 Mk.3—£7.98

(Mains transformer, if required) £5.98

PZ.5 30v. un stabilised

(not suitable for Project 60 tuner) £4.98

PZ.6 35v. stabilised

(not suitable for IC. 12) £7.98

Project 605

Sinclair
Project 605
Amplifier



the easy way to
buy and build
Project 60
without
soldering

Project 605 in one pack contains one PZ.5, two Z.30's, one Stereo 60 and one Masterlink, which has input sockets and output components grouped on a single module and all necessary leads cut to length and fitted with clips to plug straight on to the modules thus eliminating all soldering

Complete with comprehensive manual, post free
All you need for a superb 30 watt high fidelity stereo amplifier

£29.95

Order form

Please send

I enclose cash/cheque/money order.

Name _____

Address _____

PE/9/73

SINCLAIR RADIONICS LTD., LONDON ROAD
ST. IVES, HUNTINGDONSHIRE PE17 4HJ

sinclair

Add 10% V.A.T. to all prices quoted on page opposite and above

Practical Electronics September 1973

SANSEI TEST EQUIPMENT




10 IN ONE

Mini Lab, 10 instruments in one. Including AC and DC Voltmeter, Ohm Meter, etc.

£11-95

including VAT & P.P.

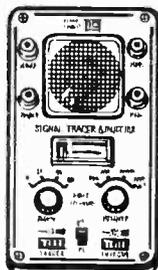

SIGNAL TRACER/INJECTOR

Designed to receive audio frequency, built in amplifier with high gain of 60dB.

£11-55

including VAT & P.P.


SIG MITTER

Powerful trouble shooting signal injector.

Model SE260.

£2-20

including VAT & P.P.

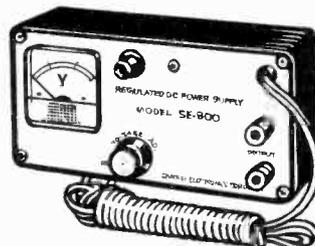

DC POWER SUPPLIES

Regulated power supply variable up to 15V 0.5A. Model SE800. Ideal for development work.

£11

including VAT & P.P.

NEW HIGHLY SENSITIVE MULTITESTERS

Model M650 with mirror scale.

£7-70

including VAT & P.P.



Associates Ltd.

Cricketfield Lane, Bishop's Stortford, Herts.
Telephone 0279 56347

Do you suffer from tired eyes due to bright lights, or need a dimmer light for watching television in comfort. Well, we have the answer, a

GREENBANK DIMMER SWITCH

Just look at these features:

- ★ Velvet dim to full brightness at the touch of a finger
- ★ Positive off position, using on-off switch
- ★ Built-in radio interference suppressors
- ★ Controls up to 300 watts
- ★ Straight replacement for a standard light switch

All this for only

£3-75
complete

This price includes V.A.T., also P. & P. Why not write or phone now? Please send C.W.O. to:

GREENBANK ELECTRONICS

94 New Chester Road
New Ferry, Bebington
Cheshire L62 5AG
Tel. 051-645 3391

BABANI PRESS

NEW TITLES! AVAILABLE NOW


..... FROM ALL GOOD RADIO COMPONENT AND HI - FI SHOPS, BOOK SHOPS, MAIL ORDER COMPANIES AND MOST LARGER BRANCHES OF W. H. SMITH & SON LTD IN MAJOR TOWNS

- BP13 ELECTRONIC NOVELTIES FOR THE MOTORIST
BY B. B. BABANI - 50p
Contains 33 Solid State D. I. Y. projects complete with circuit diagrams.
- BP15 CONSTRUCTORS MANUAL OF ELECTRONIC CIRCUITS FOR THE HOME
BY B. B. BABANI - 50p
Contains 17 Solid State D. I. Y. projects complete with circuit diagrams.
- 200 HANDBOOK OF PRACTICAL ELECTRONIC MUSICAL NOVELTIES
BY B. B. BABANI - 50p
Contains 12 Solid State D. I. Y. projects complete with circuit diagrams.

BERNARDS(publisher's)LTD

VEROSTRIP

LENGTH 8-5"

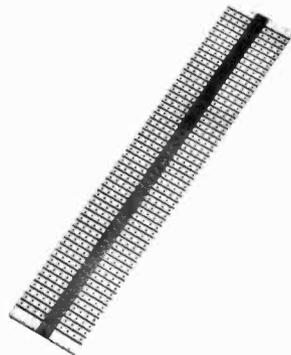


WIDTH 1-5"

Available from your Local Retailer

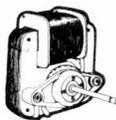0-1 and 0-15 pitch Vero Strip is suitable for all applications where Tag Boards can be used.



VERO ELECTRONICS LTD.
INDUSTRIAL ESTATE
CHANDLERS FORD HANTS.



MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snp at 72p. Postage 20p for first one then 10p for each one ordered.

MUSIC ON TAPE

A further buy enables us to offer these at an even lower price—namely 65p each or 5 for £2-50. Send for list of titles. We can't repeat when sold out.

BALANCED ARMATURE UNIT

500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits. 87p each, 10 for £3-76.

CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system. 88p each or 10 for £3-42.

12 VOLT 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price £2-20, plus 20p post & packing.

Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £6-33 plus 65p post.

BAKELITE INSTRUMENT CASE

Size approx. 6 1/2" x 3 1/2" x 2" deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs, etc. Price 50p each. Paxolin lid 11p extra.

MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole, 6 way—1 pole, 12 way. All at 22p each.

CONNECTING WIRE

7-0076 Copper conductors. 500 metre drums available in the following colours: Red/Brown, Yellow, Green/Grey, Blue/Green, Red/Orange, Green/White, Grey/White, Blue/Orange, Brown/Brown/White, Red/Grey, Blue/Grey, Blue/Brown. Price £2-20 per drum plus 40p post. State alternative colours. Ditto—but with 200 metres. Price £1-38 per drum plus 20p. Ditto—but with 100 metres. Price 83p per drum.

DOOR SWITCH

As fitted to refrigerators, etc. Switches off as door closes. White 17p each. Black 15p each.

GOODMANS P.M. SPEAKERS

8in x 5in hi flux 15 ohm coil very suitable for use with Mullard Unilux stereo amplifier or with the EP9000 in its own. £1-65 plus 20p post each. 7in x 4in also 15 ohm and suitable for use with the EP9000—not quite such good quality of course. Price £1-05 each.

MICRO SWITCH

5 amp changeover contacts. 11p each. 10 for 99p. 15 amp Model 15p. Changeover 15p each.

U.V. LIGHTING

Useful for fluorescence in metals and for looking for water marks, etc., also for fitting over tropical fish tanks—African violets and other indoor plants which must have U.V. for healthy growth. The outfit comprises of a 12in U.V. tube—choke—starter holder and tube ends. Price £2-20 plus 20p post.

SOIL HEATING KIT

Suitable for garden frame or propagating shelf, etc. Comprises 40W mains transformer, heating wire, connection strip and insulated wire with connection diagram. £1-85 plus 20p post.

80 WATT TUBULAR ELEMENTS

Brass encased with beaded flux ends. Standard replacements in most absorption type refrigerators but also has dozens of other uses. 48p each or 10 for £4-82.

SPIT MOTOR

200-250V Induction Motor, driving a Carter gear box with 1 1/2in. of output drive shaft running at 5 revs per minute. Intended for roasting chickens also suitable for driving models—windmills, coloured disc lighting effect, etc., etc. £2-04 plus 20p post and insurance.



MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1153 300mW power output 72p. Model 1172 750mW power output 84p. Model EP9000 4 watt power output £1-60. EP9001 twin channel or stereo pre amp. £1-92. 10% discount if 10 or more ordered.

CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower built by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using a clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering etc. etc. A real bargain at £2-05.

MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, 4 January 73. All electronic parts £2-20 post paid.

TAPE PLAYBACK UNITS

Mains operated. Made by Reditone the famous "music in the background people". These are complete units for playing tape at standard speed (3 3/4"). These have a superior motor driven fly wheel to control the tape through the capstan and also an even equally useful valve amplifier with EL84 output. In a steel case with carrying handle. Tested and in good working order £2-50 or some in need of repair but complete £3-50. Cassettes of tape pre-recorded £1-10 (please state type of music required). 75p carriage up to 200 miles then 50p per 100 miles extra.

RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker when signal stops you've found the fault. Use it on Radio, TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2-20—twin stethoscopes instead of earpiece 83p extra—post and ins. 20p.

6 MAINS TRANSFORMERS

Our Ref: MTM1 27V at 8A. Upright mounting fully shrouded—flying leads—fully tapped primary. Price £3-30. Our Ref: MTM2 12V at 1A. Upright mounting with fixing lugs, tag connection. 240V primary—12V 1A secondary. Price 83p. Our Ref: MTM3 6-3V 2A upright mounting with fixing lugs, tag connections, 240V primary 6-3V 2A secondary. Price 77p. Our Ref: MTM4 18V-1A with thermal cut-out, upright mounting with fixing lugs—tag connections. Primary 240V—secondary 18V at 1A. Price 88p. Mains Isolation MTM5. 350V earth shielded—flex leads—upright mounting lugs for fixing. Price £2-50 each. Mains Transformer Bargain. Standard mains 240V input. Secondary 2-4V 9A intermittent 5A continuous. Price 55p.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, £2-50 plus 20p post and insurance.

CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in *Wireless World* about a year ago. We can supply kit of parts for an improved and even more efficient version (*Practical Wireless*, June). Price £2-55 plus 20p post. When ordering please state whether for positive or negative systems. De-luxe model including printed circuit board, etc. £7-95.

24-HOUR TIME SWITCH

Made by Smiths, these are A.C. mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5A changeover contacts will switch circuit on or off during these periods. £2-75 post and ins. 25p. Additional time contacts 55p pair.

THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2-95, plus 20p post and insurance. Industrial model 5A £3-80.

BATTERY CONDITION TESTER

Made by Mallory but suitable for all batteries made by Ever Ready and others, most of which are zinc carbon types but also mercury manganese—nicad—silver oxide and alkaline batteries may be tested. The tester puts a dummy load on the battery and the meter scale indicates the condition depending upon which section the pointer rests. The section reads "replace", "weak" or "good". The tester is complete in its case, size 3 1/2" x 6 1/2" x 2" with leads and prods. Price £2-48 plus 20p postage.



DRILL CONTROLLER

NEW IKW MODEL Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1-65. Made up model also available. £2-75.

MAINS TRANSISTOR POWER PACK


Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip only £1-10.

SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 14in x 18in £2-54. 23in x 10in £1-10.

SUMMER OFFER!

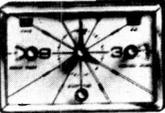Mullard Unilux stereo amplifier at pre VAT price namely £10 for the four module, control units knobs and face plate.



15A ELECTRICAL PROGRAMMER

Learn in your sleep! Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp. on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2-15 + 20p p. & p. or with glass front chrome bezel 83p extra.

PROTECT VALUABLE DEVICES FROM THERMAL RUNAWAY OR OVERHEATING

Thyristors, rectifiers, transistors, etc., which use heat-sinks can be easily protected. Simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90 deg. to 190 deg. F. or with the dial removed range setting is between 80 to 800deg. F. Price 83p.

ROCKER SWITCH

13 amp self-fixing into an oblong hole. Size approximately 1" x 1 1/2" 8p each, 10 for 81p.

THERMAL CUTOUT

A miniature device 3in dia. on one screw fixing mount—can be used for motor overload protection, fire alarm, soldering iron, switch off, etc., etc. 15 amp contacts open with flame—radiant or conducted heat. 11p each or 10 for 99p.

HONEYWELL PUSH BUTTON MICRO SWITCHES

As used in some vending machines, etc. Each switch is a changeover type rated at 15A 250V a.c. Intended for panel mounting with fixing nuts and single black push knob. Single changeover switch 28p, Double switch 42p, Triple switch 61p.

KETTLE ELEMENTS

Made by the famous A.E.I. Co. Complete with washers and combined fixing ring and plug shroud. Normal 2 round pin and flat pin earth connection and overload reset push button. 2 Models—1 1/2in. (approx.) suitable for Swan and other similar models—1 1/2in. (approx.) suitable for G.E.C. Hotpoint, etc. All quick boil 2 1/2kw elements at 240V. Price £1-38 each.

MACLAREN THERMOSTAT

Make and break 20A a.c. with the sensor probe coupled by 2 feet capillary covering range of 10-100°C—complete with large engraved control knob. Price 83p.

J. BULL (ELECTRICAL) LTD.
(Dept. P.E.), 7 Park Street, Croydon CRO 1YD
Callers to 102/3 Tamworth Road, Croydon

MEN! GIRLS!

YOU CAN EARN £50 p.w.
Plus an exciting life and a secure future.
HOW?

Get into the fabulous Computer Industry now. On the ground floor. While industry, commerce, science and governments are desperately seeking trained personnel. Give us only four to six weeks and we can train you in any one of the three vital careers in computers: (1) Programming (men and girls). (2) Operating (men and girls). (3) Key Punching (girls exclusively).

We are the only training organisation able to make this offer. And our teaching methods succeed because they combine specially prepared courses with equipment such as the unique Eduputer, exclusive to us.

Thanks to our methods, people from all walks of life have exchanged boring, under-paid, insecure jobs for careers that have meaning, prestige and security.

Past performance counts for nothing. Provided you have the aptitude (which we can discover quite simply), there is no reason why you should not get out of the rut and into Tomorrow's World—the fascinating world of Computers.

The moment you qualify—and we will help you do just that—one of our own exclusive appointments agencies will introduce you to opportunities galore. Worldwide. At no cost to you. All part of our continuing service.

What have you to lose by enquiring? Information and advice are yours for the asking. Post the coupon TODAY for full details FREE and without obligation.



London Computer Training Services

R68, Oxford House, 9-15 Oxford Street, W.1. Telephone 01-437 9906
127 The Piazza, Dept. R68, Piccadilly Plaza, Manchester 1. 061-236 2935

Please send me your free illustrated brochure on training for Computer Programming (men and girls)

Computer Operating (men and girls)

Key Punching (girls exclusively)

(Tick appropriate box)

Name _____

Address _____

Tel. _____

TO SPARK YOUR IMAGINATION!

the **SPARKRITE** Electronic Ignition Kit only **£9.35**

Kit comprises EVERYTHING
Case, cables, coil connectors,
Silcon grease.
8 page instruction leaflet.

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.


- Sustained peak performance. • Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed. • Suitable for all engines up to 8 cyls. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gunton ignition. Price, £9.35 inc V.A.T. and postage. (12 volt only State Pos or Neg. earth). Ready built unit also available £11.55 inc. V.A.T. and postage GUARANTEED 5 YEARS

ORDER NOW—send P.O./Cheque direct to:
ELECTRONICS DESIGN ASSOCIATES, Dept. PE9
82 Bath St., Walsall WS1 3DE. Phone: 33652

PSYCHEDELIC LIGHTING UNIT IN KIT FORM

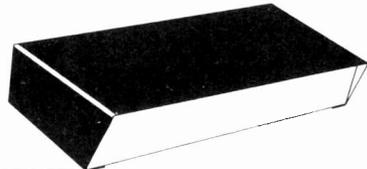Make this fascinating three-channel unit from a kit which contains all components needed to produce a reliable and entertaining display. Takes its drive from the speaker terminals of a record player, tape recorder or portable radio. Will provide a brilliant 2kW of light, using normal 240 volt coloured lamps. Price per kit, £10.40



METAL CABINETS

These attractive steel cabinets are PVC covered in a range of colours, and offer an economically priced unit for the home constructor. The chassis, which has a white satin PVC finish, provides an easily accessible building area, with an integral fascia panel. The cabinet is supplied complete with stick-on feet.

Colours available include Green, Grey, Black, White and Blue. Every effort will be made to supply a selected colour, but please give alternatives if possible.

Approximate size in inches			Price
l.	w.	d.	
8	6	3	£1.60
11	6½	3	£2.04

Other sizes to special order. HOLES PUNCHED in front or back panels to your own requirements. Please send S.A.E. for quotation.

FIXED VOLTAGE REGULATORS

TO3 case. Gives stabilised supply. MVR 5 V, MVR 12 V, MVR15 V. All priced at £1.65

VEROBOARD

	0-1	0-15
2½ × 1in	7p	7p
2½ × 3½in	27p	20p
2½ × 5in	29p	29p
3½ × 3½in	29p	29p
3½ × 5in	31p	32p

PRINTED CIRCUIT CAPACITORS

Electrolytic, low voltage, small size. Available in the following uF/V. 0.47/63, 1/63, 2.2/63, 4.7/40, 10/63, 22/40, 100/10, 9p each; 47/40, 100/63, 220/40, 470/16, 15p each; 1,000/16, 18p each.

Our CATALOGUE, priced at 25p post free, shows the majority of the R.S. range of professional components. Most are available by return of post. Prices include VAT. All orders over 50p POST FREE. S.A.E. with all queries please.

CELECTRON-E

P.O. Box No. 1, Llantwit Major, Glamorgan, Wales CF6 9YN

THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

BRAND NEW FULLY GUARANTEED DEVICES

AC107 0-22	AD162 0-37	BC148 0-11	BD137 0-50	BF188 0-44	OC19 0-39	2G371 0-18	2N2219 0-22	2N3054 0-51	2N4059 0-11
AC113 0-22	AD161 &	BC149 0-13	BD138 0-55	BF194 0-13	OC20 0-70	2G371B 0-13	2N2220 0-24	2N3055 0-55	2N4060 0-13
AC115 0-26	AD162(MP)	BC150 0-20	BD139 0-61	BF195 0-13	OC22 0-42	2G373 0-19	2N2221 0-22	2N3391 0-16	2N4061 0-13
AC117K 0-22	0-61	BC151 0-22	BD140 0-66	BF196 0-16	OC23 0-46	2G374 0-19	2N2222 0-22	2N3391A 0-18	2N4062 0-13
AC122 0-16	ADT140 0-55	BC152 0-19	BD155 0-88	BF197 0-16	OC24 0-42	2G377 0-33	2N2308 0-19	2N3392 0-16	2N4284 0-19
AC125 0-19	AF126 0-31	BC153 0-31	BD175 0-66	BF200 0-50	OC25 0-42	2G378 0-18	2N2309 0-16	2N3393 0-16	2N4285 0-19
AC126 0-19	AF115 0-27	BC154 0-33	BD176 0-68	BF222 0-10	OC26 0-28	2G381 0-18	2N2369A 0-18	2N3394 0-16	2N4286 0-19
AC127 0-19	AF116 0-27	BC157 0-20	BD177 0-72	BF257 0-50	OC28 0-55	2G382 0-18	2N2411 0-27	2N3395 0-19	2N4287 0-19
AC128 0-19	AF117 0-27	BC158 0-13	BD178 0-72	BF258 0-66	OC29 0-55	2G401 0-33	2N2412 0-27	2N3402 0-23	2N4288 0-19
AC132 0-16	AF118 0-39	BC159 0-13	BD179 0-77	BF259 0-94	OC35 0-46	2G414 0-33	2N2416 0-52	2N3403 0-23	2N4289 0-19
AC134 0-16	AF124 0-33	BC160 0-50	BD180 0-77	BF262 0-61	OC36 0-55	2G417 0-28	2N2711 0-23	2N3404 0-31	2N4290 0-19
AC137 0-16	AF125 0-28	BC161 0-50	BD185 0-72	BF263 0-61	OC41 0-22	2N388 0-39	2N2712 0-23	2N3405 0-46	2N4291 0-19
AC141 0-16	AF126 0-31	BC162 0-13	BD186 0-72	BF270 0-39	OC42 0-27	2N388A 0-61	2N2714 0-23	2N3414 0-17	2N4292 0-19
AC141K 0-19	AF127 0-31	BC168 0-13	BD187 0-77	BF271 0-33	OC44 0-17	2N404 0-22	2N2904 0-19	2N3415 0-17	2N4293 0-19
AC142 0-16	AF139 0-33	BC169 0-13	BD188 0-77	BF272 0-88	OC45 0-14	2N404A 0-31	2N2904A 0-23	2N3416 0-31	2N5172 0-13
AC142K 0-19	AF178 0-33	BC170 0-13	BD189 0-83	BF273 0-39	OC70 0-11	2N424 0-54	2N2905 0-23	2N3417 0-31	2N5457 0-35
AC151 0-17	AF179 0-55	BC171 0-16	BD190 0-83	BF274 0-39	OC71 0-11	2N427 0-46	2N2905A 0-23	2N3525 0-83	2N5458 0-35
AC154 0-22	AF180 0-55	BC172 0-16	BD195 0-94	BF275 0-66	OC72 0-16	2N588 0-46	2N2906 0-17	2N3646 0-10	2N5459 0-44
AC155 0-22	AF181 0-50	BC173 0-18	BD196 0-94	BF29 0-30	OC74 0-18	2N589 0-50	2N2906A 0-20	2N3702 0-11	2N5901 0-55
AC156 0-22	AF186 0-50	BC174 0-16	BD197 0-99	BF284 0-24	OC75 0-17	2N589 0-17	2N2907 0-22	2N3703 0-11	2N5902 0-46
AC157 0-27	AF239 0-41	BC175 0-13	BD198 0-99	BF285 0-33	OC76 0-17	2N589A 0-33	2N2907A 0-22	2N3704 0-12	2N5902 0-46
AC165 0-22	AL102 0-72	BC177 0-21	BD199 0-105	BF286 0-24	OC77 0-28	2N589 0-27	2N2923 0-16	2N3705 0-11	2N5903 0-61
AC166 0-22	AL103 0-72	BC178 0-21	BD200 0-105	BF287 0-27	OC81 0-17	2N589 0-39	2N2924 0-16	2N3706 0-10	2N5904 0-77
AC167 0-22	AS126 0-28	BC179 0-21	BD205 0-88	BF288 0-24	OC81D 0-17	2N706 0-09	2N2925 0-16	2N3707 0-12	2N5905 0-93
AC168 0-27	AS127 0-33	BC180 0-27	BD206 0-88	BF290 0-22	OC82 0-17	2N706A 0-10	2N2926 (C)	2N3708 0-08	2N5906 0-93
AC169 0-16	AS128 0-28	BC181 0-27	BD207 0-105	BF291 0-22	OC82D 0-17	2N708 0-13	2N2926 (V)	2N3709 0-10	2N5907 0-93
AC176 0-22	AS129 0-28	BC182 0-11	BD208 0-105	BF292 0-22	OC83 0-22	2N711 0-33	2N2926 (Y)	2N3710 0-10	2N5914 0-62
AC177 0-27	AS130 0-28	BC183 0-11	BD209 0-110	BF293 0-22	OC84 0-27	2N712 0-38	2N2926 (Z)	2N3711 0-10	2N5914 0-62
AC178 0-27	AS131 0-28	BC183 0-11	BD210 0-110	BF294 0-22	OC89 0-22	2N718 0-33	2N2926 (R)	2N3712 0-10	2N5914 0-62
AC179 0-31	AS132 0-28	BC183L 0-11	BF117 0-50	H8X19 0-17	OC140 0-22	2N718A 0-55	2N2926 (S)	2N3713 0-10	2N5914 0-62
AC180 0-19	AS133 0-28	BC184 0-13	BF118 0-77	H8X20 0-17	OC169 0-28	2N726 0-31	2N2926 (T)	2N3714 0-10	2N5914 0-62
AC180K 0-22	AS134 0-28	BC184 0-13	BF119 0-77	H8Y25 0-17	OC170 0-28	2N727 0-31	2N2926 (U)	2N3715 0-10	2N5914 0-62
AC181 0-19	AS135 0-28	BC184L 0-31	BF121 0-50	H8Y26 0-17	OC171 0-28	2N743 0-22	2N2926 (V)	2N3716 0-10	2N5914 0-62
AC181K 0-22	AS136 0-28	BC187 0-31	BF123 0-55	H8Y27 0-17	OC200 0-28	2N744 0-22	2N2926 (W)	2N3717 0-10	2N5914 0-62
AC187 0-24	AS137 0-28	BC207 0-12	BF125 0-60	H8Y28 0-17	OC201 0-31	2N744 0-22	2N2926 (X)	2N3718 0-10	2N5914 0-62
AC187K 0-24	AS138 0-28	BC207 0-12	BF125 0-60	H8Y29 0-17	OC202 0-31	2N744 0-22	2N2926 (Y)	2N3719 0-10	2N5914 0-62
AC188 0-24	BC107 0-10	BC209 0-13	BF125 0-61	H8Y30 0-20	OC203 0-28	2N744 0-22	2N2926 (Z)	2N3720 0-10	2N5914 0-62
AC188K 0-22	BC108 0-10	BC212L 0-12	BF125 0-61	H8Y39 0-20	OC204 0-28	2N744 0-22	2N2926 (A)	2N3721 0-10	2N5914 0-62
AC197 0-28	BC109 0-11	BC213L 0-12	BF154 0-50	H8Y40 0-31	OC205 0-39	2N1131 0-22	2N2926 (B)	2N3722 0-10	2N5914 0-62
AC198 0-22	BC113 0-11	BC214L 0-16	BF155 0-77	H8Y41 0-31	OC309 0-44	2N1132 0-24	2N2926 (C)	2N3723 0-10	2N5914 0-62
AC199 0-22	BC114 0-17	BC225 0-28	BF156 0-53	H8Y50 0-14	OC71 0-48	2N1302 0-16	2N2926 (D)	2N3724 0-10	2N5914 0-62
AC199 0-22	BC115 0-17	BC226 0-28	BF157 0-61	H8Y56A 0-14	ORP12 0-48	2N1303 0-16	2N2926 (E)	2N3725 0-10	2N5914 0-62
AC199 0-22	BC116 0-17	BC227 0-27	BF158 0-61	3Aa165 2-20	ORP13 0-48	2N1304 0-16	2N2926 (F)	2N3726 0-10	2N5914 0-62
AC199 0-22	BC117 0-17	BC231 0-29	BF159 0-66	3Aa166 2-20	ORP14 0-48	2N1305 0-19	2N2926 (G)	2N3727 0-10	2N5914 0-62
AC199 0-22	BC118 0-11	BCY32 0-33	BF160 0-44	C400 0-33	P346A 0-22	2N1306 0-23	2N2926 (H)	2N3728 0-10	2N5914 0-62
AC199 0-22	BC119 0-33	BCY33 0-24	BF162 0-44	C407 0-28	P397 0-46	2N1307 0-23	2N2926 (I)	2N3729 0-10	2N5914 0-62
AC199 0-22	BC120 0-88	BCY34 0-28	BF163 0-44	C424 0-22	ST140 0-14	2N1308 0-26	2N2926 (J)	2N3730 0-10	2N5914 0-62
AC199 0-22	BC125 0-13	BCY70 0-16	BF164 0-44	C425 0-55	ST141 0-19	2N1309 0-26	2N2926 (K)	2N3731 0-10	2N5914 0-62
AC199 0-22	BC126 0-20	BCY71 0-20	BF165 0-44	C426 0-39	T1843 0-33	2N1613 0-22	2N2926 (L)	2N3732 0-10	2N5914 0-62
AC199 0-22	BC132 0-13	BCY72 0-16	BF167 0-24	C428 0-22	U746 0-30	2N1711 0-22	2N2926 (M)	2N3733 0-10	2N5914 0-62
AC199 0-22	BC134 0-20	BCZ10 0-22	BF173 0-24	C441 0-33	2G301 0-31	2N1819 0-35	2N2926 (N)	2N3734 0-10	2N5914 0-62
AC199 0-22	BC135 0-13	BCZ11 0-28	BF176 0-33	C442 0-33	2G302 0-21	2N1890 0-50	2N2926 (O)	2N3735 0-10	2N5914 0-62
AC199 0-22	BC136 0-17	BCZ12 0-28	BF177 0-39	C444 0-39	2G303 0-21	2N1893 0-41	2N2926 (P)	2N3736 0-10	2N5914 0-62
AC199 0-22	BC137 0-17	BD121 0-66	BF178 0-33	C450 0-24	2G304 0-27	2N2147 0-79	2N2926 (Q)	2N3737 0-10	2N5914 0-62
AC199 0-22	BC139 0-44	BD123 0-72	BF179 0-33	MAT100 0-21	2G305 0-44	2N2148 0-63	2N2926 (R)	2N3738 0-10	2N5914 0-62
AD130 0-42	BC140 0-33	BD124 0-66	BF180 0-33	MAT101 0-22	2G308 0-39	2N2160 0-66	2N2926 (S)	2N3739 0-10	2N5914 0-62
AD140 0-53	BC141 0-33	BD125 0-55	BF181 0-33	MAT120 0-21	2G309 0-39	2N2162 0-39	2N2926 (T)	2N3740 0-10	2N5914 0-62
AD142 0-33	BC142 0-33	BD126 0-44	BF182 0-44	MAT121 0-22	2G339 0-22	2N2163 0-39	2N2926 (U)	2N3741 0-10	2N5914 0-62
AD143 0-42	BC143 0-33	BD133 0-72	BF183 0-44	MAT122 0-22	2G339A 0-22	2N2194 0-39	2N2926 (V)	2N3742 0-10	2N5914 0-62
AD149 0-55	BC145 0-50	BD135 0-44	BF184 0-28	MAT123 0-22	2G344 0-20	2N2217 0-24	2N2926 (W)	2N3743 0-10	2N5914 0-62
AD161 0-37	BC147 0-11	BD136 0-44	BF185 0-33	MAT124 0-22	2G345 0-18	2N2218 0-24	2N2926 (X)	2N3744 0-10	2N5914 0-62

DIODES AND RECTIFIERS

AA119 0-09	BY133 0-23	OA10 0-39
AA130 0-08	BY164 0-55	OA47 0-08
AA129 0-09	BYX38/39	OA70 0-08
AA30 0-10	0-46	OA79 0-08
AAZ13 0-11	BYZ10 0-39	OA81 0-08
BA100 0-11	BYZ11 0-33	OA85 0-10
BA116 0-23	BYZ12 0-33	OA90 0-07
BA126 0-24	BYZ13 0-28	OA91 0-07
BA145 0-16	BYZ16 0-44	OA95 0-08
BA154 0-13	BYZ17 0-39	OA200 0-07
BA155 0-16	BYZ18 0-39	OA202 0-08
BA156 0-15	BYZ19 0-31	SD10 0-06
BY100 0-17	CG62	SD19 0-08
BY101 0-13	(OA91 Eq.)	IN34 0-08
BY105 0-18	0-08	IN34A 0-08
BY114 0-13	CG65-1	IN914 0-07
BY126 0-18	(OA70-OA79)	IN916 0-07
BY127 0-17	0-07	IN414B 0-07
BY128 0-17	OA5	18021 0-11
BY130 0-18	OA58L	18951 0-07

Cut these 3 pages out and keep for reference

NEW COMPONENT PAK BARGAINS

Pak No.	Qty.	Description	Price
C 1	250	Resistors mixed values approx. (count by weight)	0-55
C 2	200	Capacitors mixed values approx. (count by weight)	0-55
C 3	50	Precision Resistors 1% mixed values	0-55
C 4	75	1/4 W Resistors mixed preferred values	0-55
C 5	5	Pieces assorted Ferrite Rods	0-55
C 6	2	Tuning Gangs, MW/LW VHF	0-55
C 7	1	Pack Wire 50 meters assorted colours	0-55
C 8	10	Reed Switches	0-55
C 9	3	Micro Switches	0-55
C10	15	Assorted Pots & Pre-Sets	0-55
C11	5	Jack Sockets 3 x 3.5m 2 x Standard Switch Types	0-55
C12	40	Paper Condensers preferred types mixed values	0-55
C13	20	Electrolytics Trans. types	0-55
C14	1	Pack assorted Hardware - Nuts/Bolts, Gromets, etc.	0-55
C15	4	Mains Slide Switches, full POINT	0-55
C16	20	Assorted Tag Strips & Panels	0-55
C17	10	Assorted Control Knobs	0-55
C18	4	Rotary Wave Change Switches	0-55
C19	3	Relays 6-24V Operating	0-55
C20	4	Sheets Copper Laminated approx. 10m x 7in	0-50

Please add 10p post and packing on all component packs, plus a further 10p on pack Nos. C1, C2, C19 and C20.

The largest selection

NEW LOW PRICED TESTED S.C.R.'S

	PIV					
	50	100	200	400	600	800
1A TO5	0-26	0-28	0-34	0-48	0-59	0-70
3A TO66	0-28	0-37	0-41	0-52	0-63	0-77
5A TO66	0-34	0-62	0-64	0-82	0-75	0-88
5A TO64	0-34	0-52	0-54	0-63	0-75	0-88
7A TO48	0-52	0-55	0-63	0-74	0-85	0-99
10A TO48	0-56	0-64	0-67	0-83	1-07	1-32
16A TO48	0-59	0-70	0-83	1-03	1-38	1-65
30A TO48	1-27	1-54	1-78	1-83	—	4-40

SIL. RECTS. TESTED

	PIV					
	300mA	750mA	1A	1.5A	3A	10A
DO7	SO16	Plastics	SO16	SO10	SO10	SO32A
50-0-04	0-06	0-06	0-08	0-16	0-23	0-66
100-0-04	0-07	0-08	0-15	0-18	0-28	0-83
200-0-06	0-10	0-07	0-16	0-22	0-27	1-10
400-0-07	0-15	0-08	0-22	0-30	0-41	1-38
600-0-09	0-18	0-11	0-26	0-38	0-50	2-05
800-0-11	0-19	0-12	0-28	0-41	0-61	2-20
1000-0-12	0-30	0-16	0-33	0-51	0-70	2-75
1200-0-12	0-37	—	0-42	0-63	0-83	—

TRIACS

	2A	6A	10A
TO-9	TO-66	TO-48	
50p	5p	6p	
100V	33	55	82
200V	55	66	89
400V	77	83	121

DIACS

FOR USE WITH TRIACS
BR100 (1032) 41p each

FREE

One 50p Pak of your own choice free with orders valued £4 or over.

BRAND NEW TEXAS GERM. TRANSISTORS

Pak No.	Eqvt
T1	8 2K3713 OC71
T2	8 1K374 OC75
T3	8 1K1216 OC81D
T4	8 2K381T OC81
T5	8 2K382T OC82
T6	8 2K344H OC44
T7	8 2K343H OC43
T8	8 2K378 OC78
T9	8 2K399A 2N1302
T10	8 2G417 AF117

All 55p each pak

2N2060 NPN SIL DUAL TRANS. CODE D1699 TEXAS. Our price 28p each.

120 VCB NIXIE DRIVER TRANSISTOR. Sim. BSS21 & C407. 2N1893 FULLY TESTED AND CODED ND 120. 1-24 19p each. TO-5 N.P.N. 25 up 17p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Eqvt. ZTX300 8p each. Any Quantity.

POWER TRANS BONANZA!

PRICE	1-24	25-99	100 up
	47p each	44p each	40p each

SILICON High Voltage 250V NPN TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded R 2400 VCB0 250/VE00 100/IC 6A/30 Watts. HFE type 20/TI 6M/HZ. OUR PRICE EACH:

PRICE	1-24	25-99	100 up
	55p	60p	44p

AD161/162 PNP M/P COMP GERM TRANS. OUR LOWEST PRICE OF 60p PER PAIR

ZENER DIODES

4000W (10-7 Case), range 2-33V, 15p each
1.5W (Top-Hat), range 2-33V, 20p each
10W (SO-10 Stud), range 2-33V, 33p each

10 amp POTTED BRIDGE RECTIFIER on heat sink. 100PIV. 99p each

NEW LINE Plastic Encapsulated 2 Amp. BRIDGE RECTS. 50V RMS 35p each
100V RMS 41p each
400V RMS 51p each
Size 15mm x 6mm.

UNIJUNCTION TRANSISTORS

Direct replacement for T1843 and BEN3000 also electrically equivalent to 2N2646 435. 1-24 30p each, 25-99 28p each, 100+ 22p each.

CADMIUM CELLS

ORP12 48p
ORP60, ORP61 44p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8. BSY-27/28/85A. All usable devices to open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

	20	For	5-55
	50	For	1-10
	100	For	1-92
	500	For	8-25
	1000	For	14-30

SIL. G.P. DIODES 4p
300mW 30 0-55
40PIV(Min.) 100 1-85
Sub-Min. 500 5-50
Full Tested 1,000 9-90
Ideal for Organ Builders.

2N3055 115 WATT SIL POWER NPN 55p EACH

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX STOCK. SEND FOR FREE LIST.

SILICON 50 WATTS MATCHED NPN/PNP BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new. VCB0 100/VE00 50/IC 10A. HFE type 100/TI 3M/HZ. OUR PRICE PER PAIR: 1-24 pre: 86p 25-99 pre: 61p 100 pre: 55p

KING OF THE PAKS Unequalled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U 1	120 Glass Sub-Min. General Purpose Germanium Diodes	0-55
U 2	60 Mixed Germanium Transistors AF/RF	0-55
U 3	75 Germanium Gold Bonded Sub-Min. like OA5, OA47	0-55
U 4	40 Germanium Transistors like OC81, AC128	0-55
U 5	60 200mA Sub-Min. Silicon Diodes	0-55
U 6	30 Sil. Planar Trans. NPN like 8BY95A, 2N706	0-55
U 7	16 Sil. Rectifiers TOP-HAT 750mA VLTG. RANGE up to 1000	0-55
U 8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	0-55
U 9	20 Mixed Voltages, 1 Watt Zener Diodes	0-55
U10	20 BAY50 charge storage Diodes DO-7 Glass	0-55
U11	25 PNP Sil. Planar Trans. TO-5 like 2N1132, 2N2904	0-55
U12	12 Silicon Rectifiers Epoxy 500mA up to 800 PIV	0-55
U13	30 PNP-NPN Sil. Transistors OC200 & 2S 104	0-55
U14	150 Mixed Silicon and Germanium Diodes	0-55
U15	25 NPN Sil. Planar Trans. TO-5 like BFY51, 2N697	0-55
U16	10 3 Amp Silicon Rectifiers Stud Type up to 1000PIV	0-55
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	0-55
U18	8 6 Amp Silicon Rectifiers BY213 Type up to 600 PIV	0-55
U19	25 Silicon NPN Transistors like BC108	0-55
U20	12 1.5 Amp Silicon Rectifiers Top Hat up to 1000 PIV	0-55
U21	30 AF. Germanium Alloy Transistors 2G300 Series & OC71	0-55
U22	30 MADT's like MHz Series PNP Transistors	0-55
U23	20 Germanium 1 Amp Rectifiers (GJM Series) up to 300 PIV	0-55
U24	25 300MHz NPN Silicon Transistors 2N708, 8BY27	0-55
U25	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	0-55
U26	12 NPN Germanium AF Transistors TO-1 like AC127	0-50
U27	10 1 Amp SCR's TO-5 can, up to 600 PIV CRS1/25-600	1-15
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	0-55
U31	20 Silicon Planar Plastic NPN Trans. Low Noise Amp 2N3707	0-55
U32	25 Zener Diodes 400mW DO-7 case 3-18 volts mixed	0-55
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	0-55
U34	30 Silicon PNP Alloy Trans. TO-5 BCY26 2S302/4	0-55
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	0-55
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	0-55
U37	30 Silicon Alloy Transistors SO-2 PNP OC200, 28322	0-55
U38	20 Fast Switching Silicon Trans. NPN 400MHz 2N3011	0-66
U39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	0-55
U40	10 Dual Transistors 6 lead TO-5 2N2960	0-55
U41	25 RF Germanium Transistors TO-5, OC45, NKT72	0-55
U42	10 VHF Germanium PNP Transistors TO-1 NKT667, AF117	0-55
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	0-55
U44	20 Sil. Trans. Plastic TO-5 BC115/NPN	0-55
U45	7 3A SCR. TO66 up to 600PIV	1-10

Code Nos. mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to BP x 25 and P21. BRAND NEW. Full data available. Fully guaranteed. Qty: 1-24 25-99 100 up Price each 69p 44p 38p

F.E.T.'S			
2N3819	31p	2N5458	35p
2N3820	55p	2N5459	44p
2N3821	34p	BFM10	65p
2N3823	31p	MPP10G	41p

NEW 6TH EDITION TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 99p each.

QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price
Q 1	20 Red spot transistors pnp	0-55
Q 2	16 White spot R.F. transistors pnp	0-55
Q 3	4 OC77 type transistors	0-55
Q 4	6 Matched transistors OC44/45/91/81D	0-55
Q 5	4 OC75 transistors	0-55
Q 6	5 OC72 transistors	0-55
Q 7	4 AC128 transistors pnp high gain	0-55
Q 8	4 AC129 transistors pnp	0-55
Q 9	7 OC81 type transistors	0-55
Q10	7 OC71 type transistors	0-55
Q11	2 AC127/128 Complementary pairs pnp/npn	0-55
Q12	3 AF116 type transistors	0-55
Q13	3 AF117 type transistors	0-55
Q14	3 OC171 H.F. type transistors	0-55
Q15	7 2N2926 Sil. Epoxy transistors mixed colours	0-55
Q16	2 GET880 low noise Germanium transistors	0-55
Q17	5 npn 2 x 8T.141 & 3 x 8T.140	0-55
Q18	4 MADT'S 2 x MAT 100 & 2 x MAT 120	0-55
Q19	3 MADT'S 2 x MAT 101 & 1 x MAT 121	0-55
Q20	4 OC44 Germanium transistors A.F.	0-55
Q21	4 AC127 npn Germanium transistors	0-55
Q22	20 NKT transistors A.F. R.F. coded.	0-55
Q23	10 OA292 Silicon diodes auto-min.	0-55
Q24	8 OA81 diodes	0-55
Q25	15 IN914 Silicon diodes 75PIV 75mA	0-55
Q26	8 6 Amp Germanium diodes sub-min IN699	0-55
Q27	2 10A 600 PIV Silicon rectifiers B18425R	0-55
Q28	2 Silicon power rectifiers BY213	0-55
Q29	4 Silicon transistors 2 x 2N690, 1 x 2N697, 1 x 2N698	0-55
Q30	7 Silicon switch transistors 2N706 npn	0-55
Q31	6 Silicon switch transistors 2N708, npn	0-55
Q32	3 pnp Silicon transistors 2 x 2N1131, 1 x 2N1132	0-55
Q33	3 Silicon npn transistors 2N1711	0-55
Q34	7 Silicon npn transistors 2N2369, 300MHz (code P397)	0-55
Q35	3 Silicon pnp TO-5, 1 x 2N2904 & 1 x 2N2905	0-55
Q36	7 2N3646 TO-18 plastic 300MHz npn	0-55
Q37	3 2N3053 npn Silicon transistors	0-55
Q38	7 pnp transistors 4 x 2N3703, 3 x 2N3702	0-55

ELECTRONIC SLIDE-RULE The MK Slide Rule, designed to simplify Electronic calculations features the following scales: Conversion of Frequency and Wavelength. Calculation of L, C and of Tuned Circuit. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and % Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 2cm x 4cm. Complete with case and instructions. Price each: £3-60

INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price
UIC00	= 12 x 7400	0-55
UIC01	= 12 x 7401	0-55
UIC02	= 12 x 7402	0-55
UIC03	= 12 x 7403	0-55
UIC04	= 12 x 7404	0-55
UIC05	= 12 x 7405	0-55
UIC06	= 8 x 7406	0-55
UIC07	= 8 x 7407	0-55
UIC08	= 12 x 7410	0-55
UIC13	= 8 x 7413	0-55
UIC20	= 12 x 7420	0-55
UIC30	= 12 x 7430	0-55
UIC40	= 12 x 7440	0-55
UIC41	= 8 x 7441	0-55
UIC42	= 8 x 7442	0-55
UIC43	= 8 x 7443	0-55
UIC44	= 5 x 7444	0-55
UIC45	= 3 x 7445	0-55

Pak No.	Contents	Price
UIC46	= 5 x 7446	0-55
UIC47	= 5 x 7447	0-55
UIC48	= 5 x 7448	0-55
UIC50	= 12 x 7450	0-55
UIC51	= 12 x 7451	0-55
UIC53	= 12 x 7453	0-55
UIC54	= 12 x 7454	0-55
UIC60	= 8 x 7460	0-55
UIC68	= 12 x 7460	0-55
UIC70	= 8 x 7470	0-55
UIC72	= 8 x 7472	0-55
UIC73	= 8 x 7473	0-55
UIC74	= 8 x 7474	0-55
UIC75	= 8 x 7475	0-55
UIC76	= 8 x 7476	0-55
UIC80	= 8 x 7480	0-55
UIC81	= 5 x 7481	0-55
UIC82	= 5 x 7482	0-55
UIC83	= 5 x 7483	0-55

Pak No.	Contents	Price
UIC86	= 5 x 7486	0-55
UIC90	= 5 x 7490	0-55
UIC91	= 5 x 7491	0-55
UIC92	= 5 x 7492	0-55
UIC93	= 5 x 7493	0-55
UIC94	= 5 x 7494	0-55
UIC95	= 5 x 7495	0-55
UIC96	= 5 x 7496	0-55
UIC00	= 5 x 7400	0-55
UIC121	= 5 x 7412	0-55
UIC141	= 5 x 7414	0-55
UIC151	= 5 x 7415	0-55
UIC154	= 5 x 7415	0-55
UIC193	= 5 x 74193	0-55
UIC199	= 5 x 74199	0-55

-the lowest prices!

74 Series T.T.L. I.C.'s

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS




		1	25	100+			1	25	100+
SN7400	0-17	0-16	0-13	0-13	SN7486	0-35	0-34	0-33	0-33
SN7401	0-17	0-16	0-13	0-13	SN7489	6-05	5-78	5-50	0-84
SN7402	0-17	0-16	0-13	0-13	SN7490	0-74	0-71	0-64	0-64
SN7403	0-17	0-16	0-13	0-13	SN7491	1-10	1-04	0-97	0-64
SN7404	0-17	0-16	0-13	0-13	SN7492	0-74	0-71	0-64	0-64
SN7405	0-17	0-16	0-13	0-13	SN7493	0-74	0-71	0-64	0-64
SN7406	0-39	0-34	0-31	0-31	SN7494	0-85	0-82	0-75	0-64
SN7407	0-39	0-34	0-31	0-31	SN7495	0-35	0-82	0-75	0-64
SN7408	0-20	0-14	0-18	0-18	SN7496	0-86	0-83	0-86	0-86
SN7409	0-20	0-19	0-18	0-18	SN7400	1-82	1-76	1-71	1-71
SN7410	0-17	0-16	0-13	0-13	SN74104	1-07	1-04	0-97	0-97
SN7411	0-29	0-24	0-26	0-26	SN74105	1-07	1-04	0-97	0-97
SN7412	0-39	0-34	0-31	0-31	SN74107	0-44	0-42	0-40	0-40
SN7413	0-32	0-29	0-27	0-27	SN74110	0-51	0-50	0-55	0-55
SN7416	0-48	0-44	0-42	0-42	SN74111	1-38	1-27	1-21	1-21
SN7417	0-48	0-44	0-42	0-42	SN74118	1-10	1-05	0-99	0-99
SN7420	0-17	0-16	0-13	0-13	SN74119	1-40	1-38	1-21	1-21
SN7422	0-55	0-53	0-50	0-50	SN74121	0-44	0-41	0-38	0-38
SN7423	0-55	0-53	0-50	0-50	SN74122	1-54	1-43	1-32	1-32
SN7425	0-55	0-53	0-50	0-50	SN74123	3-08	2-97	2-86	2-86
SN7426	0-50	0-46	0-44	0-44	SN74141	0-74	0-71	0-64	0-64
SN7427	0-50	0-46	0-44	0-44	SN74145	1-65	1-54	1-43	1-43
SN7428	0-77	0-72	0-68	0-68	SN74150	3-30	2-97	2-75	2-75
SN7430	0-17	0-16	0-13	0-13	SN74151	1-10	1-05	0-99	0-99
SN7432	0-50	0-46	0-44	0-44	SN74133	1-32	1-21	1-05	1-05
SN7433	0-88	0-83	0-77	0-77	SN74134	1-08	1-07	1-05	1-05
SN7437	0-71	0-68	0-66	0-66	SN74153	1-54	1-43	1-32	1-32
SN7438	0-71	0-68	0-66	0-66	SN74156	1-54	1-43	1-32	1-32
SN7440	0-17	0-16	0-13	0-13	SN74157	2-09	1-98	1-87	1-87
SN7441	0-74	0-71	0-64	0-64	SN74160	1-98	1-87	1-76	1-76
SN7442	0-74	0-71	0-64	0-64	SN74161	1-98	1-87	1-76	1-76
SN7443	1-43	1-38	1-32	1-32	SN74162	4-40	4-13	3-85	3-85
SN7444	1-43	1-38	1-32	1-32	SN74163	4-40	4-13	3-85	3-85
SN7445	1-98	1-95	1-93	1-93	SN74164	2-42	2-37	2-31	2-31
SN7446	1-07	1-04	0-97	0-97	SN74165	2-48	2-42	2-37	2-37
SN7447	1-10	1-07	1-05	1-05	SN74166	3-85	3-58	3-30	3-30
SN7448	1-10	1-07	1-05	1-05	SN74174	2-53	2-42	2-31	2-31
SN7460	0-17	0-16	0-13	0-13	SN74175	1-76	1-65	1-54	1-54
SN7451	0-17	0-16	0-13	0-13	SN74176	2-75	2-64	2-53	2-53
SN7453	0-17	0-16	0-13	0-13	SN74177	2-75	2-64	2-53	2-53
SN7454	0-17	0-16	0-13	0-13	SN74178	2-75	2-64	2-53	2-53
SN7459	0-17	0-16	0-13	0-13	SN74181	2-20	1-98	1-76	1-76
SN7470	0-32	0-29	0-27	0-27	SN74182	2-20	1-98	1-76	1-76
SN7472	0-32	0-29	0-27	0-27	SN74184	3-85	3-58	3-30	3-30
SN7473	0-41	0-39	0-36	0-36	SN74190	2-15	2-09	2-04	2-04
SN7474	0-41	0-39	0-36	0-36	SN74191	2-20	2-04	1-98	1-98
SN7475	0-50	0-48	0-46	0-46	SN74192	2-15	2-09	2-04	2-04
SN7476	0-44	0-43	0-43	0-43	SN74193	2-09	1-98	1-83	1-83
SN7480	0-74	0-71	0-64	0-64	SN74194	2-97	2-86	2-75	2-75
SN7481	1-32	1-27	1-21	1-21	SN74195	2-20	2-09	1-98	1-98
SN7482	0-96	0-95	0-94	0-94	SN74196	1-98	1-87	1-76	1-76
SN7483	1-21	1-16	1-05	1-05	SN74197	1-98	1-87	1-76	1-76
SN7484	1-10	1-05	0-99	0-99	SN74198	6-05	5-50	4-85	4-85
SN7485	3-96	3-85	3-74	3-74	SN74199	6-05	5-50	4-85	4-85

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0.1% DISTORTION!
HI-FI AUDIO AMPLIFIER

THE AL50

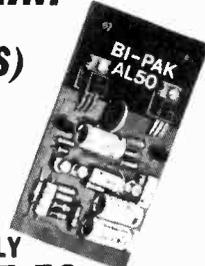

- * Frequency Response 15Hz to 100,000—1dB.
 - * Load—3, 4, 8 or 16 ohms.
 - * Distortion—better than 0.1% at 1KHz.
 - * Signal to noise ratio 80dB.
- ONLY £3.58 each**
- * Supply voltage 10-35 Volts.
 - * Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and ALSO was conceived to fill the need for all your A.F. amplification needs.
FULLY BUILT—TESTED—GUARANTEED.

STABILISED POWER MODULE SPM80



AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Main Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 68mm x 105mm x 30mm.
These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including—Disc Systems, Public Address, Intercom Units, etc. Handbook available, 10p. **PRICE £3.25**

TRANSFORMER BMT80 £2.15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.
Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

- SPECIFICATION**
- Frequency Response 20Hz - 20kHz ± 1dB
 - Harmonic Distortion better than 0.1%
 - Inputs: 1. Tape Head 1.25mV into 50K Ω
 - 2. Radio, Tuner 35mV into 50K Ω
 - 3. Magnetic P.U. 1.5mV into 50K Ω
- All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB from 20Hz to 20kHz.
- Bass Control ± 15dB at 20Hz
 - Treble Control ± 15dB at 20kHz
 - Filters: Rumble (High Pass) 100Hz
 - Scratch (Low Pass) 8kHz
 - Signal/Noise Ratio better than -65dB
 - Input overload +26dB
 - Supply +35 volts at 20mA
 - Dimensions 292mm x 82mm x 35mm



ONLY £13.15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25.30 FREE p. & p.

LINEAR I.C.'s - FULL SPEC.

Type No.	1-24	25-99	100+
BP201C-SL201C	0.70	0.59	0.50
BP710C-SL701C	0.70	0.55	0.50
BP702C-SL702C	0.70	0.55	0.50
BP702-72702	0.59	0.50	0.44
BP709-72709	0.40	0.38	0.33
BP709P-μA709C	0.40	0.38	0.33
BP710-72710	0.40	0.46	0.44
BP711-μA711	0.40	0.48	0.44
BP741-72741	0.55	0.50	0.45
μA703C	0.81	0.29	0.27
TAA263	0.77	0.66	0.61
TAA293	0.89	0.83	0.77
TAA350	1.87	1.74	1.65
EAL1000	2.90		

ROCK BOTTOM PRICES LOGIC DTL 830 Series I.C.'s

Type No.	1-24	25-99	100 up
BP930	0-13	0-12	0-11
BP932	0-14	0-13	0-12
BP933	0-14	0-13	0-12
BP935	0-14	0-13	0-12
BP936	0-14	0-13	0-12
BP944	0-14	0-13	0-12
BP945	0-28	0-27	0-24
BP946	0-13	0-12	0-11
BP948	0-28	0-27	0-24
BP951	0-72	0-66	0-61
BP962	0-13	0-12	0-11
BP9003	0-44	0-42	0-39
BP9004	0-44	0-42	0-39
BP9087	0-44	0-42	0-39
BP9099	0-44	0-42	0-39

NUMERICAL INDICATOR TUBES



MODEL	CD66	GR116	3015F Minitron	All indicators 0-9 + Decimal point. All side viewing. Full data for all types available on request.
Anode Voltage (Vdc)	170min	175min	5	
Cathode Current (mA)	2.3	14	8	
Numerical Height (mm)	16	13	9	
Tube Height (mm)	47	32	22	
Tube Diameter (mm)	19	13	12 wide	
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47	
PRICE EACH	£1.87	£1.70	£1.50	

BTL MICROLOGIC CIRCUITS

	1-24	25-99	100 up
Epoxy TO-5 case	38p	36p	29p
μL900 Buffer	38p	36p	29p
μL914 Dual 2/1p gate	38p	36p	29p
μL923 J-K flip-flop	55p	51p	49p

Date and Circuits Booklet for IC's Price 8p.

DUAL IN LINE SOCKETS

(14 & 16 Lead)	1-24	25-99	100+
TS014	0-33	0-30	0-28
TS016 16 pin type	0-34	0-35	0-33
BP814 14 pin type (low cost)	0-17	0-15	0-12
BP816 16 pin type (low cost)	0-18	0-16	0-13

BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 10p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

MAPLIN ELECTRONIC SUPPLIES

★RETURN OF POST SERVICE



1973 CATALOGUE

3rd EDITION NOW AVAILABLE

SEND NOW FOR YOUR COPY OF THIS BEAUTIFULLY PRODUCED FULLY ILLUSTRATED CATALOGUE AND WE WILL FORWARD IT TO YOU BY RETURN OF POST. PLEASE SEND 9p IN STAMPS. EVERYTHING GUARANTEED BRAND NEW MARKED BY THE MANUFACTURER

MAPLIN: Projected site of London's third airport.

RESISTORS
Carbon film 5% from 1Ω to 1MΩ, 10% from 1.2MΩ to 10MΩ. E12 series, 1W 1p; 1W 1.2p; Metal Oxide 2% 10Ω to 1MΩ. E24 series 1W 4p. Also 1W, 2½W, 5W, 10W types stocked.

POTENTIOMETERS
Miniature carbon track with ¼in. spindles. 5kΩ, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1MΩ, 2MΩ. Log or lin (and 1kΩ lin), 12p. Log or lin with switch 23p. Dual gang less switch 38p.

P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We shall be stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboard.

Send S.A.E. NOW for our detailed price lists.

YOU SIMPLY MUST SEE OUR PRICES!

8 pin DIL OP AMP
741C 36p.
14 pin 741C 45p.

McMURDO
Socket, RS8, 52p
Plug, RP8, 36p.
(As used in P.E. Sound Synthesiser.)

Diodes IN914 4p.
OA91 6p. BAX 13 5p.
IN4001 6p. IN4002
6p. IN4003 7p.
IN4004 7p. IN4005
8p. IN4006 8p.
IN4007 9p.

SEMI-CONDUCTORS

We stock a large range of transistors and I.C.s, for details please see our catalogue. LOOK! These popular devices at amazingly low prices. BC107/8/9 10p each. BC169C 12p. BFY51 16p. TIS43 (SS43) 28p. 2N706 10p. 2N2646 45p. 2N3055 49p. 2N 3819 24p.

7 SEGMENT DISPLAY
Minitron 3015F
£1.98 each.

DIN PLUGS. 3 pin, 9p. 5 pin A (180°), 5 pin B (240°), 10p each.

DIN SOCKETS. 3 pin, 5 pin A, 5 pin B, 7p each.

DIN LOUDSPEAKER. 2 pin plug, 8p. Socket 6p.

JACK PLUGS standard ¼in plastic barrel, 13p. Stereo, 25p. Bright metal barrel, 17p. Stereo, 29p.

JACK SOCKETS standard ¼in open type, 10p. Moulded 2 break, 13p. Moulded stereo 3 break, 18p.

ROTARY SWITCHES

Adjustable stop. 1 pole 2-12 way, 2 pole 2-6 way, 3 pole 2-4 way, 4 pole 2-3 way. Only 24p each.

SPECIAL IC. for organ builders. 7 stage frequency divider in one 14 pin DIL package, £2.63 or special price for pack of 12, £25.

Why not ask us to slip a data sheet in with your catalogue.

NUDES!

Clothe those naked projects with our superb instrument cases. We are sole distributors of the

Centurion

range, designed for the professional market, now available to you at special low prices. S.A.E. please for free illustrated leaflet.

HARDWARE

Wide range of nuts and bolts, plated brass and nylon types plus solder tags, shakeproof washers, etc. SOLDER 10 metres of 22 gauge multi-core, 20p. Insulating sleeving 3 sizes, 6 colours.

MISCELLANEOUS

LT700 Eagle sub-miniature O/P transformer 1200/5Ω 200mW max., 35p. Slide switch DPDT, 12p. Miniature push to make non-locking switch 12p. Silicon grease in special dispenser, 20ml, 38p.

SEE OUR CATALOGUE

for details of how you can obtain £1 worth of components.

ABSOLUTELY FREE

V.A.T. Please add 10% V.A.T. to final total. Orders and enquiries for catalogues to **MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex SS6 8LR**

Postage and packing FREE in U.K. But we have to ask you to send a 10p handling charge with order under 50p.



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME :

ADDRESS :

EB93


BLOCK CAPS please

PRINTED CIRCUIT KIT

BUILD 60 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4in x 2½in. (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXION" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Miniature Radio Receivers based on the "Trilexion" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.6in x 0.95in x 0.25in. (11) Wristwatch Radio 1.15in x 0.80in x 0.50in. (12) Ring Radio 0.70in x 0.70in x 0.50in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) Valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Valve Amplifier. (36) Push-Pull Amplifier. (37) Light-Beam Telephone "Photophone". (38) Light-Beam Transmitter. (39) Silent TV Sound Adaptor. (40) Ultrasonic Transmitter. (41) Thyristor Drill Speed Controller. (42) Light Dimmer. (43) L.C. Pre-amplifier. (44) L.C. Amplifier. (45) L.C. Intercom. (46) L.C. Radio. (47) Rhythmic Voice Receiver. (48) Biofeedback Amplifier. (49) Brainwave Detector. (50) Proximity Switch. (51) Laser Projector.

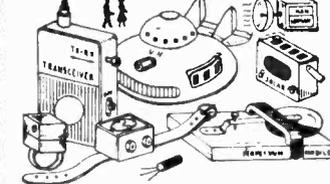Plus 10 Photoelectric Circuits, Simple Alarms, Long Range Alarms, Projector, etc.



EXPERIMENTER'S PRINTED CIRCUIT KIT

70p

Postage & Pack. 10p (UK)

Commonwealth:

SURFACE MAIL 15p

AIR MAIL 60p

Australia, New Zealand, South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXION" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Miniature Radio Receivers based on the "Trilexion" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.6in x 0.95in x 0.25in. (11) Wristwatch Radio 1.15in x 0.80in x 0.50in. (12) Ring Radio 0.70in x 0.70in x 0.50in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P/P Amplifier. (16) Intercom. (17) Valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Valve Amplifier. (36) Push-Pull Amplifier. (37) Light-Beam Telephone "Photophone". (38) Light-Beam Transmitter. (39) Silent TV Sound Adaptor. (40) Ultrasonic Transmitter. (41) Thyristor Drill Speed Controller. (42) Light Dimmer. (43) L.C. Pre-amplifier. (44) L.C. Amplifier. (45) L.C. Intercom. (46) L.C. Radio. (47) Rhythmic Voice Receiver. (48) Biofeedback Amplifier. (49) Brainwave Detector. (50) Proximity Switch. (51) Laser Projector.

YORK ELECTRICS, Mail Order Dept.
335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details and a brief description of all kits and Projects.

Build yourself a TRANSISTOR RADIO

WITH AFTER SALES SERVICE

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND.


Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Fine tone moving coil speaker. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in.

Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).


TOTAL BUILDING COSTS

£9.35

P.P. & INS. 52p
(OVERSEAS P. & P. £1.05)

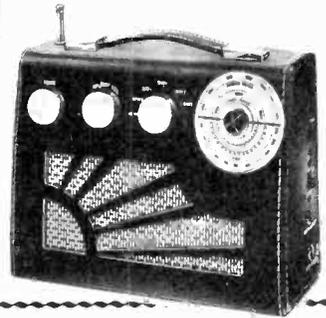

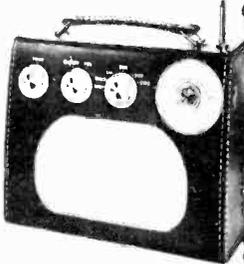
ROAMER EIGHT Mk. I NOW WITH VARIABLE TONE CONTROL



7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£7.68** P.P. & INS. 47p (OVERSEAS P. & P. £1.05)

ROAMER SEVEN Mk. IV

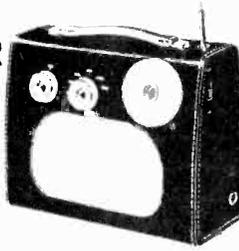


7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra

medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6.58** P.P. & INS. 47p (OVERSEAS P. & P. £1.05)

ROAMER SIX

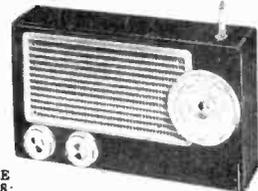


6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER

BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS **£4.38** P.P. & INS. 31p (OVERSEAS P. & P. £1.05)

POCKET FIVE

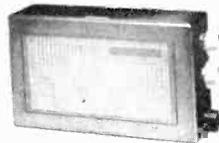

3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2in x 1 1/2in x 3 1/2in. Plans and parts price list 15p (FREE with parts).

TOTAL BUILDING COSTS **£2.50** P.P. & INS. 24p (OVERSEAS P. & P. 65p)

TRANSONA FIVE




5 TRANSISTORS AND 2 DIODES

3 TUNABLE WAVE BANDS: MW, LW AND TRAWLER BAND. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6 1/2in x 4 1/2in x 1 1/2in. Plans and parts price list 15p (FREE with parts).

TOTAL BUILDING COSTS **£2.75** P.P. & INS. 25p (OVERSEAS P. & P. 65p)

TRANS EIGHT

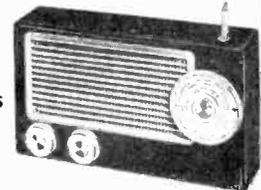

8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 3 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£4.95** P.P. & INS. 33p (OVERSEAS P. & P. £1.05)



"EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC. FROM EASY STAGE DIAGRAM FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

ALL PARTS INCLUDING CASE AND PLANS **£6.05** P.P. & INS. 33p (OVERSEAS P. & P. £1.05)

FULL AFTER SALES SERVICE

★ Callers side entrance "Lavell" Shop
★ Open 10-1, 2.30-4.30 Monday-Friday, 9-12 Saturday
★ PLEASE NOTE: ALL PRICES INCLUDE V.A.T.

RADIO EXCHANGE LTD

61a HIGH ST., BEDFORD MK40 1SA. Tel. 0234 52367
Reg. no. 788372

I enclose £..... please send items marked

ROAMER TEN	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
ROAMER EIGHT	<input type="checkbox"/>	TRANS EIGHT	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>
POCKET FIVE	<input type="checkbox"/>	EDU-KIT	<input type="checkbox"/>

Parts price list and plans for.....

Name.....

Address.....

P.E. 56

Come and listen at the year's most exciting exhibition


Join thousands of Hi-Fi enthusiasts in an atmosphere that will set your ears tingling with excitement. The 1973 Audio Festival and Fair looks like being the best yet – and will run up to and include Sunday. The international giants of the Hi-Fi industry will be there – showing the latest specialist equipment: unit audio, tape recorders (cassette, cartridge and reel-to-reel), loudspeakers, tuners, receivers, amplifiers, radios, tapes and discs. There will be continuous demonstrations in specially constructed Audio Studios – and the Sunday Mirror is giving away £500 worth of equipment as prizes in exciting competitions. Don't miss this great event.

THE 1973 INTERNATIONAL AUDIO FESTIVAL AND FAIR

Sponsored by the Sunday Mirror

OLYMPIA London

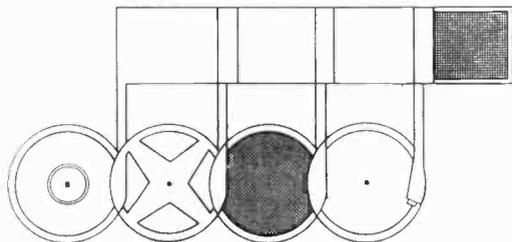Tuesday 23 October to
Sunday 28 October
Weekdays 10 am to 9 pm
Sunday 11 am to 7 pm
Admission 45p



D.I.Y.
ELECTRONIC
ORGAN KITS
AS USED BY
PROFESSIONALS
THROUGHOUT
THE WORLD



★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain, Reverberation, Percussion, Wah Wah, £406.00. ★ Console—2 x 5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain Reverberation, Percussion, 3 Couplers, etc., at £572.55.

ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE, WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT, ELECTRICAL HOUSEHOLD APPLIANCES. PLUS 5 x 10p VOUCHERS.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

YOU ARE WELCOME TO VISIT THE ONLY D.I.Y. ELECTRONIC ORGAN CENTRE IN EUROPE AT 12 BRETT ROAD, HACKNEY, LONDON, E.8. TEL. 01-986 8455

BLACK P.V.C. BOXES

For All Electrical and Special Rigs




Robust Moulding—All Insulated—
Easy to cut and drill—Self Finish
Non Rusting—Self Extinguishing

Length	Width	Depth	Price Each	P. & P. Each
3"	3"	1 1/2"	32p	11p
4"	4"	1 1/2"	38p	13p
4"	4"	2"	41p	14p
6"	3"	1 1/2"	38p	14p
6"	4"	2"	52p	14p

Allow 21 days for delivery—orders over £8 P. & P. free. Quotations given for large quantities. Other depths and larger sizes can be offered, state size required and quantity.

ADAPTABOX

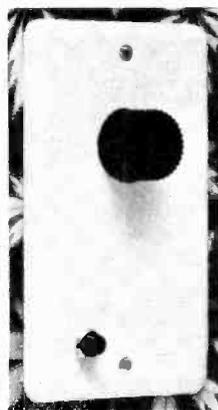Dept. P.E.2, 26 Welby Gardens, Grantham, Lincs. NG31 8BN
Tel.: Grantham (0476) 5821



GAS & SMOKE

COMPLETE parts kit
MAINS OPERATED with
flush or surface box £8.45 plus 20p
P. & P.

Parts below available separately:

TGS Sensor £1.80 plus 10p P. & P.
Transformer £1.50 plus 15p P. & P.
Speaker 50p plus 10p P. & P.

Please add 10% VAT to the above

ELECTROMECH LTD.
Ruckinge, Ashford, Kent TN26 2EF

LARGE STOCKS, ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new and to makers' specifications.

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power	60p
AC153K pnp germanium low power	32p
AC176K npn germanium low power	32p
AD161 npn germanium medium power	42p
AD162 pnp germanium medium power	40p
AF139 pnp germanium UHF	49p

NPN: BC107 13p, BC108 12p, BC109 13p, BC167 11p, BC168 10p, BC169 11p.

PNP: BC177 21p, BC178 19p, BC179 21p, BC257 12p, BC258 11p, BC259 13p.

Standard groupings available.

BD135 npn medium power	37p
BD136 pnp medium power	38p

DIODES

OA90, OA91, OA95, 6p each; OA200, 9p; OA202, 10p.


Other semiconductors: AC128, 17p; AF117, 32p; BFY51, 19p. Full lists and technical data will be found in Catalogue No. 6. See also amendments list.

Send S.A.E. for latest supplement of additional lists and price amendments to our No. 6 Catalogue

ZENER DIODES full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

DIN PLUGS AND SOCKETS

by Hirshmann, 4A rating

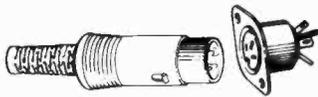


2 way LS —socket 10p, plug 12p
3 way scr.—socket 10p, plug 12p
5 way scr.—socket 11p, plug 15p

TRANSISTOR ACCESSORIES
TO3 cover, 7p; Heat sinks 1°C/W, type 6W1, undrilled, 60p.

SWITCHES

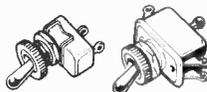1011 SPST toggle, 20p; 409 DPDT toggle, 29p (these are chrome plated, 2.5A rating); 7201 sub-miniature DPDT 250V a.c./2A, 48p.




ROTARY SWITCHES

Radiospares Miniature Mako-switch (in assembly kit form). Shaft, 48p. Waters, MBB-2P5W, 1P11W; BBM1P12W, 2P6W, 3P4W, 4P3W, 6P2W, 32p each.

WAVECHANGE SWITCHES

IP12W, 2P6W, 3P4W, 413W, 24p each.

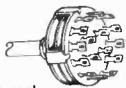

ELECTROLYTIC CAPACITORS

Rated voltage:	3V	6.3V	10V	16V	25V	40V	63V	100V
Capacity μ F	0.47	—	—	—	—	—	10p	7p
1.0	—	—	—	—	—	10p	—	7p
2.2	—	—	—	—	—	—	7p	8p
4.7	—	—	—	10p	—	—	7p	8p
10	—	—	7p	—	7p	—	8p	8p
22	—	—	—	—	—	—	7p	9p
47	7p	—	—	—	—	—	8p	7p
100	8p	7p	7p	7p	7p	9p	11p	19p
220	7p	8p	8p	8p	9p	10p	17p	27p
470	8p	9p	9p	10p	12p	17p	24p	43p
1,000	10p	12p	17p	20p	24p	40p	—	—
2,200	14p	17p	22p	25p	36p	40p	—	—
4,700	25p	28p	37p	41p	54p	—	—	—
10,000	40p	43p	—	—	—	—	—	—

Prices subject to amendment by the manufacturer.

POLYCARBONATE—5% TOLERANCE

250V up to 0.1 μ F: 100V, 0.1 μ F and above.
0.01; 0.012; 0.015; 0.018; 0.022; 0.027; 0.033; 0.047; 0.056; 4p each; 0.068; 0.082; 0.1; 0.12; 0.15; 4p each; 0.18; 0.22; 5p each; 0.27; 0.33; 6p; 0.39; 7p; 0.47; 8p; 0.56; 10p; 0.68; 11p; 1 μ F; 13p. Prices subject to amendment by the manufacturer.

Mintron Digital Counter
Type 3015F. Seven Filament segment indicators to make 0-9 + decimal point. Compatible with standard logic modules, nett £2. Decoder driver type FLL 121T nett £1.36. DIL socket, nett £2.

RESISTORS — 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω —220K Ω	E12	9	8	7.5
C	1/8W	5%	4.7 Ω —470K Ω	E24	1	0.9	0.75 nett
C	1/4W	5%	4.7 Ω —10M Ω	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7 Ω —10M Ω	E24	1-2	1	0.95 nett
C	1W	5%	4.7 Ω —10M Ω	E12	2.5	2	1.6 nett
MO	1/2W	2%	10 Ω —1M Ω	E12	4	3	2 nett
WW	1W	10%	1/20 Ω —0.22 Ω —3.9 Ω	E12	7	7	6
WW	3W	5%	1 Ω —10K Ω	E12	7	7	6
WW	7W	5%	1 Ω —10K Ω	E12	9	9	8

Codes: C = carbon film, high stability, low noise. MO = metal oxide, Electrofil TR5, ultra low noise. WW = wire wound, Plessey.


Values:
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.)

KNOBS

All grub screw fitting for $\frac{1}{4}$ in shafts. Black. For other types —see Catalogue No. 6, p. 54.

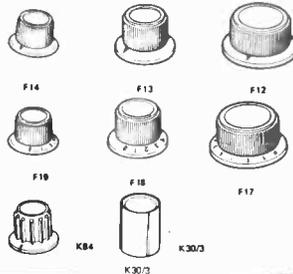F.14 (20mm) pack of 2, 32p; F.13 (26mm) pack of 2, 38p; F.12 (33mm) pack of 2, 40p; F.19 (20mm) pack of 2, 32p; F.18 (26mm) pack of 2, 38p; F.17 (33mm) pack of 2, 40p; K.B.4 (20mm) pack of 4, 40p; K30/3 (17mm) aluminium, 24p each.



POTENTIOMETERS

Rotary, carbon track, double wipe


SINGLE P20 lin. 100 Ω to 2.2M Ω , 12p; P20 log. 4.7K Ω to 2.2M Ω , 12p; P20 log. 4.7K Ω to 2.2M Ω , 12p; Dual gang lin. 4.7K Ω to 2.2M Ω , 42p; Dual log. 4.7K Ω to 2.2M Ω , 42p; Log/antilog, 10K, 22K, 47K, 1M Ω only, 42p; Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.

Only decades of 10, 22 and 47 available in ranges quoted. DUAL CONCENTRIC DP20 in any combination of 20 values, 60p; with switch, 72p.

SLIDER Lin. or log. 10K to 1 meg. in all popular values, each 26p. Control knobs blk./white/red/yel./gr./blue/dk. grey/lt. grey, 5p each.

CARBON SKELETON PRE-SETS

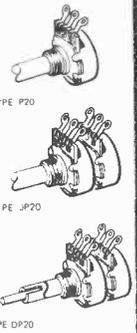Small high quality, PR lin. 100 Ω , 220 Ω , 470 Ω , 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M Ω , 5M, 10M Ω . Vertical or horizontal mounting, 5p each.



TRANSFORMERS—MAINS

MT3 30V/2A plus 4 taps	£2.85
MT103 50V/1A plus 4 taps	£2.35
MT104 50V/2A plus 4 taps	£3.50
MT127 60V/2A plus 4 taps	£3.80
13T05 13V/4A, CT	£1.25
28T05 12+12V, 2-0-2V.	£1.65

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14.90 Plus 60p part cost of carr.

Equaliser Assembly, £2.
Loudspeaker Unic 59RM109, £2.45.
Cabinet Kit (to Baxandall design), £10.45.

DISCOUNTS All items offered for sale in accordance with our stated terms of business, copy of which available on request.

Not allowed on nett price items. 10% on orders for £5 or more. 15% on orders of £15 or more. Prices subject to alteration without prior notice. Prices quoted DO NOT include V.A.T. Orders received from U.K. customers must be accompanied by an additional 10% of the nett value for V.A.T.

Overseas orders are exempt. **POSTAGE AND PACKING FREE** SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost. U.S.A. CUSTOMERS please contact ELECTROVALUE, AMERICA, P.O. BOX 27, Swarthmore, PA 19081.

ELECTROVALUE

(Dept. PE9), 28 ST. JUDE'S ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB

Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 3603

Telex 264475

Eng. Reg. No. 1047789

Registered Office: 28 St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB

You'll hardly be able to believe your ears!

Can you
really get
sound quality
like this for
less than £18?

Yes you can!
with the new

**STEREO
21**



Until now, richly satisfying sound has always cost a richly satisfying price. *But not any more!* For an almost unbelievable £17.95, you can have Stereo 21—audio for the connoisseur.

Whatever your taste in music, you can hear it on STEREO 21 the way its composers heard it in their dreams! Beethoven or Mahler . . . Ellington or Jellyroll Morton . . . Das Nibelung or Jesus Christ Superstar . . . Carols from King's College Chapel or the return of a Beatle . . . everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!

And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience!

Top-quality amplifier, BSR 8 record automatic changer turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit, no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins, all parts supplied including full instructions—all for £17.95 (plus the cost of post and packing if you buy by mail), and—round it all off—a money-back Guarantee if your pleasure in STEREO 21 is not complete!

**Just think—In only a few days
you could be giving your ears
the treat of a lifetime—AND introducing
your envious friends to
STEREO 21!**

Personal shoppers and mail order price

£17.95

Plus £1.50 P&P.

Diamond styli, if required, £1.37 extra



RADIO AND TV COMPONENTS (ACTON) LTD.

21d High Street, Acton, London W3 6NG

323 Edgware Road, London W2

Mail orders to Acton. Terms C.W.O. All enquiries stamped addressed envelope. Goods not despatched outside U.K.

VISCOUNT III— a boost in the output,

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as *value for money!* And that's something you get in abundance with VISCOUNT III. We design it . . . we make it . . . we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back. And the teak finish will harmonise and enhance virtually any style of interior decor!

The heart-stopping timbre of Tom Jones at his most virile . . . the last lingering harmonics of a solo performance by Heifetz or Menuhin . . . the pathos and the panache of Liza Minelli . . . the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have *never* experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

SPEAKERS: Duo Type II Size approx. 17in x 10½in x 6½in Drive unit 13in x 8in with parasitic tweeter Max. power 10 watts 8 ohms. Simulated Teak cabinet. £14.00 a pair. £2.20 p. & p. Duo Type III Size approx. 23½in x 11½in x 9½in Drive unit 13½in x 8½in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

PRICES: SYSTEM 1

Viscount III R 102 amplifier	£24.20	+ £1 p. & p.
2 Duo Type II speakers	£14.00	+ £2.20 p. & p.
Garrard SP25 Mk. III with MAG. cartridge plinth & cover	£18.00	+ £1.75 p. & p.
total	£56.20	

Available complete for only £49.00 - £3.50 p. & p.

PRICES: SYSTEM 2

Viscount R 102 amplifier	£24.20	+ £1 p. & p.
2 Duo Type III speakers	£32.00	+ £3.30 p. & p.
Garrard SP25 Mk III with MAG. cartridge plinth & cover	£18.00	+ £1.75 p. & p.
total	£74.20	

Available complete for £65.00 + £4 p. & p.

STILL ONLY **£49** COMPLETE



THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles it covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is 7in wide, 2in high and 4½in deep.

- * Circuit diagram and comprehensive instructions 55p free with parts.
- * Fully retractable and lockable car aerial £1.37 post paid.



CAR RADIO KIT £6.60 p. & p. 55p
Speaker with baffle and fixing strips £1.65. 23p p. & p. post free if bought with the kit. Send stamped addressed envelope for leaflet.

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

SOUND 50 45 WATT MONO AMPLIFIER. Ideal for Disco. Output Power: 45 watts R.M.S. (Sine Wave) Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control 2 inputs at 200mV into 470K. Size: 19½ x 10½ x 8ins. Amplifier £31.35 plus £1.65 p. & p. Output for 3, 8 and 15 ohm speakers.



£31.35 + £1.65 p. & p.

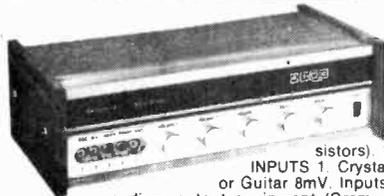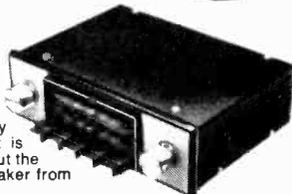


RELIANT Mk IV £13.50

*5 Electrically Mixed Inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling. INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.). All 250mV sensitivity. Output 20 watts into 8 ohms (suitable for 15 ohms). Size approx. 12½ x 6 x 3½ ins. £13.50 p. & p. 60p.

UNISOUND MODULES ONLY £7.64 + 55p p. & p.

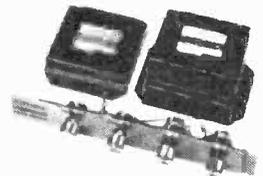For the man who wants to design his own stereo—here's your chance to start. With Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.



IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. Mains operated.


£9.90 p. & p. 80p

The Viscount III, the fabulous Stereo 21 and the Unisound Modules will all accept this unit, simply connect up.



ALL PRICES INC. VAT

The Catalogue you **MUST** have!

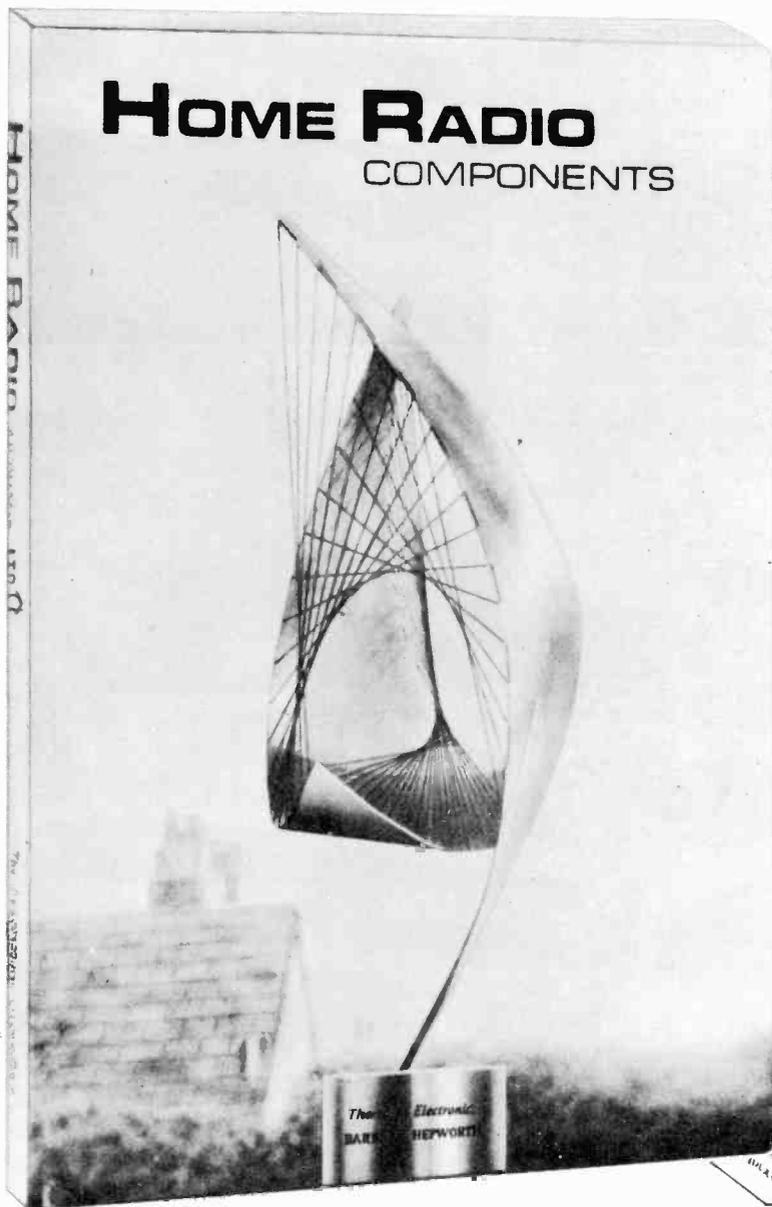

250 pages 11 $\frac{3}{4}$ " x 8 $\frac{1}{4}$ "

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Only 55p. plus 22p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 77p.

The price of 77p applies only to customers in the U.K. and to BFPO addresses.

Name _____
Address _____



HOME RADIO (Components) LTD. Regd. No. 912966, London
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

A NEW DIMENSION IN SOUND

FOUR years ago we commented upon the visionary views of the eminent musician Leopold Stokowski who had just then proposed the idea that stereo was by no means the ultimate in sound reproduction, but that a four channel system offered greater possibilities for extending musical pleasure by bringing the listener right into the midst of the performers.

Whilst applauding this somewhat revolutionary notion, we ventured to express our fears concerning the formidable nature of the task being set before the engineer. Timidity is out of place in electronics, and we should have known better!

In rather less than four years the technical problem of recording four channels upon disc in such a manner that their subsequent recovery would be possible using a normal stereo stylus has been solved. An account of the various rival systems and the current trend is given in the opening article of our new series featuring the P.E. Rondo—the first complete quadrasonic system to be offered to the constructor.

Now that the technical problems have (to all intents and purposes) been solved and both hardware and software are available, quadrasonic surround sound has become a reality and can be experienced in any home.

But what, exactly, does quadrasonic sound mean in the final analysis—in the strictly musical sense? If the ordinary listener is a little confused by what he has already sampled during demonstrations, this is not at all surprising. It is still early days for a new art. The recording companies show no single-minded approach to quadrasonics. In the US, CBS (originators of the strongly favoured SQ system) are experimenting with unconventional circular arrangements for orchestras when recording classical works in their studios, so providing the listener with the illusion of being right in the centre, on the conductor's rostrum. At home, EMI, in contrast, opts for the traditional concert platform set-up and uses the two rear channels in a rather subsidiary role, to add "concert hall ambience" to stereo.

In the case of popular music, recording engineers and producers seem permitted greater latitude to exploit the possibilities of four-channel recording. Less inhibited by nature, the pop musicians can be counted upon to make more dramatic use of the directional properties of quad, and new sound patterns will be devised, with the likelihood of the listener being assailed first from one corner then from another.

Following the establishment of stereo, the engineers accepted the next challenge and with the aid of the latest electronic technology have made the musician's dream possible. Now it is the creative artist's turn to experiment. Such a radical development in sound reproduction for the home sets a challenge for the composer and performer, in both the classical and pop areas. The impact of quadrasonics upon the world of music will be interesting to follow. It should produce some exciting and surprising sounds, though the initial period of experimentation may be a little wearing upon the listener's ears—and neck muscles.

F.E.B

Editor

F. E. BENNETT

Editorial

R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD
S. R. LEWIS B.Sc.

Art Dept.

J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN

Advertisement Manager

D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW

Phone: 01-634 4210

C. R. BROWN, *Classified*

Phone: 01-634 4301

Editorial & Advertising Offices:

Fleetway House, Farringdon St.,

London EC4A 4AD

Phone: *Editorial* 01-634 4452

Advertisements 01-634 4202

PE RONDO

QUADRAPHONIC

SOUND SYSTEM

BY R.A. COLE*

Audio systems are fast expanding into complex and very expensive set-ups offering all manner of facilities. In the PE RONDO system, PRACTICAL ELECTRONICS offers the home constructor a modular equipment housed in one case which may incorporate a selection of functions so as to form anything from a simple stereo amplifier system through to a complex AM/FM receiver/quadrasonic/stereo control and amplification system.

THE SAYING, "history repeats itself" must surely be proven when applied to recorded sound. At each stage of its development the eternal pessimists have sagely remarked that "it will never catch on"

When the first long playing records were introduced over two decades ago many record shops refused even to contemplate stocking them. The multiplicity of recording characteristics backed by various manufacturers of records caused even the hardiest of audio enthusiasts to think twice. The Jeremiahs considered that the LP was too fragile and the technical difficulties in reproduction too great.

But within a few years the LP was established and one standard recording characteristic was adopted.

STEREO

The introduction of the stereo LP caused just as much soul searching. Apart from plain disbelief that one groove could contain two signals, long and learned dissertations on recording techniques proliferated. There were even two contending methods of groove cutting, one "hill and dale" and the other "45-45" Blumlein method.

Fortunately this problem was soon decided in favour of the 45-45 method which is standard today. One of the earliest demonstration records had a commentator who spoke the historic words, "ping . . . pong", one word from each speaker, and immortalised "ping-pong" stereo.

Despite these problems the purist seems to live alongside the more gimmicky listener and all seem to be happy with their respective lots notwithstanding an occasional rumbling from the old ghosts of the past quarter century.

* Quadrasonics Ltd.

COST
£80
approx.
TO BUILD

See page 732

QUADRAPHONICS

Four channel sound has been with us now for several years and our enthusiast is just as confused as his predecessors by the old ghosts and Jeremiahs who seem to have reappeared for a 'new season of sport.'

The writer will attempt to remove as much of the confusion as he can and will clear the decks by stating that four channel sound is here to stay and that *any* of the techniques currently available enhances the enjoyment of recorded music.

Many elegant terms have been adopted in recent months to describe multichannel reproduction. The writer will use the inelegant but generally accepted nomenclature. However, when a term is confusing, definition of that term will be attempted.


Equally, whilst there are numerous multichannel reproduction techniques that *could* have replaced the present direction of development, the writer will confine himself to the present direction dealing, in detail, with the viable techniques to which the major producers of software and hardware are committed. Brief mention will be made of future trends and, as existing techniques are liable to updating, a final article in the series will include reference to the state of the art at that date.

NOMENCLATURE

Four channel reproduction is generally called **QUADRAPHONY** (Quadraphonic) conveniently analogous with **STEREOPHONY** (Stereophon c).

AMBIENCE ENHANCING. A term applied to circuits which attempt to recover ambient information from a normal stereo disc. A noteworthy system is that promoted by Dynaco. Another is shown in Fig. 1.1 by B. B. Bauer (1961).

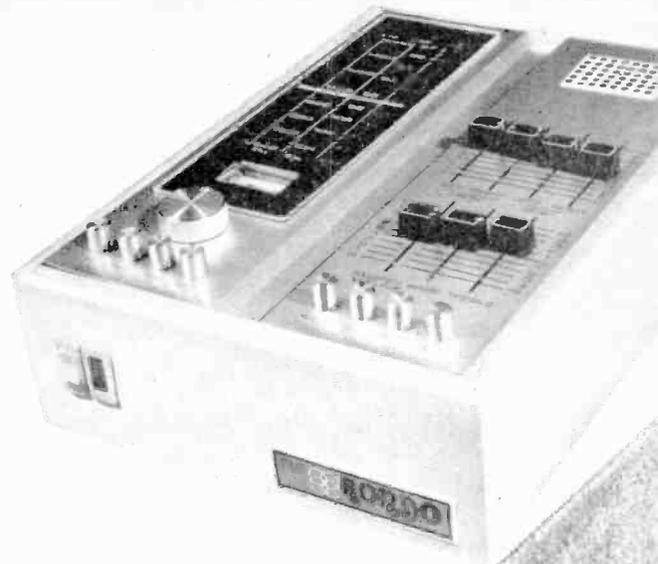DISCRETE SYSTEM. One which has four independent channels which can achieve distinct and unconnected sound placement in each channel. Quadraphonic tapes can be called discrete. "Discrete" when applied to disc reproduction is a misnomer which is perpetuated in the description of the JVC CD4 system.



Quadraphonics Par Excellence

- ◆ 4 x 20 watt power amplifier
- ◆ High-quality preamplifier and control system with wide dynamic range
- ◆ AM/FM receiver of advanced design
- ◆ CBS/SQ Quadraphonic decoder

System details and construction of the decoder follow on Page 761



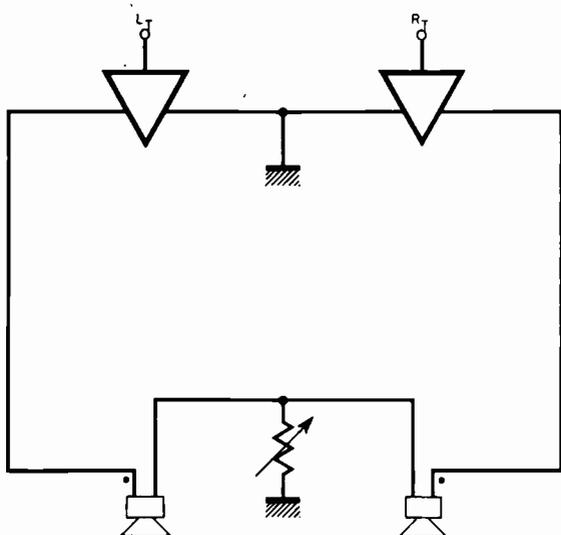


Fig. 1.1. Ambience enhancing in an attempt to recover ambient information from a normal stereo disc. This is the Bauer system developed in 1961

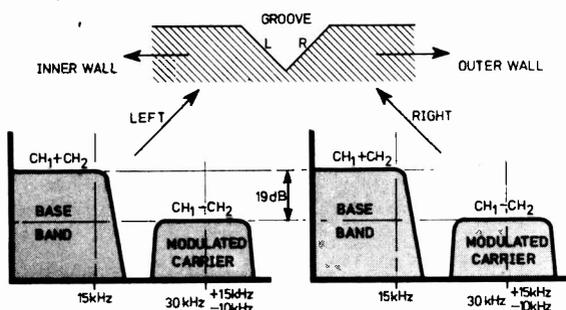


Fig. 1.2. Modulation direction and band separation on a CD4 disc

MATRIX. A term which, in Quadraphony, refers to the electronic mixing of four channels of sound into two composite channels for recording onto a disc followed by electronic re-creation of the original four channels of information. It is sometimes referred to as 4-2-4-matrixing. SQ, QS, RM and E-V are various matrixes.

CARRIER SYSTEM. For example, the JVC CD4 quadraphonic system, utilises two ultrasonic carriers and a matrix to achieve a recording on disc that can be demodulated upon playback to give four channels of information related to the original four recorded.

There are but three systems at present viable to which the major producers of hardware (equipment) and software (recordings—disc or tape) are committed and these can be broadly grouped into two. These are the JVC CD4 system, a carrier system, and the CBS SQ and Sansui QS systems, which are matrix systems.

THE CD4 SYSTEM

The CD4 system was developed by the Japan Victor Company (Nivico) and RCA, and first demonstrated publicly in September 1970. CD4 is a contraction of Compatible Discrete Four Channel. Work on similar lines was carried out by CBS before they opted for the SQ matrix.

The CD4 system combines matrixes with carriers by converting the four channels into sum and difference signals. Channel 1 + channel 2 ($CH_1 + CH_2$) is recorded on the left hand side of a 45-45 groove and $CH_3 + CH_4$ is recorded on the right hand side. The difference signals $CH_1 - CH_2$ and $CH_3 - CH_4$ modulate ultrasonic carriers and the resultants are superimposed upon the sum signals for recording.

The sum signals are called Base Bands and the difference signals are called Modulated Carriers (Fig. 1.2). The base bands are recorded to the RIAA characteristic and are the same as conventional stereo recording.

Due to a number of technical reasons the modulated carriers are frequency modulated below 800Hz and above 6kHz and phase modulated in between. (Recording is as shown in Fig. 1.3.)

Upon replay the two channel composite signals are demodulated and passed through a decoding matrix which "unscrambles" the sum and difference signals to give the four separated channels (Fig. 1.4).

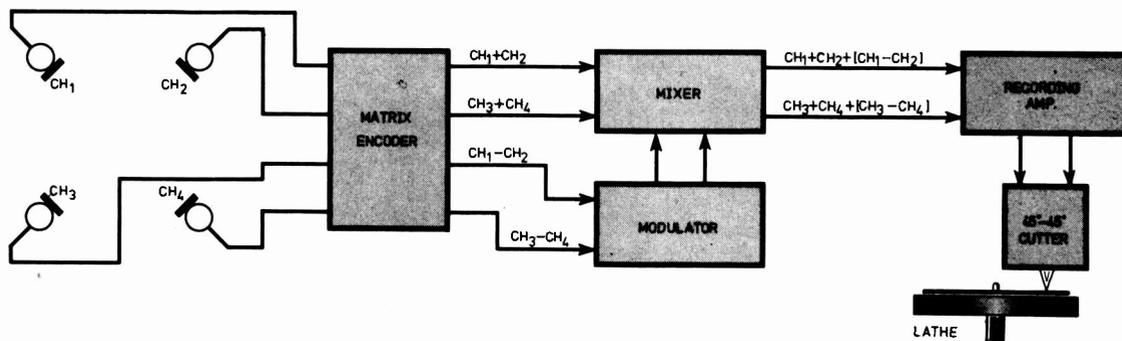


Fig. 1.3. Block schematic of the recording system used when making a CD4 disc

Due to limitations in today's recording technology the base band is limited from 30Hz to 15kHz and the 30kHz carriers are modulated in the range -10kHz to +15kHz. The CD4 specification for discs extends the upper frequency limit to 50kHz in anticipation of improvements in recording technology.

CD4 TECHNIQUES

The basic system has a number of problems which are diminished by the following techniques.

LOWER CUTTING SPEEDS

Cutting lathes have poor frequency response above 20kHz, so CD4 records are cut at half speed to compensate for this deficiency. This results in wider response but higher cost of production.

AUTOMATIC NOISE REDUCTION SYSTEM (ANRS)

A system similar to the Dolby noise reduction system is applied to eliminate noise which is generated in the difference signal path. This noise is primarily f.m. noise and crosstalk distortion.

CARRIER LEVEL CONTROL (CLC)

When the direct signal level is very high, the carrier signal can be degraded with resultant poor sound quality from the difference signals. CLC (Fig. 1.5) automatically increases the carrier level with increased direct signal level, and thus improves signal to noise ratio in the modulated carriers.

It improves abrasion resistance during playback and broadly improves pickup tolerance as well as reducing the base band interference mentioned above.

NEUTREX

This is the name of a new technique which assists the reproducing stylus to accurately trace the complex groove. The higher the baseband amplitude and the higher the frequency, the more pronounced is tracing distortion. Neutrex compensates the groove waveform to avoid the worst effects of tracing distortion as shown in Fig. 1.6 a, b and c.

CD4 STYLUS

Although CD4 records can be played with a spherical stylus of 0.5mm radius at 5 grams without

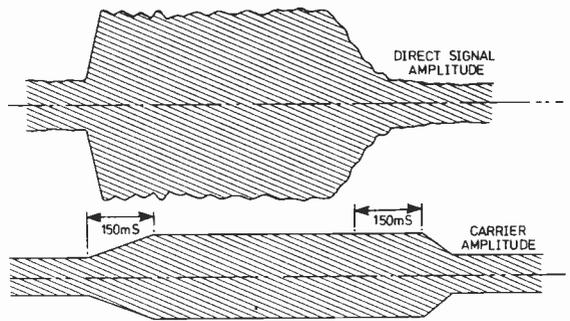


Fig. 1.5. Variations of carrier level which occur in CLC (Carrier Level Control)

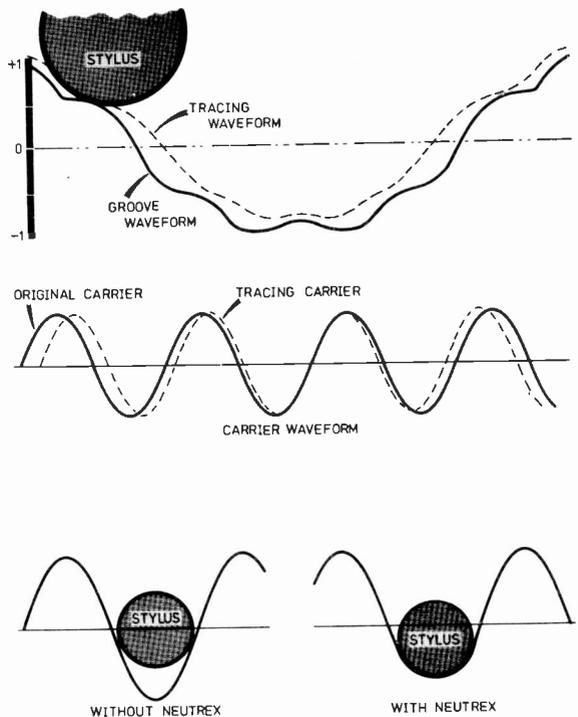


Fig. 1.6. The effects of Neutrex on the waveform traced out by the stylus

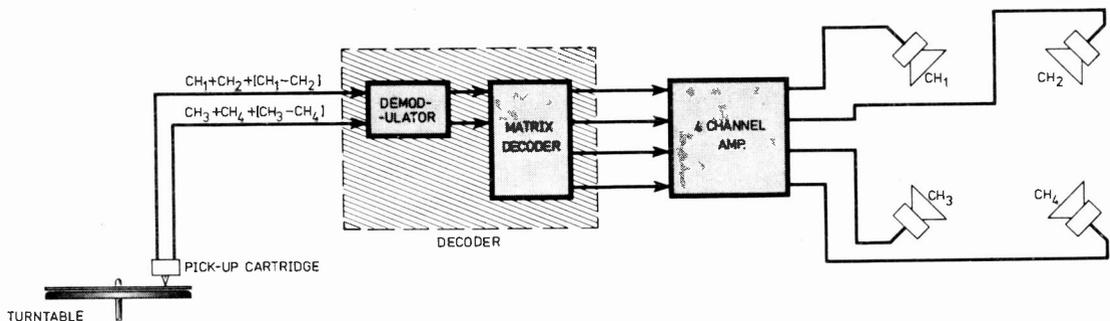


Fig. 1.4. Reversing the process of Fig. 1.3 when playing a CD4 disc

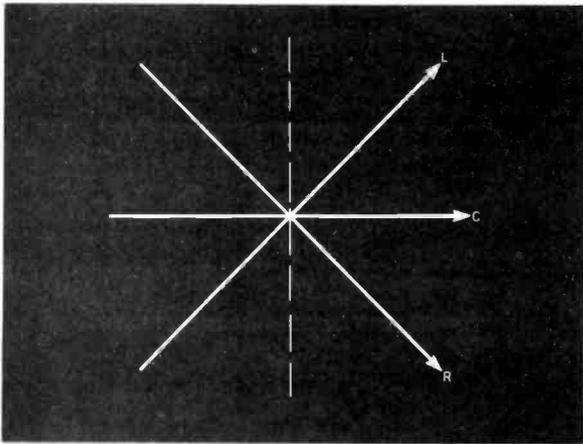


Fig. 1.7. The vector diagram for simple 45-45 stereo where the groove is modulated by two vectors at 90° to each other as shown by the lines L and R

disc. Reports as to quality are rather varied, the general consensus being that some of the "in-house" recordings from JVC are exceptional, but that most of the commercially available repertoire can only be described as old chestnuts. One can expect a noticeable improvement in all aspects of their software in future.

MATRIX SYSTEMS

A loose definition of matrix systems was given earlier. The precise definition of a particular quadraphonic matrix is only evident when expressed mathematically and such an analysis is outside the scope of this article.

There are also four psycho-acoustic principles which are significant in matrix design; the Haas effect; Front Source Dominance; Back Image Contraction and Quadrature Image Shift. The interested reader is commended for a discussion of these aspects to an article by Bauer, Gravereaux and Gust in the *Journal of the Audio Engineering Society of America*, Volume 19, Number 8, pp. 638-646.

In matrix systems the four channels are not independent and there is crosstalk between channels. The degree of crosstalk, and the channels between which the crosstalk exists, varies from system to system. Depending upon which matrix is used the sound images can be somewhat changed.

The effect of matrixing is best shown on vector diagrams. Two channel stereo can be illustrated simply by Fig. 1.7. The 45-45 groove modulations are represented by two vectors at 90° to each other and shown as the arrowed lines L and R.

If the signal recorded moves the stylus in only one of these two directions the signal passed through the system to the speakers will be only left or only right. If both these basic modulations occur simultaneously the image will appear to lie centre front. It will be seen that such a movement of the stylus is a lateral movement parallel to the record plane and that this is simply mono. Any other angular differences will result in different positional images between the two speakers.

significant wear after 100 playings, the frequency response is poor and distortion is quite high. An elliptical stylus can effect substantial improvement but specially developed styli must be used for really high fidelity reproduction.

The Shibata stylus and the Ichikawa stylus were developed for this purpose. Both are similar in concept and have around four times the contact area with the groove compared with a conventional stylus. They represent the closest practical shape to the original cutting stylus but are quite expensive due to their complexity.

It is also vital that the cartridge has a wide frequency response, up to around 45kHz, to reproduce discs of today's technology. Due to the limitation of the ending diameter of the CD4 disc groove to 5.2in, playing times are somewhat reduced but special plastics have been developed to reduce carrier wear and system deficiencies.

This remarkable technological achievement gives a viable method of quadraphonic reproduction from

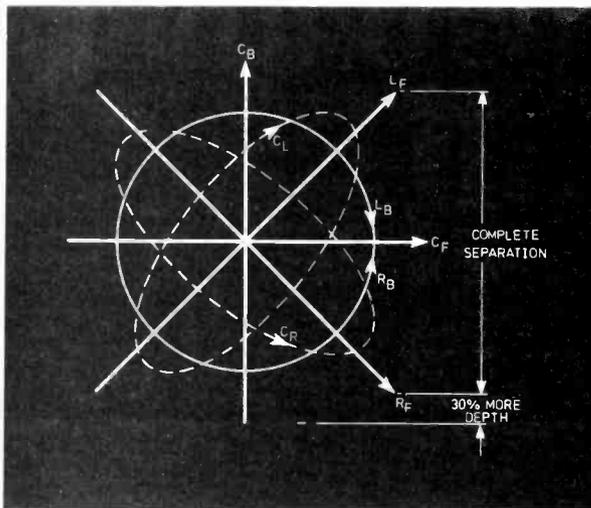


Fig. 1.8a. Vector diagram of the CBS SQ matrix

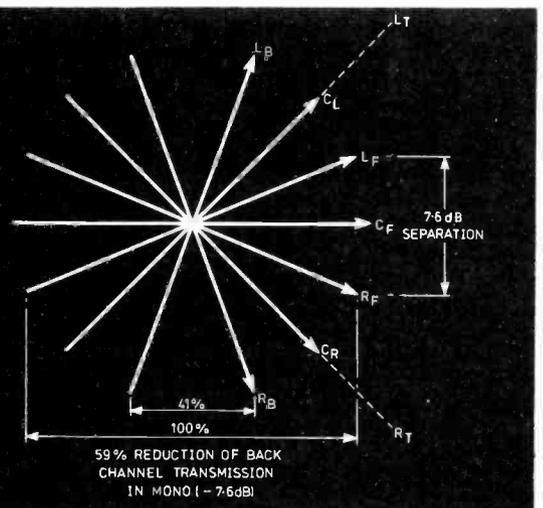


Fig. 1.8b. Vector diagram of Sansul QS-RM matrix

THE CBS SQ MATRIX

Fig. 1.8a shows the vector diagram of the CBS SQ Matrix. SQ simply stands for Stereo-Quadraphonic. It will be seen that the same three basic vectors exist in the SQ diagram as in the two channel stereo diagram of Fig. 1.7. These are the same left front (LF) right front (RF) and centre front (CF), hence the SQ matrix disc provides totally undiluted stereo information to the front loudspeakers with full channel separation.

Stylus movements in the direction marked CB provide centre back images. An additional basic modulation is provided which, for simple tones, is circular about the axis.

Clockwise modulations provide LB information and anticlockwise modulations provide RB information. This modulation appears as a helix due to the forward motion of the record groove.

Further modulations appear as ellipses rotating counter to each other representing centre left (CL) and centre right (CR) positions. LB and RB information is recorded on the left and right walls respectively but with a quarter cycle (90° phase difference)

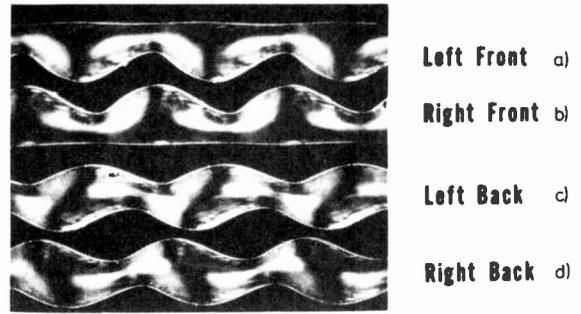


Fig. 1.9. The grooves of a stereo and an SQ modulated disc. (a) and (b) are the same as on a normal stereo disc whilst (c) and (d) show the helical modulation

primarily in classical music, have expressed the opinion that a matrix decoder of the type described above well meets the requirements for quadraphonic surround-sound reproduction.

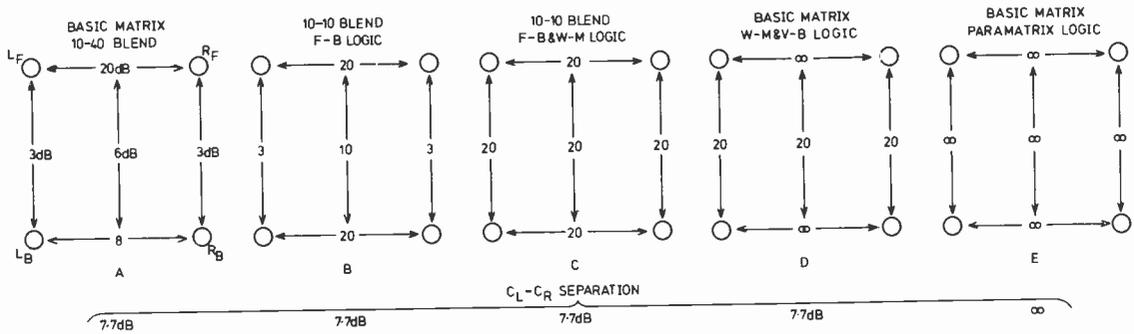


Fig. 1.11. The various stages in SQ decoder development from 10-40 fixed blend (a) to the future possibility of Paramatrix logic (e)

between them, resulting in the apparent circular motion. In recorded music the modulations are very much more complex than the simple tones represented by the helices described.

The photograph of Fig. 1.9 shows magnified grooves of an SQ record. They are all simple tones: (a) and (b) are the same as they would be on ordinary stereo record; (c) and (d) show the additional helical modulation present on an SQ disc to provide back images. The photograph clearly shows the stereo compatibility of the SQ disc which can be played by ordinary stereo cartridges to give full stereo.

The basic SQ matrix exhibits out of phase and unwanted signals at the back speakers when a signal is intended for the left front speaker. These out of phase signals are 0.707 of the level of the intended signal. Similarly out of phase signals appear at the front speakers when signals are directed to the left back speaker. The system is therefore asymmetrical.

Blend resistors added to the front and back signal pairs cancel out some of the unwanted signals with the attendant reduction of back separation to 8 dB. The so far recognised ideal blend is the 10-40 blend, where a 10% front and 40% back blend is used, and is called the 10-40 CBS SQ Matrix (See Figs. 1.10 and 1.11a). Many users, especially those interested

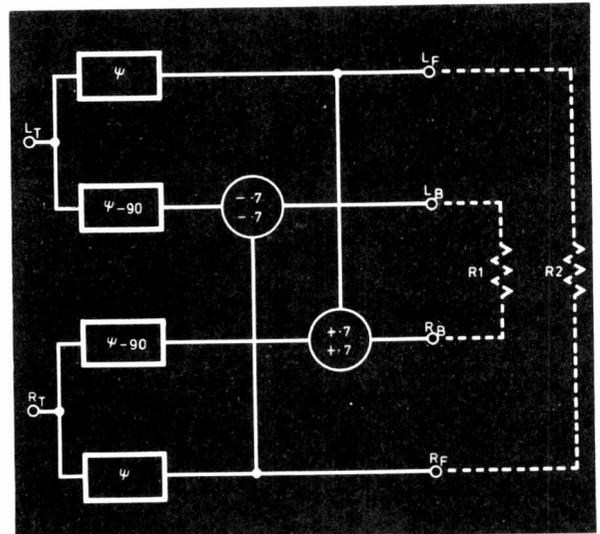


Fig. 1.10. Block diagram of a basic SQ matrix decoder. R1 and R2 provide the channel blend and the values mentioned give the recommended 10-40 blend

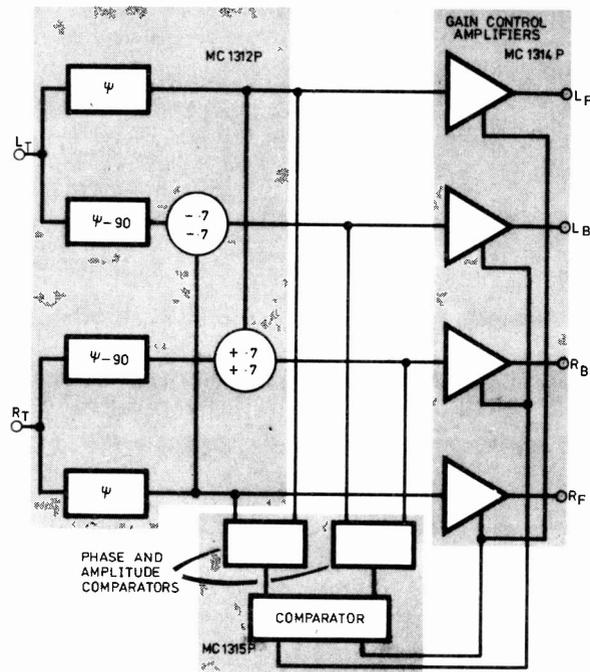


Fig. 1.12. The SQ logic-enhanced decoder using three chips, the MC1312P, the MC1315P and the MC1314P

LOGIC DIRECTED DECODERS

Greatly improved channel separation can be achieved by making use of both electronic logic and three psycho-acoustic phenomena with which we are all familiar. The first phenomenon occurs because of reverberation in a normal living room. This makes it difficult to locate the source of a steady state sound. Secondly, the origin of a varying source of sound, like speech or music, can be easily located. Finally, when there are two or more similar sources present we tend to believe that the one which we hear first is the sole source of the sound.

Logic directed circuits contain output amplifiers with voltage controlled gain characteristics which respond to predetermined amplitude and phase positions of the unwanted transferred signals as sensed by the logic. A signal in one of the front channels causes the production of two signals in the back channels identical in amplitude and in precise quadrature orientation.

This relationship is sensed by a comparator which results in instant enhancement of the front channels and rapid attenuation of the back channels. The converse is equally true and the resultant quadraphonic field approaches that produced by the four independent channels of the master tape.

With a signal to one channel only, this channel is kept open by the logic and any transferred signals are greatly attenuated thereby providing substantially discrete channels of information. These decoders are known as Front-Back (F-B) Logic Directed Decoders (See Figs. 1.11b and 1.12).

Logic directed decoders, in their simplest forms, may exhibit the effect of the logic circuit being confused by complex information. This appears as a "pumping" effect between front and back speakers.

ADVANCED LOGIC DIRECTED DECODERS

The latest advances in SQ Decoder technology have very recently been finalised and the writer thanks Mr. Benjamin B. Bauer, Vice-President C.B.S. Laboratories for his great personal assistance in these matters.

The circuit shown in Fig. 1.13 is the latest logic system and includes Wave Matching (W-M) logic and variable blend (V-B) as options.

The inter-channel separation for the front and back channel pairs is infinite in the basic matrix so only front/back separation needs to be improved.

If, for example, a transient signal is directed to left-front the W-M logic circuits recognise this as a front signal and adjust the levels between front and back so that 20dB separation in this direction is obtained. Another word for W-M is "corner-directed" logic.

If the left-front signal begins to decay and another transient signal is applied to LB the LB signal is emphasised. However, the steady state portion of the remaining LF signal becomes transferred to the LB but the ear assumes continued transmission from LF due to transient source dominance.

Thus the W-M logic can continually emphasise new transient sources in direction whilst maintaining the total power of all the preceding signals. (See Fig. 1.11c F-B and W-M Logic).

DYNAMIC BLEND

It has been previously explained how fixed 10-40 blend can enhance the separation between CF and CB signals. The same principle can be applied to logic but using a dynamic variable blend instead of fixed blend. If a CF signal, e.g. solo voice, is applied the channels at once become blended causing the signal to emerge from its proper centre-front location.

By careful design there will be almost complete front/back signal separation without any significant audible loss between front and back channel pairs. (See Fig. 1.11d W-M and V-B logic).

LATEST DEVELOPMENTS

Perhaps the most significant of the recent advances in SQ technology is the introduction of the integrated matrix chip manufactured by Motorola under CBS sponsorship, see Fig. 1.13. The MC1312 is the basic SQ Matrix Decoder and the MC1315 the Full Logic Module embodying both F-B and W-M logic. A Power Transfer Module MC1314 has the dual purpose of accepting the logic commands and translating them into enhanced quadraphonic action. It can also act as a gain control and loudspeaker balance element.

The circuit in Fig. 1.13 combines all the foregoing functions, including variable blend, which is controlled by means of an f.e.t. 2N5485 and four operational amplifiers. There is additionally provision for volume and balance (F/B, LF/RF, LB/RB) controls and a dimension control to adjust the logic action to suit ambient listening conditions. All of the logic and control functions are optional additions to the basic matrix decoder.

Reference has previously been made to Fig. 1.11 which shows the channel separations obtainable from each variation of the SQ Decoder. CL/CR separation

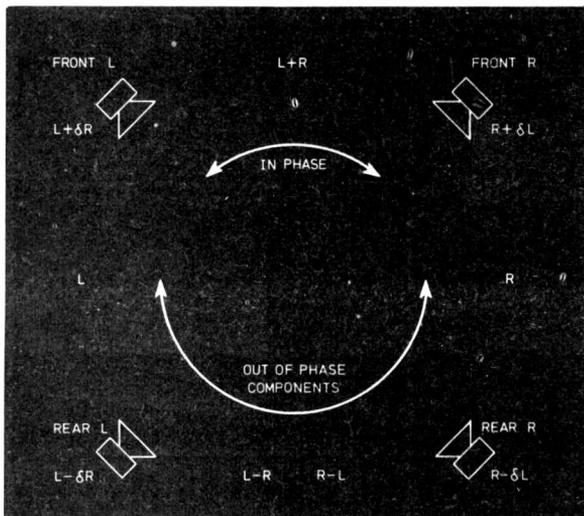


Fig. 1.14. The Sansui QS-RM system

speakers. The unwanted images (out of phase components—see Fig. 1.14) appear in the speakers either side of the speaker to which signals are being directed. This means that images appear somewhat more accurately in the direction intended.

It follows that this matrix is more symmetrical than SQ. The rear channels are also reduced to 41% of their original level for mono signals and heavy back modulations may be reduced by 2.3dB due to the need for around 30% extra cutting depth for back images. The principal loss however is of stereo compatibility.


Within its limitations the system gives acceptable results. Sansui have also developed a technique for reducing unwanted signals with the name Variomatrix.

THE FUTURE

The large companies have made such substantial capital commitments and technical advances in Quadraphonics that the course of this art is "pre-ordained" for some time to come. Work is being carried out by others in methods to reduce the bandwidth necessary for the difference paths in carrier techniques which, although reducing technical difficulties, would seem to be a retrograde step from the quality aspect.

A very interesting technique devised by Duane Cooper (University of Illinois) and Takeo Shiga (Nippon Columbia Co. Ltd.), and called a Phasor matrix, distributes the phase differences in sectors of 45° which means that the speakers either side of the wanted speaker receive signals that are +45° or -45° phase shifted.

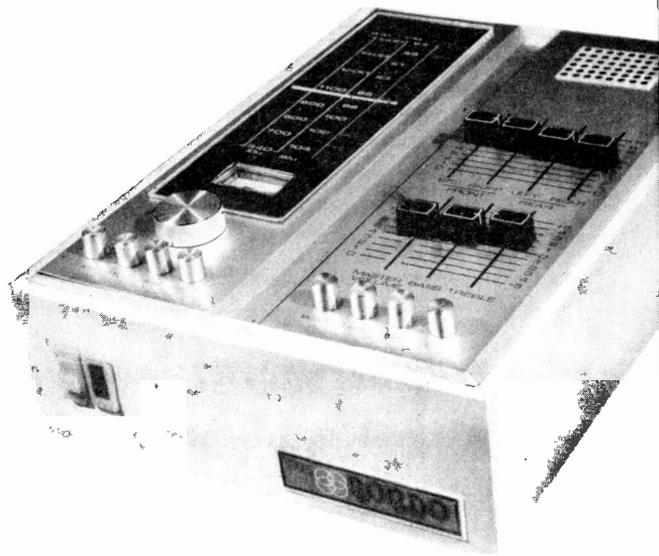This system, called BMX by Cooper, can be made more directionally accurate by the addition of more channels. These channels can be of narrower bandwidth without degrading performance. This matrix is in its early stages and has not been adopted by any recording company to date and only experimental discs have been produced so far.



COMPATIBILITY

Compatibility can be considered from two standpoints; one being compatibility of any quadraphonic system with another, and the other being compatibility with stereo material.

Quite obviously a CD4 record will not be quadraphonically compatible with matrix records. Matrix records are compatible with each other to a degree which, of course, is limited by their differences. It is possible to play an SQ record through a QS decoder or *vice versa* and obtain really enjoyable results which, although inaccurate, do enhance listening pleasure.

All are stereo-compatible but QS has a much reduced stereo separation. All matrix records can be broadcast by v.h.f. stereo radio and when received as stereo, may be decoded into quad.

CD4 records cannot be broadcast by present stereo radio transmitters. Over 200 transmitters in the U.S.A. have broadcast matrix quad and it is hoped that similar broadcasts may be undertaken by the IBA in their test v.h.f. transmissions in the U.K., later this year.

SOFTWARE AND HARDWARE

There are some 40 CD4 recordings available in the U.K. at present, mostly by JVC themselves. CBS SQ records number over 100 and also in excess of 20 have been produced by EMI. The U.S. situation is around the same for CD4 but over 200 SQ LPs are available. About 20 SQ records of European origin are listed. There are at least twelve QS records marketed.

At the June 1973 Chicago Conference more than 40 makes of record playing equipment were exhibited. All of these had built-in SQ circuitry in multiple models. Around a dozen offered facilities for integral CD4 circuitry. The big volume suppliers, who furnish over 90% of the market, offered SQ capability only.

It seems a reasonable conclusion that the availability of SQ hardware will accelerate the rate at which SQ discs become available compared with CD4.

SPECIFICATION

CBS SQ 10-40 BLEND MATRIX DECODER

Input Impedance
3M Ω typical

Distortion
0.1 per cent typical

Maximum Handling Capability
2.0V r.m.s.

Signal to Noise Ratio
Short circuit -80dB. Bandwidth 20Hz-20kHz

Channel Separation

L _F -R _F	20dB
L _B -R _B	8dB
L _F -L _B	3dB
R _F -R _B	3dB
C _F -C _R	6dB
L _C -R _C	7.7dB

Supply Voltage
+20V d.c. @ 16mA

PREAMPLIFIER

Inputs

F. M. Radio	100mV @ 50k Ω
A. M. Radio	100mV @ 50k Ω
Disc	3mV @ 47k Ω
Tape	100mV @ 50k Ω

Output
100mV @ 10k Ω to amplifier tone controls
100mV @ 10k Ω to tape recorder unaffected by volume and tone controls

Signal to Noise Ratios

Disc -60dB	} unweighted
Others -70dB	

Crosstalk
-50dB @ 1kHz

Dynamic Range
38dB before clipping

Distortion
0.05 per cent at rated sensitivity

Supply
 \pm 15V d.c. at 5mA

tone controls and balance

Inputs
2 \times 100mV @ 10k Ω from preamplifier
4 \times 100mV @ 50k Ω playback from tape (4 channel)
(inserted via balance potentiometers after tone controls)

Outputs
2 \times 100mV @ 10k Ω to quad decoder
4 \times 100mV @ 10k Ω to tape recorder (4 channel)
(into recorder before balance potentiometers and after tone controls)

Gain
Unity

Bass Control
 \pm 16dB @ 30Hz

Treble Control

+10dB	} @10kHz
-13dB	

Balance
Zero to full output on each channel

Crosstalk
-50dB @ 1kHz

Dynamic Range
38dB before clipping

Distortion
0.05 per cent at rated sensitivity

Supply
 \pm 15V d.c. @ 5mA

POWER AMPLIFIERS (two per board)

Input Impedance
10k Ω

Frequency Response
At 20W into 8 Ω continuous sine wave
-1dB from 10Hz to 20kHz
-3dB from 5Hz to 30kHz

Power Output
20W per channel into 8 Ω continuous sine wave

Total Harmonic Distortion
20W into 8 Ω <0.1 per cent
50mW into 8 Ω <0.1 per cent

Stability
Will drive electrostatic loudspeakers

Damping Factor
120 into 8 Ω

Supply
 \pm 25V d.c. @ 2.0A } for both amplifier boards
 \pm 15V d.c. @ 5mA }

TUNER

F.M. + DECODER

Frequency Range
87.5MHz to 104MHz

Sensitivity
3.0 μ V I.H.F. (Institute of High Fidelity Manufacturers)
20 μ V for 58dB signal-to-noise ratio
10 μ V for full limiting

Total Harmonic Distortion
Mono 0.6 per cent
Stereo 1.0 per cent

Stereo Separation
35dB @ 1kHz

A.M.

Frequency Range
550kHz to 1.6MHz

Capture Voltage
100 μ V at midband

Distortion
Approximately one per cent total harmonic distortion

Supply
+24V d.c. @ 100mA

SPEAKER SYSTEMS

Power Handling
20W continuous sine wave

Impedance
8 Ω

Loading
Infinite Baffle

Frequency Response
35Hz-22kHz \pm 5dB

Drive Units
2 \times HIF 13E 130mm Long Throw Units
2 \times 6.5 TW Bi 65mm Tweeters

Crossover Network
Six-element network dividing at 500Hz and 6kHz

OVERALL DIMENSIONS

Cabinet
254mm (10in) \times 120mm (4 $\frac{3}{4}$ in) (add 15mm for height of knobs) \times 326mm (12 $\frac{3}{4}$ in)

Speaker Enclosures
242mm (9 $\frac{1}{2}$ in) \times 405mm (16 $\frac{1}{4}$ in) \times 216mm (8 $\frac{1}{2}$ in)

PE RORDO

PE RONDO

SYSTEM DETAILS AND DECODER MODULE

THE PE RONDO

The current increasing interest in quadraphonics, coupled with the introduction of integrated circuit decoder chips supported by a growing bank of software has created the ideal atmosphere for the home constructor to build his comprehensive Quadraphonic System.

The PE RONDO system has been developed and planned especially for the home constructor and incorporates advanced technology throughout.

Figure 1.15 shows the system in block diagram form and a full technical specification is given elsewhere. The system incorporates power supplies,

power amplifiers, both f.m. and a.m. radio tuners, stereo decoder, quadraphonic decoder system, tone, volume, balance controls and selectors, and pre-amplifiers and characteristic compensation circuits. All this circuitry is incorporated in a neat and compact wooden case with a shallow metal plinth in which are mounted the input and output terminations.

The system is completed with a set of four loudspeakers for those who wish to make their own.

The approximate cost to build is £70 plus V.A.T. for the main unit; and £62 for the loudspeakers (4). (Suitable turntable units can be found in the price range £25-£40).

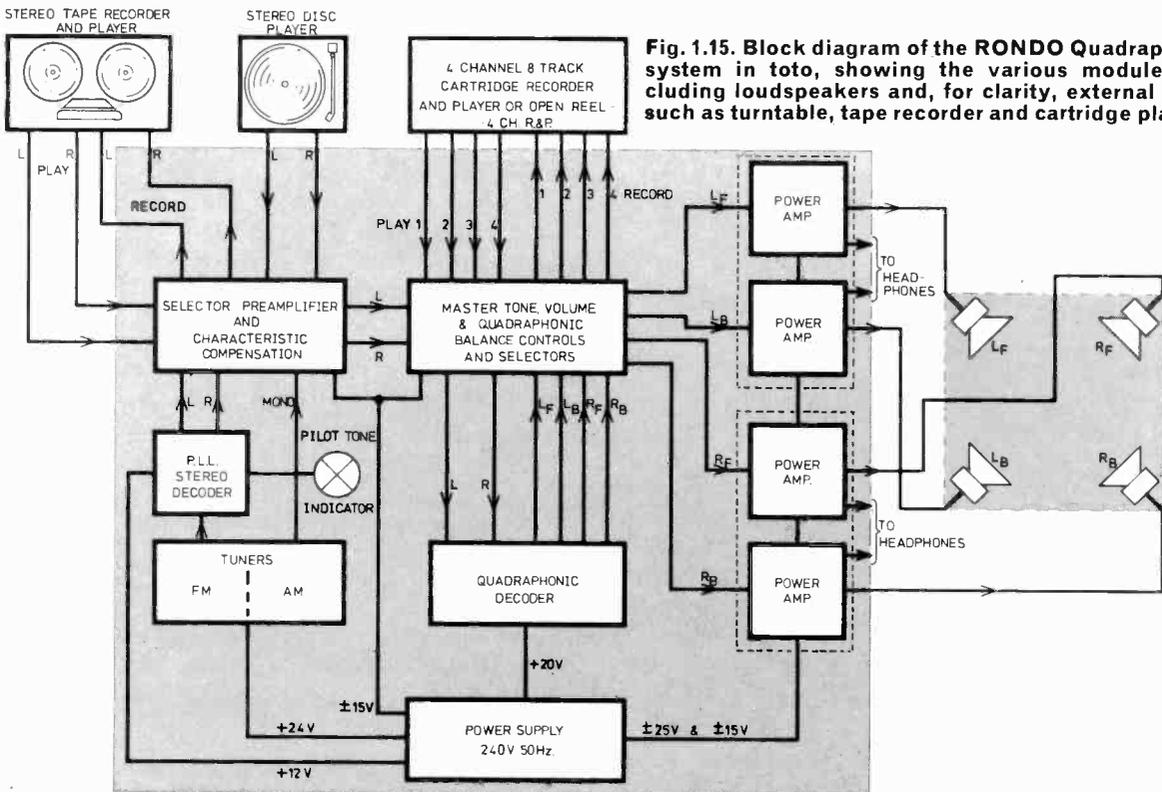


Fig. 1.15. Block diagram of the RONDO Quadraphonic system in toto, showing the various modules, including loudspeakers and, for clarity, external items such as turntable, tape recorder and cartridge player

CBS SQ DECODER MODULE

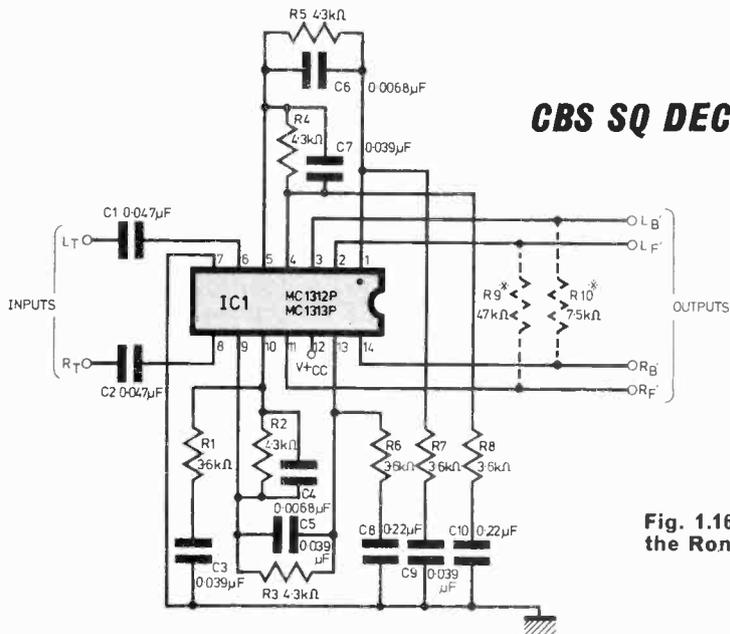


Fig. 1.16. Circuit diagram of the Rondo decoder board

Fig. 1.17. Component layout for the Rondo decoder board

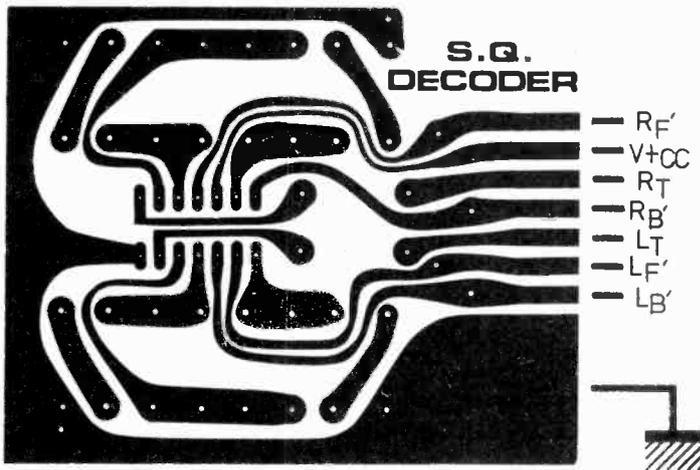
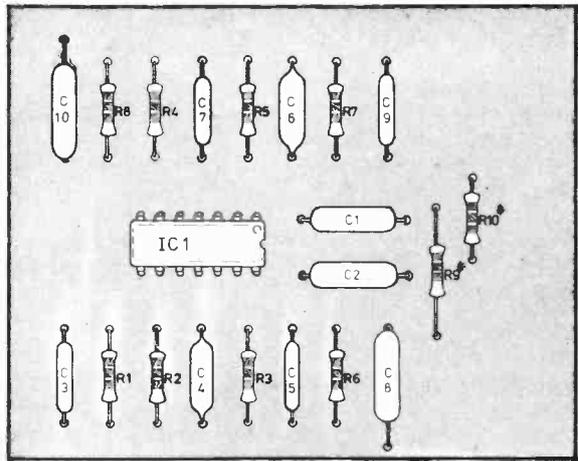


Fig. 1.18. Printed circuit copper layout for the Rondo decoder board

COMPONENTS . . .

CBS MATRIX DECODER

Resistors

R1	3.6k Ω	R6	3.6k Ω
R2	4.3k Ω	R7	3.6k Ω
R3	4.3k Ω	R8	3.6k Ω
R4	4.3k Ω	R9	47k Ω
R5	4.3k Ω	R10	7.5k Ω

see text

All 5% $\frac{1}{4}$ W carbon or metal oxide

Capacitors

C1	0.47 μ F 20% 63V	C6	0.0068 μ F
C2	0.047 μ F 20% 63V	C7	0.039 μ F
C3	0.039 μ F	C8	0.22 μ F
C4	0.0068 μ F	C9	0.039 μ F
C5	0.039 μ F	C10	0.22 μ F

All 5% 63V polyester except where stated

Integrated circuit

IC1 MC1312P CBS SQ Monolithic Decoder
Available only as part of a complete kit from CBS Licensees or retailers who have purchased as a complete kit from CBS Licensees. This is due to licensing restriction imposed by the Licensor CBS Inc.

Printed Circuit Board

Fibre glass as part of kit of parts from: Sonax Electronics, Spencer House, Brettenham Road, London, N.18.

the supply of the products to licensed equipment manufacturers only.

In the present instance CBS have given permission for supply of the i.c. to constructors provided it is sold as part of a kit for making up the decoder. All other parts of the RONDO system are available freely in the normal manner.

CONSTRUCTION

The decoder chip is packaged in a dual-in-line 14-pin package under the code number MC1312P and is marked with a dot to indicate correct orientation of the chip when mounting, as can be seen from Fig. 1.16, the circuit diagram of the decoder.

Most of the components shown external to the chip are phase shift networks referred to earlier. In addition, there are the two input capacitors, C1 and C2, which decouple the chip circuitry and the two fixed blend resistors, R9 and R10, shown dotted.

The phase shift networks have pre-determined time constants and must utilise stable components of $\pm 5\%$ tolerance.

The printed circuit board layout master is shown in Fig. 1.18 and the component layout, the opposite side of the PCB, is shown in Fig. 1.17. It will be seen that two different mounting pitches are provided for C8 and C10. This is so that these capacitors may be selected from several manufacturers offering different lead-out pitch distances.

The components are mounted on the board from the non-plated side in the configuration shown and it is probably best to mount all components and bend the leads slightly, before starting soldering, to hold the components in position. This makes certain the layout is correct before any hard-to-reverse steps are taken.

Don't forget to take care with the soldering operation, only applying the iron for long enough to make a good joint, particularly on the i.c. pins. It's all too easy to damage an i.c. with conducted heat from the pins.

After soldering, the board should be cleaned of any flux and solder splashes with a brush.

TO COME

In following articles we will deal with the construction of power supply, power and pre-amplifiers; volume and balance controls and tone controls. All the r.f. circuitry will be described including both a.m. and f.m. receivers and an associated stereo decoder for the f.m. unit. Finally suitable speakers will be described for those who wish to make their own.

The equipment described so far is, in one form or another, available commercially. However, in the articles to come, one of the very latest ideas in quadraphonics will be described—an extension of the CBS SQ matrix board using the latest logic to give front/back logic, wave matching logic, and variable blend. This latter is so new that PE readers will be amongst the first in Europe to have it.

Of course, this does not detract from the basic matrix board described in the present article, and very exciting results can be obtained with this.

Next Month: Audio amplifiers and power supply

FLEXIBILITY

Examination of Fig. 1.15 shows clearly that a number of advantages accrue from using a modular construction which integrated circuits and printed circuit boards allow.

In the first place, the system can be built in stages.

Secondly, the system can first be built as a stereo system and later converted. Indeed, the constructor can, if he wishes, make use of an existing stereo system in conjunction with a RONDO stereo section to complete the quadraphonic system.

By including suitable switching circuitry the quadraphonic system can be extended to accept any future, or for that matter existing, decoders which might become available.

The PE RONDO specification is broken down into the various sections for simplicity and ease of understanding.

THE DECODER

This first constructional article deals with the perhaps simplest but most important part of a Quadraphonic system—the decoder.

The CBS SQ 10-40 decoder chip is manufactured by Motorola under licence from CBS Inc. The licence is part of a commercial agreement involving

SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT. NEW & SECONDHAND MUSICAL INSTRUMENTS. DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES

Announcing our improved range of constructor modules

FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A "Plastic Power" Driver Transistors now available.



To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.

SA35 35W RMS uses 7 transistors and 7 diodes. Carr. paid. **£4.45**

A NEW ADDITION IS THE **SA50 at £5.65**

Carr. paid. A rugged, well built unit, capable of 50W RMS out, with all the advantages of Saxon Amplifier design and quality. Ready now.

SA100 makes an ideal unit in disco assemblies

A real glutton for work. Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid. **£10.90**

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000Hz ± 1dB	All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in its SA100
Distortion	0.2% at 1kHz	
Loads	4 to 16 ohms	
Quiescent current	15mA	
Noise	Better than -75dB	
Supply voltage	SA35-45V SA50 45/65V SA100 40-70V	
Size	4 1/2in x 4in x 1in (SA100) 4in x 3in x 1in (SA35/SA50)	

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 & SA100 AUDIO MODULES

PU45	Unstabilised supply for 2 SA25/35's	£4.90
PU70	Unstabilised supply for one or two SA100	£7.75 carr. 40p
PS45	Stabilised module for 2 SA25's or two SA35's	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted	£3.50 carr. 20p
PS70	Stabilised supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

TWO NEW PA/MIXER CONTROL UNITS

Built for hard work!

In extra slimline easy-fit case.

Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master controls. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos, etc. Standard jack sockets, compact design. In strong metal cases. All Units guaranteed for 3 years.

- HIGH AND LOW IMPEDANCE INPUTS
- BASS/TREBLE/VOLUME ON EACH PAIR
- MASTER CONTROL ON OUTPUT

M4H
4 high Z, 4 low Z inputs, 4 sets of controls. Case 10" x 8" and only 2 1/4in deep. Carr. paid. **£18.50 + V.A.T.**

M6HL
12 inputs (6 high Z, 6 low Z). Carr. paid 18" x 8" x 2 1/4". **£27.50 + V.A.T.**

Channel section modules, for building your own: gain—16 x (24dB) Tone controls—18dB swing. Carr. paid. **£3.50 + V.A.T.**

CONTROL UNITS

Mono (as shown). **£6.50**
Carr. 20p.
Stereo. **£15.80**
Carr. 30p.



Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2in x 3in x 4in deep and is finished with a smart white on black face. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass treble, mains on/off. **COMPARABLE TO UNITS AT OVER TWICE THE PRICE.** (N.B.—Stereo only has mic. Input.)

PLEASE ADD 10% FOR V.A.T. TO TOTAL VALUE OF YOUR ORDER
S.A.E. brings Saxon equipment and bargains list

120 WATT HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.
SPECIFICATION
Power output, 120W into 8 ohms
Freq. response, 20-20,000Hz ± 2dB
Input sensitivity, 200mV into 10K
Construction, Fibreglass board
Size, 8in x 4in x 4in (5in with supply)
Low distortion parallel push-pull output stage.

● 160 watts version with power supply (Carr. 50p) **£27.90**

Module only **£13.90** (Carr. 20p)
Module and power supply (Carr. 40p) **£18.95**



3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls, 2 amplifier sockets eliminate need for split leads. Up to 3kV lighting load. Smartly finished steel case. Carr. 30p. **£19.75**

SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3kV (3,000W) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.

SINGLE CHANNEL UNIT

Operates from 5-100W amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p. Carr. pd. **£8.90**

COMPLETE AMPLIFIERS

CSE 100 £34.90 carr. free

This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100W RMS and continuous signal outputs of 70W. Two individually controlled inputs with wide range bass and treble controls.



SAXON 100 £48.50 carr. free



With an RMS output of 120W speech and music, 100W continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.


LOUDSPEAKERS British made bargains!!
12in 25W 8/15 ohms £5.95 carr. 30p. 15in 50W 8/15 ohm £14.50 carr. 30p. 12in 40W 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p. 600 Watt 3 colour Light Boxes Smart Reline finish £15 carr. free.

A.K.G. MICROPHONES
D11 DHL IDEAL DISCO MIKE ONLY £9.45 (rrp £11.00). S.A.E. for special price list.


Order and personal shoppers to:
SAXON ENTERTAINMENTS LTD., 329 Whitehorse Road, W. Croydon, Surrey CR0 2HS
Telephone 01-684 6385 From 9.30 a.m.-5.30 p.m.
TRADE AND EXPORT ENQUIRIES INVITED

Prices quoted do not include V.A.T. 10% must be added on to total value of order for V.A.T.

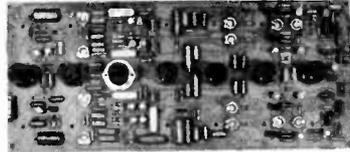TERMS OF BUSINESS
Cash with order (C.W.O.). For C.O.D. please add 35p extra, cash by regd. letter please.



PHONOSONICS P. C. BOARDS

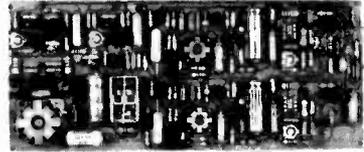

AURORA
Multichannel Sound Controlled Light (PE Apr./Aug. 71). S/c's (excl. SCR's), Rs, Cs, Pots, Cores—8 ch. £17.75; 4 ch. £10.15. Reg. PSU £3.65. PCB—4 ch. control (4 1/2in x 10 1/2in) Mk. 2—also holds rotary or slider pots £2.35. PCB (4 1/2in x 5in) Mk. 2—for PSU, Sync Gen. 8 cores, 8 SCR's, £1.35. SCR's—1A, 50p, 3A, 55p.

LOUD-HAILER AND SIREN
(Pre-amp and Siren Generator)
(PW Dec. 72). S/c's, Rs, Cs, Pot, PCB (2 1/2in x 2 1/2in) £2.20 (While stocks last). Main Amp Module PCS+ obtainable to special order, £6.

DOOR BELL YODELLER
(PE Apr. 71). S/c's, Rs, Cs, Pots, PCB (3in x 3 1/2in), £5.10. L/sprk £1.30.

GEMINI STEREO AMPLIFIER
(PE Nov. 70/Mar. 71) Stereo Sets and PCB's. Pre-amp—S/c's £1.85. Rs, Cs, Pots, Mksa-Sw's—with 1/2W MO Rs, £11.60—with 1/2W CF Rs, £8.90. PCB (3 1/2in x 10 1/2in) for sets with MO and 1/2W Rs, also holds rotary or slider pots and Mksa-Sw's, £2.10. Main Amp—Rs, Cs, Pots, £5.40. PCB (3 1/2in x 5in), £1.40. PSU—Rs, Cs, Pot, £3.70. PCB (2in x 4in), 75p.

LOGICAL RADIO CONTROL
(PE Apr./Jun. 72)—Details in lists

GEMINI STEREO TUNER
(PE Apr./Jun. 72). Rs, Cs, Pot, £3.80. PCB as publ., £1.50.

MICROPHONE MIXER
(PE Apr. 69). S/c's, Rs, Cs, Pots, £2.90. PCB (3 1/2in x 4 1/2in) also holds 6 rotary or 4 slider pots, £1.20.

POST AND PACKING
U.K. 10p per order. EXPORT at cost—please allow for this when ordering and also state, whether air or surface postage required.

BIOLOGICAL AMPLIFIER
(PE Jan./Feb. 73). P/A Set—S/c's, i.c.'s, Rs, Cs, Pots, PCB (1 1/2in x 3 1/2in), £3.70. O/P Stages (S/c's, Rs, Cs, Pots and Sw's as reqd.). Alphaphone 60p, Cardiophone 75p, Freq. Meter £1.90, Vis-Feedback 60p, Audio Amp PCT avail. to order £4.75.

ELECTRONIC PIANO
(PE Sep. 72/Jan. 73)—Details in lists

MODEL SERVO CONTROL
(PE Feb./Mar. 72)—Details in lists

8 WATT AMPLIFIER
(PW Nov./Dec. 72). Pre-amp—S/c's, Rs, Cs, Pots, Sw—Mono, £2.50; Stereo, £5.20. PCB (3 1/2in x 7 1/2in) (Stereo) also holds rotary or slider pots and Sw, £1.50. Main Amp—S/c's, Rs, Cs, Pot—Mono, £3.90; Stereo, £7.70. PCB (2 1/2in x 3in) Mono, 60p.

HI-FI TAPE LINK
(PE Mar./Apr. 73). S/c's, i.c.'s, Rs, Cs, Relay and pc-base, Pot, Cores and pc-bases, Sw's, Pots, Panel Lamp—Mono, £11.80; Stereo, £18.70. PSU, £2.50. PCB—Main Assy. (3 1/2in x 9in) (Stereo) also holds relay and cores, £1.85. PCB—Sub-Assy. (2 1/2in x 6 1/2in) (Stereo) holds Sw-assoc. Rs, Cs, Presets and mounts on Sw's, 80p.

REVERBERATION UNIT
(PW Nov./Dec. 72). S/c's, Rs, Cs, Slider Pots, T/fmr, £6.80. PCB (2in x 1 1/2in) also holds sliders, £1.20. 9in Spring Unit avail. to order, £3.75.

VIBRASONIC GUITAR PRE-AMP
(PW Sept. 70). Incl. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume. S/c's, Rs, Cs, LDR, Rotary Pots, Lamp, Coupling T/fmr, £7.75. PSU, £2.80. PCB (3 1/2in x 10 1/2in) Mk. 2, also holds 7 rotary or slider pots, £2.30.

ULTRASONIC TRANSMITTER-RECEIVER
(PE May 72). S/c's, Rs, Cs, Pot, Relay, Dual PCB (2in x 5 1/2in), £3.90. T/ducers avail. to order, £7.30 per pair.

ALSO
PCBs as published (while stocks last) for:
DIGITAL PSU (PE Aug. 72), 60p
OSCILLOSCOPE P/A (PE Aug. 72), 40p
SCORPIO (PE Nov./Dec. 71), 70p
TRIFID (PE Feb. 73), 60p

AND
DIGITRONIC (PW Mar. 73). Recd-outer PCB (1 1/2in x 3 1/2in), 60p.

V.A.T.
U.K. Orders only—add 10% to total cost of order.

TAPE NOISE LIMITER UNIT
(PE Feb. 72). S/c's, Rs, Cs, Pot, PCB (1 1/2in x 3in), £2.20. Reg. PSU and PCB (1 1/2in x 2 1/2in), £3.20.

VERSATILE LIGHT EFFECTS UNIT
Single Channel Sound Controlled Light with built-in variable strobe. (PE June 72). S/c's, Rs, Cs, Pots, T/fmrs, Keyswitch, £8.85. PCB (3 1/2in x 7 1/2in) Mk. 2, also holds pots, Sw, T/77 T/fmr, £1.50. SCR's—1A, 50p, 3A, 55p.

PHOTOPRINT PROCESS CONTROL
(PE Jan./Feb. 72). Finds exposures, controls timing, stabs, mains voltage. S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keyswitch, T/fmr, £7.60. PCB (3 1/2in x 5 1/2in) also holds pots, Sw, relay, £1.20.

SOUND SYNTHESISER (PE Current Series)
Details of PCBs and Components in list. Free mailing list service available for further information about PCBs and Sets for this project.

LIST
S.A.E. for free list and with all enquiries please.

PHONOSONICS, DEPT. PE9, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW

MAIL ORDER ONLY

WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS. ENGLAND
C.W.O. Please. P. & P. please add 10p to orders under £2
MAIL ORDER. CALLERS SATURDAYS ONLY

SEMICONDUCTORS

TRANSISTORS		DIODES		LINEAR IC's		
AC125	12p BC147	12p	OC70	10p	OA85	7p
AC126	12p BC148	12p	OC71	10p	OA90	5p
AC127	12p BC149	12p	OC72	10p	OA91	5p
AC128	12p BD131	49p	2N2218A	13p	OA200	8p
AC187	12p BD132	49p	2N2220	10p	OA202	8p
AC188	12p BF194	15p	2N2221	10p	IN914	5p
AD161	30p BF195	15p	2N2483	10p	IN4001	6p
AD162	30p BFY50	22p	2N2484	9p	IN4004	7p
AF114	12p BFY51	22p	2N2926R	9p	IN4007	8p
AF115	12p OC26	40p	2N2926G	9p	IN4148	5p
AF116	12p OC28	40p	2N2926V	9p	BYZ10	20p
AF117	12p OC35	40p	2N2926G	10p	BYZ 88 series	
BC107	9p OC42	10p	2N3014	10p	400mW 3-3V-30V.	
BC108	9p OC44	10p	2N3055	55p	WO1	30p
BC109	9p OC45	10p			WO6	36p

JACK PLUGS (CHROME ONLY) AND SOCKETS	
Standard Screened, 12p	Standard 12p
Stereo Screened, 13p	Stereo 15p
2.5mm Screened, 8p	2.5mm 7p
3.5mm Screened 10p	3.5mm 7p

DIN PLUGS & SOCKETS		COMPACT CASSETTES	
Pin: 2, 3, 4, 5 (180° or 240°)	Plugs, 12p, Socket 8p.	C60 40p, C90 55p;	C120 75p.

PHONO PLUGS AND SOCKETS: PLUGS assorted colours 5p.		SWITCHES TOGGLE SPST 18p	
Socket: Single 5p	Double 7p	SLIDE DP 1A 22p	DPDT 20p
Triple 10p		ROTARY Wafer 10p	
		I-12 Way 25p	

THYRISTOR 200V 4A 60p	
VEROBOARD	
0-1	0-15
2 1/2 x 3 1/2in	20p 18p
2 1/2 x 5in	24p 22p
3 1/2 x 3 1/2in	24p 22p
3 1/2 x 5in	27p 30p
2 1/2 x 17in	75p 60p
3 1/2 x 17in	97p 84p
5 x 17in	128p
2 1/2 x 17in (plain)	40p
2 1/2 x 17in (plain)	60p
5 x 17in (plain)	80p
Pkt. 50 pins	20p
Spot face cutter	42p
Pin insertion tool	52p

TGS GAS SENSOR HEAD (ELECTRONIC NOSE) (or detection of combustible gases, with a proven record for an extremely reliable Fire Detection, TGS Head can detect extremely low gas concentration levels without amplification. (PE July '73. "ELECTRONIC NOSE" illustrates amplified alarm system. TGS HEAD AND CIRCUIT APPLICATION DATA. PRICE £1.85.

RESISTORS

High stability low noise carbon film.		Miniature wire wound.		PRICE	
Power	Tol.	Range	Available	Values	
Watts	%	2-2-22M	E12	1-9	10-99
1/2	5%	2-2-47M	E12	1p	0-8p
1	5%	2-2-10M	E12	2p	0-8p
2	5%	1-10 ohm	E12	2p	1-6p
4	10%		E12	6p	5p

Do not mix ohmic values to obtain quantity prices. Ignore fraction

POLYESTER CAPACITORS. Axial lead type:
400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 0.0068µF, 2 1/2p, 0.01µF, 0.015µF, 0.022µF, 0.047µF, 3p; 0.068µF, 0.1µF, 0.15µF, 4p; 0.22µF, 7p; 0.33µF, 10p; 0.47µF, 13p.
160V: 0.1µF, 0.15µF, 4p; 0.22µF, 5p; 0.33, 6p; 0.47µF, 7p; 0.68µF, 10p; 1µF, 13p.
Radial lead P.C. type:
250V: 0.01µF, 0.015µF, 0.022µF, 3p; 0.033µF, 0.047µF, 0.068µF, 3 1/2p; 0.1µF, 4p; 0.15µF, 4p; 0.22µF, 0.33µF, 5p; 0.47µF, 7p; 0.68µF, 10p; 1.0µF, 11p.


ELECTROLYTIC CAPACITORS. Miniature axial lead type.
63V: 1µF, 1.5µF, 2.2µF, 3.3µF, 4.7µF, 6.8µF, 10µF, 15µF, 22µF, 47µF, 68µF, 6p each.
40V: 100µF, 6p; 150µF 25V, 6p; 25V: 220µF, 11p; 470µF, 13p; 680µF, 20p; 1,000µF, 25p.

CERAMIC CAPACITORS: 50V d.c. Plaquette body 25mm leads.
Range: 22pF-10,000pF. Price 2p each.

POTENTIOMETERS: Carbon Track 0-25W. Log and linear values		SLIDER POTENTIOMETERS 0-25W log and linear values	
5k Ω - 2M Ω Single Gang	12p	10k Ω - 100k Ω Single gang	35p
5k Ω - 2M Ω 2-gang W/switch	24p	10k Ω - 100k Ω Dual gang	50p
5k Ω - 2M Ω Dual gang	37p	Knobs	10p
1K linear single gang	12p		
Knobs Pointer type	8p		
Small Aluminium	10p		
Black chrome rim	15p		

WATFORD ELECTRONICS
35 CARDIFF RD., WATFORD, HERTS, ENGLAND.
Enclose 10p stamps for our comprehensive catalogue.

Name _____
Address _____

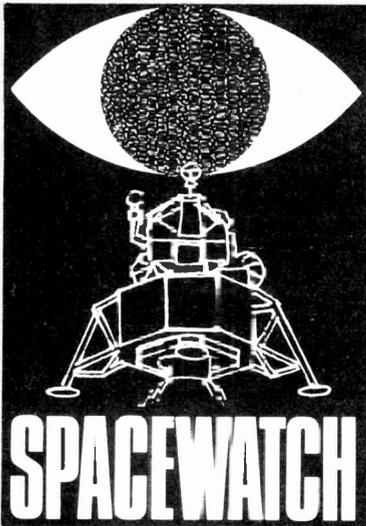

BY FRANK W. HYDE

BOULDERS OF SATURN

There has been confirmation of the reports, mentioned in the June issue, that the rings of Saturn were in fact large boulders. Measurements were made using the emission at 20 micrometre wavelength and the temperatures recorded were 89°K for the inner ring, 94°K for the middle ring and 89°K for the outer ring.

It appears that the measured temperature is dependent upon the angle the Sun makes with the rings. This fact is consistent with the boulders being of the order of 1m in diameter.

The fact that the shadow, which Saturn casts on the rings, affects the results is rather puzzling if the boulders are of the size suggested. However, there is an explanation and that is fine dust also present or alternatively that the inner ring is subject to bombardment by a particle zone similar to the Van Allen belts.

The work in this field was done by R. Murphy at the Mauna Kea observatory in Hawaii.

GRAVITY CONTROVERSY

There has been considerable controversy over the reality of the gravity waves which Weber insists he measures.

Studying new published data from the Bell laboratories, a team has made an analysis of Weber's events and has introduced the known data of geophysical and meteorological measurements and solar activity. So far there has been no confirmation and the work being carried out with new apparatus does not support Weber, in spite of its sensitivity.

This sort of investigation was also suggested by a group from Russia.

The Russians have already correlated solar activity and the variations of the magnetosphere as well as other phenomenon.

The results obtained seem to offer another explanation for the events which Weber records. The group at the Bell laboratories under Dr. J. A. Tyson have found evidence of correlation between the magnetosphere ring current and Weber's results. The extent of magnetic effects are global in extent and therefore account for the coincidences that are observed at Weber's two stations at Maryland and Argonne which are 1000km apart.

GEOMAGNETIC FLUCTUATIONS

Although Weber's instruments are magnetically shielded by steel in the form of a vacuum tank, it is suggested by the Bell team that this shielding may not be good enough at the very low frequencies involved in the geomagnetic fluctuations.

This suggestion is plausible because it could explain the daily variations that Weber observes and his interpretation too that these variations are from the galactic centre which is swept by the beams of his detectors every day.

In view of the American and Russian results, the explanation could as easily be that these changes are caused by the daily changes in the ionosphere caused by the Sun.

It is seriously suggested that the careful studies of Weber may be coloured by wishful thinking for no one could doubt the integrity of his work. The cosmologists may feel that the problems that would beset them, if Weber had proved to be right, have now been avoided.

ESRO AND SATELLITES

Magnetospheric studies have been a special programme of the European Space Research Organisation and the progress in this field was revealed recently at a symposium.

Data from the measurements and observations by ten satellites was made available. These included the results from *Heos-2*.

Some of the projects were a combined operation with *Heos-1* and *Iris*. This applied in particular to the penetration of the solar particles ejected when the Sun is active, through the magnetosphere to Earth.

It emerged from the observations that there was a peculiar precipitation pattern which formed over the

Earth's polar caps. Using *Heos-1* and *Iris* the particles could be studied in space, as well as close to the polar caps, at the same time.

The major advance in knowledge came from the results of *Heos-2*. The highly eccentric orbit of this satellite enables a region, not previously studied, 240 000km above the north pole to be explored. One of the outstanding discoveries was that the outer boundaries of the magnetosphere are some 30 per cent further out than was indicated by measurements from lower levels.

Another rather unexpected result was that it appeared that the magnetotail at the magnetopause contains a layer of electrons at energies higher than 1MeV.

Recently the neutral point on the magnetopause boundary has been studied in detail. A discovery was made here that the hot plasma comes down the cusp region at a magnetic latitude of 78°. A few degrees nearer the pole cold plasma in the ionosphere leaves to move into the geomagnetic tail.

JOINT PROJECTS

Future projects have been agreed and there is to be a joint project between ESRO and NASA for launchings in 1978 and 1979. One will be a heliocentric satellite and the data will deal with the interplanetary conditions and these will combine with the results from two others. Known as a mother and daughter pair, they will orbit close together near the Earth.

The correlation of the results of magnetic and particle measurements should resolve some of the present ambiguities. There will also be an intensive study using ground stations, balloon, rocket and satellite.

The satellite will be the *GEOS* to be launched in 1976. This will be the first geostationary satellite for Europe and will study the distribution of the thermal plasma and that of waves and energetic particles.

Many of these projected studies will be assisted by the *Skylab* programme and the shuttle programme.

There is now a great need for a settlement of the various theories and a sorting of the anomalies that exists. It is certain that some of the finer points of nuclear fission may well be revealed by the combined experiments to be made as well as completing knowledge about the interplanetary medium, the solar wind and the underlying basic measurements which are at present obscured by the equatorial electrojet and the auroral current. There are both chemical and mechanical means of achieving such objects.

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

CAR WIPER CONTROL

THE CIRCUIT in Fig. 1 was designed to overcome the shortcomings of a normal windscreen wiper set-up which does not have the facility for a slow wipe. The normal speed used in very fine rain causes the windscreen to smear and become too dry; the wiper blades judder and squeal, and their life is shortened considerably.

The circuit uses a simple u.j.t. oscillator to determine the wipe periods. The time interval is governed by the values and settings of R1, VR1 and C1. The unijunction fires when the voltage on C1 is approximately 0.7 of the supply voltage; this gives a period equal to the CR product. With the values given this varies from 2 to 22 seconds, a more than adequate range.

A linear potentiometer incorporating a switch, wired for fast wipe on switch-on, was used in the prototype unit. The scales shown in Fig. 2 show typical settings for alternative wiring for both linear and logarithmic potentiometers.

The "monostable" action of self-parking wipers is achieved with a switch connected to the wiper linkage, which is open when the wipers are at rest, see Fig. 3. This action is essential to the operation of the circuit; fortunately the vast majority of cars have self-parking wipers.

The current pulse in L1 is reflected in L2; CSR1 fires and latches on. The wipers start their cycle and switch S3 closes. The action of S3 closing puts a short across CSR1 and the current through it ceases and the thyristor switches off. The wipers continue their cycle and park normally.

As the starting surge of a wiper motor is very large a 16A thyristor was used. A heat sink for CSR1 was not used as it is only conducting for a short period at the start of each cycle and the continuous current is well below the rated value. It was decided to leave CSR1 in circuit all the time as the starting surge is well above the rating of the potentiometer switch.

A suitable pulse transformer can be made from 1½in of ferrite rod. L1 consists of 100 turns of 26swg enamelled copper wire and is covered with a layer of p.v.c. tape. L2 is wound in the same direction as L1 and consists of 150 turns of 26swg enamelled copper wire. The start of each winding should be marked with a spot of paint.

The indicator lamp could be omitted but was found to be useful, especially at low speeds when one can forget that the unit is operating after 21 seconds of nothing happening.

The only connections that need to be made to the car's electrical system are the negative earth, the positive supply from a convenient point (the "hot" wiper switch terminal), and points "A". In a car with two-speed wipers "A" should be on the lower speed.

N. E. Thomas,
London, S.W.17.

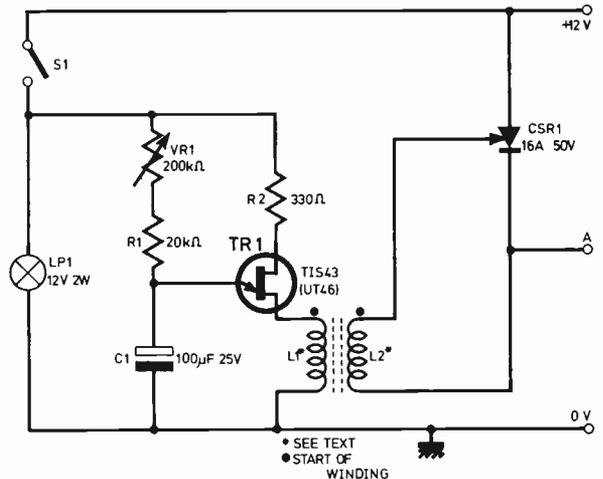


Fig. 1. Circuit diagram for unijunction car windscreen wiper controller

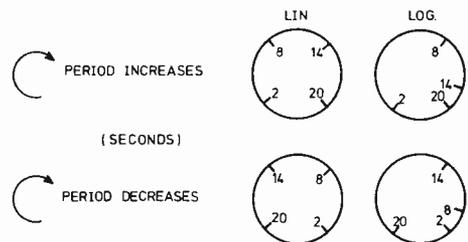


Fig. 2. Typical scale settings for linear and logarithmic potentiometers

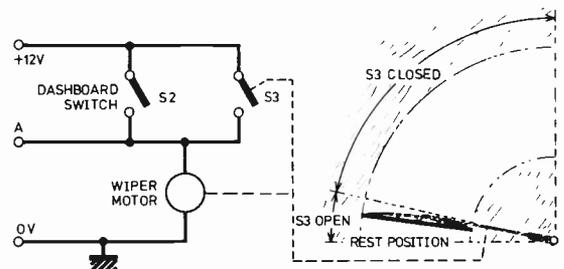


Fig. 3. Showing how the "monostable" action of the self-parking wipers is achieved

CBS SQ* FOUR CHANNEL DECODER AS SPECIFIED IN THE P.E. RONDO COMPLETE QUADRAPHONIC HI-FI SYSTEM

*REGD. CBS INC.

A COMPLETE KIT (RIGHT DOWN TO THE SOLDER) FOR THE HOME CONSTRUCTOR THAT CAN BE BUILT IN UNDER ONE HOUR WITH JUST A SOLDERING IRON AND A PAIR OF CUTTERS. JUST POP THE COMPONENTS INTO THE POSITIONS CLEARLY MARKED ON THE FIBREGLASS BOARD, CROP AND SOLDER. ALL COMPONENTS ARE OF THE HIGHEST QUALITY AND WITH CLOSE TOLERANCE PHASE SHIFT NETWORKS.

£8.00

POST FREE, INCLUDING CBS LICENCE FEE
+ 80p V.A.T.

DESPATCH GUARANTEED WITHIN 72 HOURS COMPLETE WITH LUCID INSTRUCTIONS

ANNOUNCEMENT

THE COMPLETE KIT OF PARTS FOR THE ENTIRE P.E. RONDO PROJECT WILL BE AVAILABLE FOR EACH STAGE AS IT APPEARS IN THIS MAGAZINE

*RETAIL TRADE ALSO GLADLY SUPPLIED

PHASE LOCKED LOOP STEREO DECODER

ANOTHER COMPLETE KIT THAT TAKES ABOUT 30 MINUTES TO BUILD. NO ALIGNMENT PROBLEMS AND COILS TO ADJUST. ONLY FOUR SIMPLE STEPS TO OBTAIN PERFECT STEREO FROM YOUR MONO TUNER.

1. CONNECT DECODER TO YOUR TUNER, POSSIBLY DISCONNECTING ONE OR TWO DE-EMPHASIS COMPONENTS.
2. PROVIDE +10 TO +16 VOLTS EITHER FROM YOUR TUNER OR SEPARATE POWER SUPPLY.
3. TUNE TO A STEREO BROADCAST.
4. TURN A PRESET RESISTOR UNTIL THE STEREO BEACON LIGHTS UP.

YOU THEN HAVE STEREO RADIO. COMPREHENSIVE INSTRUCTIONS PROVIDED BUT IF YOU ARE IN DOUBT JUST ASK US.

£3.40 POST FREE + 34p V.A.T.
(BEACON 34p + 4p V.A.T.)

BUILT AND TESTED

£4.40 POST FREE + 44p V.A.T.
(BEACON 34p + 4p V.A.T.)
EX-STOCK DELIVERY

SONAX ELECTRONICS

SPENCER HOUSE, BRETENHAM ROAD, EDMONTON
LONDON, N.18 TEL. 01-807 5544

Please send me:

SQ DECODER FOR P.E. RONDO
PHASE LOCKED LOOP STEREO DECODER
BUILT AND TESTED

Please tick

CHEQUE
P.O.
MONEY ORDER
ENCLOSED

NAME

ADDRESS

Block capitals please P.E.9

A DEXTER DIMMASWITCH

ALLOWS COMPLETE



LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.

600 watt £3.52 Kit form £2.97
300 watt £2.97 Kit form £2.42
All plus 12p post and packing
Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY

1 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED
TO N.M. GOVERNMENT
DEPARTMENTS, HOSPITALS,
LOCAL AUTHORITIES,
ETC.

4-STATION INTERCOM



£8.75

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft and other accessories. P. & P. 44p.

MAINS INTERCOM (new model)
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £16.40. P. & P. 60p extra.

INTERCOM/BABY ALARM



£4.65

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft connecting wire. Complete with battery. P. & P. 30p.

Transistor TELEPHONE AMPLIFIER



£3.99

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 24p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/9)
169 KENSINGTON HIGH STREET, LONDON, W.8



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

EMI 13 x 8, 3, 8 or 15 ohm	£3-03
EMI 13 x 8, 150 d/c 3, 8 or 15 ohm	£2-25
EMI 13 x 8, 450 v/w 3, 8 or 15 ohm	£3-00
EMI 13 x 8 type 350 8 ohm	£2-25
EMI 64in 8355 4 or 8 ohm	£2-60
EMI 8 x 5 d/cone roll/s 8 ohm	£2-50
Baker Group 25 3, 8 or 15 ohm	£5-00
Baker Group 25 3, 8 or 15 ohm	£7-50
Baker De Luxe 12in d/cone	£9-00
Baker Major 12in	£7-50
Kef T27	£4-87
Kef T15	£5-50
Kef B110	£9-10
Kef B200	£7-42
Kef B139	£10-72
Kef DN6	£1-82
Kef DN9	£4-12
Kef DN12	£2-37
Kef DN13	£2-75
Fane Pop 100W 8/15 ohm	£21-45
Fane Pop 50W 8/15 ohm	£12-28
Fane Pop 50W 8/15 ohm	£10-17
Fane Pop 25-2 25W 8/15 ohm	£5-94
Fane Pop 15W 8/15 ohm	£4-40
Fane Crescendo 15in 8 or 15 ohm	£27-50
Fane Crescendo 12A 100W 8 or 15 ohm	£24-20
Fane Crescendo 12B 75W bass 8 or 15 ohm	£24-20
Fane 807T 8in d/c roll/s 8 or 15 ohm	£3-16
Fane 808T 8in d/cone 8 or 15 ohm	£2-04
Goodmans Ascot 100 tweeter	£3-00
Goodmans 8P 8 or 15 ohm	£2-00
Goodmans 10P 8 or 15 ohm	£4-40
Goodmans 12P 8 or 15 ohm	£11-55
Goodmans 15P 8 or 15 ohm	£17-05
Goodmans 16P 8 or 15 ohm	£29-78
Goodmans Twinaxiom 8	£8-78
Goodmans Twinaxiom 10	£7-61
Elac 9 x 5, SRM109 15 ohm SRM114 8 ohm	£2-53
Elac 6 1/2in d/c roll/s 8 ohm	£2-32
Elac 6 1/2in d/cone 8 ohm	£2-50
Elac 4in tweeter TW4	£1-21
Wharfedale Bronze 8 RS/DD	£3-11
Wharfedale Super 8 RS/DD	£3-50
Wharfedale Super 10 RS/DD	£3-00
Coral 6 1/2in d/cone roll/s 8 ohm	£2-42
Siren 6 1/2in 3 or 8 ohm	£1-44
Richard Allan 12in d/c 3 or 15 ohm	£2-30
10in x 6in 3, 8 or 15 ohm	£1-82
8in x 5in 3 or 8 ohm	£1-30
7in x 4in 3 or 8 ohm	£1-38
2 1/2in 64 ohm or 70mm 80 ohm	86p
Adastru Hiten 10in 10W 8 or 15 ohm	£2-00
Eagle DT33 dome tweeter	£5-45
Eagle HT15 tweeter	£3-00
Eagle CT15 tweeter	£2-50
Eagle CT10 tweeter	£2-54
Eagle MHT10 tweeter	£3-74
Eagle FR4	£4-45
Eagle xover CN23 2B, 216	£1-15
Sp. matching transformer 3-15 ohm	£1-10
Celestion MF1000 25W horn 8 or 15 ohm	£10-45
Celestion PS8 (for Unilex)	£2-16
Celestion G12M 8 or 15 ohm	£15-00
Celestion G12H 8 or 15 ohm	£24-00
Celestion G15C 8 or 15 ohm	£33-00
Celestion G18C 8 or 15 ohm	£33-00


Car Stereo speakers—ask for leaflet

SPEAKER KITS

Wharfedale Unit 3	£8-25
Wharfedale Unit 4	£14-50
Wharfedale Unit 5	£21-00
Richard Allan Twinkit	£7-33
Richard Allan Triple 8	£18-78
Richard Allan Triple Assem	£16-20
Richard Allan Super Triple	£19-30
Goodmans DIN 20	£8-50
Fane Mode One	£3-90

Kefkit 2	£24-75
Kefkit 3	£26-50
Peerless 2-8	£5-50
Peerless 3-15	£10-45
Peerless 3-25	£16-00
Peerless 10-2	£2-47
Peerless 20-2	£10-41

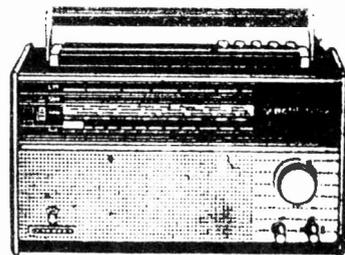Stephen speaker kits and cabinets—send for free booklet. Choosing a Speaker
PRICES INCLUDE VAT
Carriage and Insurance 50p per kit



RADIOS/CASSETTES/AMPS

Grundig Mariner TR855	£32-00
Grundig Party Boy 210	£28-00
Grundig Elite Boy 500	£24-00
Grundig Melody Boy 500	£24-00
Grundig Melody Boy 1000	£25-00
Grundig Yacht Boy 210	£31-00
Grundig RF430 mains	£23-75
Grundig RF310 mains	£21-00
Grundig Top Boy	£16-75
Grundig Satellite 1000	£116-00
Grundig C402 cassette	£27-00
Tandberg TP41	£37-75
Nordmende 7000	£87-00
BSF 9301 radio/cassette	£36-00
Bush RTP100 radio/cassette	£36-50
Tric KA2000A	£33-00
Tric KA2002	£41-00
Hitachi TRQ232S stereo cassette	£41-00
Hitachi TRQ257 cassette	£20-00
Hitachi KGT1210L radio/cassette	£37-50
Hitachi KN985	£18-70
ITT/KB Golf Preset	£21-25
ITT/KB Weekend Auto	£10-00
ITT/KB Europ	£18-00
ITT/KB SLS3 cassette	£22-82
ITT/KB Studio 60M cassette	£29-35
ITT/KB Studio 73 stereo cassette	£44-00
Koyo KTR1684 8 waveband	£40-00
Koyo KTR1770 11 waveband	£40-50

Prices include VAT.
Carriage and Insurance 50p FREE with each radio— Guide to Broadcasting Stations (160 pp)

PA/DISCO AMPLIFIERS (carr. and ins. £1)

Baker 100W	£46-00
Linear 30/40	£25-00
Linear 40/90	£30-00
Linear 80/100	£50-00

FREE with speaker orders over £7


"Hi Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and Insurance 25p per speaker (tweeters and crossovers 15p). ALL PRICES QUOTED INCLUDE VAT.

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF. Radios, etc.: 10 Swan Street, Wilmslow, Cheshire, SK9 1HF. Telephone: Wilmslow 29599.

LOGIC TUTOR EXPERIMENTS..

EXCLUSIVE OR FUNCTION

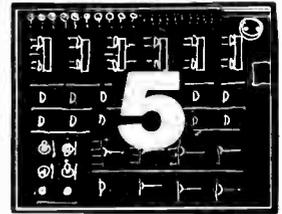

AN answer to last month's problem is shown in Fig. 5.1. In effect we are making two 3 input OR gates—using NAND logic—and then combining the outputs of these in a third OR gate. We rely on the Boolean Algebraic ASSOCIATIVE rule to permit this operation. As was the case when we simulated a six input AND we need a surprisingly large number of gates to carry out this simple operation. Frequently it is necessary to have a multi-input OR function in a logic system and many designers prefer to use discrete diode resistor logic followed by an inverter rather than integrated NAND gates when more than about four variables have to be ORed together.

EXCLUSIVE OR

This month we look at the EXCLUSIVE OR function. The normal OR truth table shows the output to be level 1 when both inputs are 1. To obtain EXCLUSIVE OR we must arrange that the output is 1 ONLY when one input OR the other is 1; when both are 1 the output must go to level 0 as shown in the truth table of Fig. 5.2. In Boolean terms we say the output (Q) is 1 when A is 1 AND B is 0 or B is 1 AND A is 0. This is written as $Q = A\bar{B} + B\bar{A}$.

It is easy enough to formulate a logic circuit that will do this using simple AND/OR/INVERT logic (Fig. 5.2.). This circuit can then be directly converted into NAND logic by substituting a NAND followed by an inverter for each of the AND gates and a NAND preceded by inverters to give the OR at the output. If you draw out the equivalent NAND circuit in full you will find that you have two pairs of inverters following each other; the effect of this is to cancel the inverting functions and the NAND circuit for EXCLUSIVE OR becomes that shown in Fig. 5.3. You can patch this up on Logic Tutor and verify that the output is 1 only when one or the other of the inputs is 1.

AN ALTERNATIVE CIRCUIT

Because EXCLUSIVE OR is a compound gate function there are various ways of arriving at a circuit that will produce the desired effect. One of the most economic ways—which is not so easy to arrive at—is shown in Fig. 5.4. This uses only four NAND gates but gives the same result as the previous circuit; try it on Logic Tutor and see. Try using Boolean

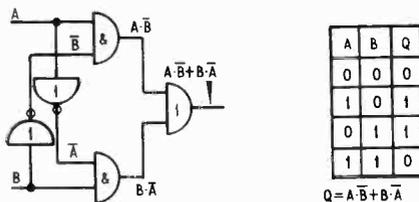


Fig. 5.2. EXCLUSIVE OR truth table and its representation in AND-OR-INVERT logic

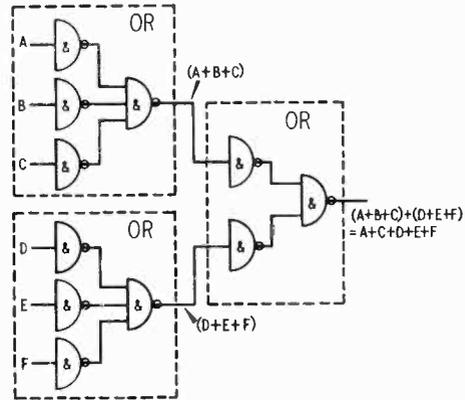


Fig. 5.1. An answer to last month's problem

Algebra and De Morgan's Theorem to show that the output is truly $A\bar{B} + B\bar{A}$ —some of the nodal expressions are given to help you. The full proof will be given next month. As an extra exercise see if you can devise any other circuits that will give the EXCLUSIVE OR function—try not to use more than six gates.

The EXCLUSIVE OR is sometimes called a "NON-EQUIVALENCE" gate. The reason for this is that you can say the output is 1 when the two inputs see different logic levels—when both inputs are the same the output goes to 0. It is thus a simple matter to convert an EXCLUSIVE OR into a comparator by inverting its output. A comparator gives an output of 1 when both inputs are the same.

by M. J. Hughes

Next month we will deal with the WIRED OR function.


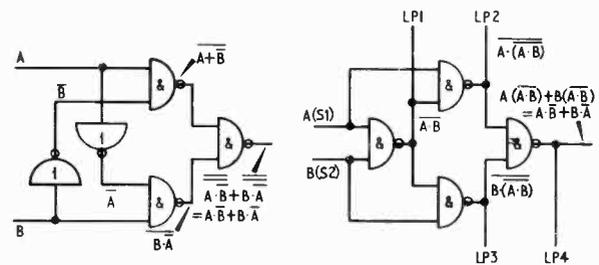


Fig. 5.3. The basic circuit of Fig. 5.2 in NAND logic showing the Boolean expressions at each node

Fig. 5.4. A more economical EXCLUSIVE OR—using four NAND gates. Use the Logic Tutor to verify the circuit is correct

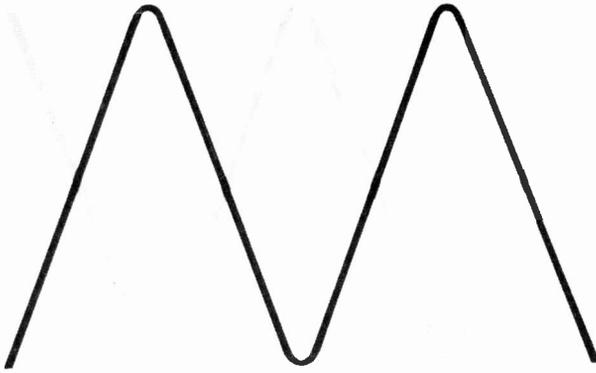

PHASING UNIT

BY D. BENFIELD

THERE is a continual demand for sound effects units which can be put together easily and cheaply by the home constructor. Indeed, it is this last feature, namely cost, which gives such devices an advantage over equivalent commercial units which are usually prohibitively expensive. To this end, the "phase box" about to be described has been made as simple as possible, consistent with an acceptable performance.

PRINCIPLE OF OPERATION

The essence of musical phase effect is to play a piece of music through two channels, with a slight time delay on one input.

To produce the required effect, the input signal is passed through a variable time delay network; the output from this is then mixed with the original signal which formed the input as shown in the block diagram of Fig. 1.

At a certain frequency, depending on the delay introduced, complete cancellation occurs during the mixing process and, by varying this frequency, the well known phasing effect is produced.

THE DELAY NETWORK

The basic circuit used to produce the required phase shift is shown in Fig. 2.

If equal amplitude sinewave inputs, of frequency f , are applied to "A" and "B," but with the input to "B" inverted with respect to "A," then the output will also be of the same amplitude, but will have a phase lag of $2 \tan^{-1}(2\pi fRC)$ degrees.

Note that when $2\pi fRC = 1$, then the phase lag is 90 degrees. Thus, assuming we have suitable anti-phase driving signals at our disposal, we can cascade two such networks and, at a frequency given by $f = 1/2\pi RC$ we would get a total phase lag of 180 degrees.

Such antiphase signals are easily obtained by using a single transistor stage with equal emitter and collector resistors. Omitting biasing arrangements, we have the circuit of Fig. 3 for a single stage of our two-stage phase delay network.

The required phasing effect is obtained by varying the frequency at which cancellation occurs in the mixer stage; this is most easily altered by making R a variable component, which means a dual-gang potentiometer since two stages are being used.

FULL CIRCUIT

The phase delay is introduced by the circuitry around TR1 and TR2 as in Fig. 4. TR3 acts as an emitter follower so that a reasonably high impedance is presented to TR2 collector circuit, in order to isolate this stage from the low input resistance of the mixer.

The operating conditions for TR1 are set up by R1 and R2, while direct coupling through VR2a and R5 to TR2 base enables further bias chains and coupling capacitors to be eliminated; similar remarks apply to TR3 stage. This does mean, however, that there is a risk of unpleasant "plops" being produced should a slider of VR2 become momentarily disconnected. To overcome this, the unused ends of VR2a, b tracks should be connected to their respective sliders, and so maintaining a bias path for TR2 or TR3.

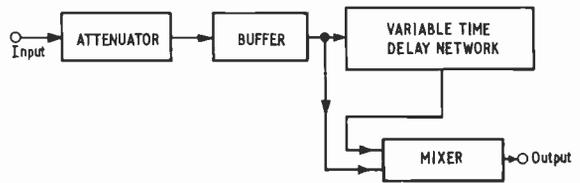


Fig. 1. Block diagram showing principle of operation


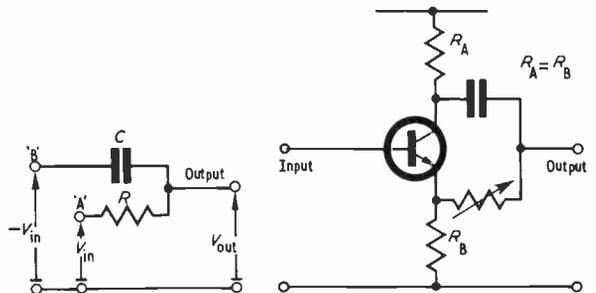


Fig. 2. The basic phase shift network employed

Fig. 3. Circuit for producing antiphase signals

COMPONENTS . . .

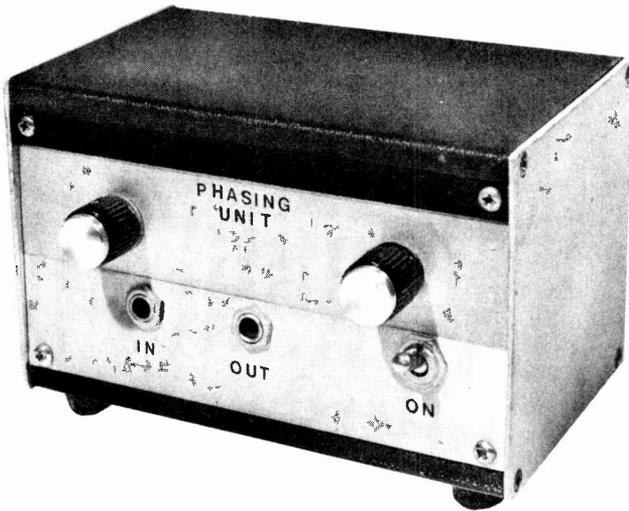

Potentiometer VR1 provides a means of controlling the output level from the unit, by attenuating the input signal. This method is to be preferred here since it enables high level sources to be used without overloading the unit, which could occur if the level control were placed at the output.

The mixer circuit uses a single transistor, TR4. Bias conditions are maintained by the potentiometer formed by R10 and R11. By this means the collector potential is set at approximately five volts, regardless of supply voltage variations.

The inputs—direct signal and phase delayed signal—are applied to the two capacitors C2 and C3. Compensation for any difference in signal level can be provided by making either or both input resistors variable.

CONSTRUCTION

The original was assembled on a small piece of 0.1in matrix copper clad Veroboard, as this permits a neat and compact layout—see Fig. 5.

Resistors

R1	100k Ω	R7	1k Ω
R2	47k Ω	R8	220 Ω
R3	1.5k Ω	R9	470 Ω
R4	1.5k Ω	R10	15k Ω
R5	220 Ω	R11	100k Ω
R6	1k Ω	R12	2.7k Ω

All resistors are $\frac{1}{8}$ W 10% carbon

Potentiometers

VR1	5k Ω log pot
VR2a, b	10k Ω + 10k Ω linear dual-gang
VR3	10k Ω linear carbon preset

Capacitors

C1	6.4 μ F, 25V elect.
C2	6.4 μ F, 25V elect.
C3	6.4 μ F, 25V elect.
C4	6.4 μ F, 25V elect.
C5	0.1 μ F, mylar
C6	0.1 μ F, mylar

Transistors

TR1-TR4 BC168 (4 off)

Switch

S1 Double pole on/off toggle

Miscellaneous

JK1, JK2 Standard jack sockets (2 off)
B1 PP3 9V, battery connectors, 0.1in Veroboard
Instrument case 6 $\frac{1}{2}$ in \times 4in \times 4in (G. W. Smith)


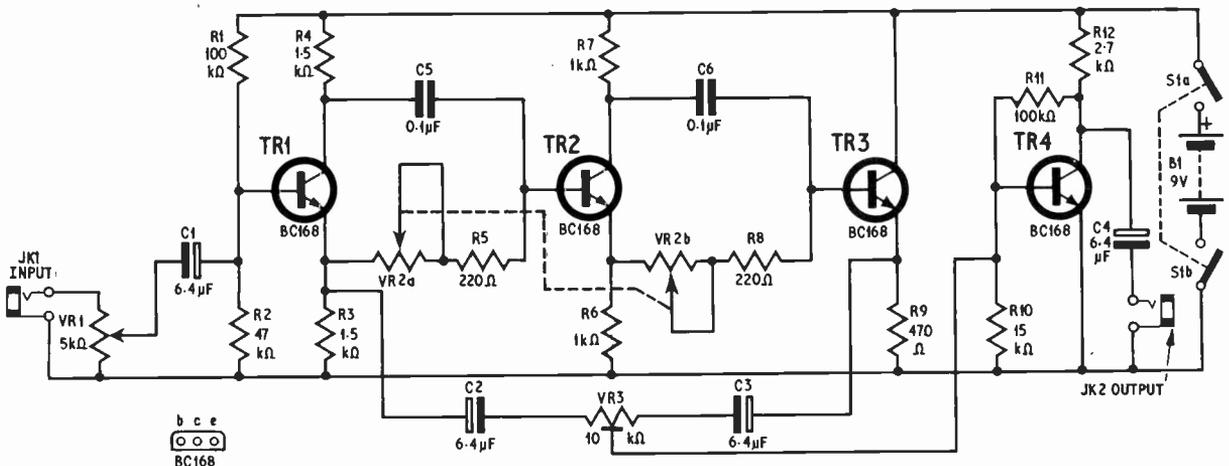
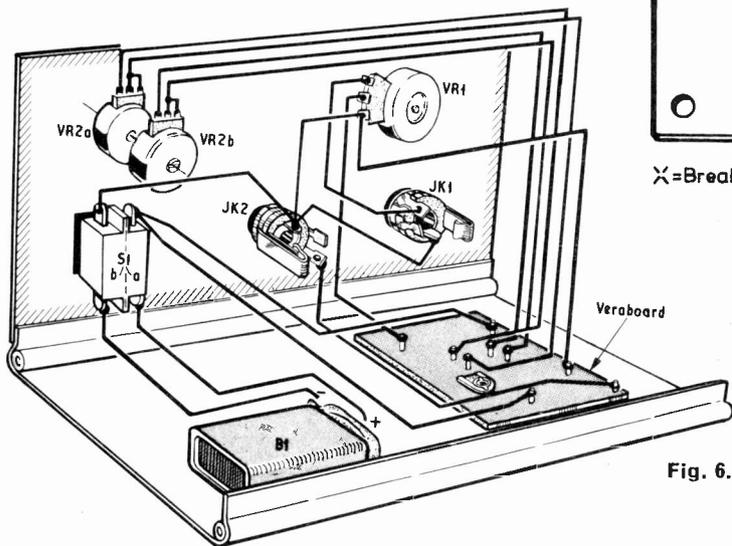


Fig. 4. Circuit diagram of Phasing Unit

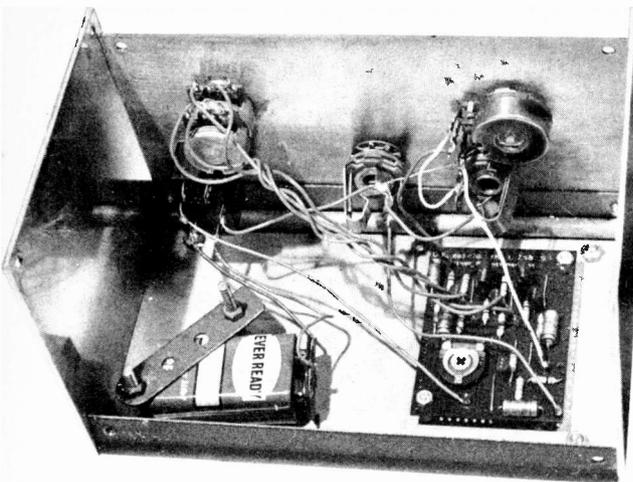

The final wiring to input, output, VR1, VR2 and on-off switch can now be carried out; Fig. 6 shows the chassis mounted component connections.

The unit is conveniently powered by a small nine volt battery, but it will work from any supply between six and twenty volts. Current drain is approximately five milliamps from a nine volt supply.

SETTING UP

Initially set VR3 to mid-position and both panel controls to their extreme counter clockwise positions. Switch on and check that current drain is about 5mA, using a suitable meter in series with the supply.

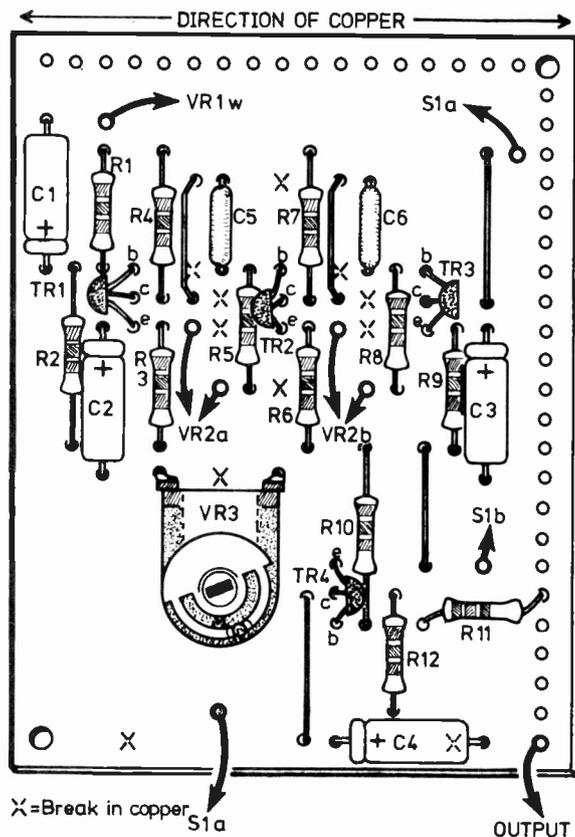


Fig. 5. Component layout and wiring on 0.1in matrix Veroboard

Fig. 6. Complete interwiring detail

The input should now be connected to a source of "white noise." Failing this however, an f.m. receiver which is not tuned to any station makes a very good substitute here. Set the level control to a convenient position whereupon the characteristic hiss should be heard.


Rotate the "phase" control VR2 to its extreme position; some sort of phasing may be heard but not much. Rotate this control back about $\frac{1}{8}$ of a revolution. Preset VR3 should now be adjusted for a minimum noise level, the correct position being fairly well defined. Upon rotating the phase control VR2 back and forth, the familiar phasing effect should now be heard. If this is not the case, check all connections, especially the links on the circuit board.

The unit may now be tried out with music input from, say, a tape recorder. The final degree of phasing heard depends largely on the content of the music used; Pop records provide a suitable starting point with their varied frequency content, and on some of these the effect can be quite startling. ★

PE Sound Synthesiser 8

ENVELOPE SHAPER

By G.D. SHAW

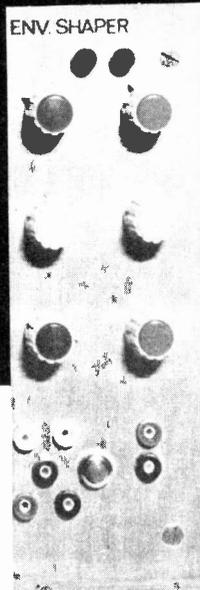

ONE of the fundamental characterising parameters of a sound is that in which the audibility of the sound varies with time. Some sounds become audible very rapidly and almost immediately die away again whilst others make a relatively slow approach to their full volume and take an even longer period to die away. The loudness modulation of any sound is known generally as the envelope and is very important in providing a feature which allows of recognition. Changes in the envelope format of an otherwise well-known sound can often change the character of the sound completely.

A simple experiment designed to illustrate this latter point involves the use of a tape recorder and a piano. Make a recording of a series of notes or chords selected from various parts of the piano register and repeat these with the sustain pedal held down. The recording should now be replayed backwards. With a four track recorder the simplest way of doing this is to unthread the recorder without rewinding, reverse the position of the spools and thread up again putting a twist in the tape so that the shiny, or backing side of the tape is towards the heads. This particular method results in a considerable loss of sound quality but illustrates the characteristic quite well. If the constructor is fortunate enough to own a mono or two track recorder in addition to a four track the recording should be made on the former machine and replayed, with spool positions reversed, on the latter.

PIANO ENVELOPE FORMAT

The change in the original sound of the piano, on reverse replay, will be found to be quite remarkable and, depending on the octave and sustain given to the original note or chord, will be found to bear a close resemblance to other musical instruments such as the organ or cello.

The piano is particularly suited to this form of experiment due to the nature of its envelope format which is characterised by a rapid rise to full volume followed by a relatively long period, dependent upon sustain pedal use, during which the volume is gradually diminishing. Fig. 8.1 illustrates a simplified form of piano envelope.

The peak volume followed by a rapid partial decay to the gradually diminishing sustain is a characteristic common to many musical sounds which are initiated by a form of percussion. Instruments such as the triangle, timpani, cymbal, glockenspiel and so on, all display similar basic characteristics in their envelopes.

Apart from the particular form of the percussive envelope the majority of sound envelopes will fall somewhere within the range of shapes illustrated in Fig. 8.2 all of which may be considered to be derivations of the basic trapezoid shown in Fig. 8.3.

The Envelope Shaper in the Sound Synthesiser is essentially a trapezoid generator in which the attack, sustain, and decay parameters are all adjustable, within the limits of the controls, to provide a range of formats similar to those illustrated in Fig. 8.2.

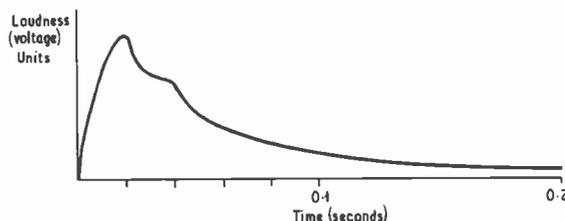


Fig. 8.1. Typical piano envelope



Fig. 8.2. Simplified range of sound envelope formats

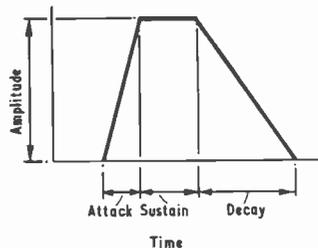


Fig. 8.3. Basic envelope trapezoid

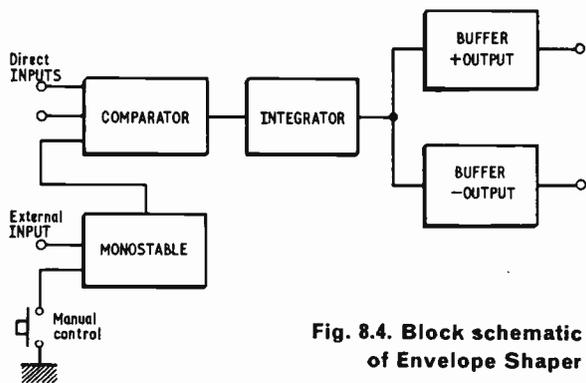


Fig. 8.4. Block schematic of Envelope Shaper

BLOCK SCHEMATIC

A schematic arrangement of the envelope shaper is shown in Fig. 8.4. The heart of the circuit is an integrator which drives two buffer amplifiers providing independent positive and negative going envelopes. The integrator itself is driven by a comparator having a variable reference level and thus any change in the input signal level to the circuit as a whole has no effect on the overall envelope amplitude. The comparator may be triggered directly by an external signal or via a monostable with a variable timing period.

CIRCUIT DIAGRAM

Fig. 8.5 shows the theoretical circuit of the envelope shaper. IC1 is the comparator which has a reference level set by R5-VR1 and ranging between 0V and -5V. Thus the comparator will recognise only negative going signals which exceed the reference level, and, with no signals present, will normally sit at its negative saturation state. Four triggering modes are catered for and selected by S1.

In the first the comparator is triggered directly by external signals arriving at the inverting input via R1 and R2.

Triggering is accomplished in the second mode by means of the keyboard synchronising pulse which is routed via R3. The pulse level swings between +10V and will thus override any other trigger signal less than -10V arriving at the comparator via R1 and R2. Equally, it is possible to combine keyboard synchronisation with other external signals providing that the peak value of these exceeds -10V.

In the third mode of operation the comparator is triggered by a capacitively coupled monostable (IC5) which is, in turn, triggered by negative going transitions in signals arriving at the external socket.

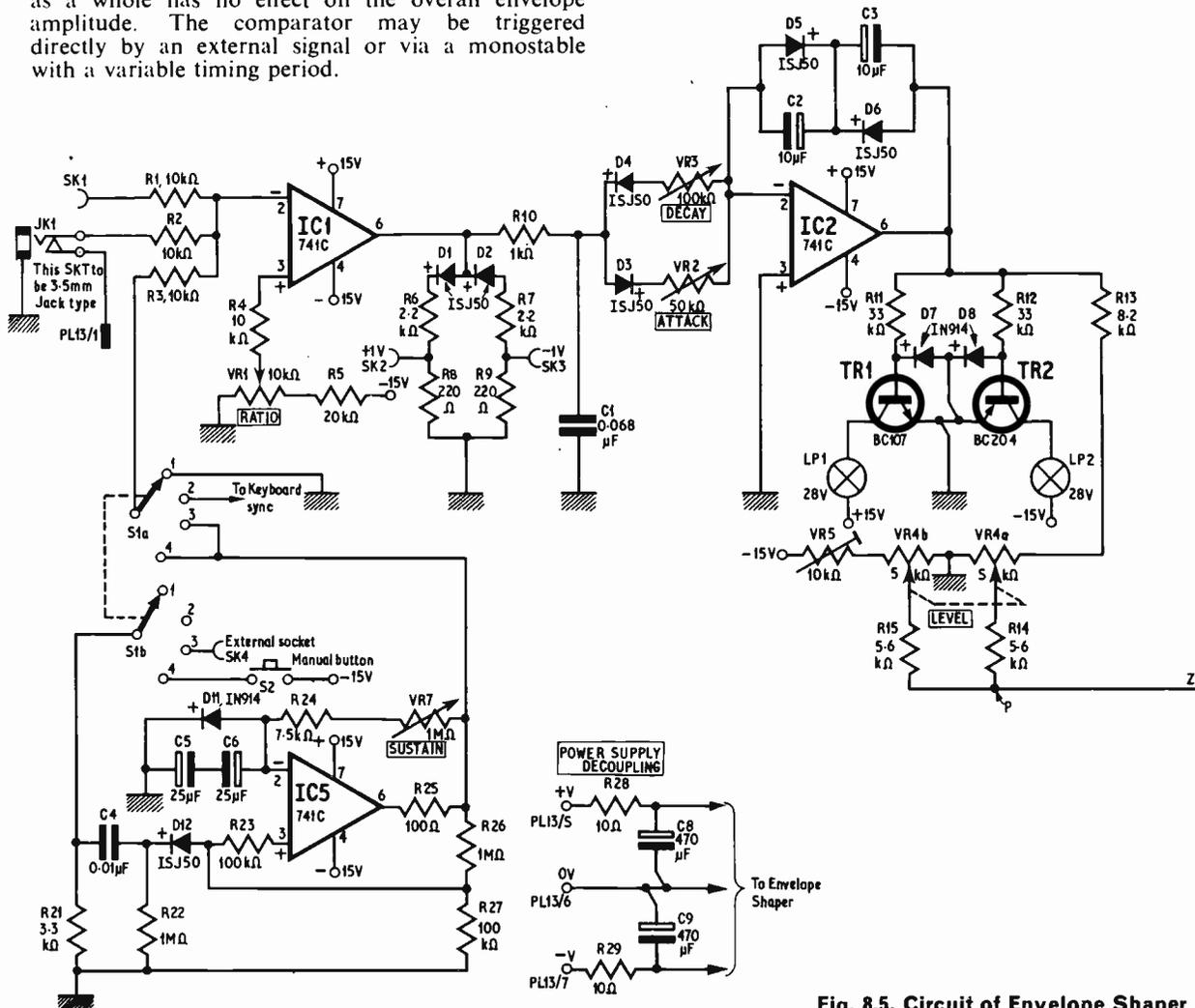


Fig. 8.5. Circuit of Envelope Shaper

In this latter mode the pulse level of the monostable swings between $\pm 14V$ and thus effectively overrides all other signals arriving at the comparator inputs.

Finally, in mode four, the monostable is triggered manually by means of a push button. In modes three and four the on period of the monostable is controlled over 100/1 range by means of VR7 and, with the value shown, can be varied between 15mS and 1,500mS. Since the shortest period of sustain is less than the combined fastest attack/decay time of about 20mS the resultant envelope is slightly lower in amplitude than it would otherwise normally be. However, for most purposes this may be adequately compensated for by adjustment of the envelope level control (VR4).

SIGNAL ROUTING

Output signals from the comparator are routed via R10 and D3/VR2 or D4/VR3 to the inverting input of the integrator built around IC2. In the absence of signals into the comparator, the provision of a negative reference level means that the comparator normally sits at negative saturation and the integrator at positive saturation. A negative-going signal greater than the reference level causes the comparator to change states and the positive going pulse is routed into the integrator via D3/VR2 and charges C3. When the trigger signal is removed, or changes polarity, C3 discharges via VR3/D4 and R10 and the original situation is restored.

The rate at which C3 charges and discharges is governed by the setting of VR2 and VR3 respectively. With both controls at minimum the fastest rate of attack or decay is determined by R10 and, with the values shown, is about 10mS. Thus the attack time can be varied by VR2 between 10mS and 500mS while the decay time can be varied by VR3 between 10mS and 1000mS.

The sustain period of the envelope signal may be varied in two ways. In the first, the on time of the comparator output pulse is determined by the period of that part of the input signal which lies above the reference level. The on time may thus be varied by adjustment of the ratio control VR1 in those instances when the comparator is triggered directly by an external signal.

In the second case the comparator is triggered by a monostable either from within the envelope shaper (IC5) or from the keyboard. In each case the on period is determined by adjustment of the monostable sustain control.

BUFFER AMPLIFIERS

The output from the integrator is routed to two buffer amplifiers of unity gain. IC3 is wired as a follower whilst IC4 forms an inverting amplifier. Interposed between the integrator and output buffers is a balancing divider network comprising R13, VR4a/b, VR5, R14 and R15.

The purpose of this network is to drop the integrator output swing to a usable level and to balance its maximum positive transition with an equal value negative voltage supplied via VR5/VR4b. Thus with the integrator sitting at positive saturation the output voltage of the network, measured at point P in the circuit, is effectively zero. Taking into account the forward drops of diodes D9 and D10 the buffer outputs will therefore swing between zero and about 3.2V.

INDICATOR LIGHTS

An indication of the state of the integrator is provided by two lamps which are switched by TR1 and TR2. With the integrator sitting at positive saturation TR1 is turned on and LP1 lights thus indicating an envelope off situation. When the integrator changes state TR1 is biased off thus extinguishing LP1 while TR2 is turned on and LP2 lights up indicating an envelope-on state.


The provision of two indicator lights is useful in those circumstances in which the envelope shaper is being operated by external signals direct into the comparator. Here the lights can provide a visual measure of the envelope on/off times in relation to the frequency of the triggering signal. For the majority of other purposes however the envelope off indicator may be considered superfluous and may be omitted from the circuitry to serve the requirements of economy. The circuit elements involved are LP1, TR1, D7 and R11.

Finally it is often useful to be able to synchronise the beginning and end of an envelope with other modules in the synthesiser. To this end diodes D1 and D2 together with dividers R6-8 and R7-9 provide pulses of 1V amplitude direct from the comparator output. As with the envelope off indicator these particular components are not necessary to the operation of the envelope shaper as such and may be omitted if automatic programming is not to be the principal function of the module.

Fig. 8.6 shows the recommended circuit board layout for the envelope shaper while Fig. 8.7 gives details of front panel and McMurdo plug wiring.

MODULE CONSTRUCTION

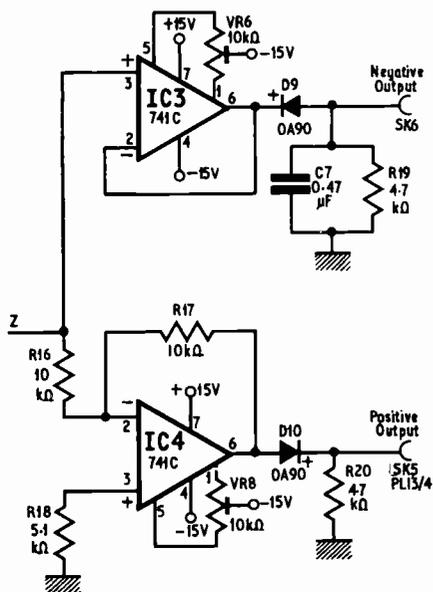Construction of the module is quite straightforward and the only critical requirement lies in the wiring of VR4a/b and the setting up of the associated



COMPONENTS . . .

ENVELOPE SHAPER

Resistors

R1-R4	10k Ω (4 off)
R5	20k Ω
R6, R7	2.2k Ω
R8, R9	220 Ω (2 off)
R10	1k Ω
R11, R12	33k Ω (2 off)
R13	8.2k Ω
R14, R15	5.6k Ω (2 off)
R16, R17	10k Ω (2 off)
R18	5.1k Ω
R19, R20	4.7k Ω (2 off)
R21	3.3k Ω
R22, R26	1M Ω (2 off)
R23, R27	100k Ω (2 off)
R24	7.5k Ω
R25	100 Ω
R28, R29	10 Ω (2 off)

All 5% $\frac{1}{2}$ watt carbon

Capacitors

C1	0.068 μ F polyester
C2-C3	10 μ F elect. 25V (2 off)
C4	0.01 μ F polyester
C5, C6	25 μ F elect. 25V (2 off)
C7	0.47 μ F polyester
C8-C9	470 μ F elect. 25V (2 off)

Potentiometers

VR1	10k Ω linear min. moulded carbon
VR2	50k Ω linear min. moulded carbon
VR3	100k Ω linear min. moulded carbon
VR4	5k Ω linear ganged moulded carbon
VR5-VR6	10k Ω carbon preset (2 off)
VR7	1M Ω linear
VR8	10k Ω carbon preset

Integrated Circuits

IC1-IC5 741C (5 off)

Transistors

TR1 BC107
TR2 BC204

Diodes

D1-D6	1SJ50 (6 off)
D7, D8	IN914 (2 off)
D9, D10	OA90 (2 off)
D11	IN914
D12	1SJ50

Miscellaneous

LP1, LP2 28V sub-miniature lamps (2 off)
SK1-SK6 2mm miniature sockets (6 off) JK1-
3.5mm miniature jack socket, S1-2 pole 6 way
switch S2-miniature push button switch.

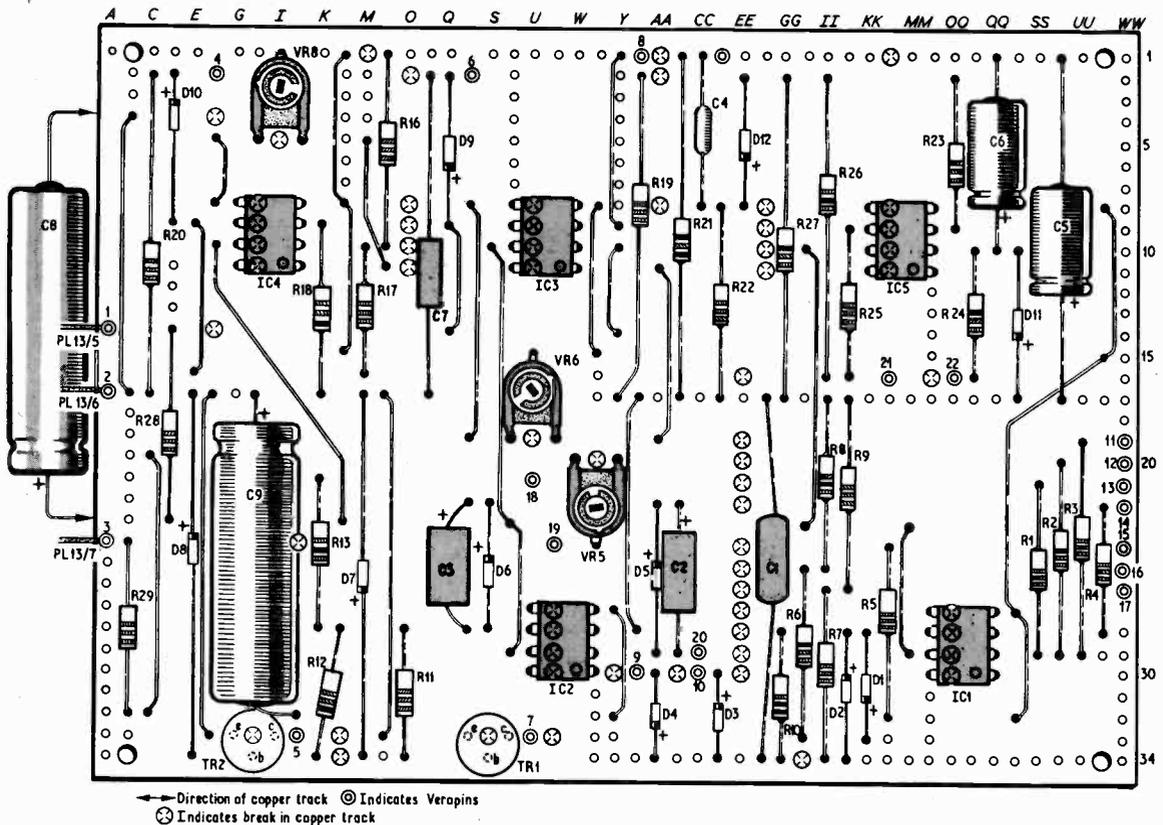


Fig. 8.6. Board layout and wiring

balancing divider. This may be done as follows. With power on, put S1 in the direct mode and set VR1 to its maximum setting. This will ensure that the integrator is sitting at positive saturation. Set VR5 to near mid-position and with VR4 at its maximum setting connect a high resistance voltmeter (5V range) between point P and ground. The voltmeter should read approximately 2.5V negative. Adjust VR5 to bring the voltmeter reading as close to zero as is possible.

Reset VR4 to minimum and progressively reduce the sensitivity of the voltmeter adjusting VR5 as necessary to maintain a zero-volt reading. This latter manipulation serves to adjust and compensate for the minimum end resistance of VR4 which should remain at its minimum setting for the next stage of adjustment. Remove the high resistance voltmeter and re-connect between the output of IC3 and ground. Connect point P directly to ground and adjust VR6 so that the output of IC3 is zero.

Repeat the measurement with the voltmeter connected between the output of IC4 and ground making any necessary adjustments to VR8 in this case. It should be borne in mind that variation of

the offset presets VR6-8 will result in an output voltage change of only a few millivolts, a 400 millivolt swing being typical when the amplifiers are run at unity gain. If the voltmeter is insufficiently sensitive it will be necessary to use an oscilloscope for this latter measurement. It is important that the measurement be made at the output pin of the buffer amplifiers as opposed to the output socket. Disconnect point P from ground and, with all other controls as initially set, swing VR4 to its maximum position and observe the change in output voltage, if any, at the output pins of IC3 and IC4.

If the overall change is within 400mV the error may be halved by adjustment of VR5 and the remaining 200mV error reduced, or eliminated, by adjustment of the offset controls VR6 and 8 on IC3 and IC4 respectively. If the error is greater than 400mV it will be necessary to adjust the value of R13 accordingly. This latter course, however, is unlikely to be necessary since the two halves of a ganged pot would normally be expected to be taken from the same batch of stators and consequently the resistive tolerance of both halves is likely to be within fairly close limits.

The adjustments detailed above are only critical if it is envisaged that the envelope shaper be used for v.c.o. programming in addition to its main purpose of amplitude modulation.

USING THE MODULE

In most commercially available synthesisers the envelope shaper usually incorporates a voltage controlled amplifier as an integral part of the circuitry. In the Sound Synthesiser however the envelope shaper is treated as a discrete entity in the interests of simplicity and thus it is not possible to route signals through it in the same way as is featured in the Moog or EMS range of instruments. Thus the description of usage of the module in this particular article will be restricted to v.c.o. programming and covered at greater length in next month's article which deals principally with the Voltage Controlled Output Amplifiers.

Reverting for a moment to the description of the operation of the Envelope Shaper it will be recalled that the envelope is initiated when the comparator switches from one saturation state to the other and that the period of sustain is essentially governed by the time for which the comparator is in its temporary state. Thus, since the attack period of the envelope occurs during the on time of the comparator, it follows that the overall sustain of the envelope is equal to the on time of the comparator less the period of attack.

This particular point is quite important because under certain conditions the set period of attack could be greater than the on time of the comparator. This means that C3 does not become fully charged and thus the envelope does not achieve its full amplitude. Fig. 8.8a illustrates the effect when, with the comparator being triggered by a repetitive signal, its on time is gradually increased either by increasing the period of the triggering signal or by adjustment of the ratio control.

If the input signal is derived from, say, two Ramp Generators and the Sample and Hold in combination and the combined amplitude adjusted such that only the peaks are greater than the comparator reference level, the resultant signal from the envelope shaper will resemble that shown in Fig.

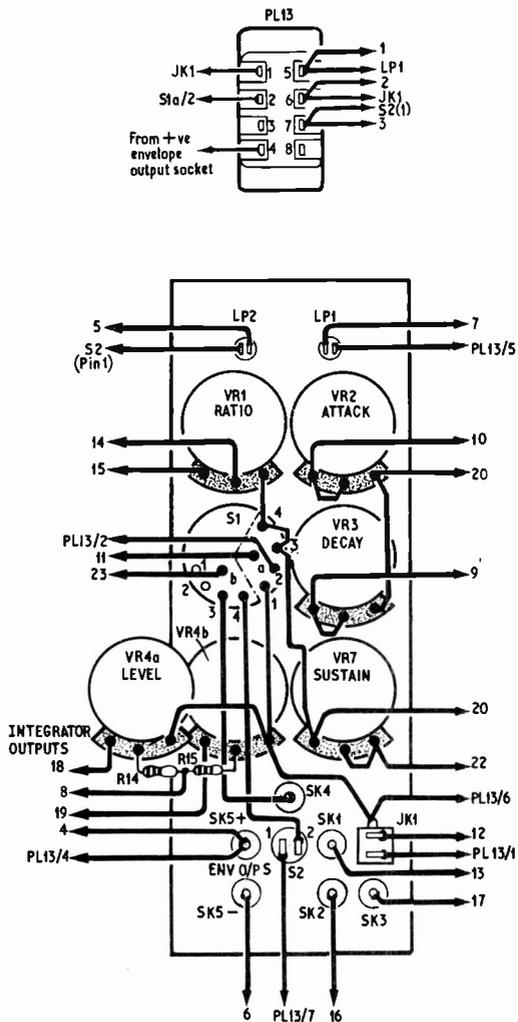


Fig. 8.7. Front panel control layout and wiring

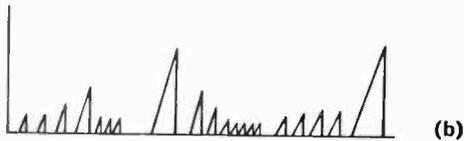
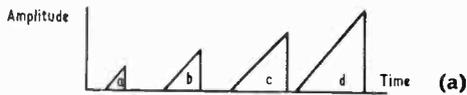


Fig. 8.8(a). Showing the effect when the attack time is longer than the on time of the comparator. Greatest effect is at 'a' and increasing the on period progressively through 'b', 'c' and 'd' increases the envelope amplitude; (b) typical envelope series resulting from the above

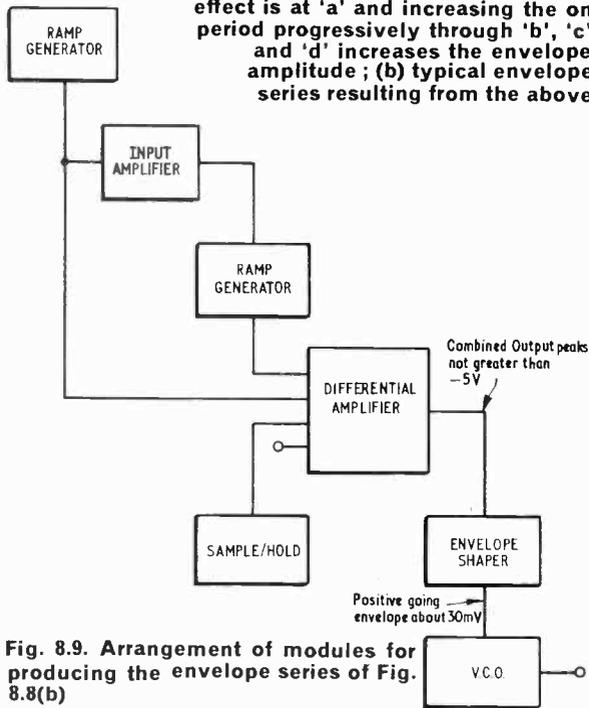


Fig. 8.9. Arrangement of modules for producing the envelope series of Fig. 8.8(b)

8.8b. If the positive going waveform is now used to program a v.c.o. which has been manually set to its maximum frequency the resultant output can be adjusted so as to provide a variety of birdsong which is very realistic. Fig. 8.9 shows a typical arrangement of modules for the provision of this type of sound.

SHIP'S SIREN

Sounds resembling a ship's siren may be synthesised by routing the envelope shaper direct to a v.c.o. and programming the envelope manually. The various controls should be set as follows: SW1 (Mode) = manual; Attack = Maximum; Decay = Minimum; Sustain = Midway; Output Level = 1/20 rotation (0.5 on a ten-point, 270 degree calibration). Use the negative going envelope and adjust the programmed v.c.o. to minimum frequency.

If the v.c.o. output is routed via the reverberation amplifier a high degree of realism may be achieved. Remember that the input to the reverberation amplifier should not exceed 500 mV peak-to-peak.

Next month: The voltage controlled output amplifiers and differential amplifier.

NEWS BRIEFS

Open University Course in Electronics

A NEW post-experience course by the Open University entitled "Electromagnetics and Electronics", aims to provide an understanding of the scientific basis of electronics and electronic circuit design. The course is intended for higher level university study in science and technology and for those who need a knowledge of electronics but who do not intend to study at a higher level.

The course assumes little prior knowledge of electronics or electromagnetics but does assume a background of scientific or technical education beyond GCE "O" level.

The course consists of 17 written correspondence units linked to 17 television and five radio programmes.

Applications are now invited for the course which starts next February and lasts until November. As with all post-experience courses no formal academic qualifications are needed. They are self-contained courses designed to teach new developments or update knowledge of a subject. The course tuition fee is £45 plus £37 for the residential summer school. Application forms are available from the Post-Experience Student Office, P.O. Box 76, Milton Keynes, MK7 6AA.

British Missile Technology for U.S.A.

UNDER a licence agreement signed in London between Marconi Space & Defence Systems Ltd. and the Raytheon Company of Massachusetts, British guided missile technology is to be sold to the U.S.A.

This agreement will enable a joint programme to be conducted between Raytheon and British industry to develop a new, medium-range, all weather, air-to-air missile based on the U.S.-Raytheon AIM-7E Sparrow, to be built in Britain by Hawker Siddeley Dynamics Ltd.

Improved Accuracy of Electrical Measurements

THE National Physical Laboratory's Division of Electrical Science have announced that, due to recent advances in measurement techniques, they are able to improve the uncertainties they are able to give in respect of a wide range of measurements. These uncertainties are offered for the calibration of high quality reference standards.

For example the uncertainty in the 1V d.c. reference has been reduced from 2 in 10^6 to 1 in 10^6 ; that of a one ohm resistance from 1 in 10^6 to 4 in 10^7 .

Bulgin Distributors

FOR those readers who have difficulty in obtaining Bulgin components we publish below a list of their current distributors for London and the Home Counties: Cables & Components Ltd., Park Avenue, London, NW10 7XN.

Home Radio (Components) Ltd., 234-240 London Road, Mitcham, Surrey, CR4 3HD.

Lugton & Co. Ltd., 209-212 Tottenham Court Road, London, W1A 2BN.

Norman Rose (Electrical) Ltd., "Norman House", 8 St. Chads Place, Grays Inn Road, London, WC1X 9HJ.

Duval Ltd., 44 George Street, Oxford.

S.D.S. (Portsmouth) Ltd., Hulsea Industrial Est., Portsmouth, PO3 5JW.

IT'S A SELECTIVE ISSUE - NEXT MONTH

FREE IN THE OCTOBER ISSUE
P.E. AUDIO I.C.
IDENTICHART

Whether you are thinking of building an amplifier or you want some ideas on using i.c.s in audio circuits the P.E. Audio I.C. Identichart is a must for you. It gives comprehensive data on over 80 i.c.s ranging from low level preamplifiers to hybrids rated at 50W. As well as data, the chart contains suggestions for using i.c.s in mixers, tape recorders, record players, etc.

Semiconductor Tester

Select—Match—Compare and measure your discrete semiconductors. A general purpose discrete semiconductor tester capable of measuring the main parameters of transistors, rectifier and signal diodes, Zener diodes, thyristors and unijunctions, as well as providing both voltmeter and ammeter functions as an added bonus.



PRACTICAL ELECTRONICS keeps you abreast of Technology

Part Two of the P.E. Rondo Quadraphonic system takes you through the audio amplifier sections of four solid-state 20W power amplifiers.

PLUS

This month we start a new series on Phase Locked Loops, the technology which makes state-of-the-art equipment like the Rondo and other a.m./f.m. systems possible.

PRACTICAL ELECTRONICS

OCTOBER ISSUE ON SALE SEPTEMBER 14, 1973



AUDIO LOGIC PROBE

BY B. WOODLAND

SIMPLE logic probes such as are used for troubleshooting in logic integrated circuit projects generally consist of a single transistor amplifier driving a lamp display. A logical 1 lights the lamp while a logical 0 has no effect.

The major drawback of such probes is the necessity to divide one's attention between the display and the equipment under test. In a complex system it is difficult to watch displays of both probe and equipment, especially if manipulations to the system are necessary to expose the faults.

The probe detailed here was devised to overcome these difficulties whilst retaining relative simplicity and low cost. A high frequency tone is emitted when the probe detects a logic 1 and a lower frequency indicates a logic 0. As a bonus the probe will give positive indication of short duration pulses which are extremely difficult to detect by other methods.

PRINCIPLE OF OPERATION

A complete circuit diagram of the probe is shown in Fig. 1. Four NOR gates are capacitively coupled in pairs to form two free running multivibrators running at two easily distinguishable audio frequencies. Neither multivibrator is able to oscillate unless its unused input (labelled X and Y) is at logical 0.

When the function switch is in the logic position the input to the lower frequency oscillator (G3 and G4) is connected directly to the probe sensor so that a logic 0 input (at Y) will sound the lower tone.

The higher frequency generator input (X) is connected indirectly to the sensor, the transistor TR1 acting as an inverter so that a logic 1 at the sensor causes a logic 0 at point X causing the higher frequency to be generated. (The preset VR1 is used to adjust the logic 0 output of TR1 to less than 0.4V with a 2.4V input, 2.4V being the minimum TTL logic 1).

AUDIO OUTPUT

The outputs of the two audio oscillators are applied to the inputs of a simple gate made from two silicon diodes. The resultant output is amplified by TR2. Strictly speaking no amplifier is needed to drive the recommended transducer (a crystal insert) but its inclusion does allow for the substitution of a medium impedance earphone for more volume.

PULSE POSITION

When the function switch is in the pulse position the probe sensor is connected to the clock input of a TTL bistable (IC2). Even a very short pulse on the sensor will cause the bistable to change state with the accompanying change in tone frequency.

POWER SUPPLY

If the suggested crystal insert transducer is used then the probe needs to be supplied with 5V at 20mA. This quite modest demand is best supplied by the circuit under test and the construction shows two crocodile clips for this purpose.

If a loudspeaker or earpiece is to be used then a separate battery supply is recommended, with the necessary changes in construction to accommodate it.

CONSTRUCTION

The circuit is built on a small piece of 0.1in Vero-board with the strips running across the width, see Fig. 2. The integrated circuits are soldered directly to the board to keep the profile low. Single cored sleeved wire is used for interwiring, the function switch and the insert being the only components not accommodated on the board.

The probe is housed in a 6in aluminium tube of 1in internal diameter. This was in fact a tube used to hold denture cleaning tablets. The crystal insert is glued to the closed end of the tube, its leads passing through holes drilled in the tube. The power supply leads pass through a hole in the side protected by a grommet. Use highly flexible and good length leads as are used on multimeters.

The sensor consists of a 2in length of brass stud-ding bolted to the plastic cap of the tube. The function switch is fixed as shown, and the circuit board is inserted into the tube after first being wrapped in a piece of plastic sheet to act as insulation. Keep leads from the circuit board to the switch and the sensor as short as is practicable.



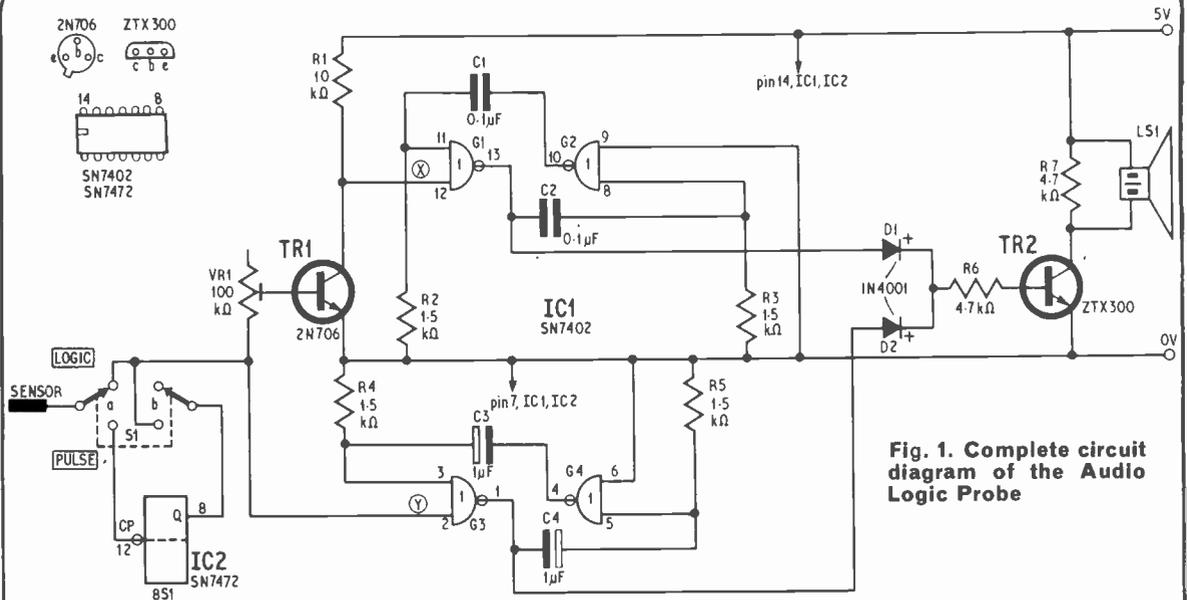


Fig. 1. Complete circuit diagram of the Audio Logic Probe

COMPONENTS . . .

Resistors

- R1 10k Ω
- R2-5 1.5k Ω (4 off)
- R6, R7 4.7k Ω (2 off)
- All $\pm 10\%$ $\frac{1}{4}$ W carbon

Potentiometer

- VR1 100k Ω miniature preset

Capacitors

- C1, C2 0.1 μ F (2 off)
- C3, C4 1 μ F 6V electrolytic (2 off)

Semiconductors

- TR1 2N706 or similar
- TR2 ZTX300 or similar
- D1, D2 1N4001 or similar (2 off)
- IC1 SN7402N
- IC2 SN7472N

Miscellaneous

- LS1 1in diameter crystal insert
- S1 D.P.D.T. miniature slide switch
- 3.6in \times 1in 0.1in Veroboard, strips running widthwise
- Brass studding and nuts, crocodile clips, aluminium container

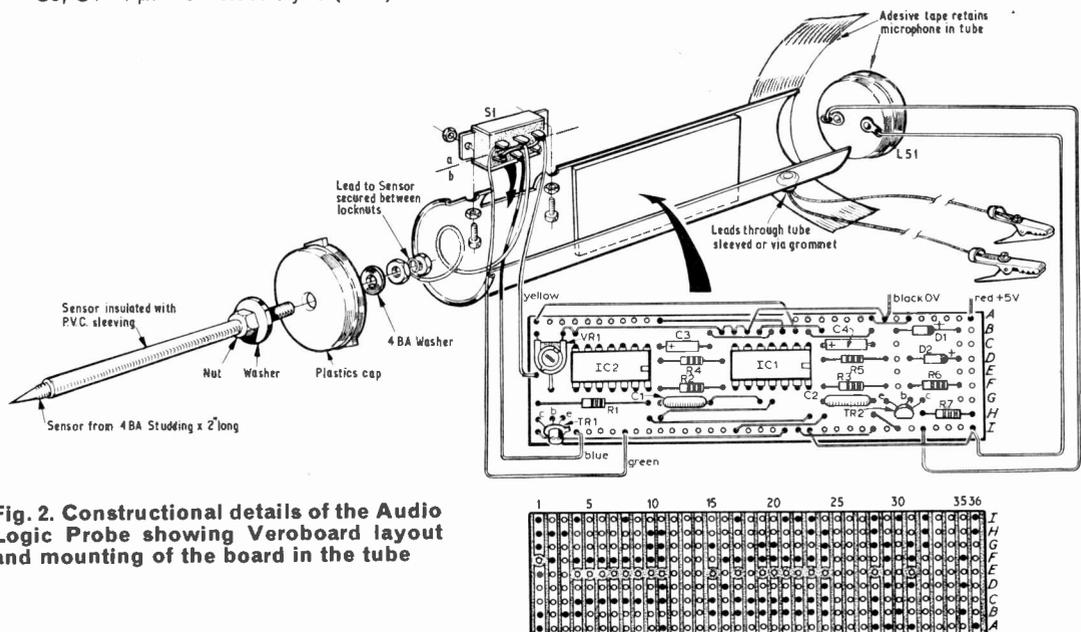


Fig. 2. Constructional details of the Audio Logic Probe showing Veroboard layout and mounting of the board in the tube

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit-£29.95! (INC.VAT)

The Cambridge – new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price – and by building it yourself you can save a further £14!

Truly pocket-sized


With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$. That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16 batteries which give weeks of life before replacement.

Easy to assemble

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

The cost? Just £29.95!

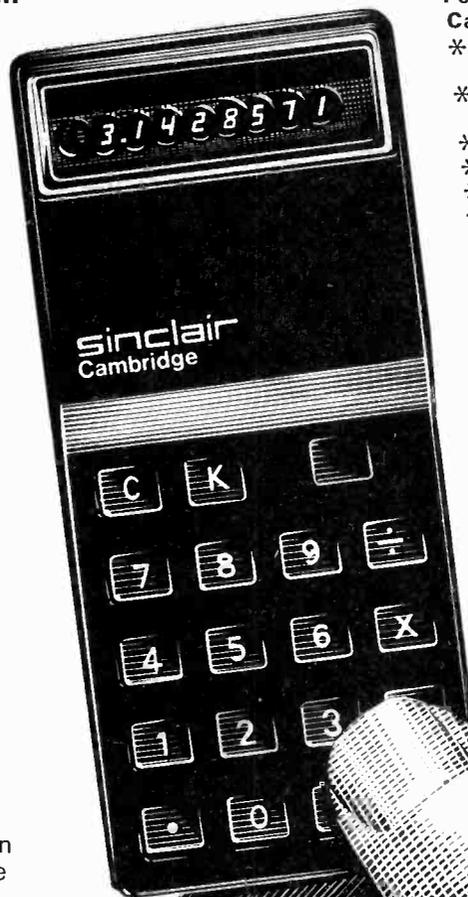The Sinclair Cambridge kit is supplied to you direct from the manufacturer – you can't get it anywhere else. Ready assembled, it costs £43.95 – so you're saving £14! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge

- * Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- * Calculates to 8 significant digits, with exponent range from 10^{-20} to 10^{79} .
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16 batteries. (Replacement set costs about 15p.)

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents:


1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more out of your money's worth.

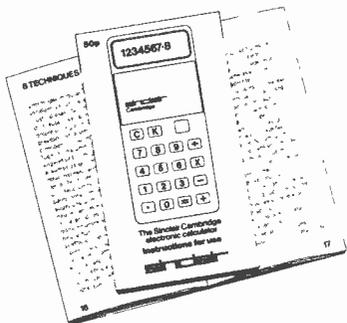But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations like:

Logs Sines Cosines
Tangents Reciprocals nth roots
Currency conversion interest
and many others...

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no: 699483 England
VAT Reg. no: 213 8170 88

Practical Electronics September 1973

Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And you benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form: £27.23 + £2.72 VAT. (Total: £29.95)

Price fully built: £39.95 + £4.00 VAT. (Total: £43.95)

To: Sinclair Radionics Ltd, London Road, St Ives, Huntingdonshire, PE17 4HJ		PE 973
Please send me	Name	_____
<input type="checkbox"/> a Sinclair Cambridge calculator kit at £27.23 + £2.72 VAT (Total: £29.95)	Address	_____
<input type="checkbox"/> a Sinclair Cambridge calculator ready built at £39.95 + £4.00 VAT (Total: £43.95)		_____
*I enclose cheque for £ _____, made out to Sinclair Radionics Ltd, and crossed.		_____
*Please debit my *Barclaycard/Access account. Account number _____		_____
*Delete as required.		_____
		PLEASE PRINT

NEW DEVICES ... APPLICATIONS

SEMICONDUCTOR GAS SENSOR

In this section we present a selection of both new devices and applications, with news of applications developed for existing devices.

Generally only basic circuit details will be given sufficient for the experimenter to create his own equipment.

THE GAS SENSOR used in the Electronic Nose (July 1973) is a device which is probably new to most readers and thus warrants a more detailed description. The sensor to be described (T.G.S.) is manufactured by Figaro Engineering, a firm based in Japan.

The T.G.S. consists of two electrodes encapsulated in a bead of bulk-type crystalline semiconductor material

heater, the driving voltage being between 1.0 and 1.5 volts. The nominal resistance of the filament is 2 ohms. The value shown for R_L is typical for low voltage applications.

When first switched on the sensor shows high conductivity until warmed up sufficiently for combination with oxygen to occur. It then settles down to a low "in air" output (see Fig. 3).

The T.G.S. will react to all the common combustible gases and vapours, for example hydrogen, propane, butane, petrol fumes, methane (natural gas), acetone benzene, etc. It will also respond to carbon monoxide, making it suitable as a smoke detector.

The sensor will not discriminate between gases but reacts to the total deoxidising effect.

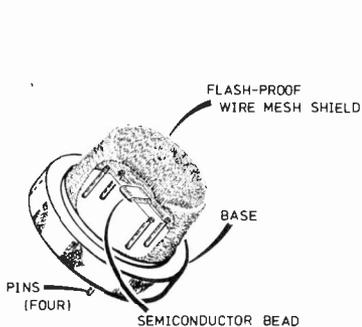


Fig. 1. Construction of the T.G.S. gas sensor

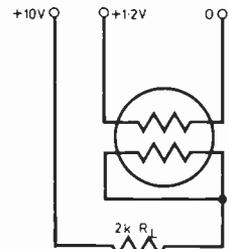
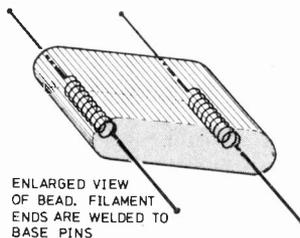


Fig. 2. The simplest circuit for use with the T.G.S

as shown in Fig. 1. This material is based on tin oxide (SnO_2) suitably doped and of n -type character.

When heated in the presence of oxygen—as happens when heated in air—anionic absorption of oxygen takes place on the surface of the material leading to a drastic reduction in the number of free electrons available and hence reduced conductivity. In contact with a deoxidising gas or vapour, cationic absorption occurs and the number of free electrons increases as does conductivity.

The sensor can be compared to a "gas dependent resistor" and the circuits built around them are similar to those built around light dependent resistors.

SIMPLE CIRCUIT

The simplest type of circuit is shown in Fig. 2 where it can be seen that one of the electrodes acts as a

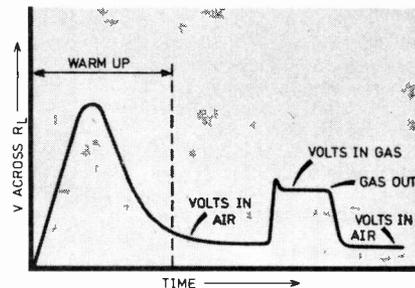


Fig. 3. After switch-on the conductivity of the sensor rises sharply as shown in this graph. After warm-up the typical response to a gas is shown

PRACTICAL POINTS

The device is symmetrical; either filament can be used as the heater. The recommended side for use as the heater is marked with a small circle punched on the screen base. The T.G.S. base will plug into a B7G valve base.

To avoid cooling of its surface the sensor should be shielded from exposure to draughts or high velocity gas flows.

The T.G.S. works equally well on a.c. or d.c., and polarity is unimportant. Fig. 4 shows a basic circuit using a.c. rather than d.c. as the source. For battery operation a dropper resistor is the easiest but the most wasteful way of obtaining a heater voltage. Other methods include d.c./a.c. inverter or separate battery, e.g. NiCad.

If an amplifying circuit is coupled to the sensor, then the total load resistance of the sensor must be kept at the recommended value (2 kilohms), i.e. if the input tends to shunt the load resistor, then the load resistor should be increased to restore the total resistance to the required value.

After storage or when the T.G.S. has been switched off for some hours, the device will conduct heavily at switch-on until its temperature has enabled the semiconductor to stabilise in air. On completion of initial stabilisation the device will only conduct the presence of deoxidising gases (see Fig. 3).

As in all semiconductors some spread of characteristics occurs and so some adjustment should be built into the circuit for calibration purposes.

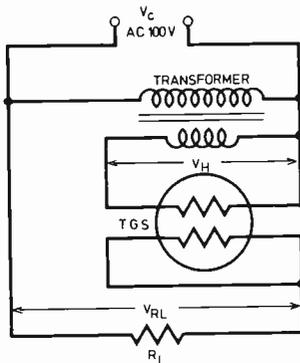


Fig. 4. This circuit shows how the T.G.S. may be used with an a.c. system

ALARM LEVEL

For domestic and marine use an alarm level of 0.2 to 0.3 per cent is recommended. This represents about $\frac{1}{5}$ of the lower explosive level in the case of bottled gas and $\frac{1}{20}$ of the lower explosive level for methane (natural gas).

The gas sensor described in this article is available from the following advertisers in P.E.—Trampus Electronix, Watford Electronics, Yates Electronics.

● PRACTICAL ELECTRONICS will be publishing another project using the gas sensor in the near future. ★

ALL READERS PLEASE NOTE

If you know someone (young or old) who would like to take up electronics as a hobby, you can do them a good turn. Bring to their attention our companion magazine EVERYDAY ELECTRONICS which specialises in simple projects and elementary theory.

The September issue contains these fascinating and inexpensive projects.

- ◆ *A Personal M.W. Radio*
- ◆ *Aquarium Thermostat*
- ◆ *Model Train Controller*

STARTING ELECTRONICS FROM SCRATCH

In the October issue, EVERYDAY ELECTRONICS launches an exciting new series explaining in simple terms basic theory and describing simple experiments that can be performed by the beginner.

Remember, Teach-In'74 starts in the October issue of EVERYDAY ELECTRONICS.

No one interested in learning about electronics can afford to miss this vital series.

THE GOOD COMPANIONS



Two magazines designed to complement each other in every way—together satisfying the needs of everyone involved in electronics.

PE

September EE on sale Friday, August 17




ELECTRONORAMA

THE loading of the cable ship *Mercury* (8,962 tons) with the first 200 miles of a £30 million telephone cable linking Britain and Canada was completed at Southampton on June 20. Handling more than 1,800 telephone conversations simultaneously the cable, CANTAT-2, will be the biggest single telephone cable across the Atlantic, carrying more telephone calls than all the existing trans-Atlantic cables combined. The cable system will be used for communication between the U.K. and mainland Europe, and Canada and the U.S.A. and will come into service early in 1974.

GROWTH IN CALLS

Being financed and operated jointly by the British Post Office and the Canadian Overseas Telecommunications Corporation, the 3,000-mile cable is being provided to meet the massive growth in telecommunications between Britain and North America. In ten years 'phone calls between Britain and Canada have risen eightfold from

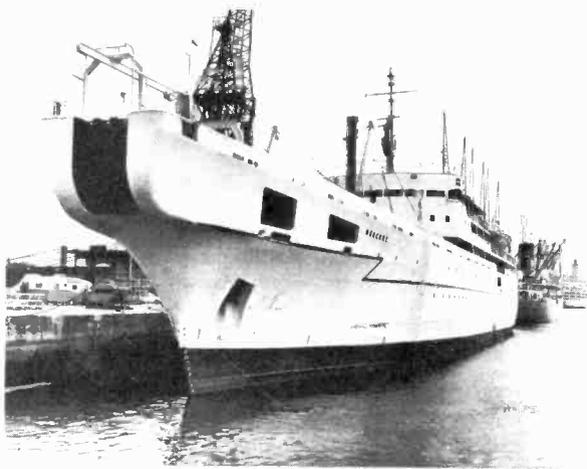The cable ship *Mercury* being loaded at the quayside at STC's Southampton plant



135,000 calls a year in 1962 to their present level of more than a million a year. This will rise again to nearly 6 million a year by 1980. Growth in calls between the U.K. and the U.S.A. has risen from half-a-million in 1962 to more than 4½ million in a year in 1972, and by 1980 this will have reached 24 million a year.

The laying of CANTAT-2, which is being manufactured by the submarine systems division of Standard Telephones and Cables Ltd., comes 20 years after Britain and the U.S.A. decided to lay the first telephone cable across the Atlantic.

Each circuit in the first telephone system cost at the time more than £294,000. In CANTAT-2 the application of modern transmission techniques has dramatically reduced the cost of each circuit to £16,500. This has been an important factor in keeping down the cost of trans-Atlantic telephone calls.


CABLE ROUTE

CANTAT-2 will run from Widemouth Bay, Cornwall to Beaver Harbour, near Halifax, Nova Scotia. It will be laid by two ships, *Mercury* and the Canadian icebreaker/cable layer *John Cabot*. Both ships are fitted with a new design of linear cable engine developed by the Post Office Research Department, and which considerably speeds cable laying.


Mercury is to lay more than 2,600 nautical miles from the U.K. and across the North Atlantic Ocean. Because of the high risk of damage by trawlers the cable is to be buried beneath the seabed where it crosses the rich fisheries of the Canadian continental shelf.

The powerful *John Cabot*, equipped with a seabed plough and assisted by a manned miniature submarine, has already started to bury a 170-mile section of the cable. A similar submarine will be used to bury some sections of cable on the U.K. continental shelf.

Mercury, laying the deep-water section of CANTAT-2, has been fitted with one of the most accurate navigation systems commercially available to enable her to chart the cable route with extreme accuracy. The system, called Hydroplot, was developed for the Hydrographic Department of the Royal Navy and uses U.S. Navy navigation satellites to pinpoint the ship's position to within 300 feet. An Elliot 905 computer integrates all the ship's other navigation aids and cable-laying information and provides a visual display unit for the navigator.

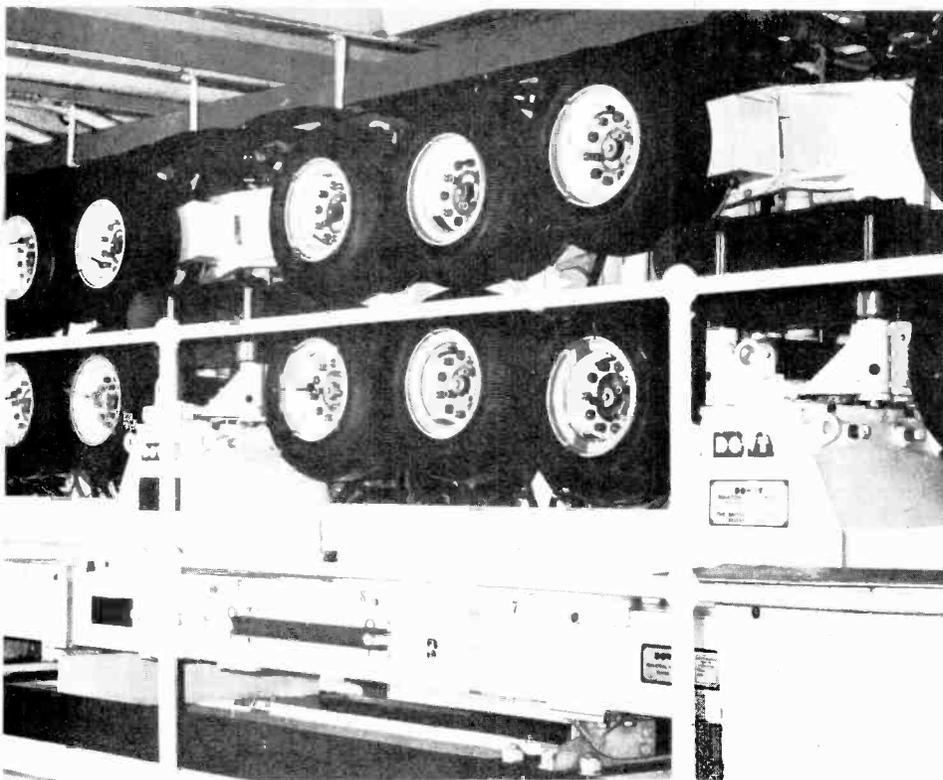

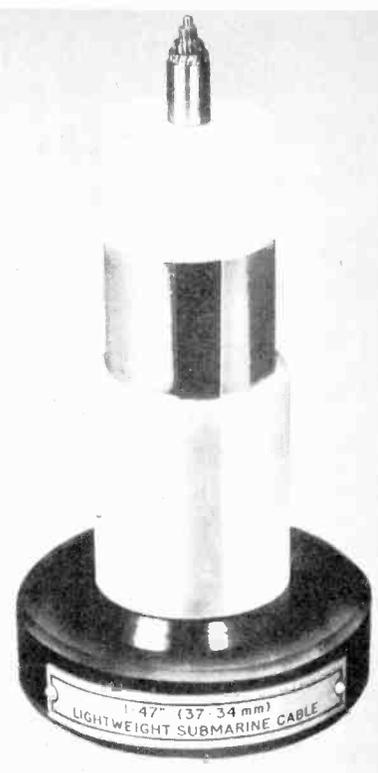The linear cable engine for drawing cable from the ship's storage tank and paying it out to the ocean floor. The wheels can expand to accommodate the torpedo shaped equalisers or repeaters



A sample of the submarine cable for deep water. External armour is added for the shore end lengths.

A specially clothed operative assembling a repeater



REPEATERS AND EQUALISERS

In order to amplify the telephone signals on their long journey, 473 special amplifiers, or repeaters, are used each being spaced at 6 mile intervals. Since these units are expected to work on the ocean floor for periods up to 25 years, quality control and testing is naturally very stringent with manufacture taking place in special clean areas.


Every 15 repeaters in the cable length an equaliser is used. These are to compensate for the small differences that occur between the gain characteristics of the repeaters and the loss characteristics of the cable sections. These can be affected by sea temperature and pressure. Inserting equalisers into the system approximately every 15 repeaters overcomes such problems. As the system is laid it is continuously monitored and tested and the data collected is used in the design and building of the final circuitry for the equaliser while the cables are at sea.

Splicing the cable into each repeater also takes place on board.

CIRCUITS

CANTAT-2's 1,840 circuits are arranged as 23 super-groups, transmitting in the frequency band 312-6,012kHz in the U.K.-Canada direction and 8,000-13,700kHz in the Canada-U.K. direction. In addition four speaker circuits of nominally 3kHz bandwidth each, use the frequency bands 6,024-6,036kHz in the U.K.-Canada direction and 7,976-7,998kHz in the Canada-U.K. direction, for system and circuit maintenance.

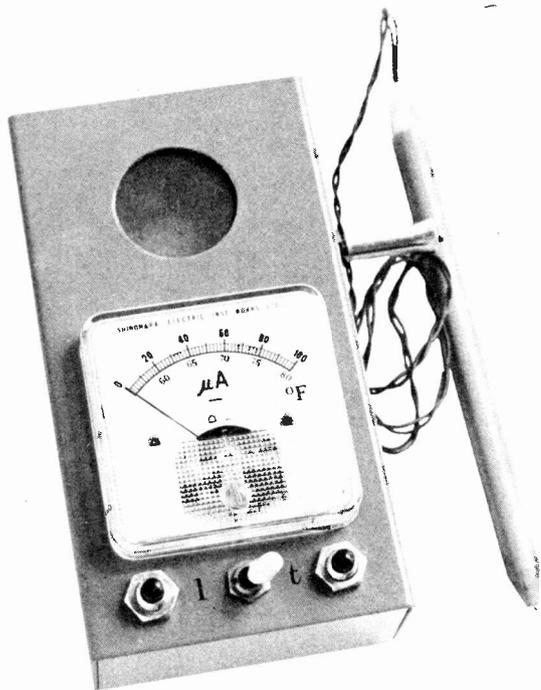The cable itself is predominantly of lightweight design and will weigh no more than five tons a mile. Less than two inches in diameter for most of its length the cable has an outer conductor of aluminium. Its strength is centred in a steel rope inside an inner copper conductor. External armour will be used to protect the cable at the U.K. shore end.



ENLARGER EXPOSURE METER & THERMOMETER

BY J.M. BARTLETT

FOR the photographer who develops and prints his own negatives there are two factors that are vitally important. The first is the temperature of the chemicals, and a thermometer is an absolute must at every stage. Developing, rinsing, fixing, and finally washing must all be done at known and controlled temperatures; in colour developing the entire process must be carried out in five or more separate operations with all the liquids controlled to within half a degree Fahrenheit of each other.

This article describes an electronic thermometer with a sensing time of only two to three seconds and a potential accuracy of 0.2 degree F, so that quick and accurate checking can be made without wondering if the thermometer has "settled down".

Secondly, the exposure time required for enlargements is usually obtained after a time consuming test strip has been made. This unit also incorporates an enlarger exposure meter that senses the amount of light in the centre of interest, or a mid tone grey area, so that a proof print can be obtained first time.

BASIC BRIDGE CIRCUIT

Both circuits have been designed around the basic bridge circuit. In Fig. 1, voltages V_A and V_B are developed in the left arm and right arm respectively. When $V_A = V_B$ no current flows in the meter and the bridge is said to be balanced. (This is when $R_A/R_B = R_C/R_D$.) If V_B falls then current will flow in the meter, the deflection set by R_M (the total resistance in the meter arm, including the internal resistance of the meter).

If the current in the two arms is very much higher than the current through the meter, then the small amount of meter current will have no significant effect on V_A and V_B . Since in these circuits the sensing components draw a current comparable to, or less than, the meter, special circuits are used to ensure that the bridge operates properly.

EXPOSURE METER

The exposure meter circuit is that part drawn above the meter in Fig. 2. It is operated by S1, a push button which ensures that the circuit is active only when required, and a long battery life is possible.

Zener diode D1 supplies a semi-stabilised voltage of 5.6V (nominal), making the response stable even with an ageing battery. VR1 and R2 form the left side of the bridge circuit (similar to R_A and R_B) but because of the high resistances involved with the light sensor one of the "special circuits" must be used.

The light sensing is done by a photo conductive cadmium sulphide (CdS) cell, an ORP 12, referred to as PCC1 on the circuit diagram, which has a resistance of nearly 10 megohms in total darkness.

As light strikes the sensitive area its resistance drops, but with the very low light intensities of interest (0.01 lux to 0.8 lux) its resistance does not drop below about 100 kilohms. The current through

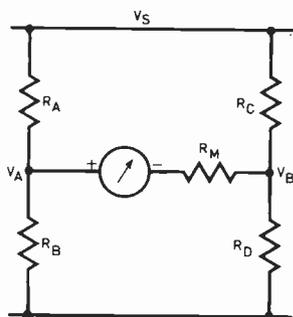


Fig. 1. Basic Wheatstone Bridge circuit

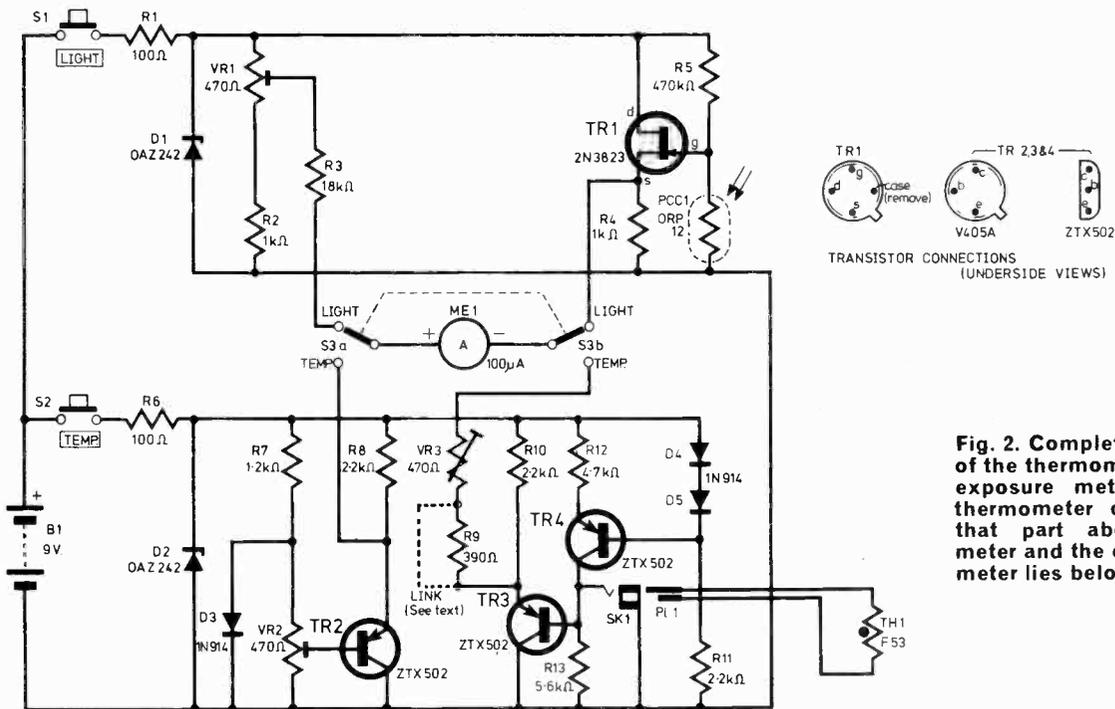


Fig. 2. Complete circuit of the thermometer and exposure meter. The thermometer circuit is that part above the meter and the exposure meter lies below it

R5 and PCC1 is therefore only in the order of a few microamps so a field effect transistor (TR1) is used to the voltage without taking current from the sensing device.

The input resistance at the gate (g) of TR1 is several megohms whereas the resistance at the source (s) is low enough to operate the meter. The voltage of TR1 source is therefore equivalent to V_B in Fig. 1.

SETTING UP

To set zero deflection on the meter cover the light cell with black adhesive tape (a finger is inadequate since it is remarkably translucent) and adjust VR1. The response of TR1 and PCC1 will vary and R3 should be selected to give the best working range for the individual user. It will be between 15 and 22 kilohms, with 18 kilohms a good starting point.

If the device gives a high deflection for long exposure times it is too sensitive, and R3 should be increased. If it gives a low reading for short exposures it is not sensitive enough and R3 should be reduced. If a deflection of $60\mu A$ for a 10 second exposure is taken as a datum point the response will be similar to the graph given (Fig. 3). Any variation, however, is really irrelevant, as the following paragraph explains.

CALIBRATION OF THE EXPOSURE METER

Select a centre of interest or mid-tone grey on the negative and, placing the unit on the base board, stop the enlarger down to give a deflection of $10\mu A$ on the meter.

Make a test strip in the conventional way and record the best exposure time. Increase the stop to give a deflection of $20\mu A$ and repeat with another test strip. Continue with several stop settings up to full scale deflection and plot a calibration curve that

COMPONENTS . . .

Resistors

R1	100 Ω	R8	2.2k Ω
R2	1k Ω	R9	390 Ω (see text)
R3	18k Ω (see text)	R10	2.2k Ω
R4	1k Ω	R11	2.2k Ω
R5	470k Ω	R12	4.7k Ω
R6	100 Ω	R13	5.6k Ω
R7	1.2k Ω		

All $\pm 5\%$ $\frac{1}{4}$ W carbon

Potentiometers

VR1-3 470 Ω miniature horizontal skeleton preset (3 off)

Transistors

TR1 2N3823
TR2-4 ZTX502 or V405A or similar (3 off)

Diodes

D1, D2 OAZ242 5.6V 230mW Zener (2 off)
D3-5 1N914 (3 off)

Light Dependent Resistor

PCC1 ORP12

Miscellaneous

TH1 F53 thermistor (ITT No. 1129E)
ME1 100 μA f.s.d. (ITT No. 8516C or SEW MR45P)
S1, S2 Push to make, release to break push-buttons (2 off)
S3 D.P.D.T. miniature toggle
PL1, SK1 3mm Jack plug and socket
Metal or plastic case (ITT No. 27524X)
B1 9V PP3 battery and connector

Printed circuit board as in Fig. 4

The meter for which the printed circuit board is designed, the thermistor and the box are available from ITT Electronic Services, Edinburgh Way, Harlow, Essex.

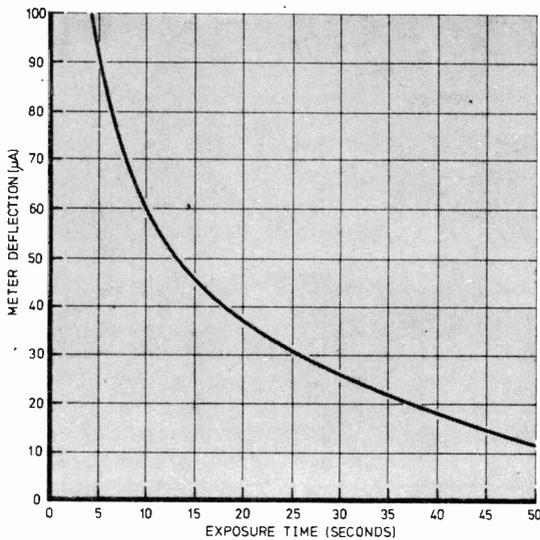


Fig. 3. Graph showing a typical calibration curve for the exposure meter

will give an exposure time against deflection. This will be the calibration curve for that particular meter but will be similar to Fig. 3.

Different paper speeds will give different exposure times but in the majority of cases it will be found that paper speeds vary very little.

DIFFUSER

The argument of "spot" metering or "general" metering is one on which there is room for individual preference. Sampling only a half inch diameter circle was found to be too critical, with small movements of the detector producing wide variations of deflections. Diffusing the whole negative at the enlarger lens can give a false reading if there is a lot of shadow, or a lot of sky, but it was found that sampling a one inch diameter circle is a good compromise. It is small enough to measure the light at the centre of interest but not so small as to be upset by a small dark (or light) patch.

The diffuser is best made from Perspex, rubbed with fine emery cloth if only clear material is available, but can also be made from any translucent material. Draughtsman's tracing film is quite tough and easily cut with scissors, but greaseproof paper is rather fragile for permanent use. It is advisable to leave fixing the diffusing window until the end since there is very little room remaining after the battery is slid into place.

A special note of warning. The light cell is sensitive to *all* light, even darkroom safelights, so the calibration *must* be done with only the enlarger switched on, the meter being read by the fringe light from the projected negative.

Depressing the push button in daylight sends the needle hard against the full scale backstop so should be avoided for obvious reasons!

The beauty of this device is that if a good print is obtained on a small enlargement the same light intensity (and meter deflection) can be reproduced for greater enlargement giving the same print contrast and quality. Alternatively, a new exposure can be measured with the new enlarger/stop conditions.

ELECTRONIC THERMOMETER

The sensing device in this thermometer is a thermistor, which is a glass-encapsulated, thermally sensitive resistor. By passing a constant current through it, a voltage is created across it, so by measuring this voltage we effectively measure its resistance, and hence its temperature.

Again a push button is used and a semi-stabilised voltage created by D2. The left arm of the bridge is R7, VR2 and D3.

Approximately 0.7 volts is developed across D3, a proportion of which is applied via VR2 to the base of TR2 which is used as an emitter follower, thus ensuring that the potential set by VR2 is not upset by the meter current. Thus the potential of TR2 emitter is very stable and at worst is only likely to vary by about 2mV.

The constant current for the thermistor is derived by R12, TR4, D4, D5 and R11. D4 and D5 each drop 0.7 volts, i.e. 1.4V total, and the emitter-base junction of TR4 drops 0.7 volts. This gives a total of 0.7 volts across R12 which is then selected to give the required current which in this case is 0.15mA.

The thermistor chosen was STC type F53 although type GL53 would have been adequate. The "GL" range can dissipate a little extra power but are physically much smaller and in some respects not quite so easy to handle, but are more rugged than the longer "F" range. There is little to choose between them and the final choice could well be left until a probe assembly has been selected.

Resistance of R13 is approximately equal to the thermistor resistance at the mid-range temperature (67.5 degrees F). Either 5.6k Ω or 4.7k Ω could be used since the actual resistance calculated was 5.2k Ω , and there is a 20 per cent tolerance to be added to, and subtracted from that.

CURRENT LIMITATION

When a current is passed through any resistor, power is dissipated within the component and it gets warm. When a thermistor gets warm its resistance falls (that is why one is being used in the first place).

Photograph showing the F53 thermistor used in the thermometer. Also shown is a GL53 thermistor (top) and the thermometer probe

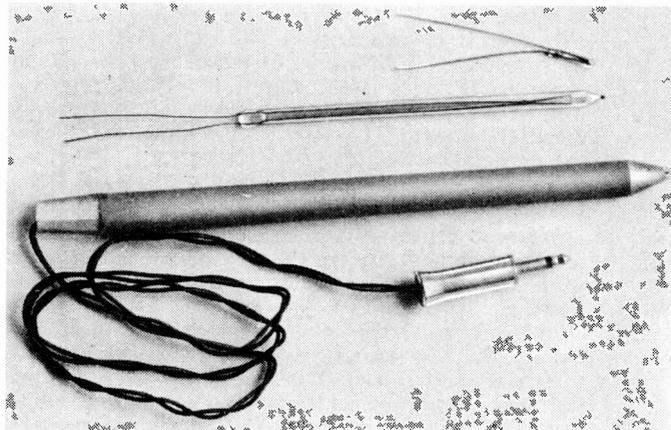


Fig. 4. Full size printed circuit board. The black areas indicate copper


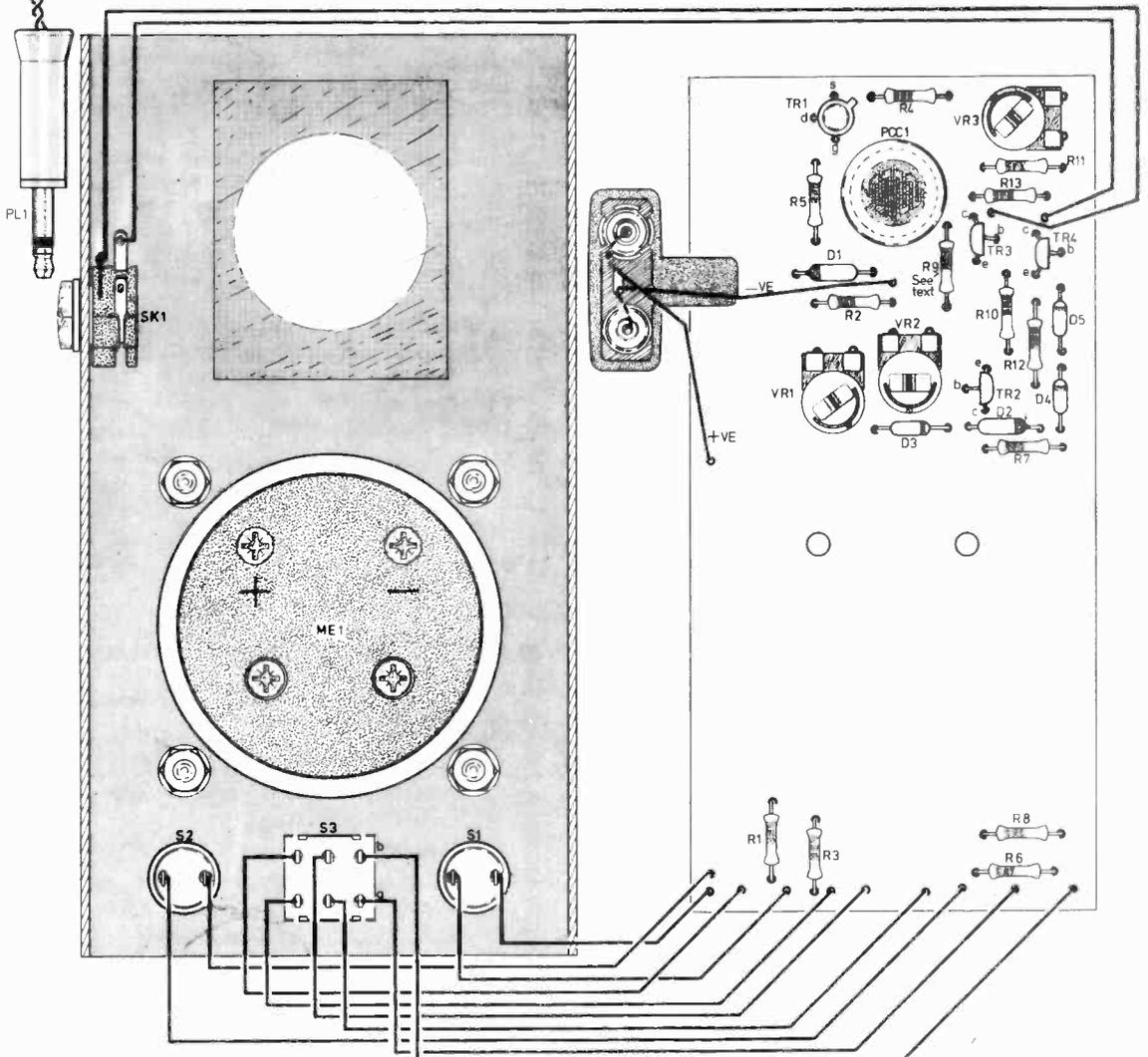
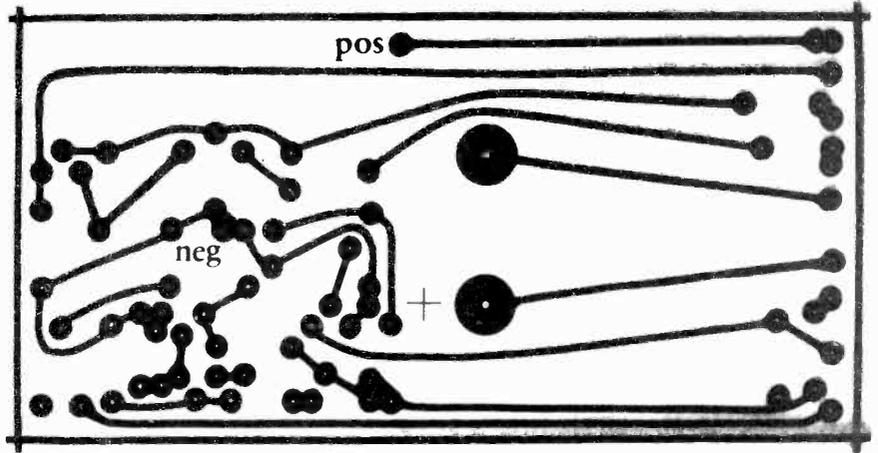


Fig. 5. Constructional details of the complete unit. The ITT meter has screw terminals which the printed circuit board is designed to fit. The probe is an old felt pen body

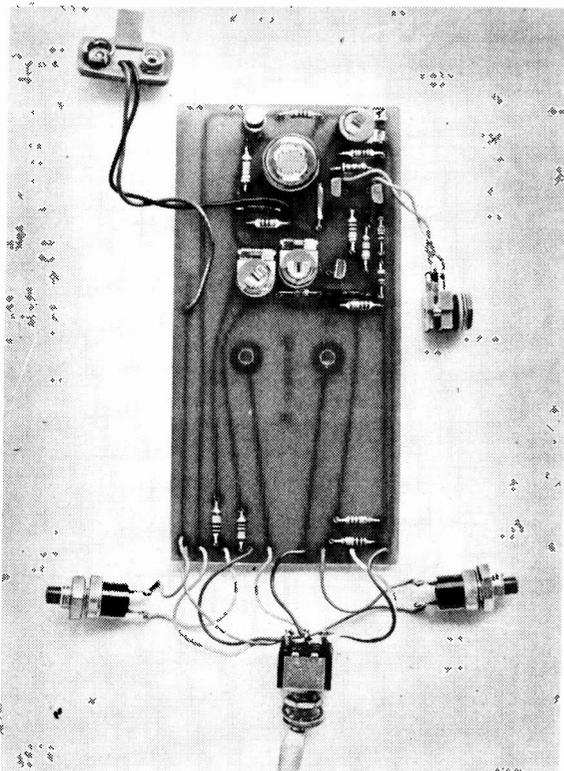

Photograph showing the internal layout of the unit

Provided it is small it matters little since the error is constant, and if it is calibrated in air and used only in air it will have no significant effect.

Similarly, if calibrated and used in liquids only the error is "calibrated out". But if a thermistor is calibrated in liquids and then used in air, the heat generated within the bead cannot be dissipated as efficiently and the bead resistance drops, making it appear hotter than it really is. The current must therefore be kept to the lowest possible if both liquid and air temperatures are to be measured.

Although primarily designed for liquids this unit might be used for air measurements as well, and by using only 0.15mA in the constant current source the air temperature registers a mere 0.05 degree F higher than the liquid temperature.

Using this small current means that another emitter follower must be used to drive the meter, with VR3 and R9 setting the full scale deflection. With these stabilising features and calibrated at zero and f.s.d. a mid point error of less than 0.2 degree F can be expected.

CALIBRATION OF THE THERMOMETER

It is intended that this should be used over a 25 degrees F change from 55 degrees F to 80 degrees F. This gives ample resolution within the 60 degrees F to 70 degrees F range which is the most popular area for photographic work, yet enables solutions to be mixed quickly by monitoring the wider range. Also the meter scale was already subdivided into five increments, so it was easy to read a temperature range that could be divided into five increments also.

The best thermometer available to the constructor must be used to calibrate the instrument since this unit can only be as good as the "standard". With the probe tip immersed in a liquid of 55 degrees F the meter is set to zero using VR2, and at 80 degrees F the full scale deflection is set by VR3; R9 will probably not be required in which case a wire link can be used in its place. Space was left for it, however, in case the voltage across the meter is low and further resistance was required to limit the current; 390 ohms will probably suffice but in rare cases it may be necessary to insert a larger value.

The fronts of SEW meters unclip, exposing the dial, whereby the temperature range can be added either with Letraset or careful printing.

MECHANICAL DETAILS

The box photographed is available from ITT Electronic Services (see Components List), and comes ready painted in a two-tone blue/grey eggshell, and the printed circuit board (Fig. 4) was designed to fit this box. Being a rather well-packed board it precluded the use of Veroboard or similar construction. However, a small plywood box could be made to take a larger board, and, if suitably polished, could still look attractive though less compact.

The one inch hole for the diffuser window was easily punched out with a "Q-max" punch, but the meter hole was a little more tricky. Unfortunately "Q-max" do not make a punch to suit so for this drill a circle of $\frac{1}{16}$ in holes and join them up with a needle file, finishing with a run round with a scraper, a slow process but an effective one.

The thermometer probe utilises a disused felt tip pen with the felt removed. The thermistor was slid down the barrel until the tip emerged, then the barrel was filled with silicone bath tub caulk which held both the wiring and thermistor firmly in place. The pen cap was retained as a tip protector for when the unit is not in use.

Components are shown mounted on the board in Fig. 5 which also shows interwiring details. The battery lies alongside the "window". The printed circuit board is held by screws to the meter.

The total cost of this unit is about £8, for which the constructor will have an instrument which would cost very much more commercially—if such an instrument existed. ★

PRACTICAL ELECTRONICS

● INDEX

An index for volume 8 (January 1972 to December 1972) is now available price 11p inclusive of postage.

● BINDERS


Easi-binders with a special pocket for storing blueprints and data sheets, etc., are available price £1.10p inclusive of postage. State required volume, e.g., Vol. 1, 2, 6.

Orders for Binders and Indexes should be addressed to the Post Sales Department, IPC Magazines Ltd., Carlton House, 66 Gt. Queen Street, London, W.C.2.

ALL OUR PRICES INCLUDE V.A.T.

BSR LATEST SUPERSLIM STEREO & MONO

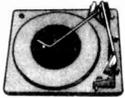Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. AC 200/250V. Size 13 1/2 x 11 1/2 in. Above motor board 8 1/2 in. below motor board 2 1/2 in.



with STEREO and MONO XTAL £8.25 Post 25p.
PORTABLE PLAYER CABINET
Modern design. Black rexine covered. Silver front grille. Chrome fittings.
Motor board out for BSR deck £4.50 Post 25p

E.M.I. WOOFER AND TWEETER KIT

Available separately. Woofer £4.25 Tweeter 1.80
Comprising a fine example of a Woofer 10 1/2 x 8 1/2 in. with a massive Ceramic Magnet, 440z. Gauss 18,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.
Impedance Standard 8 ohms
Maximum Power 12 watts
Useful Response 35 to 18,000 c/s
Bass Resonance 45 c/s
SUITABLE ENCLOSURE 20 x 13 x 9 in.
MODERN GROOVED FRONT DESIGN, TEAK FINISH



£9.90 Post 25p

SPECIAL OFFER!
SMITH'S CLOCKWORK 15 AMP TIME SWITCH
Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. interchangeable. Turn on or off at full or variable time settings. Two types available 0 to 60 minutes Type A or 0 to 6 hours Type B. Makers last list price £4.50. Brand new and fully guaranteed. Fully insulated.
OUR PRICE £1.65, or £3 pair. Post 25p
(PLEASE STATE TYPE A OR B WHEN ORDERING)



WEYRAD P50 — TRANSISTOR COILS

RA2W Ferrite Aerial 73p
Osc. P50/1AC 32p
I.F. P50/2CC 470 kc/s 36p
S.D. I.F. P50/3CC 38p
Spare Cores 3p
Mullard Ferrite Rod 8 x 1/2 in. 20p. 6 x 1/2 in. 20p.

Driver Trans. LPDTA 58p
Printed Circuit, PCA1 58p
J.B. Tuning Gang 65p
Weyrad Booklet 10p
OPTI 58p

VOLUME CONTROLS

5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.F. 25p. STEREO L/S 55p. D.F. 75p. Edge 5K.S.P. Transistor 25p.

80 Ohm Coax 4 p. rd.
BRITISH AERIALITE
AERIAL-AIR SPACED
40 yd. £1.40. 80 yd. £2.
FRINGE LOW LOSS
Ideal 825 and colour 10p yd

8in. or 10in. ELAC HI-FI SPEAKER

Dual cone plasticised lur surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 65 c/s. 8 ohm impedance. 8in 10in 12in 15in 16in 18in 20in 3770in 377

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

NEW 'SCOPES

Two new scopes from recently formed **Scopex Instruments**, are low cost precision instruments: the 4D-10 with a vertical bandwidth of 10MHz and the 4D-25 with a bandwidth of 25MHz. Both have been designed with the philosophy of combining performance with simplicity of operation. To further the philosophy Scopex introduced the "easy where it counts" triggering where the triggering point and the polarity are selected on just one control. This facility is available on both 'scopes.

The 4D-10 sells for £95 and the 4D-25 for £175. On a cost/performance basis they are both excellent value. Further details can be obtained from Scopex Instruments, Pixmore Avenue, Letchworth, Herts.

I.C. ACCESSORIES

Accessories in the integrated circuit field is a vastly growing market and readers may be interested in two new aids from **Ultra Electronics Components Ltd.**

The first item is a versatile printed circuit board for i.c.s and DIL devices. Basically it is a standard circuit card with rows of single-way connectors which will accept DIL devices.

Ideal for "knocking-up" experimental circuits, interconnection between devices is achieved by the use of patching leads. A distribution block connects to the board edge pads and enables the board to be plugged into racking systems if required.

The second item is a multi-contact "peg" or pincer which can be clamped over i.c.s and the lead-out pins in the handle used for test points. Contacts on the inside of the jaws automatically align with the i.c. pins.

When the need for desoldering i.c.s from printed circuits arises the "peg" as been found to be very useful as an extraction tool.

Two types are available at the moment, type OEC370 for 14 or 16 DIL packages with 0.1in pitch between contacts and type OEC371 for 24 to 60 contact devices with 0.1in pitch contacts.

Further particulars for both devices can be obtained from **Ultra Electronic Components Ltd.**, Fassetts Road, Loudwater, Bucks.

STEREO KIT

A compact, new stereo record system that can be simply assembled has been introduced by **Radio & T.V. Components**. At £17.95 the Stereo 21 System provided excellent sound quality on demonstration and the near 6W total output should prove more than adequate for the average living-room.

The complete system includes a BSR 3-speed deck, ceramic cartridge and twin 8in x 5in elliptical speakers. None of the units are sold separately.

Two factors have contributed in keeping down the price: direct selling from R & TV to the public and simple d.i.y. assembly. You don't need to know anything about electronics in the construction; you simply enclose the speaker components in their wrap-around casings, wire the plug, plug in and you are enjoying stereo sound.

Further information can be obtained from **Radio & T.V. Components (Acton) Ltd.**, 21 High Street, Acton, London, W.3.

CARTRIDGE PLAYER

One of the side effects of the booming in-car entertainment market lies in the problem of utilising the same source of sound for home listening. Growth in the sales of pre-recorded 8-track, stereo cartridges has not been matched by the introduction of an economic sound system capable of being used in conjunction with existing stereo equipment in the home.


Now with the Budget 8, R & T-V C has introduced a reliable, British engineered, cartridge player which retails for £9.90. Based on the latest BSR T 145 8-track cartridge playing mechanism, and incorporating its own stereo pre-amplifier stages the unit simply plugs into the auxiliary socket on most stereo audio systems to provide high quality reproduction in the home from the same cartridges used in the car.

LITERATURE


Next month P.E. is including a special i.c. audio chart which, we hope, readers will find very useful.

Whether you are thinking of building an amplifier or you want some ideas on using i.c.s. in audio circuits, the P.E. Audio I.C. Identichart gives comprehensive data on over 80 i.c.s. ranging from low level pre-amplifiers to hybrids rated at 50W.

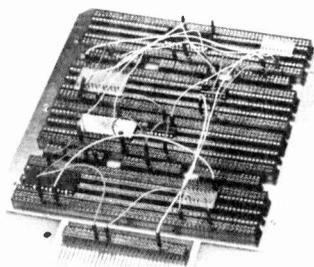
As well as data, the chart contains suggestions for using i.c.s. in mixers, tape recorders, record players etc.



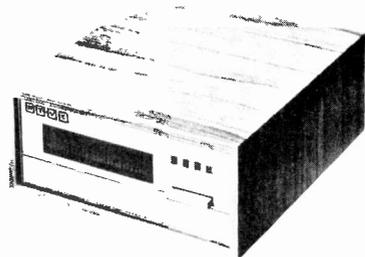Universal circuit card from Ultra Electronics




RTVC Budget 8 player

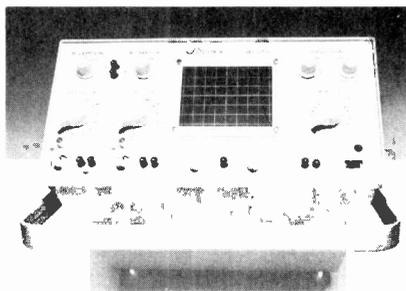

4D25 'scope from Scopex Instruments



Completed stereo 21 kit by RTVC

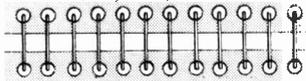

INDUSTRY NOTEBOOK

By Nexus

EXPANSION

The current boom is by no means uniform in impact across the whole of the electronics industry but there are welcome signs of expansion in many quarters.

Even conservative Ferranti is looking for a Stock Exchange listing as a way of raising more capital. Ferranti is one of the largest private companies in business in the UK and, according to reports, has no intention of "going public" in the generally accepted sense. It is still expected that the Ferranti family interests will control more than 50 per cent of voting rights.

High-flying Unitech Group has also been looking for more capital to finance the recent acquisition of Rathdown Industries and Lee Green Precision Industries. These two companies have broadened the Unitech base by adding component manufacture (mechanical counters, small pressings, precision machinings and co-axial connectors) to the Group's other activities.

One of the rising stars in the Group is Weir Electronics, acquired by Unitech in 1963 when it first moved to Bognor with a staff of only four people. I was recently at the opening, by local M.P. and Minister for Industrial Development, Christopher Chataway, of a new 30,000 sq ft production unit. Staff is now 300 and turnover £1.5 million. Extrapolating the growth curve suggests that Weir will hit £3 million turnover by 1975.

Weir is one of those fascinating companies that are honest with themselves as well as with their customers — a rare combination. They admit to having had some expensive diversions into fields (for example, in instruments) where there was little chance of success. Present (and profitable) tack is to stay a low-technology company

turning out a first-class engineering job. Huge OEM orders for stabilised power supplies for companies like Rank Xerox, ITT and Business Computers are now the backbone of the business.

But one of the really big successes for Weir could come from a comparatively low-cost electronic seat-belt interlock for cars which is now being evaluated by British and overseas car manufacturers. The new Weir development is in time for the US market where the interlock will be mandatory on all cars registered next year and thereafter.

Other new products in the pipeline include motor speed control, electronic lighting control and an as yet unspecified incursion into telecommunications.

How about unstoppable Electrocomponents Associated Group, basically our old friend Radiospares wearing a new hat? Turnover has rocketed to £7.24 million up 20 per cent, with profits up 25.8 per cent to over £1.5 million. The Electroplan subsidiary which was set up to supply instruments as a complementary operation to the component business is not yet in profit. I understand, but should be making a contribution by the end of the year.

BULLSEYE

I haven't fired a shot in anger for close on 30 years and if someone had told me when I last squeezed a trigger that one day I should destroy a tank using a laser beam I should have thought them mad. It wasn't likely that such a suggestion should have been made because the laser lay some years in the future.

Anyway, your scribe, somewhat nervous before an audience of British Army top brass, not to mention a couple of dozen foreign military attaches, successfully polished off a couple of Chieftains at 700 metres on the tank range at Bovington Camp. There was all the excitement of seeing the "enemy" going up in smoke with the added satisfaction of knowing that nobody was getting hurt.

The equipment was Solartron's SIMFIRE tank gunnery simulator which has brought the company back into the simulator business with a bang and has already scored a sales bullseye with 16 armies, while another 25 armies are evaluating it. Even the United States Army is ordering it.

Solartron started the project as a private venture but the Ministry of Defence soon became interested and backed it with a £250,000 development contract. The big payoff is now at hand.

RESEARCH

Commercial pressures over the past few years have tended to direct

research men into avenues of investigation which have some identifiable end-product in mind. But there is still plenty of "pure" research in the Philips laboratories at Eindhoven which I recently visited. As an example, I can quote the work on surfaces and surface layers which, despite the advent of the scanning electron microscope and other techniques, is still little understood and has great significance in the production process of semi-conductor devices.

But one of the most interesting developments I saw and, incidentally, of great commercial potential, was the electrochromic display. This was in 7-segment form and although passive in the sense that it is not light-emitting like gas discharge tubes or LEDs, has the enormous advantage that, once formed by the application of the appropriate voltage, the character remains when the voltage is removed until erased by re-applying the voltage with reversed polarity.

Several such devices have been described in the literature but, until now, all have had substantial disadvantages. The Philips team on the project has now reached a stage where the new device has been fully patented and so I can reveal that the principle of operation is based on the oxidation-reduction reaction of diheptylviologendibromide in water. Difficult to pronounce, perhaps, but it's a formula that works. The display is a cheerless purple-blue in colour but has excellent contrast and needs only half a volt to activate it.

To be in the top league of R and D is not easy. Philips has been in research since the early '90s (last century) when founder Gerard Philips did some of the pioneer work on filament lamps. The present score is 4,000 people in the research laboratories in Holland, France, England, Belgium and West Germany.

To keep up with the inventions and innovations that pour out of the labs, the Eindhoven patents department alone employs 200 people of which 60 are scientists. The mind boggles!

KEYBOARD KING?

In contrast to mighty Philips with 350,000 employees, watch Sammy Zilkha's bid for the throne as keyboard king. Keyboards is one of the fastest growing areas of electronic industry activity and his new but still tiny company, Alphameric Keyboards, looks all set to win a big share of it. Hardly had he announced the product, the electronic heart of which is a Zilkha-designed MOS LSI, than a joint venture agreement was being completed with an American company.

Henry's YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

INTEGRATED CIRCUITS

Why buy alternatives when you can buy the genuine article from us at competitive prices from stock. **BRANDED FROM TEXAS I.T.T. FAIR-CHILD**



Type	1/11	12/24	26/99	Type	1/11	12/24	26/99	Type	1/11	12/24	26/99
SN7400	0-20	0-18	0-16	SN7450	0-20	0-18	0-16	SN74145	1-50	1-40	1-30
SN7401	0-20	0-18	0-16	SN7451	0-20	0-18	0-16	SN74150	3-35	2-95	2-15
SN7402	0-20	0-18	0-16	SN7453	0-20	0-18	0-16	SN74151	1-10	0-95	0-90
SN7403	0-20	0-18	0-16	SN7454	0-20	0-18	0-16	SN74153	1-85	1-27	1-20
SN7404	0-20	0-18	0-16	SN7460	0-20	0-18	0-16	SN74154	2-00	1-75	1-55
SN7405	0-20	0-18	0-16	SN7470	0-20	0-18	0-25	SN74155	1-55	1-47	1-35
SN7406	0-30	0-27	0-25	SN7472	0-30	0-27	0-25	SN74156	1-55	1-47	1-35
SN7407	0-30	0-27	0-25	SN7473	0-40	0-37	0-35	SN74157	1-80	1-70	1-60
SN7408	0-20	0-18	0-16	SN7474	0-40	0-37	0-35	SN74160	2-80	2-40	2-25
SN7409	0-45	0-42	0-35	SN7475	0-55	0-52	0-50	SN74161	2-60	2-40	2-25
SN7410	0-20	0-18	0-16	SN7476	0-45	0-42	0-39	SN74162	3-40	3-25	3-20
SN7411	0-28	0-28	0-20	SN7480	1-25	1-15	1-10	SN74163	3-40	3-25	3-20
SN7412	0-42	0-40	0-35	SN7481	1-80	1-15	1-10	SN74164	2-75	2-30	2-10
SN7413	0-30	0-27	0-25	SN7482	0-87	0-80	0-70	SN74165	4-00	3-60	3-00
SN7414	0-30	0-27	0-25	SN7483	0-80	0-75	0-70	SN74166	4-00	3-60	3-00
SN7415	0-30	0-27	0-25	SN7484	0-90	0-85	0-80	SN74167	6-80	6-00	5-10
SN7420	0-20	0-18	0-16	SN7486	0-45	0-41	0-38	SN74174	4-10	3-55	3-05
SN7422	0-48	0-44	0-40	SN7490	0-75	0-70	0-65	SN74175	2-00	1-75	1-50
SN7423	0-48	0-44	0-40	SN7491A	1-00	0-95	0-90	SN74175	1-35	1-27	1-15
SN7425	0-48	0-40	0-35	SN7492	0-75	0-70	0-65	SN74176	1-60	1-35	1-20
SN7427	0-42	0-39	0-35	SN7493	0-75	0-70	0-65	SN74177	1-60	1-35	1-20
SN7428	0-50	0-45	0-42	SN7494	0-80	0-75	0-70	SN74180	1-55	1-30	1-20
SN7430	0-20	0-18	0-16	SN7495	0-80	0-75	0-70	SN74181	7-00	6-00	5-50
SN7432	0-42	0-39	0-35	SN7496	1-00	0-95	0-90	SN74182	2-40	2-00	1-80
SN7433	0-70	0-61	0-44	SN7497	6-25	5-50	5-00	SN74184	4-00	3-60	3-00
SN7437	0-65	0-60	0-50	SN74100	2-50	2-30	2-00	SN74185A	2-40	2-00	1-80
SN7438	0-65	0-60	0-50	SN74104	1-45	1-35	1-20	SN74190	1-95	1-85	1-75
SN7440	0-20	0-18	0-16	SN74105	1-45	1-35	1-20	SN74191	1-95	1-85	1-75
SN7441A	0-75	0-72	0-70	SN74107	0-50	0-45	0-40	SN74192	2-00	1-90	1-80
SN7442	0-75	0-72	0-70	SN74110	0-80	0-70	0-60	SN74193	2-00	1-90	1-80
SN7443	1-00	0-95	0-90	SN74111	0-80	0-75	0-70	SN74194	2-00	1-90	1-80
SN7445	2-00	1-75	1-60	SN74119	1-80	1-78	1-65	SN74195	1-85	1-70	1-60
SN7446	2-00	1-75	1-60	SN74121	0-80	0-65	0-50	SN74196	1-50	1-40	1-30
SN7447	1-75	1-60	1-45	SN74122	1-85	1-25	1-10	SN74197	1-50	1-40	1-30
SN7448	1-75	1-60	1-45	SN74123	2-70	2-65	2-47	SN74198	4-80	3-70	3-85
				SN74141	1-00	0-95	0-80	SN74199	4-80	3-70	3-85

PRICES OF 7400 SERIES ARE CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
LARGER QUANTITY PRICES PHONE (01) 402 4891
HIGH POWER SN 74 HOO } Now in stock - send for list No. 36
LOW POWER SM 74 LOO }

A SELECTION OF SEMI-CONDUCTORS FROM STOCK

AA530 10p	BC147 12p	BU105 15p	OC44 15p	T1843 35p	2N3055 55p
AA542 10p	BC169C 12p	BY100 25p	OC45 15p	V405A 25p	2N3440 75p
AAZ13 10p	BC182 10p	BY126 16p	OC57 50p	ZTX108 12p	2N3442 1.25
AC107 35p	BC214 15p	BY127 16p	OC71 15p	ZTX300 12p	2N3525 75p
AC126 25p	BCY32 75p	BYZ13 35p	OC72 25p	ZTX301 15p	2N3614 50p
AC127 25p	BCY34 35p	C106D 65p	OC77 45p	ZTX302 18p	2N3615 75p
AC128 25p	BCY35 25p	CE111 55p	OC81 15p	ZTX341 20p	2N3702 10p
AC176 25p	BCY42 30p	GET115 55p	OC83 25p	ZTX800 15p	2N3704 10p
AC187 25p	BCY43 25p	GET880 45p	OC140 55p	ZTX503 17p	2N3705 10p
AC188 25p	BCY55 2.50	LM309K	OC170 25p	ZG301 30p	2N3714 1.80
ACY17 30p	BCY70 15p	(T03) 1.87	OC171 30p	2N404 20p	2N3771 1.75
ACY20 20p	BCY71 20p	MAT121 25p	OC200 45p	2N627 35p	2N3773 2.00
ACY21 20p	BCY72 15p	MC340 50p	OC209 75p	2N696 15p	2N3790 2.25
ACY39 55p	BCY87 2.90	MEJ370 70p	OC292 80p	2N697 15p	2N3819 35p
AD140 50p	BCZ11 50p	MJE250 75p	OC293 50p	2N706 10p	2N3820 50p
AD149 50p	BD124 60p	MJE295 5p	OCP71 1.25	2N930 20p	2N3866 85p
AD161 85p	BD131 75p		ORP12 50p	2N987 45p	2N3903 15p
AD162 35p	BD132 80p	MJE3055	ORP60 40p	2N1131 25p	2N3906 12p
AF117 20p	BF115 25p		P346A 25p	2N1132 25p	2N4061 12p
AF118 50p	BF167 25p	KPF105 40p	RA5501A 1p	2N1302 18p	2N4062 12p
AF124 25p	BF173 25p	NKT214 20p		2N1304 22p	2N4262 15p
AF139 30p	BF179 30p	NKT216 40p	RA5508A 55p	2N1305 22p	2N4471 35p
AF186 40p	BF180 30p	NKT217 40p		2N1307 25p	2N5457 30p
AF239 40p	BF194 15p	NKT403 70p	TAA263 75p	2N1308 25p	2N5777 55p
AS927 30p	BF195 15p	NKT404 50p	TAL209 30p	2N1613 20p	2N8001 1.00
AY228 25p	BP861 25p	OA5 50p	TIP29A 50p	2N1671 1.00	2N8012 10.00
BA32 30p	BP87 1.00	OA10 35p	TIP30A 60p	2N1747 75p	2N8018 6.25
BA115 7p	BFX13 25p	OA81 10p	TIP31A 60p	2N1801 15p	2N8026 8.90
BA145 15p	BFX34 75p	OA91 7p	TIP32A 70p	2N2217 25p	2N8031 50p
BAX13 5p	BFX37 30p	OA200 7p	TIP33A	2N2221 20p	2N8033 65p
BAX16 7p	BFX88 20p	OA202 10p		2N2222 20p	2N8034 95p
BC107 10p	BFY50 20p	OC16 75p	TIP34A 1.00		2N8050 50p
BC108 10p	BFY51 20p	OC20 85p		2N2369A	40360 40p
BC109 10p	BFY52 20p	OC23 85p	TIP35A 1.50		40361 40p
BC109C 12p	BFY64 50p	OC25 85p		2N2906 20p	40362 50p
BC113 15p	BFY90 50p	OC28 65p	TIP36A	2N2926 (all)	40408 50p
BC115 12p	BLY36 8.00	OC35 50p		cols)	40486 75p
BC117 20p	BX820 15p	OC36 65p	TIP41A 75p	2N3053 20p	40636 1.10
BC143 35p	BSY27 15p	OC42 40p	TIP42A 85p	2N3054 50p	40430 1.00

QUANTITY DISCOUNTS

10% 12+ 15% 25+ ANY ONE TYPE
20% 100+ 25% 250+

From above sections except Integrated Circuits and Special Offers where discounts are included.
Minimum order value \$1 please.
Postage 7p on all orders.

SPECIAL OFFERS! SEMI-CONDUCTORS

BFY90 1000 MC/S 59p
25 + 30p
100 + 45p
500 + 40p

AF117 Mullard 25p

25 + 17p
100 + 15p
500 + 12p

OC170 Mullard 25p

25 + 20p
100 + 18p
500 + 15p
1000 + 13p

BY127 Mullard 15p

25 + 12p
100 + 10p
500 + 9p
1000 + 8p

OA202 10p

25 + 8p
100 + 7p
500 + 6p
1000 + 5p

OC35 Mullard 50p

25 + 45p
100 + 40p
500 + 35p
1000 + 30p

ZENER DIODES

400 mW 5% Miniature
BZ 88 Range

All voltages 3.3 - 33 Volt
10p each

25 + 9p
100 + 8p
500 + 6.5p
1000 + 5p

Any one type.

1 1/2 Watt 5% Wire Ends Metal Case
All voltages 6.8 - 100 Volts
20p each

25 + 18p
100 + 18p
500 + 12p
1000 + 10p

Any one type.

3 Watt Plastic Wire Ends 5% 3EZ Range
All voltages 6.8 - 100 Volts
30p each.

25 + 50p
100 + 40p
500 + 30p
1000 + 20p

1 1/2 amp miniature
IN4001 50 8
IN4002 100 7
IN4003 200 8
IN4004 400 8
IN4005 600 10
IN4006 800 12
IN4007 1000 15

1 1/2 amp miniature
PL4001 50 8
PL4002 100 9
PL4003 200 10
PL4004 400 10
PL4005 600 12
PL4006 800 15
PL4007 1000 15

SILICON RECTIFIERS WIRE WOUND PLASTIC

Type P.I.V. 1-11
1 amp miniature
IN4001 50 8
IN4002 100 7
IN4003 200 8
IN4004 400 8
IN4005 600 10
IN4006 800 12
IN4007 1000 15

1 1/2 amp miniature
PL4001 50 8
PL4002 100 9
PL4003 200 10
PL4004 400 10
PL4005 600 12
PL4006 800 15
PL4007 1000 15

NEW FREE BOOKLET (No. 36) Over 1500 TYPES—

Send for yours today!

2N2926 10p
All Colours
25 + 9p
100 + 8p
500 + 6p
1000 + 5p

2N3819 Texas 35p

25 + 30p
100 + 25p
500 + 20p
1000 + 15p

BC107, BC108, BC109 10p each

All Makes
25 + 8p
100 + 7p
500 + 6p
1000 + 5p

AD161, AD162 35p

25 + 32p each
100 + 28p
500 + 25p
1000 + 22p

2N3053 20p

25 + 18p
100 + 15p
500 + 12p
1000 + 10p

2N3055 55p

25 + 50p
100 + 45p
500 + 38p
1000 + 33p

LINEAR (C/P AMPS)

702C T05 75p
709C T09 35p
709C D.I.L. 35p
723C T09 21.00
723C D.I.L. 95p
723C - T09 24.50
741C T09 55p
741C D.I.L. 55p
747C T09 21.00
747C D.I.L. 21.00

72741P D.I.L. 60p
81NCLAIR
IC12 21.80
TOSHIBA
TH9013P
20 WATT AMP
24.47 POST PAID
TH9014P Pre Amp
21.50

DATA AND CIRCUITS REF. 42 10p

FREE WITH PURCHASES

PATENTS REVIEW...

WIND DIRECTION INDICATORS

Direction indicators are used on small sailing boats to show the wind direction relative to the heading of the boat and so help the helmsman choose the best angle to sail. Conventionally an electrical transmitter is connected to a wind vane on the masthead and the transmitter produces signals which are fed to a receiver and rotor in the cockpit. But such systems have to date been relatively insensitive.

In BP 1 290 331 from EMI a refined system is described. In Fig. 1 a star wound transmitter transformer T1 has three windings spaced by angles of 120 degrees and signals are taken from points 1, 2 and 3. A rotor winding is fed by a 400Hz signal from a converter powered by the boat's battery. The rotor is ganged to a wind vane on the boat's mast.

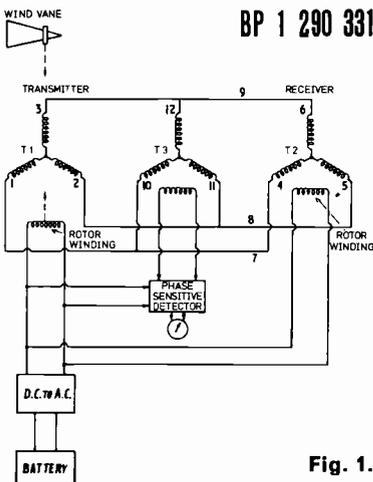


Fig. 1.

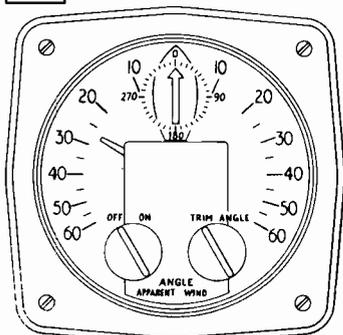


Fig. 2.

The signals from points 1, 2 and 3 are fed to points 4, 5, 6 on a second star wound transformer T2, which functions as a receiver. This receiver also has a rotor winding supplied with the 400Hz signal.

As the rotor turns with the wind direction changes the amplitudes of the a.c. currents in the leads 7, 8, 9 vary with sine and cosine functions. Corresponding fields are set up in the receiver transformer T2 and its rotor follows these. The receiver rotor is coupled to a direction pointer on a cockpit indicator (Fig. 2).

All this is conventional and the invention proper concerns the provision of a second transmitter which is formed as a third star wound transformer T3. Points 10, 11, 12 on this transformer are connected to the leads 7, 8 and 9 and this transformer has a rotor winding which is normally stationary but can be pre-set by a knob on the cockpit indicator.

The signal produced by the T3 rotor is fed to a phase sensitive detector with the 400Hz signal as its reference. For any position of T1 rotor there is one angular position of T2 rotor which produces zero voltage.

The output of the phase detector is fed to a milliammeter with a pointer which moves over an apparent wind scale on the indicator. Scale calibration is such that the pointer shows the angular deviation to one side or another of the null, determined by the angular setting of T3 rotor and represented as scale zero, see Fig. 2. The milliammeter therefore provides a highly sensitive indication of deviation with angular amplification.

Usually T3 rotor is adjusted by the trim/angle control so that the pointer reads zero when the boat is heading directly into the wind. Thereafter the pointer gives a very sensitive and very accurate indication of the wind direction relative to the boat heading.

COUGH MONITORING

Some fairly simple circuitry from Abbott Laboratories in the USA is described in BP 1 312 846. Although the main intention is to monitor the rate of coughing of a patient for diagnostic purposes, the

basic principle of the invention will be applicable to many other fields where it is desired to monitor and count the number of similar sounds above a threshold value which have occurred during a predetermined time.

The patient wears a small microphone either on his shirt collar or taped to his throat. The microphone feeds a small f.m. transmitter which transmits the cough noises to a remote receiver. See Fig. 1.

The receiver is coupled to counting circuitry and a monitoring loudspeaker by the secondary of transformer T1. The loudspeaker can also be brought temporarily into circuit to assist accurate and mutual tuning of the transmitter and receiver.

The secondary of T1 feeds the full-wave rectifier of the threshold circuit. The output of the rectifier bridge is connected across VR1.

Adjustment of VR1 slider allows the threshold level to be set so that only cough signals above a predetermined power level are passed, via C1, to the gate of CSR1. The thyristor CSR1 is normally biased into its non-conductive state.

The anode of CSR1 is connected to a conventional electrical step counter which records the number of pulses supplied to its input. Thus, the counter displays the number of coughs above the pre-set threshold level.

BP 1 312 846

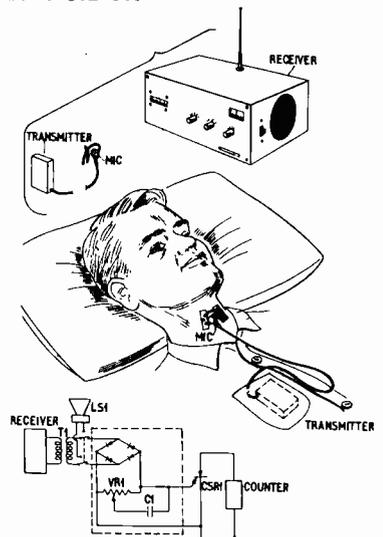


Fig. 1.

Readout —

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

First experience

Sir—Regarding Mr. Baily's letter in the July issue of P.E., I am inclined to agree with him on the subject of log-law applied to v.c.o.s.

My first experience of synthesisers was a small set up comprising three linear oscillators and two filters coupled to a spare keyboard. The intention at that time was to use it in conjunction with an organ, but at no time could it be matched to the organ. I was then informed that a "log-tuned" oscillator was the better circuit since it distributed the frequency evenly over the keyboard virtually to any range.

Having now acquired, what I call, a log-tuned synthesiser, I find no problem at all in matching it with other instruments.

Brett Ross,
Redditch, Worcs.

Extremely versatile

Sir—I have been following the P.E. Synthesiser design with interest since its advent, with a view to using the circuits in my own synthesiser which I had been designing for some time when your synthesiser came out. Whilst on the whole the circuits have been designed very well, there are some points which could be improved upon.

The most important of these is the choice of linear v.c.o.s. I am fortunate in that I have been able to play on nearly all the commercially available synthesisers, and although they vary greatly in many respects, they are united in the use of log v.c.o.s.

With log v.c.o.s a keyboard can be adjusted to accompany out of tune guitars and flat pianos, and I have fitted fifth, third, tone and semitone transpose switches, as on the Synthi AKS, to accompany tunes played in a different key to which I have learnt the tune. The range of my keyboard can be 1Hz bottom

C, 16Hz top C, or with top C nearly ultrasonic, and it is in tune over the entire range (except for a slight droop in frequency at the upper limit caused by the slow switching time of 741's). A linear keyboard is limited to the 4 octaves for which it was tuned. With all the evidence pointing to the necessity of a logarithmic response, it seems a false economy to leave out a log converter from the otherwise excellent v.c.o. design.

Regarding Mr. Baily's letter, although I agree with him in general, I must defend the use of integrated circuits and dual-rail power supplies. The 741, despite drawbacks concerning frequency response, is an extremely versatile device well suited to use in complex analogue systems like synthesisers, considerably simplifying construction of circuits in which it is used.

To use a control as a signal, or vice versa, both must cover the same voltage range. If the signals are a.c. about OV, the controls should also be centred on earth, entailing \pm power supplies. This is another feature common to all commercial synthesisers.

The patching system is the heart of a synthesiser, and although patchcords are the best choice for a modular system, I dislike them because they are inconvenient, requiring two insertions to make one link, they allow only 1-to-1 patches unless parallel inputs are provided, obscure the face of the machine and are prone to hum loops. There are also advantages, the system is easily extendable and signals can be brought in from external sources directly into the system.

The patchboard arrangements in Fig. 6.9b will not work as a resistor is required to mix outputs if more than one is connected to an input. Output impedance should be as low as possible to minimise unwanted crosstalk via outputs, and ideally all inputs should be virtual earths for good mixing, but this is of little importance for all inputs except v.c.o. frequency control.

This needs a virtual earth so that each input plugged to it has the same effect regardless of what else is connected. With the VCS3 the oscillator input impedance is 10k, and if a programming source other

than the keyboard, say joystick or vibrato oscillator is added, then the octave width needs adjusting.

Although I disagree with parts of the design, some of the modules are as good, if not better than those in any other synthesiser and I will be incorporating these without modification into my own synthesiser.

R. Gwinn,
Surbiton, Surrey.

A little unfair

Sir—Having commenced building the P.E. Synthesiser I would like to add my own comments to those of Mr. Baily in the July issue, when he criticises Mr. Shaw's designs.

Firstly, Mr. Baily is being a little unfair in his cost comparison. Agreed, we could obtain a more versatile instrument for £200 using Dewtron modules, but one must take into account the lavishly expensive external shell recommended by Mr. Shaw to house his own Synthesiser. Any prospective constructor should note that Mr. Shaw's recommended cabinet, other metalwork, nuts, bolts, McMurdo plugs and panel knobs cost about £60.

I costed the project very carefully against commercial instruments (biased naturally towards my particular requirements) and opted to work from Mr. Shaw's circuits. After all, one doesn't have to use the recommended cabinet work—the project is expensive enough without using it to exploit modular construction of dubious modular value. An additional benefit, however, is that Mr. Shaw's designs are impressive to say the least, and I should learn a lot from them.

Having said that, I must agree with Mr. Baily regarding Mr. Shaw's dismissal of logarithmic voltage/frequency relationship in the v.c.o.s. It is not so much the loss of chord facilities as in the reduction of the instrument's versatility. In fairness Mr. Shaw wanted to reduce setting up difficulties and did mention the SN76502 log amp for those who wanted to try their hands at log control.

Otherwise, my only two criticisms are: (1) the absence of a sine wave source. Electronic music composition does occasionally demand this peculiarly pure tone. (2) The absence of a band pass filter whose central frequency and spread can be controlled even manually—a necessity for composition based only on a controlled noise source.

I. Stuart-Colwill,
London, S.W.16

We have received many reader's letters in a like vein requesting a log v.c.o. design. To satisfy this, G. D. Shaw is currently designing a circuit which will be published in the near future.



WINGS APPEAL SEPT. 10th - 15th



look! electronics really mastered

...practical
...visual
...exciting!

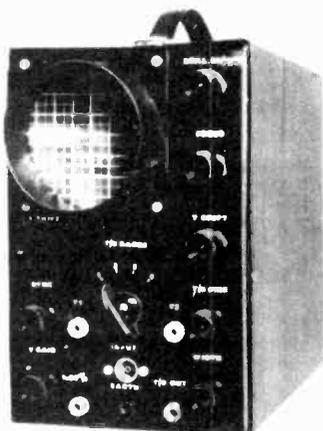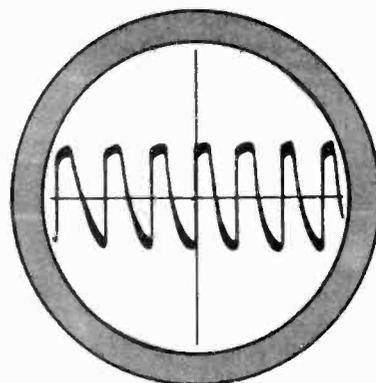no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

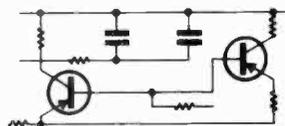2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EL93

special free gift also to all our students

RST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE

Express postage 1p per transistor, over ten post free
INTEGRATED CIRCUITS 5p + 1p each added

#p	#p	#p	#p	#p	#p	
1N21	0-17	AF212	1-50	BY210	0-45	
1N23	0-85	AS226	0-25	BY211	0-40	
1N85	0-88	AS227	0-80	BY212	0-40	
1N303	0-60	AS228	0-25	BY213	0-85	
1N206	0-50	AS229	0-30	BY215	1-25	
1N845	0-20	AS238	0-25	BY218	0-20	
1N725A	0-20	AS250	0-20	BY288C8V3	0-40	
1N914	0-05	AS251	0-40	0-10	OA2242	0-25
1N4007	0-12	AS253	0-20	BZ788C8V3	0-25	
18113	0-15	AS255	0-20	0-10	OA2246	0-25
18131	0-13	AS262	0-25	C111	0-55	
18202	0-23	AS298	0-33	CR5105	0-30	
20371	0-40	AS221	1-00	CR8140	0-45	
20381	0-25	AS223	0-75	CS4B	2-50	
20414	0-30	AC101	1-50	CS10B	3-13	
20417	0-25	AC102	0-90	DD000	0-15	
2N404	0-22	BC107	0-12	DD003	0-15	
2N897	0-15	AC108	0-12	DD006	0-18	
2N898	0-30	BC109	0-10	DD007	0-40	
2N706	0-10	BC113	0-16	DD008	0-38	
2N706A	0-12	BC115	0-20	GD3	0-33	
2N708	0-15	BC116	0-20	GD4	0-10	
2N709	0-40	BC116A	0-23	GD5	0-33	
2N1091	0-55	BC118	0-15	GD8	0-25	
2N1131	0-25	BC121	0-20	GD12	0-10	
2N1132	0-25	BC122	0-20	GE102	0-50	
2N1302	0-15	BC125	0-60	GET103	0-40	
2N1303	0-18	BC126	0-65	GET113	0-35	
2N1304	0-22	BC140	0-55	GET114	0-30	
2N1305	0-22	BC147	0-12	GET115	0-75	
2N1306	0-28	BC148	0-10	GET116	0-85	
2N1307	0-28	BC149	0-12	GET120	0-80	
2N1308	0-30	BC157	0-14	GET23	0-30	
2N2147	0-75	BC158	0-12	GET85	0-40	
2N148	0-60	BC160	0-63	GET880	0-55	
2N2160	0-61	BC169	0-14	GET881	0-25	
2N2218	0-23	BC231	0-45	GET882	0-35	
2N2219	0-25	BC232	0-85	GET885	0-35	
2N2369A	0-15	BC233	0-35	GET886	0-35	
2N2444	1-90	BC234	0-25	GET887	0-45	
2N2443	0-28	BC238	0-55	GET891	0-30	
2N2446	0-50	BC239	1-00	GJ3M	0-50	
2N2904	0-20	BC240	0-80	GJ4M	0-38	
2N2904A	0-25	BC242	0-30	GJ5M	0-25	
2N2906	0-20	BC270	0-15	GJ7M	0-50	
2N2907	0-28	BC271	0-20	HG1005	0-50	
2N2924	0-25	BC272	0-20	H190A	0-20	
2N2925	0-15	BC271	0-65	MAT100	0-20	
2N2926	0-10	BD121	1-00	MAT101	0-25	
2N3054	0-45	BD123	1-00	MAT120	0-20	
2N3055	0-45	BD124	0-80	MAT121	0-25	
2N3702	0-10	BD111	1-45	MJE520	0-65	
2N3705	0-15	BF112	0-20	MJE530	0-25	
2N3706	0-11	BF117	0-50	MJE5305	0-70	
2N3707	0-18	BF167	0-23	NKT128	0-45	
2N3709	0-10	BF173	0-25	NKT129	0-30	
2N3710	0-11	BF181	0-33	NKT211	0-25	
2N3711	0-11	BF184	0-22	NKT213	0-25	
2N3819	0-35	BF185	0-22	NKT214	0-24	
2N3927	0-35	BF194	0-13	NKT216	0-40	
2N3988	0-33	BF195	0-18	NKT217	0-45	
28301	0-59	BF196	0-15	NKT218	1-13	
28304	1-15	BF197	0-15	NKT219	0-33	
28501	0-37	BF261	0-25	NKT222	0-30	
28703	1-00	BF298	0-25	NKT224	0-25	
AA129	0-20	BF232	0-20	NKT231	0-24	
AA212	0-75	BF213	0-25	NKT275	0-20	
AZ133	0-10	BF229	0-25	NKT272	0-20	
AC107	0-35	BF230	0-28	NKT273	0-20	
AC126	0-25	BF235	0-28	NKT274	0-20	
AC127	0-25	BF263	0-20	NKT275	0-25	
AC128	0-20	BF284	0-20	NKT277	0-20	
AC187	0-20	BF285	0-25	NKT278	0-25	
AC188	0-20	BF286	0-25	NKT301	0-55	
ACY17	0-35	BF287	0-25	NKT304	0-75	
ACY18	0-27	BF288	0-22	NKT403	0-70	
ACY19	0-27	BF210	1-00	NKT404	0-60	
ACY20	0-22	BF211	1-25	NKT678	0-30	
ACY21	0-22	BF212	0-25	NKT713	0-20	
ACY22	0-18	BF218	0-45	NKT773	0-25	
ACY27	0-25	BF219	0-55	NKT777	0-38	
ACY28	0-25	BF224	0-45	O78B	0-38	
ACY30	0-65	BF244	1-00	OA6	0-12	
ACY40	0-22	BF250	0-20	OA47	0-08	
ACY41	0-22	BF251	0-20	OA70	0-10	
ACY44	0-32	BF252	0-20	OA71	0-10	
AD140	0-50	BF253	0-17	OA73	0-15	
AD149	0-50	BF264	0-45	OA74	0-15	
AD161	0-81	BF290	0-75	OA79	0-10	
AD162	0-39	BSX27	0-60	OA81	0-10	
AF106	0-30	BSX60	0-90	OA85	0-15	
AF114	0-25	BSY26	0-18	OA86	0-15	
AF115	0-25	BSY26	0-18	OA90	0-07	
AF116	0-25	BSY27	0-18	OA91	0-07	
AF117	0-20	BSY51	0-50	OA95	0-07	
AF118	0-50	BSY93A	0-12	OA200	0-08	
AF119	0-20	BSY93	0-12	OA202	0-10	
AF124	0-30	BT102/500P	1-10	OA210	0-25	
AF125	0-30	BTY42	0-92	OA211	0-30	
AF126	0-30	BTY79/100R	0-80	OA2200	0-60	
AF127	0-30	BTY79/100R	0-80	OA2201	0-45	
AF139	0-38	0-75	0-75	OA2202	0-45	
AF178	0-55	BTY79/400R	1-10	OA2203	0-45	
AF179	0-65	BY100	0-15	OA2204	0-45	
AF180	0-55	BY126	0-14	OA2205	0-45	
AF181	0-60	BY127	0-16	OA2206	0-45	
AF188	0-40	BY182	0-85	OA2207	0-45	
AFY19	1-18	BY213	0-25	OA2208	0-40	
AFZ11	1-18	BY213	0-25	ZR24	0-88	

PRACTICAL ELECTRONICS "SCORPIO" ELECTRONIC IGNITION SYSTEM



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required.

Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision.

Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7 1/2in x 4 1/2in x 2in. approx.

Complete assembly and wiring manual 25p, refundable on purchase of kit. Price: £10.50 plus 50p P. & P.

PSYCHEDELIC LIGHTING UNIT Mk. 3



This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c.

Complete assembly built and tested. Size 9in x 7in x 3in. Price £25 carr. paid.

PLEASE NOTE ALL THE ABOVE PRICES ARE SUBJECT TO V.A.T. ADJUSTMENT

DABAR ELECTRONIC PRODUCTS

98a Lichfield Street, Walsall, Staffs. WSI IJZ

TELEPHONE: WALSALL 34365

TELEGRAMS: DABELEC Walsall Staffs.

F M TUNER THOUSANDS NOW IN USE NELSON-JONES

Approved parts of this outstanding design (W.W. April 1971). Featuring 0.75µV sensitivity. Mosfet front end. Ceramic I.F. strip. Triple gang tuning, 1/2V r.m.s. output level, suitable for phase locked decoder. Designer's own PCB S.A.E. please for lists.

Solid State Tuning Indicator.

High Performance Decoder also available.

PUSH BUTTON VARICAP

Tuning now available.

Six Position push button unit with individual frequency scales. Teak case and full metalwork matches the Texan amp. Please send for details.

LIGHT EMITTING DIODES (Red)

Improved Type panel or PCB mounting with free mounting clip—clear or black. Order LEDIA. Please add postage.

Monsanto miniature PCB mounting with radial leads. Order LED2. Please add postage.

NOW ONLY 35p each with connection data + V.A.T.

7 SEGMENT LED DISPLAY

0.325in Characters 0-9 and nine letters. TTL, DTL compatible. ONLY £2.46 each, p.p. 10p. BCD-7Seg Dec Driver, £1.30 (+ V.A.T.)

INTEGREX LIMITED, DEPT. P.E.

P.O. BOX 45, DERBY DE1 1TW

Tel.: Repton (0283 89) 3580

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.

Valves, Tubes and Transistors • Closed Sat. 1 p.m.-3 p.m.


Subject C.W.O. only • Tel. 01-677 2424-7

All orders subject to V.A.T. at 10% rate. This must be added to the total order including postage.



I.L.P. (Electronics) Ltd

100 WATTS!

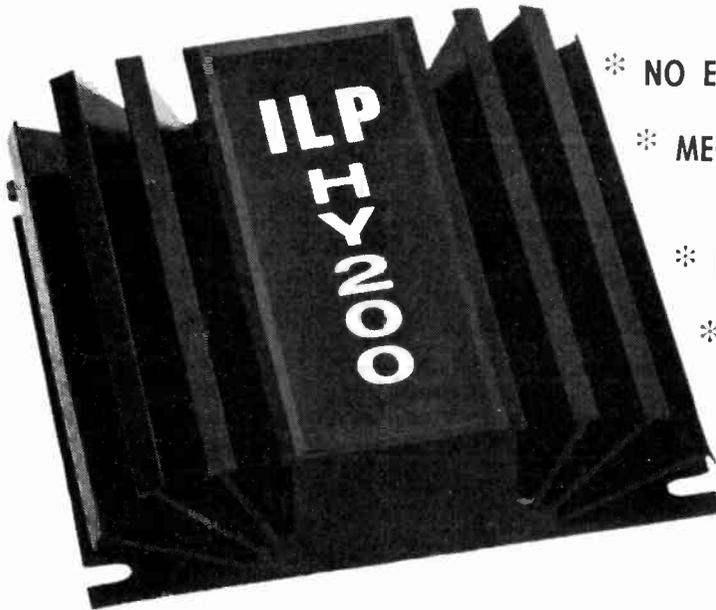

- * NO EXTERNAL COMPONENTS
- * MECHANICALLY & ELECTRICALLY ROBUST
- * INTEGRAL HEATSINK
- * HERMETICALLY SEALED UNIT
- * ATTRACTIVE APPEARANCE
- * LOW COST
- * BRITISH BUILT

With the development of the HY200, ILP bring you the first **COMPLETE** Hybrid Power Amplifier.

COMPLETE: because the HY200 uses no external components!

COMPLETE: because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.

OUTPUT POWER: 100 watts RMS; 200 watts peak music power. **INPUT IMPEDANCE:** 10k Ω . **INPUT SENSITIVITY:** 0Dbm (0.775volt RMS). **LOAD IMPEDANCE:** 4-16 Ω . **TOTAL HARMONIC DISTORTION:** less than 0.1% at 100 watts, typically 0.05%. **SIGNAL : NOISE:** better than 75Db relative to 100 watts. **FREQUENCY RESPONSE:** 10Hz-50KHz \pm 1Db. **SUPPLY VOLTAGE:** \pm 45volts. **APPLICATIONS:** P.A., Disco, Groups, Hi-Fi, Industrial. **PRICE:** £14.90 inc. VAT & P&P. Trade applications welcomed.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified study method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.


You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

Specialist Booklet

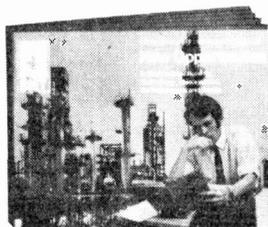If you wish to make a career in Electronics, send for your FREE copy of "NEW OPPORTUNITIES". This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. BPE19, ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK


CL BPE19

NAME (BLOCK CAPITALS)

AGE

ADDRESS

SUBJECT OF INTEREST

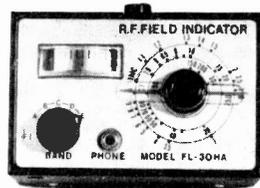

R.F. FIELD INDICATOR
Model FL-30HA. Frequency Range: 5 ranges 1Mc/s to 250Mc/s, £3-30.

TAPE RECORDER LEVEL METER
500µA, 50p



CARDIOID DYNAMIC MICROPHONE

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £4-50.



4 1/2 x 3 1/2 in METER. 30µA, 50µA or 100µA, £2-60.

MULTI-METER
Model 200H
20,000 ohm/volt, £4-80.




MULTI-METER
Model C-7081GN
Range Doubler 50,000 ohm/volt, 15µA High Sensitivity Meter, £11-25.

All items advertised in previous numbers of this magazine still available. There is 10% V.A.T. charge on total order P. & P. included. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 5. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

P.E. SOUND SYNTHESISER

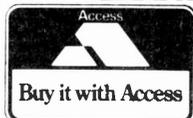

SIMPLY SEND EXACT DETAILS OF NAME AND NUMBER COPIED FROM THE FACE OF YOUR ACCESS CARD AND LEAVE THE REST TO US.

DESIGNER APPROVED KITS

The 'RING MODULATOR' I.C. **SG 3402N**

£1-74 each

ELECTRONIC ATTENUATOR **MFC 6040**

£1-00 each

ZIJ NOISE DIODE
43-5p each

mini D.I.L. 741's 32p each

while stocks last
4p stamp brings latest lists

Attractive discounts on quantity purchases.

We stock a full range of professional quality components as specified for this exciting project and many prices are down.

2% M.O. resistors now 3-2p ea. 5% low noise carbon film 1-8p ea. Cermet presets now 37-5p ea. Full range of capacitors—Ceramic, Electrolytic, Polyester, Styrene, Carbonate, Silver Mica, etc. Modular hardware kits; Dual-Rail Regulated Power Supplies; Individual component/module kits from date of publication. P.C.B. for the exciting 'Hutchinson' Tone Control Module.

EATON AUDIO P.O. Box No. 3, ST. NEOTS HUNTINGDON PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2. Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P. All prices subject to V.A.T.

BRAND NEW SEMICONDUCTORS AND COMPONENTS GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS			TTL LOGIC I.C.'s								
20301	0-15	2N3414	0-10	40318	0-02	BC125	0-15	BDY20	1-05	BSY26	0-90
20302	0-15	2N3415	0-10	40360	0-02	BC126	0-20	BDY38	0-65	BSY27	0-15
20303	0-25	2N3416	0-15	40361	0-43	BC134	0-11	BDY61	1-25	BSY38	0-20
20306	0-20	2N3417	0-21	40362	0-45	BC135	0-11	BDY62	1-00	BSY39	0-20
20309	0-85	2N3570	1-25	40363	0-61	BC136	0-15	BF115	0-23	BSY61	0-25
20345B	0-20	2N3571	0-25	40364	0-61	BC137	0-15	BF117	0-23	BSY62	0-25
20371	0-15	2N3572	0-27	40385	0-85	BC140	0-34	BF121	0-25	BSY63	0-25
20374	0-15	2N3702	0-11	40406	0-44	BC141	0-39	BF123	0-25	BSY64	0-30
2N174	0-10	2N3703	0-10	40407	0-33	BC142	0-24	BF125	0-25	BSY65	0-15
2N404	0-43	2N3704	0-14	40408	0-50	BC143	0-21	BF152	0-20	BSY78	0-40
2N456	0-75	2N3705	0-10	40409	0-38	BC144	0-24	BF153	0-20	BSY79	0-40
2N466A	0-10	2N3707	0-09	40417	0-33	BC145	0-21	BF154	0-16	BSY98A	0-09
2N457A	0-75	2N3708	0-13	40411	2-20	BC147	0-12	BF158	0-23	C111	0-03
2N481	3-25	2N3708	0-07	40414	3-55	BC148	0-12	BF159	0-27	D40N3	0-55
2N696	0-15	2N3709	0-09	40467A	0-69	BC149	0-12	BF160	0-23	GET111	0-45
2N697	0-15	2N3710	0-12	40468A	0-44	BC155	0-18	BF161	0-42	GET114	0-20
2N698	0-25	2N3711	0-09	40600	0-89	BC154	0-18	BF163	0-20	GET115	0-50
2N699	0-25	2N3712	0-05	40601	0-67	BC157	0-14	BF166	0-35	GET119	0-35
2N706A	0-12	2N3713	1-08	40602	0-46	BC158	0-13	BF167	0-21	GET135	0-50
2N708	0-18	2N3714	1-16	40603	0-83	BC159	0-14	BF173	0-34	GET538	0-20
2N709	0-33	2N3715	1-23	40604	0-50	BC160	0-27	BF177	0-29	GET880	0-30
2N711	0-20	2N3716	1-20	40636	1-16	BC167B	0-11	BF178	0-35	GET883	0-20
2N718	0-20	2N3773	3-00	40673	0-70	BC168B	0-18	BF179	0-43	GET887	0-20
2N718A	0-20	2N3779	3-15	40673	0-70	BC168C	0-11	BF180	0-35	TIP290	0-49
2N720	0-50	2N3790	2-50	AC113	0-16	BC169B	0-18	BF181	0-32	TIP30A	0-58
2N721	0-55	2N3794	2-50	AC117	0-16	BC191	0-11	BF182	0-30	TIP31A	0-62
2N914	0-22	2N3794	2-50	AC121	0-18	BC171	0-18	BF184	0-17	TIP32A	0-74
2N916	0-17	2N3792	2-50	AC126	0-25	BC172	0-11	BF185	0-17	TIP33A	0-91
2N918	0-20	2N3794	0-10	AC127	0-20	BC182	0-10	BF194	0-14	TIP35A	3-90
2N929	0-14	2N3819	0-32	AC128	0-20	BC182L	0-12	BF195	0-17	TIP36A	3-90
2N930	0-14	2N3820	0-47	AC141K	0-20	BC183	0-09	BF196	0-16	TIP41A	0-79
2N1090	0-24	2N3823	0-97	AC142K	0-25	BC183L	0-09	BF197	0-15	TIP42A	0-90
2N1131	0-20	2N3824	0-75	AC143V	0-25	BC184	0-11	BF198	0-11	TIP295	0-85
2N1182	0-20	2N3824	0-16	AC153	0-17	BC184L	0-11	BF199	0-18	TIP300	0-90
2N1302	0-16	2N3854A	0-16	AC153K	0-25	BC187	0-25	BF224J	0-19	ME0401	0-18
2N1303	0-16	2N3855	0-16	AC154	0-20	BC198	0-11	BF227	0-22	ME0402	0-20
2N1305	0-20	2N3855A	0-16	AC176	0-18	BC208	0-10	BF228	0-22	ME0411	0-17
2N1306	0-22	2N3856	0-18	AC187K	0-20	BC212K	0-10	BF238	0-22	ME0412	0-18
2N1307	0-22	2N3856A	0-18	AC188K	0-26	BC212L	0-16	BF244	0-18	ME0413	0-14
2N1308	0-25	2N3858	0-18	AC188K	0-26	BC214L	0-23	BF245	0-43	ME1120	0-25
2N1309	0-25	2N3858A	0-18	AC188K	0-26	BC237	0-09	BF246	0-43	ME4001	0-09
2N1483	0-30	2N3859	0-18	AC188K	0-26	BC238	0-09	BF247	0-49	ME4002	0-11
2N1507	0-24	2N3859A	0-18	AC191	0-27	BC239	0-09	BF248	0-18	ME4003	0-14
2N1613	0-20	2N3860	0-16	AC192	0-22	BC251	0-20	BF255	0-17	ME4101	0-10
2N1631	0-35	2N3866	0-70	AC192	0-22	BC253	0-23	BF258	0-53	ME4102	0-11
2N1637	0-38	2N3877	0-25	AC192	0-22	BC257	0-09	BF259	0-45	ME4104	0-11
2N1638	0-38	2N3877A	0-25	AC193	0-42	BC258	0-09	BF270	0-25	ME6101	0-14
2N1701	1-10	2N3900	0-20	AC193	0-65	BC259	0-18	BF272	0-53	ME6102	0-16
2N1709A	0-12	2N3900A	0-21	AC194	0-17	BC261	0-20	BF273	0-28	ME8002	0-17
2N1711	0-22	2N3901	0-33	AC171	0-17	BC262	0-18	BF274	0-28	ME8003	0-16
2N1893	0-34	2N3903	0-22	AC144	0-31	BC263	0-28	BF457	0-53	MJ400	0-78
2N2102	0-20	2N3904	0-22	AD136V	0-98	BC300	0-42	BF458	0-53	MJ420	0-60
2N2147	0-70	2N3905	0-21	AD140	0-55	BC301	0-34	BF821A	0-20	MJ421	0-88
2N2148	0-94	2N3906	0-22	AD142	0-50	BC301	0-34	BF822	0-20	MJ430	0-75
2N2192	0-40	2N4036	0-46	AD143	0-45	BC303	0-54	BF861	0-27	MJ440	0-71
2N2192A	0-40	2N4037	0-40	AD149V	0-68	BC303	0-54	BF888	0-28	MJ480	0-75
2N2193	0-40	2N4038	0-40	AD150	0-68	BC307	0-10	BF910	0-61	MJ481	0-85
2N2193A	0-40	2N4039	0-40	AD150	0-68	BC307A	0-10	BF911	0-61	MJ486	0-94
2N2194	0-27	2N4050	0-09	AD162	0-45	BC308	0-09	BF912	0-61	MJ491	1-10
2N2194A	0-27	2N4061	0-11	AD161	0-45	BC308A	0-09	BF929	0-20	MJ802	4-12
2N2196	0-37	2N4062	0-11	AD162	0-45	BC308B	0-09	BF930	0-20	MJ901	2-65
2N2196A	0-37	2N4302	0-25	AF109R	0-40	BC309	0-10	BF937	0-30	MJ1001	2-84
2N2218A	0-20	2N4303	0-47	AF114	0-25	BC309A	0-10	BF944	0-33	MJ1800	1-88
2N2219	0-37	2N4316	0-20	AF115	0-24	BC309B	0-10	BF963	0-48	MJ2500	2-92
2N2219A	0-37	2N4917	0-17	AF116	0-25	BC309B	0-10	BF968	0-28	MJ2611	3-25
2N2220	0-61	2N4918	0-50	AF117	0-25	BC309B	0-10	BF968	0-28	MJ2953	1-00
2N2221	0-20	2N4919	0-63	AF118	0-50	BC337	0-19	BF983	0-29	MJ3000	2-47
2N2221A	0-33	2N4920	0-71	AF121	0-22	BC338	0-19	BF986	0-24	MJ3001	2-79
2N2222	0-31	2N4921	0-60	AF124	0-24	BCY30	0-43	BF987	0-28	MJ3701	0-93
2N2222A	0-31	2N4923	0-60	AF125	0-20	BCY31	0-61	BF988	0-25	MJ4502	4-44
2N2269	0-11	2N5172	0-12	AF126	0-18	BCY32	1-15	BF989	0-46	MJ5340	0-47
2N2269A	0-17	2N5174	0-22	AF128	0-19	BCY33	0-18	BF990	0-35	MJ5370	0-78
2N2446	0-60	2N5175	0-25	AF170	0-25	BCY34	0-35	BFY11	0-45	MJ5381	0-80
2N2447	1-20	2N5176	0-32	AF172	0-25	BCY38	0-53	BFY12	0-35	MJ5520	0-59
2N2711	0-15	2N5190	0-92	AF178	0-55	BCY39	1-05	BFY18	0-35	MJ5521	0-73
2N2712	0-12	2N5191	0-98	AF179	0-55	BCY40	0-81	BFY19	0-35	MJ51092	1-98
2N2713	0-17	2N5192	1-24	AF180	0-55	BCY42	0-18	BFY20	0-60	MJ51102	1-57
2N2714	0-17	2N5193	1-24	AF181	0-55	BCY43	0-18	BFY21	0-60	MJ5201	1-19
2N2904	0-28	2N5194	1-10	AF200	0-35	BCY58	0-21	BFY37	0-20	MJ2901	1-56
2N2904A	0-28	2N5195	1-46	AF209	0-41	BCY70	0-17	BFY43	0-65	MJ2955	0-83
2N2905	0-33	2N5245	1-05	AF240	0-72	BCY71	0-22	BFY50	0-22	MJ1613	0-43
2N2906	0-24	2N5457	0-35	AF279	0-64	BCY72	0-13	BFY51	0-18	MM1711	0-49
2N2906A	0-24	2N5458	0-33	AF280	0-64	BCY77	0-37	BFY52	0-20	MM1732	0-64
2N2907	0-32	2N5459	0-33	AFY42	0-74	BCY78	0-40	BFY53	0-15	MM2712	0-64
2N2907A	0-32	2N5460	0-33	AFY42	0-74	BCY78	0-40	BFY53	0-15	MM2712	0-64
2N2923	0-12	2N5919	0-22	AL102	0-75	BCZ10	0-55	BFY64	0-41	MP8111	0-32
2N2924	0-15	2N5919	0-22	AL103	0-70	BCZ11	0-50	BFY76	0-22	MP8112	0-40
2N2925	0-18	2N5919	0-22	AL103	0-70	BCZ11	0-50	BFY76	0-22	MP8113	0-47
2N2926	0-18	2N5919	0-22	AL103	0-70	BCZ11	0-50	BFY76	0-22	MP8A05	0-25
2N2926	0-18	2N5919	0-22	AL103	0-70	BCZ11	0-50	BFY76	0-22	MP8A06	0-25
Green	0-12	40611	0-81	AS729	0-86	BD116	0-50	BFY78	0-38	MP8A01	0-44
Yellow	0-10	40612	0-81	AS729	0-86	BD123	0-52	BFY93	0-38	MP8A12	0-40
Orange	0-10	40613	0-81	AS750	0-85	BD124	0-67	B8X19	0-13	MP8A14	0-24
2N3053	0-81	3N154	0-84	AS755	0-85	BD130	0-67	B8X20	0-14	MP8A55	0-30
2N3054	0-80	3N159	1-17	BU103	1-25	BD131	0-40	B8X21	0-20	MP8A65	0-28
2N3055	0-50	3N187	1-55	BU107	1-25	BD132	0-60	B8X26	0-40	MP8A66	0-28
2N3090	0-20	3N200	2-40	BU108	1-25	BD133	0-43	B8X27	0-84	MP8A67	0-28
2N3091	0-20	3N201	1-05	BU109	1-25	BD134	0-40	B8X28	0-25	MP8U01	0-44
2N3091A	0-22	3N201	1-05	BU113	0-13	BD137	0-55	B8X29	0-47	MP8U05	0-48
2N3391A	0-18	BC114	0-12	BD138	0-68	B8X60	0-54	B8X30	0-14		
2N3392	0-18	BC115	0-16	BD139	0-71	B8X61	0-54	B8X31	0-14		
2N3393											



NORTH AMERICAN SEMICONDUCTOR COMPANY LIMITED

TRANSISTORS

2N4310	0.540	2N4037	0.480	2N5055	0.380	2N4288	0.180	2N3646	0.130	2N3015	0.485
2N4311	0.880	2N4121	0.120	2N5056	2.000	2N4966	0.120	2N3685	0.880	2N3019	0.540
2N4312	0.540	2N4122	0.180	2N5057	2.370	2N4967	0.180	2N3686	0.580	2N3020	0.580
2N4313	0.880	2N4123	0.140	2N5058	0.880	2N4968	0.140	2N3687	0.150	2N3053	0.180
2N4314	0.280	2N4124	0.140	2N5126	0.140	2N7005	0.180	2N3688	0.150	2N3054	0.450
2N4315	0.280	2N4125	0.180	2N5129	0.080	2N7008	0.140	2N3693	0.150	2N3072	0.580
2N4316	0.280	2N4134	1.000	2N5130	0.080	2N7118	0.220	2N3694	0.150	2N3073	0.455
2N4318	0.280	2N4135	1.000	2N5131	0.100	2N7222	0.080	2N3724	0.420	2N3107	0.540
2N4320	0.880	2N4140	0.270	2N5132	0.080	2N7444	0.180	2N3724A	1.100	2N3108	0.540
2N4324	1.000	2N4141	0.280	2N5133	0.080	2N7553	0.180	2N3725	0.425	2N3109	0.540
2N4329	2.000	2N4142	0.370	2N5134	0.080	2N7800	0.270	2N3725A	1.000	2N5143	0.105
2N4330	0.280	2N4143	0.380	2N5135	0.080	2N780A	0.270	2N3734	1.170	2N5810	0.270
2N4330A	0.440	2N4200	1.070	2N5137	0.180	2N834	0.255	2N3735	2.700	BC107	0.120
2N4351	0.880	2N4200	2.000	2N5138	0.080	2N814	0.280	2N3803	0.185	BC108	0.185
2N4351A	0.880	2N4227	0.280	2N5139	0.080	2N815	0.280	2N3804	0.180	BC109	0.140
2N4352	0.880	2N4228	0.270	2N5140	0.170	2N816	0.280	2N3805	0.175	BC177	0.180
2N4353	0.280	2N4248	0.110	2N5141	0.185	2N817	0.280	2N3806	0.185	BC178	0.180
2N4359	0.240	2N4249	0.120	2N5142	0.185	2N818	0.280	2N3845	0.800	BC179	0.180
2N4360	0.480	2N4250	0.180	2N1711	0.220	2N829	0.185	2N3846	1.280	BC21A	0.340
2N4361	0.280	2N4257	0.175	2N1893	0.270	2N829A	0.740	2N3947	1.370	BC21B	0.340
2N4362	0.480	2N4258	0.220	2N1890	0.280	2N830	0.180	2N2369	0.155	BC262A	0.360
2N4364	0.280	2N4259	0.240	2N2017	0.870	2N830A	0.080	2N2369A	0.170	BC262B	0.380
2N4368	0.880	2N4258A	0.275	2N2102	0.375	2N856	0.220	2N2483	0.210	BC263A	0.380
2N4369	0.480	2N4274	0.135	2N2152	0.485	2N860	2.210	2N2484	0.240	BC263B	0.380
2N4344	0.880	2N4275	0.125	2N2182A	0.375	2N865	1.000	2N2508	0.710	BCY70	0.155
2N4350	0.790	2N4313	0.280	2N2193	0.470	2N1131	0.225	2N2510	0.710	BCY71	0.220
2N4352	0.150	2N4384	0.210	2N2193A	0.670	2N1132	0.225	2N2511	1.130	BCY72	0.128
2N4353A	0.790	2N4385	0.240	2N2194	0.485	2N1420	0.215	2N2586	1.000	BF328	0.455
2N4354	0.280	2N4386	0.280	2N2195	0.680	2N1813	0.180	2N2604	1.380	BF83	0.740
2N4345	4.000	2N4400	0.180	2N2196	0.485	2N3564	0.180	2N2605	0.640	BFX29	0.280
2N4346	1.280	2N4401	0.240	2N2195A	0.670	2N3565	0.110	2N2657	3.070	BFX30	0.330
2N4347	1.750	2N4402	0.180	2N2217	0.275	2N3566	0.120	2N2658	4.980	BFX8	0.280
2N4348	1.000	2N4403	0.240	2N2218	0.280	2N3567	0.120	2N2690	3.080	BFX85	0.280
2N4349	2.100	2N4416	0.110	2N2218A	0.240	2N3568	0.170	2N2891	3.080	BFX86	0.230
2N4350	2.000	2N4817	0.180	2N2219	0.240	2N3569	0.180	2N2894	0.220	BFX87	0.220
2N4353	0.130	2N4843	0.080	2N2219A	0.270	2N3676	1.220	2N2894A	0.085	BFY28	0.210
2N4354	0.280	2N4854	0.170	2N2221	0.180	2N3678	0.120	2N2904	0.225	BFY50	0.180
2N4355	0.455	2N4855	0.170	2N2221A	0.280	2N3638A	0.120	2N2904A	0.255	BFY51	0.180
2N4356	0.455	2N4856	0.170	2N2222	0.100	2N3639	0.280	2N2905	0.270	BFY52	0.190
2N4355	0.790	2N4857	0.170	2N2222A	0.240	2N3640	0.280	2N2905A	0.280	BSY38	0.170
2N4358	0.485	2N4858	0.170	2N2223	0.180	2N3641	0.180	2N2906	0.220	BSY39	0.170
2N4359	0.485	2N4859	0.170	2N2223A	0.280	2N3642	0.180	2N2906A	0.245	BSY51	0.200
2N4362	0.530	2N4870	0.180	2N2270	0.080	2N3643	0.180	2N2907	0.210	BSY52	0.200
2N4363	0.870	2N4871	0.240	2N2287	0.080	2N3644	0.180	2N2907A	0.220	BSY53	0.200
2N4368	0.480	2N4872	0.280	2N2293	1.280	2N3645	0.180	2N3011	0.180	BSY54	0.200
								2N3012	0.530	BSY55A	0.130

THYRISTORS

Type No.	Price	IT (RMS)	V DROM
NAS106F	0.250	4A	50
NAS106A	0.310	4A	100
NAS106B	0.380	4A	200
NAS106D	0.380	4A	400
NAS106F	0.283	6A	50
NAS206A	0.340	6A	100
NAS206B	0.485	6A	200
NAS206D	0.653	6A	400
NAS306F	0.313	8A	50
NAS306A	0.380	8A	100
NAS306B	0.480	8A	200
NAS306D	0.725	8A	400
NAS406F	0.360	10A	50
NAS406A	0.434	10A	100
NAS406B	0.584	10A	200
NAS406D	0.812	10A	400
NAS806F	0.438	16A	50
NAS806A	0.543	16A	100
NAS806B	0.830	16A	200
NAS806D	1.015	16A	400

NAS1640	0.342	1.6A	400
NAS4510	0.260	4.5A	100
NAS4520	0.480	4.5A	200
NAS4540	0.840	4.5A	400
NAS6510	0.380	6.5A	100
NAS6520	0.440	6.5A	200
NAS6540	0.700	6.5A	400
NAS8510	0.430	8.5A	100
NAS8520	0.480	8.5A	200
NAS8540	0.770	8.5A	400
NAS10010	0.480	10A	100
NAS10020	0.520	10A	200
NAS10040	0.840	10A	400

EPOXY 4 AMP AND 6 AMP BRIDGE RECTIFIERS

Type No	IF	VRM	Price
N7001	4A	50PIV	0.320
N7012	4A	100PIV	0.380
N7013	4A	200PIV	0.430
N7014	4A	400PIV	0.580
N7015	4A	600PIV	0.755
N7021	6A	50PIV	0.380
N7022	6A	100PIV	0.430
N7023	6A	200PIV	0.540
N7024	6A	400PIV	0.850
N7025	6A	600PIV	0.810

TRIACS WITH INTERNAL TRIGGERS

Type No.	Price	IT (RMS)	V DROM
NASQ1610	0.310	1.6A	100
NASQ1620	0.330	1.6A	200
NASQ1640	0.380	1.6A	400
NASQ4510	0.380	4.5A	100
NASQ4520	0.440	4.5A	200
NASQ4540	0.710	4.5A	400
NASQ6510	0.480	6.5A	100
NASQ6520	0.480	6.5A	200
NASQ6540	0.780	6.5A	400
NASQ8510	0.480	8.5A	100
NASQ8520	0.580	8.5A	200
NASQ8540	0.830	8.5A	400
NASQ10010	0.580	10A	100
NASQ10020	0.580	10A	200
NASQ10040	0.880	10A	400

2 AMP ENCAPSULATED PLASTIC BRIDGE RECTIFIERS

N6001	2A	50PIV	0.350
N6002	2A	100PIV	0.380
N6003	2A	200PIV	0.460
N6004	2A	400PIV	0.430
N6005	2A	600PIV	0.500


PLASTIC RECTIFIER

1N4001	0.080
1N4002	0.080
1N4003	0.080
1N4004	0.100
1N4005	0.110
1N4006	0.120
1N4007	0.130

TRIACS

Type No.	Price	IT (RMS)	V DROM
NAS1610	0.295	1.6A	100
NAS1620	0.314	1.6A	200

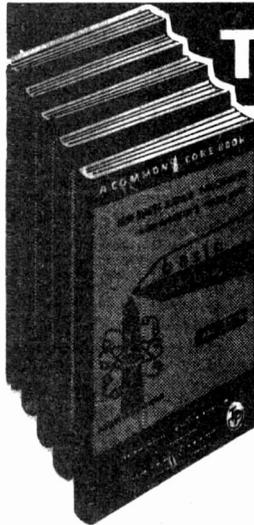Available from **THE RADIO SHOP**
 16 CHERRY LANE, BRISTOL BS1 3NG
 Tel. Bristol 421196. Open Mon.-Sat. 9.00 a.m.-5.30 p.m.



The Pictorial Method

BASIC ELECTRICITY (5vols) BASIC ELECTRONICS (6vols) TELEVISION (3vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

WHAT READERS SAY

"EVERYTHING IS MADE SIMPLE" which makes reading a pleasure.
V.S., Farley

"BOOKS ARE WONDERFUL" thank you.
A.C.S., Colwyn Bay

I earnestly believe these manuals make the subject become a "Cake Walk".
S.S., Lewisham

Amazed to see so much information and in such a self-explanatory way.
S.F., Huddersfield

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....
 BASIC ELECTRICITY 5 parts £4.50
 BASIC ELECTRONICS 6 parts £5.40
 BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage and Packing.
YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME

BLOCK LETTERS

FULL POSTAL

ADDRESS

POST NOW FOR THIS OFFER!

AUDIOTRONIC MODEL ATM.1

Top value 1,000 o.p.v. pocket multimeter.
 Ranges: 0/10/50/250/1,000V. A.C. and D.C. D.C. Current 0-1mA/100mA.
 Resistance: 0/150 Kohms. Decibels: -10 to +22dB. Size: 90 x 60 x 28mm. Complete with test leads. £2-50. Post 15p.



LT 601 MULTI-METER

New style 20,000 O.P.V. pocket multimeter. 5/25/50/250/500/2,500V d.c. 10/50/100/500/1,000V a.c. 50µA/250A. 6K/6 meg ohms. -20 to +22dB. £3-75. Post 20p.



MODEL TH-12

20,000 O.P.V. Overload protection. Slide switch selector. 0/0.25/2.5/10/50/250/1,000V d.c. 0/10/50/250/1,000V a.c. 0/20µA/25/250mA d.c. 0/3K/30K/300K/3 meg. -20 to +20dB. £4-97. Post 15p.



RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 O.P.V. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1,000V d.c. 2.5/10/50/250/500/1,000V a.c. D.C. current 100µA/1/10/100mA/1A. Resistance 300 ohms/330/300K/3MΩ. Complete with instructions and sturdy steel carrying case. OUR PRICE £2-97. Post 25p.



MODEL FL486

20KΩ/V d.c. 8KΩ/V a.c. Mirror scale. 0/6/3/12/30/120/600V d.c. 3/30/120/600V a.c. 50/600µA/60/600mA. 10/100K/1 Meg/10 MegΩ. -20 to +46dB. £2-97. Post 12p.



MODEL 500 30,000 O.P.V.

with overload protection mirror scale 0/0.5/2.5/20/25/100/250/500/1,000V d.c. 0/2.5/10/25/100/250/500/1,000V a.c. 0/50µA/5/30/300mA. 12 amp. d.c. 0/60K/6 Meg./60 MegΩ. £2-95. Post paid. Leather case £1-75.



U4812 MULTIMETER

Extremely sturdy instrument for general electrical use. 687 O.P.V. 0/0.3/1.5/7.5/30/60/150/300/600/900V d.c. and 75mV. 0/0.3/1.5/7.5/30/60/150/300/600/900V a.c. 0/300µA/1.5/6/15/60/150/600mA/1.5/6 amp. d.c. 0/1.5/15/60/150/600MA/1.5/6 amp. a.c. 0/200Ω/3k/30kΩ. Accuracy Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £2-50. Post 25p.



HIOKI MODEL 700X

100,000 O.P.V. Overload protection. Mirror scale. 0/30/6/1.2/1.5/8/6/12/30/60/120/300/600/1,200V d.c. 1.5/3/6/12/30/60/150/300/600/1,200V a.c. 15/30µA/3/6/30/60/150/300mA/6/12 amp. d.c. 2K/200K/20 meg. -20 to +63dB. £13-50. Post 20p.



MODEL C-7080 EN

Giant 6in mirror scale. 20,000 O.P.V. 0/0.25/1/2.5/10/50/250/1,000/5,000V d.c. 0/2.5/10/50/250/1,000/5,000V a.c. 0/50µA/1/10/100/500mA/10 amp. d.c. 0/2K/200K/20 meg. -20 to +50dB. £13-95. Post 35p.



ALL PRICES ARE EXCLUSIVE OF 10% VAT

370 WTR MULTIMETER

Features a.c. current ranges. 20,000 O.P.V. 0/0.5/2.5/10/50/250/500/1,000V d.c. 0/2.5/10/30/250/500/1,000V a.c. 0/50µA/1/10/100mA/1/10 amp. d.c. 0/100mA/1/10 amp. a.c. 0/5K/50K/500K/5MEG/50MEG. -20 +62dB. £15. Post 25p.



TMK LAB TESTER

100,000 O.P.V. 61in scale buzzer short circuit check. 100,000 OPV d.c. 5/Volt a.c. D.c. volts: 0-5, 2-5, 10, 50, 250, 1,000V. A.c. volts: 3, 10, 50, 250, 500, 1,000V. D.c. current: 10, 100µA, 10, 100, 300mA, 2.5, 10A. Resistance: 1K, 10K, 100K, 10 meg, 100 meg. Decibels: -10 to +49dB. Plastic case with carrying handle, size 7 1/2in x 6 1/2in x 3 1/2in. P. & P. 25p.



Model 9-100TR MULTIMETER/TRANSISTOR TESTER

100,000 O.P.V. mirror scale/overload protection. 0/0.12/0.6/3/12/30/120/600V d.c. 0/6/30/120/600V a.c. 0/12/600µA/12/300mA/12 amp. d.c. 0/10 K/1 MEG/100 MEG. -20 to +50dB. 0-01-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £13-50. Post 25p.



LB3 TRANSISTOR TESTER

Tests Ico and B. Pnp/npn. Operates from 9V battery. Complete with all instructions, etc. £3-95. Post 20p.



LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with all instructions, etc. £4-50. Post 20p.



MODEL 449A IN CIRCUIT TRANSISTOR TESTER

Checks true a.c. beta input. Checks Ico. Checks diodes in/out. Checks SCR, etc. Beta HI 10-500 LO 2-50 Ibc0 0-5000µA. 220/240V a.c. operation. £17-50. Post 25p.



KAMODEN HM-350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and D.C. current. Amplification factor of NPN, PNP, transistors, diodes, SCRs, etc. 4" x 4 1/2" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. £12-50. Post 30p.



TE-65 VALVE VOLTMETER

28 ranges. D.c. volts 1.5-1,500V. a.c. volts 1.5-1,500V. Resistance up to 1,000 megohms. 200/240V a.c. operation. Complete with probe and instructions. £17-50. Post 30p. Additional probes available: R.F. £2-12; H.V. £2-50.



KAMODEN 72.200 MULTITESTER

High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/0.06/0.3/3/30/120/600/1,200V d.c. 0/3/12/60/300/1,200V a.c. 0/10µA/1/2mA/120mA/600mA/12A d.c. 0/12A a.c. -20 to +63dB. 0/2kΩ/200kΩ/2MΩ/200MΩ. £16-95. Post 30p.



MODEL U4811 SUB-STANDARD MULTI-RANGE VOLT AMMETER

Sensitivity 330 ohms/Volt a.c. and d.c. Accuracy 0-5% d.c. 1% a.c. Scale length 165mm. 0/300/750µA/1.5/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5 amp. d.c. 0/3/7.5/15/30/75/150/300/750mA/1.5/3/7.5 amp. a.c. 0/75/150/300/750V d.c. 0/750V/1.5/3/7.5/15/30/75/150/300/750V a.c. Automatic cut out. Supplied complete with test leads, manual and test certificates. £49. Post 50p.



KAMODEN HM720B F.E.T. V.O.M.

Input impedance 10MΩ. Ranges: 0/0.25/1/2.5/10/50/250/1,000V d.c. 0/2.5/10/50/250/1,000V a.c. 0/25µA/2.5/25/250MA d.c. -20 to +62dB. 0/5k/50k/500k/5MΩ/500MΩ. £14-95. Post 30p.



TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0/1/003/1/3/1/10/30/100/300V. R.M.S. 4eps. -1.2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. a.c. £17-50. Carr. 25p.



TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER

Battery-operated, 11 meg input. 26 ranges. Large 4 1/2in mirror scale. Size 3 1/2in x 4 1/2in x 2 1/2in. D.c. volts 0.3-1,200V. A.c. volts 3-300V R.M.S. 8-0-800V P-P. D.C. Current 0-12-12MA. Resistance up to 2,000M ohm. Decibels -20 to +51dB. Complete with leads/instructions. £17-50. P. & P. 20p.



MODEL L-55 FET V.O.M.

Input impedance 10 meg ohms. 0/0.3/1.2/8/30/120/600V d.c. 0/3/12/60/120/600V a.c. 0/120µA/120µA/600µA. 0/1K/100K/10 meg/100 meg ohms. £15-97. Post 25p.



KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1,000 Megohms, 500 Volt. Meter operated. Wide range clear meter 4 1/2" x 4". Complete with deluxe carrying case, batteries, instructions. £19-95. Post 30p.



MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 40KHz-280MHz in 9 coils 50µA meter. 9V battery operation. Size 180mm x 80mm x 40mm. £12-50. Post 20p.



TO-3 PORTABLE OSCILLOSCOPE

8in tube, Y amp. Sensitivity 0-1V p-p/CM. Bandwidth 1.5cps-1.5MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0-9V. p-p/CM. Bandwidth 1.5cps-800KHz. Input imp. 2 meg Ω 20pF. Time base 5 ranges 10cps-300KHz. Synchronisation. Internal/external. Illuminated scale 140mm x 215mm x 330mm. Weight 15 1/2lb. 220/240V a.c. Supplied brand new with hand-book. £47-50. Carr. 50p.



CI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits VERT. AMP. Bandwidth 10MHz. Sensitivity at 100KHz 7 V RMS/mm. 0-1-25; HOR. AMP. Bandwidth 500KHz. Sensitivity at 100KHz, V RMS/mm. 0-3-25; Pre-set triggered sweep 1-3,000µsec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220mm x 360mm x 430mm, 15-250V a.c. operation. £39. Carr. paid.



RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5MHz Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in x 4in C.R.T. Calibrated triggered sweep from 0-20µsec. to 100 mill-sec per cm. Free running time base 50 Hz-1MHz. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual. £87. Carr. paid.



TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 KHz-500 MHz on 6 bands. Directly calibrated. Variable R.F. attenuator audio output. Xtal socket for calibration. 220/240V a.c. Brand new with instructions. £17-50. Carr. 37p. Size 140mm x 215mm x 170mm.



TE22 SINE SQUARE WAVE AUDIO GENERATORS

Sine: 20c/s to 200 kc/s on 4 bands. Square: 20c/s to 30 kc/s. Output impedance 5,000 ohms. 200/250V a.c. Supplied brand new and guaranteed with instruction manual and leads. £17-50. Carr. 37p.



ARF-300 AF/RF SIGNAL GENERATOR

All transistorised, compact, fully portable, AF sine wave 18 Hz to 250 KHz. AF square wave 18 Hz to 100 KHz. Output sine/square 10V. P-P. RF 100 KHz to 200 MHz. Output 1v. maximum. Operation 220/240V A.C. Complete with instructions and leads. £29-95. Post 50p.



MODEL AT201 DECADE ATTENUATOR

Frequency range 0-200KHz. Attenuator 0-11 dB. 0-1dB step. Impedance 600 ohms. Max. Input power 30dBm. Size 180mm x 90mm x 55mm. £12-50. Post 37p.



BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Size 18-200,000 Hz. Square 18-50,000 Hz. Output max. +10dB (10 K ohms) Operation internal batteries. Attractive 2-tone case 7 1/2in x 5in x 2in. Price £17-50. Carr. 17p.



AUTO TRANSFORMERS

0/115/230V. Step up or step down. Fully shrouded.

80W	£2-10	P. & P. 18p
150W	£2-70	P. & P. 18p
300W	£3-60	P. & P. 23p
500W	£5-25	P. & P. 38p
1000W	£7-50	P. & P. 38p
1500W	£10-20	P. & P. 43p
2250W	£17-25	P. & P. 60p
5000W	£35-00	P. & P. 61p

MCA-220 AUTOMATIC VOLTAGE STABILISER

Input 88-125V a.c. or 175-250V a.c. Output 120V a.c. or 240V a.c. 200VA rating. £11-97. Post 60p.





HIGH QUALITY CONSTRUCTION KITS
Appointed stockist at all branches
Complete with comprehensive, easy to follow instructions, and covered by full guarantee
Post and packing 15p per kit

AF20	Mono transistor amplifier	£4.80
AF30	Mono transistor pre-amplifier	£2.61
AF310	Mono amplifier (use two for stereo)	£5.91
ATS	Automatic light control	£2.58
A130	Photo cell switching unit	£5.70
A150	400W Triac light dimmer/speed control	£4.80
AT55	1.200W Triac light dimmer/speed control	£4.70
AT56	2.200W Triac light dimmer/speed control	£4.80
AT60	Psychronic light control, 3 channel	£7.80
AT65	Psychronic light control, single channel	£4.55
MF81	Medium wave transistor radio	£3.33
MF55	FM transistor transmitter, 1 channel	£2.70
MF75	FM transistor receiver	£2.88
MF310	FM tuner unit	£15.81
HF320	De-use FM tuner unit	£24.12
HF330	Stereo decoder for HF310/HP325	£9.96
MF395	Aerial amplifier for AM/FM bands, I, II, III	£7.80
GP310	Stereo pre-amp for use with 2x AF310	£21.27
GU330	Tremolo unit for guitars etc.	£7.50
NT10	Power supply 100 mA 15V 2A 12V unstab	£8.15
NT300	Professional stabilized power supply 2x 30 Volt 2.2 Amp	£12.51
NT305	Transformer converter 12/15V AC/DC to 6V, 7.5V or 9V DC	£4.50
NT310	Power supply 240V AC to 2x 18V DC	£4.80
NT315	Power supply 240V AC to 4x 15V DC 500 mA	£8.57

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality at low cost. All models—Input 230V, 50/60 c/s. Variable output 0-260V.

MODEL S-260 GENERAL PURPOSE BENCH MOUNTING



1 amp	£7.00
2.5 amp	£8.05
3 amp	£11.75
8 amp	£15.90
10 amp	£22.50
12 amp	£23.80
20 amp	£29.00
25 amp	£38.00
40 amp	£52.50

MODEL S-260B

Panel mounting	
1 amp	£7.00
2.5 amp	£8.05

Carriage and Packing Extra

RP214 REGULATED POWER SUPPLY
Solid state. Variable output 0-24V d.c. up to 1 amp. Dual scale meter to monitor voltage and current. Input 220/240V a.c. Size 185 x 85 x 105mm. £8.97. Post 25p.




PS.200 REGULATED P.S.U.

Solid state. Variable output 5-20V d.c. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240V a.c. Size 7 1/2in. x 5 1/2in. x 3 1/2in. £19.95. Post 25p.



PS.1000B REGULATED POWER SUPPLY

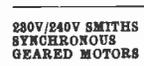Solid state. Output 6, 9 or 12V d.c. up to 3 amps. Meter to monitor current. Input 220/240V a.c. Size 4in. x 3 1/2in. x 5 1/2in. £11.97. Post 25p.



230V/240V SMITHS SYNCHRONOUS GEARED MOTORS
Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 RPH CW. 50p each. Post 12p.



POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing, 1/2in dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1000 ohms. 96p. P. & P. 10p.

50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1.85. P. & P. 10p.

100 WATT. 1.5/10/25/50/100/250/500/1000 or 2500 ohms. £1.95. P. & P. 15p.

SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

TYPE 8W.100 100mm x 80mm Fronts

50µA	£4.15
50-0-50µA	£3.95
100µA	£3.95
100-0-100µA	£3.90
500µA	£3.70
1mA	£3.60
20V d.c.	£3.60
50V d.c.	£3.60
300V d.c.	£3.60
1 amp d.c.	£3.60



TYPE MR.52P 4 1/2in. x 4 1/2in. Fronts

50µA	£4.40
50-0-50µA	£4.25
100µA	£4.25
100-0-100µA	£4.05
500µA	£3.90
1mA	£3.80
5 amp d.c.	£3.60
10 amp d.c.	£3.60
30V d.c.	£3.60
50V d.c.	£3.60
150V d.c.	£3.90
300V d.c.	£3.95
100-0-100µA	£3.85
300V a.c.	£3.85
8 Meter 1mA	£3.90
500µA	£2.55
VU Meter	£3.90
1 amp a.c.*	£3.90
5 amp a.c.*	£3.90
10 amp a.c.*	£3.90
20 amp a.c.*	£3.90
30 amp a.c.*	£3.90



TYPE 8D.880 82.5mm x 110mm Fronts

10mA	£3.10
50mA	£3.10
100mA	£3.10
500mA	£3.10
1 amp	£3.10
5 amp	£3.10
10 amp	£3.10
5V d.c.	£3.10
10V d.c.	£3.10
20V d.c.	£3.10
100-0-100µA	£3.35
300V d.c.	£3.30
15V a.c.	£3.30
1mA	£3.10
5mA	£3.10




TYPE 8D.640 63.5mm x 85mm Fronts

50µA	£3.05
50-0-50µA	£3.05
100µA	£3.00
100-0-100µA	£3.00
200µA	£3.00
500µA	£3.00
1mA	£2.90
5mA	£2.90
10mA	£2.90
50mA	£2.90
100mA	£2.90

TYPE 8D.460 46mm x 59.5mm Fronts

50µA	£2.80
50-0-50µA	£2.80
100µA	£2.75
100-0-100µA	£2.75
200µA	£2.70
500µA	£2.70
1mA	£2.65
5mA	£2.60
10mA	£2.60
50mA	£2.60
100mA	£2.60
500mA	£2.60

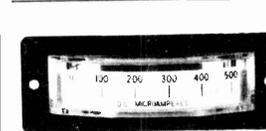

"SEW" EDGEWISE METERS

TYPE PE.70. 3 1/2in. x 1 1/2in. x 2 1/2in. deep.

50µA	£3.75
50-0-50µA	£3.60
100µA	£3.60
100-0-100µA	£3.50
200µA	£3.40

***MOVING IRON—ALL OTHERS MOVING COIL**
Please add postage

240° Wide Angle 1mA Meters

MW1-6 60mm square	£3.97
MW1-8 80mm square	£4.97

230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. Post 10p (100 lots £40). Quantities available.

TYPE MR.32P. 1 1/2in. square Fronts.



200mA	£3.25
300mA	£3.25
500mA	£3.25
750mA	£3.25
1 amp	£3.25
2 amp	£3.25
5 amp	£3.25
10 amp	£3.25
3V d.c.	£3.25
50µA	£2.55
50-0-50µA	£2.50
100µA	£2.45
100-0-100µA	£2.40
200µA	£2.35
500µA	£2.35
1mA	£2.35
1-0-1mA	£2.35
2mA	£2.25
5mA	£2.25
10mA	£2.25
20mA	£2.25
50mA	£2.25
100mA	£2.25
150mA	£2.25

TYPE MR.45P. 2in. square Fronts.

50µA	£2.70
50-0-50µA	£2.65
100µA	£2.60
100-0-100µA	£2.50
200µA	£2.50
500µA	£2.50
1mA	£2.40
5mA	£2.40
10mA	£2.40
50mA	£2.40
100mA	£2.40
500mA	£2.40
1 amp	£2.40

"SEW" BAKELITE PANEL METERS

TYPE MR.65. 3 1/2in. square Fronts.



1 amp	£2.60
5 amp	£2.60
15 amp	£2.60
30 amp	£2.60
50 amp	£2.60
5V d.c.	£2.60
10V d.c.	£2.60
20V d.c.	£2.60
50V d.c.	£2.60
150V d.c.	£2.60
300V d.c.	£2.60
500µA	£2.50
500-0-500µA	£2.50
1mA	£2.50
1-0-1mA	£2.50
5mA	£2.50
10mA	£2.50
50mA	£2.50
100mA	£2.50
500mA	£2.50
1 amp a.c.*	£2.60
5 amp a.c.*	£2.60
10 amp a.c.*	£2.60
20 amp a.c.*	£2.60
30 amp a.c.*	£2.60

"SEW" EDUCATIONAL METERS



TYPE ED.107. Size overall 100mm x 90mm x 106mm.
A new range of high quality moving coil instruments ideal for school experiments and other bench applications. The 3in. mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

50µA	£2.90
100µA	£2.90
1mA	£2.95
50-0-50µA	£3.40
10-0-1mA	£3.95
1A d.c.	£5.95
5A d.c.	£5.95
10V d.c.	£5.95
20V d.c.	£5.95
50V d.c.	£5.95
300V d.c.	£5.95
Dual range	
600mA/5A d.c.	£7.00
5V/50V d.c.	£7.00

TYPE 8-80 80mm square Fronts

50µA	£3.50
50-0-50µA	£3.40
100µA	£3.40
100-0-100µA	£3.30
500µA	£3.35
1mA	£3.30
20V d.c.	£3.30
50V d.c.	£3.30
300V d.c.	£3.30
1 amp d.c.	£3.00
5 amp d.c.	£3.00
300V a.c.	£3.00
VU Meter	£3.70

Send S.A.E. for new 8-page list of Semiconductor and Valves

ALL PRICES ARE EXCLUSIVE OF 10% V.A.T.



ALSO SEE FOLLOWING PAGES

G.W.S. G.W.SMITH & CO (RADIO) LTD

UNR 30 RECEIVER




4 Bands covering 500kHz-30MHz. BFO Built-in Speaker 220/240V a.c. Brand new with instructions.
OUR PRICE £15.75 Carr. 37p

UR-1A RECEIVER



4 Bands covering 500kHz-30MHz. PET, 8 Meter. Variable BFO for SSB. Built-in Speaker. Bandspread. Sensitivity Control. 220/240V a.c. or 12V d.c. 121 x 42in x 7in. Brand new with instructions.
OUR PRICE £25.00 Carr. 37p

SKYWOOD CX203 RECEIVER

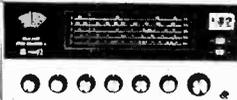

Solid state. 5 bands covering 200-420kHz and 0.55 to 30MHz. Illuminated slide rule dial. Bandspread Aerial tuning. BFO, AVC, ANL, 8 meter AM/FM, 88 B. Integrated speaker and phone socket. 220/240V a.c. or 12V d.c. Size 325 x 286 x 150mm. Complete with instructions and circuit.
OUR PRICE £32.50 Carr. 50p

LAFAYETTE HA-600 RECEIVER



General coverage 160-400kHz, 500kHz-30MHz. PET front end, 2 mech filters, product detector, variable BFO, noise limiter, 8 Meter Bandspread, RF Gain. 15in x 9in x 8in. 18 lb. 220/240V a.c. or 12V d.c. Brand new with instructions.
OUR PRICE £50.00 Carr. 50p

TRIO 9R59DS RECEIVER




4 bands covering 550kHz-30MHz continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. 88B-CW. ANL. Variable BFO. 8 meter. Sep. bandspread dial. 1F frequency 445kHz audio output 15W. Variable RF and AF gain controls. 115/250V a.c. Size: 7in x 13in x 10in with instruction manual.
OUR PRICE £49.50 Carr. Paid

FULL RANGE OF TRIO STOCKED



EMI LOUDSPEAKERS

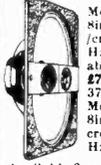

Model 350. 13in x 8in with single tweeter/crossover. 20-20,000 Hz. 15W RMS. Available 8 or 15 ohms. £7.25 each. P. & P. 37p.
 Model 450. 13in x 8in with twin tweeters/crossover. 20-20,000 Hz. 8W RMS. Available 8 or 15 ohms. £3.62 each. P. & P. 25p.

SPECIAL OFFER!

STEREO SPEAKERS

Matched pair of bookshelf speakers. Deluxe teak veneered finish. Size 14 1/2 in x 9in x 7 1/2 in. 8 ohms. 8W RMS. 15W peak. Complete with DIN lead.
OUR PRICE £12.95 Carr. 50p

OUR PRICE £12.95 Carr. 50p

HA-10 STEREO HEADPHONE AMPLIFIER



All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 500/1000Ω. Output 50mW.
OUR PRICE £6.97 P. & P. 20p

OUR PRICE £6.97 P. & P. 20p

MP7 MIXER PREAMPLIFIER



5 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9in x 5in x 3in. Inputs: Mics: 3 x 3inV 50K, 2 x 3in 600 ohm. Phono: 100mV 50K. Phono ceramic 4mV 1 meg. Output 250mV 100K.
OUR PRICE £8.97 P. & P. 20p

OUR PRICE £8.97 P. & P. 20p

1021 STEREO LISTENING STATION



For balancing and gain selection of loudspeakers, with additional facility for stereo headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets 6in x 4in x 2 1/2in.
OUR PRICE £2.25 P. & P. 20p

OUR PRICE £2.25 P. & P. 20p

EA.41 REVERBERATION AMPLIFIER



Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2 in x 3in x 4 1/2 in.
OUR PRICE £7.50 P. & P. 15p

OUR PRICE £7.50 P. & P. 15p

AUDIOTRONIC

ACD660 STEREO CASSETTE DECK

A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter, normal/chrome tape selector, twin VU meter, slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/DIN line input sockets, 3.5mm noise input sockets, etc. etc. Frequency response 100-8kHz (100-12kHz CrO2). S/N -45dB. Crosstalk -45dB. Separation -35dB. Noise limiter -6dB at 10kHz. Complete with phone connecting leads.
OUR PRICE £39.50 Carr. & Ins. 50p

OUR PRICE £39.50 Carr. & Ins. 50p

AHP8A 8 TRACK STEREO TAPE PLAYER

Incorporates built-in amplifiers giving 21 x 2W r.m.s. output. Push button track selector, illuminated track indicators, slider controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output impedance 8 ohms. 220/240V a.c.
OUR PRICE £17.25 Carr. & P. 50p, plus V.A.T.

OUR PRICE £17.25 Carr. & P. 50p, plus V.A.T.

AHP8D 8 TRACK STEREO TAPE DECK

Can be used with most hi-fi amplifiers. Push button track selector and illuminated track indicators. Attractive cabinet with black and silver trim. Output level 750mV. 220/240V a.c.
OUR PRICE £11.95 Carr. & P. 50p, plus V.A.T.

OUR PRICE £11.95 Carr. & P. 50p, plus V.A.T.

STEREO HEADPHONES

LSH20. Individual volume controls. Stereo mono switch. 8 ohms. 40-19,000Hz.
£3.50 P. & P. 30p

LSH30. Open back type. Individual tone and volume controls. 8 ohms. 30-20,000Hz.
£5.50 P. & P. 30p

LSH40. Two way speaker system. Individual volume controls. 8 ohms. 20-20,000Hz.
£6.95 P. & P. 30p

LSH60. 3in speaker units. 8 ohms. 20-20,000Hz. Complete with zippered carrying case.
£8.50 P. & P. 30p

LQH400. 4-channel dynamic headphones. Each earpiece has 4 drive units. 4-32 ohms. 20-20,000Hz.
£9.95 P. & P. 30p

LSH50. Electrostatic with self powered energiser and control unit with headphone/speaker selector. 4-32 ohms. 20-24,000 Hz.
£15.95 P. & P. 30p

RANGE OF HIGH QUALITY EQUIPMENT DOLBY 'B' NOISE REDUCTION UNITS



Reduce tape hiss by 30dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 16 1/2 in x 8 in x 3 1/2 in. a.c. 00/250V.
OUR PRICE £34.50 P. & P. 50p

PROCESS TWO

For use with cassette and tape recorders. Freq. res. 30Hz-20kHz. ±2dB. Off tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. S/N better than 70dB. Supplied with test cassette or tape as required.
OUR PRICE £34.50 P. & P. 50p

OUR PRICE £34.50 P. & P. 50p

PROCESS FOUR

For use with semi professional tape recorders. Freq. res. 30Hz-20kHz. ±2dB. S/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.
OUR PRICE £50.00 P. & P. 50p

OUR PRICE £50.00 P. & P. 50p

ACR14 BATTERY MAINS CASSETTE RECORDER

Portable twin track mono recorder with automatic recording level control. Built in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW. 220/240V a.c. or 6V d.c. operation. Complete with remote control microphone, mains lead, earpiece and batteries.
OUR PRICE £10.50 P. & P. 50p

AR1000 Sportsman AM/FM Portable

5 wavebands covering M: 535 - 1065kHz; F.M.: 88-108MHz; A.I.R.: 108 - 135MHz; P.B.: 147-174MHz; W.B.: 162.5MHz. Large horizontal slide dial with logging scale. Slider volume and squelch controls. 7 section telescopic aerial for F.M. and built in ferrite bar for A.M., A.F.C. 3in speaker. Earpiece socket. Green leatherette covered cabinet with metal side panels. Size 152 x 79 x 219mm. Battery/mains operation.
OUR PRICE £11.50 P. & P. 35p

AMB500 MULTI BAND RADIO

5 wavebands covering MW 535-1605kHz and F.M. 88-174MHz. All transistor. Battery or mains operation. Built-in aerial and 8 section telescopic aerial. Complete with batteries, shoulder strap and earpiece.
OUR PRICE £6.95 P. & P. 35p

AMR-9000 GLOBAL AM/FM PORTABLE

10 wavebands covering A.M.: 535-1605kHz; L.W.: 150-380kHz; M.B.: 1.6-4.0MHz; S.W.1: 4.0-8.0MHz; S.W.2: 8.0-16.0MHz; S.W.3: 16.0-24.0MHz; P.S.B.1: 30-50MHz; P.S.B.2: 148-174MHz; F.M.: 88-108MHz; A.I.R.: 108-136MHz. Features time zone map and timing dial. Large clear scale. Telescopic aerial and built-in aerial. A.F.C. on P.M. 6in x 4in speaker and personal earpiece. Battery/mains operation. Size 345 x 133 x 305mm.
OUR PRICE £36.00 P. & P. 50p

SAVE UP TO 33 1/3% OR MORE! GWS

RECORD DECK PACKAGES



Carriage and Packing 75p

Complete units with Stereo cartridge ready wired in plinth and cover.

GARRARD	
2025 T/C/TAHCD	£10-85
SP25 111/G800	£15-00
SP25 111/M44E	£18-45
SP25 111/M44-7	£16-10
SP25 111/M55E	£16-90
SP25 111 Module/M75-6	£19-45
AP76/G800	£23-50
AP76/G800E	£25-95
AP76/M44E	£24-95
AP76/M55E	£25-65
AP76/M75ED	£31-70
AP76/M75EJ	£27-85
AP76 Module M75-6	£29-10
AP96 Module M75-6	£33-20
ZERO 1008 Module/M93E	£44-15

B.S.R. McDONALD	
TD100/G800	£7-40
MEP60/G800	£15-00
MP60/TPD1/G800	£15-80
MP60/M44-7	£16-60
HT70/TPD1/G800	£19-20

GOLDRING	
GL72/G800	£31-50
GL75/G800	£38-85
GL75/G800E	£39-15

GOODMANS	
TD100/G800 Teak	£40-85
TD100/G800 White	£48-80

LEAK	
Delta/M75-6	£43-95

PHILIPS	
GA105/GP200	£13-80
GA160/GP200 Teak	£19-50
GA212/GP400	£45-25
GA308 (less cartridge)	£23-85
GA308 P.U.	£32-75

PIONEER	
PL12D (Less cartridge)	£31-75
PL15D (Less cartridge)	£44-25
PL41D (Less cartridge)	£104-75
PL50 (Less cartridge)	£98-90
PL61 (Less cartridge)	£110-30
PLA35 (Less cartridge)	£61-85

THORENS	
TD160/Ortofon M15E Super	£66-95
TD125 AB/11/Ortofon M15E	£104-95
TD165/Ortofon M15E Super	£59-60

WEARFEDALE	
Linton/M44-7 Teak	£23-70
Linton/M44-7 White	£23-90

SINCLAIR PROJECT 60 PACKAGE DEALS




2 x Z30/Stereo 60/PZ5	£15-95. P. & P. 37p.
2 x Z30/Stereo 60/PZ6	£18-00. P. & P. 37p.
2 x Z50/Stereo 60/PZ8	£20-25. P. & P. 37p.
Transformer for PZ8	£3 extra.

Active Filter Unit	£4-45.
Project 60 FM Tuner	£14-95.
Pair of Q16 Speakers	£10-70.
Sinclair Project 605	£20-97. P. & P. 37p.

All Sinclair Products in stock:
 2000 Stereo Amplifier, £29-95;
 3000 Stereo Amplifier, £28-95;
 2000/3000 Stereo Tuner, £26-30;
 Q830 Speakers, £29-98 pair, P. & P. 50p extra on above items.

SUPER AKAI HI-FI BARGAINS

CS35 STEREO CASSETTE RECORDER

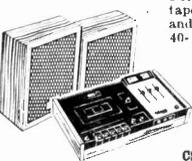

For conventional or Chromium Dioxide tape. 4 track record/playback. Volume and tone controls. Frequency response 40-16kHz (using CrO2 tape), distortion better than 2%, wow and flutter better than 0.2% RMS. Complete with pair of matching AKAI CS88 speakers. Rec. Price £96.10. **OUR PRICE £56-50** P. & P. 50p

CASSETTE, P. & P. 50p.	
GXC40D Deck	£57-20
GXC40 Recorder	£67-20
GXC40T Deck/Receiver	£99-05
GXC45 Deck	£78-25
GXC46D Dolby Deck	£55-55
GXC46 Recorder	£59-95
GXC80D Deck	£87-65
GXC85D Dolby Deck	£92-65

CARTRIDGE (P. & P. 50p)	
CR81 Deck with amps.	£65-40
CR81D Deck	£53-60
CR81T Recorder/Receiver	£92-75
CR8088 4 channel Recorder	£114-25
CR8088S 4 channel Recorder	£93-65

TAPE (P. & P. 75p)	
4000DS Deck	£59-95
4000DS Dust Cover	£3-95
172L Recorder	£80-85
X5000 Recorder	£82-50
X20 111 Deck	£105-20
GX220D Deck	£123-55
GX221D	£138-40
GX280D Deck	£198-50
GX370 Deck	£211-50

TAPE CASSETTE (P. & P. 75p)	
GX1900D Deck	£144-50

RECORD DECKS



Carriage & Packing 50p	
B.S.R. McDONALD	
C114 Mini	£3-85
C129 Mono	£5-50
C137	£7-90
510/TPD1	£13-95
610	£10-55
610/TPD1	£15-45
710	£21-15
810	£28-30
MP60	£25-25
MP60/G800	£10-90
MP60/TPD1	£13-20
MP60/TPD2	£11-25
HT70	£11-60
HT70/G800	£14-25
HT70/TPD1	£16-65

CONNOISSEUR	
BD1 Kit	£9-10
BD1 Chassis	£11-35
BD1/SAU2/Plinth/Cover	£27-60
BD2/SAU2/Chassis	£22-70
BD2/SAU2/Plinth/Cover	£28-20

GARRARD	
2025 T/C Stereo	£6-85
SP25 111	£9-25
SP25 111/Acos GP104	£8-50
SP25 111/G800	£10-95
SP25/M75-6	£13-90
AP76	£18-00
SL65B	£11-15
SL72B	£17-75
SL95B	£21-15
4015	£24-97
ZERO 100	£34-10
ZERO 1008	£31-40

GOLDRING	
G199	£18-99
G101P/C	£18-99
G169/2	£15-75
G172	£20-97
G175/P	£27-80
G175	£26-60
GL75P	£24-40
GL78 P/C	£48-55
GL85/P/C	£59-55

THORENS	
TD125/11	£56-60
TD125 AB/11	£55-65
TD165C	£48-40
TD165	£41-70

HOMER INTERCOMS



Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.

2 Station £2-97. P. & P. 15p.
 3 Station £5-25. P. & P. 15p.
 4 Station £6-82. P. & P. 17p.

SH628 STEREO HEADPHONES



Outstanding value. Soft earpads, adjustable headband. 8-16 ohms. 20,000 Hz. Complete with lead and stereo plug.

OUR PRICE £1-87 P. & P. 30p

TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (i.e. 600 ohms). Frequency response 200-4,000 Hz.

OUR PRICE £2-25 P. & P. 30p

LHO2S STEREO HEADPHONES



Lightweight headphones with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6 ft cord and plug.

OUR PRICE £1-95 P. & P. 30p


BH001 HEADSET AND BOOM MICROPHONE



Moving coil. Headphone imp. 16 ohms. Mike imp. 200 ohms. Ideal for language teaching, communications.

etc. Complete with leads and plugs. **OUR PRICE £4-95** P. & P. 30p


FM TUNER CHASSIS

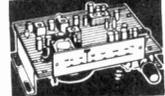

8 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in x 4in x 2 1/2in 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108MHz. Ready built ready for use.

OUR PRICE £5-95 P. & P. 20p
 Stereo Multiplex Adaptor £4-97.

SPECIAL PURCHASE!

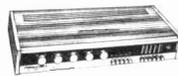

3408 STEREO TUNER AMP. Covers FM 88-108 MHz. Five push button tuning scales. 8+8 watts rms. Inputs for stereo ceramic cartridge and tape, etc. Separate bass, treble, balance and volume controls.

OUR PRICE £31-50 Carr. 50p

3416 STEREO TAPE DECK



4 track. 7 1/2, 3 1/2 i.p.s. Stereo/mono record/play. 7in reels. Inputs for dynamic mikes, radio, gram. Complete with cover.

OUR PRICE £41-95 Carr. 75p

VAT

All prices are subject to

10% VAT

(10p in the £)

Order with confidence by post - but remember to add 10% VAT (10p in the £) to total value of goods including carriage/packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY.

SEND LARGE S.A.E. FOR FULL HI-FI DISCOUNT LIST

G.W.SMITH & CO(RADIO)LTD

ALL MAIL ORDERS TO
 UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ
 TELEPHONE 01-205 3735

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

CENTRAL LONDON			
257/8, Tottenham Court Rd, W.1.	Tel: 01-580 0670	311, Edgware Road, W.2.	Tel: 01-262 0387
10, Tottenham Court Rd, W.1.	Tel: 01-637 2232	382, Edgware Road, W.2.	Tel: 01-723 4194
27, Tottenham Court Rd, W.1.	Tel: 01-636 3715	152/3, Fleet Street, E.C.4.	Tel: 01-353 2833
87, Tottenham Court Rd, W.1.	Tel: 01-580 3739	378, Harrow Road, W.9.	Tel: 01-286 9530
21, Old Compton Street, W.1.	Tel: 01-437 9369	ESSEX	
3, Lisie Street, W.C.2.	Tel: 01-437 8204	98, South Street, Romford.	Tel: Romford 20218
118, Edgware Road, W.2.	Tel: 01-437 9155	SURREY	
193, Edgware Road, W.2.	Tel: 01-723 9789	1046, Whitgift Centre, Croydon.	Tel: 01-681 3027
	Tel: 01-723 6211	27 & 21, Eden Street, Kingston.	Tel: 01-546 7845
		32, Hill Street, Richmond.	Tel: 01-948 1441

ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY



CREDIT TERMS FOR CALLERS (£50 and over)

ALL EQUIPMENT IS BRAND NEW, FULLY GUARANTEED AND OFFERED WITH FULL AFTER SALES SERVICE

All items and prices are correct at 20-7-73 but subject to change without notice. E & O. E.



TRANSISTORS


1 DOCKYARD, STATION ROAD, OLD HARLOW, ESSEX
Phone Harlow 37739

P/P 10p. Price list S.A.E. (Saturday callers welcome)

ALL PRICES INCLUDE VAT

£19.50 ELECTRONIC DIGITAL CLOCK

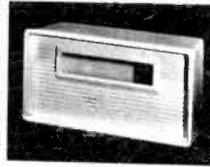(For complete kit of parts including case.)



This 4 digit 24 hour clock is available to readers at this special price for 1 month only. Parts would normally cost over £25. Kit of parts includes twelve IC's, indicators, and a smart white plastic case.

74 Series TTL

1		25		1		25		1		25	
SN7400	1p	15p	SN7423	55p	50p	SN7450	18p	15p	SN7489	6-05p	5-85p
SN7401	18p	15p	SN7425	55p	50p	SN7451	18p	15p	SN7490	74p	72p
SN7402	16p	15p	SN7427	49p	46p	SN7453	18p	15p	SN7491	1-10p	1-04p
SN7403	16p	15p	SN7428	77p	72p	SN7454	16p	15p	SN7492	74p	72p
SN7404	16p	15p	SN7430	18p	15p	SN7460	16p	15p	SN7493	74p	72p
SN7405	16p	15p	SN7432	49p	46p	SN7470	33p	29p	SN7494	85p	72p
SN7406	38p	35p	SN7433	94p	82p	SN7472	41p	39p	SN7495	85p	72p
SN7407	38p	35p	SN7437	72p	69p	SN7473	41p	39p	SN7496	95p	92p
SN7408	20p	18p	SN7438	72p	69p	SN7474	41p	38p	SN74100	1-80p	1-75p
SN7409	20p	18p	SN7440	18p	15p	SN7475	50p	47p	SN74104	1-09p	1-06p
SN7410	17p	15p	SN7441	74p	70p	SN7476	44p	43p	SN74105	1-09p	1-06p
SN7411	27p	25p	SN7442	74p	70p	SN7480	78p	70p	SN74107	44p	42p
SN7412	38p	35p	SN7443	1-43p	1-37p	SN7481	1-32p	1-29p	SN74110	81p	89p
SN7413	32p	29p	SN7444	1-43p	1-37p	SN7482	97p	95p	SN74111	1-37p	1-27p
SN7416	47p	43p	SN7445	2-00p	1-92p	SN7403	1-20p	1-15p	SN74118	1-10p	1-05p
SN7417	47p	43p	SN7446	1-07p	1-02p	SN7484	1-10p	1-05p	SN74119	1-47p	1-37p
SN7420	16p	15p	SN7447	1-10p	1-03p	SN7485	3-96p	3-85p	SN74121	44p	41p
SN7422	55p	50p	SN7448	1-10p	1-03p	SN7486	36p	35p	SN74122	1-54p	1-43p

* Devices may be mixed to qualify for Price Breaks
* 100 Plus less 10% off 25 plus break

Linear Integrated Circuits

301 DIL	50p	723c DIL	99p
301 TO99	55p	723c TO99	95p
301 8 PIN DIL	48p	741c 8 PIN DIL	38p
301A DIL	68p	741c 14 PIN DIL	39p
301A TO99	69p	741c TO99	41p
301A 8 PIN DIL	66p	747c DIL	46p
307 DIL	69p	748c DIL	39p
307 TO99	69p	748c TO99	41p
307 8 PIN DIL	66p	748c TO99	41p
308 TO99	6-55p	1437 DIL	1-27p
308A TO99	6-40p	1458 TO99	1-27p
709c DIL	35p	3046 DIL	84p
709c TO99	31p	7503 DIL	1-27p



Electrolytic Capacitors

4 VOLT		16 VOLT		40 VOLT	
47µF	6½p	15µF	6½p	47µF	6½p
100µF	6½p	33µF	6½p	100µF	9p
220µF	6½p	68µF	6½p	150µF	10p
330µF	6½p	150µF	6½p	220µF	11p
1000µF	13p	220µF	6½p	470µF	19p
4700µF	29p	680µF	9p	680µF	25p
		1000µF	17p	1000µF	25p
		1500µF	25p	2200µF	44p
		2000µF	43p		
6.3 VOLT		25 VOLT		63 VOLT	
33µF	6½p	10µF	6½p	1µF	6½p
68µF	6½p	22µF	6½p	2.2µF	6½p
150µF	6½p	47µF	6½p	4.7µF	6½p
470µF	11p	100µF	8p	6.8µF	6½p
680µF	13p	220µF	10p	10µF	6½p
1500µF	18p	470µF	13p	22µF	6½p
2200µF	18p	680µF	20p	68µF	10p
3300µF	26p	1000µF	22p	100µF	11p
		2000µF	39p	150µF	13p
		5000µF	68p	220µF	19p
				470µF	19p
				1000µF	22p
				1500µF	26p
				2200µF	44p

BARGAIN PACKS

Unmarked Packs
Pack of 25 IN4148 55p

Pack of 10 BC108 (unmarked) 55p
BC107 (Plastic can) 55p

Pack of 10 Plastic BC109 55p

Pack of 10 BC169 (unmarked) but tested 55p

2N2846 (unmarked) 33p each

Pack of 10 2N2906G 55p
unbranded but tested

Unmarked but fully tested 2N3055 33p
1-9 plus 27p

FULLY MARKED TYPES

AD161, AD162 M/P 59p
1-9 plus 53p

BC107-BC108 BC109 9p
1-9 plus 8p
100 plus 6½p

BC 182L ·3·4·212·4 9p
1-9 plus 8p

AC127 or AC128 1-9 plus 18p
100 plus 11p

ZENER DIODES

400 MW/5% Miniature BZY 88 Range 8p each

1 watt 5% All voltages 6.8 - 200 Volts 14p each

10 watt 5% All Voltages 7.5 - 100 Volts 51p each

Transistors

AC107 16p	BC138 38p	BF260 29p	OC44 14p	Diodes & Rectifiers
AC126 14p	BC142 38p	BF329 18p	OC46 14p	
AC127 13p	BC143 33p	BF330 18p	OC70 23p	
AC128 13p	BC144 30p	BF390 37p	OC71 14p	IN914 8p
AC142K 22p	BC145 26p	BFX84 28p	OC72 14p	IN916 8p
AC141K 20p	BC147 9p	BFX85 14p	OC81 14p	IN4148 8p
AC176 15p	BC148 9p	BFX86 22p	OC82 14p	2N184 10p
AC187 13p	BC149 9p	BFX87 28p	OC84 28p	IN4007 22p
AC187K 20p	BC153 16p	BFX88 28p	TIP29A 53p	IN113 17p
AC188 13p	BC154 17p	BFY50 21p	TIP30A 64p	IN120 17p
AC188K 20p	BC157 18p	BFY51 17p	TIP31A 84p	IN121 16p
ACY17 24p	BC158 15p	BFY52 17p	TIP32A 78p	IN130 9p
ACY18 21p	BC159 14p	BFY84 89p	TIP33 1-55	IN131 11p
ACY19 25p	BC167 18p	BFY90 72p	TIP34A 18132 13p	IN132 13p
ACY20 22p	BC168 11p	BXS20 19p	TIP35A 18922 13p	IN133 13p
ACY21 23p	BC169 11p	C407 22p	TIP36A 18940 9p	IN134 13p
ACY22 18p	BC177 15p	C426 33p	TIP37 18940 9p	IN135 13p
ACY39 65p	BC179 15p	C428 31p	TIP38A 18940 9p	IN136 13p
AD140 40p	BC182L 9p	C450 17p	TIP41A 79p	IN137 13p
AD142 44p	BC183L 9p	MP8111 36p	TIP42A 91p	IN138 13p
AD143 39p	BC184L 9p	MP8112 42p	TIP43 13p	IN139 13p
AD149 38p	BC186 33p	MP8113 35p	TIP44 13p	IN140 13p
AD150 60p	BC121L 11p	MP8121 33p	TIP45 13p	IN141 13p
AD161 25p	BC190 11p	MP8122 44p	TIP46 13p	IN142 13p
AD162 28p	BC214L 11p	MP8123 50p	TIP47 13p	IN143 13p
AD M/W 50p	BC258 9p	NKT211 25p	TIP48 13p	IN144 13p
AF114 14p	BC259 9p	NKT212 28p	TIP49 13p	IN145 13p
AF115 14p	BC267 14p	NKT214 25p	TIP50 13p	IN146 13p
AF116 14p	BC268 15p	NKT217 55p	TIP51 13p	IN147 13p
AF117 14p	BC290 40p	NKT261 23p	TIP52 13p	IN148 13p
AF118 92p	BC301 32p	NKT271 20p	TIP53 13p	IN149 13p
AF124 27p	BC302 30p	NKT274 20p	TIP54 13p	IN150 13p
AF139 39p	BC303 50p	NKT275 25p	TIP55 13p	IN151 13p
AF239 41p	BC304 40p	NKT403 71p	TIP56 13p	IN152 13p
AL100 77p	BCY70 17p	NKT405 83p	TIP57 13p	IN153 13p
AL102 69p	BCY71 31p	NK7603F 86p	TIP58 13p	IN154 13p
AL103 55p	BCY72 17p	NKT613G 33p	TIP59 13p	IN155 13p
ASY26 31p	BD123 66p	NKT673G 33p	TIP60 13p	IN156 13p
ASY27 40p	BD130 50p	NKT677G 33p	TIP61 13p	IN157 13p
AU103 99p	BD131 88p	NKT677G 33p	TIP62 13p	IN158 13p
AU110 41-10	BD132 90p	NKT677G 33p	TIP63 13p	IN159 13p
AU111 77p	BD135 42p	NKT677G 33p	TIP64 13p	IN160 13p
BC107 9p	BD136 50p	NKT7132 32p	TIP65 13p	IN161 13p
BC108 9p	BD141 1-87	NKT7732 32p	TIP66 13p	IN162 13p
BC109 9p	BD142 50p	OC19 55p	TIP67 13p	IN163 13p
BC113 154p	BF159 33p	OC20 55p	TIP68 13p	IN164 13p
BC116 16p	BF173 29p	OC23 33p	TIP69 13p	IN165 13p
BC125 15p	BF177 25p	OC26 24p	TIP70 13p	IN166 13p
BC126 25p	BF178 29p	OC28 33p	TIP71 13p	IN167 13p
BC132 16p	BF179 35p	OC29 33p	TIP72 13p	IN168 13p
BC134 16p	BF194 15p	OC35 38p	TIP73 13p	IN169 13p
BC135 16p	BF195 17p	OC36 38p	TIP74 13p	IN170 13p
BC137 16p	BF244 27p	OC41 14p	TIP75 13p	IN171 13p

MULLARD POLYESTER'S

MULLARD POLYESTER CAPACITORS C280 SERIES
250V P.C. mounting: 0-01µF, 0-015µF, 0-22µF, 34p, 0-33µF, 0-47µF, 0-068µF, 4p, 0-1µF, 41p 0-15µF, 0-22µF, 54p, 0-33µF, 7p, 0-47µF, 81p, 0-68µF, 12p, 1-0µF, 14p, 1-5µF, 22p, 2-2µF, 87p

MULLARD POLYESTER CAPACITORS C296 SERIES
400V: 0-001µF, 0-0015µF, 0-0022µF, 0-0033µF, 0-0047µF, 21p, 0-0068µF, 0-01µF, 0-015µF, 0-22µF, 0-33µF, 31p, 0-47µF, 0-068µF, 0-1µF, 41p, 0-15µF, 61p, 0-22µF, 81p, 0-33µF, 11p, 0-47µF, 14p, 0-68µF, 12p, 1-0µF, 14p, 1-5µF, 22p, 2-2µF, 87p

VOLUME CONTROLS

Potentiometers
Carbon track 500 Ω to 2-2M Ω
Log or Linear
50 Single 13p, Dual gang (stereo) 44p
Single type with D.P. switch 18p extra.

SLIDE POTENTIOMETERS

55mm, TRACK
SINGLE GANGED, LOG or LIN 1k to 1M, 45p each
TWIN GANGED, LOG or LIN 1k to 500k, 66p each.

CARBON SKELETON PRESETS

Small high quality type (linear only).
All values 100-5 meg ohms.
-1 watt 51p each
-2.5 watt 81p each

VEROBORD

	0-15 Matrix	0-1 Matrix
24in x 34in	19p	26p
24in x 5in	28p	28p
34in x 34in	28p	28p
34in x 5in	33p	32p

5in x 17in (plain) 94p
Vero Pins (bag of 36) 22p
Vero cutter, 50p; Pin insertion Tools (0-1 and 0-15 matrix) at 81p.

SLIDE SWITCH

SPST 11p each, D.P.D.T. 13p each.

MINIATURE NEON LAMPS

240V or 110V 1-4 5p, 5 plus 44p each.

MINITRON DIGITAL INDICATOR TYPE 3015F

Reads 0-9 and decimals (Data Sheet on request)
ONLY £1.50
16 DIL Socket 33p
Driven by 7457 £1-05

RECTIFIERS

P.I.V.	1 AMP	1.5 AMP
50	IN4001 44p	PL4001 8p
100	IN4002 44p	PL4002 9p
200		

How to build an Electronic Sound Synthesizer for only £100

Don't let the amazingly low price fool you. This is the real thing.

By following our current constructional project you can put together an electronic sound synthesizer incorporating many of the facilities to be found in far more expensive designs. These include — in addition to filtering, mixing and reverberation — a waveform generator with variable exponential attack and delay. You can simulate the sounds of piano and harpsichord along with a wide range of instrumental and electronic sounds.

An Approach to Amplifier Design.

The second article in this important series analyses the relationship between negative feedback design and steady state forms of distortion. It also discusses transient phenomena as a major factor in design theory and looks at several designs in this context.

Wireless World

September issue 20p

CRESCENT RADIO LTD


11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT. No. 11 MAYES RD. LONDON N22 6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY) 13 SOUTH MALL, EDMONTON, N.9 803 1685

"CRESCENT" BUBBLE LIGHT SHOW

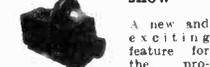

A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour makes the music you produce more interesting and will appeal to the visual as well as the audio senses. This budget system compares very favourably with the more sophisticated and much higher priced models.


Specification—Projector: 150W, convection cooled, at 30ft the projected image = 16ft; Motor: 1 rev per 2 min. Liquid Wheel: 6in diameter multicolour. The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use, £15; 6in Liquid Wheel, £5 = £20 + 75p carr.

TRI-VOLT BATTERY ELIMINATOR




Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2½in x 2½in x 3½in. Our Price £2.75 plus 10p P. & P. Same model suitably wired for the Philips Cassette £3 plus 10p P. & P.

DIGITAL CLOCK KIT

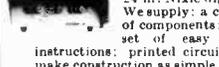

24-hr. Nixie dig. clock kit. We supply: a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. £22.50 + 50p P. & P. Please send S.A.E. if you require more information.

AL20 5 WATT AUDIO AMPLIFIER

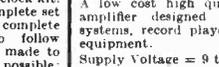

A low cost high quality 5 watt audio amplifier designed for use in stereo systems, record players and other audio equipment. Supply Voltage = 9 to 30 volts. Frequency = 50 to 25 kHz. Overall Size = 3in x 2½in x 1½in approx. Full technical data and diagrams with each module. All guaranteed and a bargain at £2.63 plus 5p P. & P.

200/250V MAINS RELAY



Heavy duty contacts, 2,500 Ω coil. All new and unused D.P.D.T. mains relays 50p + V.A.T. Carr. Free. Special quantity price: £40 per 100 relays.

A MAINS TRANSFORMER




Fused Primary 240V. Secondary 220V @ 50mA, 6.3V @ 1A. This transformer is made to a very high standard and is a small size: 2in x 2½in x 2½in. 63p plus 15p P. & P.

TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. x 3½in. x 1½in. This converter supplies 6, 7½ or 9 volts and is transistor regulated. A real money saving device for £2.50 plus 10p P. & P.


V.A.T. From 1st April, 1973, will you please include on your Total (Goods plus Postage and Packing) Value Added Tax at the Standard Stated Rate.

STEREO/MONO HEADPHONE VOLUME CONTROL BOX

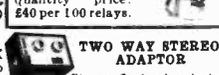

Plug stereo phones into this control box and you then incorporate a right and left hand volume control and a stereo/monoswitch. Complete with stereo jack plug and 2m cable. A bargain at £1. P. & P. 10p.

TWO WAY STEREO ADAPTOR

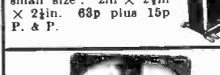


Stereo Jack plug to two stereo free sockets, complete with 110mm cable. For connecting two stereo inputs into one. A bargain at 65p. plus 5p P. & P.

MINI LOUSPEAKERS

2½in 80 ohm, 50p; 2½in 40 ohm, 50p. Please include 5p P. & P. on each L.S.



CRESCENT CASSETTES

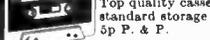


Top quality cassettes at unbeatable prices (complete with standard storage case): C50 25p, C90 38p, C120 48p plus 5p P. & P.

"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT



This fantastic little box approx. 4" x 3" x 2½" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at £7.50 plus 10p.

LOW VOLTAGE AMPLIFIER

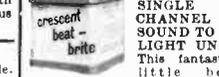


5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier. £1.75 plus 13p P. & P.

PSYCHEDELIC LIGHT CONTROL UNIT




Three Channel: Bass—Middle—Trebble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) £18.50 plus 38p P. & P.

EMI LOUSPEAKER 450

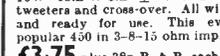

10W 13in x 8in ± two 2½in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp. £3.75 plus 38p P. & P. each.

7in x 4in LOUSPEAKER

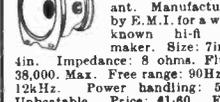

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1.60. Free postage on this item.

parts for PRACTICAL ELECTRONICS projects

After many requests, Electro Spares are now supplying lists of components for all the projects featured in "Practical Electronics", commencing with May 1973 issue. Just forward an S.A.E. (preferably 9" x 4" minimum), and state which project is of interest to you—we will forward an individually priced list of the components required.

No need to buy a full kit—you need only purchase the parts you require at any one time.

All Electro Spares supplied components are new, branded products of reputable manufacturers, and carry full makers' guarantee.

We regret we cannot supply lists for projects published before May 1973 issue.

"ONE SOURCE" BUYING MAKES SENSE—IT CAN SAVE YOU TIME, MONEY AND POSTAGE

"p.e." f.m. varicap stereo tuner

Electro Spares offer a kit of high quality parts to the published specification for this remarkable tuner, featured in "Practical Electronics", May 1973.

Features include pushbutton "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy, "no problem" construction, requiring only a few simple setting up adjustments with a D.C. Voltmeter. Uses **NEW** pre-set modules for R.F. and I.F. circuits—no circuit alignment. High efficiency integrated circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator.

Fibre Glass P.C. Board, neat slim line cabinet, with brushed aluminium front panel, push buttons, etc., etc.

IDEAL FOR USE WITH THE "TEXAN", "P.E. GEMINI" AND ANY GOOD QUALITY STEREO AMPLIFIER.

Please send S.A.E. for full details.

"p.e. gemini" stereo amplifier

QUALITY HI-FI FOR THE HOME CONSTRUCTOR

30 Watts (R.M.S.) per Channel into 8 ohms!
Total Harmonic Distortion 0.02%!
Frequency Response (-3 dB) 20Hz - 100kHz!

We are still continuing to supply components for this fabulous amplifier, which is now recognised as practically the ultimate in High Fidelity. We know of no better unit for the home constructor, and can supply a booklet, containing full specification, complete constructional information, wiring diagrams, fault finding guide, etc., etc., price 55p plus 4p postage.

Our **new, low** comprehensive price list is supplied with each booklet, or supplied separately on receipt of large S.A.E.

FOR PEOPLE WHO REQUIRE THE BEST—IT HAS TO BE THE "p.e. gemini"

NOTE OUR NEW ADDRESS—WITH NEW MAIL ORDER DEPARTMENT FOR QUICK EFFICIENT SERVICE.
PLEASE PAY US A CALL—VISITORS WELCOME—EASY PARKING.

Electro-Spares

288 Ecclesall Road

Sheffield S11 8PE

Tel.: Sheffield 668888

"THE COMPONENT CENTRE OF THE NORTH"

COMPARE OUR PRICES

Speaker Bargains	2p	ACOS GP91/28C or GP91/38C stereo compatible	90
E.M.I. 131n x 8in 3, 8 & 15 ohms		ACOS GP94 stereo ceramic	1.50
plain	2.00	ACOS GP95 stereo ceramic	1.15
with tweeter	2.25	ACOS GP96 stereo ceramic	1.50
twin tweeter	3.50	9THAC Sonotone stereo ceramic (diamond)	1.70
Type 350 -20 watt with tweeter 8 ohms. P.P. 37p.	7.25	9THAC/G Sonotone stereo ceramic (diamond) simline	1.70
8in x 5in 3, 8 & 15 ohms	1.10	ACOS GP97/2C mono crystal	1.15
6 1/2" (93850) 8 ohm	2.20	ACOS GP101 compatible crystal	65
8" (14/1000) 8 ohm 10 watt	4.00	19-TI Sonotone stereo crystal	80
EMI 31" Tweeter C/Magnet 8 ohm	1.00	Postage 5p per cartridge	
FANE 7in x 4in 3 & 8 ohms	90		
8in 8 ohm, dual cone	2.10		
CELESTION 8in 15 ohm	1.40		
BAKER GROUP 25 12in 25W 8 or 15 ohm	6.00		
Postage 25p per speaker			
5" 8 ohm c/magnet P.P. 10p	80		
2 1/2in 8 or 64 ohm P.P. 10p	45		
Kit-form cabinets, teak			
(17in x 10in x 6in)	2.95		
with a 13in x 8in or 8in cut out			
18in x 11in x 9in with 13in x 8in cut out for EMI 350	23.95		
(12in x 12in x 6in) with a 8in x 5in or 8in cut out	2.25		
(please specify cut out)			
Add 35p per cabinet for post & packing			
Microphone Bargains	2p		
CM 20 Crystal Hand	45		
DX143 Dynamic, cassette-type stick	1.00		
CM70 PLANET stick metal, switch crystal	1.45		
DM160 Dynamic uni-dir, ball metal	3.75		
UD130 50K/600 ohm uni-dir, ball metal	4.50		
TW209 Lesson dual imp ball metal uni-dir	5.75		
Condenser Mike uni-dir 600 ohm	7.95		
Guitar mike	45		
Lapel type, crystal	40		
Postage 17p each			
Cartridges— with standard fittings & styli	2p		

ACOS GP91/28C or GP91/38C stereo compatible 90
ACOS GP94 stereo ceramic 1.50
ACOS GP95 stereo ceramic 1.15
ACOS GP96 stereo ceramic 1.50
9THAC Sonotone stereo ceramic (diamond) 1.70
9THAC/G Sonotone stereo ceramic (diamond) simline 1.70
ACOS GP97/2C mono crystal 1.15
ACOS GP101 compatible crystal 65
19-TI Sonotone stereo crystal 80
Postage 5p per cartridge

Battery Eliminators
240v input 6 or 9v d.c. output at 160 mA 1.99
12v d.c. input (for cars, fits in lighter socket) 6, 7 1/2 or 9v d.c. output at 300 mA 2.50
P. & P. 10p

Tapes—"MYLAR" base finest quality British made.
5in 600ft 36p 5 1/2in 1800ft 85p
5in 900ft 45p 7in 1200ft 65p
5in 1200ft 60p 7in 1800ft 80p
5 1/2in 900ft 49p 7in 2400ft 95p
5 1/2in 1200ft 65p 7in 2400ft 95p
Postage 9p each

Plastic Library Cases for
5in Reels 18p 7in Reels 21p
5 1/2in Reels 19p P. & P. 5p each

THIS MONTH'S SPECIAL OFFER

EMI Loudspeaker Enclosure Kit (LEK 450/8). Comprising 2 EMI 450 Speakers (8 ohm 10 watt, T/Tweeter plus cross-over) and 2 EMI Cabinet Kits 18" x 10" x 11". Plus acoustic wadding, glue, screws, instructions, etc. Recom. Retail price £29.90. Bargain at £18.00 inc. VAT, plus 50p P. & P.

Add 10% V.A.T. on prices incl. P. & P.

RIVERSDALE ELECTRONICS

ALL OUR MERCHANDISE IS FULLY GUARANTEED

Mail Order Dept. E9/73,
P.O. Box 470,
Manchester M60 4BU
SEND 25p FOR
COMPLETE CATALOGUE

FIRST TIME EVER at £42.50.
Solatron CD71152 Double Beam Oscilloscope d.c.—9MHz; 3mV/cm; trigger delay; crystal calibrator; 4in flat faced tube. In good working condition. Carriage £1.50.

SOLARTRON CT 316 (D3000 range). DC to 6 mcs. 3" tube. TB up to 0.75 micro secs per centimetre. Built in calibrator. Size 8 1/2" x 11" x 20". Price £22.50. Carr. £1.25.

MARCONI VALVE VOLT-METER type TR 958(CT208) DC to 100 mcs. 5" mirror backed meter complete with probe, leads etc. £12.50. Carr. £1.25.

GRATICULES. 12cm x 14cm in High Quality plastic. 30p each. P. & P. 5p.

MODERN TELEPHONES type 706. Two tone grey, £3.75 each. The same but black, £2.75 each. P. & P. 25p each.

Also **TOPAZ YELLOW** £4.50 each. P. & P. 25p.

STANDARD GPO DIAL TELEPHONE (black) with internal bell, 87p each. P. & P. 50p. Two for £1.50. P. & P. 75p. All telephones complete with bell and dial.

20Hz to 200kHz WB SINE AND SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use. 9V supply required. £6.85 each. P. & P. 25p. (Not cased, not calibrated.)

WOBBLATOR. Sweeps 8 to 45MHz ready to use. 6.3V a.c. required. £9 each. P. & P. 25p. (Not cased, not calibrated.)

CAPACITOR PACK. 50 Brand new components only 50p. P. & P. 17p.

5 MOVING COIL METERS various. £2. P. & P. 37p.
POTS—10 different values. Brand new—50p. P. & P. 17p.

COMPONENT PACK consisting of 2.2 pole 2 amp push on/off switches; 4 pots, various, brand new; 250 resistors 1/2 and 1/4 watt, many high stabs, etc. Fine value at 50p per pack. P. & P. 17p.

P.C.B. PACKS S & D. Quantity 2 each —no tiny pieces. 50p plus P. & P. 20p.

FIBRE GLASS as above £1 plus P. & P. 20p.

5 CRYSTALS 70 to 90kHz. Our choice, 50p. P. & P. 15p.

Matched pairs, 50p per pair. P. & P. 15p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot. P. & P. 10p.

ELECTRONIC TIMER UNITS—wall or bench mounting—2 Hybrid timer boards may be removed leaving excellent 12V battery charger; d.c. Power supply, etc. Price only £2.50 incl. carriage.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New 38p each. Holder 1p each. Information 5p.

PHOTOCCELL equ. OCP71, 13p each.

PHOTO-RESIST type Clare 703. Two for 50p.

AMERICAN OSCILLOSCOPE type USM24. A 10 meg scope—all min. valves complete with circuit diagram. Mains input 115 volt 50 cycles therefore £20. With step-down transformer £21.50. Carr. £1.50.

MOTOR MIN. SYNCHRONOUS. Size 1 1/2" x 2" x 1". 240V operation, 3.6 RPM, 25p each. P. & P. 5p.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.

PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 7.30 p.m. ANY DAY

CHILTMead LTD

79 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel.: Reading 582605/65916

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

OPEN ALL DAY SATURDAYS
ALL PRICES SUBJECT TO V.A.T.

RESISTORS

±W Iskra high stability carbon film—very low noise—capless construction.
±W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm.
±W 25W ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price
1/4	5%	4.7Ω-2.2MΩ	E24	1p 0.8p
1/2	10%	3.3MΩ-10MΩ	E12	1p 0.8p
1	2%	10Ω-1MΩ	E24	3.5p 3p
2	10%	1Ω-3.9Ω	E12	1p 0.8p
5	5%	4.7Ω-1MΩ	E12	1p 0.8p
10	10%	1Ω-10Ω	E12	6p 5.5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ±W, lin ±W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0-1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 6p each.

TRANSISTORS

AC107 15p	AF125 20p	BD132 75p	OC28 50p	2N3702 13p
AC126 12p	AF126 20p	BD133 75p	OC35 50p	2N3703 12p
AC127 12p	AF127 20p	BF115 25p	OC42 12p	2N3704 12p
AC128 12p	AF139 32p	BF173 20p	OC44 12p	2N3705 12p
AC131 12p	AF178 32p	BF177 28p	OC45 12p	2N3706 11p
AC132 12p	AF180 40p	BF178 32p	OC70 12p	2N3707 12p
AC176 12p	AF181 40p	BF179 32p	OC71 12p	2N3708 10p
AC187 22p	BC107 9p	BF180 32p	OC72 12p	2N3709 11p
AC188 22p	BC108 9p	BF181 32p	OC81 12p	2N3710 11p
AD140 50p	BC109 9p	BF194 15p	OC82D 12p	2N3711 11p
AD149 35p	BC147 13p	BF195 15p	2N2904 20p	2N3711 11p
AD161 33p	BC148 13p	BF197 15p	2N2926G 9p	40360 35p
AD162 36p	BC149 13p	BF200 32p	2N2926Y 9p	40361 35p
AF114 20p	BC157 14p	BFY50 20p	2N2926G 9p	40362 40p
AF115 20p	BC158 14p	BFY51 20p	2N2926G 9p	40408 40p
AF116 20p	BC159 14p	BFY52 20p	2N3054 58p	ZTX302 15p
AF117 20p	BC187 22p	BU105 22.5p	2N3055 60p	ZTX502 20p
AF124 22p	BD131 75p	OC26 45p		

ZENER DIODES

400mW 5% 3.3V to 30V, 12p.

WIRE WOUND POTS, 3W, 10, 25, 50Ω and decades to 100kΩ, 35p.

DIODES

RECTIFIER

BY127 1250V	1A	12p
BZ100 800V	6A	25p
BZ113 200V	6A	20p
IN4001 50V	1A	7p
IN4004 400V	1A	8p
IN4007 1000V	1A	10p

SIGNAL

OA85	7p
OA90	5p
OA91	5p
OA202	7p
IN4148	8p
BA114	8p

BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2 1/2in = 10p; 9in x 2in = 7p

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.
SINGLE 10K, 25K, 100K, log or lin. 40p.
DUAL GANG, 10K + 10K etc. log or lin. 60p.
KNOB FOR ABOVE 12p.
FRONT PANEL 65p.
18 Gauge panel 12in x 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

THERMISTORS

VA10555	15p
VA10665	15p
VA1077	15p
R53	£1.35

THYRISTORS

2N5060 50V 0.8A	30p
2N5064 200V 0.8A	47p
CR51/40 400V 1A	25p
106F 50V 4A	40p
400V 4A	55p

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 21p. 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p. 0.047μF, 0.068μF, 0.1μF, 4p. 0.15μF, 6p. 0.22μF, 7.5p. 0.33μF, 11p. 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF 3.5p, 0.15μF 4.5p. 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 7.5p. 0.68μF, 11p. 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p. 0.033μF, 0.047μF, 0.068μF, 3.5p. 0.1μF, 4p. 0.15μF, 0.22μF, 5p. 0.33μF, 6.5p. 0.47μF, 8.5p. 0.68μF, 11p. 1.0μF, 13p. 1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 21p. 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3.5p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD O15/6/7 RANGE REPLACES C426, C457 RANGES

(μF/V) 1/0/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6.3, 33/40, 47/4, 47/10, 47/25, 47/40, 47/63, 68/6.3, 68/16, 100/4, 100/10, 100/25, 100/40, 150/6.3, 150/16, 150/25, 220/4, 220/10, 220/16, 330/4, 330/10, 470/6.3, 5p each. 68/63, 150/40, 220/25, 330/16, 470/10, 680/6.3, 1,000/4, 9p. 100/63, 150/63, 220/40, 470/25, 680/16, 1,000/10, 1,500/6.3, 12p. 220/63, 470/40, 680/25, 1,000/16, 1,500/10, 2,200/6.3, 15p. 330/63, 680/40, 1,000/25, 1,500/16, 2,200/10, 3,300/6.3, 4,700/4, 18p.

SOLID TANTALUM BEAD CAPACITORS

0.1μF 35V	2.2μF 35V	22μF 16V
0.22μF 35V	4.7μF 35V	33μF 10V
0.47μF 35V	6.8μF 25V	47μF 6.3V
1.0μF 35V	10μF 25V	100μF 3V

VEROBOARD

0-1	0-15
2 1/2 x 3 1/2	22p
2 1/2 x 5	16p
3 1/2 x 3 1/2	24p
3 1/2 x 5	24p
17 x 2 1/2	27p
17 x 3 1/2	75p
17 x 5	78p
17 x 5 (plain)	82p
17 x 3 1/2 (plain)	60p
17 x 2 1/2 (plain)	42p
2 1/2 x 5 (plain)	11p
2 1/2 x 3 1/2 (plain)	12p
Pin insertion tool	52p
Spot face cutter	42p
Pkt. 50 pins	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	13p
Stereo screened	35p	3.5mm screened	8p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p. Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable 22p/metre.

BATTERY ELIMINATOR

£1 50
9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600μF 64V	74p	2500μF 64V	80p	4500μF 16V	50p
2500μF 40V	74p	3200μF 100V	£2.60	4500μF 25V	£1.68
2500μF 50V	58p	3200μF 50V	58p	5000μF 50V	£1.10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF	10p	0.1μF	13p	0.22μF	20p
0.022μF	12p	0.47μF	13p	0.47μF	22p

POLYSTYRENE CAPACITORS 160V 2 1/2% 10pF to 1,000pF E12 Series Values 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs oxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but excluding gas, £2. Mains operated detector £5.20. 12 or 24V battery operated audible alarm £7.30. As above for PP9 battery, £6.40.

PRINTED BOARD MARKER

97p
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

LARGE RANGE ITT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

7400	1-11	12-24	25-99	100+	7448	185	175	170	165	7418	100	82	73	64
7401	p	p	p	p	7450	18	16	14	13	74121	43	40	38	36
7402	18	16	14	13	7451	18	16	14	13	74141	100	95	90	85
7403	18	16	14	13	7453	18	16	14	13	74145	150	140	135	130
7404	20	18	16	14	7470	30	28	25	24	74150	330	280	250	220
7405	20	18	16	14	7472	30	28	27	26	74151	110	100	95	89
7406	50	45	40	35	7473	40	38	36	35	74152	120	110	105	95
7407	56	50	44	38	7474	40	37	36	32	74154	200	180	170	160
7408	36	30	27	23	7475	55	52	50	49	74155	150	120	100	86
7409	36	30	27	23	7476	40	36	32	30	74156	130	120	100	96
7410	18	16	14	13	7480	100	95	90	85	74180	155	136	112	105
7411	23	21	20	18	7481	125	115	110	105	74190	195	190	185	180
7412	36	30	27	23	7482	100	96	90	85	74191	195	190	185	180
7413	34	28	26	22	7483	100	97	95	92	74192	200	190	180	164
7416	45	43	39	34	7484	120	115	110	105	74193	200	180	170	150
7420	18	16	14	13	7485	250	245	240	230	74196	200	190	180	170
7421	36	30	27	23	7486	45	42	37	33	74197	200	195	180	170
7426	32	29	23	20	7490	75	67	60	52					
7430	20	18	16	14	7491A	100	92	87	79					
7432	40	36	32	28	7492	75	70	65	60	709	14 pin DIL			32p
7440	20	18	16	14	7493	75	68	60	52	741	8 pin DIL			34p
7441	80	75	70	65	7494	95	90	85	80	741	14 pin DIL			28p
7442	80	75	70	65	7495	105	100	95	90	723	14 pin DIL			35p
7443	125	120	115	115	7496	100	90	80	85	747	14 pin DIL			85p
7447	175	165	150	120	74100	250	240	235	230	748	8 pin DIL			35p

LINEAR IC's

709	14 pin DIL	32p
741	8 pin DIL	34p
741	14 pin DIL	

CBS SQ*

FOUR CHANNEL DECODER

As specified in the

P.E. RONDO

COMPLETE QUADRAPHONIC HI-FI SYSTEM

*REGD. CBS INC

- COMPLETE KIT OF HIGH GRADE SPECIFIED PARTS
- FIBREGLASS BOARD—COMPONENT POSITIONS MARKED
- COMPREHENSIVE INSTRUCTIONS ENABLE CONSTRUCTION TO BE COMPLETED IN LESS THAN ONE HOUR
- ONLY A SOLDERING IRON AND A PAIR OF CUTTERS REQUIRED
- DESPATCH GUARANTEED WITHIN 72 HOURS

ONLY £8.80

Including Postage, VAT and CBS licence fee

SPECIAL ANNOUNCEMENT

A COMPLETE KIT OF PARTS FOR EACH STAGE OF THE **P.E. RONDO** WILL BE AVAILABLE AS IT APPEARS IN THIS MAGAZINE

STUDIO ELECTRONICS

P.O. BOX No. 18, HARLOW, ESSEX CM18 6SH
Telephone: Harlow 25457

PLEASE SUPPLY ONE P.E. RONDO CBS SQ DECODER KIT
I ENCLOSE £8 80

NAME _____

ADDRESS _____

P.E.9

SINGLE CHANNEL SOUND-TO-LIGHT CONVERTER



WITH LIGHT DIMMER
Max. Load 2kW at 250V a.c.

Price includes ready built and tested module, edge connector/mounting bracket, dimmer potentiometer, audio sensitivity potentiometer, full connecting data. Price £7.90 inc. VAT + 25p P. & P.


EXTRA FACILITIES. Push-button for Manual Pulsing, 25p extra. Photocell for turning on the lights as the ambient light decreases, 75p extra.

THREE CHANNEL FILTER UNIT

When used with three single channel modules this unit filters the sound into bass, middle and top frequencies enabling three coloured light displays to be shown. Independent sensitivity controls on each channel. Ready built and tested.

Price £8.40 inc. VAT + 15p P. & P.

OIL WHEEL PROJECTOR

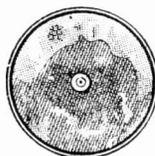

Build your own using our **MULTI-COLOURED OIL WHEEL AND MOTOR KIT**
Suitable for mounting on virtually all Slide Projectors.

Kit contains:

★ 6in dia. or 4in dia. OIL WHEEL (please state size required when ordering).

★ Suitable Miniature mains motor.

★ Full instructions.

For Professional Discotheque use or home enjoyment. Price £7.15 inc. VAT & P. & P.

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

- Pack No.
- 500 Carbon resistors, 1, 1, 1, 2W.
 - 100 Electrolytic Condensers.
 - 250 Ceramic, Polystyrene, Silver Mica, etc. Condensers.
 - 250 Polyester, Polycarbonate, Paper, etc. Condensers.
 - 25 Potentiometers, assorted.
 - 250 High-stab. 1%, 2%, 3% resistors.
 - 50 Assorted Tagstrips.
 - 1lb wt. Assorted Nuts, bolts, washers, spacers, etc.
 - 25 Assorted switches, rotary, lever, micro, toggle, etc.
 - 50 Preset Potentiometers.

ALL COMPONENTS NEW AND UNUSED
£1 + 25p P. & P. per pack 25 for 5 packs post free.

G.T. ELECTRONICS

267 Acton Lane, London W4 5DG
01-994 6275

If you have difficulty in obtaining

PRACTICAL ELECTRONICS

Please place a regular order with your newsgent or send 1 year's subscription (£2.65) to Subscription Department, Practical Electronics, Tower House, Southampton Street, London WC2E 8QX

SINCLAIR EQUIPMENT



Project 60 FM Tuner	£15	(£1.70)
2 Z30/Stereo 60/PZ8	£18.75	(£2.05)
2 Z30/Stereo 60/PZ6	£18.85	(£2.25)
2 Z50/Stereo 60/PZ8/Trans	£23.20	(£2.70)
Z30 £3.50 (55p) Stereo 60	£7.80	(98p)
Z50 £4.30 (63p) Trans for PZ8	£2.95	(50p)
PZ5 £3.87 (59p) 2000 Amp	£24.50	(£2.65)
PZ6 £6.30 (83p) 3000 Amp	£31.50	(£3.35)
AFU £4.50 (65p) 2000 Tuner	£27	(£2.90)
PZ8 £6.40 (84p) 3000 Tuner	£27	(£2.90)
Q16 £5.90 (79p) Project 605	£20.98	(£2.40)

PROJECT 60 KIT £2.50 (36p)
Our extremely popular kit contains the extra capacitors, din plugs and sockets, cable and fuseholder needed to complete Project 60.

IC RADIO CHIP TBA651 £2.10 (32p)
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2.10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1.75 (29p).


S-DECS AND T-DECS

S-DECS £1.44 (25p)


T-DECS £2.88 (39p)

µ-DEC A £3 (41p)

16 dif IC carriers £1.20 (17p)

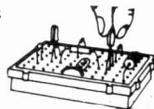

SINCLAIR SUPER IC12

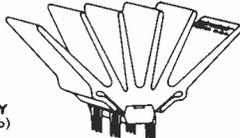

ONLY £2 (31p)

Max. supply volts 28. Power 6 Watts rms. Complete with free printed circuit board and 44-page instruction book.

SWANLEY IC TOMORROW £2.50 (36p)

The World's most powerful IC amplifier. Similar to the above but operates at 35 volts max, supply and gives 12 Watts rms output. Manufactured for us by a leading semiconductor company. Supplied with our instructions and a 6-month guarantee, but no printed circuit.

KITS FOR IC12 AND IC TOMORROW

Except for the power kits and speakers, all items suit both integrated circuits.

DELUXE KIT

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.45 (25p). Stereo model with balance control £3.30 (44p).

IC12 POWER KIT

A set of components to construct a 28V 0.5A power supply £2.27 (45p).

IC TOMORROW POWER KIT

A set of components to construct a 35V 1A power supply £2.97 (52p).

LOUDSPEAKERS FOR THE IC12

5in 8ohm £1 (21p). 5in x 8in 8ohm £1.45 (26p). 10in x 6in 15ohm £2.20 (44p).

PREAMPLIFIER KITS

Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1.30 (24p). Stereo model £2.30 (34p). Type 2 for ceramic or crystal pickups. Mono 60p (17p). Stereo £1.20 (23p).

SEND S.A.E. FOR FREE LEAFLET ON KITS

SINCLAIR EXECUTIVE CALCULATOR



Now only £45 (£4.70)

SWANLEY ELECTRONICS

32 Goldsel Road, Swanley, Kent

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from schools, etc., welcome. Send S.A.E. for free leaflet on kits, IC Tomorrow and TBA651. Mail order only. No callers, please.

BRITAIN'S FASTEST SERVICE!



A SELECTION FROM OUR COMPREHENSIVE CATALOGUE

ALL ITEMS ARE BRAND NEW AND FULLY GUARANTEED

AA119	50p	BCY72	15p	CA3018A	£1.19	NKT406	62p	1N4002	7p	2N5777	45p
AC107	8p	BD124	75p	CA3020	£1.55	NKT713	25p	1N4003	20p	2N6027 (D13T1)	45p
AC126	25p	BD131	75p	CA3028A	86p	NKT713	25p	1N4004	10p		
AC127	25p	BD132	75p	CA3035	£1.53	NKT781	20p	1N4005	15p		
AC128	24p	BD131/132	£1.50	CA3043	£1.73	NGT710	25p	1N4006	15p	3N84	£1.30
AC128 AC176	44p	BDV20	85p	CA3044	£1.42	OA47	8p	1N4007	15p	3N128	73p
AC151	20p	BF115	23p	CA3046	86p	OA79	8p	1N4148	4p	3N140	82p
AC152	25p	BF183	35p	CA3048	£2.34	OA81	8p	1N4500	14p	3N152	82p
AC153	28p	BF187	35p	CA3052	£1.80	OA80	8p	1N4504	14p	3015F	£2.00
AC176	20p	BF173	28p	CA3065	£1.42	OA81	5p	1N4508	25p	3015G	£2.00
AD151/176K	50p	BF177	25p	CA3088E	£1.53	OA85	5p	1544	7p	7400	20p
AD178	17p	BF178	31p	CA3089E	£2.18	OA90	5p	15920	7p	7401	20p
AD188K	23p	BF180	35p	CA3090Q	£4.70	QA202	7p	15940	8p	7402	20p
AC187/188K	40p	BF194	15p	CD4001AE	54p	OC20	97p	2N404	23p	7403	20p
ACV17	27p	BF195	15p	CD4009AE	£1.50	OC25	37p	2N4696	15p	7404	25p
ACV18	20p	BF196	15p	CD4011AE	54p	OC28	70p	2N4697	17p	7405	25p
ACV19	20p	BF200	35p	CD4012AE	54p	OC29	70p	2N4698	30p	7408	25p
ACV20	20p	BF254	14p	CD4013AE	54p	OC35	90p	2N705	10p	7409	25p
ACV21	19p	BF255	15p	CD4015AE	£2.92	OC38	63p	2N706A	12p	7410	20p
ACV22	19p	BFX13	25p	CD4017AE	£2.92	OC41	40p	2N708	16p	7413	20p
AD140	55p	BFX28	25p	CD4018AE	£2.92	OC42	40p	2N911	50p	7419	20p
AD149	50p	BFX84	25p	CD4020AE	£3.25	OC44	20p	2N914	20p	7420	20p
AD151	37p	BFX85	34p	CD4024AE	£2.00	OC45	20p	2N918	42p	7425	35p
AD162	37p	BFX86	35p	CR1/051C	54p	OC71	20p	2N929	25p	7440	24p
AD151/162	74p	BFX87	30p	CR1/401C	71p	OC72	20p	2N930	20p	7442	£1.18
AF106	20p	BFX88	25p	CRS340AF	£1.53	OC75	25p	2N1131	24p	7443	£1.45
AF114	25p	BFY50	15p	CRS340AF	£1.53	OC76	25p	2N1132	24p	7444	£2.00
AF115	25p	BFY51	15p	CZ6	50p	OC77	40p	2N1302	17p	7445	£1.45
AF116	25p	BFY52	15p	D10 (NTGD10)	OC81	20p	2N1303	17p	7446	£1.45	
AF117	25p	BFY53	17p		OC81D	20p	2N1304	24p	7447	£1.25	
AF118	44p	BFY90	£1.05	RT84	£2.80	OC83	23p	2N1305	24p	7450	20p
AF124	25p	BP101	75p	TC190	85p	OC84	23p	2N1306	24p	7451	20p
AF125	40p	BP106	85p	RC20	48p	OC136	50p	2N1307	30p	7453	20p
AF126	17p	BRY38	40p	JA24	£2.00	OC170	25p	2N1308	34p	7459	20p
AF136	47p	BSX19	16p	LIC709C-5	42p	OC171	30p	2N1309	34p	7460	20p
AF186	40p	BSX20	16p	LIC709C-8	42p	OC171M	42p	2N1559/CRV1	40p	7470	45p
AF236	50p	BSX21	20p	LIC723C-5	£1.02	ORP12	50p	401C	71p	7472	32p
AF279	55p	BSY27	20p	LIC723C-14	£1.00	ORP90	40p	2N1613	15p	7473	45p
ASV26	25p	BSY28	25p	LIC741C-5	45p	ORP61	40p	2N1711	15p	7474	45p
ASV27	30p	BSY28A	25p	LIC741C/B	40p	ORP89	50p	2N1893	54p	7475	45p
ASV28	22p	BY100	20p	MC1363L	£1.75	PN70	8p	2N2218	33p	7476	45p
ASV29	30p	BY127	22p	MC1305P	£2.80	PN71	8p	2N2218A	44p	7480	87p
BA138	15p	BTY79 400R	£1.80	MC1307P	£1.85	PN107	7p	2N2219	36p	7482	87p
BAX16	9p	BT100	£1.80	MC1310P	£2.85	PN108	7p	2N2219A	35p	7483	£1.32
BB103	19p	BT106	£1.28	MC1330P	80p	PN109	7p	2N2236	17p	7486	33p
BB104	20p	BZ198C-1	13p	MC1352P	£2.80	PK3819(2N3819)	7p	2N2269	15p	7490	70p
BB105	30p	BZ198C-3V6	13p	MC1468L	£4.20	SC1460	£2.80	2N2899A	17p	7491A	£1.28
BC107	13p	BZ198C-3V9	13p	MC1468L	£2.88	SC1460	£2.80	2N2484	42p	7492	£1.28
BC107/BC177	33p	BZ198C-4V3	13p	MFC4000B	65p	ST2	28p	2N2646	45p	7493	75p
BC108	12p	BZ198C-4V7	13p	MC4024P	£2.20	SL103A	50p	2N2904	44p	7494	£1.13
BC108/BC178	28p	BZ198C-5V1	13p	MC4044P	£2.20	SL403A (Rect)	80p	2N2904A	44p	7495	80p
BC109	13p	BZ198C-5V6	13p	MFC8000	£1.83	SL803A	80p	2N2905	85p	7496	£1.48
BC109/BC179	33p	BZ198C-6V2	13p	MFC8000	£1.15	SL803A	80p	2N2905A	75p	74100	£1.84
BC109C	14p	BZ198C-6V8	13p	MFC8010	£2.80	SL403D (IC)	80p	2N2924	18p	74107	52p
BC117	15p	BZ198C-7V5	13p	MFC8040	£2.24	Amp.)	£2.50	2N2925	20p	74121	43p
BC140	30p	BZ198C-8V2	13p	MFC9020	£2.12	TAA283	£1.12	2N2926	16p	74141	£1.00
BC147	10p	BZ198C-9V1	13p	MAJ571	85p	TAA293	87p	2N3053	24p	74150	£1.35
BC148	9p	BZ198C-10V	13p	MAJ520	65p	TAA310	£1.25	2N3054	85p	74151	£1.10
BC149	15p	BZ198C-11V	13p	MAJ521	65p	TAA320	75p	2N3055	85p	74152	£1.35
BC157	15p	BZ198C-12V	13p	MAJ2955	£1.00	TAA381	45p	2N3228	£1.10	74154	£2.00
BC158	11p	BZ198C-13V	13p	MAJ3055	80p	TAD100	£1.87	2N3391A	23p	74155	£1.00
BC159	12p	BZ198C-15V	13p	MAJ480	87p	TAD110	£1.87	2N3525	£1.04	74156	£1.55
BC147/157	22p	BZ198C-16V	13p	MAJ481	£1.25	TIL112	£2.00	2N3702	10p	74190	£1.80
BC148/158	20p	BZ198C-18V	13p	MAJ481	£1.35	TIL209	35p	2N3703	10p	74191	£1.80
BC149/159	22p	BZ198C-20V	13p	MAJ802	£4.12	TIP31A	80p	2N3704	10p	74192	£1.74
BC167	11p	BZ198C-22V	13p	MAJ802	MJ4502	TIP32A	70p	2N3705	10p	74193	£1.74
BC168	18p	BZ198C-24V	13p	MAJ802	£2.56	TIP41A	85p	2N3706	10p	74198	£1.50
BC169	11p	BZ198C-27V	13p	MAJ900	£1.00	TIP42A	£1.00	2N3707	10p	74197	£1.50
BC199C	12p	BZ198C-30V	13p	MAJ1000	£1.50	TIS43	30p	2N3708	8p		
BC177	20p	BZ198C-39V1	13p	MAJ4502	£4.44	VA10666	15p	2N3709	10p	40250	80p
BC178	16p	BZ198C-12V	70p	MPF102	37p	VA1039	15p	2N3710	10p	40308	40p
BC179	20p	BZ198C-15V	70p	MPF103(2N5457)	40p	VA1040	15p	2N3711	10p	40310	40p
BC182	18p	BZ198C-18V	70p	MPF104(2N5458)	40p	VA1077	15p	2N3773	£2.50	40311	40p
BC182L	10p	BZ198C-24V	70p	MPF104(2N5458)	40p	W01	30p	2N3819	28p	40312	40p
BC183	8p	BZ198C-27V	70p	MPF105(2N5459)	40p	W05	31p	2N3820	60p	40320	40p
BC183L	10p	BZK61C-7V5	23p	MPF105(2N5459)	40p	W02	32p	2N3823E	20p	40360	50p
BC184	13p	BZK61C-8V2	23p	NKT0033	95p	W04	33p	2N3826	30p	40381	45p
BC184L	12p	BZK61C-9V1	23p	NKT0033	95p	W06	35p	2N3866	£1.10	40392	45p
BC192	12p	BZK61C-10V	23p	NKT211	25p	W08	44p	2N3904	28p	40406	52p
BC212L	10p	BZK61C-11V	23p	NKT212	25p	ZTX107	12p	2N3906	28p	40407	40p
BC238	16p	BZK61C-12V	23p	NKT213	25p	ZTX108	11p	2N4058	13p	40408	54p
BC238/308	28p	BZK61C-13V	23p	NKT216	46p	ZTX100	13p	2N4080	11p	40409	62p
BC257	9p	BZK61C-15V	23p	NKT217	50p	ZTX302	16p	2N4061	11p	40410	62p
BC258	9p	BZK61C-18V	23p	NKT218	25p	ZTX303	15p	2N4062	11p	40430	£1.13
BC259	12p	BZK61C-20V	23p	NKT219	25p	ZTX304	15p	2N4441	70p	2N4468A	40p
BC307	18p	BZK61C-22V	23p	NKT221	18p	ZTX314	11p	2N4444	£2.28	40511	£1.82
BC308	18p	BZK61C-24V	23p	NKT224	18p	ZTX320	30p	2N4871	40p	40512	£1.82
BCY30	25p	BZK61C-24V	23p	NKT225	20p	ZTX330	18p	2N4990	60p	40575	£1.54
BCY31	25p	BZK61C-27V	23p	NKT229A	12p	ZTX500	14p	2N4991	45p	40576	£1.48
BCY32	50p	BZK61C-30V	23p	NKT281	25p	ZTX501	15p	2N5245	45p	40600	70p
BCY33	20p	CA3004	£2.25	NKT351	75p	ZTX502	17p	2N5457(MPF)	40p	40601	70p
BCY34	40p	CA3011	£1.40	NKT401	75p	ZTX503	17p	2N5457(MPF)	40p	40602	45p
BCY38	30p	CA3011	£2.20	NKT402	77p	ZTX504	45p	2N5458(MPF)	40p	40603	70p
BCY58	18p	CA3013	£1.30	NKT403	85p	1N914	4p	104	40p	40699	£1.00
BCY70	18p	CA3014	£1.52	NKT404	80p	1N3754	20p	2N5458(MPF)	40p	40673	80p
BCY71	30p	CA3018	80p	NKT405	75p	1N4001	7p	105	40p	40730	£1.50

ELECTROLYTIC AXIAL LEADS

Mfd	Working Voltage	Price	Mfd	Working Voltage	Price
1 0	40V	7p	100	16V	6p
1 0	10V	5p	100	25V	5p
2 2	25V	7p	100	60V	7p
2 2	63V	5p	100	40V	10p
4 7	40V	5p	220	25V	8p
10	25V	5p	220	40V	9p
10	63V	6p	470	25V	12p
22	25V	6p	1000	25V	16p
22	45V	6p	2200	40V	30p
47	25V	6p	4700	16V	33p
47	40V	6p			

CAPACITORS—METALLISED POLYESTER

Stock values MFD Price each

0 01	0 015	0 022	0 033	3p
0 047	0 068	0 10		4p
0 150	0 220			5p
0 33</				

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

FOR SALE

FIBRE OPTICS

Flexible Light Pipe for conveying light to inaccessible positions. Fibroflex Type 1. Glass 1-14mm effective dia. PVC sheathed, 44p per metre. (VAT inc.), P. & P. 10p. Any quantity.

Polariser Sheet up to 1 sq. ft. max. size. 161p per sq. in. (VAT inc.), P. & P. up to 6 in. square 10p; over 6 in. square 30p

- ★ Cut down glare
- ★ See those nitix tubes
- ★ Cross them for light control
- ★ Make your own strain gauge for plastics and glass

Circuit Board Etching Kits. Full instructions. £1-37½ (VAT inc.), P. & P. 14p

Photographic CDS Light Cells—used (with part of original circuit free), 33p (VAT inc.), Post free.

All items are strictly C.W.O.

From: **ARVIN SERVICE COMPANY**
12 CAMBRIDGE ROAD
ST. ALBANS

TV LINE OUT-PUT TRANSFORMERS

Tidman Mail Order Ltd., 236 Sandycroft Road, Richmond, Surrey TW9 2EG
01-948 3702

CATALOGUE NO. 18. Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. **ARTHUR SALLIS RADIO CONTROL LTD.**, 28 Gardner Street, Brighton, Sussex.

LARGE QUANTITY test equipment, receivers, transceivers, meters, variacs, P.S.U.S. Over 1,000 items for immediate disposal. S.A.E. plus 25p. Refund on purchase over £2. F.J.C., Colne Mill, Alvington, Lydney, Gloucester.

SEEN MY CAT? 5,000 Items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

PRACTICAL ELECTRONICS. Vols. 1, 2, 3. Bound. Vols. 4, 5 not bound. Offers. Box 51.

SERVICE SHEETS

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 15p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

MUSICAL INSTRUMENTS

HALO—the new gear as supplied to Hawkwind. Solid Gold Cadillac. Tone generators £12-11, ring modulators £12-77, fuzz box £11-34, Wah-wah £11-81, treble boost £8-81. Contact: HALO, Estuary House, Exmouth, Devon.

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

BOOKS AND PUBLICATIONS

Component problems ?

—write to us for our free catalogue. Send a stamped addressed envelope to Dept. PE1

J. T. Eden Electronics
P.O. Box 5
LANCASTER LA1 3HZ

DIGITAL COMPUTER Logic and Electronics. A four volume Self-instructional course, £2-99 post free. Money back assurance. **CAMBRIDGE LEARNING**, 8a Rose Crescent, Cambridge.

LADDERS

LADDERS, 24½ft £9-80, carr. 80p. Please add 10% V.A.T. to total order. Leaflet. **HOME SALES LADDER CENTRE (PEE2)**, Haldane, Halesfield (1) North, Telford, Salop. Tel. 0952-586644.

EDUCATIONAL

TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commences September 10th. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: **London Electronics College, Dept. B/9, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.**

ENGINEERS. Get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Buildings, etc., FREE book from: **BIET (Dept. ZC BPE 30), Aldermaston Court, Reading, RG7 4PE.** Accredited by CACC.

A SUCCESSFUL CAREER IN RADIO

Get the success you deserve—take an ICS home study course. Pass C&G, M.P.T. exams **FIRST TIME!** Free books, Low cost Personal tuition. Send **TODAY** for FREE Guide on Radio, TV, Electronics, Electrical Engineering.

Name _____

Address _____

ICS

Dept. 730T
Stewarts Road,
London SW8 4UJ

RECEIVERS AND COMPONENTS

RESISTORS — UNREPEATABLE CLEARANCE LINE, TOP QUALITY CARBON FILM

½, ¼, 1/10, 1/20, 1/50, 1/100 watt 5% Tol. Std. Limited No. 2% Hi-Stab. ½ & ¼ W. only. Wide Choice Values, E24 Series but **NOT COMPLETE RANGES** Values, your choice in 5s, nearest Subs. given if not available.

5% Std. 55p/100, £5/1,000 No V.A.T.
Hi-Stabs. 75p/100, £6/1,000 Post Free C.W.O.

Special Offer 1,000 Assorted £3. Min. 100 different types given.

WRAP RESISTORS, 9 Ellen Close North Petherton, Som.
Tel.: N. Petherton 662501

TUNBRIDGE WELLS. Components from Teleservice. S.A.E. or call in for list. Special offers, limited quantity; Matched AD161/2, 68p; 10 transistors similar 2N3702/3 unmarked, 32p; 12 1N914/6, 20p unmarked; air spaced twin gang receiver tuning capacitors, unused, 50p; thin grey connecting flex, 1p yd. Minimum order 40p, post free, but add 10% V.A.T. 108 Camden Road, Tunbridge Wells, Kent. Tel. 31803.

5—N-Channel FETs 3819E—£1

Full specification devices complete with circuit details for building voltmeter, timer, ohmmeter, etc.
Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LTD.
45 Station Road, Gerrards Cross, Bucks.
MAIL ORDER ONLY

BRAND NEW COMPONENTS by return. Electrolytics 16V, 25V, 50V—0.47, 1, 2.2, 4.7, 10 mF, 4p; 22, 47, 100 (50V, 5p); 100, 51p (50V, 7p); 220, 6p (50V, 8p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02, 2p; 0.04, 0.05, 3p; 0.068, 0.1, 3½p. Polystyrene 63V E12 series 10-1,000pF, 2p; 1,200-10,000pF, 3p. Miniature highstab resistors, 5%, E12 series—Carbon Film ¼W, 1Ω-10MΩ (10% over 1 MΩ). Metal Film ¼W, 10Ω-2.2MΩ and 1W, 27Ω-10MΩ all 3p each. Postage 8p. **The C.R. SUPPLY CO.**, 127 Chesterfield Road, Sheffield, S8 0RN.

M. & M. ELECTRONIC SUPPLIES

ALL ELECTRONIC COMPONENTS
SUPPLIED BY RETURN OF POST

ALL BRAND NEW AND GUARANTEED

- ★ MOTOROLA
- ★ FAIRCHILD
- ★ TEXAS
- ★ SIEMENS
- ★ GENERAL ELECTRIC
- ★ MULLARD
- ★ FERRANTI
- ★ R.S. COMPONENTS

S.A.E. QUOTATIONS BY RETURN OF
POST. MAIL ORDER ONLY.

ALL MAIL TO:

11 ANDREW STREET, WALTON
LIVERPOOL L4 4DS

Trampus electronics

Add 10% VAT (A) to all prices. All brand new, no rejects. Money Back Warranty.
5V DIGITAL INDICATOR: 0-9DP socket and filter £1.45.

LED TYPE 4' 0-9DP DIL £2.25 each; 6x £2.10 each; 4 digit type £11.

LIGHT EMITTING DIODES. All with data and panel clip. TTL 200 P dia. 25p. Red 1" dia. type 33p. Green 15p. INPRA RED beam LED £1.10.

GAS detector £1.89. Ultrasonic transducer £2.

DALCO PCB resist marking pen 60p. Copper board 12" x 6" SRBP 40p. FeC etch PAK 10p.

INTEGRATED CIRCUITS: with data if required.
IC LITE SWITCH: Photo amp/trigger 40mA/11-20V relay or TTL 87p. DII relay £1.10.

IC digital clock

MOS/LSI type: 28 pin, 4 or 6 digit, 12/24hr. Ch1 with socket £18. PCB 11" £21.49.
DVM voltmeter £12. Data 38p. 3W AF amp £1.24.

741 DII 8 pin 28p; 709 10p. DII 20p; 748 20p; mono 710 38p. 555 TIMER/mono/astable osc. clock 98p.

REGULATORS: 1A 6 to 20V £1.49; 723 57p.
RECEIVER: ZN414 £1.19. Mini Rx Kit £1.99.

1310 stereo decoder for tuner £2.69. KIT £3.45.

NEW LOW PRICES

GATES 7400/1/2/3/4/5/10/20/30/40/50, etc., 14p each. 7413 27p; 7441 75p; 7447 £1.09; 7470, 7472 28p; 7473, 7474 36p; 7475 60p; 7476 32p; 7490 59p; 7492 87p; 7490 89p; 7483 £1.10; 7486 87p; 7493 78p; 7494 83p; 7495 88p; 7496 89p; 74121 45p; 74141 99p; 74190/1/2/92/93/96 £2.39. DIL

PLUGS/IC case 10mm high 16 pin 35p.
DIL SOCKETS: low or high profile 8/14/16 pin 18p.

SEMICONDUCTORS:
2N3055 40p; BC107 8p; BC108 8p; BC109 8p;
BC147/8/9 10p; BC167/8/9 13p; BC177/8/9 15p;
BC182/3/4 10p; TRANSFORMER: 1A 6 and 12V £1.
BD131/2 55p; BFY50/51/52 13p; T1843 UJT 24p;

2N706 11p; 2N2369 12p; 2N2926/8 8p; 2N2646 40p; 2N3053 17p; 2N3055 40p; 2N3614 55p;
2N3702/3/4/5/6/7/8/9/10/11 All 8p each.

FETS: 2N3819 27p; 2N3823 29p; RCR 400V 1A 23p; 4A 55p. TRANSFORMER: 1A 6 and 12V £1.

CAPACITORS: Disc 22pF to 0.1µF 4p. 25V electrolytic 10, 50, 100µF 5p; 1,000µF 15p. PRESETS 5p each. RESISTORS 1W 5% 14p each.

CARBON POTS 12p each. Dual 40p. Switch +12p.
All Din Plugs 13p; sockets 9p; Vero RRP.

FLUORESCENT LIGHTS 12VOLT £2.79

13" 8 watt fully built with diffuser.

TRO and GDBAR communications and Hi-Fi retailer. ELECTRONIC ORGANS from 367.

PW ELECTRONIC CAR IGNITION KIT £6.47.
VAT: YOU MUST ADD 10% (A) to all prices.

FREE CAT. S.A.E. Data sheets 8p each. P. & P. 8p. C.W.O. P.O. BOX 28, BRACKNELL, BERKS.

PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.
0.47µF: ±5% 30p; ±3% 40p; ±1% 80p
1.0µF: ±5% 40p; ±3% 60p; ±1% 60p
2.2µF: ±5% 60p; ±3% 90p; ±1% 75p
4.7µF: ±5% 70p; ±3% 90p; ±1% 81-10
6.8µF: ±5% 95p; ±3% £1.15; ±1% £1.80
10µF: ±5% £1.10; ±3% £1.40; ±1% £1.80
15µF: ±5% £1.60; ±3% £2.10; ±1% £2.70

TANTALUM BEAD CAPACITORS. Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (78 capacitors) £5.

NEW 1-TRANSISTORS. BC107, BC108, BC109. All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178 at 35p each or 3 for 95p.

POPULAR DIODES. IN914, 7p each; 8 for 50p; 18 for £1. IN916, 9p each; 6 for 50p; 14 for £1. IS44, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5mA. All new and marked. Price 9p each; 6 for 50p; 14 for £1. Special offer 6 off each voltage (65 zeners) £4.25.

RESISTORS. Carbon film 5%, 1W at 40°C, 1W at 70°C. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special pack—10 off each value 2-21Ω (730 resistors) £5.

440V A.C. CAPACITORS. 0.1µF, size 1 1/2in x 1/2in, 25p; 0.25µF, size 1 1/2in x 3/4in, 30p; 0.47 and 0.5µF, size 1 1/2in x 3/4in, 35p; 1.0µF, size 2in x 1/2in, 45p; 2.0µF, size 2in x 1/2in 75p.

SILICON PLASTIC RECTIFIERS 1.5A—Brand new wire-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

5p post and packing on all orders below £5. Please add 10% VAT to all orders

MARCO TRADING
Dept. E9, The Maltings, Station Road
Wem, Shropshire

COMPUTER PANELS 6 assorted. No rubbish. £1 (25p). M.C. METERS 3 assorted 2in-3in, £1-15 (25p). 5 DIG. RESETTABLE COUNTER 15/25V. Works on 12V, £2-20 (15p). SILICON DIODES 650V 1A. 10 on 18p board 35p (5p). New 800V IA. 6-25p (5p). UNIT WITH 4 x BFY51. 4 Silicon Diodes, 4 Zeners, caps and resistors 45p (8p).

COPPER CLAD PAX. PANELS 5 1/2in x 5 1/2in 6 for 38p (10p). WIRE ENDED NEONS 10-50p (8p). Bank of 5 with 5-C407 driver trans. 50p (8p). UNIT WITH 25V D.C. MOTOR 2 relays: 2 motorised switches, mass of gears, etc. £2 (30p).

THREE BANK 12 WAY MIDGET UNISELECTOR 250 ohm coil £2-25 (15p). POLYSTYRENE CAPACITORS 125V. 100, 150, 180, 220, 300, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 0-01, 0-012. 22p dozen (8p). Mixed with 5/mica 100-50p c.p.

2LB ASSORTED COMPONENTS £1-60 c.p.
2LB ASSORTED COMPUTER PANELS £1-60 c.p.

Lists computer panels, etc. 10p stamps refunded on purchase.

J.W.B. RADIO
75 HAYFIELD RD., SALFORD 6, LANCs.

Postage in Brackets Mail Order Only
Closed for Holidays—September 1st-16th

20 FREE RESISTORS

1W Carbon Film, any mix, with all August orders ADD 10% VAT to total. BRAND NEW FULL SPECIFICATION COMPONENTS: BC107B, BC108A/B/C, BC109B/C, all 8p. BFY51 13p, BCY70 15p, 2N4058 12p, 2N3819 25p, 2N3704 10p, 2N3702 10p, 2N3055 35p, 2N2926GRN 9p, OC45/71 10p, MICRO 741 27p. Diodes: CA90 9p, IN4141 IN914p. Zeners: BY258 ser. 8p. Tant. Bead Caps. 8p. Carbon Film Res. 1W 5%: 28p for 50 any mix. (22Ω-2.2M). Iskra 1W 35p for 50. All E12 ser. Paks as before. Money back if not satisfied.

ADFONIC (P69)
18 Yaw Lane, Ashley, New Milton, Hants
GU32 5BA

C.W.O. P. & P. at cost 10p min. Lists Free. Mail Order Only.

RADIO & TELEVISION AERIAL BOOSTERS £2-95, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs, UHF-VHF televisions £7-50. (Carr. £1-50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ransbottom, Bury, Lancs.

R.T. SERVICES (MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Veroboard 6x5 0-1 Matrix, 2 for £1. 4x4 0-1 Matrix, 4 for £1. 12x3 0-15 Matrix, 75p each.

Mullard A.M. Module. I.F. Strip, LPI166, £1.10 inc. P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2 1/2 x 2 1/2 in with circuit, £1-37 inc. P.P.

Crouzet Geared Motors, 10-30-60 r.p.m. New, £1-54 inc. P.P.

UHF TV Tuners. Transistorised, £1-65 inc. P.P.

3BP1 with Base and Screen, £2-75 inc. P.P.

VCR138 CRT. New, boxed, £3-30 inc. P.P.

Brand New Panel VU Meters, 4 1/2 x 3 1/2 in calibrated, £3-30 inc. P.P.

Transformers: 7.5V 1A, 66p inc. P.P. P.P. 18-0-18V, 200mA + 24V, 77p inc. P.P.

9-0-9V, 100mA, 69p inc. P.P. 12-0-12V, 100mA 69p P.P. 20V, 1A 88p inc. P.P.

Transformers: 52-0-52V, 1A + 22-0-22V, 200mA, £2-20 inc. P.P.

P.C. Board. S/S, 5 1/2 x 5 1/2 in, 10 for 70p inc. P.P.

Panel with 5-200 PIV 1A SCRs + 14 OA200 diodes plus components 70p inc. P.P.

2,500 mfd 100V capacitor 4 1/2" x 1 1/2". New, 85p inc. P.P.

Panel Meter 50µA. Brand new, 4 1/2" x 3 1/2". £3-30.

BRAND NEW FULL SPEC. DEVICES SATISFACTION

OR YOUR MONEY BACK

U.K. ORDERS—Add 10% VAT to total

MICROCIRCUITS: 709 24p; 710 36p; 723 51p; 741 (14 pin) 27p; 748 37p; PA230 60p;

FET Op. Amp. £1-62. SOLDERCON IC PIN SOCKETS 0.5p per pin. SOCKETS: 14 pin DIL HI or LO 12p each. RECTIFIERS: 1A: 50V 3p; 100V 4p; 200V 4p; 400V 5p; 800V 6p; 1,000V 7p. ZENERS: BZY88C 2-7V to 33V 8p each. DIODES: IN916 4p; OA90 6p; IN4148 4p. LED Panel Lamp with Bush and Data 26p. DALO PC RESIST PEN 68p.

TRANSISTORS: 2N2926 BROWN 5p; 2N3053 15p; 2N3055 12p; 2N3702 10p; 2N3704 10p; 2N3819 26p; 2N4058 12p; BC107A 8p; BC108B 8p; BC109B 8p; BC109C 8p; BCY70 15p; BFY50/51/52 13p; OC44/45/71/72 12p; AF114/5/6/7 12p; AC126/7/8 12p.

Above prices on 2nd July—check our list.

JEF ELECTRONICS (P.E.9)

York Works, 12 York Drive, Grappenhall, Warrington WA4 2EJ. Mail Order Only.

C.W.O. P. & P. at cost. 10p min. List Free.

DRY REED INSERTS

Overall length 1.85" (Body length 1.1").

Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 69p per doz.;

£4.12 per 100; £30.25 per 1,000; £275 per 10,000. All carriage paid.

G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 34897

MISCELLANEOUS

PSYCHEDELIC MINI-STROBE

A VERY POWERFUL, POCKET-SIZED STROBE-LIGHT that is SELF-CONTAINED and you can take anywhere. Go to parties and really BRAIN-FREEZE them with DAZZLING PSYCHEDELIC EFFECTS and STOP-MOTION FLASHES. Boffin's new MINI-STROBE kit constitutes a fully solid-state electronic device which is COMPLETE with FUTURISTIC case/reflector unit, printed-circuit board, electronics, and source-lamp—the only extra is a battery which you can buy locally. The whole thing can be easily built in a few hours. A veritable FLICKERING FASCINATOR! Adjustable flash-rate. GET ONE (or two) NOW and BEGIN STEALING THE THUNDER at DISCOS and PARTIES with your own POCKET-LIGHTNING!

SEND £2-10 (inc. VAT) for YOUR MINI-STROBE. MAIL ORDER ONLY

To: Boffin Projects
4 Cunliffe Rd., Stoneleigh, Ewell, Surrey

AT LAST YOU CAN TRANSMIT AND FORGET ABOUT LICENCE EXAMINATIONS

because this Ministry approved transmitter/receiver kit does not use R.F. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5-80 (inc. VAT) NOW
S.A.E. for details) MAIL ORDER ONLY
TO: 'BOFFIN PROJECTS'
DEPT. KE2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY

12 VOLT FLUORESCENT LIGHTS

(as illustrated by Thonn/AEI)



Beat power cuts. Be independent. Ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v is available. Guaranteed for six months. Ready to use at:

12 ins. 8 watt £3-86 post paid } including
21 ins. 13 watt £4-82 post paid } V.A.T.

Callers welcome.

For lists or enquiries, large s.a.e.

SALOP ELECTRONICS, 23 WYLE COP
SHREWSBURY, SHROPSHIRE

P.E. SYNTHESIZER KNOB KIT

Complete kit as Feb. issue £3-91 post free
43 knobs, 7 calibrated discs.
DE LUXE KIT as above but £5-89 post free
calibrated for programming.

Inclusive postage and V.A.T.

RE-AN PRODUCTS LTD.
Burnham Road, Dartford, Kent
Tel.: Dartford 20785

standard german plugs & sockets

WITH EARTHING CONTACTS

Plug131

34p

incVAT

With cable

side entry



Socket200

£1.10

incVAT

Twin socket

outlet to

fit wall box

Socket210

61p

incVAT

For bench

mounting



Socket230

55p

incVAT

For chassis

mounting

Postage & packing—1 item 3p each additional item 2p
over 10 post free TRADE ENQUIRIES WELCOME

michael wheeler ltd 01-388 0575
18-19 WARREN STREET LONDON W1P 5DB

ALUMINIUM SHEET to individual sizes or in standard packs, 3p stamp for details. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

BURGLAR AND FIRE ALARMS. Complete Master Control Module now available from our own panels. Ideal for all Alarm/switching circuits with data sheet, etc. £6-85. Complete Alarm kits £49-50. Magnetic Switches, Sensors, Panels, available. CASTLE ALARMS, P.O. Box W06, Windsor, Berks.

NEW FROM ELBON

L.E.D.'s (Red Emitting) ideally suited for panel indicators

Price only: 33p each or £2-50 for 10

Light SENSITIVE SWITCHES

Two types available giving wide operating voltages:

LITE-IC2 11V-20V working — £1 each — £8-50 for 10

LITE-IC3 20V-30V working — £1 each — £8-50 for 10

Applications include: Relay, Triac or Logic Drive, automatic light switching and door control, beam/break detection — burglar alarm, batch counting and code reading.

BARGAIN PACK!

2 LITE-IC2, 2 LITE-IC3 and 5 LED's all for £5-00

ALL PRICES INCLUDE VAT, PACKING AND CARRIAGE

Please send C.W.O. to:

LITE-IC, ELBON, SUMMERFIELD,
THE CRESCENT, WEST WITTERING, SUSSEX

LOW COST LEDS

MLED 500 in standard T092 package for P.C. mounting. MV54 is $\frac{1}{2}$ size, 2 mm, miniature. Both provide visible red light from 1-65V, 20mA. 150 Ω resistors available for 5V d.c. (TTL) operation.

	5	10	25	50	100
MLED 500	£1-10	£2-20	£3-74	£6-60	£2-65
MV54	£1-10	£2-09	£3-32	£6-05	£2-10
150 Ω	—	11p	22p	44p	—

MAR'S TAILS: Spray of several thousand glass fibres, ready to use as part of decorative displays. £11 each including P. & P. and VAT.

POLARISERS for light control, glare reduction, modulators, stress analysis, S/N enhancement for displays.

HN32 Linear Polariser, for Kerr cells, etc.

HRCP7 Red Circular Polariser, for LED displays.

HNC37 Neutral Circular Polariser, for c.r.t.s, meters, etc.

Send 9 x 6in S.A.E. for full details of the above plus our full range of Fibre Optics.

FIBRE OPTIC SUPPLIERS

P.O. Box 702 LONDON W10 6SL

Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 76 $\frac{1}{2}$ p)

SEND 5" 7" S.A.E. FOR DETAILS TO:

CROFTON ELECTRONICS
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

THERMOCOUPLES

Acramet and Acraspeed thermocouples, from IC are:-

Extremely accurate for fluid, gas or metal temperature measurement.

Individually calibrated and carry a certificate plus a one year guarantee.

Available with immersion or contact, non-earthed, multiples, boss or plug.

Details available on request.

International Combustion Limited,
Sinfon Lane,
Derby DE2 9GJ

METER REPAIRS. Ammeters, Voltmeters, Multi-Range meters, etc., also Linear scale Transistorised Ohmmeters for sale. METER REPAIRS, 39 Chesholm Rd., London N16 0DS.

LIMITED QUANTITY PVC insulated connecting wire: reputable brand. 14/0076, £2 per 500 yds.; 1/029 and 7/0076, 50p per 100 yds. All post paid. Various others. S.A.E. list. PALMER, 68 Clyst Valley Road, Clyst St. Mary, Exeter.

ELECTRONICS FANATICS

whether beginner or advanced — we offer a range of over 35 SUPER projects.

Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's just GOT TO BE LEADS TO INTEREST YOU in the science-fiction-world of BOFFIN.

GET YOUR CATALOGUE — SEND JUST 15p NOW!

MAIL ORDER ONLY

TO: BOFFIN PROJECTS
4 CUNLIFFE ROAD
STONELEIGH, EWELL
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

GLASS FIBRE P.C. BOARD—large supplies available. $\frac{1}{8}$ in single sided one ounce copper, 2p per 3 sq in (under 1ft); 75p per sq ft (over 1ft). $\frac{1}{4}$ in double sided one ounce copper, 1p per sq in (under 1ft); \$1 per sq ft (over 1ft). Please add 10p per sq ft postage and packing. We can cut to your size at 1p per cut. SOLID STATE LIGHTING, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

ENAMELLED COPPER WIRE

S.W.G.	1/1b Reel	1/1b Reel
10-14	£1-15	65p
15-19	£1-15	65p
20-24	£1-18	68p
25-29	£1-25	75p
30-34	£1-30	80p
35-40	£1-40	85p

Please add 10% to all above prices to cover VAT
The above prices cover P. & P. in U.K. Supplied by

INDUSTRIAL SUPPLIES

102 Parrswood Rd., Withington, Manchester 20
Telephone No. 061-224 3553

CONSTRUCTION AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

CLEARING LABORATORY, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, MC relays, components, etc. Lower Beeding 236.

R. & P. ELECTRONICS

Sound to Light, s/ch. 750W	£8
Strobe Units, 3 o/p 750W	£8
10W Amp Modules 24v	£3-75
Drill Speed Controllers	£2-80
Light Dimmers 250W	£1-99
1 b. Paks Mixed Components	50p

14 QUEENS RISE, RINGWOULD
DEAL, KENT

All prices include VAT and P. & P.

BUILD YOUR NEXT PROJECT in a Bec (Book end chassis) Contemporary design with wooden end cheeks. Three standard sizes. S.A.E. with enquiries please. H.M. ELECTRONICS (PE3), 275a Fulwood Road, Sheffield, S10 3BD. Tel. 55051.

NEW EDITION TV ENGINEERS' POCKET BOOK

P. J. McGoldrick Price £2.65

THE RADIO AMATEUR'S HANDBOOK 1973 by A.R.R.L. Price £2.95.

1-2-3-4 SERVICING CASSETTES by F. H. Belt. Price £2.30.

110 THYRISTOR PROJECTS USING SCRs AND TRIACS by R. M. Marston. Price £1.50.

VIDEO TAPE PRODUCTION AND COMMUNICATION TECHNIQUES by J. L. Efrein. Price £1.40.

INTEGRATED CIRCUIT POCKET BOOK by R. G. Hibberd. Price £2.60.

AUDIO SYSTEMS HANDBOOK by N. H. Crowhurst. Price £1.35.

BEGINNER'S GUIDE TO PRACTICAL ELECTRONICS by R. H. Warring. Price £1.40.

SIMPLE TRANSISTOR PROJECTS FOR HOBBYISTS AND STUDENTS by L. Steckler. Price £1.35.

PRINCIPLES OF TRANSISTOR CIRCUITS by S. W. Amos. Price £1.65.

NEW IC FET PRINCIPLES AND PROJECTS by K. W. Sessions. Price £1.20.

GETRANSISTOR MANUAL. Price £1.20. *ALL PRICES INCLUDE POSTAGE*

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books


19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185
Closed Saturday 1 p.m.

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HANDY!
TIDY!

DISCOUNT
PRICES

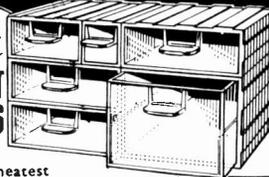

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/1D and 2D have removable space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES
ALL INTERLOCK

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins / 2½ins). £1.25 DOZEN.

DOUBLE UNITS (2D) (5ins x 4½ins / 2½ins). £2.10 DOZEN.

TREBLE (3D) £2.20 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £3.25 for 8, **EXTRA LARGE SIZE (6D1)** £3.10 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £6 and over DEDUCT 5% in the £
Orders £10 and over DEDUCT 7½% in the £
Orders £20 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10, Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES
Please add 10% V.A.T. to total remittance

IVORYET LIMITED

(Dept. PE9) 124 Cricklewood
Broadway, London, N.V.2
Tel. 01-450 4844

Please mention
**PRACTICAL
ELECTRONICS**
when replying to
ADVERTISEMENTS

ELEKTROKIT

12 Lauderdale Road
London, W.9

Telephone 01-286 0011

LIGHT DIMMER. Kit contains all parts including circuit and construction data, 480 watts, fully suppressed. Price £2.10

SCORPIO IGNITION SYSTEMS (P.E. Nov. 1971), £9.50. This kit includes all the parts for the assembly of this popular and reliable system. The hardware and the construction data are included.

Send for details of kits available (please enclose S.A.E.).

All kits sent POST FREE within the limits of the U.K.

Please note, prices shown do not allow for V.A.T. Please add 10% to your order.

PARTBRIDGE MAINS ISOLATION TRANSFORMER. Pri: 105-250V, 3V steps, Sec: 240V, 13 amps. £15, carr. pack. £1.

PARMECO MAINS TRANSFORMER isolated windings. Pri: 200-250V, Sec: 90-120V at 4.5 amp., £4, carr. pack. 50p.

GARDNER'S POTTED TRANSFORMER, 0-250V. Pri: 200-250V. Sec. Input: 18V 300mA, 30V 150mA, 6V 250mA output. Size: 3in x 2½in x 2½in. £1, p.p. 20p. Ex equip. tested.

RIPLEY MAINS TRANSFORMER. Pri: 110V-240V, Sec: 12-5V: 0.12-5V 750mA 7V:0.7 V1A, £1, p.p. 25p.

MAINS TRANSFORMER. Pri: 100-250V, Sec: 22:0.22 200mA, 22:0.22 100mA 0.24V 20mA/A, 80p, p.p. 25p.

TRANSISTOR OUTPUT TRANSFORMER. Ratio 8:1, 120mH. Centre tap 2 watts. output, 20p, p.p. 3p.

SMOOTHING CHOKE, 11MH, 1½in x 1½in x 1½in, 80p, p.p. 7p.

BELLING LEE INSULATED TERMINALS. Red or Black, 5 amp max. 10p pair, p.p. 4p.

FINNED ALUMINIUM HEATSINK. 9in x 1½in. Ready drilled, 80p, p.p. 7p.

FINNED ALUMINIUM HEATSINK. 9in x 8in x 1½in. in C.: 4 x 2N3055, £2, p.p. 25p.

SUB-MIN. CROC. CLIPS. Red or Black, insulated 4p. Min. quantity, 6, p.p. 4p.

GARRARD MAG. TAPE DECKS: 1½p.s., 50V, solenoid operated brakes, etc. Mains voltage motors £7-50 each, p.p. 60p.

MOTEK 3 speed tape deck (1½in x 3½in x 7½in) reel to reel 7in mains operated, £7-50, p.p. 60p.

10 REED SWITCHES operated by push buttons and magnets, 80p, p.p. 25p.

COMPONENT PANEL 6 s'crs (200V 4 amps), 6 condensers, 12 resistors, 80p, p.p. 8p.

COMPONENT PANEL 9 (9CA FJH131) (1-CA300), 1 crystal 7-68KHz + various other components, £1, p.p. 8p.

COMPONENT PANEL, 4 x 500 mfd, 50V d.c. cap. 1 x 2N1218, 1 x 2N11468, 2 x 2N598, plus various other components, 10p, p.p. 8p.

NEON PANEL, 24 neon's, wire ended, 90-240V, 80p p.p. 4p.

MAINS NEONS
Red or Green. Size: ½in x ½in x 1½in. 15p, p.p. 4p.

LEVER ACTION P.O. 1000 TYPE SWITCHES
Lock 4-pole changeover, 15p, p.p. 4p. Ex equip. Lock 2-pole changeover, 10p, p.p. 4p. Ex equip.

MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,500µF 64V, 7,100µF 40V, 50p each. 20,000 30V, 25,000 25V, 35,000 15V, 80p each, p.p. 10p.

MULLARD FULLWAVE RECTIFIERS
6-48V, 15 amp, 75p, p.p. 9p.

BELLING LEE 1.5 amp in-line rubber covered interference suppressor, 25p, p.p. 8p.

RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.

SOLENOIDS 12 VOLT FULL ACTION
2½in x 1½in x 1½in, 40p, p.p. 8p.

SOLENOIDS 12-24V d.c. pull action 1½in x 1½in x 1½in, 40p, p.p. 5p.

SOLENOIDS 240V a.c. pull action 2½in x 1½in x 1½in, 50p, p.p. 9p.

BANGMO WESTON TIME LAPPED METER
Mains operated, 1½in x 1½in x 2½in, £1-50 p.p. 7p.

ARROW RELAY, 240V a.c. coil, double pole change over, 1 make contact's 10A, 240V a.c., 25p, p.p. 5p.

OMRON MK2 MIDGET POWER RELAY, 12V d.c. Double pole changeover. New, 70p, p.p. 5p.

STC MINIATURE RELAY 280Ω, perspex cover, double pole changeover, 6-15V new, 35p, p.p. 5p.

STC VARLEY, miniature relays 700Ω, perspex cover, 4 pole changeover, 40p, p.p. 5p.

POTTER BRUMFIELD 12V d.c. 3 pole changeover with base, contacts rated 7A d.c., £1, p.p. 10p.

TELESCOPIC AERIALS
Chromed 7in closed, 28in extended, 6 section ball jointed base, 28p, p.p. 5p new.

MULLARD 4 DM 180 indicators in plastic holder/cover, ex equip., size approx. 1½in x 1½in x ½in, 86p, p.p. 5p.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA:200 Diodes: 1 reed relay: 1 AZ 229 zenner ass. capacitor/resistors. Power supply 22V, 250 mA d.c. Output 240V a.c., £1, p.p. 20p. Ex equip.

WIRING CABLE
Size: 1-020. Various colours. 350yds, 60p, p.p. 23p.

TAPE POSITION INDICATOR
Re-settable 3 digits, 30p, p.p. 5p.

All orders add 10% V.A.T.

**FIELD
ELECTRIC
LIMITED**

3 Shenley Road
Borehamwood, Herts.
Tel.: 01-953 6009

EX COMPUTER PC PANELS
2 x 4in packed with semiconductor and top quality resistors, capacitors, diodes, etc. Guaranteed min. 35 transistors plus data. 10 boards 50p (9p).

SPECIAL BARGAIN PACK
25 boards £1 (25p). Panels with 4 power transistors sim OC28 50p (9p).

ELECTROLYTICS
68,000µ 16V, 4½ x 2in dia. 25,000µ 25V, 20,000µ 30V, 5,000µ 90V, 35,000µ 15V, 8,000µ 55V, 4½ x 3in dia. 50p (15p). 15,000µ 15V, 10,000µ 35V, 4½ x 2in dia. 30p (10p). (2,000µ 25V wire ends 15p (5p), 12 for £1-50 (15p).

20A DIODES 4 for £1 (7p)

3A DIODES 4 for 50p (5p)

8 BLACK TOGGLES dpst 50p (8p).

250 MIXED CAPACITORS 60p (8p)

250 MIXED RESISTORS 60p (8p)

150 HI-STAB RESISTORS 60p (8p)

200 SI PLANAR DIODES

UNTESTED 50p (5p)

SUB-MIN. CO-AX. PLUGS & SKTS. 4 pairs 50p (5p)

REED RELAYS, MIXED 10 for 50p (5p)

MICRO SWITCHES 8 for 50p (8p)

ASSORTED RELAYS 8 for £1 (12p)

MIN. GLASS NEONS 12 for 50p (5p)

10 WAY TERMINAL BLOCKS

QH BULBS 12V 55W 10 for 55p (5p)

PAPST EXTRACTOR/BLOWER FANS 50p (5p)

100 cfm 4½ x 4½ x 2in. £3-50 (28p)

Postage and package shown in brackets.
Please add 10% VAT to prices.

KEYTRONICS

(Mail Order only)

44 EARLS COURT ROAD

LONDON W8

01-478 8499

BUILD A CHORDING PROFESSIONAL SYNTHESISER



The Synthesiser shown above is the **Dewtron "Apollo" A.1**, which we sell ready-built to professionals. Believe it or not, it uses the **SAME** precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts. **VCO-2 STABLE, PRECISION V/C OSCILLATOR** gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. £24 each or £27 each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. £17. OFT-1 chording module £9. Modules (except VCO-1) guaranteed two years.

With over 7 years' unblemished reputation in these pages, **Dewtron** continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading groups. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.J. Approved by the Association of Musical Instrument Industries. Send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.


254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES CASH SAVINGS

by buying modules and parts in bulk!
All modules are available separately:
Ring Modulator RM2, £8. Voltage-controlled Oscillator VC01, £10-50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £13. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £10. etc., etc. **ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE.** Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £5-50. REVERB Module and spring unit £15. V.A.T. 10% extra. V.A.T. paid orders over £75.

CASED AMPLIFIERS

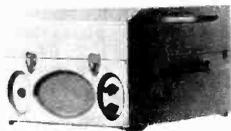

Polished wooden cabinet 14 x 13 x 9in with hinged lid containing a sensitive (20µV) 4-valve amplifier with tone and volume controls, giving about 3 watts output to the 7 x 4in 3Ω speaker. Also a

non-standard single motor tape deck. Easily converted to record player, guitar practice amp., baby alarm, etc. Supplied in good working condition with circuit diagram. Mains operated. Only £3 (£1 up to 200 miles, £1-20 over). Special cassettes £1 (25p). Spare heads 40p. Damaged machines from £1-50 to callers only. Amplifier chassis, 2 ECC83, EL84, EZ80 £1-65 (35p).

COMPUTER PANELS

Type A: 4 OC35, 4 GET103, etc., 50p; Type D: 4 OC36, 8 GET 103, etc., 60p (5p each). Type E: 4 OC29, 4 trimpots, 4 ACY19, 8 other transistors, 35 diodes, etc. £1 (10p). Parcel of 12 top quality boards £2 (25p). 7lb of lower quality including some broken £2 (40p), 56lb £12 (c.p.). Boards from 5p to callers. Pack of boards containing at least 500 components, including 50 transistors 60p (15p).

7lb BARGAIN PARCELS

Hundreds of new components—capacitors, resistors, switches, crystals, pots, PC boards, etc. Outstanding value £1-65 (35p). 500 assorted resistors, good selection £1 (15p); 40 asstd. pots £1 (25p); 300 asstd. capacitors, all types £1 (25p). Heavy duty heat sinks 6 x 5 x 3in, weight 3lb with 2 power transistors, OC36 or 2N1146A £1 (25p). Large selection of panel meters for callers. Audio oscillator 50Hz-20kHz, BFO No. 8 £10; RF Signal generator, Marconi TF144G, 85kHz-25MHz from £12. 741C TO99 or 8 pin DIL 32p; BC107/9 14 for £1; 2N3055 35p. Veroboard in stock. Oscilloscopes available—also lots of odd units suitable for spares. Components in bulk supplied, e.g. 20,000 assorted resistors £25; 100,000 £80.

Post in brackets, small parts 3p. VAT NOT INCLUDED. S.A.E. list, details.

GREENWELD ELECTRONICS (PE3)

24 Goodhart Way, West Wickham, Kent. SHOP at 21 Deptford Broadway, SE8 (next to old cinema). Callers most welcome. Tel. 01-692 2009.

STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP (as in 'W.W.' July '72)
MOTOROLA MC1310P

EX STOCK DELIVERY

Specn. Separation: 40dB 50Hz-15kHz. Distortion: 0-3%. I/P level: 560mV rms. O/P level: 485mV rms per channel. Input impedance: 50k. Power requirements: 8-12V @ 16mA. Will drive up to 75mA stereo 'on' lamp or LED. Simple to build.

KIT COMPRISES FIBREGLASS PCB (Printed and tinned), Resistors, I.C., Capacitors, Preset Potm. and Instructions. Only £3-40 post free + V.A.T.

LIGHT EMITTING DIODE (Red) Suitable as stereo 'on' indicator. For above with panel mounting clip and instructions. Only 29p + p.p. + V.A.T.

MC1310P only £2-77 + p.p. 6p + V.A.T.
14 PIN DIL SOCKETS. 16p each + V.A.T.

NOTE—As the supplier of the original decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.

Fi-Comp Electronics

BURTON ROAD, EGGINGTON, DERBY DE4 6GY

BAKER 12" MAJOR £9-90

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £12-50

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 13in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUDSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W	£8-80	Superb 12 in. 20W	£16-50
Major 12 in. 20W	£9-90	Group 25 12 in. 25W	£8-80
Deluxe 12 in. 15W	£11-00	Group 35 12 in. 35W	£9-90

ALL PRICES
INCLUDE V.A.T.

BAKER LOUDSPEAKER CO., BENSAM MANOR PASSAGE
THORNTON HEATH, SURREY Tel. 01-684 1665
LOUDSPEAKERS CATALOGUE AND ENCLOSURE PLAN 5p

Which of these 165 career opportunities could earn you £10... £15...even £30 extra a week?

How to qualify in your spare time for a better job

Make yourself *worth* more and you'll earn more. It's as simple as that. There are always plenty of people to do the routine work - but, right now, key jobs are going begging for lack of suitably qualified men to fill them. *The basic qualification is technical know-how.* When you've got that, you're in demand - out in front.

Are you ambitious - willing to set aside about 60 minutes a day for home study? If you are, B.I.E.T. can give you the technical knowledge you need - change your entire future prospects.

It's easier than you think...

Make no mistake about it - you *could* do it. Most people have unused ability. A low-cost B.I.E.T. course helps you discover this hidden ability - makes learning enjoyable and so much easier than it used to be. The B.I.E.T. simplified study system gets results fast.

We've successfully trained thousands of men at home - equipped them for higher pay and better, more satisfying jobs, steered them safely through City and Guilds examinations - enabled many of them to put letters after their name.

With the help of B.I.E.T., you too could soon be on your way to better things.

OTHERS HAVE DONE IT — SO CAN YOU

Many of the successful B.I.E.T. students who get a recognised qualification never thought they had the brains to do it. But you don't need outstanding brain-power or talent - not even any special education. With enthusiasm, a little determination and a B.I.E.T. home training, ordinary, average ability will see you through. We've proved it over and over - *thousands* of times, in fact!

BEST VALUE FOR MONEY HE EVER OBTAINED.

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course" - *Student D.I.B., Yorks.*

HE GOT OUT OF A BAD JOB INTO ONE HE LOVED.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects" - *Student J.A.O., Dublin.*

HE MADE FOUR TIMES AS MUCH MONEY.

"My training with B.I.E.T. quickly changed my earning capacity and in the next few years, my earnings increased fourfold" - *Student C.C.P., Bucks.*

FREE 76-PAGE BOOK

can put you on the road to success through a B.I.E.T. Home Study Course. It's yours for the asking, without obligation. Post coupon for your FREE COPY TODAY!



ACT NOW - DISCOVER FOR YOURSELF

It costs no more than a stamp to find out how we can help you. Tick the subject that interests you. Then post the coupon (or write). We'll send you an interesting 76-page book that will open up for you a whole new world of opportunity - and it's FREE.

B.I.E.T., Aldermaston Court, Reading RG7 4PF.

In a job you really enjoy

Choose from this list

- | | | |
|---|--|--|
| MECHANICAL
A.M.S.E. (Mech.) <input type="checkbox"/>
C & G Agric. Mechanics <input type="checkbox"/>
Diesel Eng. <input type="checkbox"/>
Eng. Inspection <input type="checkbox"/>
Eng. Metallurgy <input type="checkbox"/>
Inst. Eng. & Tech. <input type="checkbox"/>
Inst. Motor Ind. <input type="checkbox"/>
Mainten. Eng. <input type="checkbox"/>
Mechanical Eng. <input type="checkbox"/>
Sheet Metal Work <input type="checkbox"/>
Welding <input type="checkbox"/> | DRAUGHTSMANSHIP
A.M.I.E.D. <input type="checkbox"/>
Design of Elec. Machines <input type="checkbox"/>
Die & Press Tool Design <input type="checkbox"/>
Electrical Draughtsmanship <input type="checkbox"/>
Gen. Draughtsmanship <input type="checkbox"/>
Jig & Tool Des. <input type="checkbox"/>
Techn. Drawing <input type="checkbox"/> | Constructional Engineering <input type="checkbox"/>
Construction Surveyors Institute <input type="checkbox"/>
Clerk of Works <input type="checkbox"/>
Geology <input type="checkbox"/>
Health Eng. <input type="checkbox"/>
Hydraulics <input type="checkbox"/>
Inst. of Builders <input type="checkbox"/>
Inst. Works & Highway Sup. <input type="checkbox"/>
Painting & Dec. <input type="checkbox"/>
Public Hygiene <input type="checkbox"/>
Road Engineer. <input type="checkbox"/>
Structural Eng. <input type="checkbox"/>
Surveying <input type="checkbox"/> |
| ELECTRICAL & ELECTRONIC
A.M.S.E. (Elec.) <input type="checkbox"/>
C & G Agric. Mechanics <input type="checkbox"/>
C & G Elec. Eng. <input type="checkbox"/>
C & G Elec. Inst. <input type="checkbox"/>
C & G Elec. Tech. <input type="checkbox"/>
Computer Elect. <input type="checkbox"/>
Elec. Maths <input type="checkbox"/>
Elec. Science <input type="checkbox"/>
Electronic Eng. <input type="checkbox"/>
Electrical Eng. <input type="checkbox"/>
Install & Wiring <input type="checkbox"/> | RADIO & TELE-COMMUNICATIONS
Colour TV <input type="checkbox"/>
C & G Radio TV <input type="checkbox"/>
Electronics <input type="checkbox"/>
C & G Telecomm. <input type="checkbox"/>
Tech. <input type="checkbox"/>
Prac. Radio Elec. (with kit) <input type="checkbox"/>
Radio Amateurs Exam. <input type="checkbox"/>
Radio Servicing & Repairs <input type="checkbox"/>
Radio & TV Eng. <input type="checkbox"/>
Trans. Course <input type="checkbox"/>
TV Main. & Serv. <input type="checkbox"/> | GENERAL
Council of Eng. Inst. <input type="checkbox"/>
Farm Science <input type="checkbox"/>
General Educat. <input type="checkbox"/>
Gen. Plastics <input type="checkbox"/>
Pract. Maths <input type="checkbox"/>
Pract. Slide Rule <input type="checkbox"/>
Pure & Applied Maths <input type="checkbox"/>
Refrigeration <input type="checkbox"/>
Rubber Tech. <input type="checkbox"/>
Sales Engineers <input type="checkbox"/>
Tech. Report <input type="checkbox"/>
Writing <input type="checkbox"/>
Timber Trade <input type="checkbox"/>
University Ent. <input type="checkbox"/> |
| MANAGEMENT & PRODUCTION
Auto. Control <input type="checkbox"/>
Computer Prog. <input type="checkbox"/>
Electronic Data Processing <input type="checkbox"/>
Estimating <input type="checkbox"/>
Foremanship <input type="checkbox"/>
Inst. Cost & Man. <input type="checkbox"/>
Accountants <input type="checkbox"/>
Inst. Marketing <input type="checkbox"/>
Management <input type="checkbox"/>
Metrication <input type="checkbox"/>
Motor Trade Man. <input type="checkbox"/>
Network Plan. <input type="checkbox"/>
Numerical Cont. <input type="checkbox"/>
Operational <input type="checkbox"/>
Research <input type="checkbox"/>
Personnel Man. <input type="checkbox"/>
Planning Eng. <input type="checkbox"/>
Production Eng. <input type="checkbox"/>
Quality Control <input type="checkbox"/>
Salesmanship <input type="checkbox"/>
Storekeeping <input type="checkbox"/>
Work Study <input type="checkbox"/>
Works Management <input type="checkbox"/> | AUTO & AERO
Aero Eng. <input type="checkbox"/>
A.M.I.M.I. <input type="checkbox"/>
A.E.C. Cert. <input type="checkbox"/>
Auto Engineer. <input type="checkbox"/>
Auto Repair <input type="checkbox"/>
C & G Auto. Eng. <input type="checkbox"/>
Garage Management <input type="checkbox"/>
MAA/IMI Dipl. <input type="checkbox"/>
Motor Vehicle Mechanics <input type="checkbox"/> | CONSTRUCTIONAL
A.M.S.E. (Civil) <input type="checkbox"/>
Architecture <input type="checkbox"/>
Building <input type="checkbox"/>
Building Drawing <input type="checkbox"/>
Build. Foreman <input type="checkbox"/>
C & G Agric. Mechanics <input type="checkbox"/>
Carpentry & Join. <input type="checkbox"/>
Civil & Municipal <input type="checkbox"/>
Engineering <input type="checkbox"/> |

PLUS 58 'O' & 'A' LEVEL GCE SUBJECTS

tick here

Coaching for many major exams, including C & G and assistance in OXCI/HNC.

IT PAYS TO BE QUALIFIED! POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Aldermaston Court, Reading RG7 4PF **QK** **BPE00**
Please send full details and FREE 76-Page Book, without obligation.

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____ AGE _____

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY



Published approximately on the 15th of each month by IP Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand: Gordon & Gotch (A/S) Ltd.; South Africa: Central News Agency Ltd.; Rhodesia and Zambia: Kingstons Ltd.; East Africa: Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2.65 (£2.13.0). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's

BUILD THE TEXAN

YOUR COMPLETE AUDIO-ELECTRONIC STORES

More of everything at the right price. All your electronic requirements within 200 yards - call and see for yourself.

★ FREE TEAK CASE with complete kits!

FEATURES: New slim design with 6 ICs, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardners low field slim line transformer. Fibre glass PC panel. Complete chassis work.


HIGH QUALITY & STABILITY ARE PREDOMINANT FEATURES—DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES: On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, Input selector: Mag. P.U. Radio Tuner, Aux. Can be altered for Mic, Tape, Tape head etc. (Parts list Ref. 20 on request). Constructional Details Ref. No. 21. 30p.

SPECIAL KIT PRICE **£28.50** P. & P. 45p **COMPLETE WITH FREE TEAK CABINET**

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

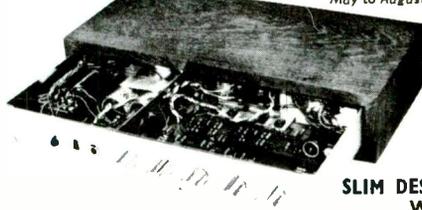(As featured in "Practical Wireless" May to August 1972)



SLIM DESIGN WITH SILVER TRIM

Overall chassis size 14 1/2 in. x 6 in. x 2 in. high

Designer approved kits distributed by Henry's!

ELECTRONIC KITS

Henry's introduce new huge range of audio and electronic kits now in stock, everything supplied, tremendous value. Detailed list Ref. No. 14 on request.

I.C. RECEIVER

ZN414 Radio integrated circuit as featured in Practical Wireless, January, 1973. Article reprint Ref. No. 19. 10p.

BATTERY TAPE DECK

Garrard 9V tape deck with heads, etc. As previously advertised. Limited quantity. £9.50. Post 30p.

LEARN A LANGUAGE

Recorded Cassettes with step by step phrase books. French, German, Spanish, Italian. £1.36 per course. £3.00 per set of four.

DISCO SPOTBANK

As illustrated on the front cover of Practical Wireless, April, 1973. £12.75. P. & P. 35p.

HI-FI EQUIPMENT

Warehouse prices with BIG DISCOUNTS plus DEMONSTRATIONS (for callers) and GUARANTEES.

FREE 24-page detailed brochure (Ref. No. 17). ★ You can see the savings ★

HIGH QUALITY CASSETTES

The best U.K. low noise tapes but at a special price. "Living Sound" cassettes meet the highest international standard (IEC94A). Fantastic price savings.

	C60	C90	C120
3 for	£1.00	£1.33	£1.62
6 for	£1.80	£2.57	£3.15
10 for	£2.80	£4.20	£5.00

Full guarantee. Post paid. Made by EMI especially for Henry's.

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and new I.C. circuits. PRICE PER PAIR £5.90. Post 10p.

MARRIOTT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO
 "17" High Impedance £2.00
 "18" Med. Impedance £2.00
 "36" Med.-Low Imp. £3.50
 Erase Heads for above 75p
 "63" 2 track mono - High Impedance £1.75
 "43" Erase Head for above 75p

7 SEG & NIXIE TUBES

(Post 15p per l to 6)
 XN3, XN13, GN6 0-9 side view with data, 85p.
 GNP.7, GNP.8 0-9 side view with decimal points and data, 95p.
 3015F 7 seg. £2 each, £7 per 4 with data.
 12 and 24 hour clock circuits. Ref. No. 31 15p.

MINIATURE AMPLIFIER

5 transistor. 300mW o/p. Fixed volume and sensitivity control 9 volt operated. £1.75 each, p.p. 15p.

QUALITY SLIDER CONTROLS

60mm stroke singles and ganged. Complete with knobs. 5kΩ, 10kΩ, 25kΩ, 100kΩ, 250kΩ, 500kΩ, 1 meg. Log and Lin. 40p each, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ, Log and Lin. ganged. 60p each.

LOW COST HI-FI SPEAKERS



E.M.I. Size 13 1/2 in x 8 in and Ceramic Magnet

TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.

TYPE 150TC Twin cone version £2.75. Post 22p.

TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.50. Post 25p.

TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.50. Post 28p.



POLISHED CABINETS 150, 150TC, 450 £4.60. Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 OHM)
SERIES 6 (Assembled 150TC) per pair £16.50. Post 70p.
SERIES 8 (Assembled 450) per pair £18.95. Post 70p.

ML3 MW/LW TUNER TO BUILD



Uses Mullard Module. Slow motion tuning. Built-in battery. Ferrite aerial. Overall size 7 in x 2 1/2 in x 3 1/2 in. TOTAL COST TO BUILD £4.85. Post 15p. All parts sold separately—Leaflet No. 6.

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave Bands plus Medium Wave Bandspread for extra selectivity. 600mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7.90, p.p. 32p (Batt. 22p).

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed. Post paid

PRICE 55p (40p FOR CALLERS)

PLUS! FIVE 10p VOUCHERS

Send to this address—Henry's Radio Ltd. (Dept. PE), 3 Albermarle Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303", see above.

TEST EQUIPMENT

Just a selection

- SE250B Pocket Pencil Signal Injector, £1.90
 - SE500 Pocket Pencil Signal Tracer, £1.50
 - THL33D Robust 2 K/Volt, £4.55; with case £4.95
 - TE15 Grid Dip Meter 440 KHz—280 MHz, £13.45
 - 500 30 K/Volt Multimeter, £9.25; with leather case, £10.50
 - 200H 20 K/Volt Multimeter, £4.20; with case £4.95
 - AF105 50K/V Multimeter, £8.50; with case, £9.50
 - U4341 AC/DC Multimeter with transistor tester with steel case, £10.50
 - TE20D RF Generator 120KHz—500MHz, £16.50. Carr. 35p
 - TE22D Audio Generator 20Hz—200KHz, £17.50. Carr. 35p
 - CI-3 3in Pulse Scope 10Hz—10MHz, £39.00. Carr. 50p
 - TE65 Valve Voltmeter 28 ranges, £17.50. Carr. 40p
- ALL NONBREM MODELS IN STOCK



BUILD THIS VHF FM TUNER

5 TRANSISTORS 300kc/s BANDWIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. TOTAL £6.97, p.p. 20p. Mki Decoder Kit £5.97. Built IC Decoder £6.50. Tuning meter unit £1.75.



Mains unit (optional) Model PS900 £2.47. Post 20p. Mains unit for Tuner and/or Decoder PS6/12 £3.25. Post 20p.

PA—DISCO—LIGHTING

- UK's Largest Range—Write phone or call in. Details and demonstrations on request.
- DJ30L 3 Channel sound to light unit, 3kV. £29.50
- DJ40L 3 Channel Mic (Built-in) to light, 3kV. £38.75
- DJ70S 70 watt Disco amp/mixer, £49.75
- DISCOAMP 100 watt Disco amp/mixer, £65.85
- DJ105S 30 watt Disco amp/mixer, £32.25
- Anti-Feedback Quality Mic, £11.50
- DJ500 50 watt PA amplifier, £43.95
- DJ700 70 watt £52.75
- DJ1000 100 watt £63.00
- Group 300 150 watt rms Group Valve amplifier, £86.00
- Portable discos—details on request
- Credit terms for callers



- FIBRE OPTICS
- LIGHTING MICS
- EFFECTS
- PROJECTORS
- SPOTS
- DIMMERS
- STANDS
- MIXERS
- SPEAKERS
- Everything for PA—Disco—Lighting.
- FREE Stock List Ref. No. 18.

SINCLAIR PROJECT 60 MODULES—SAVE POUNDS

- Z30 £3.57 Z50 £4.37
- STEREO 60 £7.97 PZ5 £3.97
- PZ6 £6.37 PZ8 £4.77.



Transformer for PZ8 £2.95.

- Active Filter Unit £4.45.
- Stereo FM Tuner £16.95.
- IC12 £1.80 Q16's £15 pair.
- Post, etc. 20p per item.

- PACKAGE DEALS Post 25p
- 2 x Z30, Stereo 60, PZ5 £15.95
- 2 x Z30, Stereo 60, PZ6 £18.00
- 2 x Z50, Stereo 60, PZ8 £20.25
- Transformer for PZ8 £2.95
- PROJECT 60S KIT £19.95

VAT All prices are exclusive of 10% VAT which must be added to all orders inc. carr./packing. (Note: Catalogue is not subject to VAT).

See earlier page of this magazine for transistors, I.C.'s and Semiconductor prices. Latest List Ref. No. 36 on request

E & OE

Henry's RADIO LIMITED
 EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
 354-356 High Fidelity and Tape Equipment 01-402 5854/4736
 309 PA-Disco-Lighting High Power Sound 01-723 6963
 303 Special offers and bargains store
 All mail to 303 Edgware Road, London W2 1BW

Open: 9 am-6 pm
 6 days a week
 (303 closed Thursday)
 All stores open all day Saturday