

PRACTICAL

ELECTRONICS

NOVEMBER 1973

20p

10p


FREE INSIDE! VEROBOARD

SUITABLE FOR THE CONSTRUCTION
OF ANY OF THE 4 PROJECTS
FEATURED IN OUR

8 PAGE 8 SUPPLEMENT

- LIGHT-OPERATED DEVICE
- WAA WAA
- DIODE THERMOMETER
- TOUCH SWITCH

STAGE LIGHTING DIMMER

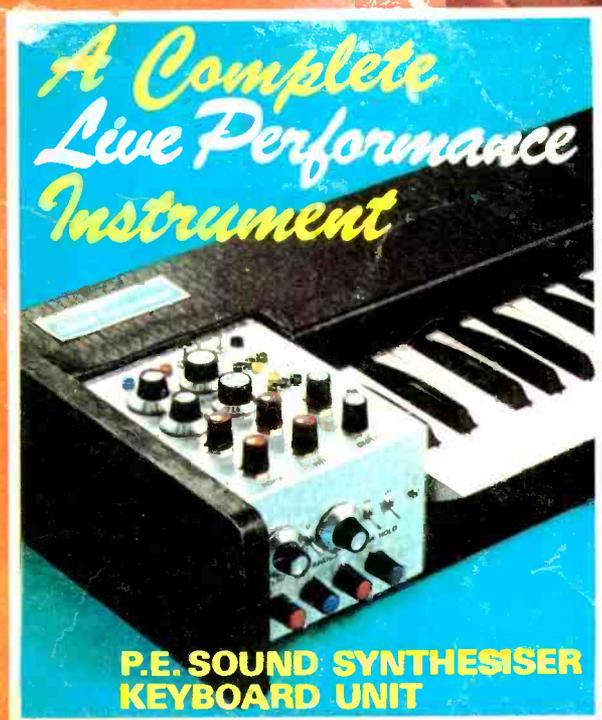

is this the price you pay?

Probably if you're still using an ordinary soldering iron Ordinary soldering irons can cause damage to transistors and integrated circuits - damage which wastes time and costs money. Now, with the unique ANTEX X25 and CCN low leakage soldering irons no harm can come to the most delicate equipment, even when soldered 'Live'.
(You could be making quite a saving).
All prices include V.A.T. at 10%



MODEL X25

220-240 Volts or 100-120 Volts.

The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C.

This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally-made 40 and 60 watt soldering irons, due to its unique construction advantages.

Fitted long-life iron-coated bit 1/8", 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed.

PRICE: £1.93 (rec. retail). P & P 8p.

Suitable for production work and as a general purpose iron.



MODEL CCN


220 volts or 240 volts. The 15 watt

miniature model CCN also has negligible leakage.

Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft.

Fitted long life iron-coated bit 3/32", 4 other bits available 1/8", 3/16", 1/4" and 3/64".

PRICE: £2.15 (rec. retail). P & P 5p.

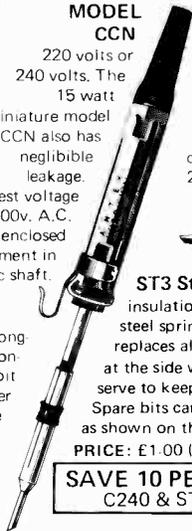

MODEL G - 18 watt miniature iron, fitted with long life iron-coated bit 3/32". Voltages 240, 220 or 110. **PRICE: £2.15** (rec. retail). P & P 5p.




MODEL C - Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 3/64" to 3/16". Voltages 240, 220, 110, 50 or 24. **PRICE: £1.93** (rec. retail). P & P 5p.




ST3 Stand - This stand is made from high grade insulation material with a chromium plated strong steel spring. It is suitable for all models and replaces all previous stands. The two sponges at the side which are easily replaceable, serve to keep the soldering bits clean. Spare bits can be accommodated as shown on the illustration.

PRICE: £1.00 (P & P 8p).

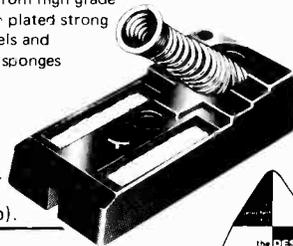

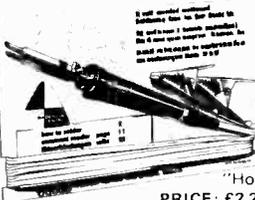
SAVE 10 PENCE X25 & ST3 or C240 & ST3 for £2.83 (P & P 13p).



MODEL MLX KIT

Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder"

PRICE: £2.27 (rec. retail). P & P 12p

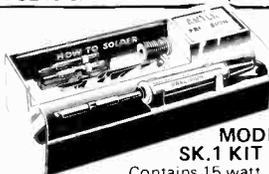

MODEL SK.1 KIT


Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE: £3.25 (rec. retail). P&P12p

MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.

PRICE: £2.97 (rec. retail) P & P 8p.

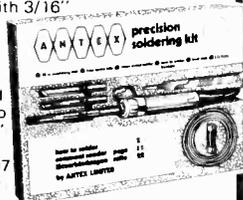

From radio or electrical dealers, car accessory shops or in case of difficulty direct from:-
ANTEX LTD. FREEPOST
(no stamp required) **PLYMOUTH**
PL1 1BR Tel: 0752 67377.

- Please send the ANTEX colour catalogue.
- Please send the following:

I enclose cheque/P.O./Cash (Giro No. 2581000)

NAME

ADDRESS

PRACTICAL ELECTRONICS

VOLUME 9 No. 11 NOVEMBER 1973

CONSTRUCTIONAL PROJECTS

- STAGE LIGHTING DIMMER** *by R. Liffen*
A four channel system for controlling 13kW of lighting 950
- P.E. RONDO QUADRAPHONIC SOUND SYSTEM—3** *by R. A. Cole*
Power supplies and main chassis details 956
- P.E. SYNTHESISER—10** *by G. D. Shaw*
Keyboard unit—Log Law Oscillators 964
- SEMICONDUCTOR TESTER—2** *by J. H. Perkin*
General purpose discrete semiconductor tester 982

GENERAL FEATURES

- LOGIC EXPERIMENTS—7** *by M. J. Hughes*
The half adder 963
- AUTOMATED MAIL** *by F. J. Morris*
Survey of electronics in the postal service 973
- NEW DEVICES . . . APPLICATIONS**
A four digit calculator using an LSI MOS integrated circuit 980
- PHASE LOCKED LOOPS—2** *by J. B. Dance*
Phase locked loops in f.m. and a.m. demodulators, and frequency synthesisers 989
- INGENUITY UNLIMITED**
P.S.U. protection—Servo amplifier—Car lights monitor 995

NEWS AND COMMENT

- EDITORIAL—Take Your Pick** 949
- SPACEWATCH** *by Frank W. Hyde*
Black Holes—Comet Kohoutek—Mars Vehicles 955
- ON THE FRINGE** *by Gerry Brown*
The more unusual aspects of electronics 960
- INDUSTRY NOTEBOOK** *by Nexus*
What's happening inside industry 986

SPECIAL SUPPLEMENT—AUTUMN QUICKIES

DIODE THERMOMETER—WAA WAA—OPTOELECTRONICS—TOUCH SWITCH

FREE INSIDE THIS ISSUE: VEROBOARD PRINTED WIRING BOARD

Our December issue will be published on Friday, November 9, 1973

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, to any part of the world, £2.65. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

Exciting...the Stereo 21!

Can you really get sound quality like this **FOR LESS THAN £19?** YES, YOU CAN! WITH THE NEW

STEREO 21

Until now, richly satisfying sound has always cost a richly satisfying price. *But not any more!* For an almost unbelievable **£18.45**, you can have Stereo 21—audio for the connoisseur! Whatever your taste in music, you can hear it on STEREO 21 the way its composers heard it in their dreams! Beethoven or Mahler... Ellington or Jellyroll Morton... Das Nibelung or Jesus Christ Superstar... Carols from King's College Chapel or the return of a Beatle... everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!



And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience!

Top-quality amplifier, BSR turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins all parts supplied including full instructions—all for £18.45 (plus the cost of post and packing if you buy by mail), and—to round it all off—a money refund if not satisfied if your pleasure in STEREO 21 is not complete!

Just think—in only a few days you could be giving your ears the treat of a lifetime—AND introducing your envious friends to STEREO 21!


Personal shoppers and mail order price
£18.45 INCLUDING VAT plus £1.50 p. & p.

Diamond stylus, if required, £1.37 extra
Suitable pair of stereo headphones with individual lever controls, if required £3.85.

EMI SPEAKERS AT UNBELIEVABLE PRICES

950 Kit. Five matched speakers and crossover unit for handling up to 45 watts, from 20 to 20,000 Hz. Huge—19in x 14in (approx.) high efficiency 16, 500-gauss bass unit built on a heavy diecast frame. The four 10,000 gauss tweeters, each 3½in dia. approx., are fed by the crossover with a critically adjusted signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2in others 0.5in. Recommended list price £44.

OUR PRICE £25.00 + £1.50 p. & p

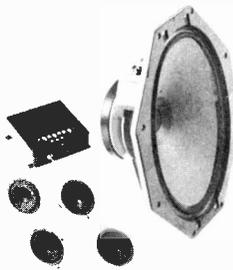

15in 14A/780. Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3in voice coil.

Recommended retail price £40.80.

OUR PRICE £18.70 + £1.50 p. & p.

Just write your order giving your credit card number. **DO NOT SEND YOUR CARD**



RADIO AND TV COMPONENTS (ACTON) LTD, 21C HIGH STREET ACTON, LONDON W3 6NG · 323 EDGWARE ROAD, LONDON W2

Edgware: 9 a.m. to 5.30 p.m., half day Thurs.
Acton: 9.30 a.m. to 5 p.m. Closed all day Wed.; also see opposite.
Mail orders to Acton. Terms C.W.O. All enquiries Stamped Addressed Envelope. Goods not despatched outside U.K.



RTVC VISCOUNT III

a boost in the output.

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as *value for money!* And that's something you get in abundance with VISCOUNT III. We design it... we make it... we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the magnificent Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back. And the teak finish will harmonise and enhance virtually any style of interior decor!

The heart-stopping timbre of Tom Jones at his most virile... the last lingering harmonics of a solo performance by Heifetz or Menuhin... the pathos and the panache of Liza Minelli... the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have *never* experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

SPEAKERS: Duo Type II Size approx. 17in x 10½in x 6½in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet £14.00 a pair, £2.20 p. & p. Duo Type III Size approx. 23½in x 11½in x 9½in. Drive unit 13½in x 8½in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

PRICES: SYSTEM 1

Viscount III R 102 amplifier	£24.20 + £1 p. & p.
2 Duo Type II speakers	£14.00 + £2.20 p. & p.
Garrard SP25 Mk. III with	
MAG. cartridge plinth & cover	£18.00 + £1.75 p. & p.
total	£56.20

Available complete for only £49.00 - £3.50 p. & p.

PRICES: SYSTEM 2

Viscount R 102 amplifier	£24.20 + £1 p. & p.
2 Duo Type III speakers	£32.00 + £3.30 p. & p.
Garrard SP25 Mk III with	
MAG. cartridge plinth & cover	£18.00 + £1.75 p. & p.
total	£74.20

Available complete for £65.00 + £4 p. & p.

STILL ONLY **£49** COMPLETE



THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles it covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2-5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.


Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modularised IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4½in deep.
* Circuit diagram and comprehensive instructions 55p free with parts.
* Fully retractable and lockable car aerial £1.37 post paid.

CAR RADIO KIT £6.60 p. & p. 55p


Speaker with baffle and fixing strips £1.65. 23p p. & p., post free if bought with the kit. Send stamped addressed envelope for leaflet.

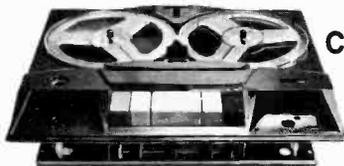If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.



PE TAPE LINK CONSTRUCTORS

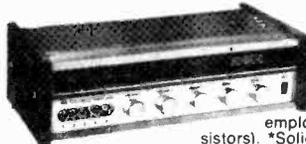Suitable 3 speed tape deck, **less heads.** Caters up to 5½ins. spools. 240V AC mains. Unused but store soiled hence no warranty. £1 p. & p. **£4.00**




RELIANT Mk IV £13.50

*5 Electrically mixed inputs. *3 Individual Mixing controls. *Separate bass and treble controls common to all 5 inputs. *Mixer employing F.E.T. (Field Effect Transistors). *Solid State Circuitry. *Attractive Styling.
INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram. Tuner, Monitor, Organ, etc.). All 250mV sensitivity. Output 20 watts into 8 ohms (suitable for 15 ohms). Size approx. 12½ x 6 x 3½ ins.
£13.50 p. & p. 60p.

UNISOUND MODULES

ONLY £7.64 + 55p p. & p.

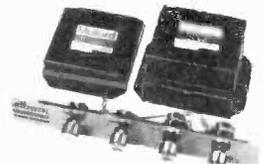For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.



IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. Mains operated.



The Viscount III, the fabulous Stereo 21 and the Unisound Modules will all accept this unit, **£10.60p. & p. 80p** simply connect up.

ALL PRICES INC. VAT

SEE OPPOSITE PAGE FOR ADDRESS DETAILS

Even Better All Round Sound Reproduction!



New, Improved BD2 Turntable By *Connoisseur*

Manufactured by:- A. R. Sugden & Co. (Engineers) Ltd.,
Atlas Mill Road, BRIGHOUSE, Yorkshire HD6 1ER.
Telephone: Brighouse (04847) 2142. Telegrams & Cables: Connoisseur, Brighouse.
Come and visit us at Stand No. F4 at the International Audio Festival

KEEP WARM AT A COOL PRICE.

Slash central heating costs with AMKIT.

If you can put in electric wiring, you can install Amkit. The unique nylon pipe hot water central heating system, that you install yourself in hours.

Look at these advantages:

- No soldering
- No 'T' junctions
- No special equipment
- No leaks, no lagging, no corrosion
- No structural upheaval

Just reliable, effective central heating (Guaranteed 25 years) at a saving of between £150 & £250. This famous system has been successfully marketed since 1968.

Clip the coupon, and we'll tell you more.

To Autocon Manufacturing Co.
Spring House, 10, Spring Place, London, NW5, 3BH
Please send your brochure telling me all about Amkit.

Name.....
Address.....

PE3



or see for yourself at: THE AMKIT D.I.Y. CENTRE,
15, Procter St., London, W.C.1. (opp Holborn Undgnd).
Open Mon-Fri 9.30 am-5.30 pm. Sat 9 am-1 p.m.

SPECIAL 40 MHz SCOPE—SOLARTRON CD1212 ONLY £50. Has to be a snag. There are no plug-in Y amps available.

TB—100 nanosecs per cm to 5 secs per cm in 24 calibrated ranges. 20 nanosecs per cm with times 5 expansion. Sin flat faced tube. Trace locator. 0.2 microsec signal delay. Built-in calibrator 1kHz square wave. 200 micro volts to 100 volts in 18 calibrated ranges. Tube sensitivity 3 V/cm. Main Frame Y Amp boosts this to better than 200 MV per cm at 40 MHz, 240V 50 Hz input. Complete with full manual including plug-in circuits. Come and see one working or Carriage £1.50. **MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH.** 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for ONLY £5.50. P. & P. 25p. (Not cased, not calibrated.)

NEW WIDE RANGE WOBBLATOR

5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for I/O-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V A.C. and use within minutes of receiving. All this for ONLY £5.75p. P. & P. 25p. (Not cased, not calibrated.)

20 Hz to 200 kHz WB.

SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermistor stabilised. Ready to use, 9V supply required. £7.85 each. P. & P. 25p (Not cased, not calibrated.)

GRATICULES. 12cm x 14cm high quality plastic 15p each. P. & P. 5p. 12" Long Persistence CRT, full spec. Price £12.50 to include V.A.T. & carr.

COMPONENT PACK consisting of 5 pots, various, brand new; 250 resistors $\frac{1}{2}$ and $\frac{1}{4}$ watt, many high stabs, etc. Fine value at 50p. P. & P. 17p.

P.C.B. PACKS 5 & D. Quantity 2sqft —no tiny pieces. 50p plus P. & P. 20p. **FIBRE GLASS** as above £1 plus P. & P. 20p.

5 CRYSTALS 70 to 90kHz. Our choice, 25p. P. & P. 15p.

5 MOVING COIL METERS various £2. P. & P. 37p.

CAPACITOR PACK—50 Brand new components only 50p. P. & P. 17p.

POTS—10 different values. Brand new—50p. P. & P. 17p.

TRIMMER PACK. 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, 25p the lot. P. & P. 10p.

FLAT FACED 4" Twin Beam Tube, type CV2193. Green trace. Brand new £4 each. P. & P. 37p.

LIGHT EMITTING DIODES (Red) from Hewlett-Packard. Brand New 38p each. Holder 1p each. Information 5p.

PHOTOCELL equ. OCP71, 13p each.

PHOTO RESISTOR type Clare 703 Two for 50p.

MODERN TELEPHONES type 706. Two-tone grey, £3.75 each. The same but black, £2.75 each. P. & P. 25p each.

Also **TOPAZ YELLOW** £4.50 each. P. & P. 25p.

IDEAL EXTENSION Telephones with standard GPO type dial, bell and lead coding. £1.75 each. P. & P. 25p.

DELIVERED TO YOUR DOOR 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.

PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 6.30 p.m. ANY DAY


CHILMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech. College) Tel.: Reading 502605/65916



I.L.P. (Electronics) Ltd

100 WATTS!

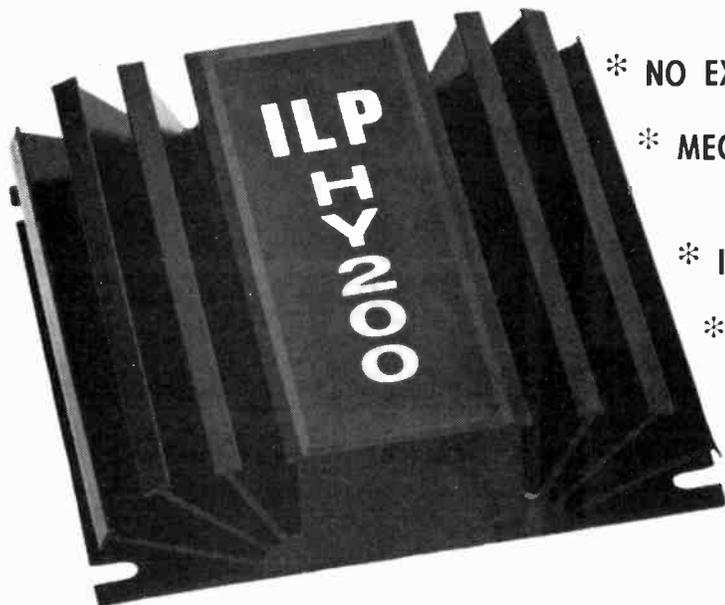

- * NO EXTERNAL COMPONENTS
- * MECHANICALLY & ELECTRICALLY ROBUST
- * INTEGRAL HEATSINK
- * HERMETICALLY SEALED UNIT
- * ATTRACTIVE APPEARANCE
- * LOW COST
- * BRITISH BUILT

With the development of the HY200, ILP bring you the first **COMPLETE** Hybrid Power Amplifier.

COMPLETE: because the HY200 uses no external components!

COMPLETE: because the HY200 is its own heatsink!

By the use of integrated circuit technique, using 27 transistors, the HY200 achieves total component integration. The use of specially developed high thermally conductive alloy and encapsulant is responsible for its compact size and robust nature.

The module is protected by the generous design of the output circuit, incorporating 25amp transistors. A fuse in the speaker line completes protection.

Only 5 connections are provided, input, output, power lines and earth.


OUTPUT POWER: 100 watts RMS; 200 watts peak music power. **INPUT IMPEDANCE:** 10k Ω . **INPUT SENSITIVITY:** 0Dbm (0.775volt RMS). **LOAD IMPEDANCE:** 4-16 Ω . **TOTAL HARMONIC DISTORTION:** less than 0.1% at 100 watts, typically 0.05%. **SIGNAL : NOISE:** better than 75Db relative to 100 watts. **FREQUENCY RESPONSE:** 10Hz-50KHz \pm 1Db. **SUPPLY VOLTAGE:** \pm 45volts. **APPLICATIONS:** P.A., Disco, Groups, Hi-Fi, Industrial. **PRICE:** £14.90 inc. VAT & P&P. Trade applications welcomed.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

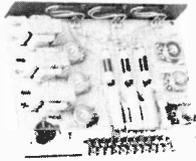Mk III Sound to Light Unit Chassis Version



The audio drive voltage is derived directly from the amplifier output or across the speaker load. The unit converts the audio-frequency signals into a three-coloured light display when used with coloured flood lamps or similar; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size: 9in x 7in x 3in. Price £27.50.


MN3 3 Channel I.C. Mixer Kit



Three channel I.C. audio mixer kit MN3 is specially designed for the home constructor or educational project. Suitable for use in domestic audio, discotheque and simple p.a. applications. The MN3 mixer kit has the following features: Advanced design using 5 ICs; Slider fader level controls mounted directly to p.c. board; Full range Bass and Treble controls; Uses top grade components with fibreglass ready-drilled and tinned printed circuit board and the unit may be operated from twin 9V batteries (PP3) if required.

As optional extras, an attractive ready-punched facia panel and control knobs are available. The unit is available as a ready built mixer with facia. Size: 9.5in x 4.8in x 1.5in (with facia). Construction manual available separately at 25p. Kit Price £11.

STL/I Single Channel Sound to Light Unit

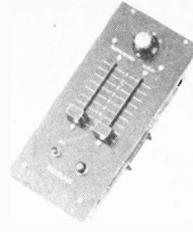


Single channel "Sound to Light" unit with 60mm slider fader controls for audio trigger level and background load dimmer. This unit is switchable for response to High, Mid. and Low frequency audio signals, selected by facia control. A D.J. "pulse-flash" push button is fitted for manual flashing of the lamp load together with neon load indicator. Maximum Load: 1kW at 240V a.c. Size: 8in x 3.6in x 3in. Price £14.30.

Practical Electronics "Scorpio" Electronic Ignition System Kit



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc. Case size: 7.25in x 4.5in x 2in approx. Complete assembly and wiring manual 25p. Price £12.10.

STL/3 Sound to Light Unit

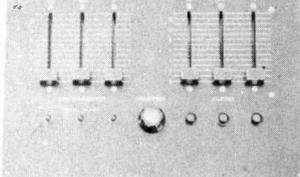

The performance of this unit is similar to the Mk III chassis version above, but is provided with an attractive black anodised facia panel and designed to mount directly into equipment desks or cabinets. High, Mid. and Low frequency channel sensitivity controls employ 60mm slider faders for present-day attractive appearance and ease of use. Size: 11in x 8.5in x 4in. Price £42.35.

AUDIO EFFECTS

CREATE "PHASE" EFFECT ON YOUR RECORDS-TAPES, ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9V BATTERY (not supplied). COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD AND FULL INSTRUCTIONS. KIT PRICE £2.86.

All prices quoted include postage and VAT. S.A.E. for further details.

DABAR ELECTRONIC PRODUCTS
98 LICHFIELD STREET, WALSALL
STAFFS WS1 1UZ

become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free! Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
P.O. BOX 156, JERSEY

NAME: _____ ADDRESS: _____ EB 113

BLOCK CAPS please

CASED AMPLIFIERS



Polished wooden cabinet 14 x 13 x 9in with hinged lid containing a sensitive (20μV) 4 valve amplifier with tone and volume controls, giving about 3 watts output to the 7 x 4in 3Ω speaker. Also included

is a non-standard single motor tape deck. Easily converted to record player, guitar practice, baby alarm, etc. Supplied in good working condition with circuit diagram. Mains operated. Only £3 (£1 up to 200 miles, £1.20 over). Special cassettes, £1 (25p). Spare heads, 40p. Damaged machines from £1.50 to callers only. Discounts on quantity. Amplifier chassis, 2 x ECC83, EL84, EZ80, £1.65 (35p).

71b BARGAIN PARCELS

Hundreds of new components—capacitors, resistors, switches, crystals, pots, PC boards, etc., etc. Outstanding value, £1.65 (37p). **COMPUTER PANELS:** Type E: 4 OC29, 4 ACY19, 8 other transistors, 35 diodes, etc., £1 (10p). Type H: 12 ASZ20+176 R's, C's & D's, 60p (10p). Parcel of 12 top quality boards, inc. power transistors, trimpots, IC's, etc., £2 (25p); 100 for £15 (£1); 1,000 £75 (£3); 3lb of lower quality, £1 (25p); 7lbs, £2 (40p); 56lbs, £12 (c.p.d.). Pack of boards containing at least 500 components including 50 transistors, 60p (15p).

NEW COMPONENTS: 741C TO99 or 8 pin DIL, 32p; BC107-9, 8p or 14 for £1; 2N3055, 35p; 10+, 32p; 50+, 29p. OC140 25p; OC170 15p; BFY18 12p; BCY72 8p.

PANEL METERS: Clearing 200 meters from 10p each to callers only. Oscilloscopes available, also lots of odd units for spares. TF144G sig. gen. 85kHz-25MHz, from £12-£22. Oscilloscopes available: CD71152 from £35. CD1212, etc. BFO No. 8 audio oscillator 50Hz-20kHz, £10. 10x crystals, 25 asstd., 75p (25p); 4p8w switches, 40p (10p); 2-8pF beehive trimmers, 5p; 3 x 2 1/2in 15A thermocouple meters, £1 (10p); delay line unit, operating around 1MHz with 7 transistor amplifier. Short delay, 40p; long delay, 60p (10p each). 1MΩ pots, 5p. 500 asstd. resistors £1 (15p); 20,000 £25 (£1); 100,000 £80 (£2); 300 asstd. capacitors £1 (25p). Post in brackets, small parts 3p. VAT NOT INCLUDED—ADD 10% TO TOTAL. S.A.E. list, enquiries.


GREENWELD ELECTRONICS (PE5)

All mail to 24 Goodhart Way, West Wickham, Kent, BR4 0ES. Shop at 21 Deptford Broadway, SE8 (next to old cinema). Tel. 01-692 2009. Callers most welcome. Also 38 Lower Addiscombe Road, Croydon.

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN - PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loud-speaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio.
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier
- Parts price list and plans 40p (free with parts)
- *10 Transistors
- *3 1/2" Loudspeaker

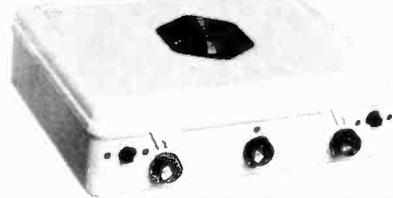

TOTAL BUILDING COSTS

£7-23 P.P. & INS. 44p
(+10% VAT 72p) (OVERSEAS P.P. £1-85p)

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW.


Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange. Attractive all white case with red grille and carrying strap. Size 9 1/2in x 7in x 2 1/2in approx. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£6-95** P.P. & INS. 44p
(+10% VAT 69p) (OVERSEAS P. & P. £1-85)



POCKET FIVE

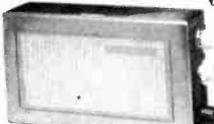3 Tunable wavebands, MW/LW and Trawler Band, 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker, attractive Black and Gold Case. Size 5 1/2in x 1 1/2in x 2 1/2in approx. Plans and parts price list 15p (FREE with parts).



Total Building Costs **£2-28**
(+10% VAT 25p) P.P. & Ins. 24p (OVERSEAS P. P. £1-25)



Total Building Costs **£2-50** P.P. & Ins. 25p
(+10% VAT 26p) (OVERSEAS P. & P. £1-25)

TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 16p (FREE with parts).

TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW. and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£4-48** P.P. & INS. 33p
(+10% VAT 44p) (OVERSEAS P. & P. £1-25)

ROAMER SIX 6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS **£3-98** P.P. & IN. 31p
(+10% VAT 39p) (OVERSEAS P. & P. £1-85)

NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9in x 4 1/2in x 2 1/2in approx. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£2-73** P.P. & INS. 30p
(+10% VAT 27p) (OVERSEAS P. & P. £1-25)

EV6 Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, loudspeaker, etc. MW/LW coverage. Push Pull Output. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£3-60** P.P. & INS. 30p
(+10% VAT 36p) (OVERSEAS P. & P. £1-25)

EV7 Case and looks as above. 7 transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. Parts price list and easy build plans 20p. Free with parts.

TOTAL BUILDING COSTS **£4-08** P.P. & INS. 31p
(+10% VAT 40p) (OVERSEAS P. & P. £1-85p)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch, 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6-98** P.P. & INS. 47p
(+10% VAT 69p) (OVERSEAS P. & P. £1-85)



ROAMER TEN WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS, 9 TUNABLE WAVE BANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND. Latest 4 1/2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Fine tone moving coil speaker. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£8-50** P.P. & INS. 52p
(+10% VAT 85p) (OVERSEAS P. & P. £1-85)

Components include: Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine tone moving coil Speaker; Terminal Strip; Ferrite Rod Aerial; 2 Plugs and Sockets; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three 1/2in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£5-50** P.P. & INS. 33p
(+10% VAT 56p) (OVERSEAS P. & P. £1-85)

EDU-KIT

Build Radios, Amplifiers, etc., from easy stage diagrams.



Five units including master unit to construct.

TOTAL BUILDING COSTS **£5-50** P.P. & INS. 33p
(+10% VAT 56p) (OVERSEAS P. & P. £1-85)

RADIO EXCHANGE LTD

*Callers side entrance "Lavelle" shop
*Open 10-1. 2.30-4.30. Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52367 Reg. No. 788372

I enclose £ _____ for _____
Name _____
Address _____

P.E.57

NEW VAT INCLUSIVE PRICES

OVERSEAS CUSTOMERS DEDUCT ONE ELEVENTH.

74 Series TTL

INTERNATIONALLY KNOWN BRANDS
1st GRADE DEVICES AT NEW
ROCK BOTTOM PRICES

SN7400	16p	SN7473	40p
SN7401	16p	SN7474	40p
SN7402	18p	SN7475	50p
SN7410	17p	SN7476	44p
SN7413	30p	SN7490	69p
SN7420	16p	SN7492	74p
SN7447	99p	SN7493	74p

This range will be increased continuously. Please enquire about any devices not listed.

PRICE BARRIER SLASHED

LED READOUTS

0.3in high characters 14pin Oil



Ref LED 1

£1.99 + 20p VAT = £2.19

Veroboard



Copperclad Plain Extra		0.1in	0.15in	0.15in P & P
2 1/2in x 1in	61p	61p	—	—
2 1/2in x 3 1/2in	22p	18p	11p	—
2 1/2in x 5in	26p	23p	13p	—
3 1/2in x 5in	26p	23p	—	—
3 1/2in x 5in	30p	30p	19p	—
17in x 2 1/2in	74p	55p	47p	10p
17in x 3 1/2in	99p	77p	51p	10p
17in x 5in	—	—	82p	10p

DIP Breadboard, 4.15in x 6.15in, 110p.
Verostrip, 8.5in x 1.5in, 26p. Spot-Face Cutter, 40p. Pin Injection tool (state 0 pins or 0.15in), 52p. Terminal pins, 20p (pack of 36)—state size.

I.C. SOCKETS



Dual-in-Line	
8 pin 13p	16 pin 17p
14 pin 15p	24 pin 26p
—	36 pin 39p
—	40 pin 44p
—	28 pin 30p

HEAT SINKS

TV2 for TO-66 15p. 5F for TO-5
TV3 for TO-3 16p. 18F for TO-18



DIP10 2 for SL403D
DIP14/5 for EA1,000



10DN400 4 4Y-1 4



46p 35p



46p 35p

BRIDGE RECTIFIERS



P.I.V	1 amp	R.M.S	2 amp
100V	20p	50V	35p
200V	22p	100V	40p
600V	25p	200V	45p
1000V	38p	400V	50p

RECTIFIERS

P.I.V	1 amp	3 amp
50	1N4001 61p	1N5400 15p
100	1N4002 71p	1N5401 16p
200	1N4003 9p	1N5402 17p
400	1N4004 9p	1N5404 22p
600	1N4005 11p	1N5406 26p
800	1N4006 13p	1N5407 30p
1000	1N4007 16p	1N5408 33p

BY100	16p	BY133	23p
BY103	22p	BY164	55p
BY105	16p	BY176	£1.65
BY126	16p	BY182	£1.65
BY127	16p	BY250	25p

OR

FILAMENT INDICATOR
MINITRON 3015F 6 G



at BREAKTHROUGH
PRICE £1.49

Cheapest Opto yet GaAsp LED's



LED 2. 0.125"	26p
LED 3. 0.175"	17p
LED 4. 0.125"	69p
LED 5. 0.175"	75p

Remember **Vat Inclusive Prices**

DIGITAL CLOCK



on a chip

Just imagine, one MOS LSI I.C. eliminating 15 MSI I.C.'s and numerous other components. Either:

12 or 24 hour, 4 or 6 digit
50 or 60Hz operation
leading zero suppression
single voltage supply
similar to DIGITRONIC in
P.W. March 1973.

Only £7.99

With 4 LED's £16.59
With 6 LED's £20.75

CHROMASONIC electronics

RESISTORS

Rating	Type	Tolerance	Range	Price Each
1/4 watt	Metal Glaze	±5%	E12 Series 51Ω to 100KΩ	5p
1/4 watt	Carbon Film	±5%	E24 Series 51Ω to 330KΩ	1p
1/4 watt	Metal Oxide Film	±2%	E24 Series 10Ω to 1MΩ	41p
1/4 watt	'Cermet' Thick Film	±2%	E12 Series 56Ω to 150KΩ	8p
1/4 watt	Carbon Film	±5%	E24 Series 10Ω to 10MΩ	11p
1/4 watt	Carbon Composition	±0.5Ω	2.2Ω, 2.7Ω, 3.3Ω, 3.9Ω, 4.7Ω	41p
1 watt	Carbon Composition	±0.5Ω	5.6Ω, 6.8Ω, 8.2Ω	51p
1 watt	Carbon Film	±10%	E12 Series 10Ω to 10MΩ	3p
2 watt	Carbon Film	±5%	E12 Series 10Ω to 10MΩ	6p
2 1/2 watt	Wire Wound	±5%	E12 Series 0.22Ω to 0.47Ω	10p
2 1/2 watt	Wire Wound	±10%	E12 Series 1Ω to 270Ω	10p
5 watt	Wire Wound	±5%	E12 Series 0.5Ω to 8.2KΩ	10p
10 watt	Wire Wound	±5%	E12 Series 0.5Ω to 6.8KΩ	11p
10 watt	Wire Wound	±5%	10KΩ, 15KΩ, 20KΩ, 25KΩ, 33KΩ	17p
15 watt	Wire Wound	±5%	10Ω to 6.8KΩ	13p

DISCOUNTS: 10% on any 100 or more mixed value or wattage. 25% on any 100 or more same value and same wattage.

CAPACITORS

MULLARD C333, 629 and 630 series
—Ceramic Plate E12 series from
1.8pF to 0.022μF, 5p.

CERAMIC DISC—LOW VOLTAGE—
0.01μF, 0.022μF, 0.047μF, 5p;
0.1μF, 0.22μF, 0.47μF, 6p.

POLYSTYRENE (160V)—From 10pF
to 0.01μF in multiples of 10pF, 15pF,
22pF, 33pF, 47pF and 68pF, 3p.

MYLAR PLATE (100V)—1000 pF,
2000pF, 5000pF, 2p, 0.01μF, 0.02μF,
0.04μF, 0.05μF, 3p; 0.068μF, 0.1μF,
5p; 0.2μF, 6p.


MULLARD C280 (250V POLYESTER)
—0.01μF, 0.015μF, 0.022μF,
0.033μF, 0.047μF, 3p; 0.068μF,
4p; 0.1μF, 0.15μF, 4p; 0.22μF,
5p; 0.33μF, 7p; 0.47μF, 9p; 0.68μF,
12p; 1.0μF, 14p; 1.5μF, 22p;
2.2μF, 26p.

new

stabilised

POWER PACK/CONVERTER

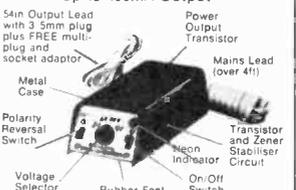Switched 3, 6, 7.5 or 9 volts.
Up to 400mA Output



Our Price £3.99 + P. & P. 16p.
Unstabilised Version of above
Other Eliminators (unstabilised)*

6 volts at up to 50mA	£1.65
9 volts at up to 50mA	£1.65
9 volts (miniature) up to 50mA	£2.09
6 + 6 volts at up to 50mA	£2.75
9 + 9 volts at up to 50mA	£2.75
7 1/2 volts for Cassette Players (small)	£2.20
3, 4, 6, 7.5, 9, 12 volts at up to 400mA	£3.75

Fully Stabilised* Car Battery Converter, giving switched outputs of 6, 7.5 or 9 volts

P. & P on all models 16p. £5.49

TRANSISTORS AND DIODES

AC107	16p	AF179	71p	BC214L	11p	BF177	28p	BSX20	18p	TC44	46p
AC126	13p	AF239	41p	BC268	15p	BF178	29p	BSX21	22p	TC28D	81p
AC127	13p	AF236	33p	BC327	26p	BF179	33p	BSY9SA	13p	TP141A	87p
AC128	13p	BC107	18p	BC328	24p	BF180	33p	BU105	£1.75	TP42A	99p
AC176	15p	BC108	10p	BCY70	17p	BF181	35p	BU105.02	£1.92	TS43	—
AC187	22p	BC109	10p	BCY72	17p	BF184	27p	D13V	53p	TS73	£2.10
AC187K	20p	BC114	15p	BCZ10	28p	BF185	27p	MJ4000	£1.48	TS91	33p
AC188	22p	BC117	22p	BCZ11	28p	BF184	15p	MJ4010	£1.48	ZN697	16p
AC188K	20p	BC147	20p	BD137	57p	BF195	17p	OC240	33p	ZN1307	21p
ACV17	22p	BC148	9p	BD124	82p	BF196	16p	MJE2955	£1.82	ZN1708	16p
ACV18	21p	BC149	9p	BD131	82p	BF197	16p	MJE3055	£1.92	ZN914	24p
ACV19	25p	BC157	13p	BD132	83p	BF200	25p	MPP102	27p	ZN1302	20p
AD120	22p	BC158	22p	BD131/2 PR	£1.48	BF201	27p	MPP103	41p	ZN1303	26p
AD140	40p	BC159	14p	BD133	83p	BF244B	27p	MPP104	45p	ZN1304	24p
AD149	38p	BC168B	11p	BD135	42p	BF262	25p	MPP105	45p	ZN1305	24p
AD161	38p	BC169	12p	BD136	42p	BF263	25p	MPP106	49p	ZN1306	24p
AD162	38p	BC172	20p	BD137	57p	BF272	£1.21	OC240	33p	ZN1307	21p
AD161/2 PR	50p	BC172	17p	BD138	74p	BF390	37p	OC25	38p	ZN1308	27p
AF114	14p	BD174B	35p	BD139	75p	BF528	£1.01	OC36	38p	ZN1309	27p
AF115	14p	BC177	22p	BD140	91p	BFW10	67p	OC44	13p	ZN1613	22p
AF116	14p	BC178	20p	BD141	91p	BFW11	67p	OC45	13p	ZN1711	22p
AF117	14p	BC179	24p	BD202	£1.15	BFW87	38p	OC71	15p	ZN1953	52p
AF118	92p	BC182L	9p	BC203	£1.15	BFX29	43p	OC72	15p	ZN2160	£1.54
AF124	24p	BC183L	9p	BC204	£1.15	BFX30	37p	OC75	13p	ZN2219	41p
AF125	22p	BC184	9p	BF109	57p	BFX88	26p	OC81	21p	ZN2346	55p
AF126	22p	BC184L	9p	BF115	55p	BFY50	16p	OC83	22p	ZN2905	46p
AF127	22p	BC187	27p	BF160	25p	BFY51	16p	OC40	22p	ZN2924	46p
AF139	35p	BC212L	11p	BF167	27p	BR100	43p	OC170	27p	ZN2928 all	10p
AF172	35p	BC213L	11p	BF173	22p	BR139	44p	OC171	27p	ZN3053	22p

ZENERS

All 5% tolerance

BZ188	400mW, 3.3V to 33V	11p
1ZS, 1W, 3.3V to 100V		18p
BZ270, 2.5W, 7.5V to 75V		27p

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N.9 803 1685

"CRESCENT" BUBBLE LIGHT SHOW



A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour makes the music you produce more interesting and will appeal to the visual as well as the audio senses.

This budget system compares very favourably with the more sophisticated and much higher priced models. Specification—Projector: 150W, convection cooled, at 30ft the projected image = 16ft; Motor: 1 rev per 2 min. Liquid Wheel: 6in diameter multicolour. The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & can be purchased separately. A bargain—Projector with Motor ready for instant use, £15.6in Liquid Wheel, £5 = £20 + 75p carr.

TRI-VOLT BATTERY ELIMINATOR



Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2½in x 2½in x 3½in. Our Price £2.75 plus 10p P. & P. Same model suitably wired for the Philips Cassette £3 plus 10p P. & P.

TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. x 3½in. x 1½in. This converter supplies 6, 7½ or 9 volts and is transistor regulated. A real money saving device for £2.50 plus 10p P. & P.

MINI LOUSPEAKERS

2½in 80 ohm, 50p; 2½in 40 ohm, 50p. Please include 5p P. & P. on each L.S.

DIGITAL CLOCK KIT



24-hr. Nixie dig. clock kit. We supply: a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. £29.50 + 50p P. & P. Please send S.A.E. if you require more information.

V.A.T. From 1st April, 1973, will you please include on your Total (Goods plus Postage and Packing) Value Added Tax at the Standard Stated Rate.

200/250V MAINS RELAY

Heavy duty contacts, 2,500 Ω coil. All new and unused D.P.D.T. mains relays 50p + V.A.T. Carr. Free. Special quantity price: £40 per 100 relays.

STEREO/MONO HEADPHONE VOLUME CONTROL BOX



Plug stereo phones into this control box and you then incorporate a right and left hand volume control and a stereo/monoswitch. Complete with stereo jack plug and 2m cable. A bargain at £1. P. & P. 10p

TWO WAY STEREO ADAPTOR



Stereo Jack plug to two stereo free sockets, complete with 110mm cable. For connecting two stereo inputs into one. A bargain at 65p. plus 5p P. & P.

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U.BUILD.IT

We supply the three modules for you to build this Disco Group-P.A. amplifier into the cabinet of your choice.

- ★ THE POWER AMP MODULE TP100W 170W r.m.s. eq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm). £14.28, carr. 45p.
- ★ THE PRE-AMP MODULE Four control pre-amp, Vol., Bass, Treble, Middle controls. Designed to drive most amplifiers using F.E.T. first stage. £3.98, carr. 25p.
- ★ THE POWER SUPPLY MODULE PS100

is supplied complete with the mains transformer. £9.68, carr. 50p. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. If you purchase all three modules. £25, carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers.

EMI LOUSPEAKER 450



10W 13in x 8in ± two 2½in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-16 ohm imp. £3.75 plus 38p P. & P. each.

7in x 4in LOUSPEAKER



A top quality speaker ideal where small size is important. Manufactured by F.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1.60. Free postage on this item.

CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60 28p, C90 38p, C120 48p plus 5p P. & P.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT



Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) £18.50 plus 38p P. & P.

"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT




This fantastic little box approx. 4" x 3" x 2½" when connected to the output of a sound source from 1 to 100 watts produces a psychedellic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at £7.50 plus 10p.

LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier. £1.75 plus 13p P. & P.

If you require more information please send S.A.E.

RING BOARD PRINTED CIRCUITS

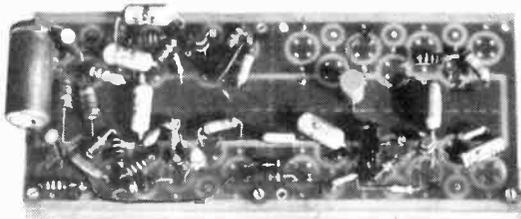

Photograph shows a circuit built on RING BOARD containing 42 components

RING BOARD is a fantastic new, quick and easy method to transfer an electronic diagram to a workable printed circuit. Normal price per full board, 55p. Special Opening Price 47p. Normal price per half board, 33p. Special Opening Price 26p. Normal price per quarter board, 22p. Special Opening Price 16p. RING BOARDS can be cut into half and quarter boards and still retain the same characteristics.

Full instructions of method with each RING BOARD purchased. RING BOARDS are:

1. Simple to use.
2. Little or no planning.
3. Positive and negative rails easily recognised.
4. Can be used with split voltage systems.
5. Build what you like when you like.
6. Neat and professional finish.
7. Flux varnished for easy soldering.

RING BOARD PRINTED CIRCUITS
259 Chesterfield Road, Sheffield S8 0RT

A CASE FOR "IMPEX"

Problem: I have a tuner, timer, mixer and digital clock for which I require suitable cases.
Answer: "IMPEX" Instrument Cases.

Problem: All the instruments are different sizes.
Answer: "IMPEX" have a standard range of 48 sizes.

Problem: I want them to be robust and stylish.
Answer: "IMPEX" cases were designed to be functional and attractive.


Problem: I don't think I could afford them; they sound expensive.
Final Answer: "IMPEX" cases are very competitively priced. Find out how they answer all your problems. Details from:

"IMPEX"
15 QUEENS STREET, NEWCASTLE UPON TYNE NE1 3UG

Dimmit

range of light dimmers

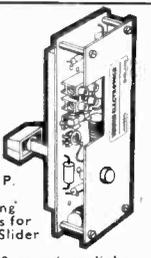Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer, linear operation, interference suppression, 60mm slider range; size 12½ x 4 cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £5.50 inc. VAT, add 10p P. & P. Also available in 2kW, with separate heatsink.



The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for use on lamps, heaters, motors, etc. Rotary and Slider control versions. Ratings: 400W, 1,000W, 2,000W.

NEW addition to Dimmit range—Model SL800 sound to light converter. Modulates the light in time with sound. Built-in microphone. Just place unit near any sound source—radio, hi-fi, tv, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Black A1 case—size 12 x 4.7cm. Full instructions. £6.50 inc. VAT, add 10p P. & P. Send 10p for complete illustrated catalogue and price list.

YOUNG ELECTRONICS Mail Order Dept.
54 Lawford Road, London NW5 2LN. Telephone 01-267 0201

YES, "YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS"! ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic ASTRAD 17 and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! THIS ONE SUPERSEDES ALL EARLIER MODELS! It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £18.50—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with £80 radios! *Send quickly, from receipt of goods test on mail order 7 day approval, refund if not delighted. Or call. Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra-perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of space-ship and satellite communications. Yes, EVERY WAVEBAND instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during the day including all normal transmissions. VHF, FM/USW, AM, LW, MW, SW, etc. locally, local & new stations not yet operational, an messages from all over the world! Expensive TURRET TUNER side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial! BUT WAIT! Take it only 7 days—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39in approx. It's also a fabulous CAR RADIO. Can also be used through extension amplifier, tape recorder or public address system. SIZE 13in x 10in x 4in overall approx. Magnificently designed in highly polished cases. Made to give years of perfect service. Purer & sweeter tone than ever. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With WRITTEN GUARANTEE, manual with simple operating instructions & circuit diagram. PLUS ultra sensitive earphone for personal listening. ONLY £18.50 (with mains/battery eliminator £2.25 extra). BOX, POST, ETC. 45p. NO MORE TUNING! BUT WAIT! For only 7 days you get the sensational! "COMPUTERISED" WORLD TUNING GUIDE (it enables you to zone and time in a flash for transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. NO GUESSING! NO MESSING!) PLUS Standard 'longlife' batteries and Converter Plug. (Sorry—We cannot change these new radios for any earlier model purchased.) Send quickly to Uxbridge Road address, or call at either Store. But HURRY! SHOPERTUNISIES SAVE YOU £££'s.

THOUSANDS OF MILES REDUCED TO INCHES? 1973 RUSSIAN RADIO TECHNOLOGY SHRINKS THE WORLD! *COMPUTERISED?

THIS FANTASTIC
EARTH SHRINKER

YES, 24,904 miles
SHRUNK TO ONLY 33 x 10 x 4 1/2
inches approx?

28 TRANSISTORS AND DIODES!
WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW, LW, USW.)

BATTERY MODEL £18.50 BOX POST ETC. 45p
MAINS/BATTERY ELIMINATOR £2.25 extra

BRAND NEW FABULOUS **ASTRAD 17**
PORTABLE RADIO & COMMUNICATIONS
RECEIVER



*MUST YOU PAY UP TO £80?

FIRST TIME EVER!
*NOW AVAILABLE WITH fabulous 'COMPUTERISED' WORLD TUNING GUIDE!
NO MORE GUESSWORK—INSTANT DATA at your fingertips—enables you to ZONE & TIME IN A FLASH for transmissions the world over!

THIS OFFER ONLY FROM US!

BUY ONE FROM US! **SAVE £23.03 NOW!**
fabulous BRAND NEW **SOLID STATE**
This equipment's got EVERYTHING!

BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER



WITH REMOTE CONTROL MICROPHONE

RECOMMENDED RETAIL PRICE
OUR PRICE £20.97 CARR. ETC. 50p

Shopertunities "thunder" ahead with an offer that's FANTASTIC (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous VHF, AM/FM Radio AND Cassette Tape Recorder & Player combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord). Record and play back anything, anywhere! IMPORTERS RECOMMENDED RETAIL PRICE £44! WE OFFER AT UNDER HALF PRICE! Wonderful features: * Press-button Keyboard Control Panel or latest MASTER SWITCH CONTROL! * "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! * Separate ON/OFF and HI-LO volume controls! * Heavy duty built-in speaker! * Earphone (for personal listening or monitoring) and extension speaker sockets! * Remote control microphone! * Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (DESIGNS VARY SLIGHTLY.) Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. AND the amazing built-in full circuit VHF, AM/FM Radio gives you superb CLARITY of tone, incredible station selection, Unique rotating Station Selector Dial—gets, locally, local city and regional stations in every part of the country, plus B.C. National, V.H.F. Picks up dozens of foreign stations. Fabulous in your car! You could pay £££'s more for a Car Radio or Car Cassette player ALONE! £20.97, carr. etc., 50p—NO MORE TO PAY! Complete with simple instructions, remote control microphone with on/off switch and microphone stand. WITH WRITTEN GUARANTEE. Send quickly, test on mail order 7 day approval from receipt of goods, refund if not delighted. Or call. BONUS OFFER: Batteries and Cassette Tape 28p extra if required. Callers: ACCESS & BARCLAY CARDS ACCEPTED AT BOTH STORES

FIRST TIME EVER! *SAVE £16.02!
BRAND NEW AC/DC BATTERY/MAINS

Cassette TAPE RECORDER & PLAYER

With remote control microphone.



FIRST CLASS MAKERS

WE COULD CHARGE UP TO £26.97!

OUR PRICE **£10.95** POST ETC. 50p

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW a superb de luxe portable BATTERY/MAINS tape recorder and player—and incredible Shopertunities bring it to you for ONLY £10.95. Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest MASTER SWITCH control) AND AUTOMATIC LEVEL CONTROL. No fiddling with awkward tape and reels, just "SLAP-IN" a cassette and off you go! (Takes 30, 60, or 90 minute standard cassette tapes obtainable everywhere.) Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful tone from a whisper to a roar! Complete—record anywhere, indoors or out! Runs on standard batteries AND 220/240V AC mains. Separate jacks for remote control microphone, etc. Size 9 1/2in x 5in x 2 1/2in approx. Design can vary slightly. With carry handle. WRITTEN GUARANTEE and full instructions. Importers (Recommended selling price £26.97) OUR PRICE ONLY £10.95, post, etc. 50p. NO MORE TO PAY! *Send quickly, from receipt of goods test on mail order 7 day approval—refund if not delighted. Or call at either of our stores. BONUS OFFER—Cassette tape, Standard batteries AND microphone stand 35p extra if required.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores.—(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn Store.)

SHOPERTUNITIES LTD.

Dept. PE/NC/32, 164 UXBIDGE RD. (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.

DISCOUNTS UP TO

60%

FULL 12 MONTH AFTER SALES SERVICE

with probably the best discounts offered in the U.K.

ALL PRICES ARE INCLUSIVE OF V.A.T.

FANTASTIC OFFER GARRARD SP25 Mk III.

Goldring G800. Teak finish, plinth and tinted cover with mains lead and DIN plug and screened lead. All fully wired. Please add £1-75 for P. & Ins. **£14-95**

TURNTABLES

Please add 95p P. & P. & Ins.

BSR MP60	£9-05
Garrard SP25 Mk.III	£9-25
Garrard SL65B	£12-75
Garrard AP76	£16-75
Garrard 401	£25-95
Garrard Zero 100 (single)	£37-45
Garrard Zero 100 (Auto)	£37-45
Goldring GL85/P. P. & C.	£59-30
Goldring G101/P. P. & C.	£19-75
Goldring GL72	£21-90
Goldring GL72/P	£28-50
Goldring GL75	£27-35
Goldring GL75/P	£32-95
Goldring GL75 Lid	£3-55
Goodmans TD100 P. & C. C800	£47-15
Cart	£59-95
Thorens TD125	£92-50
Thorens TD160 AB & C	£44-95
Thorens TD165-AB & C	£44-95
Wharfedale Linton with cart.	£25-50

TUNERS

Please add 95p P. & P. & Ins.

Alpha Highgate FT150	£32-95
Amstrad Multiplex 3000	£23-90
Lowther FM Mk 8 N/P	£42-75
Lowther FM Mk 9 N/P	£32-95
Metrosound FMS 20 Mk II	£37-75
Rogers R/brook FET 4 (Cha.)	£32-95
Rogers R/brook FET 4 (Cased)	£36-50
Sinclair PRO60 Mod	£14-90
Sinclair cased tuner	£25-30

Speakers

£1-65 for P. & P. (per pair)

Amstrad Acoustra 1500	£26-90
Amstrad Acoustra 2500	£30-75
Apollo 13B	£15-95
B & W DMS	£38-50
Celestion Ditton 15	£50-75
Celestion Ditton 44	£79-95
Goodmans D/Maxim	£39-70
Goodmans Mezo 3	£49-95
Goodmans Havant	£34-95
Keletron KS4	£13-95
Keletron KS8	£22-50
Sinclair Q16	£10-95
Sinclair Q30	£30-95
Wharfedale Denton II	£26-80

Speaker Units

Wharfedale Linton Kit	£16-85
Wharfedale Glendale Kit	£29-95
Goodmans Din 20 Kit	£14-75

Prices correct at time of going to press (E. & O.E.) and are subject to alterations.



GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE11), 174 Pentonville Road, London, N.1. Tel. 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue
Ilford, Essex. Tel. 01-550 1086

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

MAIL ORDERS. Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

AMPLIFIERS

Please add 95p P. & P. & Ins.

Amstrad 8000 Mk II	£15-85
Amstrad IC2000 Mk II	£34-85
Amstrad Integra 4000	£22-95
Alpha Highgate FA400	£32-25
Global 10 + 10	£19-75
Global 20 + 20	£25-95
Keletron 700	£19-25
Keletron 1500	£24-95
Metrosound ST20E Mk II	£29-45
Metrosound ST60	£49-70
Rogers R/brook (Ch.)	£41-15
Rogers R/brook Mk III (Ca.)	£44-35
Rogers R/bourne (Ch.)	£54-25
Rogers R/bourne (Ca.)	£56-75
Sinclair 2000	£24-00
Sinclair 3000	£30-50
Sinclair 605	£21-45
Sinclair PRO 60 2 x Z30/PZ5	£16-40
Sinclair PRO 60 2 x Z30/PZ6	£19-45
Sinclair PRO 60 2 x Z50/PZ8	£19-45
Trans.	£25-25
Sinclair AFU (Filter Unit)	£4-95
Sinclair Stereo 60 Pre-amp.	£7-35
Sinclair Z30 Amp.	£3-85
Sinclair Z50 Amp.	£4-50
Sinclair PZ5 Power Supp.	£4-20
Sinclair PZ6 Power Supp.	£6-15
Sinclair PZ8 Mains Trans.	£4-95
Sinclair PZ8 Power Supp.	£6-15

TUNER/AMPLIFIERS

Please add £1-10 P. & P. & Ins.

Alpha FR 3000	£61-35
Goodmans Module 80	£59-90
Goodmans Mod. 80 Com.	£106-50
Goodmans Mod. 90	£74-75
Goodmans One-Ten	£86-50
Rogers R/brook (Ch.)	£61-95
Rotel I50A	£45-25
Rotel 200A	£57-95
Wharfedale WE40 Receiver	£69-95

PLINTH & COVERS

£3-20




For Garrard SP25, 2025 TC, 3000, BSR, McDonald, MP60 £3-08 P. & P. 71p. For AP76, SL72B, SL95B, etc. £4-75 + 71p P. & P.

CARTRIDGES

Please add 11p P. & P. & Ins.

Goldring G850	£22-75
Goldring G800	£3-95
Goldring G800E	£6-35
Goldring G800SE	£11-00
Shure M3D	£3-30
Shure M44E	£4-45
Shure M55E	£5-00
Shure 75ED Type 2	£9-95
Shure V15	£28-00
Shure M75EJ Type 2	£8-15

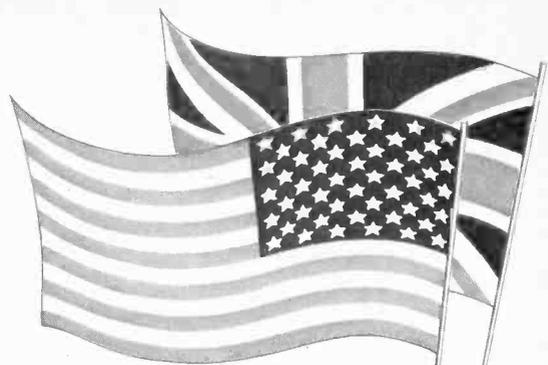

The leading U.K. & U.S.A. electronic Manufacturers use

ERSIN MULTICORE SOLDER

containing 5-cores of non corrosive extra active flux.

YOU TOO CAN USE THIS RELIABLE SOLDER

obtainable from your retailer. (ask for 'ERSIN MULTICORE')




Multicore Solders Ltd.

Maylands Avenue,
Hemel Hempstead, Hertfordshire, HP2 7EP
Tel: Hemel Hempstead 3636 Telex: 82363

PSYCHEDELIC LIGHTING UNIT IN KIT FORM

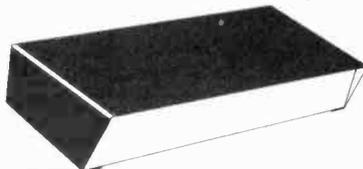Make this fascinating three-channel unit from a kit which contains all components needed to produce a reliable and entertaining display. Takes its drive from the speaker terminals of a record player, tape recorder or portable radio. Will provide a brilliant 2kW of light, using normal 240 volt coloured lamps. Price per kit, £10-40



METAL CABINETS

These attractive steel cabinets are PVC covered in a range of colours, and offer an economically priced unit for the home constructor. The chassis, which has a white satin PVC finish, provides an easily accessible building area, with an integral fascia panel. The cabinet is supplied complete with stick-on feet. Colours available include Green, Grey, Black, White and Blue. Every effort will be made to supply a selected colour, but please give alternatives if possible.

Approximate size in inches			Price
l.	w.	d.	
8	6	3	£1-60
11	6	3	£2-04

Other sizes to special order. HOLES PUNCHED in front or back panels to your own requirements. Please send S.A.E. for quotation.

FIXED VOLTAGE REGULATORS

TO3 case. Gives stabilised supply. MVR 5 V, MVR 12 V, MVR15 V. All priced at £1-65

VEROBOARD

2 1/2 x 1in	0-1	0-15
	7p	7p
2 1/2 x 3 1/2 in	27p	20p
2 1/2 x 5in	29p	29p
3 1/2 x 3 1/2 in	29p	29p
3 1/2 x 5in	31p	32p


PRINTED CIRCUIT CAPACITORS

Electrolytic, low voltage, small size. Available in the following uF/V. 0-47/63, 1/63, 2-2/63, 4-7/40, 10/63, 22/40, 100/10, 9p each; 47/40, 100/63, 220/40, 470/16, 15p each; 1,000/16, 18p each.

Our CATALOGUE, priced at 25p post free, shows the majority of the R.S. range of professional components. Most are available by return of post. Prices include VAT. All orders over 50p POST FREE. S.A.E. with all queries please.

CELECTRON-E

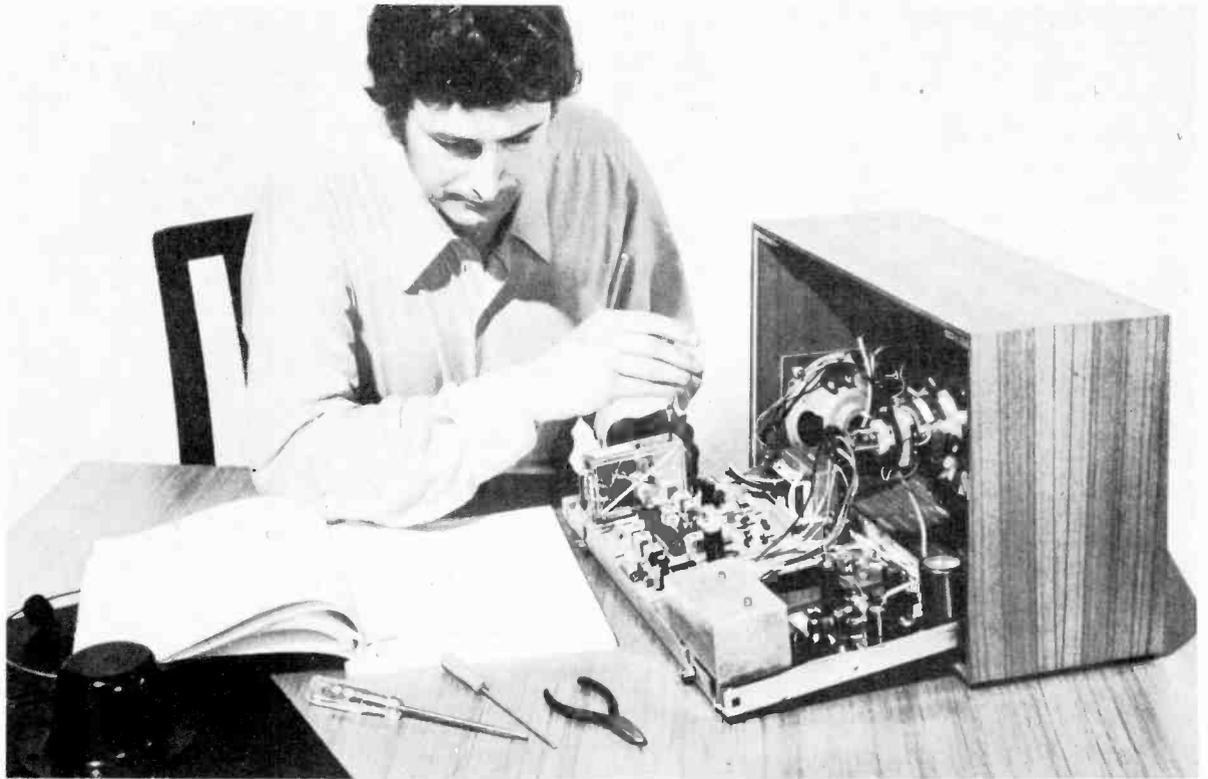P.O. Box No. 1, Llantwit Major, Glamorgan, Wales CF6 9YN



LEARN about MODERN TV Design by building this Heathkit 12" B/W Portable

on the new Heathkit GR-9900 portable 12" UHF Monochrome Television kit. A unique chance to double the pleasure available from any other television set — because you build this yourself.

We've used the latest modular construction and advanced design concepts to produce an outstandingly high performance TV worthy of the Heathkit name. All the main electronics are mounted on two easy-to-assemble printed circuit boards—this plus the use of no less than four integrated circuits perform the complex function of IF, video, sound, line frame and scan. Factory pre-aligned coils make alignment very easy and there are four presettable pushbutton controls for channel tuning—a luxury found in very few other models. The quality and fidelity is therefore excellent, and of a far higher standard than most ready-built televisions in the shops.

The GR-9900 is portable too—equally at home on

the mains or off your 12 volt battery for car, boat or caravan use. Add to this Heath's world renowned experience in the design of equipment for first-time kit builders, and you will be impressed on all counts of engineering, styling, and performance.

The instruction manual is surprisingly simple with big, clear illustrations to map out your way. Would-be TV engineer? Here's your chance to learn—by actually building a television yourself. The manual not only shows you how to get 100% personalised quality control on your own; in the event of anything going wrong, a Trouble-Shooting section enables you to find the fault—and, in most cases, to put it right unaided.

The GR-9900 is a kit you'll be proud to build and own. You have a choice of fully finished cabinets in teak or modern white and the kit price, £62.70 (carriage extra), includes a FREE high performance indoor aerial.

FREE Heathkit Catalogue

Contains something for everyone: Hi-Fi Stereo, Testers & Instruments, SWL, Metal Detectors... even a Battery charger Kit. Mail the coupon... Today!

Heath (Gloucester) Limited,
Gloucester GL2 6EE.

LONDON showroom
233 Tottenham Court Road
Tel 636 7349



Choose cash or Heath Monthly Budget Plan

(Mail order prices and specifications subject to change without notice)

Please send me a FREE Heathkit catalogue

Name _____

Address _____

HEATH

Schlumberger

Heath (Gloucester) Limited, Dept. PE/11/73
Gloucester GL2 6EE. Telephone 0452 29451

Henry's

UK'S LARGEST RANGE OF TRANSISTORS, IC'S RECTIFIERS, ALL SEMICONDUCTOR DEVICES
BEST PRICES · RETAIL · TRADE · EXPORT & INDUSTRIAL



FREE BOOKLET

All types of
TRANSISTORS · RECTIFIERS
BRIDGES · SCR's · TRIACS
INTEGRATED CIRCUITS
F.E.T. · LIGHT DEVICES
OVER 1500 DIFFERENT DEVICES



MORE DEVICES
NEW PRICES
NEW RANGES
THIS IS A MUST
FOR ALL
SEMI-CONDUCTOR
USERS!

ENTIRELY NEW 1973 EDITION (ask for Booklet No. 36)
SEND FOR YOUR FREE COPY TODAY!

INTEGRATED CIRCUITS, VERY IMPORTANT—ONLY BRANDED IC'S ARE TO THE FULL MANUFACTURERS' SPECIFICATIONS. ALL OTHERS ARE NOT. HENRY'S SELL ONLY BRANDED INTEGRATED CIRCUITS... FROM TEXAS · I.T.T. · FAIRCHILD · SIGNETICS... SO WHY BUY ALTERNATIVE OR UNDER SPEC. DEVICES WHEN YOU CAN PURCHASE THE GENUINE ARTICLE FROM US EX STOCK... NEED WE SAY MORE!



Type	1-12-30-99	Type	1-12-30-99
SN74001	20 18 16	SN74126N	89 69 80
SN74011	20 18 16	SN74132N	72 72 68
SN74011AN	38 38 38	SN74136N	83 83 85
SN74021	20 18 16	SN74141N	1-00 90 80
SN74031	20 18 16	SN74142N	2-88 2-88 2-82
SN7403AN	38 38 38	SN74145N	1-44 1-44 1-28
SN74041	24 21 18	SN74147N	2-80 2-80 1-83
SN74051	20 18 16	SN74148N	2-01 2-01 1-58
SN7405AN	44 44 44	SN74151N	1-15 1-15 1-00
SN74061	40 38 38	SN74153N	1-08 1-08 95
SN74071	38 38 38	SN74154A	2-80 2-80 2-01
SN74081	25 22 19	SN74155N	1-55 1-55 1-00
SN74091	38 38 38	SN74156N	1-09 1-09 1-00
SN7409AN	44 44 38	SN74157N	1-09 1-09 95
SN74101	20 18 16	SN74159N	2-44 2-44 2-14
SN74111	25 23 21	SN74161N	1-58 1-58 1-38
SN74121	28 28 25	SN74162N	1-58 1-58 1-38
SN7412AN	38 38 38	SN74172N	5-78 5-78 5-04
SN74131	30 27 25	SN74173N	1-86 1-86 1-45
SN74141	72 72 68	SN74174N	1-00 1-00 1-57
SN74161	30 27 25	SN74175N	2-01 2-01 1-78
SN74171	30 27 25	SN74176N	1-44 1-44 1-28
SN74201	20 18 16	SN74177N	1-44 1-44 1-28
SN74221	38 38 38	SN74180N	1-44 1-44 1-28
SN7422AN	37 37 37	SN74181N	5-18 5-18 4-58
SN74231	37 37 37	SN74182N	1-44 1-44 1-28
SN74251	37 37 37	SN74183N	1-72 1-72 1-51
SN74271	37 37 37	SN74185N	1-18 1-18 1-08
SN74281	48 43 37	SN74188N	6-48 6-48 5-87
SN74301	20 18 16	SN74190N	2-80 2-80 2-01
SN74321	27 37 32	SN74191N	2-80 2-80 2-01
SN74331	48 43 38	SN74192N	2-80 2-80 2-01
SN7433AN	57 57 50	SN74193N	2-80 2-80 2-01
SN74371	48 43 37	SN74194N	1-72 1-72 1-51
SN74381	57 57 50	SN74195N	1-18 1-18 1-08
SN74401	20 18 16	SN74196N	1-58 1-58 1-38
SN7441AN	55 79 73	SN74197N	1-58 1-58 1-38
SN74421	85 79 78	SN74198N	2-18 2-18 2-02
SN74431	1-60 1-27	SN74199N	2-88 2-88 2-82
SN74441	1-60 1-27		
SN74451	2-18 2-16		

PRICING OF SN7400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX
SN74 (HIGH POWER), SN74 (LOW POWER) series in stock. Send for List 36 free on request. Low Profile Sockets, 14 pin, 15p, 16 pin, 17p, 8 pin, 14p.

TRANSISTORS—A selection

For full list send for booklet 36 today

£p	£p	£p	£p	£p	£p
AAZ13	10 BC169C	14 BY100	15 OC36	65 V405A	25 2N3614
AC107	35 BC182	12 BY127	15 OC44	18 ZTX108	10 2N3702
AC128	20 BCY32	35 BY213	35 OC45	18 ZTX300	14 2N3714
AC187	20 BCY39	1-00 C106D	55 OC72	15 ZTX302	18 2N3771
ACY17	35 BCY55	2-50 GET111	55 OC77	25 ZTX500	15 2N3773
ACY39	65 BCY70	15 GET115	75 OC77	55 ZG301	40 2N3779
AD149	50 BCY71	20 GET880	55 OC81	28 2N697	15 2N3819
AD161	39 BCY72	13 LM309K	1-87 OC83	25 2N706	10 2N3866
AD162	39 BCY74	80 MAT121	25 OC140	65 2N930	20 2N3903
AF111	20 BF112	45 ME440	1-06 1-06	92 2N160	45 2N4062
AF118	50 BF115	22 MJE520	65 OC200	55 2N1132	25 2N4126
AF139	30 BF180	33 MJE3055	75 OC202	90 2N1304	22 2N4871
AF186	40 BF194	13 MPF105	46 OCP71	1-00 2N1613	20 2N5457
AF239	44 BFY13	25 NKT217	45 ORP12	55 2N1671	1-00 2S001
ASV27	30 BFX34	55 NKT404	60 ORP60	45 2N2147	75 2S026
BA115	10 BFX88	22 OAS	60 P346A	26 2N1660	65 2S035
BA213	20 BFY13	50 OJ1	10 TL209	25 2N2926	10 4Z050
BC107	12 BFY51	20 OA200	9 TIF29A	49 2N3053	20 40361
BC108	12 BFY64	45 OA202	10 TIF30A	58 2N3054	45 40362
BC109	12 BFY90	75 OC16	85 TIP31A	61 2N3055	45 40408
BC109C	14 BLY36	6-25 OC20	1-25 TIP41A	74 2N3440	50 40486
BC113	16 BSX200	15 OC28	65 TIP42A	90 2N3442	1-00 40636
BC147	12 BU105	2-20 OC35	35 TIS43	26 2N3525	80 40430

All types offered subject to availability. Prices correct at time of press. E. & O.E.

TBA 800 5 WATT I.C.
 Suitable alternative to SL403D, 5/30 volt operated, 8/16 ohm 5 watt output.
 With circuits and data £1-50.



SINCLAIR IC12
 With circuits and data. 6 W IC with printed circuit board 28V operated, £1-80.



ZN414 IC
 Integrated circuit radio as featured by many magazines. (PW Jan. 73 Reprint Ref. No. 19 for 10p), £1-20.



TOSHIBA POWER AND PREAMPLIFIER MODULES
TH9013P 20W power amplifier 22-0-22 or single 45V operated, £4-57.
TG9014P Stereo on two channel preamplifier, £1-50. (Circuit book No. 42 price 10p).



ULTRASONIC TRANSUCERS

Operate at 40kHz up to 100 yds. Ideal remote switching and signalling complete with data transmitter and receiver, new I.C. circuits. Per pair, £5-90.
TA 960 I.C. with socket £1-80.

3015F 7 SEC.

IC size complete with data price £2 each or 4 for £7. (Digital clock circuits Ref. No. 31, 15p).



TRANSISTORS—SPECIAL OFFERS

2N3035	BY127
25 47p each	75 12p each
100 42p each	100 10p each
500 39p each	500 9p each
1000 34p each	1000 8p each

AFI17

25 15p each	100 13p each
500 12p each	500 9p each
1000 10p each	

OC35

25 46p each	100 42p each
500 39p each	500 34p each
1000 30p each	

ZENER DIODES

400mW BZY88/ BZX83, 10p
 3·3V—33V, 10p each.
 1·3V 5% Mir alternate Tubulars.
 IN4700 series.
 From 3·3V—33V, 18p each.
 10V. Stnd. Mounting ZS series 6·8V—100V 5%, 40p each.

LINEAR I.C. £p

702C (T05)	75
709C (T05)	39
709C (DIL)	39
723C (T09)	90
723C (DIL)	90
728C (T09)	45
741C (T05)	50
741C (DIL)	50
747C (T09)	1-00
747C (DIL)	1-00
748C (DIL)	61

SILICON RECTIFIERS

1 amp series.
 IN4001 to IN4007. From 8p each.
 1-5 amp.
 PL4001 to PL4007. From 8p each.
 3 amp.
 PL7001/IN5400. From 14p each.
 Send for full list 36.

SEMI-CONDUCTOR QUANTITY DISCOUNTS

10% 12+; 15% 25+; 20% 100+
 All one type except where quantity discounts shown.
 Min. order £1-00 please.

10% VAT TO BE ADDED TO ALL ORDERS

MORE OF EVERYTHING AT HENRY'S
 Cover of this magazine.
BEST VALUE

TRIACS—Stud Mounting with accessories

3 AMP RANGE	1-11
Type P.I.V. Price ea.	
SC35A	200V 85p
SC35D	400V 90p
SC35E	500V £1-20
6 AMP RANGE	
SC40A	100V 90p
SC40B	200V 95p
SC40D	400V £1-20
SC40E	500V £1-50
10 AMP RANGE	
SC45A	100V £1-05
SC45B	200V £1-15
SC45D	400V £1-45
SC45E	500V £1-85
15 AMP RANGE	
SC50A	100V £1-45
SC50B	200V £1-65
SC50D	400V £1-95
SC50E	500V £2-25



TRIACS—Additional Types

40430 TRIAC (T066)	85p
40669 TRIAC (Plastic)	95p
40486 TRIAC (T05)	75p

NEW RANGES BRIDGE RECTIFIERS

FEATURES SMALL SIZE & LOW COST
250 M/A ± AMP P.I.V.
 B025/05 50 16p
 B025/10 100 18p
 ± x x pin dia.
 1 AMP
 Type P.I.V. Price ea.
 B05/05 50V 20p
 B05/10 100V 22p
 B05/20 200V 23p
 B05/40 400V 25p
 B05/60 600V 27p



2 AMP

Type P.I.V. Price ea.

B1/05	50V	25p
B1/10	100V	25p
B1/20	200V	28p
B1/60	600V	30p

3 AMP

Type P.I.V. Price ea.

W005	50V	29p
W01	100V	30p
W02	200V	32p
W06	600V	35p

1 x pin tubular

2 AMP PS

B2/05	50V	35p
B2/10	100V	40p
B2/20	200V	45p
B2/60	600V	50p
B2/100	1000V	55p

1 x pin tubular

3 AMP PS

B4/100	100V	55p
B4/200	200V	59p
B4/400	400V	65p
B4/600	600V	75p
B4/800	800V	£1-00

1 x pin tubular

5 AMP PS

B6/05	50V	65p
B6/10	100V	70p
B6/20	200V	80p
B6/40	400V	90p
B6/60	600V	£1-00

1 x pin tubular

7 AMP (T048)

CRS 3/05AF	50V	40p
CRS 3/10AF	100V	40p
CRS 3/20AF	200V	45p
CRS 3/40AF	400V	55p
CRS 3/60AF	600V	65p
CRS 3/AMP	400V	60p
CRS 5/400V	5/400V	60p

7 AMP (T048)

CRS 7/100	100V	60p
CRS 7/200	200V	67p
CRS 7/400	400V	85p
CRS 7/600	600V	95p

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment

Henry's

PANEL METERS · TRANSFORMERS · CONTROLS · RELAYS
 IRONS · TOOLS · VALVES · POT CORES MOST TYPES OF COMPONENTS
 You need a catalogue! 55p post paid complete with Discount Vouchers



UK's
**LARGEST RANGE
 OF KITS &
 GADGETS**



TEST EQUIPMENT MULTIMETERS

(carr., etc. 30p)
200H (M210) 20kV Slimline with case, £4-95
TH133D 2kV Robust with case, £4-95
U437 10kV Steel case, A.C. up to 40kHz, £4-95
U4324 20kV with A.C. current ranges, £8-00
AF105 50kV with leather case, £9-50
U4313 20kV A.C. current. Steel case, £10-50
U4341 Plus built in transistor tester, £10-50
Model 500 30kV, £9-95

OTHER EQUIPMENT


SE250B Pocket Signal Injector, £1-90, Carr. 15p
SE500 Pocket Signal Tracer, £1-50, Carr. 15p
TE15 Grid Dip Meter 440kHz—280MHz, £13-45, Carr. 30p
TE40 A.C. Millivoltmeter 1-2MHz, £18-75, Carr. 35p
TE65 28 Range Valve Voltmeter, £19-25, Carr. 40p
TE20D 120kHz—500MHz RF Generator, £16-95, Carr. 40p
TE21D 20Hz—200kHz Audio Generator, £18-75, Carr. 40p
SE350A Deluxe Signal Tracer, £9-95, Carr. 20p
SE400 Volts/ohms/R-C sub./RF field/RF gen., £11-25, Carr. 20p

A SELECTION OF INTERESTING ITEMS

C3025 Compact transistor tester, £5-50, P. & P. 15p
13100 Mono mag cart preamp, £1-95, P. & P. 15p
E1310 Stereo mag cart preamp, £4-95, P. & P. 25p
 Earphone telephone amplifier, £6-15, P. & P. 25p
D1203 Telemp with PU coil, £3-60, P. & P. 20p
LL1 Door Intercomm. and chime, £11-95, P. & P. 25p
Chattalite (lights as you talk), £13-90, P. & P. 20p
1kV Dimmer/controller, £3-00, P. & P. 10p
9in Twin spring unit, for Reverbs, £2-75, P. & P. 15p
16in Twin spring unit, for Reverbs, £6-50, P. & P. 25p
Car Tachometer Electronic, £7-50, P. & P. 15p

VHF 205 Marine band converter, £3-95, P. & P. 15p
B2005 4 Ch. mic. mixer, £2-95, P. & P. 15p
B2004 2 Ch. stereo mixer, £4-75, P. & P. 15p

BUILD THIS RADIO

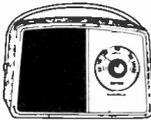

PORTABLE MW/LW RADIO KIT using Mullard RF/IF module. Features MW—bandspread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts £7-98 (battery 22p). Carr. etc. 32p.

EXCLUSIVE: SPECIAL OFFERS

MW/LW CAR RADIO + or — earth with speaker and fixings. £6-50 carr./pack. 30p.
8 TRACK CAR STEREO (— earth) with speakers, in pods and fixings. £12-50 carr./pack. 40p.
HANIMAX HC1000 battery cassette recorder, £10-50 carr./pack. 25p.
HANIMAX HC2000 battery/mains cassette recorder. £13-50 carr./pack. 30p.
AKAI GCX40 stereo cassette recorder, £59-95 carr./pack. 50p

Pair Akai ADM microphones. £6-95 carr./pack. 20p.

5 WAVEBAND PORTABLE TWIN SPEAKER RADIO FM/MW/SW/ AIR-CRAFT — PUBLIC SERVICES. £10-45 carr./pack. 30p.

P O R T A B L E CASSETTE TAPE PLAYER — for car or carry around. £7-25 carr./pack. 20p.

HANIMAX POCKET CALCULATOR with % key. £33-50.

SPECIAL PURCHASES

AVOMETER MOVEMENTS

AVO 8 or 9 50mA MOVEMENTS. Ex Brand New AVO's. £3-50, Post 20p.


UHF TV TUNERS CHANNELS 21 to 64

Brand new transistorised geared tuners for 625 Line Receiver IF output. £2-50, Post 20p.

EASY TO BUILD KITS BY AMTRON— EVERYTHING SUPPLIED

Model No.	£
310 Radio control receiver	3-00
300 4-channel R/C transmitter	5-75
345 Superhet R/C receiver	5-08
450 TV sweep generator	10-24
455 AM signal generator	9-25
460 FM signal generator	9-91
65 Simple transistor tester	1-18
110 3VW amplifier	2-87
120 12VW amplifier	3-88
125 Stereo control unit	4-20
130 Mono control unit	3-52
605 Power supply for 115	3-88
610 Power supply for 120	4-08
615 Power supply for 2 x 120	4-85
230 AM/FM aerial amplifier	2-79
240 Auto parking light	5-18
275 Mic. preamplifier	5-83
480 Electronic voltmeter	17-51
485 0-12V 300mA STAB. supply	9-68
570 LF generator 10Hz—1mHz	12-60
575 Sq. wave generator 20Hz—20kHz	12-87
590 SWR meter	10-24
620 Hi-CAD barger 1-2-12V	7-47
630 STAB. Power supply 6-12V 0.25-0-1A	7-65
690 D.C. motor speed Gov.	2-63
700 Electronic Chaffinch	5-96
705 Windscreen wiper timer	5-56
760 Acoustic switch	8-87
780 Metal Detector (electronics only)	7-27
790 Capacitive burglar alarm	6-96
810 Dynamic Compressor	6-79
835 Guitar preamp	3-75
840 Delay car alarm	5-20
875 CAP. Discharge ignition for car engine (-Ve Earth)	10-68
80 Scope calibrator	1-98
25 Level indicator	5-50
430 3mHz Millivoltmeter	18-23
525 120—160mHz VHF timer	9-33
715 Photo cell switch	6-93
795 Electronic continuity tester	3-88
860 Photo timer	12-04
871 Slide projector auto feed control	8-72
235 Acoustic alarm for driver	6-96
465 Quartz XTAL checker	7-89

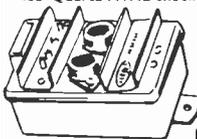ALL KITS OFFERED
 SUBJECT TO STOCK
 AVAILABILITY



BUILD THIS TUNER

MW/LW Radio tuner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built-in battery. Excellent results. Size: 7in x 2½in x 3½in. All parts £4-85, Carr. 15p.

MULTI-USE AND RADIONIC KITS

	£
10-1 10 Projects	3-60
50-1 50 Projects	8-00
150-1 150 Projects	13-20
Telephone Communicator X20 20 (Elec)	7-20
X40 40 (radio) Projects	4-95
(Carr./Pack. 40p)	9-45

ALL TRANSISTOR CIRCUITS WITH HANDBOOKS

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT TO BE ADDED TO ALL ORDERS. UK post, etc. 15p per order unless stated.



GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted record/play and oscillator/erase heads. Wind and rewind controls. Takes up to 4in spools. Brand new complete with head circuits. £9-50, Carr. 30p.

TOP QUALITY SLIDER CONTROLS


60mm stroke high quality controls covatec knobs (post, etc. 15p any quantity).
Singles Log and Lin
 5kΩ, 10kΩ, 22kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1 Meg. 45p each.
ANGED Log and Lin
 10kΩ, 22kΩ, 50kΩ, 100kΩ, 250kΩ. 65p each. (Quantity discounts available). Complete with knobs.
MARRIOT TAPE HEADS
4 TRACK MONO or 2 TRACK STEREO
 '17' High Impedance, £2-00; '18' Med. Impedance, £2-00; Erase Heads for '17' and '18', 75p; '63' 2 track mono-Hi Imp., £1-75; '43' Erase Head for '63', 75p. (Post, etc. 15p any quantity).
 R730/E73 2 Track Mono Record Erase Low Imp., 75p pair.

SINCLAIR AND MINIATURE AMPLIFIERS

AMPLIFIERS (Carr. etc. 20p).	£
4-300 0.3 watt 9 volt	1-75
104 1 watt 9 volt	2-20
304 3 watt 9 volt	2-50
535 3 watt 12 volt	2-85
EI208 5 watt 12 volt	4-50
608 10 watt 24 volt	4-10
410 10 watt 28 volt	4-95
Z30 15 watt 30 volt	3-57
EI206 30 watt 45 volt	9-75
Z50 30 watt 50 volt	4-37
EI210 24 watt 125 12 volt	5-25
RE500 5 watt mains operated Amplifier with controls	6-30
SAC14 7 + 7 watt Stereo with controls	8-00
SAC30 15 + 15 watt Stereo with controls	11-00

SINCLAIR UNITS (Carr. 20p)	£
Z30 3-57	4-37
Stereo 60 Preampifier	7-97
PZ5	3-97
PZ6	6-37
PZ8 (for Z50)	4-77
TRANS.	2-95
AFU	4-45

SINCLAIR PACKAGE DEALS. Post 25p	£
2 x Z30, Stereo 60, PZ5	15-95
2 x Z30, Stereo 60, PZ6	18-00
2 x Z50, Stereo 60, PZ8	20-25
Transformer for PZ8	2-95
PROJECT 605 KIT	19-95

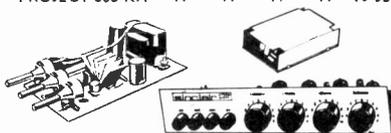

POWER SUPPLIES FOR EVERY PURPOSE

(All cases unless stated chassis)
470C 6/7/9V 300mA. (Includes Multi-Adaptor for Tape Recorders etc.), £1-95, Post 20p
Car Lighter Voltage Adaptors 300mA (State Voltage 6V, 7½V, 9V), £1-95 each. Post 25p
SC202 3/6/7/9V 400mA. £3-25, Carr. 30p
HC244R. Sealed version, £4-25, Carr. 30p
P500 9V 500mA. £2-80, Post 20p
P11 24V 500mA (chassis), £2-80, Post 20p
P15 26/28V 1 amp (chassis), £2-70, Post 20p
P1080 12V 1 amp (chassis), £3-25, Post 20p
P1081 45V 0.9 amp (chassis), £4-40, Post 20p
P12 4—12V 0.4—1 amp. £6-75, Post 30p
SE101A 3/6/9/12V 1 amp (Stab.), £9-15, Post 25p
RP164 6/7/9/12 1 amp (Stab.), £9-95, Post 30p

FIBRE OPTICS
 0.01 dia. Mono Filament, £1-50 per 25 metre reel.
 0.13 dia. 64 Fibres Sheathed, £1-00 per metre.
 SPRAYS 15mm dia. Mares Tails, £9-50.



Henry's RADIO LIMITED

SEE FACING PAGE FOR ADDRESSES

EDGWARE ROAD, W2

Henry's

DISCOUNT HI-FI, TV, TAPE AND CAR ENTERTAINMENT

Low prices means less VAT - Henry's give full guarantees and demonstrations for callers. Plus big savings. Also at Modern Electrics (Retail) Ltd., 120 Shaftesbury Avenue, W.1.—Your Sony dealer.

**BEST VALUE
IN U.K.**



STEREO AMPLIFIERS

(Carr./packing 50p)	£
AKAI: AA5200	61-70
AA5500	78-50
AA5800	117-50
AMSTRAD: IC2000 Mk. II	29-50
4000	23-10
EAGLE: TSA149	25-10
TSA151	34-85
AA2	30-80
AA4	42-45
AA5	55-95
HOWLAND WEST: DA1000	22-45
HENELEC TEXAN: Kit	28-50
HENELEC TEXAN: Built	35-00
NIKKO: TRM300	25-95
TRM400	32-50
PIONEER: SA500A	34-25
ROTEL: RA211	34-65
RA311	41-15
RA611	60-80
RA810	75-75
RA1210	92-50
SINCLAIR: 2000	22-95
3000	28-95
TANDBERG: TA300	66-50
TELETON: SAQ206B	22-50
SAQ307	22-50
GA202	28-50

STEREO RADIO TUNERS

(Carr./packing 50p)	£
AKAI: AT550	60-50
AT580	94-50
AMSTRAD: 3000	23-55
EAGLE: AAB	40-50
TST152	29-45
HENELEC: Stereo Kit	21-00
Built	24-95
HOWLAND WEST: DA1000T	25-35
PIONEER: TX500A	48-75
ROTEL: RT222	32-65
RT322	43-75
RT322	65-40
RT992	39-25
SINCLAIR: 2000	26-95
3000	26-95
TELETON: GT202	30-50

DECODERS/SYNTHESIZERS

(Carr. etc. 30p)	£
DYNACO QUADRATOR	16-90
EAGLE: AA10	12-00
AA26	16-35
TATE 1	7-95
TATE 2 } Chassis	15-75
TATE 3 } Chassis	15-75
TATE 4 } Chassis	19-95
TATE 7 } Boxed	25-95

MATCHED SPEAKER SYSTEMS

Recommended pairs 8 ohms	£
RANK DOMUS	£
150	26-95 pair
175	33-75 pair
250	53-75 pair
MARSDEN HALL	£
110, 10W	22-50 pair
150, 15W	27-50 pair
200, 20W	34-50 pair
DYNACO	£
A10	43-00 pair
A25 } 20-60W	69-00 pair
A35 } 79-00 pair	
WHARFEDALE	£
Denton 2, 18W	27-20 pair
150, 120W	32-65 pair
Triton, 25W	40-80 pair
Melton II 25 watts	51-80 pair
LEAK	£
150, 18W	32-65 pair
250, 18W	44-30 pair
CELESTION	£
120, 20W	37-80 pair
County, 25W	33-60 pair
15, 30W	50-40 pair
44, 44W	81-20 pair

U.K.'s largest stockists for KEF Acoustic Research, Mordaunt Short and Cambridge audio speakers. In stock and on demonstration. Phone for keenest price.

STEREO MAGNETIC CARTRIDGES

(Carr. etc. 15p)	£
SHURE	£
M3Dm £3-20; M44.7 £3-95; M44E £4-25; M55E £4-95; M44G £4-20; M75G/IIIB £6-75; M75EDII £8-50; M75EIII £7-95; M75GII £7-25.	
GOLDRING	£
G850 £2-85; G800 £3-95; G800H £3-95; G800E £5-95; G800SE £10-00; G820 £6-70; G820E £10-00; G820SE £13-35.	
AD.35	£
Q36 £10-70; Q32 £8-70; Q30 £5-90.	
GRADO	£
FTR £5-25; F3E £11-25; FTE £8-25; MZ £18-75.	

EMPIRE

999REX 3-70; 999QUX 4-80; 999EXE 8-50; 999TEX £14-95.	
RONETTE	£
SM500/7	4-60
SM500/5	4-60
SM500/E	6-95

RECORD DECK PACKAGES

(Carr./packing 75p)	£
*Less cart.—rest with	
(HL): SP25 III/1800 or H	15-95
(M): SP25 III/M7565	19-45
(HL): AP76/G800	25-55
(M): AP76/M7565	29-10
(HL): GL75 P/C	33-50
(HL): GL75 P/C G800	36-65
(HL): GL75 P/C G800E	39-15
(HL): MP60 TPD1 G800	15-80
HT70(TPD1) G800	19-50
RANK DOMUS	£
BD200	43-60
BA400	53-95
*Pioneer PL12D	31-75
*Thorens TD165	43-80
*Thorens TD160C	50-80

STEREO COMPACTS

complete with speakers	£
(Carr./packing £1.25)	
Fidelity UA3	39-90
Sanyo G2601KL	125-50
Sanyo G2615N	71-95
Sanyo GXT4520KL	103-50
Sanyo GXT4730KL	97-50

Philips GF908	99-65
RH802	159-95
RH36	57-20
GF836	41-75
RH811/RH441	84-95
RF839	55-95
GF829	39-95
GF815	47-75
GF808	65-75
RH814/RH411	93-50
GF603	19-95

8 TRACK STEREO HOME UNITS

(Carr./packing 70p)	£
Amerlex ACR301	£48-00
(With MW/FM stereo radio).	

PORTABLE TV BATTERY—MAINS

(Carr./packing £1.00)	£
Elizabethan TV (9in)	43-50
Crown 9TV (9in)	46-50
Elizabethan T12 (12in)	43-95
Teleton TV12 (12in)	46-95
Sanyo 10T150 (12in)	49-95

STEREO PHONES

CASSETTE PLAYER

FOR CAR—HOME AND AROUND

Actually the price far below the quality of the superb player. It is of beautiful quality both in sound and looks. Features wind, rewind, volume and tone controls. Speaker is very good indeed. Comes complete with earphone, batteries. Full guarantee. Optional adaptor to run off car or mains.

MADE TO ORDER £12.50 OUR PRICE

£7.25 CAR CIGAR LIGHTER PLUG-IN ADAPTOR £1.95 MAINS ADAPTOR £1.95

DOLBY/NRU

(Carr./packing 30p)	£
Teleton SNR100D	29-50
Philips N6720	15-00
Teac AN60/AN80/AN180 stocked.	

BATTERY CASSETTE RECORDERS

(Carr. etc. 30p)	£
Amerex 100	11-00
Wien ET1008	14-40
Philips EL3302	16-60
N2203	15-95
N2211	13-90
Sanyo M1101	13-90
M1102	12-95

BATTERY/MAINS CASSETTE

(Carr. etc. 35p)	£
Wien RT452	13-65
Amerex AC101	12-00
Elizabethan LZ315	12-25
Amerex AC104	16-00
Philips N2204	20-75
N2205	29-50
Pye 9115	27-75
9118	21-20
Hitachi TRQ291	27-50
Sanyo M2000G	23-25
MR4010	28-95
M4000G	49-50
BASF CC9201	37-25
Hitachi TRQ2335	49-50

BATTERY/MAINS RADIO CASSETTE RECORDERS

(Carr. etc. 30p)	£
Amerex ACR200	22-00
ACR201	30-00
Elizabethan LZ416	27-25
LZ516	29-10
50-75	
BASF CC9301	50-75
Philips RR322	28-75
RR413	33-90
RR415	48-30
Sanyo M4141	39-50
M2400W	31-50
M2400FG	31-50
M4400FG	62-50
Grundig C250	47-95
Hitachi TRK1240E	29-50
TR1161	35-10
KCT1210L	33-50

STEREO RECORDER DECKS

(Carr./packing 50p)	£
Cassette	£
Philips N2506	44-50
Philips N2410	87-10
SE12	91-50
Tandberg TCD3000	112-00
Akai CS30D	50-65
CS33D	62-50
GXC36D	65-15
GXC40D	57-40
GXC38D Dolby	81-45
GXC46D Dolby	89-15
GXC45D	92-65

TEAC: A250/A350/A450 stocked.	
Real to Reel	£
Akai 400DS	62-50
Tandberg 3321X/3341X	107-70
Large range Akai/Tandberg/Revox/Teac stocked.	
8 Track	£
Akai CR81D	53-60
CR80DS5	93-65

STEREO PHONES

(carr./packg. 20p.)	(carr./packg. 20p.)	£
Pioneer: SE20A	SE90	£5-90
SE30A	SE9-45	£5-50
SE16-35	SE120	£7-90
SE125	SE11-15	£5-40
SE140		
Accessories:		
H1012/ JB3 Junction Box	£1-40	
IB3DE Din Junction Box	£1-60	
JBL111 De Luxe Junction Box	£1-95	
0250	£2-75	
Phone Switch	£4-75	
Control Boxes: G1301 (two phones) £2-62; G1305 Controller £2-15; FF17 2—pairs (Sliders) £6-25; Koss: TWA £4-30; Koss: TSA £4-95; Koss: T10A £8-50; HW Mk.III Controller £6-90.		

IN CAR ENTERTAINMENT

Car radios (carr./packg. 35p).	£
MW/LW complete with speakers. Shira £25-70; ST2000 £31-50.	
MW/Stereo FM (carr./packg. 35p) complete with speakers. Sharp AR953 car radio £36-50; Lear Jet 277 (plus 8 track) £42-65.	

STEREO RECORDERS

(Carr./packing 70p)	£
Akai I721L	67-20
Cassette	£
Akai GXC40 Dolby	67-95
GXC46 Dolby	89-95
Philips N2400/RH411	63-75
N2401/RH411	74-50
N2401S/RH411	79-95
N2405/RH401	49-50
8 Track	£
Akai CR81	66-20
8 Track Player Decks	£
(Carr./packing 35p)	
Elizabethan 8/LZ1	13-40
McDonald/BSR TDB5	12-75
TDB3V	15-25

STEREO TUNER—AMPLIFIERS

(Carr./packing 75p)	£
Akai AA8030	92-50
Goodmans Module 80	59-20
Goodmans Module 90	75-75
Goodmans One/Ten	88-50
Pioneer SX525	90-75
SX 626	124-75
Rotel RX150A	41-95
RX200A	53-95
RX400A	64-95
RX600A	90-00
RX800	114-50
RX154A	78-30
Tandberg TR200MPX	85-00
TR1000MPX	125-35
TR1010MPX	135-75
Teleton TSF55	57-70

YOU CAN PAY BY BARCLAYCARD OR ACCESS

For callers or by phone

01-402 4736

Easy credit terms for callers to 309 and 354-356

ALSO STOCKED AND DEMONSTRATED

Armstrong — Acoustic Research — Cambridge Audio — Leak — Lux — Marantz — Quad — Revox — Sansui — Tandberg — Sugden — Wharfedale — Goodmans — Celestion — Grundig — Kef — Teac — Bose — Sherwood

Call or phone 01-402 4736 for best prices

10% VAT to be added to ALL ORDERS. Prices and description correct at time of press E & OE. All goods offered subject to stock availability.

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open- 9 am-6 pm
6 days a week
All stores open all day Saturday

RST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
Express postage 1p per transistor, over ten post free
INTEGRATED CIRCUITS 5p + 1p each added

IN	SP	AFZ	SP	BYZ	SP	OAZ	SP	ZS	SP
IN21	0-17	AFZ12	1-50	BYZ10	0-45	OAZ209	0-40	ZS170	0-10
IN23	0-85	AFZ26	0-25	BYZ11	0-40	OAZ210	0-40	ZS271	0-18
IN85	0-88	AFZ27	0-20	BYZ12	0-40	OAZ211	0-40	ZT21	0-25
IN263	0-60	AFZ28	0-20	BYZ13	0-35	OAZ222	0-45	ZT43	0-25
IN256	0-60	AFZ29	0-30	BYZ15	1-25	OAZ223	0-45	ZTX107	0-18
IN645	0-85	AFZ36	0-25	BYZ16	0-60	OAZ224	0-45	ZTX108	0-10
IN726A	0-20	AFZ50	0-20	BYZ88C3V3		OAZ241	0-22	ZTX300	0-14
IN914	0-05	AFZ51	0-40		0-10	OAZ242	0-22	ZTX304	0-24
IN4007	0-12	AFZ53	0-20	BZY88C3V3		OAZ244	0-25	ZTX500	0-16
18113	0-15	AFZ55	0-20		0-10	OAZ246	0-22	ZTX503	0-15
18131	0-13	AFZ56	0-20	C111	0-55	OAZ290	0-22		
18202	0-22	AFZ62	0-25	C8S1105	0-65	OC16	0-25		
2G371	0-40	AFZ68	0-88	C8S1405	0-65	OC18T	0-38		
2G381	0-25	AFZ71	0-30	C84B	2-50	OC19	0-50		
2G414	0-30	AU101	1-50	C810B	3-18	OC20	1-25		
2G417	0-25	AU101	1-50	DD000	0-15	OC22	1-00	7400	0-20
2N404	0-22	BC107	0-12	DD003	0-15	OC23	1-25	7401	0-20
2N697	0-15	AC106	0-12	DD006	0-18	OC24	1-10	7402	0-20
2N698	0-30	BC109	0-12	DD007	0-40	OC25	0-40	7403	0-20
2N706	0-10	BC113	0-16	DD008	0-38	OC26	0-25	7404	0-20
2N706A	0-12	BC115	0-20	GD3	0-38	OC28	0-65	7405	0-20
2N708	0-15	BC116	0-20	GD4	0-10	OC29	0-65	7406	0-20
2N709	0-40	BC116A	0-23	GD5	0-38	OC30	0-40	7407	0-40
2N1091	0-55	BC118	0-15	GD8	0-25	OC35	0-55	7408	0-20
2N1131	0-25	BC121	0-20	GD12	0-10	OC36	0-65	7409	0-20
2N1132	0-25	BC122	0-20	GD12	0-10	OC36	0-65	7410	0-20
2N1302	0-18	BC125	0-68	GET103	0-40	OC42	0-40	7411	0-22
2N1303	0-18	BC126	0-65	GET113	0-35	OC43	0-70	7412	0-22
2N1304	0-22	BC140	0-55	GET114	0-30	OC44	0-18	7413	0-20
2N1305	0-22	BC147	0-12	GET115	0-75	OC44M	0-17	7415	0-20
2N1306	0-22	BC148	0-10	GET116	0-65	OC45	0-18	7416	0-20
2N1307	0-22	BC149	0-12	GET120	0-60	OC49M	0-18	7417	0-20
2N1308	0-22	BC147	0-14	GET122	0-40	OC49	0-27	7422	0-28
2N1309	0-22	BC158	0-12	GET875	0-50	OC57	0-60	7423	0-40
2N219	0-75	BC160	0-68	GET880	0-55	OC58	0-60	7425	0-27
2N148	0-40	BC169	0-14	GET881	0-25	OC59	0-60	7427	0-37
2N2160	0-61	BCY31	0-45	GET882	0-35	OC66	0-60	7428	0-43
2N2218	0-23	BCY32	0-25	GET885	0-35	OC70	0-18	7430	0-20
2N2219	0-25	BCY33	0-25	GET885	0-35	OC71	0-15	7432	0-37
2N2369A	0-16	BCY33	0-25	GET885	0-35	OC71	0-15	7433	0-43
2N2444	1-09	BCY38	0-55	GET941	0-45	OC73	0-60	7437	0-48
2N2813	0-22	BCY39	1-00	GJ3M	0-50	OC74	0-20	7438	0-48
2N2846	0-50	BCY40	0-80	GJ4M	0-38	OC75	0-20	7440	0-20
2N2904	0-20	BCY42	0-80	GJ5M	0-25	OC76	0-20	7441AN	0-22
2N2904A	0-25	BCY70	0-15	GJ7M	0-50	OC77	0-55	7442	0-25
2N2908	0-20	BCY71	0-20	HG1005	0-50	OC78	0-25	7451	0-20
2N2924	0-22	BCY71	0-20	HG100A	0-60	OC79	0-30	7452	0-20
2N2925	0-15	BCZ11	0-65	MAT100	0-20	OC81	0-28	7453	0-20
2N2926	0-10	BD121	1-00	MAT101	0-25	OC81D	0-28	7454	0-20
2N3054	0-45	BD123	1-00	MAT120	0-20	OC81M	0-20	7460	0-20
2N3055	0-45	BD124	1-00	MAT121	0-25	OC81DM	0-18	7470	0-22
2N3702	0-11	BDY11	1-45	MJES20	0-65	OC81Z	0-45	7472	0-22
2N3705	0-12	BF115	0-22	MJES255	1-10	OC82	0-22	7473	0-44
2N3706	0-11	BF117	0-20	GE5055	0-75	OC82D	0-25	7474	0-48
2N3707	0-11	BF167	0-23	NKT128	0-45	OC83	0-25	7475	0-59
2N3709	0-10	BF173	0-25	NKT129	0-30	OC84	0-25	7476	0-45
2N3710	0-11	BF181	0-23	NKT211	0-25	OC114	0-38	7480	0-80
2N3711	0-11	BF184	0-22	NKT213	0-25	OC122	1-00	7482	0-87
2N3819	0-85	BF185	0-22	NKT214	0-24	OC123	1-10	7483	1-20
2N5027	0-53	BF194	0-13	NKT216	0-40	OC129	0-40	7484	1-00
2N5088	0-22	BF195	0-13	NKT217	0-45	OC140	0-65	7486	0-50
2S801	0-59	BF196	0-15	NKT218	1-13	OC141	0-80	7490	0-75
2S804	1-15	BF197	0-15	NKT219	0-33	OC169	0-20	741AN	1-10
2S801	0-87	BF961	0-25	NKT222	0-30	OC170	0-25	7492	0-72
2S703	1-00	BF989	0-25	NKT224	0-25	OC200	0-55	7493	0-75
AA129	0-20	BFX12	0-25	NKT251	0-24	OC201	0-55	7494	0-85
AAZ13	0-10	BFX13	0-25	NKT271	0-20	OC201	0-50	7495	0-85
AC107	0-85	BFX20	0-28	NKT272	0-20	OC202	0-90	7496	1-00
AC126	0-25	BFX35	0-60	NKT273	0-20	OC203	0-55	7497	4-32
AC127	0-25	BFX63	0-98	NKT274	0-20	OC204	0-65	74100	2-16
AC128	0-20	BFX84	0-25	NKT275	0-25	OC205	1-00	74101	0-61
AC187	0-20	BFX86	0-25	NKT276	0-25	OC207	1-00	74110	0-57
AC188	0-20	BFX86	0-25	NKT277	0-25	OC207	1-00	74111	0-86
AC197	0-35	BFX87	0-25	NKT304	0-75	OC470	0-30	74118	1-00
AC198	0-27	BFX88	0-22	NKT403	0-70	OC71	1-00	74119	1-92
AC199	0-27	BFY10	1-00	NKT404	0-60	ORP12	0-55	74121	0-57
AC200	0-22	BFY11	1-25	NKT678	0-30	ORP60	0-45	74122	0-80
AC21	0-22	BFY17	0-25	NKT713	0-30	ORP61	0-45	74123	1-44
AC22	0-18	BFY18	0-45	NKT773	0-25	S1PT	0-30	74145	1-44
AC227	0-25	BFY19	0-55	NKT777	0-45	ORP61	0-45	74150	2-30
AC228	0-25	BFY24	0-45	07B	0-38	SFT308	0-38	74151	1-15
AC239	0-65	BFY44	1-00	OA6	0-12	ST722	0-38	74154	2-30
AC240	0-22	BFY50	0-20	OA47	0-08	ST7231	0-63	74155	1-15
AC241	0-22	BFY51	0-20	OA70	0-10	SX681	0-20	74157	1-09
AC244	0-38	BFY52	0-20	OA71	0-10	SX681	0-45	74170	2-88
AD140	0-40	BFY53	0-17	OA72	0-10	SX681	0-45	74171	1-80
AD149	0-50	BFY64	0-45	OA74	0-15	SX640	0-75	74174	2-98
AD161	0-39	BFY90	0-75	OA79	0-10	SX641	0-75	74175	1-29
AD162	0-39	B8X27	0-60	OA81	0-10	SX642	0-60	74176	1-44
AF106	0-30	B8X60	0-98	OA85	0-15	SX644	0-85	74180	2-30
AF114	0-25	B8Y26	0-18	OA86	0-15	SX645	0-85	74191	2-30
AF115	0-25	B8Y26	0-18	OA86	0-15	SX645	0-85	74192	2-30
AF119	0-20	BSY27	0-18	OA91	0-07	V30/201P	0-75	74193	2-30
AF117	0-20	BSY51	0-60	OA90	0-07	V60/201P	0-75	74193	2-30
AF118	0-60	BSY95A	0-12	OA200	0-08	V60/201P	0-75	74194	1-72
AF119	0-20	BSY95	0-12	OA202	0-10	XA101	0-10	74195	1-44
AF124	0-30	BT102/500R	1-10	OA210	0-25	XA102	0-18	74196	1-58
AF125	0-40	BTY42	0-92	OA211	0-20	XA151	0-15	74197	1-58
AF126	0-30	BTY79/100R	0-75	OA200	0-45	XA152	0-15	74197	1-58
AF127	0-30	BTY79/100R	0-75	OA201	0-45	XA161	0-25	74198	3-16
AF139	0-33	BTY79/400R	1-10	OA202	0-45	XA162	0-25	74199	2-88
AF178	0-65	BY100	0-15	OA203	0-45	XB101	0-43		
AF180	0-65	BY126	0-14	OA204	0-45	XB102	0-30	Plug In sockets	
AF181	0-50	BY127	0-15	OA205	0-45	XB103	0-35	—low profile	
AF186	0-40	BY182	0-85	OA206	0-45	XB113	0-30	14 pin DIL	
AFY19	1-18	BY213	0-85	OA207	0-45	XB121	0-43	16 pin DIL	0-15
AFZ11	1-15	BY213	0-85	OA208	0-45	ZR24	0-63	0-17	

Open daily to callers: Mon.-Fri. 9 a.m.-5 p.m.

Valves, Tubes and Transistors • Closed Sat. 1 p.m.-3 p.m.

Terms C.W.O. only • Tel. 01-677 2424-7

All orders subject to V.A.T. at 10% rate. This must be added to the total order including postage.

QUALIFY TO EARN MORE MONEY In a better job

Exciting new career opportunities! They're just waiting to be grasped—in the ever-growing industries of electronics, radio and television. And with ICS behind you, you can soon win the qualifications you need to assure your career success. Win them in your own time, in your own home, by starting an ICS learn-as-you-earn correspondence course now. You get personal, individual attention from really expert and experienced tutors. We teach you the theory, we teach you the practice. Books and components are provided. So is all the assistance, all the backing you need. We also have a complete range of courses at the ready for people keen to score success in other fields. Whatever qualification you're after, we can help you get it, whether you're pushing ahead where you are or switching to something completely new. Take your first step now towards a better paid, more assured future. Send for your FREE Careers Guide today.

Take one of these courses

- Society of Engineers Graduateship (Electrical Engineering)
 - C & G Telecommunications Technicians Certificates
 - C & G Electrical Installation Work
 - C & G Certificate in Technical Communication Techniques
 - C & G Radio Amateurs
 - MPT General Certificate in Radio Telegraphy
 - Audio, Radio and TV Engineering and Servicing
 - Electronic Engineering Maintenance, Engineering systems
 - Instrumentation and Control systems
 - Computer Engineering and Technology
 - Electrical Engineering, Installations, Contracting Appliances
 - Self-build radio courses
 - ... or take one of these if your future lies in other fields
 - GCE O and A Level
 - Basic foundation for success in a thousand and one careers—recognised by everybody.
 - All Boards—64 subjects
 - Management, Marketing and Business
 - Instruction in the latest proved principles and techniques used in each highly specialised area.
 - Personnel
 - Administrative
 - Works
 - Transport
 - Business
 - Industrial
 - Sales
 - Marketing
 - Advertising
 - Marketing
 - Public Relations
 - Sales
 - Business
 - Computers
 - Purchasing
 - Book-keeping
 - Work Study
 - Storekeeping
 - Small Business Owners
 - Fire Service
 - Promotion and Institute of Fire Engineers
 - Police
 - Entrance and Promotion
 - * Courses for appropriate professional exams available in addition to ICS Diploma courses.
- POST TODAY FOR FREE DETAILS**
- # ICS your key to a brighter better future
- To: International Correspondence Schools, Dept. 230X
Intertext House, Stewarts Road, London SW8 4UJ.
- Name
- Address
- Age Occupation
- Accredited by the Council for the Accreditation of Correspondence Colleges.

<p>NEW! NEW! NEW! NEW!</p> <p>An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.</p> <p>Method Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.</p> <p>Light sensitive aerosol spray £1 Developer and Etchant 50p (plus postage)</p>		<p>SILICON P.N.P.</p> <table border="1"> <thead> <tr> <th></th> <th>Voltage</th> <th>Frequency</th> <th>Price</th> </tr> </thead> <tbody> <tr><td>BCY71</td><td>45</td><td>200MHz</td><td>12p</td></tr> <tr><td>BFS92</td><td>100</td><td>70MHz</td><td>20p</td></tr> <tr><td>BFS95</td><td>40</td><td>70MHz</td><td>17p</td></tr> <tr><td>BFX12</td><td>25</td><td>210MHz</td><td>10p</td></tr> <tr><td>2N2906</td><td>60</td><td>200MHz</td><td>15p</td></tr> <tr><td>2N3702</td><td>40</td><td>100MHz</td><td>11p</td></tr> <tr><td>2N3703</td><td>50</td><td>100MHz</td><td>12p</td></tr> </tbody> </table>			Voltage	Frequency	Price	BCY71	45	200MHz	12p	BFS92	100	70MHz	20p	BFS95	40	70MHz	17p	BFX12	25	210MHz	10p	2N2906	60	200MHz	15p	2N3702	40	100MHz	11p	2N3703	50	100MHz	12p	<table border="1"> <tbody> <tr><td>AF124</td><td>20</td><td>75MHz</td><td>20p</td></tr> <tr><td>AFY19</td><td>32</td><td>350MHz</td><td>20p</td></tr> <tr><td>ASY32</td><td>25</td><td>5MHz</td><td>20p</td></tr> <tr><td>ASZ21</td><td>15</td><td>450MHz</td><td>20p</td></tr> <tr><td>GET113</td><td>32</td><td>—</td><td>10p</td></tr> <tr><td>GET120</td><td>32</td><td>2 watts</td><td>10p</td></tr> <tr><td>OC123</td><td>50</td><td>1MHz</td><td>10p</td></tr> <tr><td>OCP70</td><td>Light-sensitive</td><td>—</td><td>20p</td></tr> <tr><td>2N1307</td><td>30</td><td>10MHz</td><td>15p</td></tr> <tr><td>2N1309</td><td>30</td><td>15MHz</td><td>15p</td></tr> <tr><td>2N443</td><td>60</td><td>150 watts</td><td>10p</td></tr> </tbody> </table>		AF124	20	75MHz	20p	AFY19	32	350MHz	20p	ASY32	25	5MHz	20p	ASZ21	15	450MHz	20p	GET113	32	—	10p	GET120	32	2 watts	10p	OC123	50	1MHz	10p	OCP70	Light-sensitive	—	20p	2N1307	30	10MHz	15p	2N1309	30	15MHz	15p	2N443	60	150 watts	10p	<table border="1"> <tbody> <tr><td>BXY27</td><td>Varactor Diode. "S" Band.</td><td>£1</td></tr> <tr><td></td><td>Cut-off, 70 GHz</td><td></td></tr> <tr><td>BXY28</td><td>Varactor Diode. Cut-off, 100GHz</td><td>£1</td></tr> <tr><td>BXY32</td><td>Frequency Multiplier. "X" Band, 150GHz</td><td>£1</td></tr> <tr><td>BXY35A/C</td><td>Frequency Multiplier. "X" Band, 25GHz</td><td>£1</td></tr> <tr><td>BXY36C/D</td><td>Frequency Multiplier. "X" Band, 75GHz</td><td>£1</td></tr> <tr><td>BXY37C/D</td><td>Frequency Multiplier. "X" Band, 100GHz</td><td>£1</td></tr> <tr><td>BXY38C/E</td><td>Frequency Multiplier. "X" Band, 120GHz</td><td>£1</td></tr> <tr><td>BXY39C/D</td><td>Frequency Multiplier. "X" Band, 150GHz</td><td>£1</td></tr> <tr><td>BXY40D/E</td><td>Frequency Multiplier. "X" Band, 180GHz</td><td>£1</td></tr> <tr><td>BXY41C/D/E</td><td>Frequency Multiplier. "X" Band, 200 GHz</td><td>£1</td></tr> <tr><td>CV7777</td><td>(AAY51) Microwave Mixer Diode, 18GHz</td><td>£2</td></tr> <tr><td>CAY10</td><td>Microwave Detector Diode, 250GHz</td><td>£5</td></tr> <tr><td>AEY13</td><td>Microwave Tunnel Diode, 6GHz</td><td>£5</td></tr> <tr><td>AEY16</td><td>Microwave Tunnel Diode, 10GHz</td><td>£10</td></tr> <tr><td>AEY17</td><td>Microwave Detector, 18 GHz</td><td>£3</td></tr> <tr><td>AEY31A</td><td>Microwave Detector, 18 GHz</td><td>£3</td></tr> <tr><td>BAW95</td><td>Schottky Barrier Diode, 12GHz</td><td>50p</td></tr> </tbody> </table>		BXY27	Varactor Diode. "S" Band.	£1		Cut-off, 70 GHz		BXY28	Varactor Diode. Cut-off, 100GHz	£1	BXY32	Frequency Multiplier. "X" Band, 150GHz	£1	BXY35A/C	Frequency Multiplier. "X" Band, 25GHz	£1	BXY36C/D	Frequency Multiplier. "X" Band, 75GHz	£1	BXY37C/D	Frequency Multiplier. "X" Band, 100GHz	£1	BXY38C/E	Frequency Multiplier. "X" Band, 120GHz	£1	BXY39C/D	Frequency Multiplier. "X" Band, 150GHz	£1	BXY40D/E	Frequency Multiplier. "X" Band, 180GHz	£1	BXY41C/D/E	Frequency Multiplier. "X" Band, 200 GHz	£1	CV7777	(AAY51) Microwave Mixer Diode, 18GHz	£2	CAY10	Microwave Detector Diode, 250GHz	£5	AEY13	Microwave Tunnel Diode, 6GHz	£5	AEY16	Microwave Tunnel Diode, 10GHz	£10	AEY17	Microwave Detector, 18 GHz	£3	AEY31A	Microwave Detector, 18 GHz	£3	BAW95	Schottky Barrier Diode, 12GHz	50p			
	Voltage	Frequency	Price																																																																																																																																									
BCY71	45	200MHz	12p																																																																																																																																									
BFS92	100	70MHz	20p																																																																																																																																									
BFS95	40	70MHz	17p																																																																																																																																									
BFX12	25	210MHz	10p																																																																																																																																									
2N2906	60	200MHz	15p																																																																																																																																									
2N3702	40	100MHz	11p																																																																																																																																									
2N3703	50	100MHz	12p																																																																																																																																									
AF124	20	75MHz	20p																																																																																																																																									
AFY19	32	350MHz	20p																																																																																																																																									
ASY32	25	5MHz	20p																																																																																																																																									
ASZ21	15	450MHz	20p																																																																																																																																									
GET113	32	—	10p																																																																																																																																									
GET120	32	2 watts	10p																																																																																																																																									
OC123	50	1MHz	10p																																																																																																																																									
OCP70	Light-sensitive	—	20p																																																																																																																																									
2N1307	30	10MHz	15p																																																																																																																																									
2N1309	30	15MHz	15p																																																																																																																																									
2N443	60	150 watts	10p																																																																																																																																									
BXY27	Varactor Diode. "S" Band.	£1																																																																																																																																										
	Cut-off, 70 GHz																																																																																																																																											
BXY28	Varactor Diode. Cut-off, 100GHz	£1																																																																																																																																										
BXY32	Frequency Multiplier. "X" Band, 150GHz	£1																																																																																																																																										
BXY35A/C	Frequency Multiplier. "X" Band, 25GHz	£1																																																																																																																																										
BXY36C/D	Frequency Multiplier. "X" Band, 75GHz	£1																																																																																																																																										
BXY37C/D	Frequency Multiplier. "X" Band, 100GHz	£1																																																																																																																																										
BXY38C/E	Frequency Multiplier. "X" Band, 120GHz	£1																																																																																																																																										
BXY39C/D	Frequency Multiplier. "X" Band, 150GHz	£1																																																																																																																																										
BXY40D/E	Frequency Multiplier. "X" Band, 180GHz	£1																																																																																																																																										
BXY41C/D/E	Frequency Multiplier. "X" Band, 200 GHz	£1																																																																																																																																										
CV7777	(AAY51) Microwave Mixer Diode, 18GHz	£2																																																																																																																																										
CAY10	Microwave Detector Diode, 250GHz	£5																																																																																																																																										
AEY13	Microwave Tunnel Diode, 6GHz	£5																																																																																																																																										
AEY16	Microwave Tunnel Diode, 10GHz	£10																																																																																																																																										
AEY17	Microwave Detector, 18 GHz	£3																																																																																																																																										
AEY31A	Microwave Detector, 18 GHz	£3																																																																																																																																										
BAW95	Schottky Barrier Diode, 12GHz	50p																																																																																																																																										
<p>NEWER THAN NEW!!!</p> <p>Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.</p> <table border="1"> <tbody> <tr><td>75mm x 100mm</td><td>33p</td></tr> <tr><td>150mm x 100mm</td><td>66p</td></tr> <tr><td>150mm x 200mm</td><td>£1.32</td></tr> </tbody> </table>		75mm x 100mm	33p	150mm x 100mm	66p	150mm x 200mm	£1.32	<p>SPECIAL OFFER</p> <p>UNI-JUNCTION TRANSISTOR SIMILAR TO 2N246 25p</p> <table border="1"> <tbody> <tr><td>BC108</td><td>30</td><td>150MHz</td><td>10p</td></tr> <tr><td>BC109</td><td>30</td><td>150MHz</td><td>10p</td></tr> <tr><td>BF179</td><td>225</td><td>125MHz</td><td>40p</td></tr> <tr><td>BF180</td><td>30</td><td>625MHz</td><td>25p</td></tr> <tr><td>BFW58</td><td>80</td><td>80MHz</td><td>15p</td></tr> <tr><td>BFX43</td><td>30</td><td>500MHz</td><td>20p</td></tr> <tr><td>BFX86</td><td>40</td><td>50MHz</td><td>17p</td></tr> <tr><td>BFY53</td><td>30</td><td>50MHz</td><td>10p</td></tr> <tr><td>BSX19</td><td>40</td><td>500MHz</td><td>10p</td></tr> <tr><td>BSX67</td><td>30</td><td>200MHz</td><td>12p</td></tr> <tr><td>2N697</td><td>60</td><td>40MHz</td><td>12p</td></tr> <tr><td>2N709</td><td>15</td><td>900MHz</td><td>30p</td></tr> <tr><td>2N718</td><td>60</td><td>60MHz</td><td>12p</td></tr> <tr><td>2N753</td><td>25</td><td>250MHz</td><td>12p</td></tr> <tr><td>2N744</td><td>20</td><td>300MHz</td><td>12p</td></tr> <tr><td>2N1613</td><td>75</td><td>60MHz</td><td>17p</td></tr> <tr><td>2N2220</td><td>60</td><td>250MHz</td><td>15p</td></tr> <tr><td>2N3053</td><td>60</td><td>100MHz</td><td>17p</td></tr> <tr><td>2N3707</td><td>30</td><td>—</td><td>12p</td></tr> <tr><td>2N5179</td><td>20</td><td>900MHz</td><td>40p</td></tr> </tbody> </table>		BC108	30	150MHz	10p	BC109	30	150MHz	10p	BF179	225	125MHz	40p	BF180	30	625MHz	25p	BFW58	80	80MHz	15p	BFX43	30	500MHz	20p	BFX86	40	50MHz	17p	BFY53	30	50MHz	10p	BSX19	40	500MHz	10p	BSX67	30	200MHz	12p	2N697	60	40MHz	12p	2N709	15	900MHz	30p	2N718	60	60MHz	12p	2N753	25	250MHz	12p	2N744	20	300MHz	12p	2N1613	75	60MHz	17p	2N2220	60	250MHz	15p	2N3053	60	100MHz	17p	2N3707	30	—	12p	2N5179	20	900MHz	40p	<p>HIGH FREQUENCY, POWER</p> <table border="1"> <tbody> <tr><td>BFR64</td><td>40</td><td>1200MHz</td><td>£1</td></tr> <tr><td>BLY89A</td><td>35</td><td>650MHz</td><td>£5</td></tr> <tr><td>BLY93A</td><td>60</td><td>500MHz</td><td>£5</td></tr> <tr><td>BLY218</td><td>36</td><td>1200MHz</td><td>£2</td></tr> <tr><td>2N709</td><td>15</td><td>800MHz</td><td>15p</td></tr> <tr><td>2N3926</td><td>36</td><td>250MHz</td><td>10p</td></tr> </tbody> </table>		BFR64	40	1200MHz	£1	BLY89A	35	650MHz	£5	BLY93A	60	500MHz	£5	BLY218	36	1200MHz	£2	2N709	15	800MHz	15p	2N3926	36	250MHz	10p	<p>MICROWAVE DEVICES</p> <table border="1"> <thead> <tr> <th></th> <th>Price</th> </tr> </thead> <tbody> <tr><td>CL8300</td><td>Gunn effect oscillator, 9.4GHz</td><td>£40</td></tr> <tr><td>CL8370</td><td>Gunn effect oscillator, 9.5GHz</td><td>£10</td></tr> <tr><td>CL8380</td><td>Gunn effect oscillator, 10.5GHz</td><td>£10</td></tr> <tr><td>CL8390</td><td>Gunn effect oscillator, 11.5GHz</td><td>£10</td></tr> <tr><td>CL8430</td><td>Gunn effect oscillator, 9.35GHz</td><td>£40</td></tr> <tr><td>CL8450</td><td>Gunn effect oscillator, 9.35GHz</td><td>£40</td></tr> <tr><td>CL8470</td><td>Gunn effect oscillator, 9.35GHz</td><td>£40</td></tr> </tbody> </table>			Price	CL8300	Gunn effect oscillator, 9.4GHz	£40	CL8370	Gunn effect oscillator, 9.5GHz	£10	CL8380	Gunn effect oscillator, 10.5GHz	£10	CL8390	Gunn effect oscillator, 11.5GHz	£10	CL8430	Gunn effect oscillator, 9.35GHz	£40	CL8450	Gunn effect oscillator, 9.35GHz	£40	CL8470	Gunn effect oscillator, 9.35GHz	£40
75mm x 100mm	33p																																																																																																																																											
150mm x 100mm	66p																																																																																																																																											
150mm x 200mm	£1.32																																																																																																																																											
BC108	30	150MHz	10p																																																																																																																																									
BC109	30	150MHz	10p																																																																																																																																									
BF179	225	125MHz	40p																																																																																																																																									
BF180	30	625MHz	25p																																																																																																																																									
BFW58	80	80MHz	15p																																																																																																																																									
BFX43	30	500MHz	20p																																																																																																																																									
BFX86	40	50MHz	17p																																																																																																																																									
BFY53	30	50MHz	10p																																																																																																																																									
BSX19	40	500MHz	10p																																																																																																																																									
BSX67	30	200MHz	12p																																																																																																																																									
2N697	60	40MHz	12p																																																																																																																																									
2N709	15	900MHz	30p																																																																																																																																									
2N718	60	60MHz	12p																																																																																																																																									
2N753	25	250MHz	12p																																																																																																																																									
2N744	20	300MHz	12p																																																																																																																																									
2N1613	75	60MHz	17p																																																																																																																																									
2N2220	60	250MHz	15p																																																																																																																																									
2N3053	60	100MHz	17p																																																																																																																																									
2N3707	30	—	12p																																																																																																																																									
2N5179	20	900MHz	40p																																																																																																																																									
BFR64	40	1200MHz	£1																																																																																																																																									
BLY89A	35	650MHz	£5																																																																																																																																									
BLY93A	60	500MHz	£5																																																																																																																																									
BLY218	36	1200MHz	£2																																																																																																																																									
2N709	15	800MHz	15p																																																																																																																																									
2N3926	36	250MHz	10p																																																																																																																																									
	Price																																																																																																																																											
CL8300	Gunn effect oscillator, 9.4GHz	£40																																																																																																																																										
CL8370	Gunn effect oscillator, 9.5GHz	£10																																																																																																																																										
CL8380	Gunn effect oscillator, 10.5GHz	£10																																																																																																																																										
CL8390	Gunn effect oscillator, 11.5GHz	£10																																																																																																																																										
CL8430	Gunn effect oscillator, 9.35GHz	£40																																																																																																																																										
CL8450	Gunn effect oscillator, 9.35GHz	£40																																																																																																																																										
CL8470	Gunn effect oscillator, 9.35GHz	£40																																																																																																																																										
<p>£1 100 WATT RESISTORS 100 CERAMIC CAPACITORS 100 DIODES</p> <p>POSTAGE 20p</p>		<p>£1 1 VEROBOARD CUTTER 5 2 1/2 in x 0.15 BOARDS 50 SQ. IN "ODD PIECES" VERO</p> <p>POSTAGE 20p</p>		<p>£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108, ETC.</p> <p>POSTAGE 20p</p>		<p>£1 6 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS AND CAPACITORS</p> <p>POSTAGE 27p</p>																																																																																																																																						
<p>£1 100 RESISTORS 100 CERAMIC CAPACITORS 100 POLYSTYRENE CAPACITORS</p> <p>POSTAGE 20p</p>		<p>£1 100 RESISTORS 100 CERAMIC CAPACITORS 50 MULLARD POLYESTER CAPACITORS</p> <p>POSTAGE 20p</p>		<p>£1 1 TRANSISTORISED SIGNAL TRACER KIT 1 TRANSISTORISED SIGNAL INJECTOR KIT</p> <p>POSTAGE 20p</p>		<p>£1 100 RESISTORS 100 CAPACITORS (ASSORTED TYPES)</p> <p>POSTAGE 20p</p>																																																																																																																																						
<p>POSTAGE (MINIMUM) 20P PER ORDER</p>				<p>ALL GOODS PLUS 10% V.A.T.</p>																																																																																																																																								

D.I.Y. ELECTRONIC ORGAN KITS AS USED BY PROFESSIONALS THROUGHOUT THE WORLD



★ Portable—4 octave keyboard with 10 voices, 3 pitches—vibrato, £145.29. ★ Console—5 octave keyboard with 10 voices, 3 pitches. Keyboard can be split into solo and accompaniment. Vibrato, built in amplifier and speaker £250.93. ★ Console—2 x 4 octave keyboards and 13 note pedal board, 29 voices, Vibrato, Delay Vibrato, Sustain, Reverberation, Precussion, Wah Wah, £406.00. ★ Console—2 x 5 octave keyboards and 32 note pedal board, 32 voices. Vibrato, Delay Vibrato, Sustain Reverberation, Precussion, 3 Couplers, etc., at £572.55.

ALL COMPONENTS CAN BE BOUGHT SEPARATELY. SEND 50p FOR LATEST CATALOGUE, WHICH INCLUDES SPECIALIZED COMPONENTS, HI-FI EQUIPMENT, ELECTRICAL HOUSEHOLD APPLIANCES. PLUS 5 x 10p VOUCHERS.

ELVINS ELECTRONIC MUSICAL INSTRUMENTS

YOU ARE WELCOME TO VISIT THE ONLY D.I.Y. ELECTRONIC ORGAN CENTRE IN EUROPE AT 12 BRETT ROAD, HACKNEY, LONDON, E.8. TEL. 01-986 8455

LASKY'S

1974

CATALOGUE

FREE Send this coupon with 15p for post and inclusion on our regular mailing list.

NAME

ADDRESS

.....

AUDIOTRONIC HOUSE, THE HYDE, LONDON, NW9 6JJ

parts for **PRACTICAL ELECTRONICS** projects.

"One Source" buying makes sense—saves you time, money and postage.

"P.E. RONDO" QUADRAPHONIC SOUND SYSTEM

Complete kits for the entire P.E. Rondo Project will be available as this appears in the magazine. These contain top quality components with fibre glass p.c. board, etc. etc.

"P.E." F.M. VARICAP STEREO TUNER

Electro Spares offer a kit of high quality parts to the published specification for this remarkable tuner, featured in "Practical Electronics", May 1973.

Features include pushbutton "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord).

Easy "no problem" construction requiring only a few simple setting up adjustments with a d.c. Voltmeter.

Uses NEW pre-set modules for R.F. and I.F. circuits—no circuit alignment. High efficiency integrated circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator.

Fibre Glass P.C. Board, neat slim-line cabinet, with brushed aluminium front panel, pushbuttons, etc. etc.

IDEAL FOR USE WITH THE "TEXAN", "P.E. GEMINI" AND ANY GOOD QUALITY STEREO AMPLIFIER.

"P.E. GEMINI" STEREO AMPLIFIER

QUALITY HI-FI FOR THE HOME CONSTRUCTOR.

30 Watts (R.M.S.) per Channel into 8 ohms!

Total Harmonic Distortion 0.02%!

Frequency Response (—3 dB) 20 Hz—100kHz!

We are still continuing to supply components for this fabulous amplifier, which is now recognised as practically the ultimate in High Fidelity. We know of no better unit for the home constructor, and can supply a booklet, containing full specification, complete constructional information, wiring diagrams, fault finding guide, etc. etc., price 55p plus 4p postage.

Our *new, low* comprehensive price list is supplied with each booklet, or prices for components supplied separately on receipt of large S.A.E.

FOR PEOPLE WHO REQUIRE THE BEST—IT HAS TO BE THE "p.e. gemini"

ALL PARTS for Varicap tuner and Gemini amplifier supplied separately.

Please send S.A.E. for full details of any of the above or call yourself. Visitors welcome—easy parking.

**ELECTRO
SPARES**

The Component Centre of the North.

288 Ecclesall Road
Sheffield S11 8PE
Tel.: Sheffield (0742)
668888

es

NEW QUICK and EFFICIENT MAIL ORDER DEPARTMENT

P.E. SOUND SYNTHESISER



SIMPLY SEND EXACT DETAILS OF NAME AND NUMBER COPIED FROM THE FACE OF YOUR ACCESS CARD AND LEAVE THE REST TO US.

'DESIGNER APPROVED KITS'

The 'RING MODULATOR' I.C.

SG 3402N

£1.74 each

TRANSISTOR ARRAY

ML 3046P

75p each

Z1J NOISE DIODE

43.5p each

mini D.I.L.

741's 32p each

while stocks last

4p stamp brings latest lists

Attractive discounts on quantity purchases.

We stock a full range of professional quality components as specified for this exciting project and many prices are down.
2% M.O. resistors now 3.2p ea. 5% low noise carbon film 1.8p ea. Cermet presets now 37.5p ea. Full range of capacitors—Ceramic, Electrolytic, Polyester, Styrene, Carbonate, Silver Mica, etc. Modular hardware kits; Dual-Rail Regulated Power Supplies; Individual component/module kits from date of publication. P.C.B. for the exciting 'Hutchinson' Tone Control Module.

EATON AUDIO P.O. Box No. 3, ST. NEOTS HUNTINGDON PE19 3JB

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2. Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P. All prices subject to V.A.T.



TO SPARK YOUR IMAGINATION!

the **SPARKRITE**

Electronic Ignition Kit

only

£9.35


Kit comprises EVERYTHING
Case, cables, coil connectors,
Silicon grease,
8 page instruction leaflet.

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance.
- Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls.
- Longer spark plug life.
- Longer battery life.
- Contact breaker burn eliminated.
- Purer exhaust gas emission.

A new development from the manufacturers of Gunton Ignition. Price: £9.35 inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available £11.55 inc. V.A.T. and postage. GUARANTEED 5 YEARS.

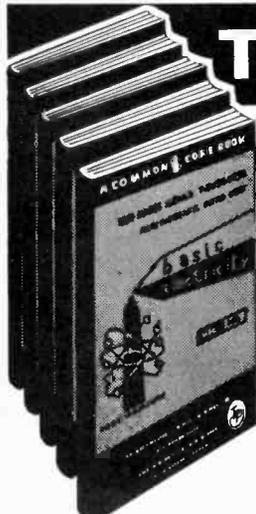ORDER NOW—send P.O./Cheque direct to:
ELECTRONICS DESIGN ASSOCIATES, Dept. PE11
82 Bath St., Walsall WS1 3DE. Phone: 33652



The Pictorial Method

BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE

Should you be, in any way dissatisfied with the **MANUALS** your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

Delighted with the excellent publication. As a retired electrical engineer, Electronics is a new field for me to take up as a hobby.
H.W., Leamington

Although they are very instructive they are very easy and quickly read.
L.T., Swansea

Many thanks indeed including my own and heartiest appreciation of a fine set of volumes and at such an almost nominal price.
B.L., Trowbridge

To The **SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP**

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £4.50

BASIC ELECTRONICS 6 parts £5.40

BASIC TELEVISION 3 parts £3.60

Tick Set(s) required. Prices include Postage and Packing.

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME
BLOCK LETTERS

FULL POSTAL.....

ADDRESS

POST NOW FOR THIS OFFER!

LARGE STOCKS, ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new and to makers' specifications.

ELECTROVALUE

Electronic Component Specialists

TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power	60p
AC153K pnp germanium low power	32p
AC176K npn germanium low power	32p
AD161 npn germanium medium power	42p
AD162 pnp germanium medium power	40p
AF139 pnp germanium UHF	49p
NPN: BC107 13p, BC108 12p, BC109 13p, BC167 11p, BC168 10p, BC169 11p.	
PNP: BC177 21p, BC178 19p, BC179 21p, BC257 12p, BC258 11p, BC259 13p.	

Standard groupings available.
BD135 npn medium power 37p
BD136 pnp medium power 38p

DIODES

OA90, OA91, OA95, 6p each; OA200, 9p; OA202, 10p.


Other semiconductors: AC128, 17p; AF117, 32p; BFY51, 19p. Full lists and technical data will be found in Catalogue No. 6. See also amendments list.

Send S.A.E. for latest supplement of additional lists and price amendments to our No. 6 Catalogue

ZENER DIODES

full range E24 values: 400mW: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

DIN PLUGS AND SOCKETS

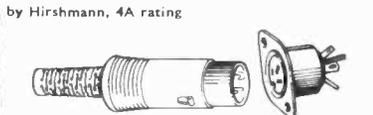

by Hirshmann, 4A rating

2 way LS —socket 10p, plug 12p
3 way scr.—socket 10p, plug 12p
5 way scr.—socket 11p, plug 15p

TRANSISTOR ACCESSORIES

TO3 cover, 7p; Heat sinks 1°C/W, type 6W1, undrilled, 60p.

SWITCHES

1011 SPST toggle, 20p; 409 DPDT toggle, 29p (these are chrome plated, 2.5A rating); 7201 sub-miniature DPDT 250V a.c./2A, 48p.

ROTARY SWITCHES

Radiospares Miniature Maka-switch (in assembly kit form). Shaft, 48p. Wafers, MBB-2P5W, IP111W: BBM/IP12W, 2P6VW, 3P4VW, 4P3VW, 6P2VW, 32p each.

WAVECHANGE SWITCHES

IP12W, 2P6VW, 3P4VW, 413W, 24p each.

ELECTROLYTIC CAPACITORS

Rated voltage:	3V	6.3V	10V	16V	25V	40V	63V	100V
Capacity μ F	0-47	—	—	—	—	—	10p	7p
	1-0	—	—	—	—	10p	—	7p
	2-2	—	—	—	10p	—	7p	8p
	4-7	—	—	10p	—	—	7p	8p
	10	—	—	—	7p	8p	7p	8p
	22	—	—	7p	7p	7p	7p	9p
	47	7p	—	8p	8p	8p	7p	9p
	100	8p	7p	7p	7p	7p	9p	12p
	220	7p	8p	8p	8p	9p	10p	17p
	470	8p	9p	9p	10p	12p	17p	24p
	1,000	10p	12p	12p	17p	20p	24p	40p
	2,200	14p	17p	22p	25p	36p	40p	—
	4,700	25p	28p	37p	41p	54p	—	—
	10,000	40p	43p	—	—	—	—	—

Prices subject to amendment by the manufacturer.

RESISTORS - 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 Ω -220K Ω	E12	9	(see note below)	7.5
C	1/8W	5%	4.7 Ω -470K Ω	E24	1	0.9	0.75 nett
C	1/4W	5%	4.7 Ω -10M Ω	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7 Ω -10M Ω	E24	1.2	1	0.95 nett
C	1W	5%	4.7 Ω -10M Ω	E12	2.5	2	1.6 nett
MO	1/2W	2%	10 Ω -1M Ω	E24	4	3	2 nett
WW	1W	10%	1/20 Ω -3.9 Ω	E12	7	7	6
WW	3W	5%	1 Ω -10K Ω	E12	7	7	6
WW	7W	5%	1 Ω -10K Ω	E12	9	9	8


Codes: C = carbon film, high stability, low noise. MO = metal oxide, Electrofil TR5, ultra low noise. WW = wire wound, Plessey.

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

KNOBS

All grub screw fitting for pin shafts. Black. For other types see Catalogue No. 6, p. 54.

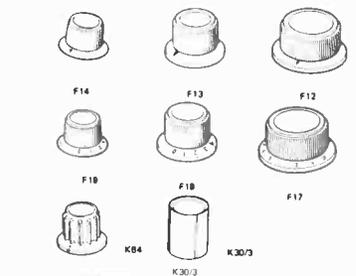F.14 (20mm) pack of 2, 32p; F.13 (26mm) pack of 2, 38p; F.12 (33mm) pack of 2, 40p; F.19 (20mm) pack of 2, 32p; F.18 (26mm) pack of 2, 38p; F.17 (33mm) pack of 2, 40p; KB.4 (20mm) pack of 4, 40p; K30/3 (17mm) aluminium, 24p each.



TRANSFORMERS—MAINS

MT3 30V/2A plus 4 taps	£2.85
MT103 50V/1A plus 4 taps	£2.55
MT104 50V/2A plus 4 taps	£3.50
MT127 60V/2A plus 4 taps	£3.80
13TOS 13V/1A, CT	£1.25
28TOS 12+12V, 2-0-2V.	£1.65

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS. 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14.90 Plus 60p part cost of carr.

Equaliser Assembly, £2.
Loudspeaker Unit 59RM109, £2.45.
Cabinet Kit (to Baxandall design), £10.45.

POLYCARBONATE—5% TOLERANCE

250V up to 0-1 μ F: 100V, 0-1 μ F and above.
0.01; 0.012; 0.015; 0.018; 0.022; 0.027; 0.033; 0.047; 0.056; 0.063; 0.068; 0.082; 0.1; 0.12; 0.15; 4p each. 0.18; 0.22; 5p each. 0.27; 0.33; 6p. 0.39 7p. 0.47 8p. 0.56 10p. 0.68 11p. 1 μ F 13p. Prices subject to amendment by the manufacturer.

Minitron Digital Counter

Type 3015F. Seven Filament segment indicators to make 0-9 + decimal point. Compatible with standard logic modules, nett £2. Decoder driver type FLL 121T nett £1.36. DIL socket, nett £2.

POTENTIOMETERS

Rotary, carbon track, double wipe
SINGLE P20 lin. 100 Ω to 2.2M Ω , 12p; P20 log. 4.7K Ω to 2.2M Ω , 12p; JP20 log. 4.7K Ω to 2.2M Ω , 12p; Dual gang lin. 4.7K Ω to 2.2M Ω , 42p; Dual log. 4.7K Ω to 2.2M Ω , 42p; Log/antilog, 10K, 22K, 47K, 1M Ω only, 42p; Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.
Only decades of 10, 22 and 47 available in ranges quoted.
DUAL CONCENTRIC DP20 in any combination of P20 values, 60p; with switch, 72p.
SLIDER
Lin. or log, 10K to 1 meg. in all popular values, each 26p.
Control knobs blk./white/red/yel./gr./blue/dk. grey/lt. grey, 5p each.

CARBON SKELETON PRESETS
Small high quality, PR lin. 100 Ω , 220 Ω , 470 Ω , 1K, 2K, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M Ω . Vertical or horizontal mounting, 5p each.

DISCOUNTS

All items offered for sale in accordance with our stated terms of business, copy of which available on request.
Not allowed on nett price items. 10% on orders for £5 or more. 15% on orders of £15 or more.
Prices subject to alteration without prior notice. Prices quoted DO NOT include V.A.T.
Orders received from U.K. customers must be accompanied by an additional 10% of the nett value for V.A.T.
Overseas orders are exempt.
POSTAGE AND PACKING FREE
SURCHARGE 10p on small mail orders under £2.
Overseas orders carriage and insurance charged at cost. U.S.A. CUSTOMERS please contact ELECTROVALUE, AMERICA, P.O. BOX 27, Swarthmore, PA 19081.

ALL OUR PRICES INCLUDE V.A.T.

BSR LATEST SUPERSLIM STEREO & MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 month guarantee. AC 200/250V. Size 18½ x 11½ in. Above motor board 3½ in. Below motor board 2½ in. with STEREO and MONO XTAL £8.25 Post 25p. **PORTABLE PLAYER CABINET** Modern design. Black resin covered. Silver front grille. Padded Lid. Chrome fittings. Motor board cut for BSR deck £4.50 Post 25p



4 Transistor Mono Amplifier

Powerful 3 watt output. 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make. Size 8in wide x 4in deep x 3in high. **PRICE £5.95** Post 25p

Suitable 7in x 4in speaker, £1.

BSR JUNIOR SINGLE PLAYER

Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono £4.95 compatible cartridge.



GARRARD DECCA HI-FI DECK

Single play Stereo/Mono Derram transcription head and arm. Four speeds. 10½in turntable. Anti-rumble filter. Bias compensation. Laboratory motor. **SPECIAL PRICE £18.50** Post 25p Ideal for Deck Decks



METAL PLINTH AND PLASTIC COVER

Cut out for most Garrard or B.S.R. Most will play with cover in position. 12" x 14" x 7½ in. Covered in black leatherette. **£4.95** Post 35p

ALSO AVAILABLE IN SOLID NATURAL MAHOAGANY WAX POLISHED FINISH—AT SAME PRICE

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13½ x 10 x 3½ in. Player unit clips to loudspeakers making it extremely compact, overall size only 13½ x 10 x 8½ in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls. **£25** Post 25p



Attractive Teak finish Weight 13 lb. **£25** 85p Carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

Single pole two-way surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights etc. Variable knob. Turn on or off at full or intermediate settings. Two types available type A 0 to 60 minutes or type B 0 to 6 hours. Fully insulated. Makers last list price £4.50. Brand new and fully guaranteed. **OUR PRICE £1.65** P. & P. 15p or £3 pair (STATE TYPE A OR B WITH ORDER.)



BLANK ALUMINIUM CHASSIS. 18 a.w.g. 2½in sides 6 x 4in 45p; 8 x 6in 53p; 10 x 7in 65p; 12 x 8in 85p; 14 x 9in 90p; 16 x 9in 90p; 12 x 3in 50p; 16 x 10in £1. ALUMINIUM BOXES 3 x 3 x 3in 60p; 4 x 4 x 4in 70p; 6 x 4 x 4in 90p; 8 x 4 x 4in £1.12; 4 x 4in £1.30. ALUMINIUM PANELS 18 a.w.g. 6 x 4in 9p; 8 x 6in 15p; 14 x 3in 16p; 10 x 7in 19p; 12 x 5in 20p; 12 x 8in 28p; 16 x 8in 28p; 14 x 9in 34p; 12 x 12in 40p; 16 x 10in 50p. PAXOLIN PANEL 10 x 8in 15p. 1½ inch DIAMETER WAVELENGTH SWITCHES. 25p. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way, 25p each. 1 p. 2-way, or 4 p. 2-way, or 4 p. 3-way, 25p. TOGGLE SWITCHES. sp. 14p; dp. 22p; dp. dt. 22p. Sub-miniature, sp. 30p; dp. 37p; dp. dt. 45p.

BRITISH FM/VHF TUNING HEART 88 to 108 Mc/s British made. 2 Transistors ready aligned requires 10-7 Mc/s I.F. Complete with tuning gang. Connections supplied but some technical experience essential. **Our price £3.95** Post 20p

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 16 or 18 or 20V d.c. at 100mA or less. PLEASE STATE VOLTAGE REQUIRED. **£2.20** Post 20p Details S.A.E. Size 3½ x 1½ x 1½ in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V d.c. operation. Size: 1½ x 1½ x 1½ in. Response 25 c/s to 25 kc/s. 28 dB gain. For use with valve or transistor equipment. **99p** Post 20p Full instructions supplied. Details S.A.E.

NEW TUBULAR ELECTROLYTICS	CAN TYPES
2/300V 14p	250/25V 14p
4/350V 14p	500/25V 20p
8/450V 18p	1000/25V 35p
16/450V 22p	1000/50V 47p
32/500V 50p	8 + 8/450V 22p
25/25V 10p	8 + 16/450V 25p
50/50V 10p	16 + 16/450V 40p
100/25V 10p	32 + 32/350V 55p
	100 + 50 - 50/350V 55p

LOW VOLTAGE ELECTROLYTICS
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.
500mF 12V 15p; 25V 20p; 50V 30p.
1000mF 12V 20p; 25V 35p; 50V 47p; 100V 70p.
2000mF 6V 25p; 25V 42p; 50V 57p.
2500mF 50V 82p; 300mF 25V 47p; 50V 85p.
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.
CERAMIC 1pF to 0.1mF 4p. Silver Mica 2 to 500mF 4p.
PAPER 350V-0.1 4p; 0-5 13p; 1mF 15p; 2mF 150V 15p.
500V-0.01 to 0.05 4p; 0.1 5p; 0.25 8p; 0.47 25p.
SILVER MICA. Close tolerance 1%. 2-2-500pF 8p; 580-2.200pF 10p; 2.700-5.600pF 20p; 6.800pF-0.01, ml 30p each.
TWIN GANG. "0-0" 20pF; 176pF, 85p.
Slow motion drive 35pF + 385pF weight, 10 watt, 50p.
500pF standard type; amber 3-sec. 500pF £1.60.
SHORT WAVE SINGLE. 10pF, 30p; 25pF, 55p; 50pF, 65p.

SHORT WAVE SINGLE GANG. Precision Silver Plated Gangable Tuning Condensers. **50p** each Values up to 100pF. Section Couplers supplied FREE with two or more gangs.

NEON PANEL INDICATORS 250V AC/DC. Amber 20p. RESISTORS: 1W, ½W, 1W, 20p, 1p; 2W, 5p. 10Ω to 10MΩ. HIGH STABILITY. ½W 2%, 10 ohms to 8 meg., 10p. Ditto 5%. Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt. 10 ohms to 100k 10p each; 0.5 ohm to 2 ohms 10p. TAPE OSCILLATOR COIL Valve type 35p. FERRITE ROD 8 x ½in 20p; 8 x ¼in 20p; 3 x ¼in 10p.

MAINS TRANSFORMERS ALL POST 25p each

Eagle MT12 12-0-12V 50mA	90p
250-0-250 80 mA 6.3V 7.5 8 9 10 11 12 13 14 15 16 17 18 19 20 21 22 23 24 25 26 27 28 29 30 31 32 33 34 35 36 37 38 39 40 41 42 43 44 45 46 47 48 49 50 51 52 53 54 55 56 57 58 59 60 61 62 63 64 65 66 67 68 69 70 71 72 73 74 75 76 77 78 79 80 81 82 83 84 85 86 87 88 89 90 91 92 93 94 95 96 97 98 99 100	£2.50
300-0-350 80 mA 6.3V 3.5A, 6.3V 1A or 5V 2A	£3.00
300-0-300V 120mA, 6.3V 4A CT., 6.3V 2A	£3.25
MINIATURE 200V 20mA, 6.3V 1A 2p; 2 x 2in. 75p	
MIDGET 220V 45mA, 6.3V 2A 2p; 2 x 2in. 90p	
HEATER TRANS. 6-3V 2A	60p
GENERAL PURPOSE LOW VOLTAGE Tapped outputs at 2 amp. 3, 4, 5, 6, 8, 10, 12, 15, 18, 24, 30 and 30V £2.80	
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £2.25	
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £3.80	
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8.75	
3 amp, 5, 8, 10 and 13V £1.00; Ditto 5 amp £1.20; 3 amp, 3, 5, 8, 10, 13 and 5-0-5V £1.30; Ditto 5 amp, £1.60; 6-0-6V 500mA 95p; 12V 1 amp 95p; 12V 300mA 75p; 12V 500mA 85p; 12V 750mA 95p; 40V 1 amp £1.75.	
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £2.25; 500W £6.25; 750W £10; 1000W £15	
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12V, 1 amp £1.50; 2 amp £1.80; 4 amp £2.50	
BATTERY CHARGERS. Ready built with leads and clips 4 amp £2; 4 amp £4; 5 amp £4.50.	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs. 1 amp 40p; 2 amp 55p; 4 amp 85p.	

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V 3 amps 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. **£10** Carr. Famous make (Value £18) OUR PRICE £10 Carr. Can be used as 800 watt auto transformers 240-110V.

SET OF 3 MOTORS FOR COLLARO STUDIO TAPE DECK

£2.50 Post 50p

VOLUME CONTROLS 80 ohm Coax 4p yd. Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p. STIFF L/S 50p. FINE LOW LOSS 10p per EdgeK.S.P. Transistor 25p. Ideal 625 and colour. p yd Wire Wound controls 1½in dia. 3 Watts. 10 ohms to 100K British Made with long jin spindles jin dia. 45p each. HELICAL POT 10K LIN. List £3. Bargain 75p. DUAL CONCENTRIC POT 500K LOG AND 500K LIN D.P. switch. Inner spindle 3½in; outer spindle 2½in 75p.

E.M.I. 13½ x 8in. SPEAKER SALE!

With twin tweeters. And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. **£4.50** Post 25p



With fared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-80 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. **£2.75** Post 25p

Bookshelf Cabinet 16 x 10 x 9in. Teak finish Post 25p

GOODMANS 6½in. HI-FI WOOFER 8 ohm. 10W. Large ceramic magnet. Special Cambic cone surround. Frequency response 30-12,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. Suitable Cabinet 12 x 8 x 6 £4 Suitable Tweeter £2 **£4**



ELAC CONE TWEETER The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3½ x 3½ x 2½ in deep. Rating 10W, 8 ohm or 15 ohm models. **£1.90** Post 20p. Crossover 95p

GOODMANS 8in. WOOFER

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass response 30-8,000 cps. Ideal bass unit for **£3.75** Hi-Fi system.



LOUDSPEAKERS P.M. 3 OHMS. 7 x 4in £1.25; 6½in £1.50; 8 x 5in £1.60; 8in £1.75; 10 x 6in £1.90; 10in £2.00. **SPECIAL OFFER:** 80 ohm, 2½in 2in 35 ohm, 2in. 3in; 5in 25 ohm, 2½in dia; 3in dia; 15 ohm, 3½in dia; 5in; 6 x 4in; 7 x 4in; 8 x 5in TYPE 3 ohm, 2½in, 2½in, 3½in, 5in dia (6 x 4in, 8 ohm, £1.50). RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8in diameter 4W £2.50, 10 in diameter 5W £2.50; Post 25p. 12in diameter, 3W, £2.95; 3 or 8 or 15 ohm models. **SPEAKER COVERING MATERIALS.** Samples Large S.A.E. Horn Tweeters 2-16Kc/s. 8W 8 ohm or 15 ohm £1.95 De Luxe Horn Tweeters 2-18Kc/s. 15W, 15 ohm £3.50 TWO-WAY 3,000 c.p.s. CROSSOVERS 3, 8 or 15 ohm 95p

TWO-WAY CROSSOVER NETWORK 3,000 c/s With variable tweeter attenuator giving accurate high/low frequency balance. Mounted on panel 5½in x 4½in with control knob, tweeter and woofer leads and input. **£2.20** Post terminals. Suitable for 3 to 8 ohm impedance.


VALVE OUTPUT TRANSFORMER 25p. MIKE TRANSFORMER MU metal 100-1 £1.25. 5 WATT MULTI RATIO. 3, 8 and 15 ohms, 80p. PUSH-PULL VALVE OUTPUT TRANSFORMERS. 50 watt. £11.50 100 watt £14.00

ELECTRO MAGNETIC PENDULUM MECHANISM

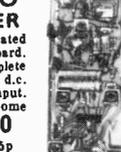1.5V d.c. operation over 100 hours continuous on SP2 battery, full adjustable speed and speed. Ideal display, teaching electro magnetism or for metronome. **95p** Post 20p

BRITISH MADE STEREO MULTIPLEX DECODER

Brand New. 7 transistors plus integrated circuit. Fibre glass printed circuit board. Size 2½ x 6½ x 1½ in. Pre-aligned. Complete with stereo beacon indicator. 12V d.c. operation. 400mV output for 100mV input. Full instructions for any FM Tuner. Some technical experience essential. **£6.50** Post 15p



DIPOLE LOFT AERIAL £1.50. 80 OHM CABLE 4p yard. 300 OHM CABLE 5p yard.

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. OUTLET BOXES, SURFACE MOUNTING 25p. BALANCED TWIN RIBBON FEEDER 800 ohms, 5p yd. JACK SOCKET Std. open-circuit 14p, closed circuit 25p; Chrome Lead Socket 45p; Phone Plug 5p; Phone Socket 6p; JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 12p DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p DIN SOCKETS Lead 3-pin 18p; 5-pin 15p; DIN PLUGS 10p; 5-pin 25p. VALVE HOLDERS 5p; CERAMIC 8p; CAN 5p.

ALL PRICES INCLUDE VAT MINIMUM POST AND PACKING

RADIO COMPONENT

Illustrated Catalogue Brochure, Radio Books & Components Lists 10p Written guarantee.

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT £5-75

THE PAIR, Post 25p. (Available separately. Woofer £4-25; Tweeter £1-90)

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in with a massive Ceramic Magnet, 440x Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms
Maximum power 12 Watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9 in. MODERN DESIGN, TEAK WOOD FINISH.



£9-90 Post 25p



8in. or 10in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8in. 10 watts. 10in. 12 watts.

£3-75

TEAK VENEER HI-FI SPEAKER CABINETS Fluted Wood Fronts

MODEL "A". 20 x 13 x 9 in. For 18 in. dia. or 10in speaker. £9-90 Post 25p

MODEL "B". 16 x 10 x 9 in. For 13 x 8 in. or 8 in. speaker £5-50 Post 25p

MODEL "C". 16 x 8 x 6 in. For 8 x 6 in. £4-40 Post 25p

LOUDSPEAKER CABINET WADDING 18in wide, 15p ft.



BARGAIN AM TUNER. Medium Wave. Transistor Superhet £4-95

Ferrite aerial. 9 volt. £4-95

BARGAIN 4 CHANNEL TRANSISTOR MONO AMPLIFIER. Add music to highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. £3-95

STEREO VERSION OF ABOVE £5-95

BARGAIN FM TUNER. 88-108 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. £12-85


BARGAIN FM TUNER. £8-85

As above less cabinet.

BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. £4-50

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. £2-50 Post 15p

Leaflet S.A.E. £2-50 Post 15p

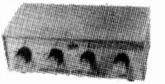

BAKER MAJOR 12" £9-90



30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. £12-50 Post Free

Please state 3 or 8 or 15 ohms. Post 25p

BAKER "BIG SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-15,000 cps. Bass Resonance 55 cps.

GROUP "25" £8-80 Post Free
12in 25 watt
3, 8 or 15 ohms.

GROUP "35" £9-90 Post Free
12in 35 watt
3, 8 or 15 ohms.

GROUP "50" £22-00 Post Free
15in. 50 watt
8 or 15 ohms.

NEW 12in VERSION £17-60



MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm a.c. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E.



£49 Carr. £1-00

CALLERS ONLY! DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version, 4 inputs, 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc. 4, 8 and 15 ohm Loudspeaker matching. £59

Q MAX CHASSIS CUTTERS

A die, punch and Allen Screw		Sizes 1 1/2" Square, with key	
Size 1 1/2" Square, with key	74p	Size 1 1/2" Square, with key	£1-70
Key "A" for above	83p	Key "B" for above	10p
Key "B" for above	90p	2" Square, with key	25-50
Key "C" for above	92p	2 1/2" Square, with key	25-50
Key "D" for above	99p	3" Square, with key	25-50
Key "A" for above	£1-00	4" Square, with key	25-50
Key "B" for above	£1-15	5" Square, with key	25-50
Key "C" for above	£1-20	6" Square, with key	25-50
Key "D" for above	£1-35	8" Square, with key	25-50
Key "E" for above	£1-55	10" Square, with key	25-50

SLIDER VOLUME CONTROLS



Available in both LOG and LINEAR type. Size 3 1/2 x 1 x 1/2 in. with knobs. 25K, 10K, 50K, 500K, 100K, 250K, 500K, 1 MEG, 2 MEG. 65p EACH

DELUXE 4 POLE MOTOR

1,400 r.p.m. reversible 42 Watt, spindle 1 1/2 x 7/32in, size 3 1/2 x 3 in. As illustrated. 240V a.c. mains. £1-95 Post 25p

E.M.I. GRAM MOTOR

120V or 240V a.c. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 in. £1-00 Post 25p

ONE RPM GEARED MOTOR

240V a.c. mains. Ideal for displays/disco lightwheels. £1-25 Post 25p

BAKER HI-FI SPEAKERS HIGH QUALITY—BRITISH MADE REGENT

12in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps
Flux Density 12,000 gauss
Useful response 45-13,000cps
3 or 8 or 15 ohm models.

£8-80 Post Free

DE-LUXE Mk II 12in. 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance 30cps
Flux Density 14,000 gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£11 Post Free

SUPERB 12in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 16,500 gauss
Useful response 20-17,000cps
8 or 15 ohms models.

£16-50 Post Free

AUDITORIUM 12in. 25 watts

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs, Ideal for Hi-Fi and Discos-theques.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£15-40 Post Free

AUDITORIUM 15in 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discos-theques, Electronic instruments and the home.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000cps
8 or 15 ohms models.

£22 Post Free

Hi-Fi Enclosure Manual containing 20 plans, designs, crossover data and cubic tables. 42p. Post Free.

WAFER HEATING ELEMENTS

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 x 1/2 in. Operating voltage 200/250V, a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe, Black heat. British-made for use in photocopyers and print drying equipment. Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convecter Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1-50)

ALL POST PAID—Discounts for quantity.

CALLERS WELCOME • CUSTOMERS FREE CAR PARK • OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m. (Closed for Lunch 1.15-2.30)

SPECIALISTS 337 WHITEHORSE ROAD • CROYDON

(Export: Remit cash and extra postage.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS


EMI 13 x 8, 3, 8 or 15 ohm	£2-03
EMI 13 x 8, 150 d/c 3, 8 or 15 ohm	£2-25
EMI 13 x 8, 450 t/w 3, 8 or 15 ohm	£3-60
EMI 13 x 8 type 350 8 ohm	£2-25
EMI 8 1/2 in 93850 4 or 8 ohm	£2-80
EMI 8 x 5 d/cone roll/s 8 ohm	£2-50
Baker Group 25 3, 8 or 15 ohm	£3-80
Baker Group 35 3, 8 or 15 ohm	£7-50
Baker De Luxe 12in d/cone	£9-82
Baker Major 12in	£7-50
Kef 127	£4-87
Kef 115	£5-50
Kef B110	£8-16
Kef B200	£7-42
Kef B139	£10-72
Kef DN8	£1-92
Kef DNS	£1-37
Kef DN12	£4-12
Kef DN13	£2-75
Fane Pop 100W 8/15 ohm	£21-45
Fane Pop 60W 8/15 ohm	£12-28
Fane Pop 50W 8/15 ohm	£18-17
Fane Pop 25/2 25W 8/15 ohm	£5-84
Fane Pop 15W 8/15 ohm	£4-40
Fane Crescendo 15in 8 or 15 ohm	£27-50
Fane Crescendo 12A 100W 8 or 15 ohm	£24-20
Fane Crescendo 12B 75W bass 8 or 15 ohm	£24-20
Fane 8077 8in d/c roll/s 8 or 15 ohm	£3-85
Fane 8087 8in d/cone 8 or 15 ohm	£2-64
Goodmans Argent 100 tweeter	£3-80
Goodmans 8P 8 or 15 ohm	£3-80
Goodmans 10P 8 or 15 ohm	£4-49
Goodmans 12P 8 or 15 ohm	£11-55
Goodmans 18P 8 or 15 ohm	£17-05
Goodmans 18P 8 or 15 ohm	£29-70
Goodmans Twinaxiom 8	£9-79
Goodmans Twinaxiom 10	£7-61
Elec 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£2-53
Elec 6 1/2 in d/c roll/s 8 ohm	£3-22
Elec 6 1/2 in d/cone 8 ohm	£2-59
Elec 4in tweeter TW4	£1-21
Wharfedale Bronze 8 RS/DD	£3-11
Wharfedale Super 8 RS/DD	£5-50
Wharfedale Super 10 RS/DD	£9-80
Coral 6 1/2 in d/cone roll/s 8 ohm	£2-42
Siren 6 1/2 in 3 or 8 ohm	£1-44
Richard Allan 12in d/c 3 or 15 ohm	£2-80
10in x 5in 3, 8 or 15 ohm	£2-80
8in x 5in 3 or 8 ohm	£1-38
7in x 4in 3 or 8 ohm	£1-38
2 1/2 in 64 ohm or 70mm 80 ohm	£5p
Adastra Hiten 10in 10W 8 or 15 ohm	£2-80
Eagle DT33 dome tweeter	£3-45
Eagle HT15 tweeter	£3-66
Eagle CT5 tweeter	£1-25
Eagle CT10 tweeter	£2-54
Eagle MHT10 tweeter	£3-74
Eagle FR4	£4-45
Eagle xover CN23, 28, 216	£1-15
Sp. matching transformer 3-15 ohm	£1-10
Celestion MF1000 25W horn 8 or 15 ohm	£10-45
Celestion PS8 (for Unilux)	£2-16
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G18C 8 or 15 ohm	£33-00

Car Stereo speakers—ask for leaflet.

SPEAKER KITS

Wharfedale Unit 3	£8-25
Wharfedale Unit 4	£14-50
Wharfedale Unit 5	£21-00
Richard Allan Twinkit	£7-33
Richard Allan Triple 8	£16-78
Richard Allan Triple Assem.	£18-20
Richard Allan Super Triple	£19-38
Goodmans DIN 20	£8-58
Fane Mode One	£9-00

Kefkit 2	£24-75
Kefkit 3	£35-50
Peerless 2-8	£5-50
Peerless 10-2	£3-47
Peerless 20-2	£10-41
Helma XLK 25 (pair)	£18-17
Helma XLK 50 (pair)	£37-18
Stephen speaker kits and cabinets—send for free booklet "Choosing a Speaker"	
PRICES INCLUDE VAT.	
Free with orders over £7—"Hi-Fi Loudspeaker Enclosure" book. All units guaranteed new and perfect. Prompt despatch. Carriage and insurance: speakers 35p each, speaker kits 75p each, tweeters and crossovers 20p each. Carriage and insurance 50p per kit.	

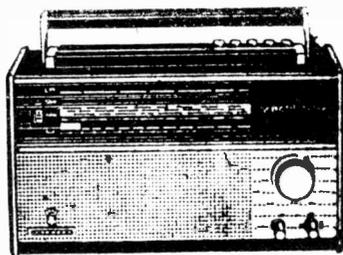

RADIOS/CASSETTES/AMPS

Grundig RF310	£21-25
Grundig Signal 500	£27-00
Grundig Mariner TR865	£32-00
Grundig Elite Boy 500	£27-00
Grundig Melody Boy 500	£27-00
Grundig Melody Boy 1000	£38-75
Grundig Yacht Boy 210	£34-25
Grundig RF430 mains	£27-00
Grundig RF310 mains	£22-75
Grundig Top Boy	£16-75
Grundig Satellit 1000	£121-00
Grundig C230 cassette	£28-00
Grundig C402 cassette	£27-00
Tandberg TP41	£37-75
BASF 9301 radio/cassette	£58-00
Bush VTR178 5 band (inc. AIR)	£29-00
Trio KA2000A	£33-00
Trio KA2002	£41-00
ITT/KB Coit	£9-95
ITT/KB Golf Preset	£21-25
ITT/KB Weekend Auto	£16-00
ITT/KB Europa	£18-00
ITT/KB SL53 cassette	£22-82
ITT/KB Studio 60M cassette	£29-32
ITT/KB Studio 73 stereo cassette	£44-00
Koyo KTR1664 8 waveband	£40-00
Koyo KTR1770 11 waveband	£58-50
Koyo KTR1883 5 band (inc. AIR)	£23-50
TEC 200 Radio/Cassette	£31-00
Prices include VAT.	
Carriage and insurance 75p. FREE with each radio—world radio stations book.	

PA/DISCO AMPLIFIERS (carr. and ins. £1)

Baker 100W	£48-00
Linear 30/40	£25-00
Linear 40/60	£30-00
Linear 80/100	£55-00

FREE with speaker orders over £7

"Hi Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch. Carriage and insurance 25p per speaker (tweeters and crossovers 15p). ALL PRICES QUOTED INCLUDE VAT.

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF. Radios, etc.: 10 Swan Street, Wilmslow, Cheshire, SK9 1HF. Telephone: Wilmslow 29599.

A DEXTER DIMMASWITCH

ALLOWS COMPLETE



LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.

600 watt £3.52 Kit form £2.97
300 watt £2.97 Kit form £2.42

All plus 12p post and packing


Prices include VAT. Please send c.w.o. to:

DEXTER & COMPANY

1 ULVER HOUSE
19 KING STREET
CHESTER CH1 2AH
Tel: 0244-25883

AS SUPPLIED
TO H.M. GOVERNMENT
DEPARTMENTS, HOSPITALS,
LOCAL AUTHORITIES,
ETC.

4-STATION INTERCOM

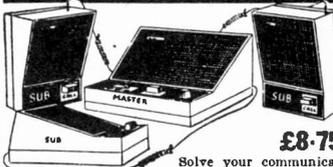

£8-75

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 6ft and other accessories. P. & P. 17p.

MAINS INTERCOM (new model)

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £18-85. P. & P. 60p extra.

INTERCOM/BABY ALARM



£4-85

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 6ft connecting wire. Complete with battery. P. & P. 33p.

Transistor TELEPHONE AMPLIFIER



£4-25

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/11)
160 KENSINGTON HIGH STREET, LONDON, W.8

COMPREHENSIVE HOME CONSTRUCTOR KITS

AS SPECIFIED IN THE P.E. RONDO

COMPLETE QUADRAPHONIC HI-FI SYSTEM

CBS SQ* MATRIX DECODER <small>*TM CBS INC.</small>	COMPLETE KIT	£8.00	POST FREE INC. CBS LICENCE FEE + V.A.T. 80p
PREAMPLIFIER BOARD	COMPLETE KIT	£3.00	POST FREE + V.A.T. 30p
MASTER VOL./TONE/ BALANCE BOARD	COMPLETE KIT	£8.50	POST FREE + V.A.T. 85p
POWER AMP. BOARD & HEATSINK (STEREO PAIR)	COMPLETE KIT PER BOARD	£7.50	POST FREE + V.A.T. 75p
POWER SUPPLY BOARD COMPLETE		£5.00	POST FREE + V.A.T. 50p
MAIN SMOOTHING CAPACITORS		0.75	POST FREE + V.A.T. 7p
MAINS TRANSFORMER	COMPLETE KIT	£6.25	POST FREE + V.A.T. 62p
CHASSIS—PUNCHED & DRILLED	COMPLETE KIT	£2.25	POST FREE + V.A.T. 22p

PHASE LOCKED LOOP STEREO DECODER

COMPLETE KIT THAT TAKES ABOUT 30 MINUTES TO BUILD.

1. CONNECT DECODER TO YOUR TUNER, POSSIBLY DISCONNECTING ONE OR TWO DE-EMPHASIS COMPONENTS.
 2. PROVIDE +10 TO +16 VOLTS EITHER FROM YOUR TUNER OR SEPARATE POWER SUPPLY.
 3. TUNE TO A STEREO BROADCAST.
 4. TURN A PRESET RESISTOR UNTIL THE STEREO BEACON LIGHTS UP.
- YOU THEN HAVE STEREO RADIO. COMPREHENSIVE INSTRUCTIONS PROVIDED.

£3.40 POST FREE + 34p V.A.T.
(BEACON 34p + 4p V.A.T.)

BUILT AND TESTED **£4.40** POST FREE + 44p V.A.T.
(BEACON 34p + 4p V.A.T.)
EX-STOCK DELIVERY

THESE DESIGNER-APPROVED KITS ARE AVAILABLE AS PUBLISHED

SONAX

ELECTRONICS

SPENCER HOUSE
BRETTENHAM ROAD
EDMONTON
LONDON, N.18

Telephone
01-807 5544

TRADE ENQUIRIES WELCOME

PLEASE SEND ME:

CBS SQ DECODER
PREAMPLIFIER BOARD
MASTER VOLUME BOARD
POWER AMP. BOARDS
POWER SUPPLY BOARD
SMOOTHING CAPACITORS
MAINS TRANSFORMER
CHASSIS
STEREO DECODER KIT
STEREO DECODER BUILT
AND TESTED

BLOCK CAPITALS PLEASE

NAME

ADDRESS

PLEASE TICK BOX

MONEY
ENCLOSED

£

CHEQUE

P.O.

MONEY ORDER

P.E. 11

The largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors—COMPONENT VALUE £1.50. 3 for ONLY 55p + p & p 30p
SPECIAL. As above PLUS Power Transistors ONLY 55p each + p & p 15p
STABILISED POWER MODULES
 Complete with circuit diagrams, etc. 90p each + p & p 15p
FAXOLINE BOARDS 7½ x 9" approx. 4 for 30p + p & p 20p.

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16½ x 4" approx. 2 for 55p

DECON-DALO 33pC Marker

Etch resistant printed circuit marker pen 90p each

VEROBOARDS

Packs containing approx. 50sq. ins. various sizes, all 0.1 metric 55p

REPANCO CHOKES & COILS

RF Chokes
 CH1. 2.5mH 25p CH2. 5.0mH 25p
 CH3. 7.5mH 25p CH4. 10mH 25p
 CH5. 1.5mH 25p

COILS

DRX1 Crystal set 56p DRR2 Dual range 45p

COIL FORMERS & CORES

NORMAN 4" Cores & Formers 7p
 1" Cores & Formers 8p

SWITCHES

DF/DT Toggle 25p SP/ST Toggle 18p

FUSES

1½" and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A
 QUICK-BLOW 4p ea. ANTI-SURGE 5p ea.

EARPHONES

Crystal 2.5mm plug 38p
 Crystal 3.5mm plug 38p
 8 ohms 2.5mm plug 25p
 8 ohms 3.5mm plug 25p

DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.60

3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

2-WAY CROSSOVER NETWORK

K4007. 80 ohms Imp. Insertion loss 3dB £1.21

SELECTED RESISTORS

R1. Our mix, ¼ watt carbon—50 for 55p

CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

INSTRUMENT CASES



(Black Vinyl covered)

No.	Length	Width	Height	Price
BV1	8"	5½"	2"	90p
BV2	11"	6"	3"	£1.20

ALUMINIUM BOXES

BA1	5½"	4"	1½"	42p
BA2	4"	4"	1½"	41p
BA3	4"	2½"	1½"	41p
BA4	5½"	4"	1½"	47p
BA5	4"	2½"	2"	41p
BA6	3"	2"	1"	34p
BA7	7"	5"	2½"	66p
BA8	8"	6"	3"	84p
BA9	6"	4"	2"	84p

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.-Thurs. 9.15-6 p.m. Sat. 9.15-5.30. Late Night Shopping until 7 Fri. Tel. 61693

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1.84

Chrome Finish Model 60 £1.50



Ref. 36A. Record/Stylus Cleaning Kit 28p
 Ref. 43. Record Care Kit £2.85
 Ref. 31. Cassette Head Cleaner 54p
 Ref. 32. Tape editing Kit £1.54
 Model 9. Wire Stripper/Cutter 83p

Ref. P. Hi-Fi Cleaner 31p
 Ref. 32A. Stylus Balance £1.38
 Ref. J. Tape Head Cleaning Kit 51p
 Ref. 34. Cassette Case £1.27
 Ref. 56. Hi-Fi Stereo Hints & Tips 32p

ANTEX SOLDERING IRONS

X25. 25 watt £1.93

CCN 240. 15 watt £2.15

Model G. 18 watt £2.15

SK2. Soldering Kit £2.86

STANDS: ST1 £1.21. ST2 77p

SOLDER: 188WG Multicore Toz 82p

228SWG 7oz 82p. 188SWG 22ft 82p

228SWG Tube 22p

ANTEX BITS AND ELEMENTS

Bits No.

102 For model CN240 ½" 28p

102 For model CN240 ¾" 28p

1100 For model CCN240 ½" 28p

1101 For model CCN240 ¾" 28p

1102 For model CCN240 1" 28p

1020 For model G240 ½" 28p

1021 For model G240 ¾" 28p

1022 For model G240 1" 28p

50 For model X25 ½" 37p

51 For model X25 ¾" 37p

52 For model X25 1" 37p

ELEMENTS

ECN 240 £1.16 ECCN 240 £1.16

EG 240 £1.16 EX 25 £1.16

ANTEX HEAT SINKS 10p

V A T included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack No. Qty. Description Price

C1 250 Resistors mixed values approx. count by weight 0.55

C2 200 Capacitors mixed values approx. count by weight 0.55

C3 50 Precision Resistors 0.1%, 0.01% mixed values 0.55

C4 75 ¼W Resistors mixed preferred values 0.55

C5 5 Pieces assorted Ferrite Rods 0.55

C6 2 Tuning Ganga, MW/LW VHF 0.55

C7 7 Pack Wire 50 metres assorted colours 0.55

C8 10 Reed Switches 0.55

C9 3 Micro Switches 0.55

C10 15 Assorted Pots & Pre-Sets 0.55

C11 5 Jack Sockets 3 x 3.6m 2 x Standard Switch Type 0.55

C12 40 Paper Condensers preferred types mixed values 0.55

C13 20 Electrolytics Trans. types 0.55

C14 1 Pack assorted Hardware—Nuts/Bolts, Grommets, etc. 0.55

C15 4 Mains Toggle Switches, 2 Amp D/F 0.55

C16 20 Assorted Tag Strips & Panels 0.55

C17 10 Assorted Control Knobs 0.55

C18 4 Rotary Wave Change Switches 0.55

C19 3 Relays 6—24V Operating 0.55

C20 4 Sheets Copper Laminate approx. 10" x 7" 0.55

PLUGS AND SOCKETS

SOCKETS

PS 35 DIN 2 Pin (Speaker) 0-06

PS 36 DIN 3 Pin 0-10

PS 37 DIN 5 Pin 180° 0-10

PS 38 DIN 5 Pin 240° 0-10

PS 39 Jack 2.5mm Switched 0-09

PS 40 Jack 3.5mm Switched 0-10

PS 41 Jack 1" Switched 0-17

PS 42 Jack Stereo Switched 0-26

PS 43 Phono Single 0-06

PS 44 Phono Double 0-10

PS 45 Car Aerial 0-09

PS 46 Co-Axial Surface 0-09

PS 47 Co-Axial Flush 0-14

INLINE SOCKETS

PS 21 D.I.N. 2 Pin (Speaker) 0-13

PS 22 D.I.N. 3 Pin 0-17

PS 23 D.I.N. 5 Pin 180° 0-17

PS 24 D.I.N. 5 Pin 240° 0-17

PS 25 Jack 2.5mm Plastic 0-10

PS 26 Jack 3.5mm Plastic 0-12

PS 27 Jack 1" Plastic 0-24

PS 28 Jack 1" Screened 0-28

PS 29 Jack Stereo Screened 0-22

PS 30 Jack Stereo Screened 0-22

PS 31 Phono Screened 0-14

PS 32 Car Aerial 0-15

PS 33 Co-Axial 0-17

PLUGS

PS 1 D.I.N. 2 Pin (Speaker) 0-11

PS 2 D.I.N. 3 Pin 0-12

PS 3 D.I.N. 4 Pin 0-15

PS 4 D.I.N. 5 Pin 180° 0-14

PS 5 D.I.N. 5 Pin 240° 0-15

PS 6 D.I.N. 6 Pin 0-15

PS 7 D.I.N. 7 Pin 0-15

PS 8 Jack 2.5mm Screened 0-10

PS 9 Jack 3.5mm Plastic 0-09

PS 10 Jack 3.5mm Screened 0-12

PS 11 Jack 1" Plastic 0-13

PS 12 Jack 1" Screened 0-18

PS 13 Jack Stereo Screened 0-29

PS 14 Phono 0-06

PS 15 Car Aerial 0-15

PS 16 Co-Axial 0-10

CABLES

CP 1 Single Lapped Screen 0-06

CP 2 Twin Common Screen 0-08

CP 3 Stereo Screened 0-08

CP 4 Four Core Common Screen 0-23

CP 5 Four Core Individually Screened 0-30

CP 6 Microphone Fully Braided Cable 0-10

CP 7 Three Core Mains Cable 0-07

CP 8 Twin Oval Mains Cable 0-06

CP 9 Speaker Cable 0-04

CP 10 Low Loss Co-Axial 0-10

CARBON POTENTIOMETERS

Log and Lin

4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M

VC 1 Single Less Switch 0-14

VC 2 Single D.P. Switch 0-28

VC 3 Tandem Less Switch 0-44

VC 4 1K Lin Less Switch 0-14

VC 5 100K Log anti-Log 0-14

HORIZONTAL CARBON PRESETS

0-1 watt 0-06 each

100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

BOOK BARGAIN BUNDLE

8 Books comprising
 2 Transistor Equivalent Books
 1 Radio and Electronic Colour Code and Data Chart
 1 Radio Valve Guide PLUS
 3 other Constructional books on Receivers, FM Tuners, etc.
 Also 1 General Constructional book
Value £3 Our Price £2 10p p & p

BP1 Handbook of Transistor Equivalents and Substitutes 40p

BP2 Handbook of Radio, T.V. and Industrial Tube & Valve Equip. 40p

BP3 Handbook of Tested Transistor Circuits 40p

BP4 International Handbook of the World's Short Wave, Medium and Long Wave Radio Stations and FM/TV Listings 35p

BP5 Handbook of Simple Transistor Circuits 35p

BP7 Radio & Electronic Colour Codes and Data Chart 15p

BP8 Sound and Loudspeaker Manual 50p

BP9 38 Practical Tested Diode Circuits for the Home Constructor 35p

BP11 Practical Transistor Novelty Circuits 40p

129 Universal Gram-Motor Speed Indicator 8p

138 How to make FM & TV Aerials, Bands 1, 2 and 3 18p

141 Radio Servicing for Amateurs 20p

146 High Fidelity Loudspeaker Enclosures 37p

156 Transistor Circuits Manual No. 1 15p

160 Coil Design & Constructional Manual 80p

161 Radio, TV and Electronics Data Book 25p

170 Transistor Circuits for Radio Controlled Models 40p

174 Transistor Subminiature Receivers 32p

176 Transistor Test Equipment and Servicing Manual 25p

176 Transistor Audio Amplifier Manual 40p

177 Modern Transistor Circuits for Beginners 40p

178 A Comprehensive Radio Valve Guide, Book 5 30p

183 How to Receive Foreign TV Programmes on your set by simple modifications 32p

185 Tested Shortwave Receiver Circuits using MAT's 30p

187 The TSL Mark 4 Valved FM Tuner and its construction 20p

196 Reactance-Frequency Chart for Audio & RF use 15p

Resistor Colour Code Disc Calculator 10p

CARTRIDGES

ACOS GP91-1SC. 200mV at 1.2cm/sec £1.16

ACOS GP93-1. 280mV at 1cm/sec £1.65

ACOS GP96-1. 100mV at 1cm/sec £2.65

TTC J-2005. Crystal/HI Output 95p

TTC J-20 10C Crystal/HI Output Compatible £1.10

TTC J-200 CB Stereo/HI Output £1.60

TTC J-2105 Ceramic/Med. Output £1.64

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, ¼ watt available in PAKS of 50 pieces, assorted into the following groups:—

R1 50 Mixed 100 ohms-820 ohms 40p

R2 50 Mixed 1K ohms-8.2K ohms 40p

R3 50 Mixed 10K ohms-82K ohms 40p

R4 50 Mixed 100K ohms-1 Meg. ohms 40p

THESE ARE UNBEATABLE PRICES—LESS THAN 1p EACH INCL. V.A.T.


BI-PAK SUPERIOR QUALITY LOW-NOISE CASSETTES

C60, 32p; C90, 41p; C120, 52p

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

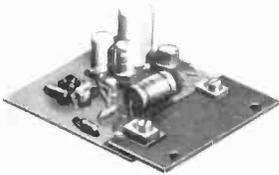

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S.

The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f = 1KHz	0.26%
LOAD IMPEDANCE	-	8-16 Ω
INPUT IMPEDANCE	f = 1KHz	100 kΩ
FREQUENCY RESPONSE -3dB	Po = 2 WATTS	50 Hz-25KHz
SENSITIVITY for RATED O/P	Vs=25V. R1=8Ω f=1KHz	75mV. RMS
DIMENSIONS	-	3" x 2 1/2" = 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power out for 2% T.H.D. (RL = 8Ω f = 1KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL 10. 3 watts	£2-10
AL 20. 5 watts	£2-50
AL 30. 10 watts	£3-01

POWER SUPPLIES

PS 12. (Use with AL10 & AL20)	85p
SPM 80. (Use with also AL30 & AL50)	£3-25
FRONT PANELS PA 12 with Knobs	£1-00

PRE-AMPLIFIERS

PA 12. (Use with AL10 & AL20)	£4-85
PA 100. (Use with AL30 & AL50)	£13-15

TRANSFORMERS

T481 (Use with AL10 & AL20)	£1-38 P & P 15p
T638 (Use with AL20)	£1-93 P & P 15p
BMT80 (Use with AL30 & AL50)	£2-16 P & P 25p

PA12 PRE-AMPLIFIER SPECIFICATION

The PA12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with ceramic cartridges while the auxiliary input will suit most magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm x 84mm x 36mm.

Frequency response—
20Hz-50KHz (-3dB)
Bass control—
± 12dB at 60Hz
± 14dB at 14KHz
Treble control—
1 Meg. ohm
Sensitivity 300mV
*Input 1. Impedance
± 30 K ohms
Sensitivity 4mV

EA1000 AUDIO AMP MODULE 5 WATTS R.M.S.


Module Tested and Guaranteed. Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

SPECIAL OFFER £2 each while stores last

The STEREO 20

The "Stereo 20" amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm x 14 cm x 5.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The "Stereo 20" has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25KHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control ± 12dB at 60Hz typically 0.26% at 1 watt. Treble con. ± 14dB at 14kHz.

£13-48

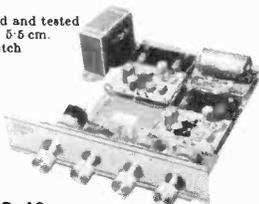

50W pk 25w (RMS)

0.1% DISTORTION!
HI-FI AUDIO AMPLIFIER

THE AL50

★ Frequency Response 15Hz to 100,000—1dB.

★ Load—3, 4, 8 or 16 ohms.

★ Distortion—better than .1% at 1KHz.


★ Signal to noise ratio 80dB.

ONLY
£3-58 each

★ Supply voltage 10-35 Volts.

★ Overall size 63mm 105mm x 13mm.

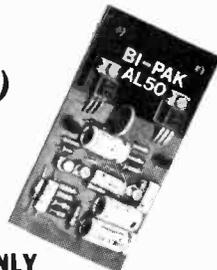
Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs.
FULLY BUILT—TESTED—GUARANTEED.



STABILISED POWER MODULE SPM80

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm.

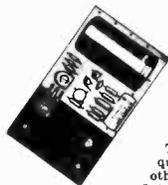These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including—Disc Systems, Public Address, Intercom Units, etc. Handbook available 10p
PRICE £3-25



TRANSFORMER BMT80 £2-15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

Frequency Response	20Hz-20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs: 1. Tape Head	1.25 mV into 50K Ω
2. Radio, Tuner	35 mV into 50K Ω
3. Magnetic P.U.	1.5 mV into 50K Ω
All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters: Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than -65dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm x 82mm x 35mm

ONLY £13-15

SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £25-30 FREE p. & p.

All prices quoted in new pence Giro No. 388-7006
Please send all orders direct to warehouse and despatch department


BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 11p. Overseas add extra for airmail.
Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

The Catalogue you **MUST** have!

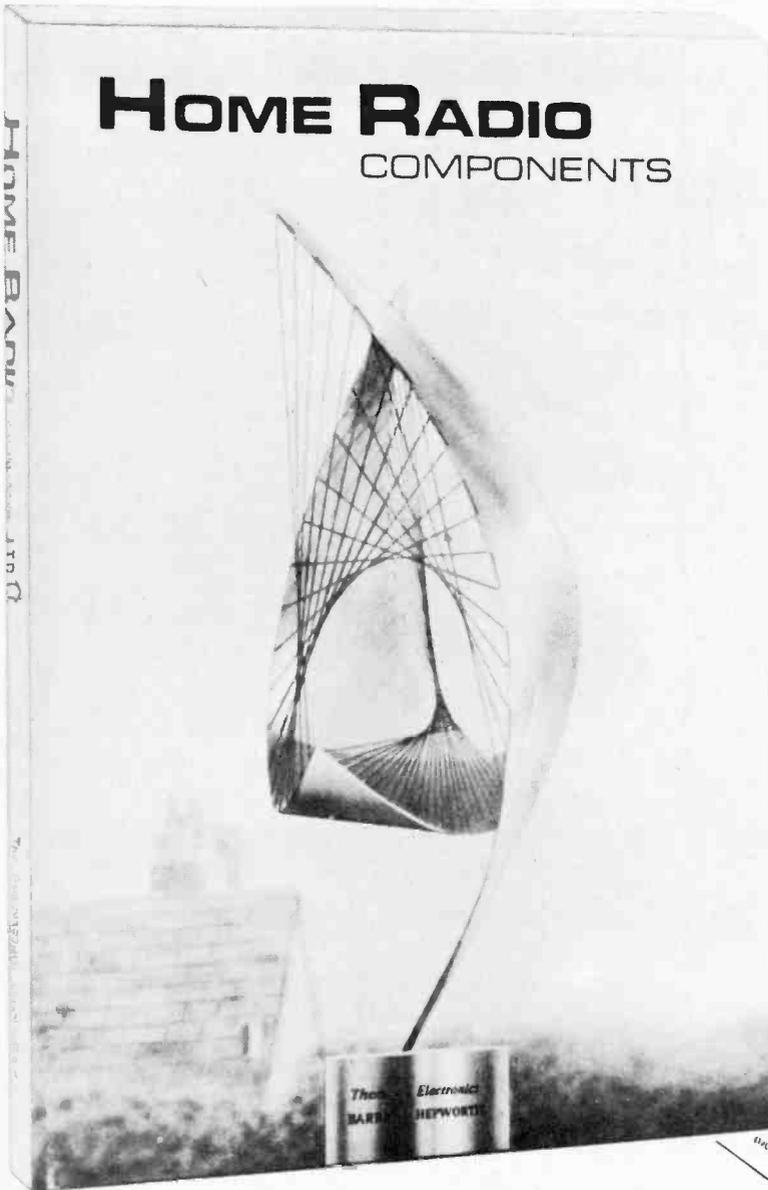

250 pages 11 $\frac{3}{4}$ " x 8 $\frac{1}{4}$ "

6,785 electronic components clearly listed and indexed

1,750 pictures

10 free Vouchers each worth 5p.

Price list regularly updated

Bookmark with useful list of technical abbreviations

Details of our popular Credit Account Service and our Easy Ordering System are included in the catalogue.

Only 55p. plus 22p POST AND PACKING

POST THIS COUPON
with cheque or P.O. for 77p.

The price of 77p applies only to customers in the U.K. and to BFPO addresses.

Name _____
Address _____



HOME RADIO (Components) LTD.
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

TAKE YOUR PICK

THE tendency towards larger and more ambitious projects is a perfectly natural development in the wake of technological advancement. Not everyone wants to become involved in building the more complex project, that is true. But this expansive side of home construction should be welcomed by all the genuine enthusiasts, since it provides an opportunity for amateurs to keep up to date with the latest developments and techniques and to make practical use of them as and when they feel so inclined.

It is worth considering, also, the beneficial effect on the retail components market arising from the demand generated by some larger projects. Such demands encourage suppliers to hold a wide variety of stocks and to seek out lines in components they might not otherwise contemplate handling. A healthy and venturesome retail trade is to the advantage of everyone who purchases components, whether in large or small quantities.

The needs and interests of constructors vary widely, but so far as generalisation can go, it seems reasonable to suppose that out of the whole, a majority of constructors confine their activities to the more simple kind of project. New-comers undoubtedly start this way too, although many will in due course feel the compulsion to pursue their hobby to greater heights. Our recognition of the need for small simple designs is reflected in this month's special supplement. This contains details of four uncomplicated but useful and highly adaptable circuits, any of which can be assembled on the piece of printed wiring board presented free with this issue of Practical Electronics.

Returning now to larger projects, it may be recalled that the virtues of modular construction were discussed here last February when the P.E. Sound Synthesiser made its debut. With the synthesiser main unit now completed, this month's article in the series introduces the complementary keyboard unit.

It will interest many readers to learn that over the past 12 months the complete synthesiser has been handled by a number of professional musicians, and its unique creative possibilities—both as a composing machine and as a live performance instrument—have been established and enthused upon. Moreover, it has been confirmed that the keyboard unit on its own does constitute a valuable and versatile instrument for live performance. For example, it will meet the needs of many musical groups, being able to provide novel avant-garde accompaniment.

This feasibility is another bonus or "spin off" from the modular approach. It confirms the importance of considering both the *whole* and the *parts*, where many large and ambitious projects are concerned.

F.E.B.

Editor

F. E. BENNETT

Editorial

R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.

J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager

D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW

Phone: 01-634 4210

C. R. BROWN, *Classified*

Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.,
London EC4A 4AD
Phone: *Editorial* 01-634 4452

Advertisements 01-634 4202

FOUR CHANNELS OF INDEPENDENT CONTROL . . .

THIS Stage Lighting Dimmer was built to the specific requirements of an amateur revue company. It consists of four independent channels each capable of dimming 13 amps (3250 watts) of incandescent (not fluorescent) lighting. The number of channels may be increased as necessary providing the current capability of the input is uprated.

SYSTEM DESCRIPTION

Each of the four dimmable channels is controlled by a linear slider fader. Any channel can be switched to a Master Fader which is a double unit made up of two stereo slider potentiometers. The Master has control over all channels simultaneously when required.

Each channel has a mimic light next to the fader control which gives a visible representation of the relative brilliance of the lights plugged into that channel.

A preset potentiometer in each channel allows the cutoff point of each channel to be adjusted for different wattage lamps with differing thermal capacities.

Interference suppression is included and the dimmers are mounted in an earthed box to reduce radiation.

The output to each channel is fed *via* a 13 amp switched socket and input from the mains is taken *via* a 60 amp fused switch which can act as a "Master Blackout" control when it is necessary to cut out all the lamps in the fastest possible time.

CIRCUIT OPERATION

Each of the four channels uses an identical circuit which uses a triac to control the current through the lamps. The basis of this circuit is shown in Fig. 1.

A triac is a four layer semiconductor device with three terminals. It will only conduct when a voltage is applied to the gate (g) terminal and will then continue conducting in either direction even when the gate voltage is removed. It will cease to conduct when the current through it drops below a threshold level known as the holding current.

The circuit shown in Fig. 1 varies the average current through the lamps by controlling the point in the mains cycle at which the triac is triggered into conduction. This method of control is known as phase control.



STAGE LIGHTING

EACH CAPABLE OF DIMMING $3\frac{1}{4}$ kW OF LIGHTING

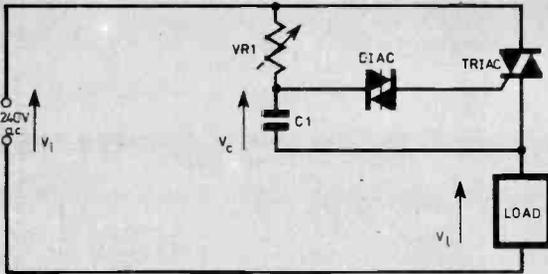


Fig. 1. The basic phase control triac circuit. The waveforms in different parts of the circuit are shown right

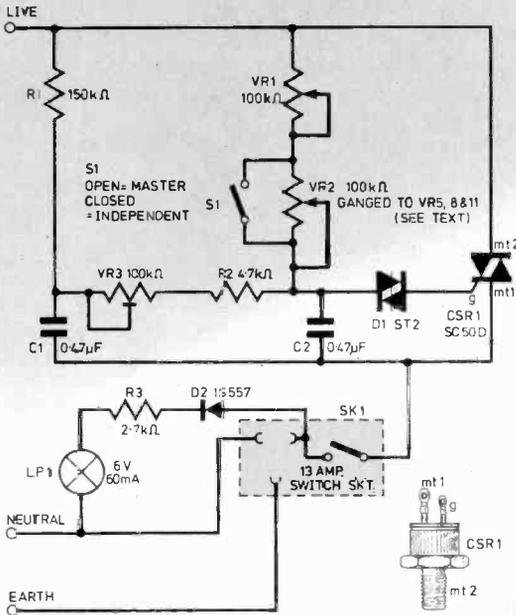
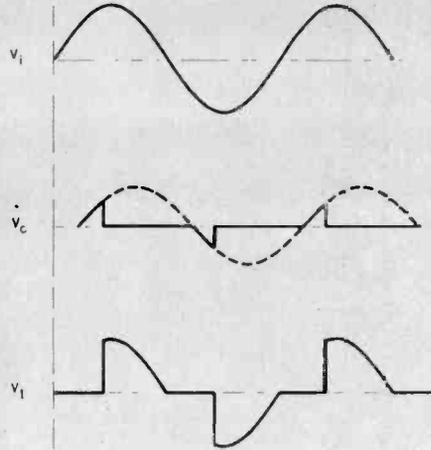


Fig. 2. The circuit of one of the control channels of the Stage Lighting Dimmer. Four identical channels are used in the unit

Referring to Fig. 1, capacitor C1 and variable resistor VR1 form a phase shift circuit which alters the phase of the signal at their junction with respect to the applied mains voltage.

The diac in series with the triac gate is a four-layer device which presents a high impedance until the voltage across it exceeds a value known as the breakdown voltage (about 30 volts) when it presents a low impedance. When the breakdown voltage is reached the capacitor C1 discharges into the gate of the triac causing it to conduct. Typical waveforms are also shown in Fig. 1.


COMPLETE CIRCUIT

In the actual circuit used, shown in Fig. 2, VR1 is the Channel Fader and VR2 is one section of the Master Fader which can be over-riden by S1 to give independent control. VR1 and C2 form the phase control network and R1 and C1 are additions to provide smooth control at low light levels.

The current supplied by R1 and C1 is determined by VR3 in series with R2. VR3 can be used to

DIMMER

By R. Liffen

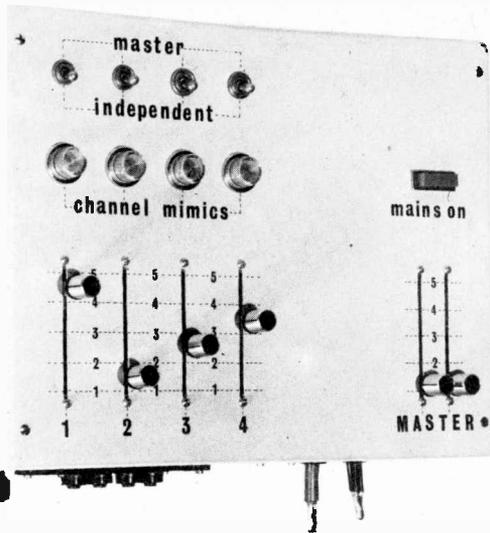

Photograph showing the layout of the components on the front panel and the output sockets mounted on the side of the case. Another two sockets are similarly fixed the other side

preset the extinguishing point of the lamp when the Channel Fader is fully down. There are two modes of use for VR3: it may be used to fully extinguish a lamp which would otherwise "sing" (due to the filament vibrating in the presence of small residual spiky current; alternatively it may be set so that the filament glows dull red, which enables a big lamp to be taken to full brightness quickly.

MIMIC CIRCUIT


Components D2, R3 and LP1 form a "mimic" circuit to give a visual indication of the lamp brightness. D2 and R3 simply reduce the mains voltage down to six volts. The four resistors (R3 and its counterparts) dissipate nearly 10 watts each and must be placed in a well ventilated position.

Note the special connection between the switch-board 13 amp socket and D2. This is necessary because with no lighting load plugged in, the leakage through the triac will give a glow in the mimic lamp which can be disturbing to the lighting operator. With no lamp plugged in, the channel should be switched off at the socket.

The point to connect D2 will be found as a copper rivet head on the rear of the socket and should be verified with an ohmmeter.


LOAD CONNECTION

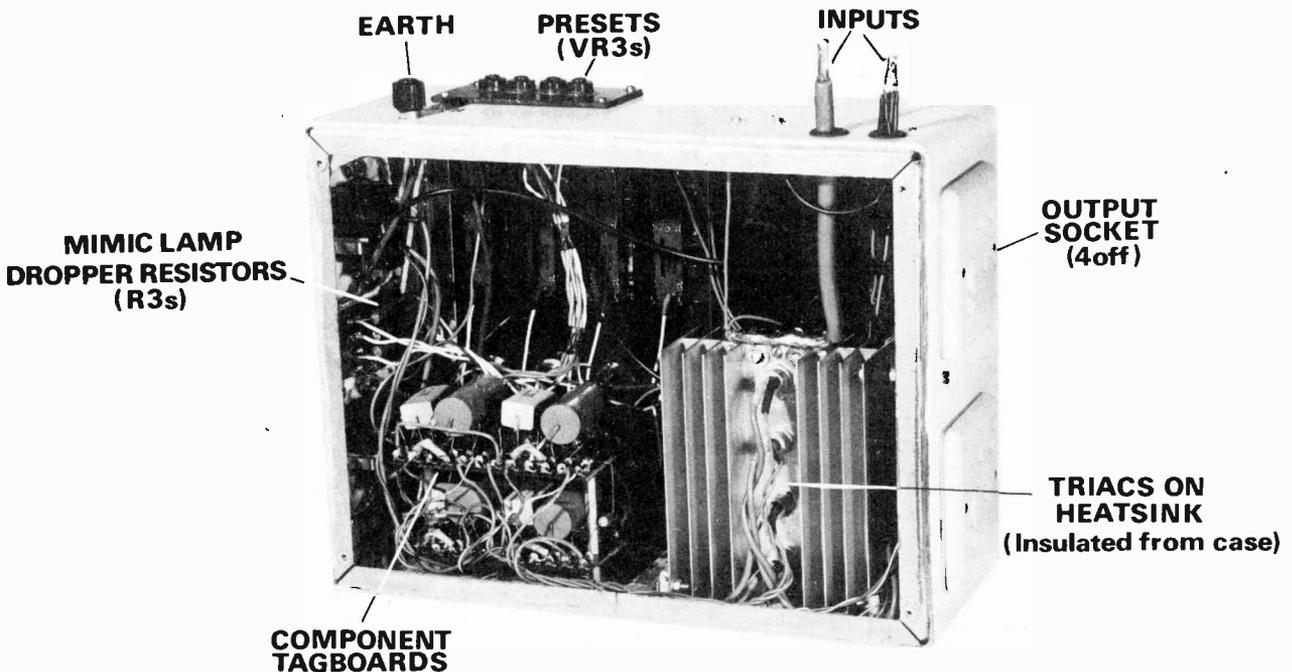The load is connected on the neutral side of the triac. This reduces the risk of electric shock from



Photograph showing the arrangement of the triac heatsink, the presets, the tagboards and the input connections within the case. *The heatsink must not touch the earthed case*

Fig. 3. Block diagram showing the four circuits of Fig. 2 interconnected and the extra components needed to complete the unit

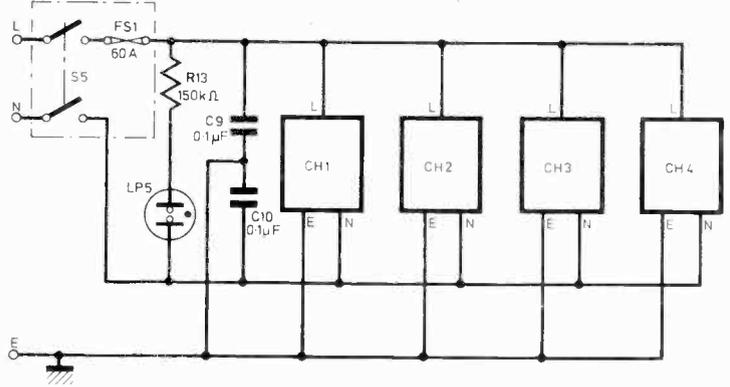

defective lamps, since the lamp is at neutral rather than live when faded down. It also enables all the triacs to be mounted on a heatsink without insulating washers although this has the disadvantage that the heatsink is live and must therefore be insulated from the case.


The triac, though a bi-directional device, operates best with the main terminal 2 (mt2) live with respect to mtl. For the SC50D mt2 is the threaded stud.


Interference suppression is obtained using two capacitors (C9 and C10) connected between the supply lines as shown in Fig. 3. Also seen on Fig. 3 is the mains indicator neon and the 60 amp fused switch.

CONSTRUCTION

The dimmer was designed to be mounted on a wall so the control box and the switched fuse were

Fig. 4. Layout of the components on the tagboard and interwiring for one of the four channels. Components should be mounted on the front panel, the case and the tagboards, and then interwiring should be done using this diagram and Fig. 3 as a guide. Wires which carry the current to the lamps should be heavy duty to reduce heating effects.

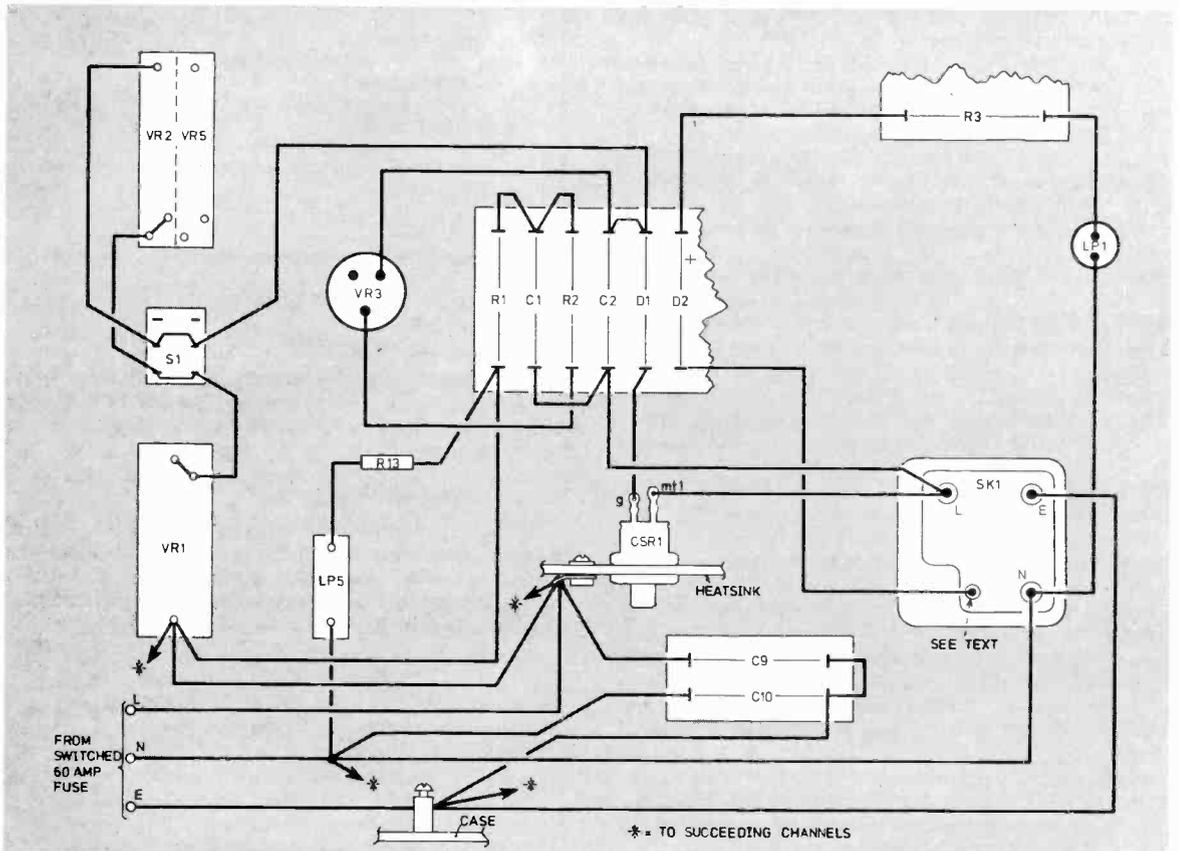

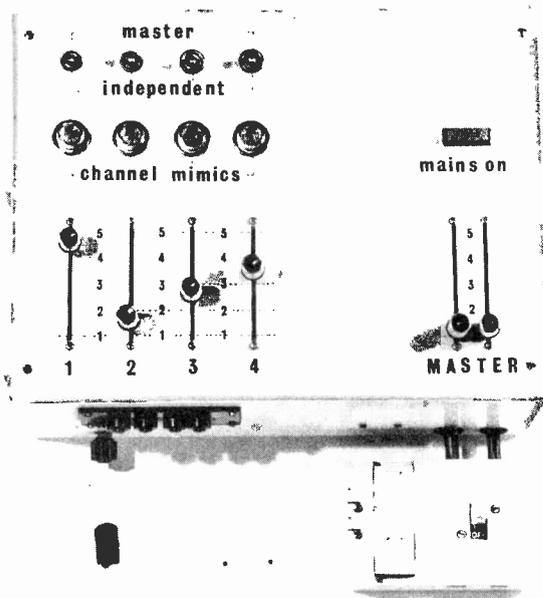

Photograph showing the completed unit and 60 amp switched fuse mounted on the backing board

fitted on a wooden panel fitted with mounting brackets (see photograph). The metal box used for the prototype is not generally available but any aluminium or steel box of sufficient size (13in × 10in × 5in) can be used.

The four triacs are mounted on a large heatsink which is connected to the live input via the switched fuse. A smear of heat-conducting grease should be applied before the triacs are bolted in position.

All the small components are mounted on two tagboards as shown in Fig. 4. The only exceptions are the four mimic lamp resistors (R3 etc.) which are mounted on a separate tagboard in a ventilated position.

The m.e.s. lampholders must be of the type which have both lamp terminals insulated from the case as neither must touch the case which is earthed.

The four preset potentiometers (VR3 etc.) are mounted on the outside of the case so that they are easily adjusted.

The output sockets are mounted two on either side of the case. The tagboards are mounted on pillars.

Plastic brackets are used to support the heatsink without it touching the case. Make sure that the lid of the case does not touch it when fitted.

Vents must be cut in the case to allow air to circulate if none are present.

Front panel layout is not critical, the photographs showing the prototype layout. Note that the two stereo sliders which form the Master Fader should be mounted as close as possible to each other so that they may be moved together. They may be physically joined with a metal bracket if this is desired.

Cables capable of carrying the 60 amp input current must be used for connection to the unit. A heavy duty earth cable should be connected to the case using a screw terminal.

COMPONENTS . . .

Resistors

- R1 150k Ω
 - R2 4.7k Ω
 - R3 2.7k Ω
- } $\frac{1}{2}$ watt carbon
10W wirewound

Potentiometers

- VR1 100k Ω linear slider
- VR2 100k Ω + 100k Ω linear stereo slider (each channel uses half of one)

Capacitors

- C1, C2 0.47 μ F 400V (2 off)

Semiconductors

- D1 Diac type ST2 (Henry's Radio)
- D2 1S557, BY100 or any 400V 1A diode
- CSR1 SC50D 400V 15A Triac (Henry's)

Miscellaneous

- LP1 6V 60mA m.e.s. lamp and holder
- SK1 13A switched mains socket (MK2957) + mounting plate MK2200 21L
- S1 Mains on/off switch

The components above are required for each of the four channels, i.e. four of each (except VR2) are required. The components below are required to complete the unit

Resistor

- R13 150k Ω (not needed if included with neon)

Capacitors

- C9, C10 0.1 μ F 1000V (2 off)

Miscellaneous

- LP5 Mains neon indicator
- S5 M.E.M. 60A switch/fuse
- 12 way tagboards (2 off)
- 4 way tagboard
- Screw terminal, 6in × 6in × 2in finned heatsink, plastic brackets, 16mm copper double insulated (p.v.c./p.v.c.)

PRACTICAL POINTS

To reduce the interference effects of the unit it should be used on a supply separate from that being used by any microphone or musical instrument amplifiers, i.e. the 60 amp cables to the input should be taken to the nearest low impedance mains supply, the local "main feeder."

Ordinary household ring main circuits will not handle the unit on full load. In the case of a house or small hall the connections should be made direct to the fuse box, having first checked that the incoming mains can supply 13kW.

Footlights present a special problem since they are often close to stage microphone cables. If possible use footlight feeder cable which has an earth screen totally enclosing the conductors.

The slots in the box for the faders was made using a Monodex metal cutter.

A heavy duty soldering iron is necessary for soldering the 60 amp cables.

Total cost of the unit was approximately £35. ★



BY FRANK W. HYDE

BLACK HOLES

There are many enquiries about "black holes" and not surprisingly they are mostly of the form "What is a black hole?"

The term "hole" is the main difficulty, just as it was with solid state devices. Perhaps this is because usually a hole is some space which is at an angle to a surface.

Since the situation is one of concentration of matter and energy it is better to use the word concentration. The new name then is a "black concentration" and in this case it means that energy and matter is not radiating outwards but is concentrated away from the observer. It is, therefore, a black condition.

Proceeding from there, imagine that the Sun in following its life course goes through the process of normal star evolution and death. It will expand to many times its present size to become a Red Giant. In expanding it will cool down and as the fuel of it becomes consumed the gravitational forces will cause it to contract to about one per cent of its volume. This will mean that it will become very hot again. It will then acquire a new name, that of White Dwarf. Its brightness will have increased and so will its density so that a cubic inch would weigh many tons.

However, by the nature of the process there is a limit to the compression and in the case of the Sun it will probably remain as a White Dwarf, gradually cooling down.

GRAVITATIONAL COLLAPSE

In the case of stars more massive than the Sun the energy produced during the life cycle may be such as to make the stage from Red Giant to White Dwarf much more

concentrated. In this case a state of gravitational collapse may occur and a "black concentration" will take place.

Not only does this effect apply to the star itself but also to the surrounding media. In this condition it is possible that other concentrations of matter nearby are sucked into the area.

The advent of gravitational collapse is likely to arise after the transition from Red Giant to White Dwarf. This could be because the White Dwarf stage is not a halting point as it were, and the energy of the shrinking from Red Giant may over-run the White Dwarf point. In this case the enormous energies will build up to a catastrophic explosion and a supernova would be the result. This will appear as an extremely bright object and parts of the original star will be flung out at fantastic speeds of the order of hundreds of miles a second. There will be left a small highly concentrated mass, the neutron star. This is the Pulsar according to the accepted current theory.

Sometimes the energy is so great that the situation is not ended at this point and the collapse goes beyond the neutron star point. It is here that the condition of the "black hole" is reached.

It is not easy to accept the implications of this manner of events. It would mean that no light or radiation of any kind comes out of this concentration.

The gravitational field is so great that in the comparatively short distance involved (if the Sun became a "black hole" it would be only two miles in diameter) matter in moving inwards from the "surface" would stretch out from the observer. In fact, there would persist for some time an image of the original matter and this would not appear to change for a very long time. In effect there would be a reversal of all the conditions that are regarded as normal.

NEW LOOK

At this point it is time to ask whether physicists have to take a new look at the whole situation. It would seem that there are no universal laws, but rather that the laws depend upon conditions as they are found. This is not merely a matter of reality but also of profound philosophical implications. It may be that other views will be expressed and that this interpretation is in itself rejected.

There is still no direct evidence, for the existence of the "black hole" but work which is going on at the moment may help to clear up the matter. It is hoped that there will be sufficient data shortly to report on the progress of a new project aimed at providing new evidence.

COMET KOHOUTEK

The comet Kohoutek, which is likely to make a sensational appearance and will be visible to the naked eye for four months or so, will be at its peak in December when it will be visible in full daylight. It will be visible to the naked eye from about the first of November.

There was not time for the organisation of a probe to intercept this comet though in other fields the early warning of its advent is useful. Professional gatherings have been held to set up a study programme and to avoid unnecessary duplication of observations.

Studies will be made in infra-red and observations in the 50-100 micrometre wavelengths will be made from a jet plane. It may well be that a programme will be set for observations from *Skylab*.

It so happens that a number of dispersed observations from automatic satellites and a probe will be able to provide useful data. Satellites *OSO-3* and *OSO-7* will be able to make photographic observations and *Mariner 10* will be able to monitor the inter-planetary medium as it proceeds on its journey to Venus and Mercury.

All these study programmes will help to practice different techniques which can be used for the special observations of Halley's comet which is due in 1986.

LIGHTS IN THE SKY

Three years ago a search for fluorescent pulses, induced by X-ray photons, was made. During this observation the fast atmospheric pulsations of light were discovered. Since this discovery there have been observations which threw more light on these effects.

At Ankara H. Ögelman has made observations with baselines of 175 and 3,300 kilometres. The results of this work are being correlated, but first results seem to indicate that these FAP's, as they are called, appear from discrete directions and are more frequent than was supposed.

The energies are being measured and later results will appear in this column.

MARS VEHICLES

Considerable re-design may be necessary for the manned vehicles to Mars because of the high radiation levels that might be normally encountered.

This conclusion arises from the examination of the materials of the *Apollo* spacecraft after returning from the Moon. The extent of the radiation has supplied the solution and it is thought a re-arrangement of the present design will be possible to overcome this hazard.

POWER SUPPLY BOARD

COMPONENTS . . .

POWER SUPPLY

Resistors

R32 1.5k Ω
 R33 470 Ω
 R34 470 Ω
 R35 39 Ω
 R36 33 Ω
 All $\frac{1}{4}$ W 10%.

Capacitors

C19 3,500 μ F 40VW
 C20 3,500 μ F 40VW
 C21 1,000 μ F 16VW
 C22 1,000 μ F 16VW
 C23 1,000 μ F 35VW
 C24 1,000 μ F 25VW
 C25 1,000 μ F 25VW
 C26 1,000 μ F 25VW
 All elect.

Semiconductors

D1 to 8 BK32
 (2 in parallel) Semicron.
 D9 to 12 B40 C1000
 Semicron.
 D13 24V Zener.
 D14 & 15 15V 10% Zener.
 D16 20V Zener.
 D17 18V Zener.
 All Zeners are 400mW
 TR6 TIP29

Transformer

T1 Primary 240V a.c.
 Secondaries
 1, 20-0-20V a.c., 4A.
 2, 24V a.c. $\frac{1}{2}$ A.

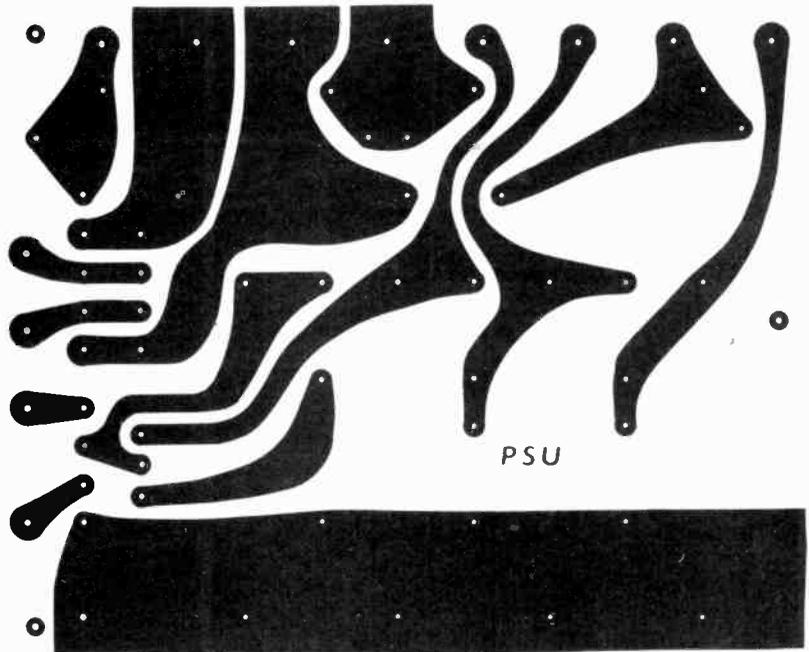


Fig. 3.2. Circuit board master for the Rondo power supply

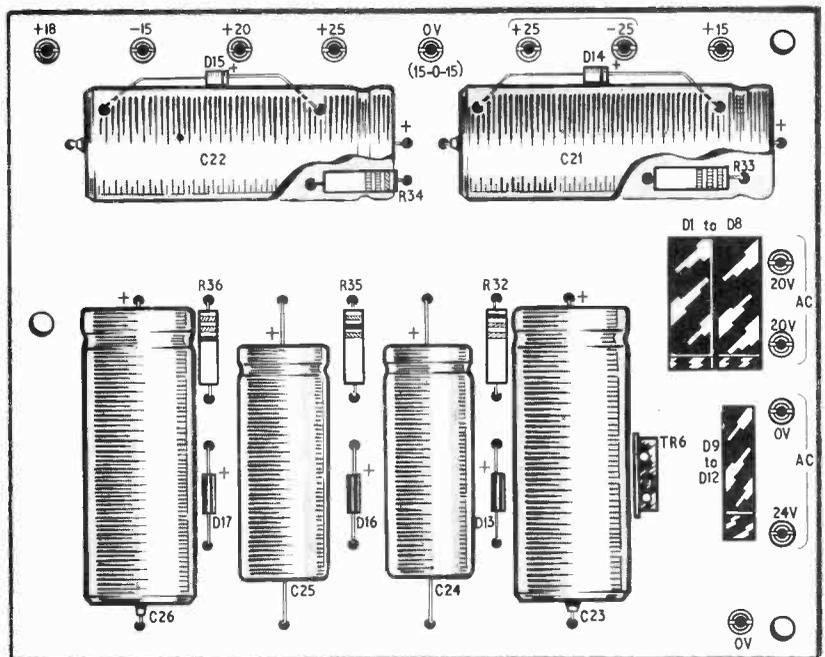


Fig. 3.3. Component layout for the power supply board viewed from the component side

MAIN CHASSIS DETAILS

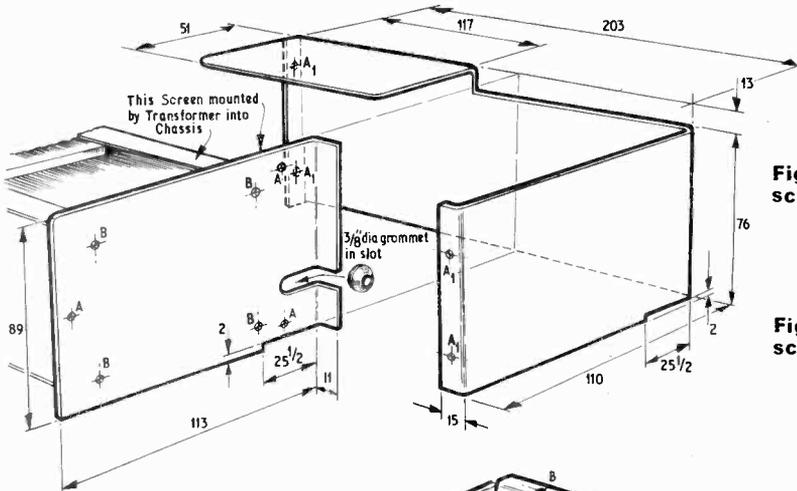


Fig. 3.5. Transformer screen metalwork details

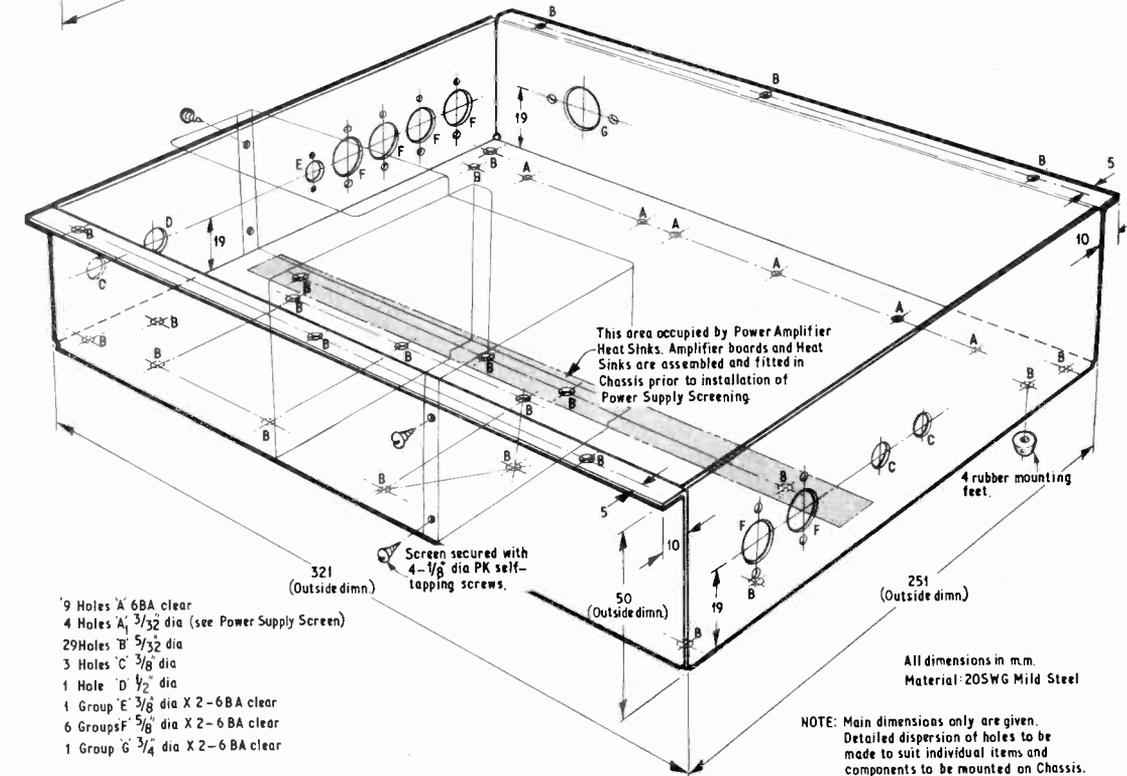


Fig. 3.6. Power supply screen metalwork details

Fig. 3.4. Main supporting chassis metalwork shown in general detail in the fabricated form and with external critical dimensions for simplicity. There should be no reinforcement where the sides meet, as the sides must be able to be pressed inwards when the wooden sleeve is fitted

POWER AMPLIFIERS SUPPLY

The dual rail supply is, as shown in Fig. 3.1, derived from a 20-0-20V transformer T1 winding with a 4A capacity rectified by two bridge rectifiers D1-D8 in parallel. The expedient of using two smaller (at lower cost) unmatched, bridge rectifiers in parallel is open to criticism because of "current hogging". That is, that the rectifier with the lower impedance will have a higher current flow. The rectifiers have been chosen so that, under all operating conditions, there are no detrimental effects due to this phenomenon.

The transformer centre tap is taken direct to the junction of two 3,500 μ F main smoothing capacitors C19, C20, joined negative to positive, and the rectified d.c. supply to the free positive and negative terminals of these capacitors respectively. The d.c. voltage, after rectification, is around +25 to -25V. (The centre zero is at earth potential.) The supplies to the main power amplifier output stages are taken direct from the main smoothing capacitors.

OTHER BOARD SUPPLIES

All the 748's are fed from ± 15 V d.c. rails obtained by dropping through resistors R33, R34 from the ± 25 V supplies smoothed by two 1,000 μ F capacitors C21, C22. As these rails do not have to be at precisely 15V but the i.c.s have to be protected against exceeding a maximum rating of 18V, they are "clamped" to 15V by two Zener diodes (D14 and D15).

The positive rail and negative earth supply is obtained from a separate winding on the transformer T1. This winding is 24V a.c. at 250mA and is rectified by a 1A bridge rectifier, D9 to D12, smoothed and then regulated by a series regulator circuit TR6, R32 and D13 to 24V d.c. and smoothed again.

From this point is taken the supply to the varicap diodes of the f.m. tuner.

A further ladder of droppers, Zeners and smoothing capacitors produces 20V d.c. to the SQ decoder, 18V d.c. to the a.m. tuner, f.m. tuner head transistors, i.f. stages and the stereo multiplex decoder. The values of the ladder are chosen so that either the a.m. or f.m. tuner may be on, or both tuners off, without disturbing the voltages of the other supplies significantly.

The components C26 and C27 and resistor R37, together with D18 are associated with the tuner unit (yet to be described) and in fact appear on that unit's board. They are shown here merely for completeness.


CONSTRUCTION

The power supply p.c.b. master negative is shown in Fig. 3.2 which indicates the simplicity of the circuit in practice.

The component layout appears in Fig. 3.3 which is self explanatory. Capacitors C19 and C20 are too large for board mounting and are in fact clamped in the main chassis.

MAIN CHASSIS

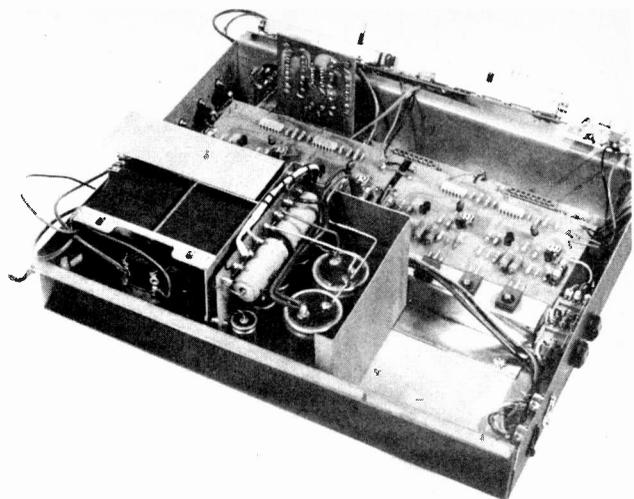The main chassis member is a rectangular box-form which in fact sits on its back in the final assembly. Thus it is used as a trough with components mounted within it rather than in the more conventional manner.



General view of the "trough" form of the main chassis for the Rondo showing the orientation of the power amplifiers and power supply with some of the general wiring in place. Plug and socket holes are not sized as this will depend on items selected

The chassis is shown in the bent-up form in Fig. 3.4. The material used for the prototype was 20 s.w.g. mild steel plate but of course this may present some difficulties to constructors since it is not easy to bend. Thus it is possible to use 16 s.w.g. "half-hard" aluminium sheet which is somewhat easier to bend or, indeed, to fabricate the structure from flat sheets cut to size. For this reason only the major dimensions have been given as it is felt that each constructor will probably adopt his own style of construction.

It should be added that the chassis, in the prototype design, contains all the various parts of the system and supports the outer wooden case and fascia which is in the form of a sleeve which slips over the unit and is fastened to the chassis.

PLUGS AND SOCKETS

As individual constructors may wish to vary the types and sizes of plugs and sockets used the positioning shown is open to variation to suit though of course major shifting of components is not advised as this can create feedback paths for which the equipment is not designed.

CHASSIS SCREENS

The power supply includes the mains transformer, board and main smoothing capacitors and the whole is placed behind a shield to cut down hum pick-up at the pre-amplifier and elsewhere.

Two screens are used, as illustrated in Fig. 3.5 and 6. The smaller acts as a support for the power supply p.c.b. and is fastened to the transformer using 4BA screws. The p.c.b. is then attached to the screen using 6BA screws and $\frac{1}{8}$ in spacers.

The larger screen is assembled later in the sequence and is held in place using self-tapping screws.

Note that the transistors in the power amplifier last month should be type MJE3055K

Next month we will finalise the mechanical assembly details and discuss the unit interwiring

Gerry Brown . . .

ON THE FRINGE



DOGGED RESISTANCE

Honestly, the trouble to which people go in order to maintain their various equilibria.

The latest in this mania for status quo manipulation appeared in a letter to a professional U.S. magazine. This, in fact, took the form of a reply to an earlier piece of correspondence which complained about noise from a barking dog, and which simply requested "Help! Widget wanted to drive the Mutts Nuts."

Help, if this is what it could be referred to, appeared a month later as a package deal comprising a 20kHz oscillator and (twenty watt!) amplifier combo driving a hi-fi tweeter horn. The suggestion was, that by continuous use, although no human would be able to hear the thing, poor ole' Fido would make such an awful din that his ever-loving owner, thinking he'd gone out of his tiny mind, would be just itching the next day to have him put down!

Now no one could accuse me of holding any torches for the canine community, nevertheless, I cannot help feeling that this is a singularly pernicious use of electronics.—One couldn't help noticing that the correspondent had asked to have his name withheld!


LSI or AU PAIR?

The number of times we have to hear about the feasibility of robot "flunkies" in the home, and how extraordinarily easy it's all going to be once they're installed. All you need is a handful of super-LSI chips, and you'll never look back! No doubt, the electronics represent no

insurmountable problem, but how practical would something like this be, even assuming the mechanical aspects could be solved?

The variety of jobs that can be performed by automated equipment is already overwhelming; what with tumble driers, telephone answerers, record players, etc., it might even be questionable whether a place *exists* for robots in the true sense of the word. Yet, I read, just last week, that Dr George Müller of Systems Development Corporation, California, reckons that a computerised set-up of this sort would be a viable proposition within, say, ten years.

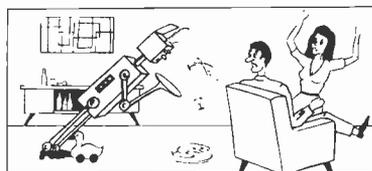Once written, I suppose, executive programmes having the same general format could be hard-wired into the devices prior to despatch. The "crunch" might come when the new owner needed to programme the confounded thing for the sundry tasks around the home.



Imagine trying to write a programme for accomplishing the "simple" job of pouring drinks. You would need to tell it to "come out of your storage cupboard", "turn left after three feet", "continue for nine feet seven inches" (at this point you might be wondering whether it only understood metric), "stop", "move right arm slowly towards cupboard right-hand handle", "grip handle gently and rotate it 180 degrees counter-clockwise" (supposing that the catch didn't release until 181 degrees?).

"Carefully open door 120 degrees, then release handle", "lower arm, and scan inside cupboard for port bottle (does robot think I mean the bottle on the left?)", "if located, remove the cork in this bottle and pour a quantity of liquid from the bottle into each of the glasses situated below the bottle rack", "ensure that each glass is only filled to the $\frac{3}{4}$ mark", etc., etc.

With such a system, one need only forget about junior's toy duck, 'plum in the middle' of the automaton's path, to give it a full-blown seizure!

A machine able to rely on learning techniques might prove to be a better proposition, always provided you could tolerate the broken glass, wine-sodden carpets, and the bill from the psychiatrist while it got the hang of things!

MAINSTREAM


By nature (I'm told) the trout is a lazy sort of fellow; loves to bask himself in the sun, and only makes a sudden dart across the current if, in his myopic way, he fancies he's seen a fly somewhere on the surface. In this life, though, there is rarely anything that escapes exploitation and the trout represents a typical case in point.

Recently, you see, the waterworks at Boran sur Oise, near Paris, have overcome some difficulties associated with the monitoring of pollution levels by recruiting the aid of this delicious member of the aquaticeae. Seemingly, ordinary detection/warning systems in this application are insufficiently sensitive; as a corollary, the waterboard's laboratory have "roped-in" three good-sized brown trout to do the job instead.

Each animal is located in a glass-sided tank fed from normal supply water and running at a rate consistent with typical river current. Normally, the trout orientates himself up-stream; however, if conditions cause the water to be slightly polluted, he'll about-turn to face downstream.

By fitting up each of the fish with tiny electrodes, an alarm can be triggered whenever all three fish do a simultaneous "flip round". Individuals turning-tail are ignored by logic ANDING circuits to avoid false alarms.

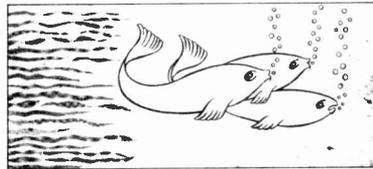Several days of this treatment do not appear to upset these creatures, in spite of the fact that if any of them stop swimming they are given an electric shock into the bargain. Since these animals are required to work in a sterile environment one wonders what technical arrangements have been made to feed 'em too!



BACK NUMBERS WANTED

Anyone who can supply the undermentioned are asked to communicate directly with the reader.

December 1971
Mr. J. Bickerscaffe, 15 Deanshill Close, Stafford.

November 1969, February to April 1970
Mr. S. R. Dunning, 103 Glebe Road, Deanshanger, Wolverton, Bucks.

July to October 1972
Mr. J. Y. T. Lee, 20 Wong Chuk Hand Road, 2nd Floor, Aberdeen, Hong Kong.

September 1972
Mr. K. R. Whitbread, 14 The Orchard, Bedford Park, London, W4 1JX.

Any Back Numbers
Mr. D. Lawrence, 8 Stringers Drive, Rodborough, Stroud, Glos.

May 1972
Mr. J. Hoppe, Murraymead, Bracknells Lane, Hartley Wintney, Basingstoke, Hants.

October, November 1972
Mr. L. Davis, 27 Highfield Avenue, Burntwood, Nr. Walsall, Staffs.

May 1969 to March 1970
T. Hall, 60 Archers Road, Marlborough Estate, Takajuna 10, Auckland, New Zealand.


August 1967
Mr. M. Ferguson, 6 Boundary Road, Thornlands, Queensland, 4163, Australia.

We regret that back numbers of Practical Electronics can no longer be supplied. We will try to publish announcements of readers' requirements (without a guaranteed date) free of charge.

look! electronics really mastered

... practical
... visual
... exciting!

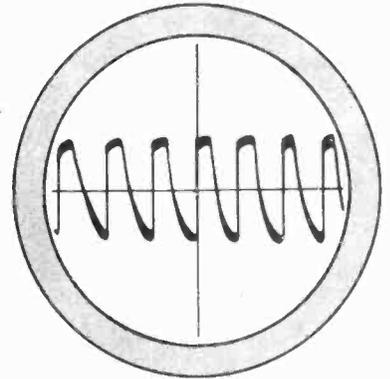no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

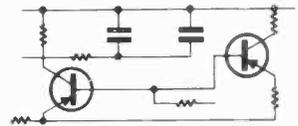2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers. etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EL113

special free gift also to all our students

Candis Ltd.

P.O. BOX 25, CANTERBURY, KENT
TEL.: CANT. (0227) 52139

THE FAMOUS WELLER NOW AVAILABLE TO YOU

- ★ TEMPERATURE CONTROLLED
- ★ IRON PLATED LONG LIFE TIP
- ★ LOW VOLTAGE ISOLATED ELEMENT

L.E.D. Red, 30p,
L.E.D. Green, 75p.
MINITRON 3015F, £1.50.
INTEGRATED CIRCUITS in 8-14
D.I.L. packages: 741 36p; 748 38p.
Hi-Fi stereo pre-amps.: TBA23 I
£1.43; CA3052 £1.30.
F.M. decoder limiter 5111A, £1.
0.25 watt audio amp. MFC4000, 45p.
Timing circuit 555V, 80p.
3 watt audio amp. SN76013, £1.75.
TIS88A, 36p; TIP41A, 70p; TIP42A,
85p.
100V 25A Plastic Power Transistors:
TIP35C £3; TIP36C £4.
2N3055 50p.

MINIATURE SWITCHES


S.P.C.O. Toggle, 35p.
S.P. Push to make, 29p.
D.P.D.T. Slide, 10p.

AEROSOLS


Freezer, 70p.
Printed Circuit Lacquer, 75p.
Silicone Grease, 75p.
Contact Cleaner, 75p.
Anti-Static Inhibitor, 85p.

SOLDERING AIDS

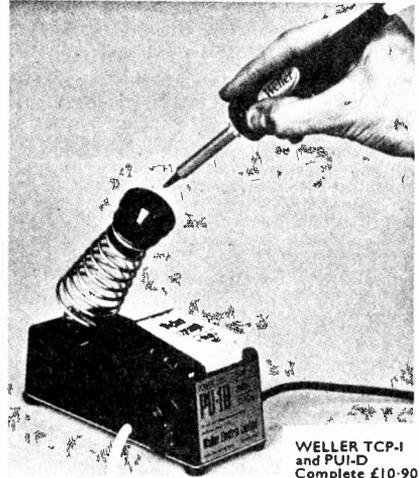ADCOLA L646 23 watt, mains iron,
£2.10.
De-Soldering braid, 60p.
18 SWG SOLDER 0.5 kilo, £1.16.
22 SWG SOLDER 0.5 kilo, £1.26.
18 SWG SOLDER 2.5 kilo, £5.50.



WELLER TCP-1
and PUI-D
Complete £10.90

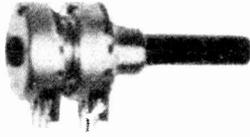

P.C. Mounting Stereo
Pots 100K Lin. 100K Log.
10K Log. all at 35p.

Please add 10% VAT to total cost of all items

All spares readily available

VARICAP STEREO TUNER F.M. ♂

(ACTUAL BEECHING UNITS)
IN STOCK

MODULES LP1185/86	£9 per pair
REGULATOR MFC4060	£0.78 each
DECODER MC1310P	£3.15 each
PRINTED CIRCUIT BOARD—GLASS FIBRE (With lettering)	£1.87 each
READY BUILT AND TESTED BOARDS	£23 + 25p postage
COMPLETED TUNERS IN TEAK CABINETS	£34 + 35p postage

(BRUSH ALU. FRONT PANEL with 6 BUTTONS, MAINS + 5 STATIONS)
VAT. INCLUDED

STILL SOME LEFT!

25 W R.M.S. DISCO AMPLIFIERS (JUKE BOX)
ONLY £10 each + 35p postage

CHASSIS CONSTRUCTION WITH POWER SUPPLY
S/C PROTECTED. DELIVERS 25W INTO 7Ω
(OR 2 × 15Ω). FROM PICK UP: SENSITIVITY
ABOUT 100 MV INTO 1 MΩ. USING 40361/40362/
MJ481/MJ491 TRANSISTORS

EACH ONE TESTED, REQUIRING ONLY A
VOLUME CONTROL


READY BUILT AND TESTED STEREO DECODERS
FOR 9V-12V SUPPLY £4.50 + 10p postage

B & B ELECTRONICS

64 MANNERS ROAD, BALDERTON, NEWARK
NOTTS. Telephone: NEWARK 6895

PHOTOELECTRIC KIT

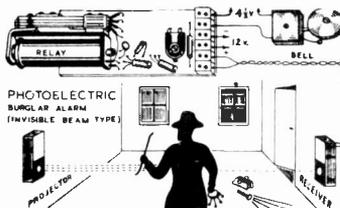CONTENTS. P.C. Chassis Board, Chemicals, Etching Manual, Infra-Red Photo-transistor, Latching Relay, 2 Transistors, Diode, Resistors, Gain Control, Terminal Block, Elegant Case, Screws, etc. In fact everything you need to build a Steady-Light Photo-Switch/Counter/Burglar Alarm, etc. (Project No. 1) which can be modified for modulated-light operation with a few additional components.



PHOTOELECTRIC KIT £2.85

Postage and Pack. 15p (U.K.)
Commonwealth
SURFACE MAIL 25p
AIR MAIL £1.40
Australia, New Zealand,
S. Africa, Canada and U.S.A.
Also Essential Data Circuits
and Plans for Building
10 Advanced Designs

INVISIBLE BEAM OPTICAL KIT

Everything needed (except plywood) for building: 1 Invisible-Beam Projector and 1 Photoell Receiver (as Illustrated). Suitable for all Photoelectric Burglar Alarms, Counters, Door Openers, etc.

CONTENTS: 2 lenses, 2 mirrors, 2 45-degree wooden blocks. Infra-red filter, projector lamp holder, screws, nails, brackets, building plans, etc. Price £1.45. Postage and Pack. 10p (U.K.). Commonwealth: Surface Mail 20p, Air Mail 50p.

LONG RANGE INVISIBLE BEAM OPTICAL KIT

CONTENTS: As above. Twice the range of standard kit. Larger Lenses, Filter, etc. Price £2.10. Postage 15p (U.K.). Commonwealth: Surface 20p, Air Mail £1.15.

BIOFEEDBACK AMPLIFIER KIT

Tunable, General-Purpose, Interference-Rejecting Differential Amplifier for experimental investigation of signals produced by the brain, heart and muscles. When used with an oscilloscope, or aural indicator, it enables you to monitor your brainwaves, learn to relax, meditate, etc.

CONTENTS: All Capacitors, Resistors, Pots, Semiconductors, I.C., Electrodes, Leads, Chassis, Case, Batteries, Plans and Instructions. Price £4.75 postage and pack. 25p (U.K.). Commonwealth: Surface 30p. Air Mail £1.

ALPHA-BETHA-THETA BRAINWAVE MONITOR KIT

Aural Brainwave Indicator for use with a Biofeedback Amplifier. Converts subsonic brain frequencies into audible signals for easy recognition.

CONTENTS: Resistors, Pots, Capacitors, Transistors, Diodes, Leads, Chassis, Case, Earphone, Battery, Plans and Instructions. Price £3.25, postage and pack. 15p (U.K.). Commonwealth: Surface 20p. Air Mail 75p.

YORK ELECTRICS Mail Order Dept.


335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send S.A.E. for full details, a brief description of all Kits and Projects

LOGIC TUTOR


EXPERIMENTS...

THE HALF ADDER

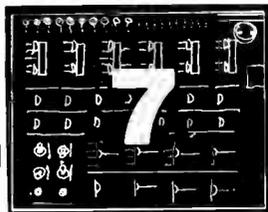

by M. J. Hughes

THE circuit we left you to puzzle over last month was another form of the EXCLUSIVE OR gate. The Boolean expressions for the various nodes are shown in Fig. 1. The outputs of the two gates that are WIRED OR'd together would have been $\bar{A} + \bar{B}$ and $A + B$ respectively without the link between them but as soon as the link is made these two functions become AND'ed together and then it is a simple matter of Boolean manipulation to show that the output function is EXCLUSIVE OR.

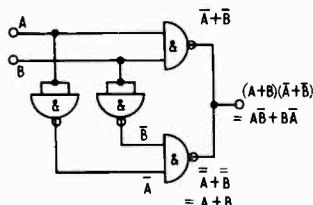

Exclusive OR truth table

A	B	AB+BA
0	0	0
1	0	1
0	1	1
1	1	0

0+0=0
1+0=1
0+1=1
1+1=0 (carry 1)

Binary Addition


It is necessary to understand the basic principle of adding together two binary integers. The rules are very simple—in fact exactly the same as in conventional denary arithmetic except that whenever you get a sum greater than 1 you must carry over a digit into the next column. Let's take the simple case of adding two single digit numbers together. We'll call the digits A and B to differentiate between them and show the sum and carry—when necessary—in the following simple table. Note that we are carrying out pure addition here and in this instance + means plus and not OR

Digit A	Digit B	Sum
0	+	0 = 0
1	+	0 = 1
0	+	1 = 1
1	+	1 = 0 (carry 1 over)

In this list of sums we have used every permutation of the two numbers. Compare the arithmetic with the truth table for the EXCLUSIVE OR gate shown in Fig. 2. If we used electrical signals to represent the numbers we wanted to add together and could accept an electrical signal as an answer you can see that the output of an EXCLUSIVE OR gate gives us a true representation of the sum of the two binary integers. It does not, however, give us the carry digit when we want to add 1 and 1. In addition we only need a carry when we have 1 AND 1 so it is a simple matter to provide this output from the same pair of inputs by introducing an AND function.

Fig. 1. Answer to last month's problem. The circuit is an EXCLUSIVE OR

Fig. 2. Comparison of binary addition with EXCLUSIVE OR truth table

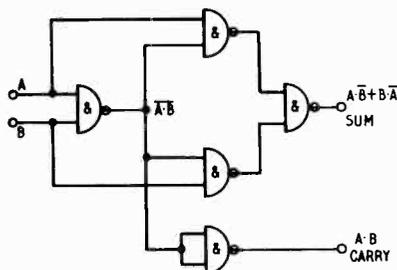

A	B	SUM	CARRY
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

Fig. 3. A half adder is an EXCLUSIVE OR plus an AND function of the inputs

Fig. 3 shows how this can be done by taking the $\bar{A}B$ function—generated at the centre node of the EXCLUSIVE OR—and inverting it. You can see that the truth table for the circuit shown in Fig. 3 is an exact replica of the answers we would wish to get when carrying out a binary addition. The circuit is called a half adder. As is often the case there are various ways of designing half adders—you now know at least three ways of making the EXCLUSIVE OR function so try making some more half adders yourself on the Logic Tutor.

You might query why this is called a half adder. The reason is that when we come to add together two multidigit numbers (see Fig. 4) our current circuit is quite capable of dealing with the least significant column (i) but when we come on to the other columns we have to be able to add together the respective digits of numbers A and B but also have to be able to add in any carry over that was generated in the previous (lesser significance) column. Thus to add multidigit numbers together we must have a circuit that can handle three inputs.

A circuit that will do this is called the full adder and we shall deal with this next month.

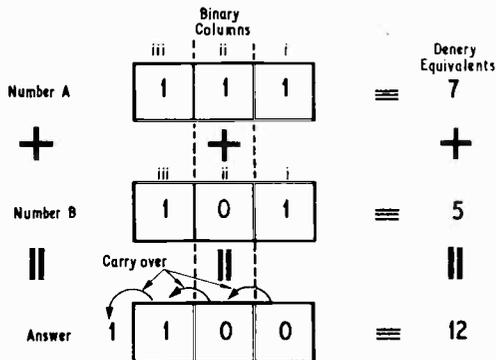


Fig. 4. When carrying out addition of two multidigit numbers a half adder is capable of dealing with column (i) but when it comes to column (ii) there must be provision for three inputs, digit (ii) of A + digit (ii) of B + possible carry over from column (i). The same applies to all higher power columns

PE Sound Synthesiser 10

KEYBOARD

With these added units the keyboard becomes a unique musical instrument . . .



WHEN the Sound Synthesiser was originally presented for publication it was the intention that it should be classed as a general purpose instrument which could be exploited in the widest possible number of ways and yet retain a basic simplicity of design and ease of construction. During the course of the series however many readers have commented that the musical capabilities of the instrument have been severely restricted by the lack of logarithmic v.c.o.s and thus the oscillator to be described in this article has been included in the keyboard unit in the hope that it will put matters right.

Prospective constructors should note that although the logarithmic v.c.o. is based on the linear v.c.o. which was described in Part 3, the parameters of operation are quite different and the setting-up is rather more critical if it is desired to operate the device within the limitations of a precise range of control voltages.

Although limited to about 11 octaves range with the design values given, it is possible to adjust the operating points to cover a much wider bandwidth. The prototype has operated quite happily from less than 1Hz to greater than 150kHz with a control voltage swing of about 11V and there is no reason to suppose that it could not reach 1MHz, or greater, if the integrator output voltage were to be reduced and a faster comparator employed. As a result it is possible that the oscillator may be suitable for a number of applications outside the sphere of sound synthesis.

The v.c.o. is shown in block schematic form in Fig. 10.1. The control voltage to the oscillator is modified in a differential input summer and then applied to a constant current generator housed in a "transistor oven". The output of the current generator is then led to an integrator/comparator stage through the medium of a current switch which is controlled jointly by the comparator and inverter. The triangular wave output is led to a waveform shaping circuit which provides a sine wave having a very low harmonic content.

DESIGN CONSIDERATIONS

It was decided that the best way of providing a log law performance to the basic v.c.o. outlined in Part 3 of the series was to utilise the entirely predictable logarithmic relationship between the base/emitter voltage (V_{be}) and collector current (I_c) of a bipolar transistor.

Start Here !

This month we start detailing the operation and construction of the keyboard unit for the synthesiser. Regular readers of P.E. who may have been put off by the apparent complexity and/or cost of the synthesiser project as a whole may be interested to learn that the facilities offered by the keyboard unit are such as to allow the instrument to be classed as a music synthesiser in its own right, and at an overall cost of less than £80. Main features of the instrument are as follows:

Two tracking oscillators featuring a variable logarithmic law which allows compatibility with a wide range of control voltages and provides square, triangular and high purity sine wave outputs.

A novel "floating" divider system which greatly simplifies tuning the instrument and by means of which the compass of the keyboard can be swung, in tune, from a low frequency of about 6Hz to a high frequency greater than 27kHz. The divider features a switchable "span" facility.

Two modulation amplifiers by means of which the oscillators may frequency modulate one another either separately or at the same time.

Two analogue memory circuits which retain the last programmed divider voltage to either oscillator. Separate portamento controls are incorporated in the hold circuits giving six values of delay from instantaneous to one second.

Two simplified envelope shapers incorporating voltage controlled amplifiers each having a variable Attack and Decay characteristic and featuring a switched percussive attack.

A simple two channel, fixed gain mixer.

Finally, the keyboard divider system incorporates a link switch which allows the two oscillators to be programmed independently by the lower 18 and upper 31 keys respectively. This particular feature greatly improves the "live performance" possibilities. An independent p.s.u. is included.

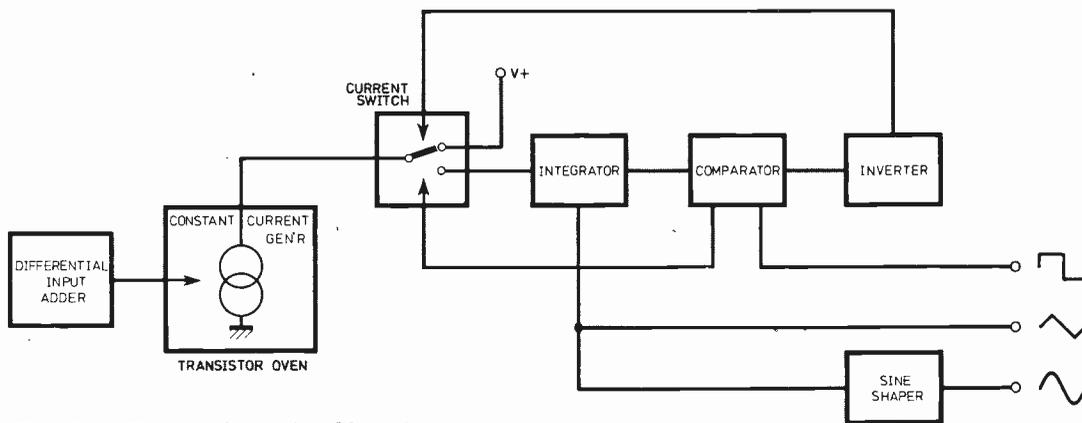


Fig. 10.1. Block schematic of logarithmic v.c.o.

Although the current generator could be almost any discrete transistor the effect of ambient temperature variations would be such as to cause the current demand to vary quite widely and thus adversely affect the "tune" of the oscillator. Consequently it was decided to make use of the inherently close thermal and electrical matching between transistors mounted in a monolithic integrated circuit — the ML3046P and CA3046 both having been tried in the prototype. Extremely close thermal stability is ensured by employing two of the transistors in the array as a heater and sensor respectively and terming the whole arrangement as a "transistor oven."

Fig. 10.2a shows a detailed arrangement of the "oven" while Fig. 10.2b shows the pin connections for the 3046 device. Fig. 10.3 illustrates how the V_{be} of transistors on the array will vary over a wide range of temperatures and provides a guide as to the actual temperature of the chip when the V_{be} of the sensing transistor is known.

In Fig. 10.2a Q1 serves as the heating element while Q2 is used to sense the temperature of the chip. The V_{be} of Q2 is compared with a reference

voltage set up by R3, VR1 and R4. The reference voltage will correspond to a temperature which is considerably higher than ambient and will thus be at a lower value than $Q2V_{be}$ when power is first applied. Thus the comparator will switch positive and turn on Q1. As the temperature of the chip rises $Q2V_{be}$ will fall to a point where it is equal to or less than the reference voltage at which time the comparator will switch negative and turn off Q1.

The criteria determining the value of R1 are as follows:—

1. The temperature of the chip must be set considerably above normal ambient conditions (say 40 degrees to 45 degrees Centigrade).
2. The combined power dissipation of Q1 and Q2 must exceed, by a wide margin, the combined power dissipation of the remaining transistors in the array.
3. The current switching of Q1 must not be so violent as to impart a significant jitter to the oscillator waveform.

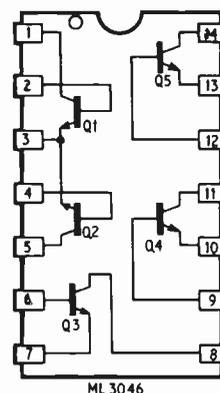
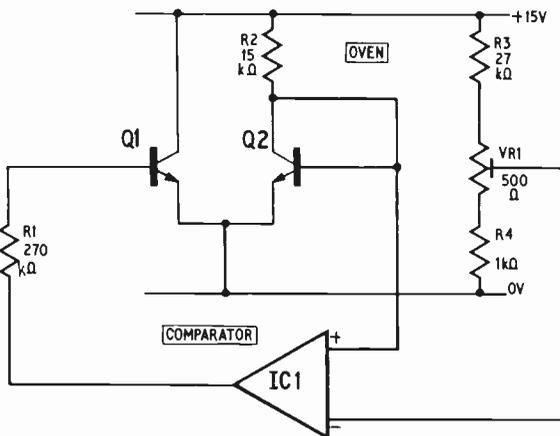


Fig. 10.2(a). Detailed arrangement of the transistor oven; (b) pin connections of the ML3046 and CA3046. Note that pin 13 must be connected to the most negative point in circuit

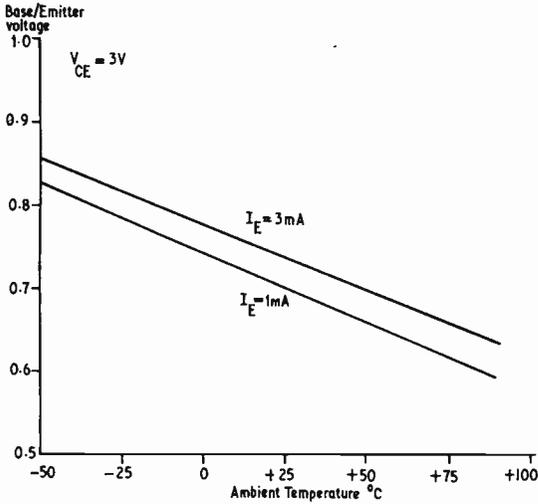


Fig. 10.3. Showing the change in V_{be} for variations in ambient temperature for the ML3046 and CA3046

In practice the value of R_1 which gives the closest approach to the above criteria is 270 kilohms. With this value it is possible to set $Q_2 V_{be}$ to 680mV, that is approximately 45 degrees Centigrade while the combined dissipation of Q_1 and Q_2 is about 90mW as opposed to the combined dissipation of Q_4 and Q_5 (the current generators) of about 1.4mW. Detailed setting-up instructions for the "oven" are given later in this article.

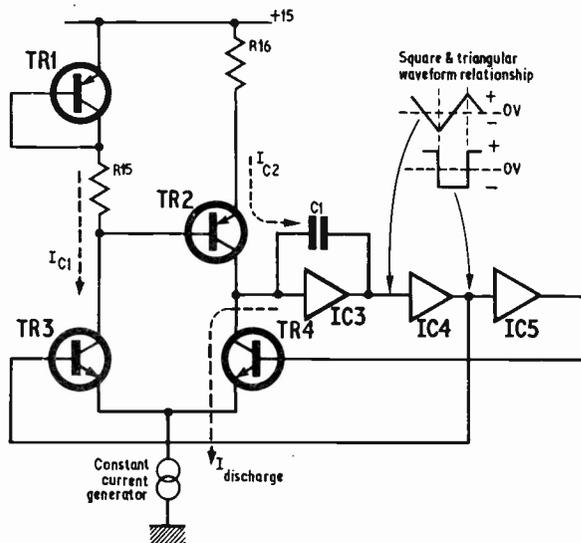


Fig. 10.4. Simplified layout of oscillator section showing operation of current switch

CURRENT SWITCH

Having thus established a thermally stable current generator it now remains to couple this to the input of the v.c.o. In the linear version of the v.c.o. a diode bridge was employed which was switched entirely by the action of the comparator. While this system could no doubt still operate satisfactorily a rather more sophisticated version has been adopted which utilises transistors in place of diodes. The so-called current switch is illustrated in Fig. 10.4. Assuming that the output of IC4 is positive to start with, the operation of the current switch is as follows.

With IC4 positive, the output of IC5 is negative and thus TR3 and TR4 are on and off respectively. With TR3 on the current generator demand will cause a drain across R_{15} and thus make the base of TR1 more negative than its emitter. TR1 will then turn on in proportion to the demand of the current generator and a current flow I_{c1} is established through TR1, R_{15} and TR3. I_{c1} will set up a p.d. across R_{15} which will have the effect of biasing on TR2 and establishing a second current flow, I_{c2} through R_{16} and TR2.

This latter current flow is entirely dependent upon the demand of the current generator which is varying the p.d. across R_{15} and thus TR2 may be said to track the demand of the current generator. The closer the matching of R_{15}/R_{16} and TR1 and TR2, the better will be the tracking and the better the symmetry of the integrator output waveform. Thermal stability is not a problem with TR1 and TR2 since the arrangement gives an equal and opposite reaction between these transistors for any variation in temperature.

I_{c2} causes the integrator to ramp negatively and at a predetermined negative level IC4 will switch negative and IC5 positive. Thus TR3 and TR4 are now off and on respectively and since TR3 is off so also is TR2 and the current generator now discharges C_1 via TR4 at a constant rate. The integrator will thus ramp positively until the switching point of IC4 is reached at which time the cycle repeats.

SINE WAVE SHAPER

The sine wave shaper used in the v.c.o. has been adapted from a design by D. T. Smith which appeared in *Wireless World* (Feb. 1973). Fig. 10.5 shows a detail of the circuit together with the waveforms presented at various points when the circuit is producing a sine wave having a low harmonic content.

The sine-shaper utilises the non-linear characteristics of a field-effect transistor in order to produce the desired output waveform and thus the operating points are quite critical. R_{20} , R_{21} and $D_{5,6}$ provide a network which allows the gate to track the input signal and apply the necessary degree of "pinch-off" as the source signal approaches its maximum on both positive and negative half-cycles. Since the gain of the f.e.t. is changing continuously relative to the input signal the device may be considered to be operating in the ohmic region as a voltage variable resistor.

In Fig. 10.5 VR_5 controls the d.c. offset of the input waveform and it is necessary to compensate for slight asymmetries which could be introduced in

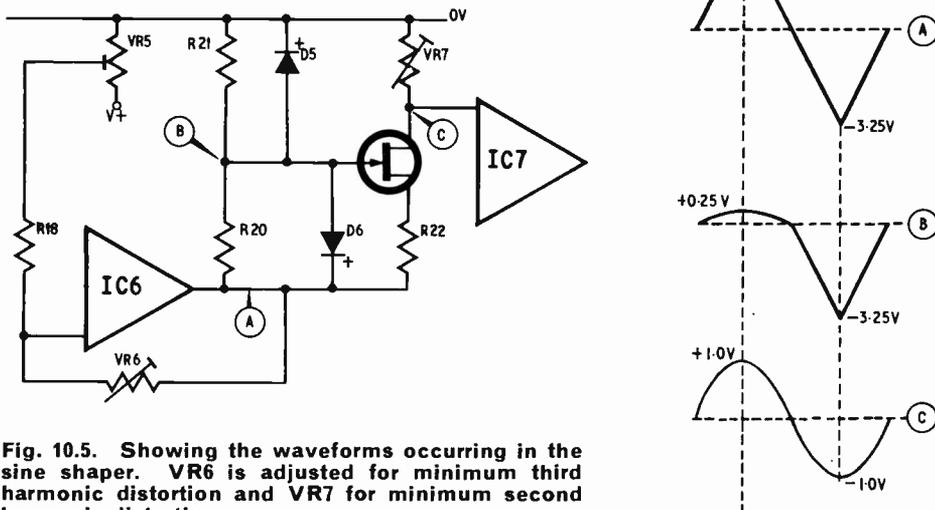


Fig. 10.5. Showing the waveforms occurring in the sine shaper. VR6 is adjusted for minimum third harmonic distortion and VR7 for minimum second harmonic distortion

the oscillator section. Over adjustment of VR5 in either direction can provide an alternative output waveform rich in harmonics.

VR6 sets the input signal level to the network. Too low a setting and the output waveform will be triangular while too much gain will give a waveform which is virtually a rounded off trapezoid. Careful adjustment of VR6 enables third harmonic distortion on the output to be reduced to a minimum.

VR7 controls the output amplitude of the signal. Too great a setting and the sine wave will become peaky while too low a setting will result in a squat, flattened out, waveform. Thus VR7 may be considered to control the second harmonic level and should be adjusted to minimise this characteristic.

BUILDING THE OSCILLATORS

The theoretical circuit of the complete oscillator module is shown in Fig. 10.6 while the recommended circuit board layout is shown in Fig. 10.7. It is strongly urged that construction of the module follows the guidelines suggested otherwise the interdependence of some of the controls is likely to make the final setting-up something of a nightmare.

Construction should start with assembly of the transistor oven, differential input summers and current generators. R1 should be 470 kilohm and left with fairly long leads to facilitate exchange during the final setting-up. Position the temperature control, preset VR1 to the R3 end of its travel to ensure that the comparator goes negative and thus turns off Q1 when power is applied. R10 should then be temporarily linked to the 0V rail and a decision taken as to the fate of R11. This resistor is optional in that it may be utilised to provide a third controlling input to the v.c.o. or it may be omitted at this stage without affecting anything. However, if it is decided to include R11 for the purpose of possible future additions to the circuitry it is important to remember that its presence could possibly compromise the setting-up of the oscillator if certain precautions are not taken.

If a third programming signal is to arrive at the oscillator from a low impedance source such as the output of another operational amplifier it is important that R11 also be temporarily linked to the 0V rail. Alternatively R11 may be left open circuit with the idea of using it only for the provision of occasional programming signals during which the tuning of the oscillator will have to be adjusted by means of VR4. In the setting-up instructions which follow R11 is open circuit.

SETTING UP

Since only one current generator can be set-up at a time the base of the second one (Q5) should be temporarily linked to the -15V rail to reduce the possibility of accidents. Set VR3 so that its value is 530 ohms. Note that if the positive lead of the ohmmeter is coupled to the -15V rail for this measurement the reading will not be compromised by the forward conduction of Q4. Set VR2 to the R6 end of its travel to ensure the minimum forward bias of Q4.

Set VR4 to its minimum setting and connect a milliammeter between the collector of Q4 and the 0V rail as shown in Fig. 10.8. As a safety precaution set the milliammeter to the 25mA range to start with. If the wiring up has been correctly carried out the milliammeter will show no reading when power is applied. On the other hand if the base of Q4 is incorrectly biased towards the positive region Q4 will pass a large current on switch-on which, besides possibly destroying the transistor, could also damage the meter.

Apply power and if no meter movement is observed reset to the 1mA range. Again there should be no obvious reading. Adjust VR2 towards the R5 end until the pointer of the meter makes a definite upward movement. At this point swing VR4 carefully over its full range and observe the maximum current drawn through Q4. The actual figure can vary quite widely at this stage and will probably be in the region 0.25-0.75mA.

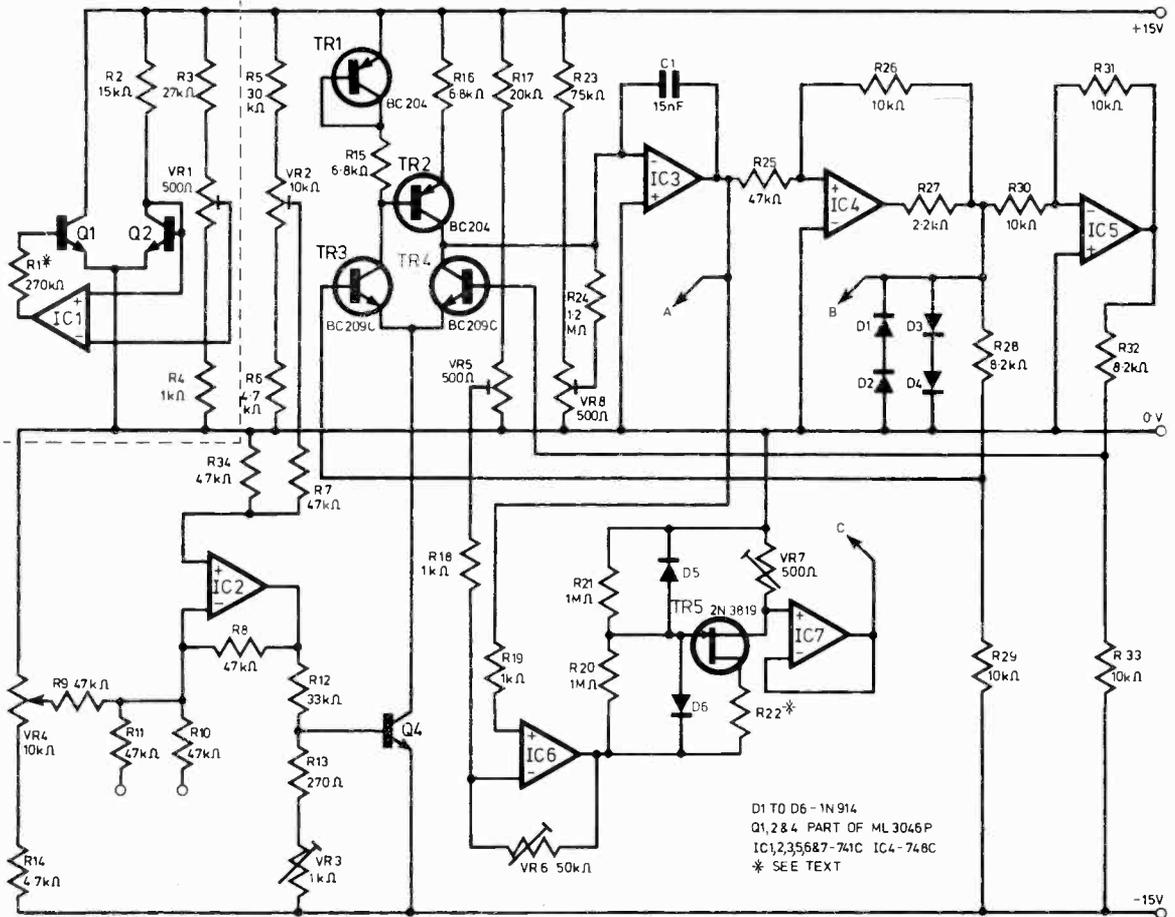


Fig. 10.6. Circuit of complete oscillator module. Points A, B and C are coupled to waveform selector switch

Set VR4 so that the meter is reading 0.2mA and place a slightly moistened finger on IC8—the transistor array. The meter reading should be seen to increase quite rapidly. Having made the above adjustments switch off and remove the meter from the collector circuit of Q4. Without disturbing the setting of any of the potentiometers temporarily link Q4 collector of the 0V rail. The same adjustments should now be made to the circuitry around Q5—having first removed the base/negative rail link.

In this case, however, leave the meter in circuit for the next stage of setting-up which entails fixing the thermal working points of the transistor oven.

Couple the oscilloscope to the output of the comparator IC1 which, at this point, will be about -14V. Carefully adjust VR1 until the comparator switches to +14V. At this time two things will start to happen. The first is that the meter will show a progressive increase in reading which, if the adjustment of VR1 has been made with care, should not exceed 1mA. The second is that within a second or so of the comparator switching positive the oscilloscope trace, which starts as a straight line, will begin to display a varying waveform.

At first the oscillation will zero about a point

approximately 12V positive, but, as the chip temperature stabilises, the zero point will move down to about +6V to +9V. Monitor the base emitter voltage of Q2 which should be in the region 650mV to 680mV.

LOW LOAD POINT

At this time all four connected transistors are contributing towards the heating on the chip. Q1 with its 470 kilohms base resistor will be passing about 3mA and contributing about 45mW, Q2 in passing 1mA will be contributing about 15mW whilst Q4 and Q5 will be contributing about 6mW jointly. These latter devices, however, are passing considerably more current than they will be required to do when coupled to their respective oscillators and running at high frequency. It is therefore necessary to establish a low load set point to ensure that the oven maintains the same temperature over the full working range of the oscillators.

On both Q4 and Q5 reduce VR4 to its setting and readjust VR2 hard over towards R6—in other words reduce the forward bias on the transistors to the absolute minimum. These adjustments will cause

VOLTAGE CONTROLLED OSCILLATORS

COMPONENTS . . .

LOGARITHMIC V.C.O.s. (2 required)

Resistors

- R1* 270k Ω (see text)
- R2* 15k Ω
- R3* 27k Ω
- R4* 1k Ω
- R5 30k Ω 2% metal oxide
- R6 4.7k Ω 2% metal oxide
- R7-R11 47k Ω (5 off) 2% metal oxide
- R12 33k Ω 2% metal oxide
- R13 270 Ω 2% metal oxide
- R14 4.7k Ω 2% metal oxide
- R15-R16 6.8k Ω 2% metal oxide
- R17 20k Ω
- R18-R19 1k Ω (2 off)
- R20-R21 1M Ω (2 off)
- R22 See text
- R23 75k Ω
- R24 1.2M Ω
- R25 47k Ω 2% metal oxide
- R26 75k Ω 2% metal oxide
- R27 2.2k Ω
- R28 8.2k Ω
- R29-R31 10k Ω (3 off)
- R32 8.2k Ω
- R33 10k Ω
- R34 47k Ω 2% metal oxide

Capacitor

- C1 15nF

Potentiometers

- VR1* 500 Ω cermet preset
- VR2 10k Ω cermet preset
- VR3 1k Ω cermet preset
- VR4 10k Ω midjet moulded carbon
- VR5 500 Ω cermet preset
- VR6 50k Ω cermet preset
- VR7 500 Ω cermet preset (see text)
- VR8 500 Ω cermet preset

Integrated Circuits

- IC1* 741C
- IC2, IC3, IC5, IC6, IC7 741C (5 off)
- IC8* ML3046P (Q1, Q2, Q4, Q5)
- IC4 748C


Transistors

- TR1-TR2 BC204 (2 off)
- TR3-TR4 BC209C (2 off)
- TR5 2N3819

Diodes

- D1-D6 IN914 (6 off)

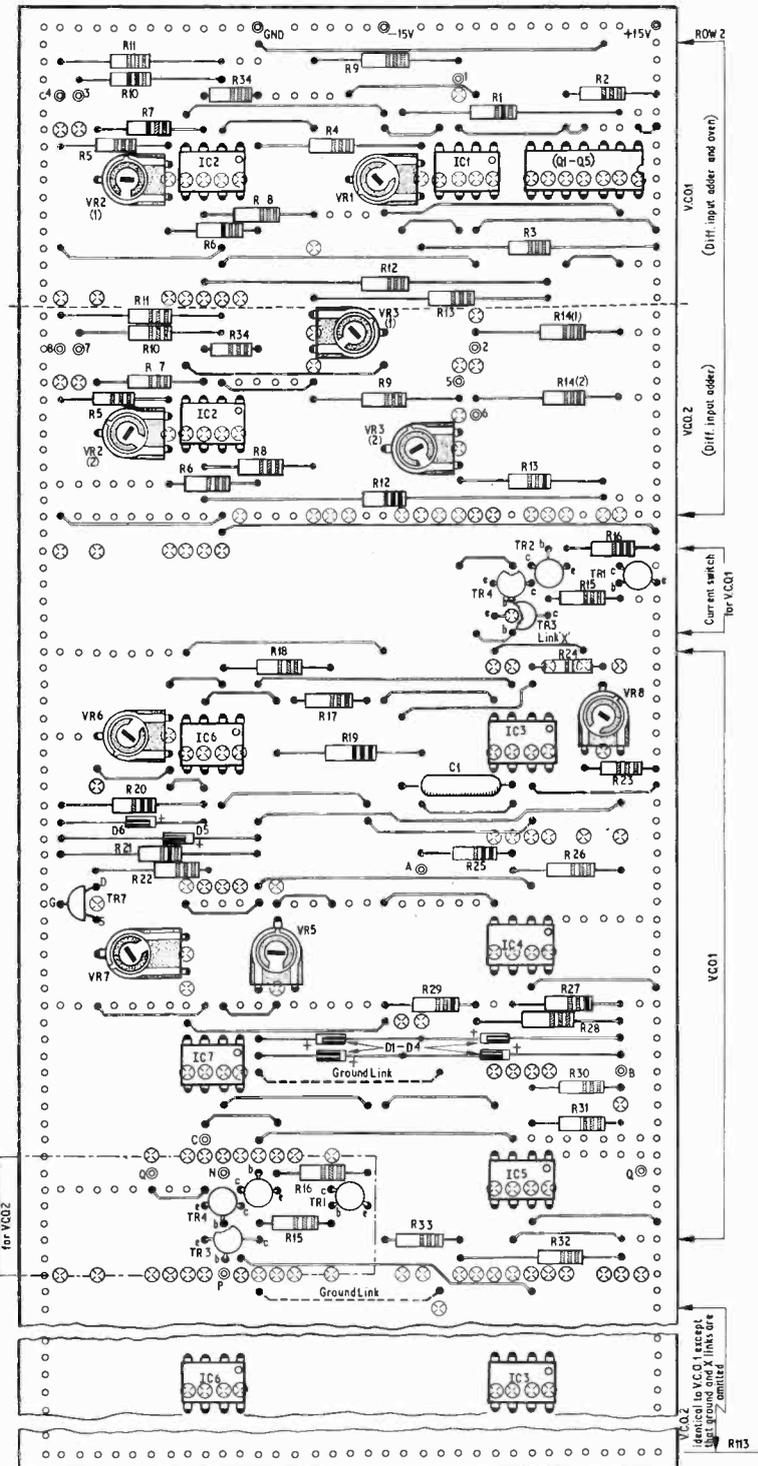Note: For components marked with an asterisk only 1 off is required.




1. Slider VR4 (1)
2. Hi-end VR4 (1)
3. R10 Control Input (1)
4. Spare Control Input (1)
5. Slider VR4 (2)
6. Hi-end VR4 (2)
7. R10 Control Input (2)
8. Spare Control Input (2)

Fig. 10.7. Board layout of oscillator module. Link point Q to Q. Link point N to junction of R33 and R33 or V.C.O.2. Link point P to junction of R28 and R29 on V.C.O.2

the oven temperature to fall and thus the comparator switching waveform will tend to move more positive and revert to a straight line trace.

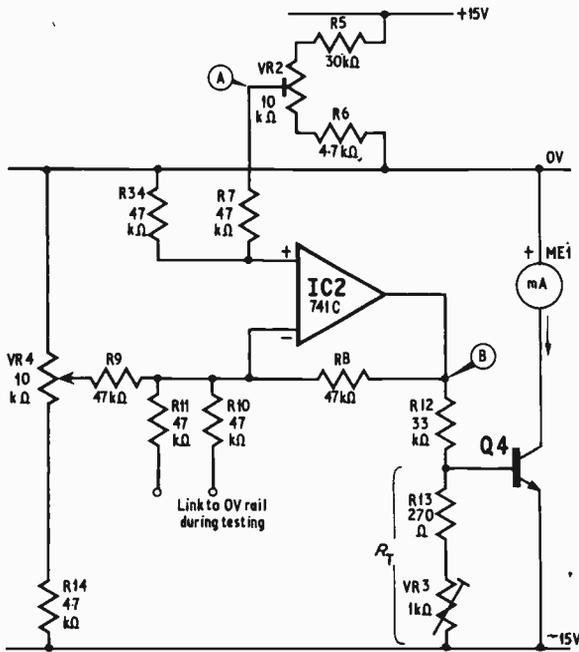Monitor the base/emitter voltage of Q2 again which, with the comparator positive, should not be greater than 680mV. If it is, or if, after a few seconds, the comparator waveform does not show signs of rippling, then the heat dissipation of Q1 is insufficient to maintain the set temperature. Much,



$$V_{BE} Q2 = 680\text{mV}; R_T = 750\Omega$$

Bias Voltage "A"	Total Voltage "B" Bias + Control	I _c	V _{BE} (Q4) (mV)
2.74	2.74	12nA (calc)	395
2.74	5.75	160nA	461
2.74	7.76	600nA	500
2.74	8.76	1.5μA	528
2.74	9.76	3.7μA	550
2.74	10.78	7.0μA	570
2.74	11.78	20.0μA	595
2.74	12.78	41.0μA	617
2.74	14.39	60.0μA	630
Referred to 0V Rail			Referred to -15V Rail

Fig. 10.8. Measurements of Q4V_{be} made with Avo 8 which illustrate the degree of error that is possible when interpreting the reading

of course, depends upon the ambient conditions when these measurements are being made and it is best to set up the low load point at the coolest temperature at which the v.c.o. is likely to be operated.

Under cool conditions therefore, if the comparator still does not ripple, it will be necessary to adjust the value of R1 to increase the current through Q1. In the prototype a value of 270 kilohms proved to be satisfactory and gave the desired comparator switching waveform at low load. The value of R1 is quite important because if it is too low the current switched by Q1 will be excessive and cause a considerable degree of jitter on the oscillator waveform.

Monitor Q2V_{be} once more and adjust VR1 as necessary to bring the voltage to 680mV. All setting-up on the prototype oscillator was carried out at this value and it is important to bear in mind that the values of all subsequent measurements bear a close relation to this figure. If Q2V_{be} is lower than 680mV this implies that the temperature of the oven is higher and thus Q4 will pass a higher current for any given value of control voltage. Since the frequency of the oscillator is linearly related to the current through Q4 then the frequency will also be higher.

The reverse will occur if the value of Q2V_{be} is higher than the specified figure. However, for small variations from the specified value, the performance of the oscillator will still remain wholly logarithmic and sufficient tolerance has been allowed in the biasing control VR2 to compensate for such variations. Once satisfied that the upper and lower temperature set points have been correctly established VR1 may be locked with a small dab of non-conductive adhesive such as Araldite. Link the bases of Q4 and Q5 temporarily to the -15V rail.

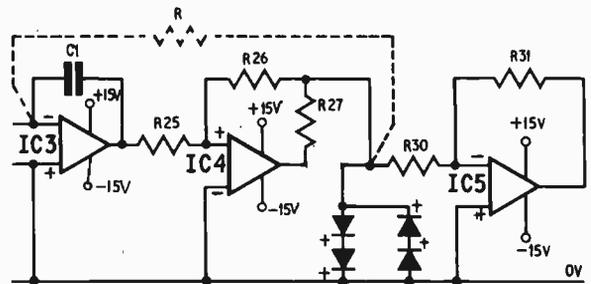


Fig. 10.9. Basic circuit elements of the oscillator and inverter (IC5). Resistor R is any value between 2kΩ and 1MΩ and is temporarily coupled as shown to prove oscillator function

PROVING THE OSCILLATORS

Fig. 10.9 shows the circuit elements involved in the construction of the oscillator section. When these items have been assembled temporarily connect a resistor of between 2 kilohm and 1 megohm from the junction of R27/R30 and the inverting input of IC3. With an oscilloscope monitoring the output of IC3 apply power and a triangular waveform will be observed at a frequency dependent upon the value of linking resistor chosen. Having proved the functioning of the oscillator assemble one current switch and couple to a current generator having first removed its base shorting link. Resistors R28/29 and R32/33 should be added at this time. The purpose of these resistors is to establish a negative bias point for transistors TR3 and TR4 in the

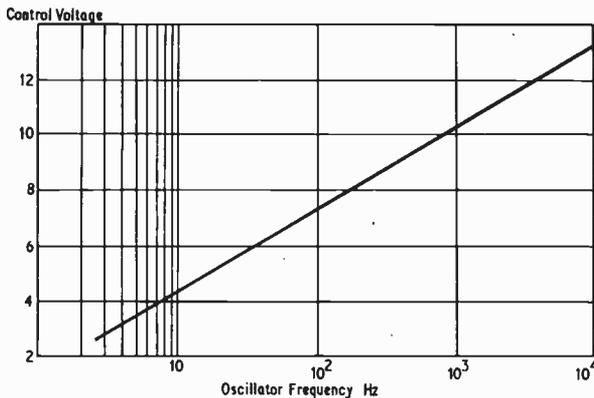


Fig. 10.10. Control voltage/frequency relationship

current switch and whereas the exact value of the resistors concerned is not entirely critical it is important that R28/32 and R29/33 be as closely matched as possible to ensure that the bias points of TR3 and TR4 are the same.

A quick check may now be made to ensure that the separate circuits work together as a complete unit. Remember to reset VR2 and VR4 to about mid position. Depending upon the setting of VR3 it is possible that rotation of VR4 will cause the oscillator to go into saturation towards either extremity but this is not important at this stage and will be dealt with during final setting up.

The next stage is to build the second oscillator following the same general pattern and, having established that it functions, begin the process of matching the performance. The closest possible matching of performance will be obtained if relatively close tolerance components have been used in the construction and, for this reason, 2 per cent resistors have been specified throughout. In particular it is prudent to obtain a matched pair of integrating capacitors (C1).

BIASING

Firstly it is necessary to establish a value of minimum bias on Q4 and Q5 which will support oscillation. Due to the inherently close electrical matching of the transistors on the 3046 the same level of bias will result in current flows through the transistors which are, for all practical purposes, identical. In the prototype it was found that the output of IC2 was at +2.74V referred to the OV rail for an oscillation frequency of 0.2Hz.

Set VR4 to its minimum position and adjust VR2 until the output voltage on IC2 (both oscillators) reaches +2.74V as above. Monitoring the integrator output waveform on both oscillators at the same time, if possible, adjust VR3 on Q4 and Q5 with the greatest care so that both oscillators are running at the same frequency—the exact rate is not critical. With VR4 still at its minimum setting apply an external control voltage to R10 on both oscillators at the same time having first broken the temporary link connecting R10 to the OV rail. A fresh 9V battery with a suitable potentiometer coupled across its terminals is ideal for the purpose of providing the control voltage.

Connect the positive end of the battery to the OV rail and the slider of the potentiometer to both R10's. With the slider hard negative monitor the

output frequencies of both oscillators, preferably at the same time, and confirm that they are running at the same frequency which should be in the region of 3kHz. Note that since the oscillators are not phase locked a certain degree of drift between them is almost inevitable and it should be the aim to reduce the amount of drift, by adjustment of VR3, to within 1 per cent or better of the frequency being monitored. Thus for a frequency of 3kHz a drift of about 30Hz would be at the limits of acceptability. Compare frequencies at various settings of the potentiometer to ensure that the frequencies and drift relationships remain stable over the full range.

OFFSETTING SATURATION

If, at the minimum setting, either or both oscillators go into saturation due to the adjustments made to VR3 it will be necessary to establish a slightly higher bias point by re-adjustment of VR2 and then repeat the whole of the setting up procedure so far outlined. Careful adjustment will result in a pair of oscillators which track the control voltages very accurately. It should not be the aim to reduce the drift between the oscillators to a very low figure as the beat frequency introduced by a drift of 0.5 per cent to 1 per cent will add interest and colour to the sound when both oscillators are being programmed in harmony. On the other hand a very low beat frequency can add quite unpleasant characteristics to a sound.

When satisfied that the oscillators are tracking over the full range of the control potentiometer the control voltage measured at the output of IC2 should be plotted against the frequency of oscillation at various points in the range. Fig. 10.10 shows the result of plotting the performance of the prototype oscillators.

F.E.T. CHARACTERISTICS

Before beginning the assembly of the sine shaper it is necessary to determine the exact characteristics of the f.e.t. which is to be used in the circuit. The two operational parameters which require to be known are the saturation current (I_{DSS}) at zero gate bias and the gate bias required to reduce the current through the device to negligible proportions. Fig. 10.11a/b illustrates the methods of making the measurements specified. If a variable voltage source

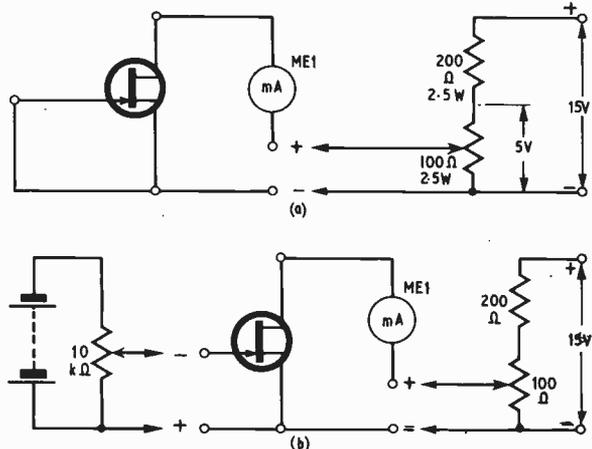


Fig. 10.11(a). Method for determining I_{DSS} at $V_{GS}=0$ (b) method for determining V_{GS} when $I_{DS}=0$

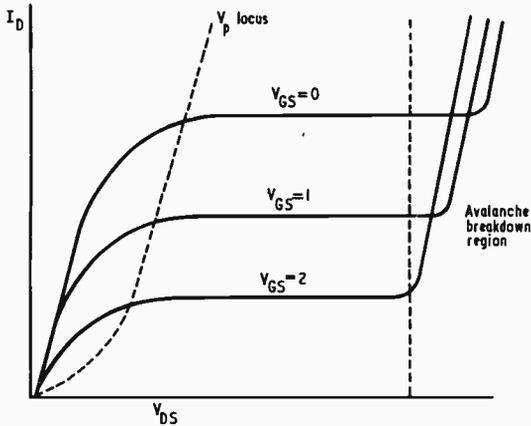


Fig. 10.12. Graph showing how V_p and I_{DSS} vary with V_{GS}

is available it is preferable to use this in the source drain circuit rather than the divider arrangement illustrated and thereby gain the benefit of greater accuracy in the measurements.

The first stage is to measure the I_{DSS} at zero gate bias. With the variable voltage source at zero volts and the milliammeter on the 1mA range gradually increase the voltage setting, plotting, at various stages, the current/voltage relationship.

The point which is of interest is that at which further increases in voltage result in only a very small increase in current through the device. The voltage at which this phenomenon first occurs is known as the pinch-off voltage (V_p) and should be carefully recorded. After the pinch-off point has been reached the voltage may be increased quite significantly with very little increase in current until the avalanche breakdown region is reached. At this point the current through the f.e.t. will increase hugely and almost instantaneously and result in the destruction of the device. Hence the requirement to plot the measurements very carefully and note the point at which V_p is reached.

Fig. 10.12 shows a typical family of curves for any one f.e.t. and depicts the way in which the pinch-off voltage reduces as the gate bias is made progressively more negative with respect to the source. The next measurement to make therefore is the point at which the current through the f.e.t. reduces to negligible proportions and the set-up for doing this is illustrated in Fig. 10.11b. Having made the connections shown and with the 10 kilohm potentiometer wiper at the positive end of its travel adjust the variable voltage source so that the meter is indicating the I_{DSS} . At this point gradually advance the wiper and note that the meter reading reduces in proportion. Switch to a lower range on the meter as required and advance until the reading is zero. At this point carefully measure and note the voltage across the gate/source of the f.e.t.

The value of resistor R22 in the sine shaper is calculated on the basis of the readings above in the following way:—

$$R22 = \frac{V_p}{2.I_{DSS}}$$

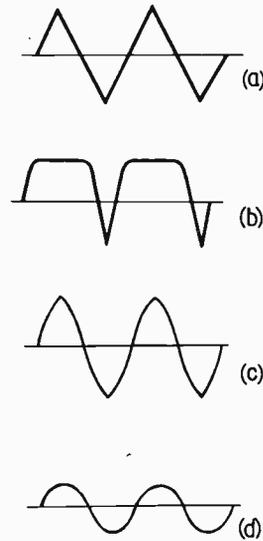


Fig. 10.13. Showing the effect on the sine shaper output waveform of adjustment of VR6 and VR7 (a), VR6 too low (b), VR6 too high (c), VR7 too high (d), VR7 too low

The V_p in the above calculation refers to the value of gate/source voltage at which the current through the f.e.t. is zero. The value of the resistor will depend on the actual characteristics of individual f.e.t.s but would normally be expected to be quite small. In the prototype, for example, R22 was 180 ohms in one shaper and 270 ohms in the other. The value of VR7 should be chosen to provide a fairly wide margin of adjustment over the calculated value of R22 and in most cases a 500 ohm preset would be satisfactory.

ASSEMBLY

Having completed the above measurements the sine shaper can now be assembled. Bear in mind that f.e.t.s can be rather tricky to handle and it is a wise precaution to solder all the other components in position before actually inserting and fixing the f.e.t.


Setting-up the sine shaper consists of adjusting the values of VR5, 6 and 7 to provide the optimum sine wave. With power on adjust VR4 so that the oscillator is running at about 3kHz and monitor the output of IC7. The preset adjustments should be made with reference to Fig. 10.13 which illustrates the various waveform characteristics associated with these controls.

If a sine-wave oscillator is available it is helpful to compare the output of the shaper with a "genuine" sine wave of the same frequency. The scale of the waveform on the oscilloscope screen should be as large as possible for this purpose. This latter procedure was carried out with the prototype shapers and resulted in a sine wave output having a total harmonic distortion of only 1 per cent. A wave analyser or distortion meter if available could enable a higher purity sine wave to be obtained.


Next month: Envelope shaper, mixer networks and analogue memories for the keyboard unit.

QUICKIES

WAA WAA


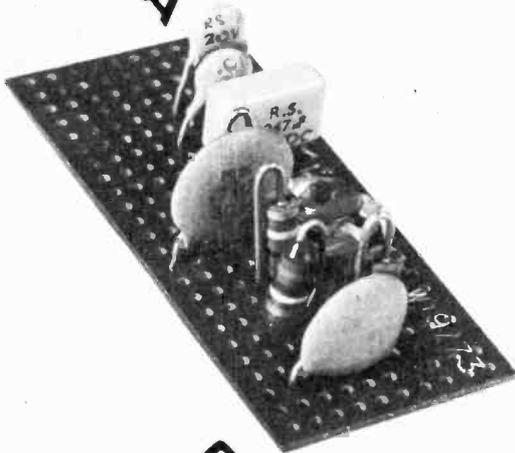


THERMOMETER

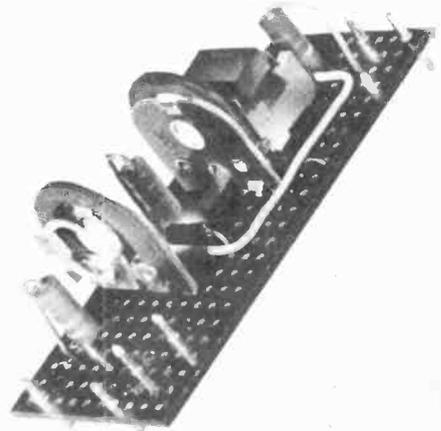

OPTOELECTRONICS

TOUCH SWITCH

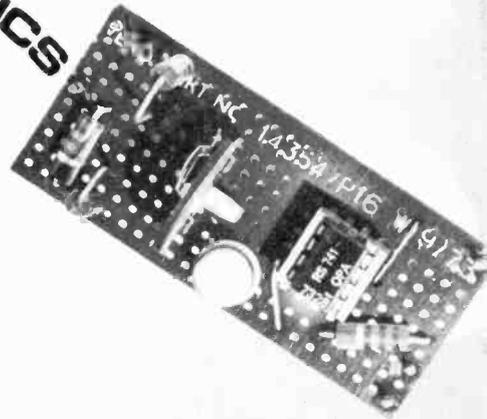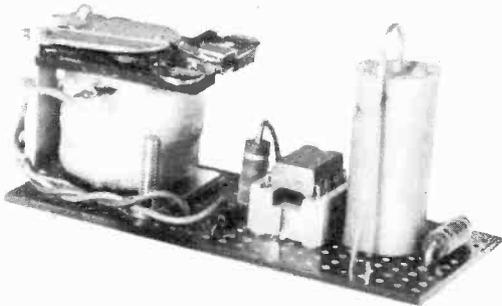


4 EASY-TO-BUILD PROJECTS FOR THE WINTER EVENINGS

THERMOMETER

A temperature measuring device
with many applications

HENRY'S RADIO 2/9/74.

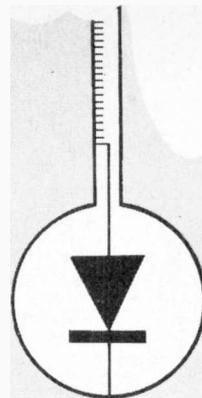

THE electronic thermometer has been proposed in various forms, usually associated with a thermistor detecting element. This latter is a resistor the value of which changes with changes in temperature, hence the name from thermal resistor.

However, whilst capable of providing an indication with fairly simple circuitry, this device is basically non-linear, the change in resistance for a given change in

temperature is not the same for all temperatures.

There is a much smaller and, in linearity terms, more accurate device readily available, the forward-biased semiconductor diode.

operating range of these diodes is quite sufficient for most applications.

Circuit

A number of alternative approaches offer themselves for use here. One could use the "bridge" method with the measuring diode set up in a bridge circuit and the amplifier looking at the bridge signal.

However, a simpler approach is to use the amplifier as a differential amplifier which can compare two input voltages, one due to the diode and the other variable in order to select the point at which the scale of the instrument starts.

Such a circuit is shown in Fig. 1, where the diode D1 is connected to vary the inverting input of the operational amplifier whilst the non-inverting input is set by the potentiometer VR1. The choice of inputs is required to give an increasing output voltage for

Diode Probe

It is admitted that the range over which a small silicon switching diode can be used in temperature terms is limited to the area which will not damage the device, namely from around -60°C to $+180^{\circ}\text{C}$. In addition, the variation of resistance and thus voltage across the diode is very small for a change in temperature of 1 degree C, in the region of 2.5 to 3.5mV.

Thus the change needs to be amplified in some way if it is to be useful.

The advent of cheap integrated circuit amplifiers has provided the answer to that problem and the

COMPONENTS . . .

Resistors

R1 22k Ω

R2 1.5k Ω

R3 1.5k Ω

All 10% $\frac{1}{4}\text{W}$ carbon

Potentiometers

VR1 10k Ω

VR2 22k Ω } skeleton presets

Diodes

D1 1N914 (or 1S914 or other silicon diode)

D2 BZY88 (5.6V) Zener diode

Integrated Circuit

IC1 741 Operational Amplifier

Miscellaneous


ME1 0-1mA Meter (see text)


Veroboard (free with this issue)

Total cost (excluding meter) about 95 pence.

Meters are available from about £2.50.

£3.45
approx.

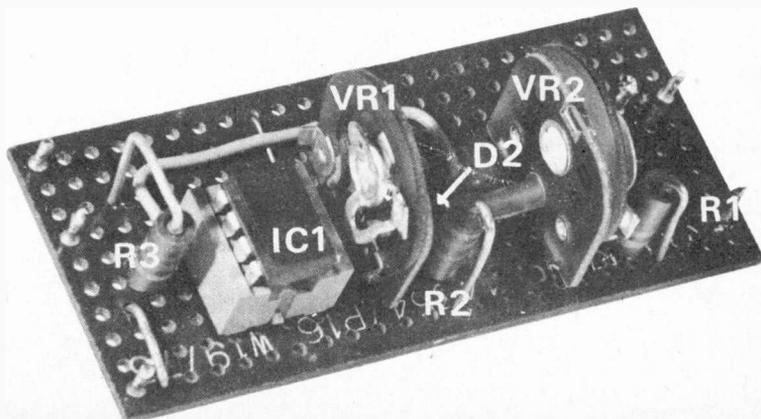

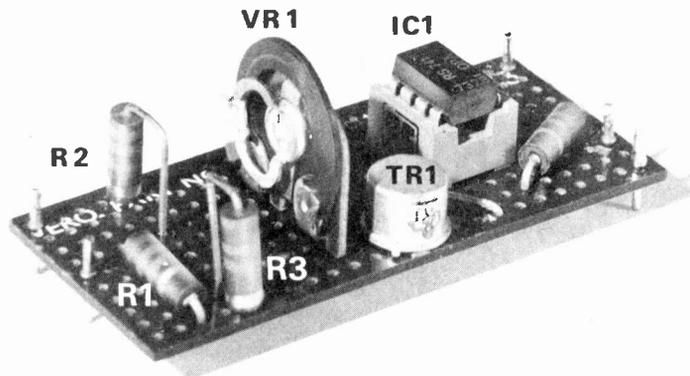

or its holder if one is used as in the prototype, and one to separate the output from VR1.

As can be seen, pins have been used to bring out the battery, input and output connections but of course wiring may be connected directly to the board if desired

Applications


A circuit of this type can be used anywhere it is necessary to measure and control as a result of light variation. A side light control for a car is a typical idea. Other automotive applications include

light actuation of a garage door, car light failure alarm and perhaps even a burglar alarm.

Similarly in the home there are many applications starting off with things like a burglar alarm, light switches to turn house illumination on after dusk both for convenience and security and the like.

In technical areas devices of this sort can be used as object counters on a production line, as end-stops for limiting machine travel, as automatic door openers and so on.

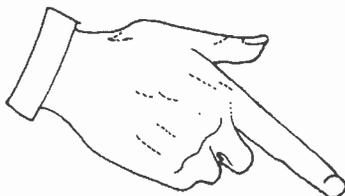Dependent on the light resistor used the equipment will be sensitive to slightly different areas of the visible light spectrum but for normal visible light work most types will suffice including the well-known ORP 12 and its brothers from Mullard. ★



TOUCH SWITCH

Multi-purpose switching by touch alone

THE touch switch has many household, commercial and industrial applications. Specific examples in each area are intrusion alarms, opening supermarket doors and safety devices for machine operators.

In principle, simply touching a wire or metal plate will cause a relay to operate. To fulfil this the intermediary circuitry must be sufficiently sensitive to detect the very small noise currents provided by the hand.

Timer Chip

Touch switch circuits usually consist of cascaded amplifier stages (f.e.t. or bipolar). Construc-

tion of these for a beginner can be irksome and the results disappointing through spurious triggering, a common condition with these circuits

A convenient and economic package which can be simply adapted for this role is the Signetics 555 timer integrated circuit. Although this is usually used to provide accurate delay periods from microseconds to hours it will suit our purpose to use this facility to provide a variable period latch for the relay.

Input sensitivity is extremely high and the chip has a useful relay drive capability so that any relay coil operating in the 6-9V range and up to 200mA.

Simple Circuit

The first thing that one notices in looking at the circuit of Fig. 1 is its simplicity and economy in parts which makes for easy construction.

Since the internal functioning of the 555 was more than adequately covered in the June 1973 issue it will suffice to say that the circuit operates as a sensitive monostable.

In the quiescent state, that is with no hand applied to the touch plate or wire, battery drain is about 7mA none of this being taken by the relay. When a hand is applied the relay coil current flows and the contacts close for a period determined by the timing constants R1 and C1.

For the component values shown the time is around 3 seconds but longer delay periods can be achieved by increasing the value of C1. With the resistor given delay periods in seconds for a particular capacitor can be approximated by the simple equation $t = 9C_1$ where C_1 is in microfarads. For a delay of an hour you would, for example, need a $400\mu\text{F}$ capacitor but leakage would no doubt affect this estimate. A practical limit for very long delays would be about $10,000\mu\text{F}$.

Triggering

The current required at pin 2 to activate the circuit need only be half a microamp which indicates the extreme sensitivity. Unfortunately this can create problems of backlash triggering particularly with inductive loads. This is obviated by the inclusion of R2

The transient suppressing diode protecting the chip can in fact be any switching diode.

Touch Off

There are times when a touch on/touch off switching facility might be required as with say, a bedside night light. For this do

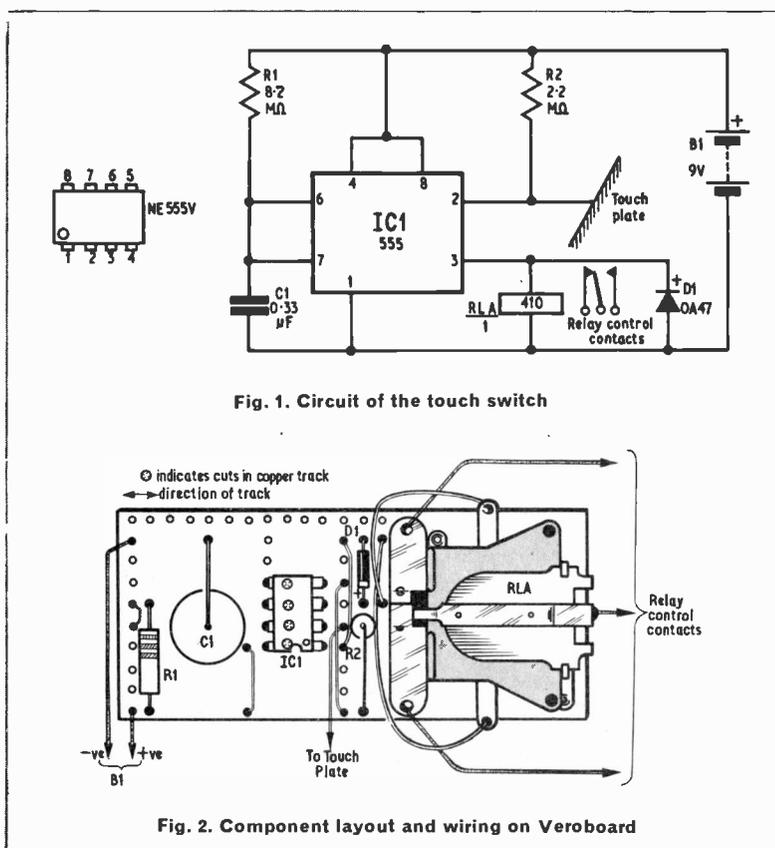


Fig. 1. Circuit of the touch switch

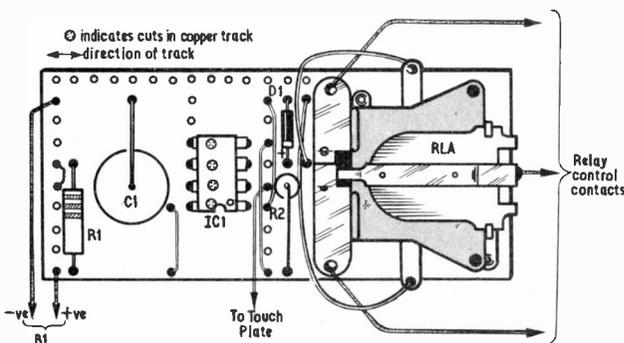


Fig. 2. Component layout and wiring on Veroboard

not connect pin 4 to the supply line but to another touch plate. A simple method of providing two adjacent touch plates is to join equal numbers of copper strips on a largish piece of Veroboard and simply wiring each "plate" to the appropriate 555 pin.


The 8 pin d.i.p. socket was included as it simplifies any future need to remove the chip either through damage or for use in another project

Other Relays

The delay periods provided by the timing component are almost independent of supply voltage. Since the 555 can be operated between 4.5 and 16V the supply rail can be lifted to accommodate other relay drive requirements but this should not exceed 16V and 200mA. ★

Construction

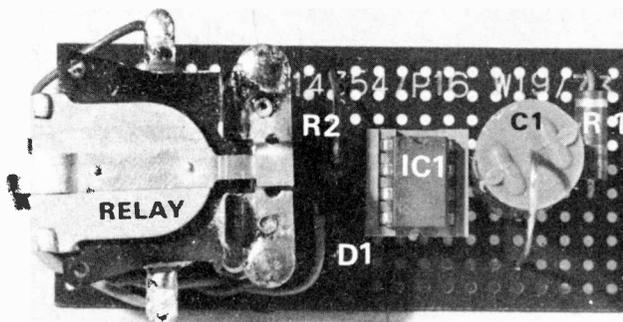The components are easily mounted on the sample Veroboard as in Fig. 2. Cuts to be made in the copper underside are also clearly shown.



COMPONENTS . . .

Resistors

- R1 8.2MΩ
- R2 2.2MΩ
- All 10% ½ watt carbon

Capacitors

- C1 0.33μF polyester (see text)

Integrated Circuit

- IC1 NE555V (Signetics)

Diode

- D1 OA47


Relay

- RLA 6V 410Ω coil (type 912 R.S.)


Miscellaneous

- Veroboard (free with this issue), 9V battery


£2 approx.

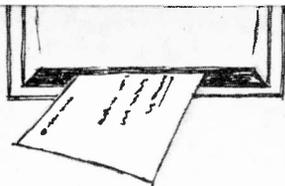

AUTOMATED MAIL

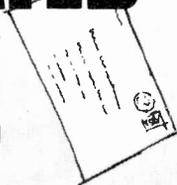

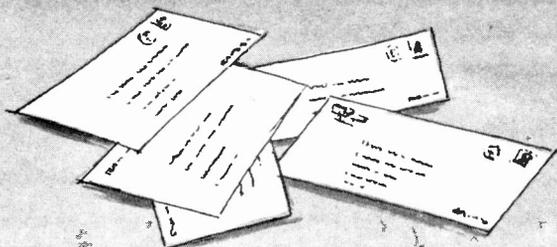By **F. J. MORRIS** B.Sc.(Eng.), A.C.G.I.



RAPID, often startling, developments which have been made in the field of telecommunications owe much to the application of electronics. But electronics are, of course, contributing to the advance of other forms of human communication. Take, for example, one of the most traditional communications systems of all—the letter post. Electronics have an essential role in the multi-million pound plans to automate Britain's postal service.

THE NEED FOR AUTOMATION

The need to automate the postal service is imperative for two major reasons. First, to reduce the service's dependence on manpower (75 per cent of all Britain's postal costs are for labour) and secondly to maintain traditionally high standards while meeting the demands of today's fast moving world.

Since each of the 35 million letters the Post Office handles every working day in this country may have to be sorted up to eight times during its journey there is clearly ample scope for mechanisation and, helped by electronics, much has already been achieved. Electronics systems are enabling machines to select, stack and sort letters automatically at speeds far higher than even the most skilful postman-sorter.

The key to automation is the British postcode system, of its kind the most advanced in the world. Postcodes have been developed as the answer, or at least a supremely effective compromise, to the so far insuperable problem of total automation through machine-read addresses. Research is progressing but apart from the obvious difficulties with machine-reading of handwritten addresses it will still be many years before even typescript addresses can be read reliably without unreasonable restrictions on inks or type faces.

The postcode, however, by expressing an address in a machine language, easily keyed and translatable electronically, enables a high degree of automatic sorting to be introduced with present technology.

THE PRESENT SITUATION

Fully mechanised sorting offices are now operating at 12 centres in Britain and the eventual total will be around 100. Progress and the eventual success of the system depend on two factors—the completion of the programme to give each of Britain's 20 million addresses its own postcode; and the subsequent use of the postcodes by the public. In fact, postcoding of the country will be completed by August this year and while use of existing postcodes is rising steadily the importance of maximum use will become clear from the remainder of this article.

THE POSTCODE

The postcode is familiar to most people but the reasoning behind its planning and form is not so widely known and its explanation is appropriate here.

In fact the principle is simple. Each code consists of between five and seven alpha-numerical characters. The first one or two alphabetic characters in the code refer to one of 121 main towns or code centres in the UK (e.g. S for Sheffield, IP for Ipswich, LS for Leeds). A number following the alphabetic characters in the first or "outward" part of the code represents a sub-division of the area (e.g. IP3, IP7, IP17). These districts are geographic units similar in concept to the familiar London postal districts, such as SE1.

Each district is sub-divided into smaller areas or sectors which are again geographic units, represented by the first character or "inward" part of the postcode (e.g. IP3 9--, LS8 5--, etc.). Finally, the last two characters of the postcode give information about a street, part of a street, or, in the case of larger firms, a single address.

Thus a complete code in the case of part of a street in Ipswich for example reads IP3 7PS with the final two letters, PS, pinpointing that part of the street—usually between 15 and 20 addresses.

INITIAL SORTING

During initial sortation specially trained operators at postcoding desks equipped with electronic keyboards read each code and print onto the envelopes a series of code marks. The complete code is translated into a pattern of up to 28 marks and printed in two rows of 14. The code marks are virtually invisible to the naked eye but glow blue under ultra-violet exposure (see Fig. 1). The glow remains for a time after the ultra-violet light has been removed and this after-glow is detected by a photo-multiplier tube and the pattern recovered.

The pattern is next translated electronically to decide into which of 144 sorting boxes the letter is to be deposited by the machine. Once the postcode has been transcribed at the coding desk repeated exposure of the code marks and subsequent reading allow fully automatic sorting of the letter during its journey until it reaches the postman who is to take it on his delivery round.

FOUR PROCESSES

While looking in closer detail at the electronics behind the coding desk and the automatic sorting machine it is necessary to follow in sequence the

*Post Office Mechanisation Branch

four processes which a letter goes through from being received in the sorting office and being slotted automatically into its sorting box on the machine. The first two processes—segregation and facing—are preparatory to the final two—coding and sorting.

When letters arrive in a fully mechanised sorting office those which can be handled by automatic sorting machinery must be segregated from those which cannot. A wide assortment of letter shapes and sizes are found in every mail collection and those that are too unwieldy or thick must be culled from the letter stream before being allowed to pass into and possibly jam, or severely damage, the automatic sorting equipment.

The letters pass through a series of ingenious processes—rotating slatted drums, tilted conveyor belts, spaced rollers—which between them allow the unsuitably sized letters to slip from, or be plucked out of the stream, collected and then sorted by hand. The remaining letters are stacked automatically and passed to the next machine—the automatic letter facer (ALF). This is the first of the automatic sorting stages to employ electronics (see Fig. 2).

AUTOMATIC LETTER FACER (ALF)

The job of ALF is to arrange the letters so that they face the same way (the stamp upwards) preparatory to the stamps being postmarked or cancelled. Additionally ALF separates First and Second class letters so that the former may be sorted later.

While the operation of letter sorting machinery relies on the glow picked up from the code-marks printed onto the envelopes at the coding desk, ALF relies on a similar glow effect but obtained from the stamps themselves. Each stamp is surfaced with bars of phosphorescent material. The number of bars differ according to the value of the stamp. This enables the machine to detect if a stamp is present on the envelope, its position and whether the letter is being sent First or Second class.

ALF first strips letters off the feed stack and accelerates them along a series of rollers to obtain a stream of letters with a small gap between each one. The letters then pass under the first of two arrays of ultra-violet (UV) lamps which causes the phosphor on the stamps to glow. The glow continues after the letter has left the UV section and passes under two photo-multiplier tubes.

One of the tubes scans the top section of the letter face (which was exposed to the UV) and the other tube looks at the bottom of the face. In the dark only a tiny current flows in the multiplier but the glow from a UV "excited" stamp boosts the current.

The change in the current is detected and if a stamp is "seen" at either end of the letter face the letter is allowed to pass on. If no glow is picked up ALF assumes that the letter is facing the wrong way up and routes the letter through a twisted belt section to turn the letter over.

Now, all facing the same way, the letters pass under a second series of UV lamps and photomultiplier tubes. This time the number of phosphor bars on the stamps are noted and the letters identified as First or Second Class. At this stage, also, underpaid letters and those bearing no stamps are spotted.

ALF actually sorts letters into five boxes (cancelling their stamps on the way) of which two are for First Class, two for Second Class and the fifth for underpaid letters. Pairs of boxes are needed so

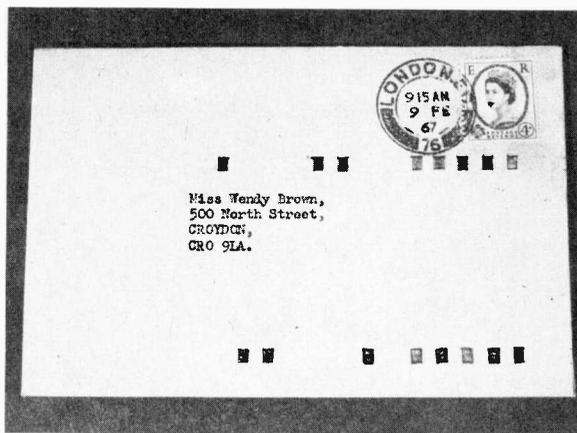


Fig. 1. A typical postcode pattern. The dots imprinted at the coding desk are normally almost invisible to the naked eye and have been outlined here

that letters with stamps in the leading position can be separated from those with stamps in the trailing position. The operator who unloads ALF correctly combines these two stacks before passing them to the next stage, the postcoding desk.

CODING DESK

The Coding Desk, with the help of an operator, provides each letter with its pattern of UV sensitive marks translated from the postcode. Where letters do not carry a postcode the operators imprint a code giving the post-town destination of the letter which enables initial automatic sorting to go ahead. But without the complete information which the correct postcode provides these letters must pass through a second coding desk to identify the delivery street

Fig. 2. Inside an automatic letter facing machine (ALF) which arranges letters so that they face the same way and the correct way up in the sorting office. ALF also separates first and second class mail and cancels the stamps, dealing with up to 20,000 items of mail an hour

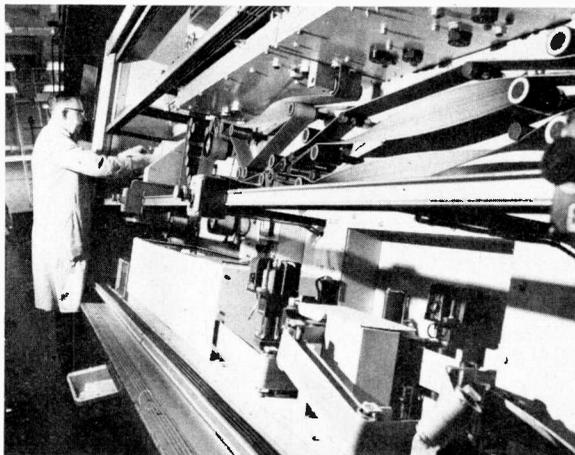


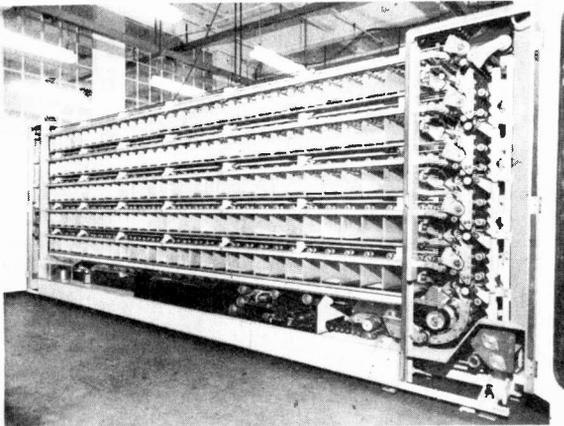


Fig. 3. Letters passing through a postcoding desk operated by a specially trained postman

when they arrive at the delivery sorting office. The full potential of the postcode is therefore missed and hence the importance of using the postcode wherever it is known.

The coding desk presents each letter at a display "window" facing the operator who is seated at a keyboard (see Fig. 3). The operator, who is a specially trained postman, types out the postcode on his keyboard which converts each character into a different pattern of binary signals on six wires.

Fig. 4. A medium speed Letter Sorting Machine with 144 selection boxes. These automatic machines read the first half of the postcode and sort the letters to their office of destination. At this office coded letters are again automatically sorted by machines which read the second half of the code and sort for the appropriate delivery postman



ELECTRONIC TRANSLATOR

The signals from each coding desk keyboard are sent to an electronic translator which contains a memory store of the patterns sent out from the keyboards. The translator recognises when the operator has completed a postcode and converts it into a pattern of 28 binary digits (bits). This 28 bit answer is then transmitted to the coding desk. Once this answer is received the coded letter is moved on to the print position.

Because the code marks are indelible the letter is held for a time in a cancel position so that the operator has time to correct any mistake before the irrevocable printing step is taken.

The information received by the translator on the code pattern to be printed applies to the letter held in the "cancel" position and must be remembered until the letter is printed. Thus two translations must be stored in the desk and kept in synchronisation as the letters pass through. From being first presented in the display window to printing the average time the letter spends in the coding desk is two seconds.

After printing, the letter is ejected and collected and stacked automatically before being passed through the sorting machine. (In delivery offices post-coded letters arriving from other offices have already been through the coding desk stage at the previous office and are simply sorted automatically down to street or single address level. Here the last part, or "inward" code is used).

THE LETTER SORTING MACHINE

Like the coding desk and ALF the sorting machine (see Fig. 4) is fed letters in stacks and has first to separate them into a stream of spaced letters. They are then passed under UV lamps to generate the glow from the imprinted code-marks which are detected by the code-mark reader.

In the reader the row of marks on the letter pass a narrow slot behind which is a photo-multiplier tube which "recognises" each mark it sees by the increased current caused in the tube. The coded marks are read and stored in the sorting machine's memory. The code is fed into a second electronic translator which returns a 15-bit pattern identifying the box to which the letter should be routed.

ROTATION

The machine continues to store the translation and passes it on in stages for every two inches of letter travel. About three feet after passing the code-reader the letter is rotated through 90 degrees to travel the remainder of the machine with its longest edge forwards.

Just before the right-angle rotation a photo-electric beam is broken to give an exact positional reference of the letter within the machine. The original code-mark translation continues to be passed on its stages while the machine keeps track of the letter. When it arrives at the appropriate sorting box the box is opened and the letter has been sorted.

If the sorting machine is being used for outward mail (that is letters which are to go on to another sorting office) the letters are taken from the boxes, bundled and sent on by road or rail in the normal way. If the machine is sorting letters which are to

be delivered in the sorting office area (inward mail) the letters are taken from the boxes and prepared for actual delivery by the postman on his round.

SYNCHRONISATION

All three of the machines described in this article, ALF, the coding desk and the sorting machine, must perform the required operation on each letter passing through the machine at the correct relative time.

To achieve this on the sorting machine and ALF it is necessary to pick up a signal to keep the electronics in synchronisation with the machine and hence the letters moving through it. This is achieved

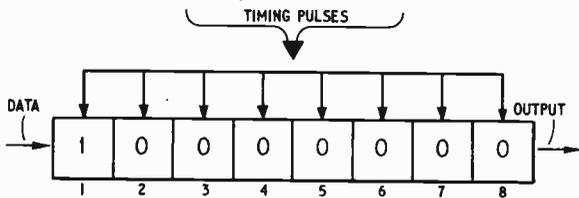


Fig. 5a. Diagrammatic representation of a shift register. The timing pulses cause the data held in each of the bistables to be shifted one place to the right

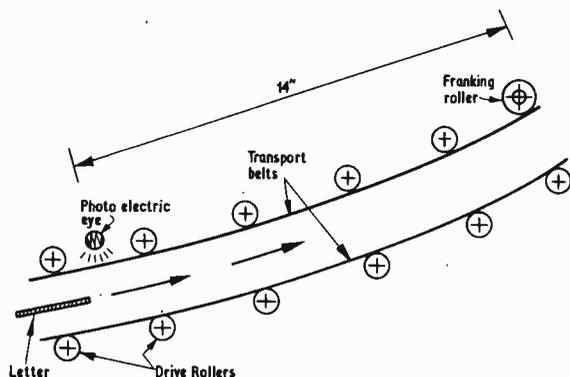


Fig. 5b. After eight shifts the letter will have reached the franking roller and a logic 1 in position 8 of the shift register causes the stamp to be cancelled

by shining a light beam through a series of holes drilled around the perimeter of a wheel driven by the machine's transport belts. A phototransistor is illuminated by the beam whenever a hole passes. The current changes in the phototransistor are detected and used to generate timing pulses which step data through electronic models of the machines and hence control the letter flow.

All the control functions of the machines follow a simple scheme. Somewhere on the machine some characteristic of the letter is inspected and the signals generated are converted to logic voltages. From this information a decision is taken as to which of a number of operations the letter should undergo. However the alternative operations may be carried out some distance down the machine and it is necessary to keep track of the letter and its data until the point of operation is reached.

SHIFT REGISTER

This letter tracking is achieved by storing the data in a shift register and moving it one place down the machine for each timing pulse received. Thus on the sorting machine and ALF each stage of the shift register represents information associated with a letter whose leading edge is in a particular 2in length of belt.

At some later stage on the machine, where the operation has to be carried out, the associated shift register stage can be looked at electronically to detect when the letter is present and then indicate the operation. The word carried down the shift register varies in complexity from a single bit on part of ALF indicating whether or not a letter has to be turned over, to the 15 bits identifying the sorting machine outlet.

The Shift Register has a vital role to play in postal machines; repeatedly information is collected some distance from the position where action is taken on it.

In simple terms, let the figure represent an 8 stage shift register which represents the occupancy of 16 inches of a machine's transport belts. When no letters are present all the stages of the shift register are at logic "0" (Fig. 5a). A photo-electric eye detects the leading edge of a letter and marks the first stage of the shift register at logic "1" so it now reads 100 000 00. Each timing pulse from the machine passes the information on stage down the register. So, after 7 pulses, stage 8 alone will be marked 000 000 01 if no more letters have entered this section of belt.

A logic circuit is used to detect stage 8 being switched to logic "1" and causes the franking roller (14 inches from the photoelectric eye) to operate, cancelling the stamp (Fig. 5b).

Shift registers can be made to carry much more information and this need not all be collected at the same time.

ELECTRONIC CIRCUITS

From the "job descriptions" of the machines involved in automated mail handling it is clear that they rely heavily on electronics for both machine timing control and data storage.

All the electronic circuits required are constructed from components soldered onto small plug-in printed circuit boards. The components used—silicon planar epitaxial diodes and transistors, metal oxide resistors and polystyrene capacitors—are all highly reliable. However reliable, of course, some failures are inevitable, in which case a new circuit can readily be inserted in exchange.

Many thousands of these circuits are in use by the Post Office throughout the country. Although more than a hundred different circuits have been developed for various tasks, perhaps a dozen commonly-used circuits form some 90 per cent of the total.

DIGITAL LOGIC

Most of these common circuits are digital logic circuits requiring inputs of either +6.6 volts (logic "0") or 0 volts (logic "1") and giving outputs at the same levels. Some of the circuits, however, have to interface between the logic system and the electro-magnetic devices used to control the machine. One

of these gives a logic output when the current in a phototransistor exceeds a certain level; another has to apply voltage to a load device (which could be a diverter or print pin solenoid) whenever its input is at 0 volts. However, not all circuits operate with logic levels at either input or output.

DOLLILOG

The range of logic circuits is often referred to as "Dollilog". This name derives from "Dollis Hill Logic" after the PO Research Station at Dollis Hill where the system was developed.

Some of the more common Dollilog circuits are described briefly in the following paragraphs together with some ideas on how they are used.

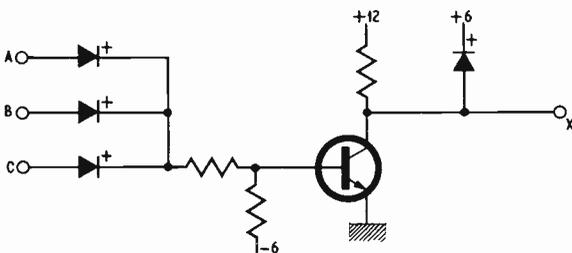


Fig. 6. Circuit diagram of a three input NAND gate used in the Dollilog system

NAND GATE

The diagram (Fig. 6) shows a three input NAND gate. The output (x) of this circuit will be at the logic "0" voltage (+6.6 volts) only if all three of the inputs (A, B and C) are at the logic "1" voltage (0 volts). In this case the transistor will be cut off.

If any one of the inputs is at the logic "0" voltage the transistor will be saturated and the output will be at the logic "1" voltage.

The NAND gate can be used to detect when several different conditions occur simultaneously and cause some process to be carried out.

Other logic circuits are used, one of which only gives the logic "1" output voltage when all three inputs are at logic "0", this being a NOR gate. Another circuit gives a logic "1" if both inputs are the same.

SCHMITT TRIGGER

The Schmitt trigger has two outputs which are never the same. The outputs states interchange whenever an input voltage exceeds one threshold or falls below another.

POWER AMPLIFIER

The power amplifier's output transistor will be saturated whenever the input to the circuit is at logic "1". The usual circuit can control loads of up to 25 watts although other high power versions exist.

BISTABLE MULTIVIBRATOR

The bistable multivibrator is another circuit which has two outputs which are always opposite. The outputs are switched by pulses applied to "set" and "reset" inputs. Bistables can be used to store information.

SHIFT REGISTER

Shift registers are arrays of bistables with a common clock input which can be pulsed to step data along the register.

NEW TECHNOLOGY

To some readers, these circuits will look a little dated. To some extent this is true; it must be remembered, however, that the system has proved satisfactory in use. The Post Office has to consider any change on this scale very seriously. Various factors have to be considered such as replacement cost, the cost of training maintenance engineers in any new system and the compatibility of any new equipment with the old.

At present, many new techniques are being tried and tested. The coding desk keyboard contains a number of DTL integrated circuits while the new memory which will replace the sorting machine's original mechanical memory is being developed using MOS integrated circuits. A new translator uses small general purpose computers rather than specially built electronic circuits. At present, however, only the relatively cheap keyboard, where size is critical, uses integrated circuits in a production item.



EE POINTS THE WAY

IN THE NOVEMBER ISSUE — AN 8 PAGE SUPPLEMENT

on constructional methods. Shows how circuits can be built on various types of circuit board, etc.

Using the supplement as an introduction almost anyone can build any of the featured projects:

★ **4 Band T.R.F. Receiver**—covers three short wavebands plus the normal medium wave—easy to build using ready wound coils throughout.

★ **Gas Alarm**—simple detector and alarm for combustible gases and vapours and smoke.

★ **Three By Three Game**—a novel game for two players.

EVERYDAY ELECTRONICS the companion magazine to *PRACTICAL ELECTRONICS*. November issue on sale **Friday, October 19** — order your copy now.

The Sinclair Cambridge... no other calculator is so powerful and so compact.

Complete kit-£24.95! (PLUS VAT)

The Cambridge – new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price – and by building it yourself you can save a further £5.50!

Truly pocket-sized

With all its calculating capability, the Cambridge still measures just $4\frac{1}{2}'' \times 2'' \times \frac{1}{8}''$. That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

Easy to assemble

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

The cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 – so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.



Features of the Sinclair Cambridge


- * Uniquely handy package. $4\frac{1}{2}'' \times 2'' \times \frac{1}{8}''$, weight $3\frac{1}{2}$ oz.
- * Standard keyboard. All you need for complex calculations.
- * Clear-last-entry feature.
- * Fully-floating decimal point.
- * Algebraic logic.
- * Four operators (+, -, x, ÷), with constant on all four.
- * Constant acts as last entry in a calculation.
- * Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- * Calculates to 8 significant digits, with exponent range from 10^{-20} to 10^{79} .
- * Clear, bright 8-digit display.
- * Operates for weeks on four U16-type batteries. (MN 2400 recommended.)

A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

Contents:

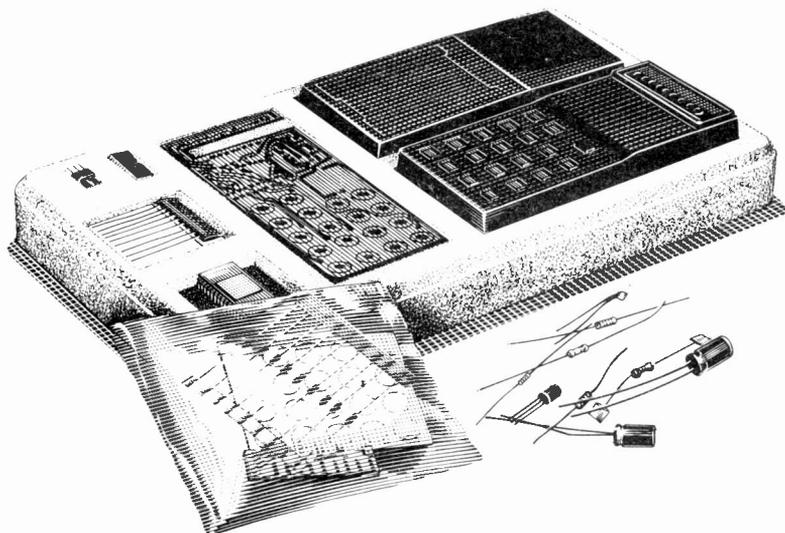
1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.



This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

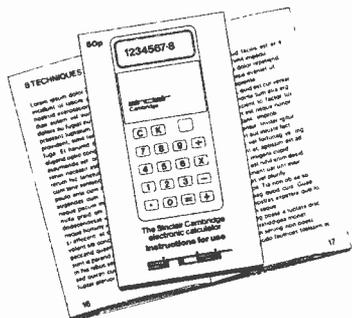But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations like:

- Logs Sines Cosines
- Tangents Reciprocals nth roots
- Currency Compound
- conversion interest
- and many others...

sinclair

Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire
Reg. no : 699483 England
VAT Reg. no : 213 8170 88

Why only Sinclair can make you this offer

The reason's simple : only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology. And *you* benefit!

Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

Price in kit form : £24.95 + £2.50 VAT. (Total : £27.45)
Price fully built : £29.95 + £3.00 VAT. (Total : £32.95)

PE/11/73

To : Sinclair Radionics Ltd, London Road,
St Ives, Huntingdonshire, PE17 4HJ

Please send me

a Sinclair Cambridge calculator kit at
£24.95 + £2.50 VAT (Total : £27.45)

a Sinclair Cambridge calculator ready
built at £29.95 + £3.00 VAT
(Total : £32.95)

*I enclose cheque for £ _____, made
out to Sinclair Radionics Ltd, and
crossed.

*Please debit my *Barclaycard/Access
account. Account number _____

*Delete as required.

Name _____

Address _____

PLEASE PRINT

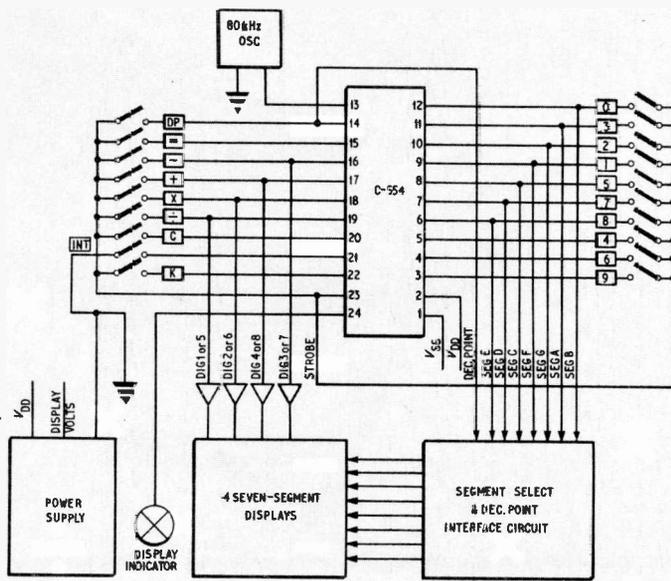


Fig. 1. Block diagram of a four digit calculator using the C554 integrated circuit

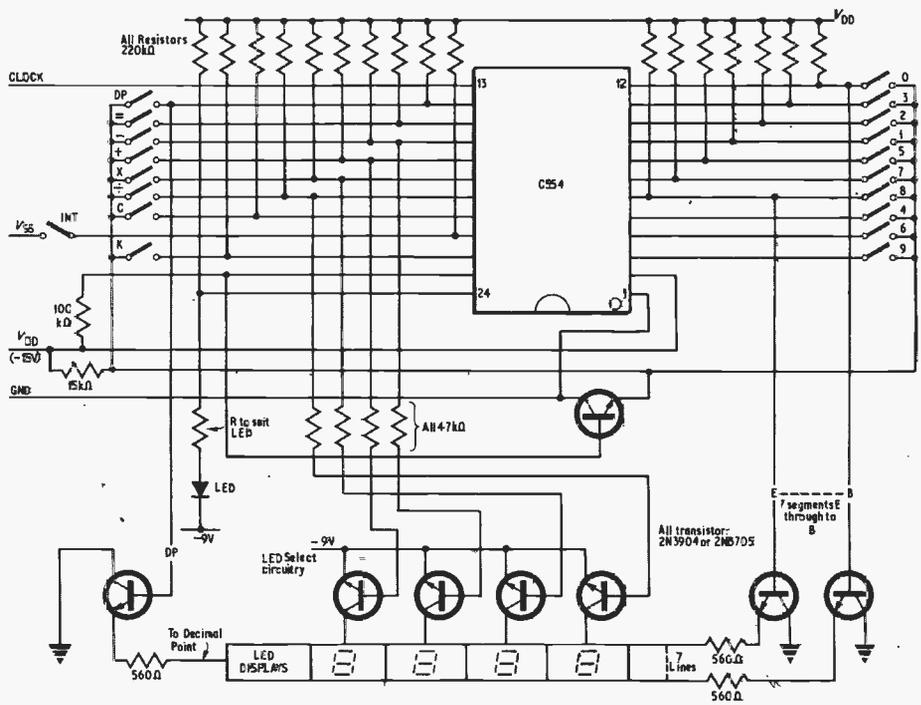


Fig. 2. A more complete circuit diagram showing l.e.d. seven segment display with all the necessary driver transistors. All voltages are with respect to the V_{SS} line

DEVICES ... APPLICATIONS

FOUR DIGIT MOS CALCULATOR I.C.

IT SEEMS only a short while ago that we were all impressed by the technology needed to put a complete calculator on one chip, yet already General Instrument Microelectronics have developed a second generation M.O.S. calculator integrated circuit. The main advantage of the new device is greatly reduced power consumption, this being made possible by reducing the necessary supply voltage from 25 volts to 15 volts.

The new calculator i.c.s. type C550 and C554, enable either eight (C550) or four (C554) digit calculators to be built. The reduction in power supply voltage is made possible by the use of new materials. The new process is called General Instrument Advance Nitride Technology (GIANT). Reduction of power supply voltage reduces chip consumption to a mere 150mW.

FOUR DIGIT CALCULATOR

Since eight digit calculator i.c.s. are most widely used the more unusual four digit i.c. (C554) will be described. This calculator needs only a four digit display so is much cheaper and probably just as useful as the eight digit type.

Fig. 1 shows the block diagram of a calculator built around the C554. All switches would be contained on a keyboard. Some of the connections to the i.c. are used both as inputs and outputs, this being done to keep the pin count down to 24. The i.c. is driven by an 80kHz clock generator.

The i.c. generates a strobe pulse at pin 23 which is fed to all the keyboard contacts except the interchange (INT) switch. If any of the keyboard contacts are closed during the strobe pulse then the appropriate input will be fed to the i.c. The strobe pulse only occupies a very small proportion of the total clock period, the rest being used to display the output.

DISPLAY

A multiplexing system is used for the output whereby each of the four digits is selected in turn. A seven segment output is generated on the same lines used as numerical inputs (pins 6 to 12) as well as decimal point information. The display can be any seven segment type such as l.e.d., liquid crystal or hot filament; the driver (interface) circuit is the only thing that needs changing.

Fig. 2 shows a more detailed circuit diagram using l.e.d. seven segment displays and single-transistor drivers. The 220k Ω resistors are needed because the MOS output transistors are "open drain" types. All voltages are specified with respect to the V_{ss} level. The 560 Ω resistors are simply to limit the current through the l.e.d.s and the 4.7k Ω resistors are to limit the transistor base current.

INTERCHANGE SWITCH

One point that has not been so far explained is the interchange switch labelled INT. The C554 has been described as a four digit device in that it only displays

four digits at a time but, in fact, it can accept up to eight digit inputs and produces an eight digit output. The interchange switch interchanges the two sets of four digits so that more accurate answers may be obtained if desired. The l.e.d. shown indicates which of the groups is being displayed. The decimal point appears in whichever group is appropriate; if the decimal point does not occur in the group being displayed it will be obvious as all the decimal points on all four digits will be illuminated.

As mentioned earlier the C554 needs a 15V power supply and an 80kHz clock input. Both of these needs can be satisfied with the circuit shown in Fig. 4. An oscillator generates the 80kHz clock pulses and its output is fed to a regulator which gives 15V at up to 10mA.

USING THE CALCULATOR

The C554 can perform all the normal arithmetic operations: addition, subtraction, multiplication and division. The true sign of answers is given if the result is negative the minus sign replacing the most significant digit so that only three digits are available.

There is a single CLEAR key which can be used to clear either the complete calculator or the last entry. If the depression of the CLEAR key is followed by pressing a function key, only the last entry will be cleared; if a digit key is pressed then the whole calculator will be cleared.

There is a CONSTANT facility whereby a result of a calculation might be stored to be used after the entry of another number. The constant store can hold a multiplier, divisor, subtrahend or addend.

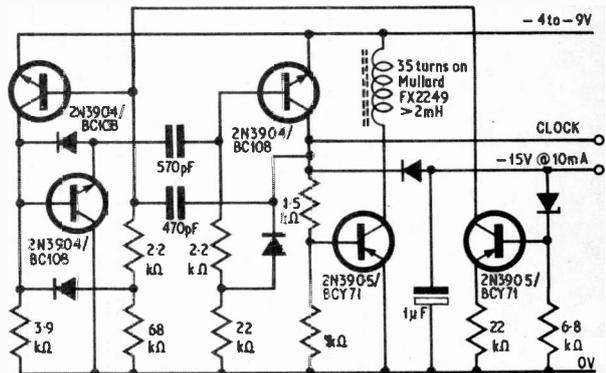


Fig. 3. A power supply and clock generator for the C554 i.c. which is all that is needed to complete the calculator in Fig. 2

Semiconductor TESTER

BY J. H. PERKIN



FOLLOWING the circuit description last month the construction of the semi-conductor Tester will be described.

CONSTRUCTION

Most of the components are mounted on 0.15in matrix Veroboard measuring $3\frac{1}{4}$ in \times $1\frac{1}{4}$ in. Breaks in the copper strips should be made as shown in the Veroboard layout of Fig. 7.

The positions of the components are shown the reverse of Fig. 7, but the layout is not critical. The resistors and capacitors are mounted first, remembering to connect the electrolytic capacitor C6 (2 μ F) the correct way round i.e. +ve to +ve. The component leads are fed through the Veroboard holes and bent so as to lie along the copper strips. The leads are then cut so that about 0.1in of lead remains on the copper strip, and then the leads are carefully soldered to the strip.

The transistors and diodes are mounted last, care being taken not to overheat the leads as this can cause component failure.

Meter face

The meter face should be modified to include all the numbers in Fig. 8. Letraset can be used for this purpose.

Case and component interconnections

The case used was a 18cm \times 15cm \times 13.5cm West Hyde MOD303.

The lettering on the front panel may be done using Letraset. The components are then mounted on the front panel and the connections shown in the circuit diagram are made. Use a different coloured wire for each connection link if possible for simplicity.

Connect one male battery connector to a female battery connector by 4in of wire for the battery "jumper" lead.

VEROBOARD PANEL

Printed Circuit Supporting Bracket

The bracket used to support the Veroboard panel may be made from aluminium sheet, 22 s.w.g. being quite suitable.

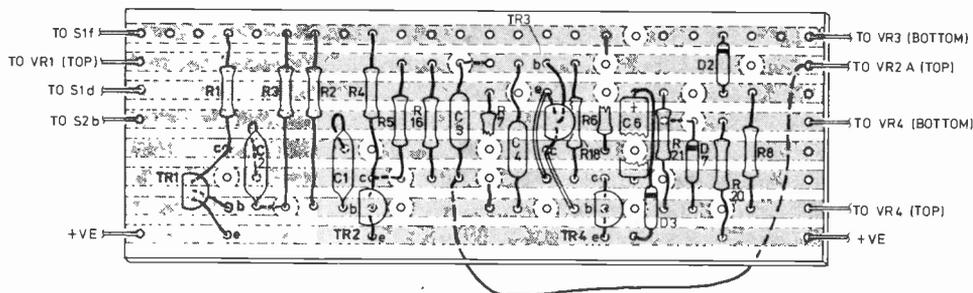


Fig. 7. Layout of the components on the Veroboard panel

Two holes should be made in the Veroboard panel to align with holes made in the bracket.

The batteries are retained in the case in the prototype using one piece of 1in wide elastic which is 8.5in long. Each end of the elastic is secured to the base of the case by a 4BA bolt, and nuts. The feet supplied with the case are now stuck to the base of the case. The test leads are made as shown in Fig 9, each lead being about 60cms long.

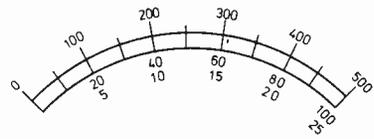


Fig. 8. The modified meter face

TESTING

Testing may be accomplished as follows, the components being tested are listed at the beginning of each test to facilitate fault finding by beginners.

1. S3, Batteries, S1A, S1B, S1C, R9, D4, D5, 52A, 52B, 526, ME1, R14, S4. Socket leads C and E.

(a) Set METER switch to I_{ce0} , DEVICE switch to PNP, and ON/OFF switch to ON:—meter should indicate zero.

(b) Connect a resistor of approximately 50 k Ω between leads C and E:—meter should read approximately 200 μ A.

(f.s.d. = 10mA).

(c) Depress F.S.D. \div 20 switch:—meter should read approximately 200 μ A.

(f.s.d. = 0.5mA). Release F.S.D. \div 20 switch.

(d) Set DEVICE switch to NPN and repeat 1(b) and 1(c).

(e) Connect lead C to lead E:—meter should read approx. 10mA (f.s.d. = 10mA).

(f) Set (METER switch to I_c and repeat (e).

(g) Disconnect lead C from lead E:—meter should read zero.

Switch OFF tester.

2. R1 to 6, R16, R21, R18, R17, VR2A, C1, C2, C3, C6, D3, D7, TR1 to TR4, S1F, S2A, 52C, Meter, R7, C4.



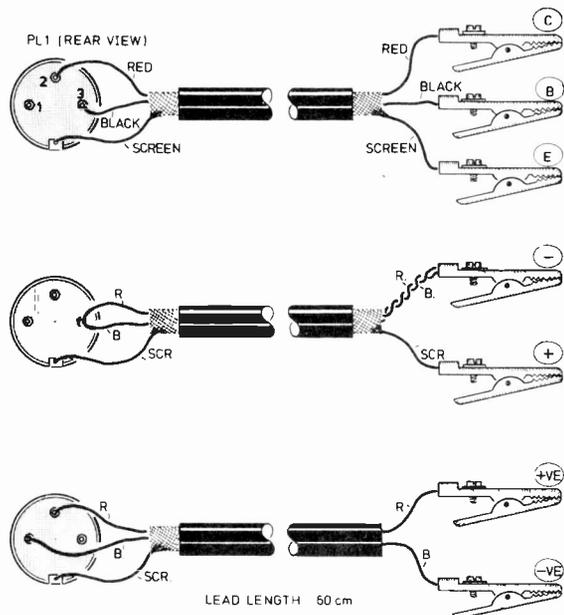


Fig. 9. Transistor, CSR and diode leads

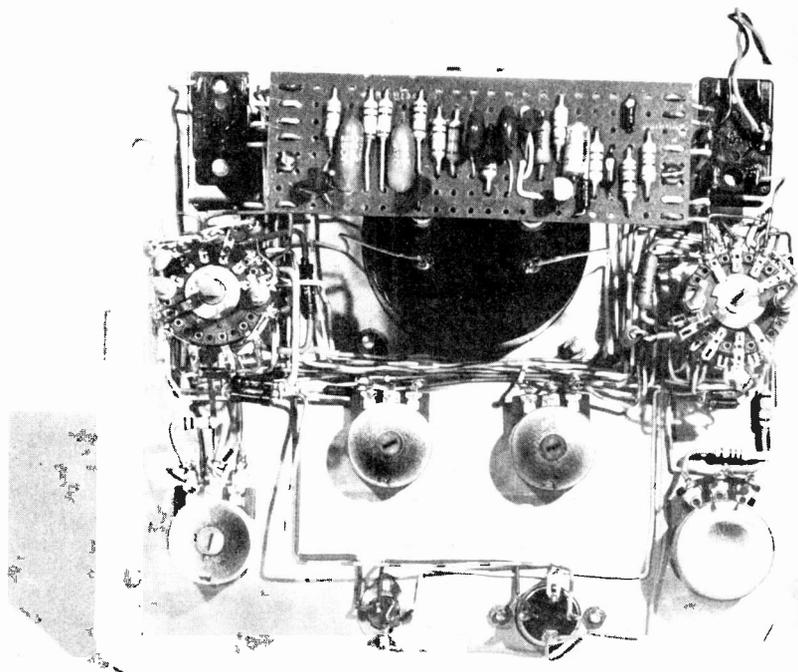Rear view of the front panel of the Semiconductor Tester



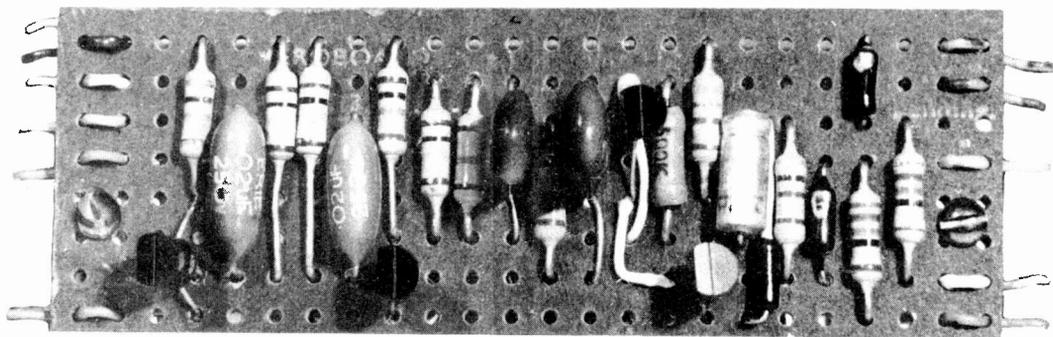

Photograph of the components on the Veroboard panel

(a) set METER switch to h_{fe} , DEVICE SWITCH TO PNP, ON/OFF switch to ON:—meter should read approx. f.s.d. If meter reading is somewhat less than f.s.d. decrease value of R16, if meter reading is greater than f.s.d. increase value of R16.

(b) Set DEVICE switch to NPN:—meter reading should remain as in 2 (a). Switch tester OFF.

3. VR1, R15, R19, C3, R22, S1E, S2D, VR2B, R10.
 (a) Connect a "working" transistor to the transistor socket SK1 or the "Flying Leads" lead C to collector, lead B to base, and lead E to emitter. Set METER switch to I_c , DEVICE switch to PNP or NPN depending on transistor type, set SET I_c to min. switch ON tester:—meter reading should increase as SET I_c control is turned from min. to max. Adjust SET I_c so that the meter current is 2mA (f.s.d. = 10mA).

(b) Set METER switch to h_{fe} and adjust h_{fe} control:—it should be possible to find a position where the meter deflection is a minimum. Switch OFF tester and remove the transistor.

4. S1F, LP1, D2, R8, VR4, R20, VR3, D1, R11, S2A, R13, R12, S2C, S4, S2B, S1E, R22, S2D, D6, R23, leads b.

(a) Set DEVICE switch to THY ZEN UJT V, METER switch to THY GATE 1, turn SET I to max. and SET V to min. short leads B and C, switch ON tester and adjust SET V from min. to max.:—meter reading should increase from zero to approx. $\frac{1}{4}$ f.s.d.

(b) Set SET V to min, depress and hold F.S.D. \div 20 switch and adjust SET V for f.s.d., release F.S.D. \div 20 switch:—meter should now be 1/20 of f.s.d. Remove short between leads B and C, switch OFF tester.

(c) Set METER switch to THY GATE V, switch ON tester, adjust SET V from min. to max.:—meter reading should decrease from 12V to 0V (f.s.d. is 25V).

(d) Set METER switch to THY HOLD I, turn SET I to min, short leads C and E, and increase SET I from min. to max.:—meter reading should increase to approximately f.s.d. when lamp L1 should be lit.

(e) Set SET I to min., depress and hold F.S.D. \div 20, increase SET I control until meter reads f.s.d., release F.S.D. \div 20:—meter should read 1/20 f.s.d.

OPERATING INSTRUCTIONS

Transistor testing

1. Connect transistor to socket SK1 or to flying leads, E to emitter B to base, C to collector.
2. Set DEVICE to PNP or NPN depending on transistor type).
3. Set METER switch to I_{ceo} , switch tester ON—meter shows I_{ceo} (f.s.d. 10mA). Operate F.S.D. \div 20 if required.
4. Set METER switch to I_c .
5. Adjust SET I_c control for required I_c on meter (f.s.d. 10mA).
6. Set METER switch to h_{fe} .
7. Adjust h_{fe} control for minimum reading. The h_{fe} is indicated on h_{fe} scale.

Diode Testing

1. Connect to socket SK1 on to flying leads of transistor lead, E to anode and C to cathode.
2. Set METER switch to I_{ceo} .
3. Set DEVICE switch to PNP, switch TESTER ON meter shows forward current (f.s.d. 10mA) $R_F = \frac{12000}{I_f \text{ (in mA)}} - 1200$.
4. Set DEVICE switch to NPN—meter shows reverse current $R_R = \frac{12000}{I_R \text{ (in mA)}} - 1200$ (F.S.D. \div 20 may be used if required)

Zener Diodes (0-10V)

1. Connect diode to socket SK1 or to flying leads of transistor lead. C to cathode E to anode, connect lead B to lead C.
2. Set DEVICE switch to THY ZEN UJT V.
3. Set SET V to min.
4. Set SET I to min.
5. Switch METER switch to THY GATE V/V, switch tester ON—meter reads Zener voltage (f.s.d. = 25V).
6. Adjust SET I from min. to max. meter reading should only change by a small amount. This check gives a rough indication of the a.c. resistance of the diode. (The current through the diode

at any point can be found by setting meter switch to THY HOLD I, I.

Note that for Zener voltages in excess of 10V it is necessary to insert a battery of known voltage between the emitter lead of the Zener diode and lead E of the tester, then Zener Voltage = meter reading + battery voltage.

Thyristor Testing

1. Connect the thyristor to SK1 or to the flying leads of the transistor testing lead anode to E, cathode to C, Gate to B.
2. Set SET V to min.
3. Set SET I to max.
4. Set DEVICE switch to THY ZEN. UJT. V.
5. Set METER switch to THY GATE I, switch tester ON.
6. Adjust SET V slowly clockwise noting the meter current. When the lamp L1 lights (thyristor conducting). Use $FSD \div 20$ if required. Meter reading to gate trigger current.
7. Set SET V to min.
8. Switch tester OFF then ON—lamp L1 should extinguish indicating that thyristor has reset.
9. Set METER switch to THY GATE V—meter indicates supply voltage.
10. Adjust SET V slowly clockwise—meter reading slowly falls then suddenly drops to zero, note the voltage (trigger voltage) at which the meter reading suddenly falls.
Gate trigger voltage = Supply voltage - trigger voltage
11. Set SET V to min.
12. Set METER switch to THY HOLD I, I.
13. Adjust SET I from max. to min. and note the point at which the meter current falls to zero, this current is the thyristor holding current. (F.S.D. $\div 20$ may be used if required).

Unijunction transistor testing

1. Set DEVICE switch to THY, ZEN, UJT, V.
2. Set METER switch to THY GATE V, V.
3. Set SET V to min.
4. Connect unijunction to SK1 on to flying leads Base 1 to C, Base 2 to E, Emitter to B.
5. Switch tester ON.
6. Adjust SET V (noting decrease in meter voltage reading until meter "kicks" when:—

$$\text{Intrinsic Standoff ratio} = \frac{\text{decrease in meter voltage}}{\text{maximum meter voltage}}$$

Using tester as a Voltmeter

1. Set DEVICE switch to PNP.
2. Set METER switch to THY GATE U, V.
3. Connect voltmeter lead to voltage to be measured

Using tester as an Ammeter (f.s.d. = 100mA or 5mA).

1. Set METER switch to THY HOLD I, I.
2. Connected current lead to current source (F.S.D. $\div 20$ may be used if required). ★

TRANSFORMERS

MAINS ISOLATING SERIES
Primary 120/240 Volts. Secondary 120/240 Volts Centre Tapped and Earth Shielded
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £ p
07	20	1 8	7.0 x 6.0 x 6.0	1.94 30
149	60	3 12	9.9 x 7.7 x 8.6	2.88 36
150	100	5 8	9.9 x 8.9 x 8.6	3.16 52
151	200	8 0	12.1 x 9.3 x 10.2	5.31 52
152	250	13 12	12.1 x 11.8 x 10.2	7.01 67
153	350	15 0	14.0 x 10.8 x 11.8	9.40 82
154	500	19 8	14.0 x 13.4 x 11.8	13.55 *
155	750	29 0	17.2 x 14.0 x 14.0	19.26 *
156	1000	38 0	17.2 x 16.6 x 14.0	24.97 *
158	2000	60 0	21.6 x 15.3 x 18.1	41.25 *

PLEASE NOTE
NEW ADDRESS
AS BELOW

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £ p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.02 27
64	75	2 4	7.0 x 6.7 x 6.1	0-115-210-240	2.00 30
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	2.42 36
66	300	6 4	9.9 x 9.6 x 8.6	"	4.70 52
67	500	12 8	12.1 x 11.2 x 10.2	"	6.98 67
84	1000	19 8	14.0 x 13.4 x 14.3	"	12.69 82
93	1500	30 4	14.0 x 15.9 x 14.3	"	18.39 *
95	2000	32 0	17.2 x 16.6 x 14.0	"	24.00 *
73	3000	40 0	21.6 x 13.4 x 18.1	"	32.67 *

TOTALLY ENCLOSED 115V AUTO TRANSFORMERS
115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets. £9.49. P & P 67p.
Also available a 20 Watt version, £2.02. P & P 22p.

LOW VOLTAGE SERIES (ISOLATED)

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Windings	P & P £ p	
111	0.5	0.25	4	4.8 x 2.9 x 3.5 0-12V at 0.25A x 2	1.02 22	
213	1.0	0.5	4	6.1 x 5.8 x 4.8 0-12V at 0.5A x 2	1.22 22	
71	2	1	12	7.0 x 6.4 x 6.1 0-12V at 1A x 2	1.60 22	
18	4	2	12	8.3 x 7.7 x 7.0 0-12V at 2A x 2	2.24 36	
70	6	3	12	8.9 x 8.0 x 7.0 0-12V at 3A x 2	2.70 42	
108	8	4	5	8.9 x 8.9 x 8.6 0-12V at 4A x 2	3.00 52	
72	10	5	6	4	9.9 x 9.6 x 8.6 0-12V at 5A x 2	3.55 52
17	16	8	8	12	12.1 x 9.9 x 10.2 0-12V at 8A x 2	5.48 52
115	20	10	11	8	14.0 x 9.6 x 11.8 0-12V at 10A x 2	6.98 67
187	30	15	15	8	14.0 x 12.1 x 11.8 0-12V at 15A x 2	12.90 82
226	60	30	32	0	17.2 x 15.3 x 14.0 0-12V at 30A x 2	23.72 *

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
112	0.5	1	4	6.1 x 5.8 x 4.8 0-12-15-20-24-30V	1.22 22
79	1	2	4	7.0 x 6.7 x 6.1	1.62 36
3	2	3	4	8.9 x 7.7 x 7.7	2.42 36
20	3	4	8	9.9 x 8.3 x 8.6	2.99 42
21	4	5	8	9.9 x 8.6 x 8.6	3.55 52
51	5	6	12	12.1 x 8.6 x 10.2	4.42 52
117	6	8	0	12.1 x 9.3 x 10.2	5.28 52
88	8	12	0	12.1 x 11.8 x 10.2	6.82 67
89	10	13	12	14.0 x 10.2 x 11.8	8.36 67

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
102	0.5	1	12	7.0 x 6.4 x 6.1 0-19-25-33-40-50V	1.60 30
103	1.0	2	12	8.3 x 7.4 x 7.0	2.34 36
104	2.0	5	8	7.9 x 8.9 x 8.6	3.25 42
105	3.0	6	12	9.9 x 10.2 x 8.6	4.41 52
106	4.0	10	0	12.1 x 10.5 x 10.2	5.84 52
107	6.0	12	0	14.0 x 10.2 x 11.8	8.63 67
118	8.0	18	0	14.0 x 12.7 x 11.8	11.27 97
119	10.0	25	0	17.2 x 12.7 x 14.0	14.13 *

Ref. No.	Ampls.	Weight lb oz	Size cm.	Secondary Taps	P & P £ p
124	0.5	2	4	7.0 x 6.7 x 6.1 0-24-30-40-48-60V	1.62 36
126	1.0	3	4	8.9 x 7.7 x 7.7	2.26 36
127	2.0	6	4	9.9 x 9.6 x 8.6	3.55 42
125	3.0	8	12	12.1 x 9.9 x 10.2	5.41 52
123	4.0	13	12	12.1 x 11.8 x 10.2	6.98 67
120	6.0	15	8	14.0 x 12.1 x 11.8	10.12 82
122	10.0	25	0	17.2 x 12.7 x 14.0	16.75 *

EQUIPMENT TRANSFORMER
Ref. 238 PRI 240V Screen Sec. 3-0 3V. RMS at 200mA. Size cm. 2.8 x 2.6 x 2.0. Weight 2oz. £1.18. P & P. 10p.


Ref. No.	Ampls.	Weight lb oz	Size cm.	P & P £ p
45	1.5	1 8	7.0 x 6.1 x 6.1	1.61 30
5	4.0	3 4	8.9 x 7.7 x 7.7	2.45 42
86	6.0	6 4	9.9 x 9.6 x 8.6	3.70 52
146	6.0	6 12	9.9 x 10.2 x 8.6	4.22 52
50	12.5	12 0	14.0 x 10.2 x 11.8	6.29 67

All ratings are continuous. Standard construction: open with folder tags and vacuum impregnation. *Carriage via B.R.S.

FULL SPEC. TRANSISTORS
BC107/108/109 12p each. 2N3055 60p each. AD161/162 60p pair + mica and bushes

ELECTROSIL RESISTORS • AVOMETERS
PLEASE ADD 10% FOR V.A.T. INCLUDING P. & P.

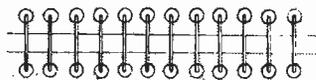BARRIE electronics
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS: ALDGATE & ALDGATE EAST



INDUSTRY NOTEBOOK

By Nexus



TOUGH FIELD

It takes a lot of guts to take on the big boys, especially in a field as tough as mobile radio-telephones. This is the field where household names like Cossor, Ultra and STC have all chucked in the sponge within the past year or so.

Pye is still undisputed market leader and Burndept, strengthened by the acquisition of Cossor and Ultra business, is second. The question is whether Dymar can succeed when better-known companies have failed?

I can report that there was no lack of confidence in the Dymar management when the company launched its new 'Lynx' range of mobiles on September 12. For one thing the Lynx, with a 20W output, has a technical edge on the competition and Dymar has prepared the sales ground well by appointing a nation-wide network of distributors and service centres.

Although Dymar as a name is not yet well known, the company has a huge back-log of experience in both design and manufacture of mobile radio. To date, Dymar has produced 30,000 mobile equipments of which half have been made under contract to other companies' designs and about 7,500 have been land or marine mobiles of Dymar's own design and manufacture.

Approximately £150,000 has been invested in the Lynx development and it could be a real winner. In fact the company expects no less than half the total 1974 turnover in Lynx with the other half split 35 per cent in marine radiotelephones, and 15 per cent in instruments of which Dymar make a range for manufacture, testing and servicing of r.f. systems.

SATELLITE NAVIGATION

While Dymar was launching Lynx in Whitehall, Redifon was launching a marine satellite navigation receiver half-a-mile away in the Strand.

The Redifon Satellite Navigator is another milestone along the road forecast by J. R. Brinkley when, earlier this year, he said the company was now fully committed to a huge modern technology programme to win a large share of the communications and navigation markets. It was on that occasion that he was able to announce that the Redifon Omega Navigator had already been fitted to 100 ships and had realised £0.5 million in revenue.

What industry observers are waiting for now is the Redifon v.h.f./u.h.f. programme. No hardware has yet been announced although R and D expenditure in this area is said to be £100,000. As part of the expansion programme a new plant is under construction in Wales which could ultimately house 1,000 workers.

BATTLE CONTINUES

The light-emitting-diode battle continues with increasing intensity. Ferranti's new green LED's are reported to be coming out of the factory at 1.5 million a year now, stepping up to a rate of 10 million a year by the Spring of '74.

Plessey's Optoelectronics and Microwave Unit at Towcester is also in on the action with a new yellow gallium phosphide device which is claimed to have a higher light output and spot brightness than any other solid state light source currently available. The Towcester Unit is also offering custom-built hybrid arrays in green, yellow and red, a typical array recently produced for a customer having 32 diodes. They are assembled and encapsulated on a metallised ceramic substrate which can include dropping resistors if required.

INSTRUMENTS— A HARD LIFE

The instrument industry is struggling back to life after three years in the doldrums. Renewed activity springs from the big investment programmes now being undertaken by many major user companies.

But the instrument business is no sinecure. John Ceresa, marketing director of Rascal Instruments, recalls that 13 years ago a 10MHz counter cost £400. By 1970, in ten years, the price had dropped 75 per cent for the same instrument in a solid state version and with much improved performance and reliability. You then found you had to

sell four times as many to make the same turnover and maybe eight times as many to make the same profit.

Another angle on the life and hard times of instrument men comes from David George, managing director of SE Laboratories, one of the companies who have been through a bad patch. He says it is suicidal for any company to try to compete in every generation of instruments. One of the ways of cutting R and D costs is to do a deal with a complementary manufacturer elsewhere in the world. SE Labs has actually done this with Data Precision Corporation in USA.

I note with interest that even Tektronix with a near stranglehold on the top end of the oscilloscope market is finding it hard to expand any further without diversifying into other fields. Although the oscilloscope market shows no signs of a decline—it is still growing at least 10 per cent a year—Tektronix has moved into programmable calculators and more recently has acquired a Californian Company which specialises in TV studio equipment.

AD-POWER WORKS!

Just when you think there are no surprises left in the industry you encounter another. I had this experience when I visited Kingshill Electronic Products who make professional quality power supplies for the universities, the Government, and the industry in general. The company is a subsidiary of Islington Metal and Plating Works Ltd., one of the pioneers of chromium plating nearly 50 years ago. The electronics off-shoot was started in 1964 by Dr. Henry Herbst who still sits in the managerial chair. His sort of company would normally have a flock of travelling salesmen chatting up potential customers and a sales programme involving appearances at major electronic exhibitions.

Not Kingshill. Herbst has never had a salesman on the road, has never shown at an exhibition. Kingshill sells on press advertising and personal recommendation. It seems to work. The production lines turn out 18,000 units a year which not only go to U.K. users but also to out-of-the-way places like Fiji and Thailand.

The premises were a surprise, too. They were originally stables for the horses of the old London horse-drawn trams. Not so unexpected is that Herbst, with a solid business now established in power supplies and a firm economic base from which to operate, is looking for new electronic fields to conquer.

PRICES NOW INCLUDE VAT SUPERSOUND 13 HI-FI MONO AMPLIFIER




A superb solid state audio amplifier. Brand new components throughout. 3 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz-30KHz \pm 3db. Fully integrated pre-amplifier stage with

separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, switchgear panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. A.C. 200/250V.

PRICE £11-60

P. & P. 40p.

DE LUXE STEREO AMPLIFIER

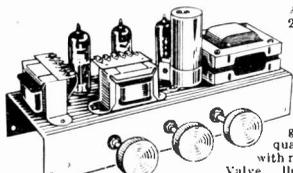

A.C. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: $\times 2$ ECL86 Triode Pentodes.

1 \times EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w x 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. **Price £9-90.** P. & P. 50p.

NEW! POWER SUPPLY UNIT

200/240V A.C. input. Four switched fully smoothed D.C. outputs giving 6V and 7.5V and 9V and 12V at 1 amp continuous (1 amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6" x 3 1/4" x 2 1/4". Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

PRICE £5

P. & P. 35p.

BLACK ANODISED 16g. ALUMINIUM HEAT SINKS. For T03, complete with mica's and bushes. Size 2 1/2in x 3in approx. 25p pair. P. & P. 6p.

HIGH GRADE COPPER LAMINATE BOARDS. 8" x 6", 5 for 55p. P. & P. 23p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half watt at 1 amp or 10-0-10, 20-0-20, 30-0-30V, at 2 amp full watt. Size 3 1/4in. x 3 1/4in w x 3in d. Price £2-10. P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V Sec. 9-0-9 at 500mA. £1 P. & P. 25p. Pri. 200/240V Sec. 12-0-12 at 1 amp. £1-10 P. & P. 25p. Pri. 200/240V Sec. 10-0-10 at 2 amp. £1-65 P. & P. 35p.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 20dB. Solid encapsulation size 1 1/4 x 1 1/4 x 1/2in. Brand new — complete with instructions. Price £1. P. & P. 15p.

3 REFERENCE ENCYCLOPEDIAS FOR ELECTRONIC ENGINEERS AND DESIGNERS, covering between them, transistor characteristics, diode and transistor equivalents. Many thousands of up-to-date European types listed.

Diode Equivalents	80p
Transistor Equivalents	90p
Transistor Characteristics	£1-20
All three together	£2-80

POST FREE

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

Open 9-5.30 Mon. to Fri. 9-5 Sat. Early closing Wed. 1p.m.

A few minutes from South Wimbledon Tube Station.

CENTRE ZERO MINIMATURE MOVING COIL METER. 100uA for balance or tuning. Approx. size 1in x 1in x 1/4in. Limited number 88p. P. & P. 12p. NEW ISSUE—Thyristor, Triac, Diac, etc. encyclopedias 95p Post Free

RECORD PLAYER BARGAINS

Main models. All brand new in maker's packing. **LATEST B.S.R. C109/C129 AUTOCHANGER UNITS.** With latest stereo/mono compatible cartridge £7-60 plus 50p P. & P. **Garrard SP25 Mk. III** with heavy precision machined die cast turntable. £10-68. Carr. 55p.

PRECISION ENGINEERED PLINTHS

Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL651B, AT660, etc., or B.S.R. C109, C129, A21, etc. Black leatherette finish. Size 12 1/2in x 14 1/2in x 3 1/2in high approx. 7 1/2in high, including rigid smoked acrylic cover). P. & P. 70p. **Now only £4-95**

LATEST ACOS GP91/18C Mono Compatible Cartridge with T/O stylus for LP/EP/78. Universal mounting bracket. £1-50. P. & P. 15p.

SONOTONE STARC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2-30. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2-30. P. & P. 15p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/Stereo/78. £1-63. P. & P. 15p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono/stereo records on mono equipment £1-50. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK II

A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 d. x 6 h. Ready built and tested. **PRICE £4-40.** P. & P. 40p. **ALSO AVAILABLE** mounted on board with output transformer and speaker. **PRICE £5-85.** P. & P. 60p.

SPECIAL OFFER!! HI-FI LOUSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16in high x 10 1/2in wide x 6in deep. Fitted with E.M.I. Ceramic Magnet 13in. cone bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £9-25

Carr. 75p.

CABINET AVAILABLE SEPARATELY

£4-95. Carr. 60p.

Also available 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. £7-15. Carr. 75p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx 3 1/2 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer.

OUR ROCK BOTTOM BARGAIN PRICE

£3-30

P. & P. 40p

LOUDSPEAKER BARGAINS

5in 3 ohm £1-05. P. & P. 15p. 7 x 4in 3 ohm £1-15. P. & P. 20p. 10 x 6in 3 or 15 ohm £1-90. P. & P. 30p. E.M.I. 8 x 5in 3 ohm with high flux magnet £1-62. P. & P. 20p. E.M.I. 13 x 8in with high flux ceramic magnet with parasitic tweeter 3, 8, or 15 ohm £2-50. P. & P. 30p. E.M.I. 13 x 8in, 3 or 8 or 15 ohm with two built-in tweeters and crossover net £4-65. P. & P. 30p.

EMI CERAMIC MAGNET HEAVY DUTY TWEETER. approx 3 1/2in. AV. 3 or 8 or 15 ohms. £1-25 plus 20p P. & P. **BRAND NEW.** 12in 15W I/FD Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly £7-50. Guitar models: 25w £7-50, 35w £9-35. P. & P. 45p each.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS. With large ceramic magnet and plasticated cone surround, 8 ohm impedance.

£2-70. P. & P. 35p.

Also available specification as above but size 10" x 6" £2-70 and size 8" round £2-60 P. & P. 35p.

12in "RA" TWIN CONE LOUSPEAKER

10 watts peak handling, 3, 8 or 15 ohm. £2-45. P. & P. 36p. **35 ohm SPEAKERS 3" 8" 15" £1-70.** P. & P. 25p.

"POLY PLAS" WIDE RANGE ELECTRO-DYNAMIC SPEAKER


Size 1 1/2in x 1 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £6-55 each. P. & P. 34p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 5 1/2in. wide. Our price 85p yd. length. P. & P. 25p per yd. (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3 1/2 jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. **PRICE £3-30.** P. & P. 25p.

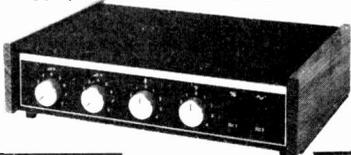HAVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output 14W 12-30,000Hz. Sensitivity better than 80mV into 1M Ω . Full power bandwidth \pm 3dB 12-15,000Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to \pm 16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1-0 amp. Overall size—12" wide x 8" deep x 3" high.


Fully detailed 7-page construction manual and parts list free with kit and send 18p plus large S.A.E.

PRICES AMPLIFIER KIT, £11-55. P. & P. 25p. (Magnetic input components 33p extra) **POWER PACK KIT, £3-30. P. & P. 35p.** **CABINET, £3-30. P. & P. 35p.**

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £23-10. Post Free.

Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosqueque use.

3-VALVE AUDIO AMPLIFIER HA34 MK II

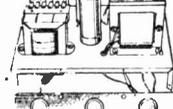

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in. w. x 4in. d. x 4 1/2in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £5-50. P. & P. 45p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4-50. P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL34s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL24s, ECC83, EP86 and EZ80 rectifier. Simple instruction booklet. 15p plus S.A.E. (Free with parts). All parts sold separately. ONLY £9-80. P. & P. 60p. Also available ready built and tested £12-10. P. & P. 70p.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

Dept. PE, 170 High St., Merton, London, S.W. 19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

PHASE LOCKED LOOPS

**PART 2:
A.M. AND F.M.
DEMODULATION
AND FREQUENCY
SYNTHESISERS**

BY J.B.DANCE M.Sc.

IN LAST MONTH'S article the basic principles of phase locked loops were described. This month we will look at the application of these principles in f.m. radio reception, a.m. demodulation and frequency synthesisers.

RECEIVER TECHNIQUES

An amplitude modulated (a.m.) radio signal consists of a high frequency sine wave, whose frequency is fixed for any particular broadcasting station, but whose amplitude varies in sympathy with the audio signal that is the information to be transmitted. The carrier frequency f_s ranges from about 200kHz up to many megahertz, whilst the audio frequency ranges from 30Hz to 15kHz. The receiver must be able to reproduce the modulating audio signal as faithfully as possible and must provide as much separation as possible between signals whose carrier frequencies are close.

T.R.F. RECEIVERS

One of the simplest forms of radio receiver is the so-called "tuned radio frequency" (t.r.f.) receiver. The basic form of this type of receiver is shown in the block diagram of Fig. 2.1.

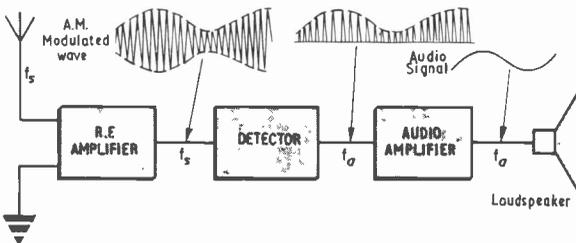


Fig. 2.1. A block diagram showing the stages in a t.r.f. receiver

The incoming signal is amplified in the radio frequency stage. No change in the frequency or in the form of the signal takes place in this stage, but tuned circuits are employed to provide selectivity and to reject unwanted signals of other frequencies.

The signal is then demodulated or detected, usually by a stage that provides some amplification. The audio signal from the detector (f_a) is fed to an audio amplifier which can provide sufficient power output to drive the loudspeaker.

The selectivity provided by receivers of this type is very limited, partly because it is not practical to employ more than about four tuned circuits operating at the radio frequency f_s . Each tuned circuit requires a separate gang of the tuning capacitor and the relatively long connections to this capacitor can lead to unwanted feedback and oscillation.


It is normally necessary to employ a fairly large value of tuning capacitor (typically 300pF to 500pF per gang) in order that the desired tuning range can be covered. This may make it impossible to design the tuned circuits for optimum Q factor (especially at high signal frequencies); the selectivity and gain therefore suffer.

The limitations of t.r.f. receivers become very noticeable at the higher frequencies. The pass band is so broad that it is impossible to obtain adequate selectivity and noise rejection, whilst the signal frequency amplification is normally inadequate in the short wave bands.

SUPERHETERODYNE RECEIVERS

Many of the disadvantages of the t.r.f. receiver can be avoided by the use of the superheterodyne principle, but some other undesirable features are then introduced. A block diagram of a superheterodyne receiver is shown in Fig. 2.2.

Fig. 2.2. A block diagram of a superheterodyne receiver. The use of an r.f. stage is optional

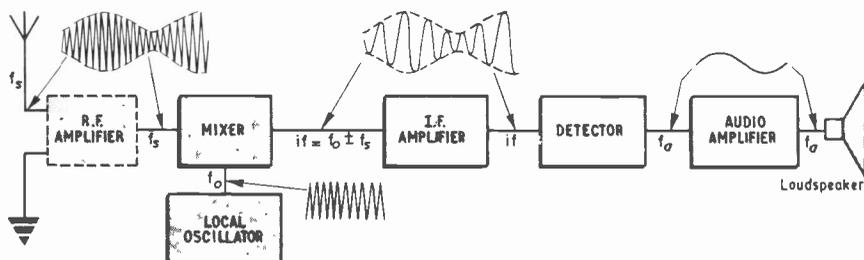

The incoming signal from the aerial at a frequency f_s may be fed into a radio frequency stage (shown dotted) or directly into the mixer stage. In the latter stage it is mixed with a frequency f_o generated by a local oscillator. The frequency f_o is varied with the frequency to which the receiver is tuned.

The output from the mixer consists mainly of the sum and difference frequencies of the signals which are fed into it, that is, $f_o + f_s$ and $f_o - f_s$. It is arranged that the frequency of one of these outputs (normally the difference frequency in receivers covering the long, medium and short wave bands) is kept constant no matter what the frequency of the input signal, f_s . This constant frequency output signal is known as the intermediate frequency or *i.f.*

The mixer stage is followed by one or more stages of amplification at the intermediate frequency. These stages involve the use of a number of tuned circuits (typically six) which resonate at the intermediate frequency.

The intermediate frequency tuned circuits are fixed tuned and they can therefore be designed with the optimum inductance/capacitance ratio for high selectivity and gain; they provide virtually all of the selectivity of the receiver. Each tuned circuit can be incorporated inside a metal can so that unwanted coupling is reduced to a minimum.

DISADVANTAGES OF SUPERHETS

Superheterodyne receivers have the disadvantage that they tend to suffer from spurious responses. Noises such as whistles may be generated when the local oscillator frequency (or one of its harmonics) beats with certain incoming frequencies. One of these undesired responses occurs at the image frequency, where a signal at a frequency of $f_s + 2i.f.$ mixes with the local oscillator frequency to form an interfering signal.

Image frequency interference may be reduced by using tuned circuits before the mixer or by using a high intermediate frequency so that the image frequency is far away from f_s and easily rejected by the tuned circuits in the r.f. amplifier, though this latter method tends to reduce selectivity.

Another disadvantage of superhets is that the tuned circuits used throughout cannot be formed on an integrated circuit chip. Integrated circuits are not only smaller but because of the ease of assembly they greatly reduce labour costs.

THE SYNCHRODYNE

The synchronodyne receiver is the forerunner of the phase locked loop and aroused great interest in the late 1940's. The synchronodyne type of receiver is illustrated in the block diagram of Fig. 2.3.

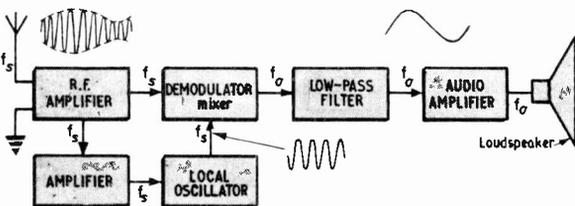


Fig. 2.3. The stages employed in a synchronodyne receiver

The signal from the aerial is fed via an optional radio frequency stage to the demodulator and also, via another amplifier stage, to a local oscillator. This signal keeps the local oscillator locked or synchronised to the input signal frequency—hence the name synchronodyne.

When the two signals of the same frequency come together in the demodulator stage (which is like the mixer of a superheterodyne), sum and difference frequencies are formed. The sum frequency, $2f_s$, is not required and is rejected by the succeeding low-pass filter. One might expect the difference frequency to be zero, but this really means that the carrier frequency is zero. In other words the output of the demodulator in Fig. 2.3 consists of the required audio signal minus the carrier.

Any interfering radio signals will not have the same frequency as the local oscillator. They therefore produce an output signal from the demodulator stage which is normally of a much higher frequency than that due to the wanted signal. The interfering signal cannot pass through the low-pass filter which follows the demodulator.

SYNCHRODYNE SELECTIVITY

One of the great advantages of the synchronodyne is that it does not obtain its selectivity by means of conventional tuned circuits, but by the use of a low-pass audio filter. This low-pass filter can be very simple (see Part 1) and can be designed to cut off at any point so as to provide the desired selectivity. It is easy to make the selectivity variable by adjusting the value of a single component.

Another important advantage of the synchronodyne receiver is that relatively few tuned circuits are employed in it. The only tuned circuit which is essential is the one in the oscillator circuit, but it is normally desirable to include some tuned circuits in the radio frequency stages to prevent very strong unwanted signals from overloading the mixer stage.

The local oscillator of a synchronodyne receiver must be locked in frequency to the wanted signal if one is to avoid the generation of beat frequencies. This type of receiver is either correctly tuned or not tuned at all. Unlike most other forms of receiver, a distorted audio output signal cannot be obtained as a result of the mis-tuning of the local oscillator.

As the local oscillator tuning is altered, the oscillator will remain synchronised to the incoming signal over a certain range, although the local oscillator signal may change in amplitude somewhat. Thus the only effect of a slight oscillator mis-tuning will be an alteration in the audio volume.

ADVANTAGES AND DISADVANTAGES

The synchronodyne receiver does not suffer from image responses. We have seen that an interfering signal at a frequency of twice the intermediate frequency plus the wanted signal frequency can produce an image response in a superheterodyne receiver; in the synchronodyne, however, the "intermediate frequency" is zero and therefore the image frequency becomes equal to the wanted signal frequency.

For domestic listening, the main objection to the use of the synchronodyne receiver is the loud whistles which are generated when one is tuning into a signal. These whistles are, of course, due to the local

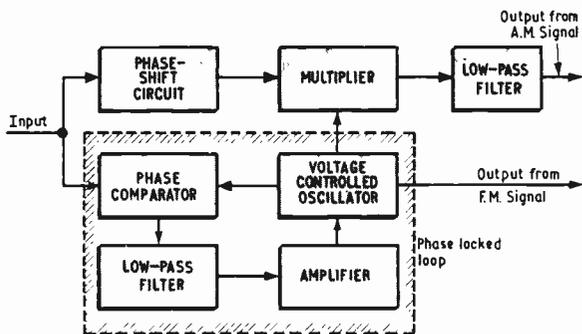


Fig. 2.4. An a.m. demodulator using a phase locked loop. The components of the loop itself are shown inside the box.

oscillator beating with the input signal before their frequencies become locked together. This problem can be overcome by the use of switched tuning.

Another reason for the limited use of synchronous receivers in the past has been the lack of simple, but effective phase locking circuits.

Other names for the synchronous receiver include "homodyne", "phase control" or "PC" receivers, synchronous detectors and phase locked detectors.

A.M. DEMODULATION

The block diagram (Fig. 2.4) shows a practical circuit for a.m. receivers using a phase locked loop.

The phase locked loop (comprising the units shown inside the dotted line) locks onto the input signal in the normal way. The voltage controlled oscillator produces a signal of the same frequency as the input signal, but it is unmodulated.

When the free-running frequency of the voltage controlled oscillator is the same as that of the incoming signal, locking will occur with these two signals 90° out of phase. In the system of Fig. 2.4, the phase shift circuit changes the phase of the input signal by 90° so that it is in phase with the output from the voltage controlled oscillator.

The two signals of the same phase are mixed in a second phase comparator or multiplier. The output from the multiplier is passed through a second low-pass filter so that only the difference frequency remains. This difference frequency is proportional to the amplitude of the input signal and is therefore the required audio output.

Systems such as that shown in Fig. 2.4 provide a higher degree of noise rejection than can be obtained from conventional a.m. demodulators which detect the peaked noise pulses.

F.M. DEMODULATION

The voltage controlled oscillator is normally designed so that its frequency is linearly related to the applied control voltage. As this latter voltage keeps the voltage controlled oscillator frequency the same as the incoming signal frequency, the control voltage is linearly related to the frequency deviation of the input signal.

In other words, the output voltage from the system (Fig. 1.1.) is the demodulated audio signal when the incoming signal is a frequency modulated one. The voltage controlled oscillator produces a greatly amplified copy of the input signal from which most of the noise has been removed.

One might expect that a very simple f.m. receiver could be constructed by merely feeding the input signal to the phase locked loop. In actual practice, however, a somewhat more complex system than this must be employed.

Currently available phase locked loops cannot operate at frequencies above about 60MHz. Most f.m. signals will therefore have to be converted to a lower frequency before they are passed to the phase locked loop. However, it seems likely that phase locked loops will be available at some future date which can operate at typical f.m. frequencies (about 100MHz) and it may then be possible to construct an f.m. receiver without the use of a frequency converter.

SENSITIVITY

Although phase locked loops can operate with a signal of just under a millivolt, some problems do arise if one wishes to operate them from an input of about $10\mu\text{V}$ (such as one may obtain from a receiving aerial at a considerable distance from the transmitter). It is generally better to amplify the signal before feeding it to the phase locked loop. Some tuned circuits are usually included in the system before the phase locked loop in order to reject signals which could produce spurious responses.

The phase locked loop may be employed to demodulate both narrow and wide band f.m. signals. It offers greater linearity than can be obtained by any other means and is therefore especially suitable for high fidelity systems.

At the other extreme, phase locked loops are employed in communications receivers where they are excellent for recovering weak signals in a noisy region of the radio spectrum.

FREQUENCY SYNTHESISERS

Frequency synthesisers are required for use in radio communications networks which will generate any one of a large number of frequencies with great accuracy at the touch of a button. For example, an aircraft navigation/communication band synthesiser may be required to produce frequencies in the range 108 to 136MHz at 50kHz intervals so as to cover each of the 560 channels.

Such frequency synthesisers can be designed using banks of quartz crystals and tuned circuits. However, it is normally more economic to employ a single quartz crystal to provide one accurate reference frequency and to obtain the other frequencies from it by the use of a phase locked loop together with a digital pulse frequency dividing circuit. This system has the additional advantage that fewer spurious frequencies are generated.

The basic system used in a phase locked loop frequency divider is illustrated by the block diagram of Fig. 2.5. The reference frequency is generated by a very stable quartz crystal controlled oscillator which is kept in a special constant temperature oven. If the frequency of this oscillator is 100kHz, the pulses may be divided in frequency to produce, perhaps, a 1kHz signal. The latter is fed as the reference signal to the input of the phase locked loop of Fig. 2.5.

DIVIDER CIRCUIT

The main difference between the frequency synthesiser circuit of Fig. 2.5 and the simple phase locked loop is the inclusion of a frequency divider circuit

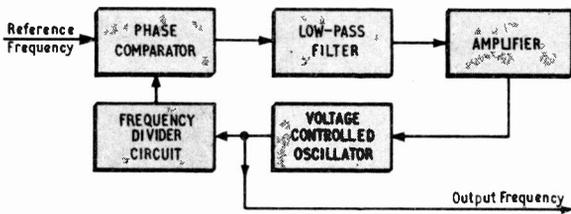


Fig. 2.5. The building blocks of a simple frequency synthesiser using a phase locked loop

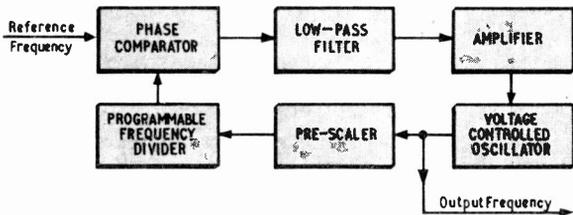


Fig. 2.6. In this type of frequency synthesiser a fast divider (the pre-scaler) is used to divide the pulse frequency.

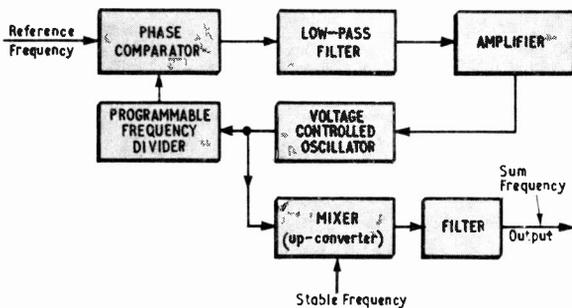


Fig. 2.7. Because phase locked loops can handle only relatively low frequencies, a mixer can be used to multiply the voltage controlled oscillator frequency.

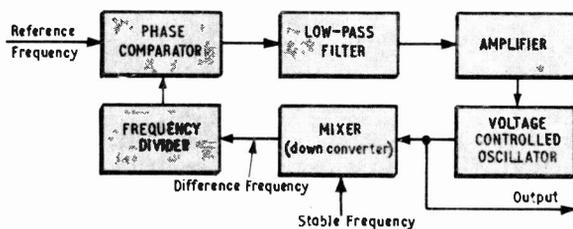


Fig. 2.8. In this type of frequency synthesiser a mixer is used to reduce the high voltage controlled oscillator frequency for the divider stage

between the voltage controlled oscillator and the phase comparator. This enables the voltage controlled oscillator to operate at a much higher frequency than the input reference signal.

If the reference signal has a frequency of 1kHz and the frequency divider is set so that it divides by, say, 569, the phase locked loop will come into lock when the voltage controlled oscillator frequency is 569kHz.

This frequency is divided so that it produces the same frequency as the input reference signal. In order to obtain any other output frequency from the voltage controlled oscillator, it is only necessary to change the factor by which this frequency is divided before it is fed to the phase comparator.

All frequencies generated in this way have the same stability as the reference frequency.

HARMONIC LOCKING

Phase locked loops will lock to a multiple of the input frequency, but the locking range decreases as higher and higher harmonics are used, since the amplitude of such harmonics is low.

Harmonic locking can be used in frequency synthesisers, but in general one should not attempt to lock a phase locked loop to a harmonic higher than about the tenth.

HIGHER FREQUENCIES

Digital frequency synthesisers are often required which will provide outputs of the order of some hundreds of megahertz. Voltage controlled oscillators can generate such frequencies, but programmable counters which can operate at above about 25MHz are very expensive.

It may therefore be more economic to operate the voltage controlled oscillator at a lower frequency and to multiply this frequency by a number of cascaded frequency multiplier stages. However, such a system has the disadvantage that tuned circuits are required in the multiplier stages and these must be re-tuned whenever the frequency is changed.

A more convenient system is shown in Fig. 2.6. The output from the voltage controlled oscillator is divided in frequency by a pre-scaler before being passed to a programmable frequency divider.

Other techniques for obtaining high frequency outputs include mixing the output from the voltage controlled oscillator with a stable frequency. The sum frequency is the required output, as shown in Fig. 2.7.

In yet another system, the output from the voltage controlled oscillator is mixed with a stable reference frequency and the difference frequency output is used to operate the programmable frequency divider. This type of system is illustrated in Fig. 2.8.

If a signal from a frequency synthesiser is fed to the mixer stage of a radio receiver together with the input signal, one can select the signal to be received merely by choosing the ratio by which the voltage controlled oscillator signal is divided. The drift in the tuning of such a system is quite negligible, since the reference frequency is crystal controlled.

Next month this series will continue with a review of the types of phase locked loops available from various manufacturers together with practical examples of the circuits in which they can be used.

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

OPEN ALL DAY SATURDAYS

PLEASE ADD 10% VAT

RESISTORS

±W Iskra high stability carbon film—very low noise—capless construction.
±W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm.
±W 2% ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price
±	5%	4.7Ω-2.2MΩ	E24	1-99 100+
±	10%	3.3MΩ-10MΩ	E12	1p 0-8p
±	2%	10Ω-1MΩ	E24	3-5p 3p
±	10%	1Ω-3.9Ω	E12	1p 0-8p
±	5%	4.7Ω-1MΩ	E12	1p 0-8p
±	10%	1Ω-10Ω	E12	6p 5-5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0-5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ±W, lin ±W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELTON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.
mounting (0.1 matrix).
Sub-miniature 0-1W, 5p each. Miniature 0-25W, 7p each.

TRANSISTORS

AC107	15p	AF139	32p	BF177	28p	OC45	12p	2N3710	11p
AC126	12p	AF178	32p	BF178	32p	OC70	12p	2N3711	11p
AC127	15p	AF180	40p	BF179	32p	OC71	12p	2N3819	32p
AC128	15p	AF181	40p	BF180	32p	OC72	12p	2N4062	12p
AC131	12p	BC107	12p	BF181	32p	OC81	12p	2N4286	20p
AC132	12p	BC108	12p	BF194	14p	OC82D	12p	2N4289	20p
AC176	15p	BC109	12p	BF195	14p	2N2646	60p	40360	35p
AC187	22p	BC147	12p	BF197	15p	2N2904	20p	40361	35p
AC188	22p	BC148	12p	BF200	32p	2N2926	10p	40362	40p
AD140	50p	BC149	12p	BFY50	20p	2N3054	58p	40408	40p
AD149	45p	BC157	14p	BFY51	20p	2N3055	60p	ZTX108	15p
AD161	33p	BC158	14p	BFY52	20p	2N3702	13p	ZTX300	15p
AD162	36p	BC159	14p	BUY105	20p	2N3703	12p	ZTX302	20p
AF114	20p	BC187	22p		£2.25	2N3704	13p	ZTX500	15p
AF115	20p	BD131	75p	OC26	45p	2N3705	12p	ZTX503	20p
AF116	20p	BD132	75p	OC28	50p	2N3706	11p		
AF117	20p	BD133	75p	OC35	50p	2N3707	12p		
AF118	38p	BF115	25p	OC42	12p	2N3708	10p		
AF126	20p	BF173	20p	OC44	12p	2N3709	11p		

ZENER DIODES

400mW 5% 3.3V to 30V, 12p. | WIRE WOUND POTS, 3W, 10, 25,
50Ω and decades to 100kΩ, 35p.

DIODES

DIODE RECTIFIER	1A	12p	SIGNAL	7p
BY127	1250V	1A	OA85	7p
BZY10	800V	6A	OA90	5p
BZY13	200V	6A	OA91	5p
IN4001	50V	1A	OA202	7p
IN4004	400V	1A	IN4148	8p
IN4007	1000V	1A	BA114	8p

BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2 1/2in = 10p; 9in x 2in = 7p

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.
SINGLE 10K, 25K, 100K log. or lin. 40p.
DUAL GANG, 10K + 10K etc. log. or lin. 60p.
KNOB FOR ABOVE 12p.
FRONT PANEL 65p.
18 Gauge panel 12in x 4in with slots cut for use
with slider pots. Grey or matt black finish com-
plete with fixings for 4 pots.

THERMISTORS

VA10555	15p
VA10665	15p
VA1077	15p
RS3	£1.35

THYRISTORS

2N5060 50V 0-8A 30p,
2N5064 200V 0-8A 47p,
CR51140 400V 1A 25p,
106F 50V 4A 40p, 106D
400V 4A 55p.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 2 1/2p. 0.0068µF, 0.01µF,
0.015µF, 0.022µF, 0.033µF, 3p. 0.047µF, 0.068µF, 0.1µF, 4p. 0.15µF, 6p. 0.22µF, 7 1/2p.
120V: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 3p. 0.1µF 3 1/2p. 0.15µF 4 1/2p.
0.22µF, 5p. 0.33µF, 6p. 0.47µF, 7 1/2p. 0.68µF, 11p. 1.0µF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01µF, 0.015µF, 0.022µF, 3p. 0.033µF, 0.047µF, 0.068µF,
3 1/2p. 0.1µF, 4p. 0.15µF, 0.22µF, 5p. 0.33µF, 6 1/2p. 0.47µF, 8 1/2p. 0.68µF, 11p. 1.0µF, 13p.
1.5µF, 20p. 2.2µF, 24p.

MYLAR FILM CAPACITORS 100V

0.001µF, 0.002µF, 0.005µF, 0.01µF, 0.02µF,
2 1/2p. 0.04µF, 0.05µF, 0.068µF, 0.1µF, 3 1/2p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD O15/6/7

(µF/V) 1/63, 1/5/63, 2/2/63, 3/3/63, 4/7/63, 6/8/40, 6-8/63, 10/25, 10/63, 15/16, 15/40,
15/63, 22/10, 22/25, 22/63, 33/6/3, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6/3, 68/16,
100/4, 100/10, 100/25, 150/6/3, 150/16, 220/4, 220/6/3, 220/16, 330/4, 330/16, 330/40,
150/25, 220/25, 330/10, 470/6/3, 7p. 68/63, 150/40, 220/40, 330/16, 1,000/4, 10p. 470/10,
680/25, 11p. 100/63, 150/63, 220/63, 1,000/10, 12p. 470/25, 680/16, 1,500/6/3, 13p.
470/40, 680/25, 1,000/16, 1,500/10, 2,200/6/3, 18p. 330/63, 680/40, 1,000/25, 1,500/16,
2,200/10, 3,300/6/3, 4,700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

0.1µF	35V	2.2µF	35V	22µF	16V	12p
0.22µF	35V	4.7µF	35V	33µF	10V	
0.47µF	35V	6.8µF	25V	47µF	6.3V	
1.0µF	35V	10µF	25V	100µF	3V	

VEROBOARD

0-1	0-15
2 1/2 x 3 1/2	22p
2 1/2 x 5	24p
3 1/2 x 3 1/2	24p
3 1/2 x 5	27p
17 x 2 1/2	75p
17 x 3 1/2	100p
17 x 5 (plain)	82p
17 x 3 1/2 (plain)	60p
17 x 2 1/2 (plain)	42p
2 1/2 x 5 (plain)	12p
2 1/2 x 3 1/2 (plain)	11p
Pin insertion tool	52p
Spot face cutter	42p
Sph. 50 pins	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p. Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable 22p/metre.

BATTERY ELIMINATOR

£1.50
9V mains power supply. Same size as PP9 battery.

LARGE (CAN) ELECTROLYTICS

1600µF	64V	74p	2500µF	64V	80p	4500µF	16V	50p
2500µF	40V	74p	2800µF	100V	£2.60	4500µF	25V	£1.68
2500µF	50V	58p	3200µF	16V	50p	5000µF	50V	£1.10

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01µF	10p	0.047µF	13p	0.22µF	20p
0.022µF	12p	0.1µF	13p	0.47µF	22p

POLYSTYRENE CAPACITORS 160V 2 1/2p.

10pF to 1,000pF E12 Series Values 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.
Detector GDI, £2. Kit of parts for detectors including GDI and P.C. board but excluding case. Mains operated detector £5-20. 12 or 24V battery operated audible alarm £7-30. As above for PP9 battery, £6-40.

PRINTED BOARD MARKER

Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

LARGE RANGE ITT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

1-11	12-24	25-99	100+	7448	185	175	170	165	74118	100	82	73	64
7400	P	P	P	7450	18	16	14	13	74121	43	40	38	36
7401	18	16	14	7451	18	16	14	13	74141	100	95	90	85
7402	18	16	14	7453	18	16	14	13	74145	150	140	135	130
7403	18	16	14	7454	18	16	14	13	74150	330	280	250	220
7404	20	18	16	7460	18	16	14	13	74151	110	100	95	89
7405	20	18	16	7470	30	28	25	24	74153	120	110	105	95
7406	50	45	40	7472	30	28	27	23	74154	200	180	170	160
7407	50	45	40	7473	40	38	36	30	74155	150	120	100	96
7408	36	30	27	7474	40	36	32	28	74156	130	120	100	96
7409	36	30	27	7475	35	32	30	28	74180	155	136	112	105
7410	18	16	14	7476	40	36	32	30	74190	195	190	185	180
7411	23	21	20	7480	100	95	90	85	74191	195	190	185	180
7412	36	30	27	7481	125	115	110	105	74192	200	190	180	164
7413	34	28	26	7482	100	96	90	85	74193	200	180	170	150
7416	45	43	39	7483	100	97	95	92	74196	200	190	180	170
7420	18	16	14	7484	120	115	110	105	74197	200	195	180	170
7421	36	30	27	7485	250	245	240	230					
7426	32	29	23	7486	45	42	37	33					
7430	20	18	16	7490	75	67	60	52					
7432	40	36	32	7491A	100	92	85	79	709	14 pin DIL			40p
7440	20	18	16	7492	75	70	65	60	741	8 pin DIL			40p
7441	80	75	70	7493	75	68	60	52	741	14 pin DIL			38p
7442	80	75	70	7494	95	90	85	80	723	14 pin DIL			95p
7443	125	120	115	7495	105	100	95	90	747	14 pin DIL			85p
7447	17												

P.E. RONDO

FULL SPECIFICATION KITS

Complete designer approved kits. Full data and even solder included. Top quality PCBs and components.

- * **CBS-SQ MATRIX DECODER**
£8.00 Post Free + 80p VAT
- * **PRE-AMP BOARD, COMPLETE**
£3.00 Post Free + 30p VAT
- * **MASTER VOL/TONE/BAL. BD.**
£8.50 Post Free + 85p VAT
- * **POWER AMP BOARD + HEAT-SINK**
£7.50 Post Free + 75p VAT
- * **POWER SUPPLY BOARD**
£5.00 Post Free + 50p VAT
- * **MAIN SMOOTHING CAPS**
£0.75 Post Free + 7p VAT
- * **MAINS TRANSFORMER**
£6.25 Post Free + 62p VAT
- * **PUNCHED CHASSIS**
£2.25 Post Free + 22p VAT

PHASE LOCKED LOOP STEREO DECODER

EASY TO BUILD!
(Approximately 30 mins.)

- EMPLOYS MC1310 IC
- REQUIRES 10-15v d.c.
- NO INSTRUMENTS NEEDED TO SET UP
- SIMPLE INSTRUCTIONS SUPPLIED

COMPLETE KIT £3.40

Plus 34p VAT

AUTOMATIC BEACON FITTING

34p + 3p VAT Extra

All other items will be offered as published
TRADE GLADLY SUPPLIED

STUDIO ELECTRONICS

P.O. BOX No. 18, HARLOW, ESSEX CM18 6SH

Telephone: Harlow (02796) 25457

ORDER—PLEASE SEND

- | | | |
|----------------|--------------------------|----------|
| CBS-SQ DEC. | <input type="checkbox"/> | ENCLOSED |
| PRE-AMP | <input type="checkbox"/> | |
| MASTER VOL. | <input type="checkbox"/> | £..... |
| POWER AMPS | <input type="checkbox"/> | CHEQUE |
| (2 for RONDO) | <input type="checkbox"/> | P.O. |
| POWER SUPPLY | <input type="checkbox"/> | M.O. |
| CAPACITORS | <input type="checkbox"/> | |
| TRANSFORMER | <input type="checkbox"/> | |
| CHASSIS | <input type="checkbox"/> | |
| STEREO DECODER | <input type="checkbox"/> | |

NAME

ADDRESS

PEI

UNDERSTANDING SOLID-STATE ELECTRONICS

Basic course in semiconductor theory, Texas Inst. Price £1.40

104 EASY TRANSISTOR PROJECTS YOU CAN BUILD by R. M. Brown. Price £1.30.

INTEGRATED CIRCUIT POCKET BOOK by R. G. Hibberd. Price £2.60.

HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER by P. J. Guy. Price £1.60.

50 PHOTOELECTRIC CIRCUITS AND SYSTEMS by P. S. Smith. Price £1.35.

COLOUR TV WITH PARTICULAR REF. TO PAL SYSTEM by G. N. Patchett. Price £3.10.

GETTING STARTED WITH TRANSISTORS by L. E. Garner. Price £1.30.

TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard. Price £1.90.

FOUNDATIONS OF WIRELESS AND ELECTRONICS by M. G. Scroggie. Price £2.00.

THE RADIO AMATEUR'S HANDBOOK 1973 by A.R.R.L. Price £2.95.

BEGINNER'S GUIDE TO PRACTICAL ELECTRONICS by R. H. Warring. Price £1.60.

ELECTRONIC ORGAN SERVICING GUIDE by R. G. Middleton. Price £2.40.

ALL PRICES INCLUDE POSTAGE

THE MODERN BOOK CO.


BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-723 4185

Closed Saturday 11p.m.

INTER-LOCKING PLASTIC STORAGE DRAWERS

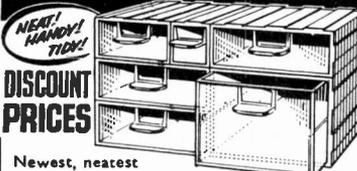

NEARLY HANDED!
DISCOUNT PRICES

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/1D and 2D have removable space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins). £1.40 DOZEN.

DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins). £2.30 DOZEN.

TREBLE (3D) £2.50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £3.60 for 8, **EXTRA LARGE SIZE (6D1)** £3.40 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £10 and over DEDUCT 5% in the £
Orders £20 and over DEDUCT 7½% in the £
Orders £50 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES

Please add 10% V.A.T. to total remittance

(Dept. PE12) 124 Cricklewood
Broadway, London, N.W.2
Tel. 01-450 4844

FLAIR SUPPLIES


SINCLAIR EQUIPMENT



- | | | |
|---------------------------|----------------|----------------|
| Project 60 FM Tuner | 415-95 (£1.85) | |
| 2 Z30/Stereo 60/PZ5 | 416-75 (£2.05) | |
| 2 Z30/Stereo 60/PZ6 | 418-85 (£2.25) | |
| 2 Z50/Stereo 60/PZ8/Trans | £23.20 (£2.70) | |
| Z30 £3.50 (55p) | Stereo 60 | £7.80 (98p) |
| Z50 £4.30 (63p) | Trans for PZ8 | £2.95 (50p) |
| PZ5 £3.47 (57p) | 2000 Amp | £2.95 (£2.70) |
| PZ6 £6.30 (83p) | 3000 Amp | £31.50 (£3.35) |
| AFU £4.40 (64p) | 2000 Tuner | £27 (£2.90) |
| PZ8 £6.40 (84p) | 3000 Tuner | £27 (£2.90) |
| Q16 £3.90 (79p) | Project 605 | £20.98 (£2.40) |

PROJECT 60 KIT £2.70 (49p)
Our extremely popular kit contains the extra capacitors, din plugs and sockets, cable and fuse-holder needed to complete Project 60.

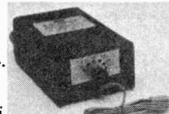BATTERY ELIMINATOR BARGAIN £3.60 (58p)
Introducing the most versatile battery eliminator ever offered with a high current output that makes it suitable for operating most battery tape recorders, record players, cassette recorders and shavers. Input 200/240V. Output voltage selected by front panel switch may be set to 3V, 4.5V, 6V, 7.5V, 9V and 12V, at 500 mA.



IC RADIO CHIP TBA631 £2.10 (32p)
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2.10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors, and IF filters is available to go with the chip for £1.75 (29p).

S-DECS AND T-DECS

S-DECS £1.44 (25p)

T-DECS £2.88 (40p)


µ-DEC A £3.18 (43p)

16 dit IC carriers £1.20 (17p)



SINCLAIR SUPER IC12 £2.10 (43p)

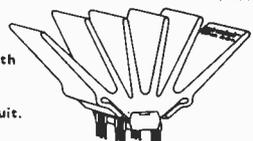Supplied complete with free 44-page instruction booklet and printed circuit.



DELUXE KIT FOR THE IC12
Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.53 (26p). Stereo model with balance control £3.50 (46p).

BASIC KITS FOR THE IC12
Contains components for P.C. board and volume and simple tone controls. Mono version £1.25 (24p). Stereo model with balance control £2.90 (40p).


IC12 POWER KIT
A set of components to construct a 28V 0.5A power supply £2.47 (50p).

LOUDSPEAKERS FOR THE IC12
5in 8 ohm £1.10 (27p). 5in x 8in 8 ohm £1.55 (37p). 10in x 6in 15 ohm £2.20 (44p).

PREAMPLIFIER KITS FOR THE IC12
Type 1 for magnetic pickups, mics and tuners, with 3 position equalization switch. Mono model £1.30 (24p). Stereo model £2.30 (34p). Type 2 for ceramic or crystal pickups. Mono 60p (17p). Stereo £1.20 (23p).

SEND S.A.E. FOR FREE LEAFLET ON KITS

SINCLAIR EXECUTIVE CALCULATOR

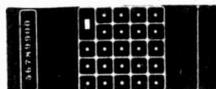

Now only £34.95 (£3.70)

SWANLEY ELECTRONICS

32 Goldsel Road, Swanley, Kent

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Mail order only. No callers, please.

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

PSU PROTECTION

WHEN using a regulated PSU to reduce a supply voltage there is always the danger of component failure in the PSU and consequent damage to the equipment. A fuse will protect equipment when an excess of current is drawn but might be too slow to cope with overvoltage conditions.

In Fig. 1 the values shown suit a car battery supply being used to drive a battery tape recorder at 7.5V. The load requirement is 300mA and the trip voltage was set to 8V to protect the recorder in the event of regulator fault.

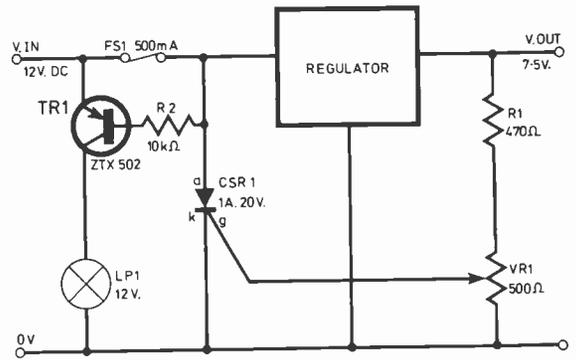


Fig. 1. Power supply protection circuit

R1 and VR1 form a potential divider which samples the output voltage as set by adjustment of VR1. The CSR1 is selected to carry at least twice the fuse rating. The full supply voltage is connected to the input of the regulator.

Transistor TR1 is held biased off by R2 and CSR1 so that the lamp LP1 is held off. If the output voltage rises above a set trip value then CSR1 will conduct, FS1 will blow and TR1 will be supplied with base current via R2 and the lamp will light up.

J. Sadler,
Cheshire.

R/C SERVO AMPLIFIER

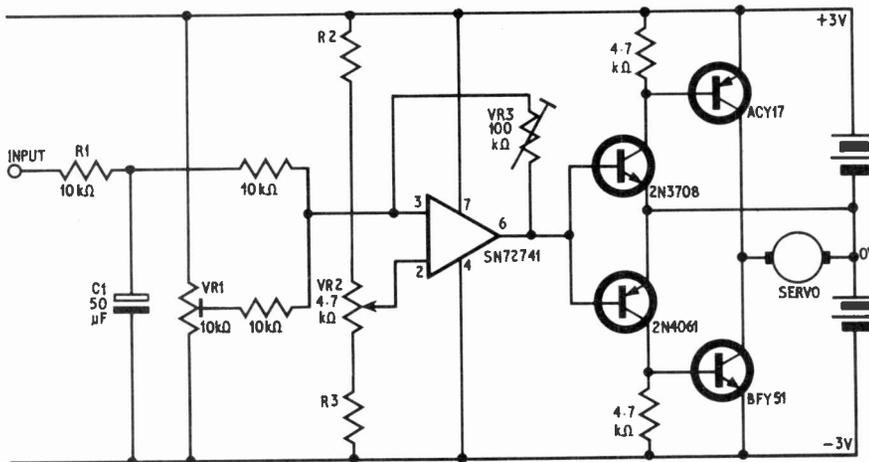


Fig. 1. Circuit diagram for the servo amplifier

A DIGITAL proportional decoder was published in the series *Logical Radio Control* (no issues available) and I have developed the following servo amplifier to go with such a device, see Fig. 1. Using a 741 operational amplifier for compactness, the circuit accepts the positive-going pulses, of variable length, from the decoder. These are integrated by R1 and C1 to give a d.c. which, using my decoder, varies from +0.2 to +1.2V.

Potentiometer VR1 is adjusted to give a value equivalent to minus the centre voltage at its wiper. In my case this is -0.7V. The 741 is used as a summation amplifier.

If VR3 is set at 10kΩ so that the gain of the 741

is unity, then the output will be $1.2-0.7V = +0.5V$ at one transmitter control extreme and $0.2-0.7V = -0.5V$ at the other. In fact, the gain is set so that the output swings $\pm 3V$.

The transistors form a current amplifier to drive the servomotor and feedback from the motor is provided via the potentiometer VR2 which is ganged to the motor. The deadband of the servo may be controlled by varying VR3 and when the optimum value is found replacing with a fixed resistor.

The values of R2 and R3 are found by experiment.
P. Skan,
Sutton Coldfield.

CAR LIGHTS MONITOR

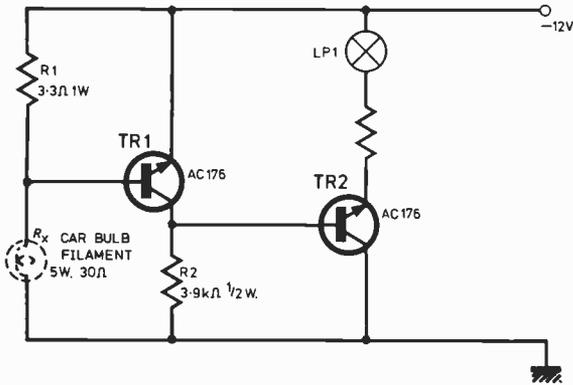


Fig. 1. Circuit diagram of the car lights monitor

PERHAPS the enclosed circuit of a car light monitor would be of interest to some of your readers. The circuit, Fig. 1, was designed to indicate the presence of a bulb failure in either the two front side lights or the two rear lights (the number plate light could also be included).

The 3.3Ω resistor R1 makes no visible difference to the bulbs light output as only approximately 1V is dropped across it. When the bulb filament R_x goes open circuit there is no forward bias to TR1 and its collector voltage rises and turns TR2 hard on, illuminating the indicator bulb LP1.

The circuit as shown will operate on positive earth cars; for negative earth cars *pnp* transistors, such as the AC128, should be used. The connecting details are shown in Fig. 2.

A wide variety of bulbs can be used in the LP1 position as long as the ratings of TR2 are not exceeded. The prototype used 6V 0.1A bulbs with 33Ω ballast resistors.

I. K. Staley,
Mansfield,
Notts.


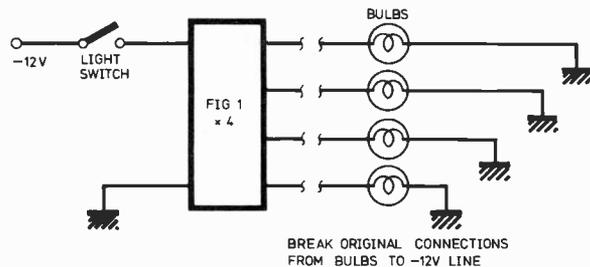


Fig. 2. Showing how the circuit is connected into the car wiring. The circuit in Fig. 1 is repeated for each light to be monitored

NEXT MONTH...

PARTY STROBE LIGHT

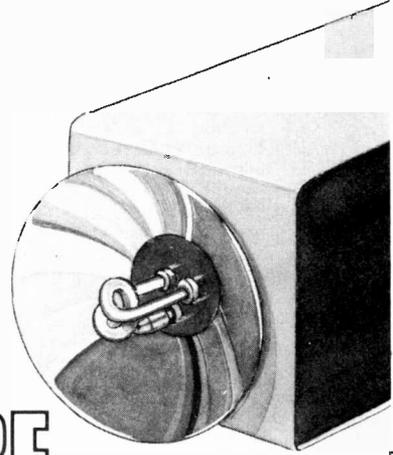

Have fun with the Party Strobe!
An easy-to-build, low cost medium power stroboscope which will amuse your friends at parties or discotheques.

VOICE OPERATED FADER

Run a super-efficient Disco—when you speak the music fades and when you stop it comes back up.

Ideal for the tape enthusiast who wants to add commentaries to his recordings.

PE BORDO

PART FOUR

PRACTICAL ELECTRONICS

DECEMBER ISSUE ON SALE NOVEMBER 9, 1973

SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT. NEW & SECONDHAND MUSICAL INSTRUMENTS. DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES

Announcing our improved range of constructor modules

FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A "Plastic Power" Driver Transistors now available.

To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.



SA35 35W RMS uses 7 transistors and 7 diodes. Carr. paid. **£4.45**

A NEW ADDITION IS THE

SA50 at £5.65

Carr. paid. A rugged, well built unit, capable of 50W RMS out, with all the advantages of Saxon Amplifier design and quality. Ready now.

SA100 makes an ideal unit in disco assemblies

A real glutton for work. Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid.

£10.90

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000Hz ± 1dB	All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in its SA100
Distortion	0.2% at 1kHz	
Loads	4 to 16 ohms	
Quiescent current	15mA	
Noise	Better than -75dB	
Supply voltage	SA35-45V SA50 45/65V SA100 40-70V	
Size	4 1/2 in x 4 in x 1 in (SA100) 4 in x 3 in x 1 in (SA35/SA50)	

Circuits, connecting instruction and application data are supplied free with all modules.

POWER SUPPLIES

FOR THE SA35, SA50 AND SA10 POWER AMPS. ABOVE

PU45	Unstabilised supply for 2 SA35's	£4.90
PU70	Unstabilised supply for one or two SA50 or SA100	£7.75 carr. 40p
PS45	Stabilised module for two SA35's	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted	£3.50 carr. 20p
PS70	Stabilised supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED

SAXON PA MIXER-CONTROL UNITS


In extra slimline easy-fit case.

Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master controls. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos, etc. Standard jack sockets, compact design. In strong metal cases. All Units guaranteed for 3 years.

● **HIGH AND LOW IMPEDANCE INPUTS**

● **BASS/TREBLE/VOLUME ON EACH PAIR**

● **MASTER CONTROL ON OUTPUT**

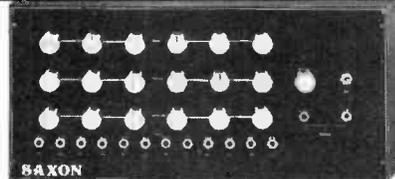

M4H

4 high Z, 4 low Z inputs, 4 sets of controls. Case 10" x 8" and only 2 1/2 in deep. Carr. paid. **£18.50 + V.A.T.**

● **M6HL**

12 inputs (6 high Z, 6 low Z) 18" x 8" x 2 1/2". Carr. paid **£27.50 + V.A.T.**

Channel section modules, for building your own; gain—16 x (24dB). Tone controls—18dB swing. Carr. paid. **£3.50 + V.A.T.**

CONTROL UNITS

Mono (as shown). **£6.50**

Carr. 20p.

For 9 v. battery operation.

As stereo model, less mic. input.

Stereo. **£15.80**

Carr. 30p.



Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2 in x 3 in x 4 in deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass treble, mains on/off. **COMPARABLE TO UNITS AT OVER TWICE THE PRICE.**

PLEASE ADD 10% FOR V.A.T. TO TOTAL VALUE OF YOUR ORDER

S.A.E. brings Saxon equipment and bargains list

● 160 watts version with power supply **£27.90** (Carr. 50p)

120 W HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.

SPECIFICATION

Power output, 120W into 8 ohms
Freq. response, 20-20,000Hz ± 2dB
Input sensitivity, 200mV into 10K
Construction, Fibreglass board
Size, 8 in x 4 in x 4 in (5 in with supply)
Low distortion parallel push-pull output stage.

Module and power supply **£18.95** (Carr. 40p)

Another Saxon winner!

SOUND AND LIGHT UNITS



3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls, 2 amplifier sockets eliminate need for split leads. Up to 3kW lighting load. Smartly finished steel case. **£19.75** Carr. 30p.

SINGLE CHANNEL UNIT

Operates from 5-100W amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p. Carr. pd. **£8.90**

COMPLETE AMPLIFIERS

CSE 100 £34.90 carr. free

This versatile unit is now available in a black vynid case and so represents even better value than ever delivering speech and music powers of up to 100W RMS and continuous signal outputs of 70W. Two individually controlled inputs with wide range bass and treble controls.

SAXON 100 £48.50 carr. free



With an RMS output of 120W speech and music, 100W continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains!!

12 in 25W 8/15 ohms £5.95 carr. 30p. 15 in 50W 8/15 ohm £14.50 carr. 50p. 12 in 40W 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p. 600 Watt 3 colour Light Boxes Smart Rexine finish £15 carr. free.

Order and personal shoppers to:

SAXON ENTERTAINMENTS LTD., 329 Whitehorse Road, W. Croydon, Surrey CR0 2HS

Telephone 01-684 6385


From 9.30 a.m.-5.30 p.m.

Prices quoted do not include V.A.T. 10% must be added on to total value of order for V.A.T.

TRADE AND EXPORT ENQUIRIES INVITED

TERMS OF BUSINESS

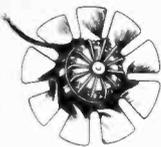Cash with order (C.W.O.). For C.O.D. please add 35p extra, cash by regd. letter please.



FAN/BLOWER

Precision-built in Germany. Dynamically balanced mains unit (200/240) continuous rated, reversible 60mA on run. Size: 5 1/2" dia. x 2 1/2" deep. Back plate is tapped for 4 fixing screws (supplied). Well under maker's price at £3. P. & P. 20p. Similar unit to above but 7 1/2" dia. x 3" deep. £4.50. P. & P. 25p.

SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1 min. divisions, approximately 1/2" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.30. P. & P. 15p.

GEARED MOTORS


"Parvalux" Reversible 100 rpm geared motor. Type SD14, 230/250V a.c., 22 lb/in. 1/2" spindle. First class condition. £7.50 each. P. & P. 50p. Also limited number only as above. BRAND NEW. £12.50 each. P. & P. 50p.

REVERSIBLE Parvalux type SD19. 240V a.c. 30rpm. 40 lb/in. Variable angle drive shaft. ABSOLUTELY AS NEW. £6.30. P. & P. 50p.

SHADED POLE Mains motor, 1 1/2" x 1 1/2" x 2" high. Double ended 1/2" shaft projecting 1 1/2" each side of motor. £1. P. & P. 20p.


OPEN FRAME shaded pole GEARED MOTORS

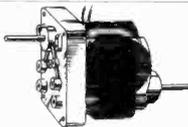(Dural gear case) 240 a.c., 28rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 3 1/2" + spindle 1" dia. as illustrated. £2.70. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.



SPIT MOTOR

5 1/2rpm. 2 1/2" x 1 1/2" x 6 1/2" high. 240V a.c. Shaft 1/2" o/d, 1 1/2" length with hexagon socket inside. £1.80. P. & P. 30p.

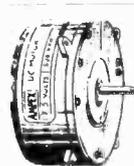

AMPEX 7.5v. DC MOTOR

This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 4500MCM. Stall load at 500mA. Draws 60mA on run. 600rpm = speed adjustment. Internal AF/RF suppression. 1" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. OUR (special quotations). P. & P. 25p. Large quantities available. 75p each. P. & P. FREE.

PRICE £3. P. & P. 25p. Large quantities available. 75p each. P. & P. FREE.

"DAVENSET" MAINS SOLENOID 1" travel, 8lb pull (approx.). Size: 2 1/2" long x 2 3/16" x 2" high. Similar in appearance to "SORENG". £1.50 P. & P. 20p.

MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V a.c. Pull at coil is approximately 1lb. £1. P. & P. FREE. Special quotes for quantities.



SOLENOIDS by WESTOOL

240 a.c. type MM6. 3lb. pull. 2 1/2" x 1 x 1 1/2". Travel 1". 85p each. P. & P. 10p.



240 a.c. type MM4. 2lb. pull. 1 1/2" x 1 1/2" x 1". Travel 1". 60p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



"DECCO" MAINS SOLENOID

Compact and very powerful. 16lb. pull. 1/2" travel which can be increased to 1" by removing captive-end-plate. Overall size: 2" x 2 1/2" x 2 1/2" high. £2. P. & P. 20p.



MAINS SOLENOID by MAGNETIC DEVICES LTD.

A beautifully constructed solenoid at half normal price. A 2-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1 1/2" x 1 1/2". Pull is approximately 2lb, plunger travel 1 1/2". Fixing eye takes up to 1/2" bolt, plunger non-captive. NEW in original maker's boxes. £1. P. & P. 20p. Large number available, special price for quantity.

"CROUZET" MOTORS Type 965

115/240V. 50Hz. 48W. Stoutly constructed. 2 1/16" dia. x 3 1/2" long plus spindle 1" x 1/2" dia. Anti-clock. £3 each. P. & P. 25p.



"RE CIRK IT" Mains 10amp cut-out

by "Neimman Electric" Germany. Eliminates fuses. Size: 2" x 1" x 1 1/2" deep. 90p each. P. & P. 10p. 10 or more 70p each. P. & P. 20p.



UNLESS OTHERWISE STATED

all items are NEW and UNUSED. Postal or carriage charges are for Gt. Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50. C.W.O., please. Company orders under £2.50, surcharge 60p, unless C.W.O.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging devices, etc. Size (60 DB) 7/32" x 5/32" x 1". (80 DB) 1" x 5/32" x 3/8". Equipment, all tested. £1.20 each. P. & P. FREE.

PLUG-IN RELAYS by SCHRACK (Perspex enclosed)

OCTAL (2e/o) 8 amp contacts at following voltages: 48 d.c., 60 d.c., 110 d.c., 110 d.c., 380 a.c.

PRICE EACH 80p.
11 pin (3 c/o) 8 amp contacts: 12 a.c., 48 d.c., 48 a.c., 60 a.c., 60 d.c., 110 d.c., 115 a.c., 240 a.c. PRICE EACH £1.

RA and RN Series (4 c/o) 3 amp Gold Plated Contacts. Handsome modern construction 1/2" x 1" x 1 1/2" high. Following voltages: 6 a.c., 12 a.c., 24 a.c., 48 a.c., 48 d.c., 60 a.c., 110 d.c., 115 a.c., 120 a.c. PRICE EACH 80p.

Base sockets for all above types 10p. Please add 10p towards P. & P. on all orders.

From JAPAN. TAKAMISAWA Perspex enclosed relays. Type MQ308 24V d.c. 600 ohms (4 c/o). Complete with base socket. 80p. P. & P. 10p.



SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!

A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3 amp at 120V, 1 1/2 amp at 240V. Size: (approx.) 1 1/2" long x 1" dia. Ideal for burglar alarms, security systems, etc. and wherever non-mechanical switching is required. 10 for £1.80. P. & P. 10p; 50 for £8; 100 for £15. P. & P. FREE over 10.




NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass base of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant, ideal for P.C.'s, etc. THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Sizes: 12" x 12", 24" x 12", 24" x 24", FULL SHEET 43" x 37" (11 sq. ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq. ft. Cut sizes (1-10 sq. ft. P. & P. 25p. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

TANGENTIAL HEATER

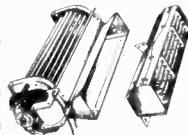Silently driven by shaded pole Mycalex motor, powerful and smooth running with aluminium impeller (outlet 5 1/2" x 1 1/2"). Mains voltage PLUS matching heater unit with spiral element. May be switched for 500 or 1,000W. £1.80. P. & P. 30p.



PLEASE ADD 10% FOR V.A.T. ON ALL PRICES SHOWN INCLUDING P. & P.

ELECTRO-TECH COMPONENTS LTD.

315/317 EDGWARE ROAD LONDON, W.2
Tel. 01-723 5667 01-402 5580



AMAZING MINI-DRILL

FOR PRECISION MODEL WORK



+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £6.35 p.p. 13p. De Luxe Professional Kit with 17 tools £9.40 p.p. 23p. Prices include V.A.T.

Money ref. g'tee. MERLIN SUPPLY CO.

Dept. PE1173, Nailsea, Bristol BS19 2LP

ELECTRONIC DETECTOR for


GAS & SMOKE

COMPLETE MAINS OPERATED parts kit & flush or surface mounting box £8.45 R & P 20p. parts available separately;


T G S 105 sensor..... £1.80 R & P 10p.
Transformer..... £1.50 R & P 20p.
P C B and circuit diagram..... £0.55 R & P 10p.

PLEASE ADD 10% VAT TO THE ABOVE

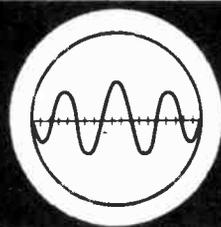
ELECTROMECH Ltd, Ruckinge, Ashford, Kent TN26 2EF



TUAC

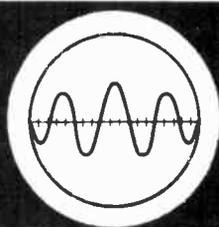

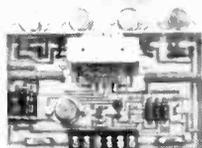NEW TUAC POWER MODULES. Now in their second successful year offering more power and quality than ever before.



TP100 ★ 125 Watts RMS continuous sine wave output
 Illustrated ★ 4 RCA 150 Watt 15 Amp output transistors
£15.25 ★ Special layer wound driver transformer
 ★ Short, open, and thermal overload protection
 ★ Compact size: 7 x 6½ x 3 in.




TL100 ★ 100 Watts RMS sine wave
 Illustrated ★ 2 RCA 15 Amp output transistors
£11.50 ★ Rugged transformer driver
 ★ Full thermal overload protection
 ★ Compact size: 5 x 5 x 3 in.

TL60 ★ 60 Watts RMS sine wave
£9.75 ★ RCA 115 Watt output transistors
 ★ Only six connections to make
 ★ Same size as TL100

Specification on all three power modules :
 All output power ratings ±1dB. Output impedance 8-15 Ohms. THD at full power 1% typically 0.5%.
 Input sensitivity 60mV into 10kΩ. Frequency response 10Hz-25kHz ±2dB. Hum and noise better than -75dB.

Power supplies vacuum impregnated Transformers with supply board incorporating stabilised pre-amp supply :

PS 125 ±50 volts for one TP100	£8 75
PS 100 ±45 volts for one TL100	£8 00
PS 60 ±40 volts for one TL60	£6 75
PSU 2 For supplying Disco Mixer	£3 50

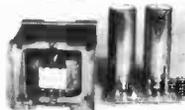

PRE AMPLIFIERS

All Tuac audio modules are constructed on glass fibre P.C. board, are ready assembled and fully tested. Low noise silicon and FET transistors together with H.S. carbon film resistors are used throughout. Extensive research has gone into the various wide range tone control circuits, producing superb sound quality from any signal. Previous range still available. 40V d.c.; 60mV o/p.

VA08 Vol. Treb, Mid and Bass Controls. HI IMP. FET I/P. Suitable Mic, Guitar, Radio, Crystal/Ceramic P.U. Sensitivity 4mV. Treb +35dB at 16kHz, Mid +20-15dB at 1kHz, Bass +20-10dB at 40Hz. **£4.22**

VA06 Vol, Treb and Bass Controls. 8mV sensitivity. Treb +28-15dB at 12kHz, Bass ±18dB at 40Hz. **£3.72**

AMF01 Tuac Auto Fade Unit fades music when you speak. Auto Mic Over-ride for Disco use. Feed Deck and Mic Pre-amps in. Auto fade O/P to main Amp. 30mV operating level. Depth and Vol. Controls. **£4.40**


VA08 ILLUSTRATED



SIZE 6½" x 2" x 1"

ALL PRICES INCLUDE V.A.T. AND POSTAGE AND PACKING

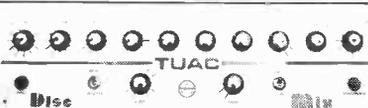ACCESS & BARCLAY CARDS ACCEPTED, JUST SEND US YOUR NUMBER. H.P. ARRANGED THROUGH PAYBONDS.



TUAC DISCOTHEQUE MIXER WITH AUTO FADE


Designed for the discerning D.J. of professional standard.

£22.50

Offering a vast variety of functions.

Controls: Mic Vol, Tone, Over-ride depth, Auto Manual Sw. Tape Vol, L & R Deck Faders, Deck Volume, Treb. & Bass. H. Phon Vol, Selector, Master Vol, on/off sw. Max. output 1V RMS. Specification as VA06. **PANEL SIZE 18" x 4½" DEPTH 3"**

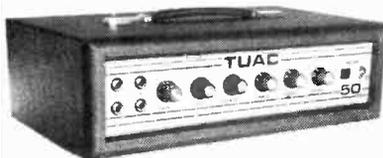TUAC HIGH POWER AMPLIFICATION—built to high standards, and built to last




50 WATT RMS SINE WAVE ALL PURPOSE AMPLIFIER

Suitable for Disco, PA, Guitar. 4 inputs, 2 volume controls. Master volume, treble, middle and bass controls. Rugged circuit, rugged leather-cloth covered case, short and open circuit protection. Tone control specification as VA08 pre-amp. **FULLY FUSED.**

50 WATT **£42.25**

100 WATT **£61.50**

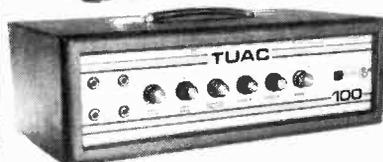

TUAC LIGHT MODULATORS

Constructed on glass fibre P.C. board, individually tested.

Three channel light modulator will control three separate sets of lights, up to 1000 Watts each set. One channel responds to the bass, one to the middle, and one to the high frequencies. Input sensitivity only 0.5 Watt! Three individual controls allow for adjustment of the three channels, and a master sensitivity control allows for input levels up to 100 Watts to be safely accommodated. Full interference suppression. Full wave control. Isolating input transformer does not affect Amplifier operation. Fully Fused.



3 Channel SILMB illus.


£17.45

SINGLE CHANNEL VERSION S2LMB

Increased capacity of 1800 Watts. Sensitivity control. Isolating input transformer does not affect amplifier operation.

S2LMB 1 Channel **£6.47**

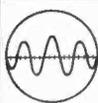MANUFACTURERS OF ELECTRONIC AND AMPLIFICATION EQUIPMENT
 SPECIALISTS IN QUALITY TRANSISTOR EQUIPMENT
 OPEN 6 DAYS A WEEK. 9.30 a.m. - 6.00 p.m.



TUAC

TRANSISTOR UNIVERSAL
 AMPLIFICATION COMPANY LTD.
 163 MITCHAM ROAD, LONDON SW17 9PG
 01-672 3137/9080

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s simplified study method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.


You LEARN—but it’s as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

Specialist Booklet

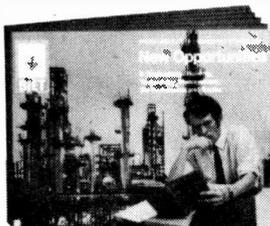If you wish to make a career in Electronics, send for your FREE copy of “NEW OPPORTUNITIES”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. BPE21 ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

CL BPE21

NAME (BLOCK CAPITALS) AGE.....

ADDRESS.....

SUBJECT OF INTEREST.....

FM TUNER

NELSON-JONES

PUSH BUTTON VARICAP

Tuning now available.

Six Position variable push button unit with individual frequency scales. Teak case and full metalwork matches the Texan amp.

Approved parts of this outstanding design. Featuring 0.75μV sensitivity. Mosfet front end. Ceramic I.F. strip. Triple gang tuning. S.A.E. please for lists.

PE RONDO

We are kit stockists for this excellent design

LIGHT EMITTING DIODES

RED only 29p each 10 + 23p

GREEN only 69p each 10 + 59p

7 SEGMENT LED DISPLAY

0.325in Characters 0-9 and nine letters. TTL, DTL compatible. ONLY £2.46 each, p.p. 10p.

Please add 10% V.A.T. for U.K. orders.

INTEGREX LIMITED, DEPT. P.E.

P.O. BOX 45, DERBY DE1 1TW


Tel.: Repton (0283 89) 3580

All items advertised in previous numbers of this magazine still available.



4 1/4 in x 3 1/4 in METER. 30μA, 50μA or 100μA, £2.86.

TAPE RECORDER LEVEL METER 500μA, 55p

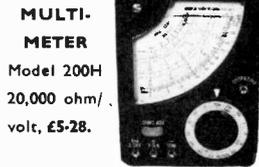


MULTI-METER Model 200H 20,000 ohm/volt, £5.28.



CARDIOID DYNAMIC MICROPHONE

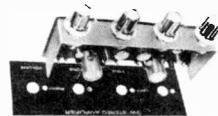Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £4.95.



3 WATT STEREO AMPLIFIER £4.30

All above prices include 10% V.A.T. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 6. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

COMPLETE TELEPHONES



EX G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY £1.05
POST & PACKING 45p EACH



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 27½p
POST & PACKING 16½p

TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	55p
B81	10	Reed Switches, 1" long dia. Highspeed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight Post & packing 15p.	55p
H4	250	Mixed Resistors. Approx. quantity counted by weight Post & packing 15p.	55p
H7	40	Wirewound Resistors. Mixed types and values	55p
H9	2	OCP71 Light Sensitive Photo Transistor	55p
H28	20	OC2001/1/2/3 PNP Silicon uncodded TO-5 can	55p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6.8-43V	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	55p
H38	30	Short lead Transistors, NPN Silicon Planar types	55p
H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945	55p
H40	20	BFY 50/2, 2N696, 2N1613, NPN Silicon uncodded TO-5	55p
H41	2	BD131/BD132 Complementary Plastic Transistors	55p

UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	55p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	55p
H20	20	BY1267 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	55p

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1.10 each



OVER
1,000,000

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

SILICON PLANAR PLASTIC TRANSISTORS

Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc.

Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9, etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 500 for £3.30, 1,000 for £5.50, 10,000 for £44.

P & P 11p per 1,000

OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.
TYPE "H" PNP Silicon, similar ZTX500 range.

8 RELAYS FOR 8 VARIOUS TYPES P & P 27½p £1.10

Our famous PI Pak is still leading in value for money

Full of Short Lead Semiconductors and Electronic Components, approx. 170.

We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P-1. Only 55p. 11p P & P on this Pak.



A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This was a project in the September 1972 edition of Television.

This complete kit of parts costs £3.85, post paid.

A MUST for Colour T.V. Alignment.

Electronic Transistor Ignition

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features: Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility. This project is a "star" feature in the September edition of "Electronics Today International" magazine. Our kit is recommended by the ETI magazine.

Complete kit including P. & P. £7.92 Ready built & tested unit £3.02 EXTRA

FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

PLASTIC POWER TRANSISTORS

NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shattering low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1 VCE Min. 15 HFE Min. 15

40 watt 1-12 13-25 26-50

90 watt 22p 20p 18p

Range 2 VCE Min. 40 HFE Min. 40

40 watt 1-12 13-25 26-50

90 watt 33p 31p 29p

38p 36p 33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

INTEGRATED CIRCUITS. We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16½p each } Now new low
16 pin type at 18p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:
B.P.I. Transistor Equivalents and Substitutes 40p
This includes many thousands of British, U.S.A., European and C.V. equivalents.
The Iliffa Radio Valve & Transistor Data Book 9th Edition: P & P 23½p 75p
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.
Send for lists of publications.

N.B.—Books are void of V.A.T.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

ALL PRICES INCLUDE 10% V.A.T. MINIMUM ORDER 55p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE. BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co. Reg. No. 820919

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

THE D·Y ELECTRONICS KIT FOR STUDENTS, TECHNICIANS AND HOBBYISTS

Now available from all leading electrical shops, the complete D-I-Y printed circuit kit. Save time and money with this latest development by GSPK in the field of home electronics.



Standard Printed Circuit Kit contains six sheets of 6" x 4" copper laminate, etchant, etching dish, tweezers, etchant measure and retails at **£4.95** including VAT plus postage and packaging -30p.



We recommend that you use the Standard Printed Circuit Kit in conjunction with the GSPK PCB Marking Pen specially designed for drawing fine line etchant resistant circuits on copper laminate. Recommended retail price including VAT is **£1.35** plus postage and packaging -15p.

The GSPK Signal Booster is designed to improve car radio reception in towns and built-up areas. It's also claimed to eliminate any loss of signal caused by rear mounted aerials with long leads. The solid state unit is plugged into the aerial lead and takes its power supply from the car battery. Is manufactured in positive and negative earth versions and costs **£3.29** including VAT plus postage and packaging -15p.



Our products are available from all leading electrical stores or write direct to-

gspk
(Sales) Limited.

Hookstone Park, Harrogate, Yorkshire HG2 7BU



NORTH AMERICAN SEMICONDUCTOR COMPANY LIMITED

TRANSISTORS

2N696	0-150	2N2219A	0-270	2N3108	0-540	2N3636	0-120	2N4135	1-500	2N5132	0-080
2N697	0-160	2N2221	0-190	2N3109	0-540	2N3636A	0-130	2N4140	0-270	2N5133	0-080
2N699	0-340	2N2221A	0-230	2N3110	0-540	2N3639	0-200	2N4141	0-290	2N5134	0-080
2N706	0-100	2N2222	0-190	2N3117	0-850	2N3640	0-200	2N4142	0-310	2N5135	0-090
2N708	0-145	2N2222A	0-245	2N3120	0-540	2N3641	0-200	2N4143	0-320	2N5137	0-100
2N718	0-230	2N2243	0-930	2N3121	0-580	2N3642	0-150	2N4208	1-870	2N5138	0-090
2N722	0-680	2N2243A	0-930	2N3133	0-280	2N3643	0-150	2N4209	2-000	2N5139	0-090
2N744	0-180	2N2270	0-390	2N3134	0-280	2N3644	0-160	2N4227	0-300	2N5140	0-170
2N753	0-180	2N2297	0-400	2N3135	0-260	2N3645	0-160	2N4228	0-370	2N5141	0-165
2N760	0-270	2N2303	1-330	2N3136	0-280	2N3646	0-130	2N4248	0-110	2N5142	0-105
2N760A	0-270	2N2368	0-150	2N3209	0-605	2N3665	0-800	2N4249	0-130	2N5143	0-105
2N834	0-235	2N2369	0-135	2N3248	1-890	2N3686	0-950	2N4250	0-150	2N5910	0-270
2N914	0-200	2N2369A	0-170	2N3249	2-020	2N3691	0-500	2N4257	0-175	BC107	0-130
2N915	0-380	2N2483	0-210	2N3250	0-300	2N3692	0-500	2N4257A	0-230	BC108	0-420
2N916	0-300	2N2484	0-245	2N3250A	0-440	2N3693	0-150	2N4258	0-245	BC109	0-140
2N917	0-330	2N2509	0-710	2N3251	0-580	2N3694	0-150	2N4258A	0-275	BC177	0-180
2N918	0-330	2N2510	0-710	2N3251A	0-620	2N3724	1-420	2N4274	0-135	BC178	0-180
2N929	0-165	2N2511	1-130	2N3252	0-680	2N3724A	1-400	2N4275	0-135	BC179	0-180
2N929A	0-170	2N2586	1-080	2N3253	0-740	2N3725	1-425	2N4313	0-250	BC261A	0-340
2N930	0-180	2N2604	1-300	2N3299	0-340	2N3725A	1-090	2N4354	0-210	BC261B	0-340
2N930A	0-680	2N2605	0-800	2N3300	0-405	2N3734	1-470	2N4355	0-240	BC262A	0-360
2N956	0-320	2N2657	3-070	2N3301	0-285	2N3735	2-700	2N4356	0-240	BC262B	0-360
2N960	2-210	2N2658	4-000	2N3302	0-420	2N3735	0-165	2N4400	0-190	BC263A	0-380
2N995	1-080	2N2890	3-800	2N3304	0-700	2N3904	0-180	2N4011	0-240	BC263B	0-380
2N131	0-235	2N2891	3-500	2N3439	0-600	2N3905	0-175	2N4402	0-190	BCY70	0-155
2N1132	0-235	2N2894	3-220	2N3440	0-460	2N3906	0-165	2N4403	0-240	BCY71	0-220
2N1420	0-215	2N2894A	0-685	2N3444	0-830	2N3945	0-500	2N44916	0-110	BCY72	0-120
2N1613	0-180	2N2904	0-225	2N3502	0-790	2N3946	1-200	2N4970	0-160	BFX86	0-210
2N1711	0-220	2N2904A	0-255	2N3503	1-150	2N3947	0-570	2N4973	0-300	BFX89	0-240
2N1893	0-270	2N2905	0-270	2N3504	0-790	2N3962	0-380	2N4964	0-170	BFX92	0-280
2N1990	0-290	2N2905A	0-300	2N3505	0-790	2N3963	0-455	2N4965	0-170	BFX93	0-330
2N2017	0-870	2N2906	0-230	2N3545	4-500	2N3964	0-500	2N4966	0-170	BFX94	0-330
2N2102	0-375	2N2906A	0-245	2N3546	1-320	2N3965	0-780	2N4967	0-170	BFX85	0-280
2N2192	0-405	2N2907	0-210	2N3547	1-750	2N4030	0-465	2N4968	0-170	BFX86	0-230
2N2192A	0-405	2N2907A	0-220	2N3548	1-900	2N4031	0-510	2N4969	0-170	BFX87	0-230
2N2193	0-470	2N3011	0-180	2N3549	2-100	2N4032	0-530	2N4970	0-160	BFX88	0-210
2N2193A	0-470	2N3012	0-230	2N3550	2-500	2N4033	0-570	2N4971	0-340	BFY80	0-190
2N2194	0-485	2N3015	0-405	2N3563	0-130	2N4036	0-480	2N4672	0-360	BFY51	0-160
2N2194A	0-530	2N3019	0-540	2N3564	0-150	2N4037	0-460	2N5055	0-200	BFY52	0-190
2N2195	0-420	2N3020	0-580	2N3565	0-110	2N4121	1-135	2N5056	2-000	BSV38	0-210
2N2195A	0-470	2N3053	0-180	2N3566	0-130	2N4122	0-150	2N5057	1-170	BSY39	0-170
2N2217	0-275	2N3054	0-450	2N3567	0-120	2N4123	0-145	2N5127	0-110	BSY51	0-200
2N2218	0-215	2N3072	0-580	2N3568	0-170	2N4124	0-145	2N5128	0-140	BSY52	0-200
2N2218A	0-245	2N3073	0-455	2N3569	0-158	2N4125	0-160	2N5129	0-090	BSY53	0-200
2N2219	0-240	2N3107	0-540	2N3576	1-220	2N4134	1-500	2N5130	0-080	BSY54	0-260
								2N5131	0-100	BSY95A	0-130

THYRISTORS

Type No	Price	IT (RMS)	V DROM
NAS106F	0-250	4A	50
NAS106A	0-310	4A	100
NAS106B	0-360	4A	200
NAS106D	0-580	4A	400
NAS206F	0-283	6A	50
NAS206A	0-348	6A	100
NAS206B	0-405	6A	200
NAS206D	0-653	6A	400
NAS306F	0-313	8A	50
NAS306A	0-389	8A	100
NAS306B	0-450	8A	200
NAS306D	0-725	8A	400
NAS406F	0-350	10A	50
NAS406A	0-434	10A	100
NAS406B	0-504	10A	200
NAS406D	0-812	10A	400
NAS806F	0-438	16A	50
NAS806A	0-543	16A	100
NAS806B	0-630	16A	200
NAS806D	1-015	16A	400

Type No.	IF	VRM	Price
N7001	4A	50PIV	0-320
N7012	2A	100PIV	0-360
N7013	4A	200PIV	0-430
N7014	4A	400PIV	0-560
N7015	4A	600PIV	0-755
N7021	6A	50PIV	0-380
N7022	6A	100PIV	0-430
N7023	6A	200PIV	0-540
N7024	6A	400PIV	0-650
N7025	6A	600PIV	0-810

TRIACS WITH INTERNAL TRIGGERS

Type No.	Price	IT (RMS)	V DROM
NASQ1810	0-310	1-6A	100
NASQ1820	0-330	1-6A	200
NASQ1840	0-360	1-6A	400
NASQ4510	0-390	4-5A	100
NASQ4520	0-440	4-5A	200
NASQ4540	0-710	4-5A	400
NASQ6520	0-420	6-5A	100
NASQ6520	0-480	6-5A	200
NASQ6540	0-780	6-5A	400
NASQ8510	0-460	8-5A	100
NASQ8520	0-500	8-5A	200
NASQ8540	0-830	8-5A	400
NASQ10010	0-500	10A	100
NASQ10010	0-550	10A	200
NASQ10040	0-880	10A	400

2 AMP ENCAPSULATED PLASTIC BRIDGE RECTIFIERS


Type No.	IF	VRM	Price
N6001	2A	50PIV	0-350
N6002	2A	100PIV	0-380
N6003	2A	200PIV	0-430
N6004	2A	400PIV	0-500
N6005	2A	600PIV	0-500

PLASTIC RECTIFIER

Type No.	Price	IT (RMS)	V DROM
NAS1610	0-295	1-6A	100
NAS1620	0-314	1-6A	200

ADD 10% to order for VAT, p. & p. 15p per order.

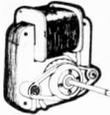Available from **THE RADIO SHOP**
16 CHERRY LANE, BRISTOL BS1 3NG
Tel. Bristol 421196. Open Mon.-Sat. 9.00 a.m.-5.30 p.m.



MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 75p. Postage 20p for first one then 10p for each one ordered.

MUSIC ON TAPE

A further buy enables us to offer these at an even lower price—namely 65p each or 5 for £2.50. Send for list of titles. We can't repeat when sold out.

BALANCED ARMATURE UNIT

500 ohm, operates as speaker or microphone, so useful in intercom or similar circuits, 37p each, 10 for £3.78.



CAR ELECTRIC PLUG

Fits in place of cigarette lighter. Useful method for making a quick connection into the car electrical system, 85p each or 10 for £3.42.



12 VOLT 1 1/2 AMP POWER PACK

This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 mF smoothing. Price £2.20, plus 20p post & packing.



Heavy Duty Mains Power Pack. Output voltage adjustable from 15-40V in steps—maximum load 250W—that is from 6 amp at 40V to 15amp at 15V. This really is a high power heavy duty unit with dozens of workshop uses. Output voltage adjustment is very quick—simply interchange push on leads. Silicon rectifiers and smoothing by 3,000mF. Price £2.35 plus 65p post.

BAKELITE INSTRUMENT CASE

Size approx. 6 1/2" x 3 1/2" x 2" deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs, etc. Price, 50p each. Paxolin lid 11p extra.



MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 25p each.



CONNECTING WIRE

7-0076 Copper conductors. 500 metre drums available in the following colours: Red/Brown, Yellow, Green/Grey, Blue/Green, Red/Orange, Green/White, Grey/White, Blue/Orange, Brown/Red, Brown/White, Red/Grey, Blue/Grey, Blue/Brown. Price £2.20 per drum plus 40p post. State alternative colours.

Screened Cable. 70076 core suitable for pick up or mic lead or for inter-connecting amplifiers. 10 metres. 35p.

DOOR SWITCH

As fitted to refrigerators, etc. Switches off as door closes. White 17p each. Black 15p each.

MICRO SWITCH

5 amp changeover contacts, 11p each. 10 for 99p. 15 amp on/off. Model 16p each. Changeover 18p each.



U.V. LIGHTING

Useful for flaw detection in metals and for looking for water marks, etc., also for fitting over tropical fish tanks—African violets and other indoor plants which must have U.V. for healthy growth. The outfit comprises of a 12in U.V. tube—choke—starter holder and tube ends. Price £2.20 plus 20p post.

80 WATT TUBULAR ELEMENTS

Brass encased with beaded flex ends. Standard replacements in most absorption type refrigerators but also has dozens of other uses. 83p each.

SPIT MOTOR

200-250V Induction Motor, driving a Carter gear box with 1 1/2in. of output drive shaft running at 5 revs per minute.

Intended for roasting chickens. Also suitable for driving models—windmills, coloured disc lighting effect, etc., etc. £2.04 plus 20p post and insurance.



SWITCH TRIGGER MATS

So thin is undetectable under carpet but will switch on with slightest pressure. For burglar alarms, shop doors, etc. 24in x 18in £1.99. 13in x 10in £1.21.

ROCKER SWITCH

13 amp self-fixing into an oblong hole. Size approximately 1" x 1" 9p each, 10 for 82p.



KETTLE ELEMENTS

Made by the famous A.E.I. Co. Complete with washers and combined fixing ring and plug shroud. Normal 2 round pin and flat pin ether connection and over-load reset push button. 2 Models—1 1/2in. (approx.) suitable for Swan and other similar models—1 1/2in. (approx.) suitable for G.E.C. Hotpoint, etc. All quick boil 2kW elements at 240V. Price £1.38 each.




MULLARD AUDIO AMPLIFIERS

All in module form, each ready built complete with heat sinks and connection tags, data supplied. Model 1133 300mW power output 72p. Model 1172 750mW power output 84p. Model EP9000 4 watt power output £1.66. (Triplex DLY STEREO. Complete £11.30.

CENTRIFUGAL BLOWER

Miniature mains driven blower centrifugal type blower unit by Woods. Powerful but specially built for quiet running—driven by cushioned induction motor with specially built low noise bearings. Overall size 4 1/2" x 4 1/2" x 4". When mounted by flange, air is blown into the equipment but to suck air out, mount it from centre using clamp. Ideal for cooling electrical equipment or fitting into a cooker hood, film drying cabinet or for removing flux smoke when soldering etc. A real bargain at £2.05.

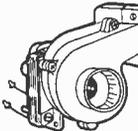

MIGHTY MIDGET

Probably the tiniest possible radio, as described in Practical Wireless, 4 January 73. All electronic parts £2.20 post paid.

TAPE PLAYBACK UNITS

Mains operated. Made by Reditune the famous "music in the background people". These are complete units for playing tape at standard speed (3 1/2"). These have a superior motor driven fly wheel to control the tape through the capstan and also an even equalizer useful valve amplifier with EL84 output. In a steel case with carrying handle. Tested and in good working order £2.50 or some in need of repair but complete £3.50. Cassettes of tape pre-recorded £1.10 (please state type of music required) 75p cartridge up to 200 miles then 50p per 100 miles extra.



6 MAINS TRANSFORMERS


Our Ref: MTM1 27V at 8A. Upright mounting fully shrouded—flying leads—fully tapped primary. Price £3.30.
Our Ref: MTM2. 12V at 1A. Upright mounting with fixing lugs, tag connections. 240V Primary—12V 1A secondary. Price 85p.
Our Ref: MTM3. 6-3V 2A upright mounting with fixing lugs, tag connections. 240V Primary 6-3V 2A secondary. Price 77p.
Our Ref: MTM4. 18V—1A with thermal cut-out, upright mounting with fixing lugs—tag connections. Primary 240V—secondary 18V at 1A. Price 85p.
Mains Isolation, 350W earth shielded—flex leads—upright mounting lugs for fixing terminals for output. Price £2.50 each.
Mains Transformer Bargain. Standard mains 240V input. Secondary 2-4V 9A intermittent 5A continuous. Price 55p.

DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work. £2.50 plus 20p post and insurance.

24-HOUR TIME SWITCH

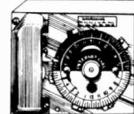Made by Smiths, these are A.C. mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5A changeover contacts will switch circuit on or off during these periods. £2.75 post and ins. 25p. Additional time contacts 55p pair.



THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2.95, plus 20p post and insurance. Industrial model 5A £3.30. Not on plate.




THIS MONTH'S SNIP

WALL THERMOSTATS

Made by the famous Smiths Instrument Co. called Colourstat. Wall mounting and in a handsome plastic case (cream and beige). Adjustable by slider (lockable) and may be set to control temperatures from around freezing through to 50°C. The slide panel is engraved and indicates "frost", "warm", "very warm", etc. The thermostat will control heaters, etc., up to 15A at normal mains voltage and is ideal for living room, bed room and greenhouse, etc. Price £1.65. Don't miss this.

THE TWENTYLITE

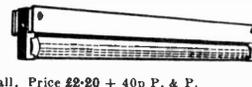Fluorescent lighting units with polyester choke and finished white enamel. 2ft. model, ideal kitchen, bedroom, hallway, porch, lift, etc., with tube. Assembled ready to install. Price £2.20 + 40p P. & P.



10 AMP. DIMMER/CONTROLLER

For the control of lighting of stage or studio or portable equipment in workshops, etc. This has socket outlets each controlled by 5 AMP Solid State Regulator. Also fitted with master switch fuse and neon indicator and terminating with 6 feet of flex. Overall length 17in. 3 1/2in. x 1 1/2in. deep. £7.50 plus 25p P. & P.

TANGENTIAL HEATER UNIT

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in cooler and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £2.85. 2kW Model as above except 2kW £2.75. Don't miss this. Control Switch 44p. P. & P. 40p.



TERMS: 10% discount if ten of an item ordered, send postage where quoted—other items, post free if order for these items is £6.00, otherwise add 20p.

Voltage Changing Transformers made by Parmeko. Upright mounting, fully shrouded and with terminal blocks for input and output. For changing mains voltage, ideal for working low voltage equipment from 230/240 mains and for increasing voltage due to losses in long leads. Voltage up or down between 190-250V 250W. Price £1.65 plus 30p post, etc.

Door Opening or Platform Rotating Motors. Very powerful motors estimated rating at 1/2 h.p. Reversible with gearbox and "V" belt drive wheel of 7in diameter. Price of motor which weighs approx. 15lb is £10. Note. These are ex-equipment but guaranteed for six months.

Gas and Smoke detector/Sensor—ref. GD1— recently referred to as the electronic nose—£2 each; circuit of smoke detector alarm included. Constructional details appeared in September's Practical Wireless, so we can supply the SLO3D at £1.75, the ZN414 at £1.35, also most other items, send for PC 10 radio parts list.

Spring Return Water Switch. As used in intercom and other similar equipment a two water 6 pole 3 way switch, spring return from centre position when turned clockwise and permanent off or on when turned anti-clockwise. Price 55p each.

A.C. Buzzers. 12V. Fix these into a box which will resonate and they will give a loud piercing note. Suitable for alarms or signal. 33p each.
Push-on Tag Connectors. These are being increasingly used on cars and domestic appliances. 2 sizes prevail, the most popular being for 3in tag. We offer these at attractive prices. 10 for 10p; 50 for 40p; 100 for 70p; 1,000 for 55p.
4 Minute Timed On Switch by Smiths. Our ref. TS AU1. This is for processing photographic plates, etc. Has a scale graduated 0-4min. Turn the pointer knob, and set it at the desired time—switch will stay closed until pointer knob returns to zero. Clockwork motor, so can be independent of mains if desired, but the switch itself is double pole, rated 250V, 15Amps. Price £1.65.

One Hour Timed On Switch by Smiths. Our ref. TS AU2. As TS AU1 except that the complete rotation of the pointer knob lasts for 1hr. Price £1.10 each.




DRILL CONTROLLER NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.95. 13p post and p. Made up model also available. £2.95.

MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v, 9v, 12v volts for up to 500mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1.10. Plus 20p postage.

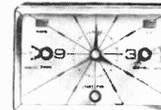Stereo Pre-amp Module. Mullard ref. LP 7182/2—transistors and all ancillary components mounted on PC board £1.32 with connection dig.



15A ELECTRICAL PROGRAMMER

Learn in your sleep! Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have a warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15 amp on/off switch. Switch-on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £2.15 + 20p p. & p. or with glass front chrome bezel 83p extra.

THERMAL CUTOUT

A miniature device 2in dia. on one screw fixing mount—can be used for motor overload protection, fire alarm, soldering iron, switch off, etc., etc. 15 amp contacts open with flame—radiant or conducted heat. 11p each or 10 for 99p.

HONEYWELL PUSH BUTTON MICRO SWITCHES

As used in some vending machines, etc. Each switch is a changeover type rated at 15A 250V a.c. Intended for panel mounting with fixing nuts and single black push knob. Single changeover switch 28p, Double switch 42p, Triple switch 61p.

MACLAREN THERMOSTAT

Make and break 20A a.c. with the sensor probe coupled by 2 feet capillary covering range of 10-100°C—complete with large engraved control knob. Price 85p.

J. BULL (ELECTRICAL) LTD.

(Dept. P.E.), 7 Park Street, Croydon CRO 1YD
Callers to 102/3 Tamworth Road, Croydon

G.W. SMITH & CO (RADIO) LTD

AUDIOTRONIC MODEL ATM.1

Top value 1,000 o.p.v. pocket multimeter. Ranges: 0/10/50/250/1,000V. A.C. and D.C. D.C. Current 0-1mA/100mA. Resistance: 0/150K ohms. Decibels: -10 to +22dB. Size: 90 x 60 x 28mm. Complete with test leads. £2-95. Post 15p.



Model 9-100TR MULTIMETER/TRANSISTOR

TESTER. 100,000 O.P.V. mirror scale/overload protection. 0/0-120/0-12/230/120/600V d.c. 0/6/30/120/600V a.c. 0/12/600µA/12/300mA/12 amp. d.c. 0/10 KΩ/1 MΩ/100 MΩ. -20 to +50dB. 0-01-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £14-95. Post 25p.



RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 O.P.V. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1,000V d.c. 2-5/10/50/250/500/1,000V a.c. D.C. current 100µA/1/10/100mA/1A. Resistance 300 ohms/300/300K/3MΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE £4-95. Post 25p.



LB3 TRANSISTOR TESTER

Tests ICO and B. Pnp/npn. Operates from 9V battery. Complete with all instructions, etc. £3-95. Post 20p.



LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audit indicator operates on two 1.5V batteries. Complete with all instructions, etc. £4-50. Post 20p.



MODEL 500 30,000 O.P.V.

with overload protection mirror scale 0/0-5/2-5/20/25/100/250/500/1,000V d.c. 0/2-5/10/25/100/250/500/1,000V a.c. 0/50µA/5/50/500mA. 12 amp. d.c. 0/60K/6 Meg/60 MegΩ. £10-50. Post paid. Leather case £1-75.



MODEL 449A IN CIRCUIT TRANSISTOR TESTER

Checks true a.c. beta in/out. Checks Ico. Checks diodes in/out. Checks SCR, etc. Beta Ht 10-300 LO 10-50 Ico 0-5000µA. 220/240V a.c. operation. £17-50. Post 25p.



U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 667 O.P.V. 0/0-3/1-5/7-5/30/60/150/300/600/900V d.c. and 750V. 0/0-3/1-5/7-5/30/60/150/300/600/900V a.c. 0/300µA/1-5/6/15/60/150/600mA/1-5/6 amp. d.c. 0/1-5/15/60/150/600MA. 1-5 amp. a.c. 0/200/3/3k/30kΩ. Accuracy Knife edge meter, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9-75. Post 25p.



KAMODEN HM-350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and D.C. current. Amplification factor of NPN, PNP, transistors, diodes, SCRs, etc. 4" x 4 1/2" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. £12-50. Post 30p.



HIOKI MODEL 700X

100,000 O.P.V. Overload protection. Mirror scale. 0/30-6/1-2/1-5/8/6/12/30/60/120/300/600/1,200V d.c. 1-5/3/8/12/30/60/150/300/600/1,200V a.c. 0/30µA/3/6/30/60/150/300mA. 0/12 amp. d.c. 2K/200K/2 Meg/20 Meg ohm -20 to +63dB. £14-95. Post 20p.



MODEL C-7080 EN

Giant 6in mirror scale. 20,000 O.P.V. 0/0-3/2-5/10/50/250/1,000/5,000V d.c. 0/2-3/10/50/250/1,000/5,000V a.c. 0/50µA/1/10/100/500mA/10 amp. d.c. 0/2K/200K/20 meg. -20 to +50dB. £13-95. Post 50p.



370 WTR MULTIMETER

Features a.c. current ranges. 20,000 O.P.V. 0/0-3/2-5/10/50/250/500/1,000V d.c. 0/2-5/10/50/250/500/1,000V a.c. 0/50µA/1/10/100mA/1/10 amp. d.c. 0/100mA/1/10 amp. a.c. 0/5K/50K/500K/5MΩ/50MEG. -20 +62dB. £17-50. Post 25p.



TMK LAB TESTER

100,000 O.P.V. 6 1/2in scale buzzer short circuit check. Sensitivity: 100,000 OPV d.c. 5/Volt a.c. D.C. volts: 0-5, 2-5, 10, 50, 250, 1,000V. A.C. volts: 3, 10, 50, 250, 500, 1,000V. D.C. current: 10, 100µA, 10, 100, 500mA, 2, 5, 10A. Resistance: 1K, 10K, 100K, 10 meg. 100 meg. Decibels: -10 to +49dB. Plastic case with carrying handle, size 7 1/2in x 6 1/2in x 3 1/2in. £19-95. P. & P. 25p.



MODEL U4311 SUB-STANDARD MULTI-RANGE VOLT AMPMETER

Sensitivity 330 ohms/Volt a.c. and d.c. Accuracy 0-5% d.c. 1% a.c. Scale length 165mm. 0/300/750µA/1-3/3/7-5/15/30/75/150/300/750mA/1-5/3/7-5/15/30/75/150/300/750V a.c. 0/3/7-5/15/30/75/150/300/750mA/1-5/3/7-5/15/30/75/150/300/750V a.c. 0/75/150/300/750V a.c. 0/75/150/300/750V a.c. 0/75/150/300/750V a.c. Automatic cut out. Supplied complete with test leads, manual and test certificates. £49. Post 50p.



KAMODEN HM720B F.E.T. V.O.M.

Input impedance 10MΩ. Ranges: 0/0-25/1/2-5/10/50/250/1,000V d.c. 0/2-5/10/50/250/1,000V a.c. 0/25µA/2-5/25/250µA d.c. -20 to +63dB. 0/5K/50K/500K/5MΩ/500MΩ. £14-95. Post 30p.



TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0/1-003/1-3/1-3/10/30/100/300V. R.M.S. 4cps.-1-2 Mc/s. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V. a.c. £17-50. Carr. 25p.



TMK MODEL 117 P.E.T. ELECTRONIC VOLTMETER

Battery-operated, 11 meg. input. 26 ranges. Large 4 1/2in mirror scale. Size 5 1/2in x 4 1/2in x 2 1/2in. D.C. volts 0-3-1,200V. A.C. volts 5-300V R.M.S. 8-0-800V P-P. D.C. Current 0-12-12MA. Resistance up to 2,000M ohm. Decibels -20 to +51dB. Complete with leads/instructions. £17-50. P. & P. 20p.



KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1,000 Megohms, 500 Volt. Battery operated. Wire range clear meter 4 1/2" x 4". Complete with deluxe carrying case, batteries, instructions. £19-95. Post 30p.




MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 40KHz-280MHz in 6 coils. 500µA meter. 9V battery operation. Size 180mm x 80mm x 40mm. £15. Post 20p.



TO-3 PORTABLE OSCILLOSCOPE

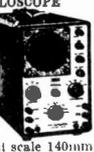8in tube, Y amp. Sensitivity 0-1V p-p/CM. Bandwidth 1-3cps-1.5MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0-9V. p-p/CM. Bandwidth 1-3cps-800KHz. Input imp. 2 meg Ω 20pF. Time base 5 ranges 10cps-300KHz Synchronisation. Internal/external. Illuminated scale 140mm x 215mm x 330mm. Weight 15 1/2lb. 220/240V a.c. Supplied brand new with handbook. £52-50. Carr. 50p.



CI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100KHz V RMS/mm. 0-1-25; HOR. AMP. Bandwidth 500KHz. Sensitivity at 100KHz. V RMS/mm. 0-2-25; Pre-set triggered sweep 1-3,000µsec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220mm x 360mm x 430mm, 115-230V a.c. operation. £39. Carr. paid.



RUSSIAN CI-18 DOUBLE BEAM OSCILLOSCOPE

5MHz Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in x 4in C.R.T. Calibrated triggered sweep from 0-2µsec to 100 µsec per cm. Free running time base 50 Hz-1MHz. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual. £87. Carr. paid.



TE-202 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 10 bands. Directly calibrated. Variable R.F. attenuator audio output, Xtal socket for calibration. 220/240V a.c. Brand new with instructions. £17-50. Carr. 37p. Size 140mm x 215mm x 170mm.




TE22 SINE SQUARE WAVE AUDIO GENERATORS

Size: 20cs to 200 kc/s on 4 bands. Square: 20cs to 30 kc/s. Output impedance 5,000 ohms. 200/250V a.c. Supplied brand new and guaranteed with instruction manual and leads. £17-50. Carr. 37p.



ARF-300 AFRF SIGNAL GENERATOR

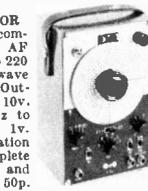All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine/square 10v. P-P. RF 100 KHz to 200 MHz. Output 1v. maximum. Operation 220/240V. A.C. Complete with instructions and leads. £29-95. Post 50p.




MODEL AT201 DECADE ATTENUATOR

Frequency range 0-200KHz. Attenuator 0-111dB. 0-1dB step. Impedance 600 ohms. Max. Input power 30dBm. Size 180mm x 90mm x 55mm. £12-50. Post 37p.




BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

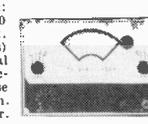Sine 18-200,000 Hz. Square 18-50,000 Hz. Output max. +10dB (10K ohms) Operation internal batteries. Attractive 2-tone case 7 1/2in x 5in x 2in. Price £17-50. Carr. 17p.




MCA.220 AUTOMATIC VOLTAGE STABILISER

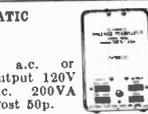Input 88-125V a.c. or 176-250V a.c. Output 120V a.c. or 240V a.c. 200VA rating. £11-97. Post 50p.



PS.200 REGULATED P.S.U.

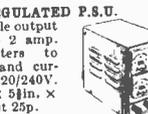Solid state. Variable output 5-20V d.c. up to 2 amp. Independent meters to monitor voltage and current. Input 220/240V. a.c. Size 7 1/2in x 5 1/2in x 3 1/2in. £19-95. Post 25p.



PS.100B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12V d.c. up to 3 amps. Meter to monitor current. Input 220/240V a.c. Size 4in x 3 1/2in x 3 1/2in. £11-97. Post 25p.




230V/240V SMITHS SYNCHRONOUS GEARED MOTORS

Built in gearbox. All brand new and boxed. 30 RPH CW; 2 RPH CW; 20 RPH CW; 2 RPH ACW; 30 RPH CW. 50p each, Post 12p.



POWER RHEOSTATS

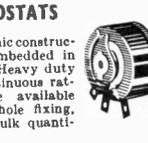High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing, 1/2in dia. shafts. Bulk quantities available.



25 WATT. 10/25/50/100/250/500/1000 ohms. 95p. P. & P. 10p.

60 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1-25. P. & P. 10p.

100 WATT. 1-5/10/25/50/100/250/500/1000 or 2500 ohms. £1-95. P. & P. 15p.

240° Wide Angle Ima Meters

MW1-6 60mm square £3-97
MW1-8 80mm square £4-97
Post extra



ALL PRICES ARE SUBJECT TO 10% VAT




HIGH QUALITY CONSTRUCTION KITS
 Appointed stockists at all branches
 Complete with comprehensive, easy to follow instructions, and covered by full guarantee.
 Post and packing 15p per kit

- AF20 Mono transistor amplifier..... £2.80
- AF30 Mono transistor pre amplifier..... £2.81
- AF310 Mono amplifier for two for stereo..... £3.31
- ATS Automatic light control..... £2.58
- AT30 Photo cell switching unit..... £3.70
- AT50 450W Trac light dimmer/switch control..... £3.32
- AT55 1 300W Trac light dimmer/switch control..... £3.70
- AT56 2 200W Trac light dimmer/switch control..... £3.90
- AT80 Psychedelic light control..... £7.80
- AT86 Psychedelic light control 3 channel..... £14.95
- HF61 Medium wave transistor radio..... £3.32
- HF67 FM transistor receiver..... £2.86
- HF310 FM tuner unit..... £16.81
- HF328 On line FM tuner unit..... £24.12
- HF330 Stereo decoder for HF310/HF325..... £9.96
- HF396 Aerial amplifier for AM/FM bands I, II, III..... £11.77
- OP310 Stereo preamp for use with 2x AF310..... £21.27
- GU330 Tremolo unit for guitars etc..... £7.50
- NT10 Power supply 100 mA 9V stab. 12V unstab..... £8.15
- NT300 Professional stereo power supply..... £12.51
- NT30 2x 30 Volt, 2.2 Amp..... £12.51
- NT305 Transistor converter 12/15V AC/DC to 6V, 7.5V or 9V DC..... £4.50
- NT310 Power supply 240V AC to 2x 18V DC at 2 Amps..... £4.80
- NT315 Power supply 240V AC to 4x 1.5V DC 500 mA..... £9.57

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

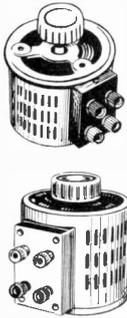Excellent quality at low cost. All models—Input 230V. 50/60 c/s. Variable output 0-260V.



MODEL S-260 GENERAL PURPOSE BENCH MOUNTING

- 1 amp..... £7.00
- 2 amp..... £8.05
- 5 amp..... £11.75
- 8 amp..... £15.90
- 10 amp..... £22.50
- 12 amp..... £23.60
- 20 amp..... £29.00
- 25 amp..... £38.00
- 40 amp..... £52.00

MODEL S-260B

- Panel mounting
- 1 amp..... £7.00
 - 2.5 amp..... £8.05

Carriage and Packing Extra

AUTO TRANSFORMERS

0/116/230V. Step up or step down. Fully shrouded.

- | | | |
|-------|--------|---------------|
| 50W | £2.95 | P. & P. 18p |
| 150W | £3.20 | P. & P. 18p |
| 300W | £4.00 | P. & P. 23p |
| 500W | £5.80 | P. & P. 33p |
| 1000W | £8.25 | P. & P. 38p |
| 1500W | £11.25 | P. & P. 43p |
| 2250W | £19.00 | P. & P. 50p |
| 5000W | £40.00 | P. & P. 1£1.8 |



230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp rating. 50p each. Post 10p (100 lots £3.0) Quantities available.



REFLEX HORN SPEAKER RUM.6

Built in driver unit. Impedance 16 ohm. Power rating 10W. Response 380-7,000Hz. Approx. size 6in x 6in. Weatherproof and shock proof.

OUR PRICE £4.97 P. & P. 30p

BVD.5 VERNIER TUNING DIAL

Approx. 7-1 ratio planetary drive vernier dials. Log scale 0-180 degrees. Blank scales 1 to 5. Scale width 4in. Dial size 3in x 3in. Overall size 7 1/2in x 4 1/2in x 1 1/2in deep including knob and coupling. 1in dia. shaft.



OUR PRICE £1.62 P. & P. 15p

1021 STEREO LISTENING STATION



For balancing and gain selection of loudspeakers with additional facility for stereo head-phones. 2 gain controls. Stereo speaker-on-off slide switch, stereo headphone sockets 6in x 4in x 2 1/2in.

OUR PRICE £2.25 P. & P. 20p

AUDIOTRONIC AHA101 STEREO HEADPHONE AMPLIFIER



All silicon transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 5V/100mV. Output 50mW per channel.

OUR PRICE £7.50 P. & P. 20p

EA.41 REVERBERATION AMPLIFIER



Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and output into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet 7 1/2in x 3in x 4 1/2in.

OUR PRICE £7.50 P. & P. 15p

MP7 MIXER PREAMPLIFIER



Microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2in x 5in x 3in. Inputs: Micro 3 x 3mV 20K, 2 x 2mV 400 ohm. Phono mag. 4mV 50K. Phono ceramic 100mV 1 meg. Output 250mV 100K.

OUR PRICE £8.97 P. & P. 20p

Send S.A.E. for new 8-page list of Semiconductors and Valves

ALL PRICES ARE SUBJECT TO 10% V.A.T.




SEW CLEAR PLASTIC PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPTS., EDUCATIONAL AUTHORITIES, ETC.
 Over 200 ranges in stock—other ranges to order. Quantity discounts available.
 Send for fully illustrated brochure.


TYPE 8W.100 100mm x 80mm Fronts

50µA.....	£4.15	100µA.....	£4.25
500µA.....	£3.95	1mA.....	£3.95
1000µA.....	£3.95	5mA.....	£3.70
5000µA.....	£3.70	10mA.....	£3.60
10mA.....	£3.60	50V d.c.....	£3.60
50V d.c.....	£3.60	300V d.c.....	£3.60
300V d.c.....	£3.60	1 amp. d.c.....	£3.60

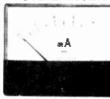


TYPE MR.85P. 4 1/2in. x 4 1/2in. Fronts

50mA.....	£3.90	100mA.....	£3.90
500mA.....	£3.90	1 amp.....	£3.90
5 amp.....	£3.90	15 amp.....	£3.90
30 amp.....	£3.95	20V d.c.....	£3.90
50V d.c.....	£3.90	50V d.c.....	£3.90
50V d.c.....	£3.90	300V d.c.....	£3.90
300V d.c.....	£3.90	100µA.....	£4.40
100µA.....	£4.40	50-0-50µA.....	£4.25
50-0-50µA.....	£4.25	100µA.....	£4.25
100-0-100µA.....	£4.05	300µA.....	£3.90
300µA.....	£3.90	5000-500µA.....	£3.90
5000-500µA.....	£3.90	1mA.....	£3.90
1mA.....	£3.90	10-1mA.....	£3.90
10-1mA.....	£3.90	5mA.....	£3.90
5mA.....	£3.90	10mA.....	£3.90

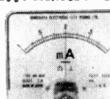

TYPE MR.38P. 1 21/32in. square Fronts.

200mA.....	£2.85	300mA.....	£2.85
500mA.....	£2.85	750mA.....	£2.85
1 amp.....	£2.85	2 amp.....	£2.85
5 amp.....	£2.85	10 amp.....	£2.85
3V d.c.....	£2.85	10V d.c.....	£2.85
15V d.c.....	£2.85	20V d.c.....	£2.85
50V d.c.....	£2.85	100V d.c.....	£2.85
100-0-100µA.....	£2.40	50V d.c.....	£2.85
50V d.c.....	£2.85	100V d.c.....	£2.85
100V d.c.....	£2.85	150V d.c.....	£2.85
150V d.c.....	£2.85	500V d.c.....	£2.85
500V d.c.....	£2.85	750V d.c.....	£2.85
750V d.c.....	£2.85	15V a.c.....	£2.85
15V a.c.....	£2.85	50V a.c.....	£2.85
50V a.c.....	£2.85	150V a.c.....	£2.85
150V a.c.....	£2.85	300V a.c.....	£2.85
300V a.c.....	£2.85	500V a.c.....	£2.85
500V a.c.....	£2.85	8 Meter 1mA.....	£2.80
8 Meter 1mA.....	£2.80	500µA.....	£2.85
500µA.....	£2.85	100µA.....	£2.85
100µA.....	£2.85	50µA.....	£2.85

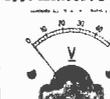

TYPE SD.880 82.5mm x 110mm Fronts

10mA.....	£3.10	50mA.....	£3.10
50mA.....	£3.10	100mA.....	£3.10
100mA.....	£3.10	500mA.....	£3.10
500mA.....	£3.10	1 amp.....	£3.10
1 amp.....	£3.10	5 amp.....	£3.10
5 amp.....	£3.10	10 amp.....	£3.10
10 amp.....	£3.10	5V d.c.....	£3.10
5V d.c.....	£3.10	10V d.c.....	£3.10
10V d.c.....	£3.10	20V d.c.....	£3.10
20V d.c.....	£3.10	50V d.c.....	£3.10
50V d.c.....	£3.10	300V d.c.....	£3.10
300V d.c.....	£3.10	15V a.c.....	£3.30
15V a.c.....	£3.30	300V a.c.....	£3.30
300V a.c.....	£3.30	5mA.....	£3.30
5mA.....	£3.30	10mA.....	£3.30
10mA.....	£3.30	50µA.....	£3.40
50µA.....	£3.40	50-0-50µA.....	£3.40
50-0-50µA.....	£3.40	100µA.....	£3.35
100µA.....	£3.35	100-0-100µA.....	£3.35
100-0-100µA.....	£3.35	200µA.....	£3.35
200µA.....	£3.35	500µA.....	£3.35
500µA.....	£3.35	1mA.....	£3.35
1mA.....	£3.35	5mA.....	£3.35
5mA.....	£3.35	10mA.....	£3.35
10mA.....	£3.35	50V d.c.....	£3.35
50V d.c.....	£3.35	300V d.c.....	£3.35
300V d.c.....	£3.35	15V a.c.....	£3.30
15V a.c.....	£3.30	300V a.c.....	£3.30
300V a.c.....	£3.30	100mA.....	£3.30
100mA.....	£3.30	500µA.....	£3.30
500µA.....	£3.30	1mA.....	£3.30
1mA.....	£3.30	5mA.....	£3.30
5mA.....	£3.30	10mA.....	£3.30
10mA.....	£3.30	50V d.c.....	£3.30
50V d.c.....	£3.30	300V d.c.....	£3.30
300V d.c.....	£3.30	15V a.c.....	£3.30
15V a.c.....	£3.30	300V a.c.....	£3.30
300V a.c.....	£3.30	100µA.....	£3.30
100µA.....	£3.30	500µA.....	£3.30
500µA.....	£3.30	1mA.....	£3.30
1mA.....	£3.30	5mA.....	£3.30
5mA.....	£3.30	10mA.....	£3.30
10mA.....	£3.30	50V d.c.....	£3.30
50V d.c.....	£3.30	300V d.c.....	£3.30
300V d.c.....	£3.30	15V a.c.....	£3.30
15V a.c.....	£3.30	300V a.c.....	£3.30
300V a.c.....	£3.30	100µA.....	£3.30
100µA.....	£3.30	500µA.....	£3.30
500µA.....	£3.30	1mA.....	£3.30
1mA.....	£3.30	5mA.....	£3.30
5mA.....	£3.30	10mA.....	£3.30
10mA.....	£3.30	50V d.c.....	£3.30
50V d.c.....	£3.30	300V d.c.....	£3.30
300V d.c.....	£3.30	15V a.c.....	£3.30
15V a.c.....	£3.30	300V a.c.....	£3.30
300V a.c.....	£3.30	100µA.....	£3.30
100µA.....	£3.30	500µA.....	£3.30
500µA.....	£3.30	1mA.....	£3.30
1mA.....	£3.30	5mA.....	£3.30
5mA.....	£3.30	10mA.....	£3.30
10mA.....	£3.30	50V d.c.....	£3.30
50V d.c.....	£3.30	300V d.c.....	£3.30
300V d.c.....	£3.30	15V a.c.....	£3.30
15V a.c.....	£3.30	300V a.c.....	£3.30
300V a.c.....	£3.30	100µA.....	£3.30
100µA.....	£3.30	500µA.....	£3.30

GWS GW.SMITH & CO (RADIO) LTD

UNR 30 RECEIVER



4 Bands covering 550kHz-30MHz. BFO Built-in Speaker 220/240V a.c. Brand new with instructions.
OUR PRICE £15.75 Carr. 37p

UR-1A RECEIVER



4 Bands covering 550kHz-30MHz. FET, 8 Meter. Variable BFO for 85B. Built-in Speaker. Bandspread. Sensitivity Control. 220/240V a.c. or 12V d.c. 121 x 42in x 7in. Brand new with instructions.
OUR PRICE £25.00 Carr. 37p

LAFAYETTE HA-600 RECEIVER



General coverage 150-400kHz. 550kHz-30MHz. FET front end, 2 mech. filters, product detector, variable BFO, noise limiter, 8 Meter Bandspread. RF Gain. 16in x 9in x 8in. 18 lb. 220/240V a.c. or 12V d.c. Brand new with instructions.
OUR PRICE £50.00 Carr. 50p

TRIO 9R59DS RECEIVER



4 bands covering 550kHz-30MHz continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW. ANL. Variable BFO. 8 meter. Sep. bandspread dial. IF frequency 445kHz audio output 1.5W. Variable RF and AF gain controls 115/250V a.c. Size: 7in x 13in x 10in with instruction manual.
OUR PRICE £49.50 Carr. Paid

FULL RANGE OF TRIO STOCKED

TRIO JR310 SSB RECEIVER



Covers 3.5, 7, 14, 21, 28, 28.5 and 29.1MHz bands, and WWV 15MHz. SSB, AM and CW. AF output more than 1W. Crystal controlled BFO for 85B. 8 meter, ANL, etc. A.C. 110/120-220/240V. Size 9.30 x 17.9 x 310mm.
OUR PRICE £75.00 Carr. Paid



TRIO JR599 RECEIVER



9 wavebands covering 1.8-29.7MHz. 144-146MHz and 10.00MHz WWV. SSB, CW, AM and FM. AF output more than 1W. 8 Meter. Switch control. BFO. Variable RF and AF controls. 4-16 ohm output and phone jack. Power requirements 100/240V a.c. 12-14V d.c.
OUR PRICE £155.00 Carr. Paid

TRIO TR2000 TRANSCIEVER

Fully transistorised portable VHF Transciever. Will transmit and receive on 6 channels between 144-146MHz. 1W transmitter. 12V d.c. internal or external supply. Built in charger for nickel cells. Power/volume switch, squelch control, channel selector, mike socket, earphone/external speaker socket. Complete with microphone. 144-48, 144-72 and 145-32 crystals.
OUR PRICE £79.50 Carr. Paid

TRIO TS515/PS515 TRANSCIEVER



High quality TS515 SSB/CW amateur band receiver covering 80, 40, 20, 15 and 10 metre bands with PS515 power supply and speaker unit. Transmit/receive frequency 3.5-29.7MHz. Output 1.5W. Power requirements 110-120/220-240V a.c.
OUR PRICE £210.00 Carr. Paid

BELTEK W5400 CAR TRANSCIEVER



Solid state mobile transceiver for 12V d.c. neg. use. Transmits and Receives on any 12 of 28 channels between 144 and 146MHz. Power output 10W and 1W switchable. Controls: Volume/on/off, squelch, channel selector. Internal 8in speaker. Complete with dynamic mike, PTT switch, three sets of crystals for 144-48MHz, 144-60MHz, 145-00MHz, mounting bracket and instructions.
OUR PRICE £75.00 Carr. Paid

HAND HELD 2-WAY WALKIE TALKIES



Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic Aerial. Complete with carrying cases.
SKYPON 100mW. £24.95 pair, post 50p.
F502 2 CHANNEL 500mW. £52.50 pair, post 50p.
F1003 3 CHANNEL 1 watt. £71.25 pair, post 50p.
LICENSE REQUIRED IN U.K.

3-STATION INTERCOM KE30



Master and two sub stations. Can be used on desk or wall mounted. Complete with cable and batteries.
OUR PRICE £5.25 Carr. Paid

AUDIOTRONIC

ACD660 STEREO CASSETTE DECK



A beautifully styled 4 track stereo deck with an outstanding specification offered at a remarkably low price. Incorporates a host of features including switchable noise filter, normal/chrome tape selector, twin VU meter, slider record/playback level control, front panel headphone socket, recording indicator lamp, phono/Din line input sockets, 3.5mm mike input sockets, etc. etc. Frequency response 100-8kHz (100-12kHz CrO2). 8/N -45dB. Crosstalk -45dB. Separation -30dB. Noise limiter -6dB at 10kHz. Complete with phone connecting leads.
OUR PRICE £39.50 Carr. Paid

AHP8A 8 TRACK STEREO TAPE PLAYER

Incorporates built in amplifiers giving 21 + 21w r.m.s. output. Push-button track selector. Illuminated track indicators, slider controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output impedance 8 ohms. 220/240V a.c.
OUR PRICE £17.25 P. & P. 50p, plus V.A.T.

AHP8D 8 TRACK STEREO TAPE DECK

Can be used with most hi-fi amplifiers. Push button track selector and illuminated track indicators. Attractive cabinet with black and silver trim. Output level 750mV. 220/240V a.c.
OUR PRICE £11.95 P. & P. 50p, plus V.A.T.

STEREO HEADPHONES

LSH20. Individual volume controls. Stereo mono switch. 8 ohms. 40-19,000Hz. **£3.50** P. & P. 30p
LSH30. Open back type. Individual volume controls. 8 ohms. 30-20,000Hz. **£5.50** P. & P. 30p
LSH40. Two way speaker system. Individual volume controls. 8 ohms. 20-20,000Hz. **£6.95** P. & P. 30p
LSH60. 3in speaker units. 8 ohms. 20-20,000Hz. Complete with zipped carrying case. **£8.50** P. & P. 30p
LQH400. 4-channel dynamic headphones. Each earpiece has 4 drive units. 4-32 ohms. 20-20,000Hz. **£9.95** P. & P. 30p
LSH50. Electrostatic with self powered energiser and control unit with headphone/speaker selector. 4-32 ohms. 20-24,000 Hz. **£15.95** P. & P. 30p

DOLBY 'B' NOISE REDUCTION UNITS



Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 161in x 8in x 31in. a.c. 100/250V2.

PROCESS TWO

For use with cassette and tape recorders. Freq. res. 30Hz-20kHz ±2dB. Off tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. 8/N better than 70dB. Supplied with test cassette or tape as required.
OUR PRICE £34.50 P. & P. 50p

PROCESS FOUR

For use with semi professional tape recorders. Freq. res. 30Hz-20kHz ±2dB. 12V better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.
OUR PRICE £50.00 P. & P. 50p

ACR14 BATTERY MAINS CASSETTE RECORDER

Portable twin track mono recorder with a t.o.m.a.t.i.c. recording level control. Built in speaker. Earpiece socket. Input for radio or record player. Fast forward and rewind. Output 500mW; 220/240V a.c. or 6V d.c. operation. Complete with remote control microphone, mains lead, earpiece and batteries.
OUR PRICE £10.50 P. & P. 50p

ACR3500 CAR RADIO

Manual tuning of Medium and Long waves. 12V pos. or neg. earth. Complete with speaker, mounting brackets and instructions.
OUR PRICE £6.50 P. & P. 50p

ACP8 8-TRACK CAR PLAYER

12V neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with pilot lamp. With speakers, mounting brackets and instructions.
OUR PRICE £12.50 P. & P. 40p

LOW NOISE CASSETTES

Top Hi-Fi quality in library cases
TYPE 8 10 25
C80 £1.99 £2.53 £5.99
C90 £1.85 £3.62 £8.99
C120 £2.29 £4.48 £10.83
P. & P. 15p Post Free
CASSETTE TAPE HEAD
CLEANER 30p each. P. & P. 6p.

AR1000 Sportsman AM/FM Portable

5 wavebands covering A.M.: 535 - 1065kHz; F.M.: 88-108MHz; A.I.R.: 105 - 135MHz; P.B.: 147-174MHz; W.B.: 182-5MHz. Large horizontal slide dial with logging scale. Slider volume and squelch control. 7 section telescopic aerial for F.M. and built in ferrite bar for A.M. A.F.C. 3in speaker. Earpiece socket. Green leatherette covered cabinet with metal side panels. Size 102 x 79 x 219mm. Battery/mains operation.
OUR PRICE £11.50 P. & P. 35p

AMB500 MULTI BAND RADIO

5 wavebands covering MW 335 - 1605kHz and F.M. 88-175MHz. All transistor. Battery or mains operation. Built in aerial and 8 section telescopic aerial. Complete with batteries, shoulder strap and earpiece.
OUR PRICE £6.95 P. & P. 35p

AMR-9000 GLOBAL AM/FM PORTABLE

10 wavebands covering A.M.: 535-1605kHz; L.W.: 150-380kHz; M.B.: 1.6-4.0MHz; S.W.1.: 4.0-8.0MHz; S.W.2.: 8.0-16.0MHz; S.W.3.: 16-24MHz; F.S.B.1.: 30-50MHz; P.B.2.: 147-174MHz; F.M. 88-108MHz; A.I.R.: 108-136MHz. Features time zone map and timing dial. Large clear scale. Telescopic aerial and built-in aerial. A.F.C. on F.M. 6in x 4in speaker and personal earpiece. Battery/mains operation. Size 345 x 133 x 305mm.
OUR PRICE £36.00 P. & P. 50p

AM/FM PORTABLE RADIO AR3000

4 wavebands covering FM 87-108MHz, MW 310-1605kHz, LW 145-285kHz, SW 5.8-12.0MHz. Push button wave change plus AFC and on/off. Thumbwheel tuning. Slider volume and tone controls. Earphone socket. Built in and telescopic aerials. Car aerial socket. Battery/Mains operation.
OUR PRICE £14.95 P. & P. 57p

DIGITAL CLOCK/RADIO AM-FM ADC. I

Covers AM 540-1600kHz. FM 88-108MHz with AFC. 24 hour lead type digital clock with one minute division time change. Illuminated dial. 24 hour alarm setting. Wake up to the sound of music or loud buzzer. Unique sleep switch will automatically turn off radio when you have gone to sleep. Slider volume control. Internal speaker plus socket for earpiece or pillow speaker. A.C. 240V. Size 254 x 92 x 178mm. Complete with earpiece, FM aerial and operating instructions.
OUR PRICE £12.50 P. & P. 50p

SAVE UP TO 33 1/3% OR MORE! GWS

SH628 STEREO HEADPHONES



Outstanding value. Soft earpads, adjustable headband. 8-16 ohms. 20-20,000 Hz. Complete with lead and stereo plug.

OUR PRICE **£1.87** P. & P. 30p

LHO25 STEREO HEADPHONES



Lightweight headphones with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6 ft cord and plug.

OUR PRICE **£1.97** P. & P. 30p

TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (d.c. 600 ohms). Frequency response 200-4,000 Hz.

OUR PRICE **£2.25** P. & P. 30p

DHO25 STEREO HEADPHONES



Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and plug.

OUR PRICE **£2.25** Carr. 50p

BH001 HEADSET AND BOOM MICROPHONE




Moving coil. Headset phone imp. 16 ohms. Mike imp. 200 ohms. Ideal for language teaching, communications.

etc. Complete with leads and plugs.

OUR PRICE **£4.95** P. & P. 30p


STEREO SPEAKERS

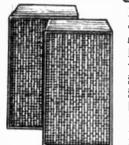

Matched pair of bookshelf speakers. De luxe teak veneered finish. Size 14 1/2 in x 9 in x 7 1/2 in. 8 ohms. 8W RMS. 16W peak. Complete with DIN lead.

OUR PRICE **£12.95** Carr. Paid

AKAI HI-FI BARGAINS

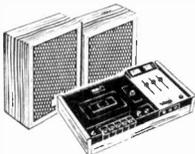

STEREO CASSETTE RECORDER

For conventional or Chromium Dioxide tape. 4 track record/playback. Volume and tone controls. Frequency response 40-16kHz (using CrO2 tape), distortion better than 2%, wow and flutter better than 0.2% RMS. Complete with pair of matching Akai CS88 speakers. Rec. Price £96.10.

OUR PRICE **£56.50** P. & P. 50p

CS355 STEREO DECK 4 track record/playback deck. Accepts chrome/regular tape cassettes. Rec. Price £68.30.

GWS PRICE **£44.45** P. & P. 50p

MICROPHONES (P. & P. 50p) ADM Dynamic (pair) £7.60

3416 STEREO TAPE DECK



4 track. 7 1/2, 3 1/2 i.p.s. Stereo mono record/play. 7in reels. Inputs for dynamic mikes, radio gram. Complete with cover.

OUR PRICE **£41.95** Carr. 75p

DIGITAL CLOCK MECHANISM DT.55B

Features 24 hour alarm setting with built in buzzer. On/off and auto alarm "deep" switch. Illuminated rotary dial with hours, minutes and seconds. Automatically turns off TV, radio, light, etc. and with autotuning will switch on again when required. A.c. 240V operation. Switch rating 250V, 3A.

OUR PRICE **£5.95** P. & P. 30p

EMI LOUDSPEAKERS

Model 350. 13in x 8in with single tweeter/crossover. 20-20,000 Hz. 15W RMS. Available 8 or 15 ohms. £7.95 each. P. & P. 37p.

Model 460. 13in x 8in with twin tweeters/crossover. 55-13,000 Hz. 8W RMS.

Available 8 or 15 ohms. £8.65 each. P. & P. 25p.

RECORD DECK PACKAGES



Carriage and Packing 75p
Complete units with Stereo Comridge ready wired in plinth and cover.

Model	Price
GARRARD 2025 TC/9TAHCD	£11-85
SP25 111/G800	£16-50
SP25 111/M44E	£17-95
SP25 111/M44-7	£17-50
SP25 111/M55E	£18-50
SP25 111 Module/M75-6	£19-45
AP76/G800	£26-45
AP76/M44E	£27-70
AP76/M44-7	£27-20
AP76/M55E	£28-30
AP76/M75ED	£34-90
AP76/M75EJ	£30-92
AP76 Module M75-6	£29-10
AP96 Module M75-6	£33-20
ZERO 1008 Module/M93E	£44-16

B.S.R. McDONALD

C114 Mono	£7-40
MP60/G800	£16-50
MP60/TPD1/G800	£18-80
MP60/M44-7	£17-50
HT70/TPD1/G800	£19-20

GOLDRING

GL72/G800	£34-20
GL75/G800	£39-10
GL75/G800E	£41-65

RECORD DECKS

Carriage & Packing 50p

B.S.R. McDONALD C114 Mono	£5-95
C129 Mono	£6-50
C137	£7-00
110/TPD1	£13-95
610	£10-55
610/TPD1	£16-45
710	£21-15
810	£22-80
MP60	£5-25
MP60/G800	£10-90
MP60/TPD1	£13-20
MP60/TPD2	£11-25
HT70	£11-80
HT70/G800	£14-25
HT70/TPD1	£16-65

CONNOISSEUR

BD1 Kit	£9-10
BD1 Chassis	£11-85
BD2/SAU2/Chassis	£22-70
BD2/SAU2/Plinth/Cover	£28-20

GARRARD

2025 TJC Loss Cartridge	£6-35
SP25 111	£9-25
SP25 111/Acos GP104	£6-50
SP25 111/G800	£10-95
SP25/M75-6	£13-90
AP76	£18-00
SL7A	£11-15
SL7B	£17-75
SL95B	£31-15
401	£24-35
ZERO 100	£34-10
ZERO 1008	£31-40

GOLDRING

G99	£22-50
G101/P/C	£22-50
GL69/2	£15-75
GL72	£26-45
GL72/P	£33-75
GL75	£32-20
GL75/P	£41-65
GL75/P/C	£56-25
HL85/P/C	£72-00

THORNS

TD125/11	£59-40
TD125AD/11	£92-05
TD160C	£50-80
TL165	£48-80

FANTASTIC OFFER! PORTABLE CASSETTE RECORDER CT5050

Instant recording and playing. Piano key controls. Automatic level control. Built in speaker. Complete with remote control microphone, carrying case and shoulder strap.

OUR PRICE **£8.50** P. & P. 50p

NEW! SINCLAIR CAMBRIDGE CALCULATOR

To build yourself. Complete kit of parts with step by step instructions to build a full specification pocket sized calculator. (Rec. Price £27.23)

OUR PRICE **£24.95**

P. & P. 50p

(Also available ready built (Rec. Price £39.95).

OUR PRICE **£27.20** P. & P. 25p

MINUTEMAN MM3 POCKET CALCULATOR

Size only 4 1/4 in x 3 in x 1 in. 8 digit display with overflow and error indicators. Floating decimal. Adds, subtracts, multiplies and divides. Chain and mixed calculations. Constant factor for series multiplication or division. Complete with batteries, instructions and case.

OUR PRICE **£23.95** P. & P. 25p

MINUTEMAN MM3M

as above with addition of memory key, percent key and a fixed or floating decimal. Complete with rechargeable batteries, a.c. adaptor, instructions and case.

OUR PRICE **£28.50** P. & P. 25p

BINATONE DS100 DIGITAL CLOCK

240V mains operation. Ivory case with large clear numbers for hours, minutes and seconds. Approx. size 6 1/2 in x 3 in x 3 1/2 in.

OUR PRICE **£4.50** P. & P. 30p

SINCLAIR PROJECT 60 PACKAGE DEALS



2 x Z30/Stereo 60/PZ5

£16.95. P. & P. 37p.

2 x Z30/Stereo 60/PZ6

£18.00. P. & P. 37p.

2 x Z30/Stereo 60/PZ8

£20.25. P. & P. 37p.

Transformer for PZ8

£3 extra.

Active Filter Unit £4.45.

Pair of Q16 Speakers £10.70.

Sinclair Project 605

£20.97. P. & P. 37p.

All Sinclair Products in stock:

2000 Stereo Amplifier, £25.95;

3000 Stereo Amplifier, £28.95;

2000/3000 Stereo Tuner, £26.80.

Q830 Speakers, £22.98 pair,

P. & P. 50p each on above items.

FM TUNER CHASSIS

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in x 4in x 2 1/2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9V battery. Coverage 88-108MHz. Ready built ready for use.

OUR PRICE **£5.95** P. & P. 20p

Stereo Multiplex Adaptor £4.97.

A1018 FM TUNER

Specification as above. Chassis but complete in cabinet with on/off switch. Size 7 1/2 in x 3 1/2 in x 5 in.

OUR PRICE **£9.65** P. & P. 30p

Stereo Multiplex Adaptor £4.97.

SPECIAL PURCHASE! BSR 8-TRACK PLAYER CHASSIS

Famous BSR 8 track chassis as used in Model T D S S complete with silver and black eucalyptus ready to fit into cabinet. Output 125mV A.C. 240V. Overall size approx. 185 x 215 x 80mm.

OUR PRICE **£8.95** P. & P. 50p

LONDON'S LARGEST STOCKS INCLUDING PRODUCTS BY-



ARMSTRONG CAMBRIDGE KEF-LUX-NIKKO SANSUI-SANYO SONY-TEAC TRANSCRIPTORS TRIO-UHER YAMAHA

Prices on request or send S.A.E. for full Discount List

ALL EQUIPMENT IS FULLY GUARANTEED AND COVERED BY 12 MONTHS FREE SERVICE!

G.W.S.MITH & CO (RADIO) LTD

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

Branch	Address	Phone
CENTRAL LONDON	257/8, Tottenham Court Rd, W.1.	Tel: 01-580 0670
	10, Tottenham Court Rd, W.1.	Tel: 01-637 2232
	27, Tottenham Court Rd, W.1.	Tel: 01-636 3715
	97, Tottenham Court Rd, W.1.	Tel: 01-580 3789
	21, Old Compton Street, W.1.	Tel: 01-437 8269
	3, Lisle Street, W.C.2.	Tel: 01-437 8204
	34, Lisle Street, W.C.2.	Tel: 01-437 9155
	118, Edgware Road, W.2.	Tel: 01-723 9789
	193, Edgware Road, W.2.	Tel: 01-723 6211
	311, Edgware Road, W.2.	Tel: 01-262 0387
	382, Edgware Road, W.2.	Tel: 01-723 4194
	152/3, Fleet Street, E.C.4.	Tel: 01-353 2833
	378, Harrow Road, W.9.	Tel: 01-286 9530
ESSEX	86, South Street, Romford.	Tel: Romford 20218
SURREY	1046, Whitgift Centre, Croydon.	Tel: 01-681 3027
	27, Eden Street, Kingston.	Tel: 01-546 7845
	32, Hill Street, Richmond.	Tel: 01-948 1441

ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY

HEAD OFFICE AND MAIL ORDER DEPARTMENT

UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ

TELEPHONE 01-205 3735

PRICES SUBJECT TO 10% VAT

Order with confidence by Post—but remember to add 10% VAT to total value of order including carriage and packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY IN CAPITALS.



TELEPHONE ORDERS ACCEPTED FROM ACCESS AND BARCLAYCARD HOLDERS

CREDIT TERMS FOR PERSONAL CALLERS (on sales of £50 and over).

All prices correct at 28-9-73 but subject to change without notice. E & O.E.

MEN! GIRLS!

YOU CAN EARN £50p.w.
Plus an exciting life and a secure future.
HOW?

Get into the fabulous Computer Industry now. On the ground floor. While industry, commerce, science and governments are desperately seeking trained personnel. Give us only four to six weeks and we can train you in any one of the three vital careers in computers: (1) Programming (men and girls). (2) Operating (men and girls). (3) Key Punching (girls exclusively).

We are the only training organisation able to make this offer. And our teaching methods succeed because they combine specially prepared courses with equipment such as the unique Eduputer, exclusive to us.

Thanks to our methods, people from all walks of life have exchanged boring, under-paid, insecure jobs for careers that have meaning, prestige and security.

Past performance counts for nothing. Provided you have the aptitude (which we can discover quite simply), there is no reason why you should not get out of the rut and into Tomorrow's World—the fascinating world of Computers.

The moment you qualify—and we will help you do just that—one of our own exclusive appointments agencies will introduce you to opportunities galore. Worldwide. At no cost to you. All part of our continuing service.

What have you to lose by enquiring? Information and advice are yours for the asking. Post the coupon TODAY for full details FREE and without obligation.



London Computer Training Services

R69, Oxford House, 9-15 Oxford Street, W.1. Telephone 01-437 9906

Please send me your free illustrated brochure on training for Computer Programming (men and girls)

Computer Operating (men and girls)

Key Punching (girls exclusively)


(Tick appropriate box)

Name _____

Address _____

Tel. _____

'BIG' Discounts

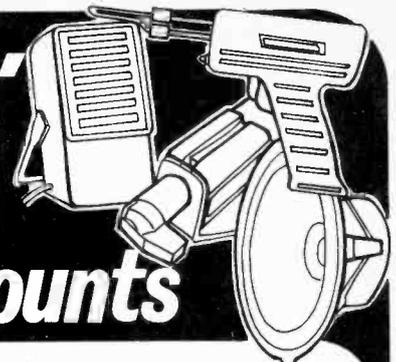

ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		GOODMANS 6in 8 ohm Dual cone	
EMI 13in x 8in 3, 8 or 15 ohm	£	EM1 13in x 8in 3, 8 or 15 ohm	1-30
Plain	2-05	FANE, 7in x 4in, 3 or 8 ohm	1-00
With Co-Axial Tweeter	2-20	8in Dual cone 8 ohm	2-40
Twin Tweeter	3-55	CELESTION 8in, 15 ohm	1-55
Type 350, 8 ohm, 20W	8-00	ADASTRA 10in, 8 or 15 ohm, 10W	2-75
6in, 8 ohm, 10W	2-70	BAKER GROUP 25 12in, 8 or 15 ohm, 25W	6-45
8in, 8 ohm, 10W	3-75		P. & P. 0-25
12in, 8 ohm, 20W	5-50	5in, 8 ohm, 5W C/Mag.	0-85
8in x 5in, C/Mag, 5W	1-20	2 1/2in, 8 ohm or 64 ohm	0-50
8in x 5in, Dual cone 8 ohm, 10W	2-45		P. & P. 0-10
ELAC 8in 8 ohm Dual cone	2-10		
TWEETER AND CROSSOVER		Dome Tweeter 8 ohm, 30W	
EMI 3 1/2in, 3 or 8 ohm C/Mag	1-00	Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-00
Cone Tweeter 8 or 15 ohm, 10W	1-90		P. & P. 0-10
Cone Tweeter 8 ohm, 3W	1-00		
Horn Tweeter 8 ohm, 20W	5-50		
KIT FORM CABINETS, TEAK VENEER, 12in x 12in x 6in with 8in, 8in x 5in or 6 1/2in and 3 1/2in cutout		13in x 8in cutout	3-25
	2-45	18in x 11in x 9in with 13in x 8in cutout for EMI 350	4-25
			P. & P. each 0-35
17in x 10in x 6in with 8in or			
MICROPHONES		TW206	
CM20 Crystal Hand	0-50	CONDENSER MIKE 600 ohm, uni-dir	7-90
CM70 Planet stick metal, switch crystal	1-55	Cassette Stick Mike with R. Control on/off switch (2-5 and 3-5mm J/Ply)	1-85
DM160 Dynamic uni-dir, ball metal	3-95	Lapel, type, crystal	0-40
UD130 50K/600 ohm, uni-dir, ball metal	4-50		P. & P. 0-15
SOLDERING IRONS		spare Bib, etc.)	
ANTEX CN240 15W	1-60	X25 25W (low leakage)	1-60
SK1 Kit (15 watt iron, 2			P. & P. 0-10
CARTRIDGES		9THAC/G 8 1/2in fit, stereo cer. diam.	
ACOS GP91/28C or GP91/38C Stereo comp	1-00	19-TI Stereo crystal	0-80
GF93/1 Stereo crystal	1-35	BR SC5M Stereo ceramic	2-25
GF94/1 Stereo crystal	1-75	SX6H Stereo crystal	1-60
GF96/1	1-35	SX5M Stereo crystal	1-60
GF96/1	1-75	X5H Mono/stereo	1-25
GP101	0-75	X5M Mono/stereo	1-25
SONOTONE 9THAC Stereo ceramic, diam.	1-80	GOLDRING G800 G850	3-35
			2-85
			P. & P. 0-05
STYLI FOR ABOVE CARTRIDGES—		GOLDRING G800	
Soapstone	0-85	G850	1-95
D. Diamond	1-25		P. & P. 0-03
BATTERY ELIMINATORS		socket) 6, 7-5 or 9 d.c. output at 300mA	
240V input 6, 7-5 or 9 300mA	2-20		2-20
12V d.c. input (fits in car lighter)			P. & P. 0-10
TAPES		7in 65p 95p	
5in	Std. 45p LP 55p DP 70p	P. & P. 1-3 each	0-09
5 1/2in	55p 65p 85p	4 or more lot	0-30
LOW NOISE CASSETTES		Cassette Head Cleaner	
C60	1-5 35p 6-10 38p 11-20 30p	P. & P. 1-5 each	0-85
C90	35p 45p 48p 40p	6-10 lot	0-03
C120	55p 52p 60p	11-20 post free	0-15
PLASTIC LIBRARY CASES for 5in Reels		7in Reels	
5in Reels	0-18	P. & P. 1-3 each	0-05
6 1/2in Reels	0-22	4 or more	0-20
CASSETTE CASES			0-10
BIB ACCESSORIES		Book, Ref. 66	
Compact Tape Head Cleaning Kit, Ref. J	0-45	Stylus Balance, Ref. 32A	1-15
Tape Editing Kit, Ref. 23	1-30	Spirit Lever, Ref. 46	0-50
Recording Tape Splicer, Ref. 20	1-15	Cassette Case (holds 12 cassettes) Ref. 34	1-00
Cassette Tape, Editing, Ref. 24	1-40	Hi-Fi Stereo Test Cassette	1-80
Cassette Salvage Kit, Ref. 29	0-40	Groove-Kleen Record Cleaner	1-80
Hi-Fi Stereo Hints and Tip			P. & P. 0-10

Send 25p for COMPLETE CATALOGUE, refundable upon first order. ALL OUR MERCHANDISE IS FULLY GUARANTEED

Riversdale Electronics

Mail Order Department PE/11
P.O. Box 470, Manchester M60 4BU.

MAPLIN ELECTRONIC SUPPLIES

★ SAME DAY SERVICE



LARGE OR SMALL Centurion

PROJECTS DESERVE A PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction. Top, base, sides and detachable rear panel, blue hammer detachable front panel finished in white.



Dimensions in inches.

Model	W	H	D	Price
120	6	2 1/2	4	£1.85
220	8	6	3 1/2	£2.65
221	8	6	6	£2.80
320	12	8	12	£5.00

Chassis for model 320 £1.75 extra.

Please send s.a.e. for free illustrated leaflet.

ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator. ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3 1/2" x 4 1/2". ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed. DMO2T (with tremulant) ONLY £14.25. DMO2 (without tremulant) £12.25.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.63 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

★ S.a.e. please for full technical details.

Trade enquiries welcome.



MAPLIN: Projected site of London's third airport.

P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We shall be stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboards. Send s.a.e. now for our detailed price lists.

YOU SIMPLY MUST SEE OUR PRICES!

Spring line reverberation unit (as specified)	£2.69
uA 7815 (15V 1.5A) voltage regulator	£2.30
REc 41A bridge rectifier	£1.06
741C 8-pin DIL	36p
MFC 6040 electronic attenuator	£0.95
SG 3402N for Ring Modulator	£1.69

CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1 63 6p	68	6.3 6p	6p
1.5 63 6p	68	16 6p	6p
2.2 63 6p	68	63 10p	6p
3.3 63 6p	100	4 6p	6p
4.7 63 6p	100	10 6p	6p
6.8 40 6p	100	25 6p	10p
6.8 63 6p	100	40 6p	12p
10 25 6p	100	63 12p	18p
10 63 6p	150	6.3 6p	12p
15 16 6p	150	16 6p	12p
15 40 6p	150	25 6p	18p
15 63 6p	160	40 10p	22p
22 10 6p	150	63 12p	1000 4 10p
22 25 6p	220	4 6p	1000 10 12p
22 63 6p	220	10 6p	1000 16 18p
33 6.3 6p	220	16 6p	1000 25 22p
33 16 6p	220	25 10p	1500 6.3 12p
33 40 6p	220	40 12p	1500 10 18p
47 4 6p	220	63 18p	1500 16 22p
47 10 6p	300	4 6p	2200 6.3 18p
47 25 6p	330	10 6p	2200 10 22p
47 40 6p	330	16 10p	3200 6.3 22p
47 63 6p	330	63 22p	4700 4 22p

Tantalum Bead

Mfd V	Price	Mfd V	Price
0-1 35 12p	10	16 14p	10p
0-22 35 12p	10	25 16p	10p
0-47 35 12p	15	16 18p	10p
1.0 35 12p	22	16 18p	10p
2.2 35 12p	47	6.3 18p	10p
4.7 35 14p	100	3 18p	10p

Trimmers—compression type

3 to 40pF	13p	20 to 250pF	18p
30 to 140pF	13p	100 to 500pF	21p

Silver Mica 50pF ± 1pF, ≥ 50pF ± 1%
2.2, 3.3, 5, 10, 18, 20, 22, 25, 27, 30, 33, 39, 47, 50, 56, 68, 75, 82, 100, 120, 150, 180, 200, 220 7p; 250, 270, 300, 330, 390, 470, 500, 560, 680, 820 8p; 1000, 1500 10p; 1800 11p; 2200 13p; 2700 16p; 3600 18p; 4700, 5000 20p; 6800 27p; 8200, 10,000 34p.

MIXED DIELECTRIC

1000VDC; 300VAC; Non-inductive.
0.001uF, 0.0022uF, 0.0033uF, 0.0047uF 7p;
0.01uF, 0.022uF 10p; 0.047uF, 0.1uF 12p;
0.22uF 23p; 0.47uF 30p.

POLYESTER FILM METALLISED 250VDC

0.01uF, 0.015uF, 0.022uF 3p; 0.033uF, 0.047uF, 0.068uF 3p; 0.1uF 4p; 0.15uF 4p;
0.22uF 5p; 0.33uF 7p; 0.47 8p; 0.68uF 12p;
1uF 14p; 1.5uF 21p; 2.2uF 25p.

Wide range of transistors, diodes and I.C.'s in stock see our catalogue for details.

PLUGS AND SOCKETS



DIN PLUGS	MAINS	RS8 8 way chassis socket	Std. 1" stereo plug
2 pin (1 flat) 8p	P360 3 pin 1.5A chassis plug with 1 line socket. Per pair 24p	SA 2190 3 pin 5A chassis plug 17p	Plastic 16p
3 pin 9p	SA 1862 Line socket for above 19p	SA 1862 Line socket for above 19p	Screened 25p
4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 10p	McMURDO	PHONO	Open mono socket 1" 10p; Moulded mono socket 1" with 2 break contacts 2p; Moulded stereo socket 1" with 3 break contacts 18p;
DIN Sockets	RP8 8 way chassis plug 36p	JACK	3.5mm. plug plastic 8p; screened 11p; open socket 8p.
2 pin 6p			
3 pin, 4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 7p			

WIRE & CABLES

Hook-up wire, 7 strand 0.2mm. PVC covered tinned copper wire for light general connexions up to 1.4A. 11 colours: black, blue, brown, green, grey, orange, pink, red, violet, white, yellow. 10 metres of any one colour 15p. Pack of 11 (1 of each colour) 10m. coils £1.50.

Single core screened 6p per metre.
Twin individually screened 8p per metre.
High quality single screened 50Ω 100pF per metre, ideal for high grade audio connexions 11p per metre.

Extra flexible 55 strand 0.1mm. PVC covered plain copper wire rated at 6A. Ideal for test leads etc. Red or black 4p per metre.

Mains 3-core miniature 2.5A black PVC covered 13 strand 0.2mm. per conductor 71p per metre.

POTENTIOMETERS

Rotary miniature carbon track 1/4" spindle

Single gang Lin or Log
5k, 10k, 20k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 12p

Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 38p.

Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 23p

PRESETS
Sub-miniature 0.1W Vert or Horiz.
100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 6p

Wirewound 10% 1W 1/4" spindle 10, 50, 100R 34p; 250, 500, 1k, 5k 33p; 10k, 37p; 25k 40p; 50k 44p.

RESISTORS

Carbon Film 1W 5% 1Ω to 1M; 10% 1.2M to 10M E12 1p	Carbon Film 1/2W 5% 1Ω to 10Ω; 10% 1.2M to 10M E12 1p
Carbon Film 1/4W 5% 1Ω to 910k E12 & E24 1p	Carbon Film 1/4W 5% 10Ω to 10M E12 3p
Carbon Film 1W 5% 10Ω to 10M E12 3p	Metal Oxide 1/2W 5% 10Ω to 1M E12 & E24 4p
Wirewound 2 1/2W 10% 0.22ohms to 0.47ohms E12 10p	Wirewound 2 1/2W 5% 1ohm to 270ohms E12 10p
E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades	E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

KNOBS

All 1/4" shaft. Grub screw fixing

Diameter shown in brackets

K30/1 (13mm) 24p; K30/3 (17mm) 22p; K30/2 (13mm) 26p; BK12 32mm long, black pointer with white stripe 6p; K30/8 (32mm) 41p; F18 (26mm) with number-etal skirt 21p; F12 (33mm) 21p; MK50 (34mm) 27p; CK4 (36mm) 141p

SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 24p.
Mains rotary DPDT 250V 2A 20p.

Push to make non-locking 12p

Slide Miniature DPDT 8p

Sub-miniature toggle DPDT (12 x 12.5 x 14mm excl. toggle) 250V 3A 61p

Toggle 250V 1.5A with ON/OFF plate 25p.

VAT Please add 10% to the final total.

For our fully illustrated catalogue please send 9p in stamps. Post and Packing FREE in U.K. (10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex.

Audio

THE HI-FI MAGAZINE FOR LEISURE LISTENING

Britain's exciting new-style magazine in music and hi-fi, AUDIO is about every important aspect of the modern sound scene—from the make-up of sound, to the latest means of reproducing it... the equipment, its installation and its operation. AUDIO examines new trends, looks at the latest discs and tapes, shows you how to get the most for your money—in clarity, definition and craftsmanship.

IN THE NOVEMBER ISSUE

OUT FRIDAY OCT. 19

**Exclusive interview with André Previn.
Tape recording for beginners. Is that heavy
turntable really necessary. Up-to-the-
minute report on Video. Record reviews.**



**DON'T MISS
THIS ISSUE
20p**

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V

All Types from 1 to 50 amp from stock.

SHROUDED TYPE
 1A £7. Post 50p 10A £22.50
 2.5A £8.05. Post 15A £25
 60p 20A £49
 5A £11.75. Post 30A £82
 75p 50A £98

CARRIAGE AND PACKING EXTRA unless shown (Panel Mounting)
OPEN TYPE
 1 amp £7, Post 50p. 2½ amp £8.05, Post 60p.



2.5 amp
 OPEN TYPE

L.T. TRANSFORMERS

All primaries 220-240V	Sec. Taps	Price Post
1 30, 32, 34, 36V at 5A		£4.70-45p
2 30, 40, 50V at 5A		£6.90-40p
3 10, 17, 18V at 10A		£5.90-50p
4 6, 12V at 20A		£6.50-60p
5 17, 18, 20V at 20A		£7.30-60p
6 6, 12, 20V at 20A		£6.90-60p
7 24A at 10A		£5.30-40p
8 4, 6, 24, 32V at 12A		£7.20-60p
9 6, 24 and 12V at 10A		£3.80-40p

RING TRANSFORMERS

Functional Versatile Educational
 These multi-purpose Auto Transformers, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer, by simply hand winding the required number of turns through the centre opening. By using the RT.100V VA Model the output could be wound to give 8V @ 12A, 4V @ 25A or 2V @ 50A, etc. Price:

RT.100VA 3-18 turns per V. £3.00, Post 35p.
 RT.1KVVA 1-82 turns per V. £8.60, Post 50p.
 RT.2KVVA 1-5 turns per V. £14.00, Post 75p.
 RT.3KVVA 1-5 turns per V. £19.00, post £1.

VOLTAGE CHANGING TRANSFORMER
 M.f.g. to highest W.D. spec. Auto wound, and tapped 0-130-160-200-250 at least 2kVA. Can also be used as 230-240V input, 115V out for U.S.A. equipment, or reverse to obtain 240V from 115V. The ideal transformer for making up solid state constant voltage unit, by use of taps the following voltages may be obtained 30-40-50-70-90V at 10 amps. Weight 40lb., length 260mm., height 190mm., width 230mm. In original maker's wooden case, £8. Carr. £1.

PARVALUX Type: SDI. S/86896/OJ
 230/250V A.C. 50 r.p.m. 7 lb/in. Continuously rated. £6. Post 30p incl. base.

600 WATT DIMMER SWITCH
 Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p.

2000 WATT POWER CONTROL
 For Power tools, Heating, Sewing Machines, Lighting, etc. £8.00. Post 27p.

VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp contacts. Fitted diecast case. Tested and in perfect condition £4.75. Post 25p.

FOOT SWITCH
 Suitable for Motors, Drills, etc. etc. 5 amp. 250 volt. Price 75p. Post 15p.

UNISELECTOR SWITCHES
NEW 4 Bank 25 Way,
 24V d.c. operation. £6.90. Post 30p.
6 Bank 25 Way, 24V d.c.,
 £7.90. Post 30p.
8 Bank 5 Way, 24V d.c. operation.
 £9.50. Post 40p.

TRIACS
GENERAL ELECTRIC POWER-GLAS TRIACS
 10 amp. Glass passivated plastic triac. Latest design from U.S.A. Long term reliability. Type SC146D 10 amp, 400 PIV, £1, Post 5p. Type SC146E 10 amp, 500 PIV, £1.30, Post 5p. (Inclusive of data and application sheet.) Suitable Dia 18p.

All Mail Orders—Callers—Ample Parking
Dept. PE11, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
 Phone 01-995 1560
 Showroom open Mon.-Fri.

STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
 Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £6.30. Post 30p.

NEW INDUSTRIAL KIT
 Ideally suited for schools, laboratories, etc. Speed adjustable 1-80 f.p.s.
 Approx. ½ output of Hy-Lyght. Price £10.50. Post 50p.

HY-LYGT STROBE MK III
 For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £12. Post 50p.

THE 'SUPER' HY-LYGT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe.

● Variable speed from 1-3 flash per sec.
 ● Reactor control circuit producing an intense white light. ONLY £20. Post 75p.

ROBUST, FULLY VENTILATED METAL CASE. For Hy-Lyght Kit including reflector £4.75. Post 25p.

Super Hy-Lyght Kit including reflector £7. Post 60p.

7-inch **POLISHED REFLECTOR** Ideally suited for above Strobe kits. Price 55p. Post 15p.

RAINBOW STROBE FOUR LIGHT CONTROL MODULE

Will operate four of our Hy-Lyght or Super Hy-Lyght Strobes in either 1, 2, 3, 4 sequence; 2 + 2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: £18. Post 50p. Send S.A.E. for details.

COLOUR WHEEL PROJECTOR

Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £18.50. Post 50p.

6 INCH COLOUR WHEEL
 As used for Disco lighting effects, etc. Price £5. Post 30p.

1 R.P.M. MOTOR
 220/240 volt a.c., 1 r.p.m. synchronous motor. 2 watt. A/clock. Spindle 10mm long. 3mm dia. Motor only 20mm deep. Fixing centres 44mm. Price £1-10. Post 5p. Suitable for above wheel.

BIG BLACK LIGHT
 400Watt Mercury vapour ultra violet lamp.

Powerful source of u.v. Innumerable industrial applications also ideal for stage, display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16. Post £1. Spare bulb £7. Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES
 4ft 40 watt. Price £5.50, Post 30p. 2ft 20 watt. £4.25. Post 25p. (For use in stan. bi-pin fittings.)

MINI. 12in 8 watt, £1-60. Post 15p. 9in 6 watt, £1-30. Post 15p. Complete ballast unit and holders for 9in and 12in tube. £1-70. Post 25p. (9in and 12in measures approx.)

ELECTRONIC ORGAN KIT
 Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1½V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3.25. Post 35p.

50 in 1 ELECTRONIC PROJECT KIT
 50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7-75. P. & P. 25p.

TRIACS
GENERAL ELECTRIC POWER-GLAS TRIACS
 10 amp. Glass passivated plastic triac. Latest design from U.S.A. Long term reliability. Type SC146D 10 amp, 400 PIV, £1, Post 5p. Type SC146E 10 amp, 500 PIV, £1.30, Post 5p. (Inclusive of data and application sheet.) Suitable Dia 18p.

All prices are subject to
10% VAT. (10p in the £)
 To all orders add 10% VAT to total value of goods including carriage/packaging.

SERVICE TRADING CO

Superior Quality Precision Made

NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.

25 WATT 10/25/50/100/250/300/500/1k/ohm 95p. Post 10p.
50 WATT 1/5/10/25/50/100/250/500/1k/1.5k/ohm £1-35. Post 10p.
100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k ohm £1-95. Post 15p.
Black Silver, Skirted knob calibrated in Nos. 1-9. 1½in. dia. brass bush. Ideal for above Rheostats, 20p each.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1)	1	2	3	4
Coil ohms				
Col. (2)	52	4-6	6M	60p*
Working d.c. volts	150	6-12	4 c/o	80p*
	185	8-12	6M	60p*
	280	8-16	2 c/o	60p*
Col. 3	410	10-18	4 c/o	70p*
Contracts	700	16-24	4M 2B	60p*
	700	16-24	4 c/o	80p*
Col. (4)	700	15-35	2 c/o HD	70p*
Price	700	16-24	6M	60p*
	700	6-12	1 c/o HD	50p*
HD= Heavy duty	700	20-30	6 c/o	80p*
	1,250	24-36	4 c/o	60p*
	2,500	36-45	6M	60p*
Incl. Base	2,400	30-48	4 c/o	50p
	9,000	40-70	2 c/o	50p*
All prices incl. P. & P.	15k	85-110	6M	50p*

9 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 5p.
12 VOLT D.C. RELAY
 3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 5p.

230 VOLT A.C. 'DIAMOND H' RELAYS (Unused)
 Three sets c/o contacts rated at 5 amps. PRICE: 55p. Post 5p. (100 lots) £40.
 24 volt A.C. 3 c/o 55p. Post 5p.

MINIATURE LATCHING RELAY
 Manufactured by Clare-Elliott Ltd. Type F. 2 c/o permanent latching in either direction. Coil 1150 ohm. 15-30 Volt D.C. Size 1/4" high, 1/2" wide, 1/4" thick. Complete with 3in. leads. New 65p. Post 5p.

BLOWER UNIT
 200-240 Volt A.C. Precision German built. Dynamically balanced, quiet, continuously rated, reversible motor. Consumption 60mA. Size 120 mm. dia. x 60 mm. deep. Price £3. Post 30p.

4 BANK 3c/o PUSH BUTTON ASSEMBLY
 Black rectangular buttons. 5 units (min. order) 85p. Post 15p.

'HONEYWELL' PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY
 Each bank comprises a c/o rated at 10 amps 240V. A.C. Black knob in. Fixing hole 3/8 in. ONE bank 30p; TWO bank 40p; THREE bank 50p. Quote for quantity.

VERY SPECIAL OFFER
 Micro Switch. 5 amp c/o contacts. M.f.g. bg. Honeywell. NEW. Twenty for £1-50. Post 10p (min. 20).

'HONEYWELL' LEVER OPERATED MICROSWITCH
 15 amps 250 volt A.C. c/contacts. In maker's carton. PRICE: 10 for £1-90, Post 15p.

INSULATION TESTERS NEW!
 Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L Bin, W 4in, H 6in, weight 6lb., 1,000V, 1,000 megohms, £34. Post 60p. 500V, 500 megohms, £28. Post 60p.

BALANCE/LEVEL METERS
 100-100 Micro Amp. Size 1½in x 1½in x 1in. Price only 70p. Post 5p.

METERS NEW! 2½in. Flush round. Available in D.C. Amps 1, 5, 10, 15, 20 or A.C. Amps 1, 5, 10, 15, 20, both types £2.00. Post 15p. Voltmeter 0-300V A.C. £2. Post 15p.

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
 Phone 01-437 0576

SPECIAL INTRODUCTORY OFFERS—IMPORTER TO CONSUMER!

ALL NEW GOODS—FULLY GUARANTEED—PLEASE ADD VAT TO TOTAL PRICES

HILLS HEADPHONE JUNCTION BOX MODEL JB-3
Designed to connect headphones to amplifier previously not fitted with headphone socket, or alternatively for remote switching. 3 position switch allows instant switching between speakers and headphones or both simultaneously.
Rec. Retail £1.75
OUR PRICE £1.25 P & P 15p



HILLS DYNAMIC HEADPHONE MODEL H-707 VS DE-LUXE
An extremely high quality headphone supplied with Padded Headphone and Earcups together with SLIDER volume controls for precise listening levels. Specially offered at an unbeatable price. 8 ohms. 20-20,000Hz.
Retail Price £7.95
OUR PRICE £5.75 P & P 25p



CAR STEREO SPEAKERS MODEL CRB-200
These dual purpose Car Speakers can be used for either shelf mounting or converted to door mounting. 5in 5 watt Speakers ensure a brilliant audio performance.
Rec. Retail £5.25* *Per pair
OUR PRICE £3.50* P & P 25p



Antex Soldering Iron CCN240, Rec. Retail £2.15. Our Price £1.80. P & P 10p
Antex Soldering Iron X25, Rec. Retail £1.93. Our Price £1.40. P & P 10p
Ferranti Radio Chip ZN414, Our Price £1.10. P & P 5p
Hills Coiled Headphone Extension Cable 15ft. Rec. Retail £2.25. Our Price £1.45. P & P 10p

"HOMER" INTERCOM
One of the leading makes. Ideal for home, office, factories, etc. This 2 station Intercom includes volume control and on-off switch. Supplied with 66ft. cable and batteries.
Rec. Retail £3.50
OUR PRICE £2.75 P & P 15p




HILLS DYNAMIC HEADPHONE MODEL H-101 VSM
Offered at a remarkably low price. Supplied with padded Headband and Earcups, adjustable volume controls with stereo and mono switch. 8 ohms imp., 30-18,000Hz.
Rec. Retail £5.25
OUR PRICE £3.75 P & P 25p




PLINTH AND COVER FOR GARRARD Sp-25 III BSR MP-80. Our Price £2.75, plus 65p P. & P.
ELAC SPEAKER, 8In 8 ohm CERAMIC AND TWEETER. £2.70, plus 20p P. & P.
OTHER ITEMS AT BARGAIN PRICES OFFERED IN OUR AUDIO COMPONENTS CATALOGUE. PLEASE WRITE FOR A FREE COPY (ENCLOSING 3p STAMP).
VAT Please add 10% to the total value of goods including postage and packing.

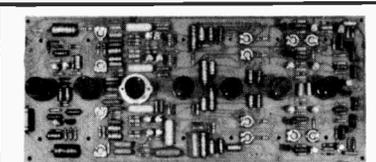HILLS COMPONENTS LTD.
UNIT No. 6, MELINITE INDUSTRIAL ESTATE, BRIXTON ROAD, WATFORD, HERTS. WD2 5SL. Tel. Watford 27711



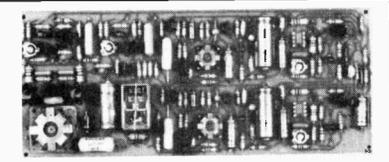PHONOSONICS NEW LOW PRICES FOR MANY PCB'S AND KITS



AURORA
Multichannel Sound Controlled Light (PE Apr./Aug. 71). S/c's (excl. SCR's), Rs, Cs, Pots, Cores—8 ch. £17.90; 4 ch. £9.95. Reg. PSU £3.65. PCB—4 ch. control (4 1/2in x 10 1/2in) Mk. 2—also holds rotary or slider pots £2.20. PCB (4 1/2in x 5in) Mk. 2—for PSU, Sync Gen. 8 cores, 8 SCR's, £1.10. SCR's—1A, 50p.

A. F. SIGNAL GENERATOR
(PE Nov. 72). S/c's, Rs, Cs, Pots, S/w's. PCB (2 1/2in x 4in) also holds S/w's, £3.15.

BIOLOGICAL AMPLIFIER
(PE Jan./Feb. 73). P/A Set—S/c's, i.c.'s, Rs, Cs, Pots, PCB (1 1/2in x 3 1/2in), £3.50. O/P Stages (S/c's, Rs, Cs, Pots and S/w's as reqd.). Alphaphone 53P, Cardiophone 66p, Freq. Meter £1.60, Vis-Feedback 55p. Audio Amp PC7 avail. to order £5.20.

LOUD-HAILER AND SIREN
(Pre-amp and Siren Generator)
(PW Dec. 72). S/c's, Rs, Cs, Pot, PCB (2 1/2in x 2 1/2in), £2.20 (White stocks last). Main Amp Module PC5+ obtainable to special order, £6.

ELECTRONIC PIANO
(PE Sep. 72/Jan. 73). PCB PRICES DOWN. Details in lists.

GEMINI STEREO AMPLIFIER
(PE Nov. 70/Mar. 71) Stereo Sets & PCBs. Pre-amp—S/c's, £1.80. Rs, Cs, Pots, Mks—S/w's—with 1/2W MO Rs, £10.90—with 1/2W or 1/4W CF Rs, £8.90. PCB (3 1/2in x 10 1/2in) for sets with MO and 1/2W Rs, also holds rotary or slider pots and Mks—S/w's, £11.90. Main Amp—Rs, Cs, Pots, £5.20. PCB (3 1/2in x 5in), £1.15. PSU—Rs, Cs, Pot, £3.70. PCB (2in x 4in), 65p.

GEMINI STEREO TUNER
(PE Apr./Jun. 72). Rs, Cs, Pot, £3.80. PCB as publ., £1.50.

8 WATT AMPLIFIER
(PW Nov./Dec. 72). Pre-amp—S/c's; Rs, Cs, Pots, S/w—Mono, £2.50; Stereo, £5.20. PCB (3 1/2in x 7 1/2in) (Stereo) also holds rotary or slider pots and S/w, £1.50. Main Amp—S/c's, Rs, Cs, Pot—Mono, £3.65; Stereo, £7.30. PCB (2 1/2in x 3in) Mono), 60p.

MICROPHONE MIXER
(PE Apr. 69). S/c's, Rs, Cs, Pots, £2.60. PCB (3 1/2in x 4 1/2in) also holds 6 rotary or 4 slider pots, £1.10.

LOGICAL RADIO CONTROL AND MODEL SERVO CONTROL
(PE Feb./Jun. 72)—Details in lists—Hurry not many left!

REVERBERATION UNIT
(PW Nov./Dec. 72). S/c's, Rs, Cs, Slider Pots, T/fmr, £6.80. PCB (2in x 1 1/2in) also holds sliders, £1.20. 9in Spring Unit avail. to order, £3.75.

VIBRASONIC GUITAR PRE-AMP
(PW Sept. 70). Incl. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume. S/c's, Rs, Cs, LDR, Rotary Pots, Lamp, Coupling T/fmr, £6.65. PSU, £2.80. PCB (3 1/2in x 10 1/2in) Mk. 2, also holds 7 rotary or slider pots, £1.75.

HI-FI TAPE LINK
(PE Mar./Apr. 73). S/c's, i.c.'s, Rs, Cs, Relay and pc-base, Pot Cores and pc-bases, S/w's, Pots, Panel Lamp—Mono, £11.80; Stereo, £18.70. PSU, £2.50. PCB—Main Circuit (3 1/2in x 9in) (Stereo) also £2.50. PCB—Sub-Assembly. (2 1/2in x 6 1/2in) (Stereo) Mk. 2 holds sliders and cores, £1.85. PCB—Sub-Assembly. (2 1/2in x 6 1/2in) (Stereo) Mk. 2 holds Sw, Rs, Cs, Presets and mounts on S/w's, 80p.

ULTRASONIC TRANSMITTER-RECEIVER
(PE May 72). S/c's, Rs, Cs, Pot, Relay, Dual PCB (2in x 5 1/2in), £3.90. T/ducers avail. to order, £6.30 per pair.

TAPE NOISE LIMITER
(PE Feb. 72). S/c's, Rs, Cs, Pot, PCB (1 1/2in x 3in), £2.20. Reg. PSU and PCB (1 1/2in x 2 1/2in), £3.10.

VERSATILE LIGHT EFFECTS UNIT
Single Channel Sound Controlled Light with built-in variable strobe. (PE June 72). S/c's, Rs, Cs, Pots, T/fmrs, Keyswitch, £8.85. PCB (3 1/2in x 7 1/2in) Mk. 2, also holds pots, Sw, T/7 T/fmr, £1.50. SCR's—1A, 50p.

ALSO
PCBs as published (while stocks last) for:
DIGITAL PSU (PE Aug. 72), 50p
OSCILLOSCOPE P/A (PE Aug. 72), 33p
SCORPIO (PE Nov./Dec. 71), 60p
TRIFFID (PE Feb. 73), 60p

PHOTOPROCESS CONTROL
(PE Jan./Feb. 72). For colour and B & W—finds exposure, controls timing, stabs, mains voltage. S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keyswitch, T/fmr, £7.50. PCB (3 1/2in x 5 1/2in) also holds pots, Sw, relay, £1.20.

AND
DIGITRONIC (PW Mar. 73). Read-out PCB (1 1/2in x 3 1/2in), 60p.

SOUND SYNTHESIZER
(PE 1973)
Details of PCBs & Components in lists. SOME PRICES DOWN.

SEMICONDUCTORS

AC128	20p	ZTX531	22p
AC176	20p	2N706	13p
AD161	40p	2N914	22p
BC107	9p	2N1304	20p
BC108	9p	2N2905	23p
BC109	9p	2N2907	22p
BC147	11p	2N3702	10p
BC148	11p	2N3704	10p
BC149	11p	2N3823E	31p
BC157	12p	2N5777	40p
BC158	12p	2N914	4p
BC159	12p	1N4001	6p
BC204	14p	1N4002	7p
BCY71	22p	1N4004	8p
BFY51	16p	1N4005	10p
BSY95A	12p	BA145	17p
OC28	45p	OA91	7p
OC71	12p	OA200	7p
OC84	24p	Z1J	50p
ORP12	48p	741C	36p
T1543	24p	(8-pin DIL)	100/63
ZTX107	9p	µA7815	£2.47
ZTX503	14p	(TO3 can)	150/63

ELECTROLYTIC

		220/10	6p
		220/16	6p
	1.0/63	6p	220/25
	2.2/63	10p	220/40
	4.7/63	6p	226/63
	10/25	6p	330/10
	10/63	6p	470/6.3
	15/40	6p	470/25
	22/10	6p	470/40
	22/25	6p	470/40
	33/6.3	6p	500/64
	33/16	6p	680/6.3
	33/40	6p	680/25
	47/6.3	6p	1000/10
	47/25	6p	1000/25
	47/40	6p	1000/40
	47/63	6p	2200/25
	100/10	6p	2200/40
	100/25	6p	3300/63
	100/40	6p	3300/100
	100/63	6p	4700/16
	150/16	6p	4700/25
	150/63	12p	4700/40

CAPACITORS

		0.1/35	12p
		0.22/25	12p
		0.47/35	12p
		1.0/35	12p
		1.5/35	12p
		2.2/35	12p
		4.7/35	12p
		10/16	12p
		10/25	12p
		15/6.3	12p
		22/16	12p
		47/6.3	12p
		47/16	25p
		100/16	25p
		100/25	25p
		220/25	40p
		330/40	50p
		3300/63	11p
		3300/100	£3
		4700/16	60p
		4700/25	75p
		4700/40	93p

POLYESTER

C280AE	250V(µF)	0.01	3p
		0.015	3p
		0.022	3p
		0.033	3p
		0.047	3p
		0.068	3p
		0.15	4p
		0.22	5p
		0.33	7p
		0.47	9p
		0.68	11p
		1.0	14p

SWITCHES

Shaft assembly	48p
Wafers	33p
Screens	(per
pk of 5)	12p
Spacers	8p
pk of 10)	8p
Rotary:	
3P4V	30p
Multipole	3p
Lever:	
4CL/4CL	£1.30
4CL/4CN	£1.30
Knobs	6p
Slip:	
DPDT	24p

NEW!

RONDO (PE current series)	
PHASING UNIT (PF Sept. 73)	
ENLARGER EXPOSURE METER AND THERMOMETER (PE SEPT. 73)	
SEMICONDUCTOR TESTER (PE OCT. 73)	
WIND AND RAIN EFFECTS (PE OCT. 73)	
DETAILS IN LISTS	
TRANSFORMERS (MAINS)	
Sub-min 12V-0-12V 50mA	£1.30
Min 0-6V 0-6V 6VA	£1.30
Min 0-12V 0-12V 6VA	£1.30
Min 0-20V 0-20V 6VA	£1.30
17 1/2V 1-6A	£1.88
0-25-30 0-25-30V 1-5A	£3.60

POST & PACKING
U.K. 10p per order. EXPORT at cost—please allow for this when ordering and also state whether air or surface mail required—kit weights are shown in our list.

V.A.T.
U.K. Orders only—add 10% to total cost or order.

LIST
S.A.E. for free itemised list and with all enquiries please.


GENERAL
All PCBs Fibreglass, Drilled, Roller-Tinned. Layout and Circuit Diagrams Free with each PCB. Unless stated "as published", PCBs are designed by Phonosonics. Pots are rotary unless stated as slider. All components are brand new, top quality, guaranteed. Prices and deliveries of individual components subject to stock availability.

PHONOSONICS, DEPT. PE11, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW **MAIL ORDER ONLY**


now...

Project 80

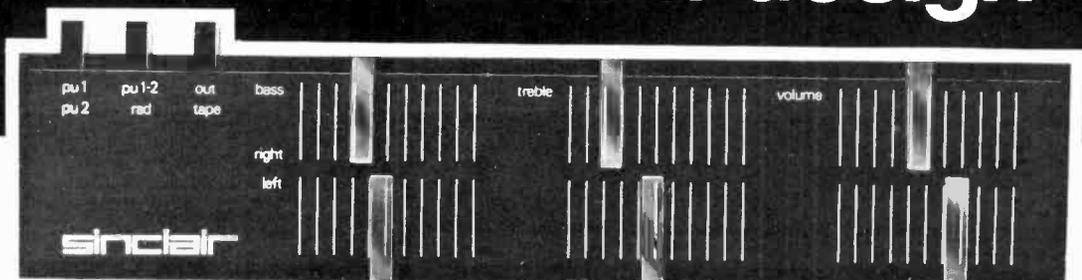... exciting new thinking
in modular hi-fi design




Stereo 80 pre-amplifier/control unit

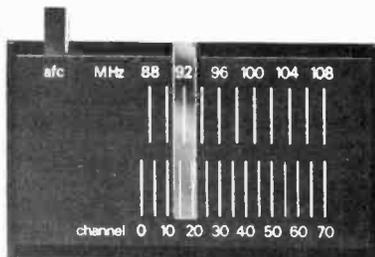

Project 80 tuner



Stereo decoder

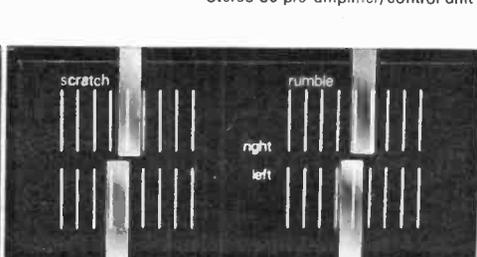

Project 80 Active Filter Unit (AFU)

the slimmest, most elegant hi-fi modules ever made



Living with hi-fi takes on new meaning now that Project 80 is here. These amazing new modules mark a brilliant technical advance all round; their size and presentation bring exciting new opportunities to install systems in ways hitherto only dreamed about but never before made practical. You can build a Project 80 system virtually anywhere and it is unbelievably simple to install and connect up. Everything that could possibly be wanted in a top quality do-it-yourself domestic hi-fi system will be found in Project 80 - compactness, elegantly ultra-modern styling, ease of fixing and operation, new control methods, and above all superb performance. New as well as popular established ideas on installation are featured on page four of this announcement to provide just a few examples of the system's fantastic versatility.

sinclair

INTERNATIONAL AUDIO FAIR STAND 58

Project 80 new modules


Stereo 80 pre-amplifier and control unit

As with other Project 80 units, the Stereo 80 is mounted by means of two bolts fixed at the rear which pass through holes drilled in the wood or plastic on which modules are to be mounted. *All the electronics are contained within the $\frac{3}{4}$ " deep front panel!* Connecting leads are taken away similarly out of sight. Each channel in the Stereo 80 has its own independent tone and volume controls operated by sliders. This enables exceptionally good environmental matching to be obtained. Provision is made for magnetic and ceramic pick-ups, radio and tape in and out. A virtual earth input stage forms part of the up-dated circuitry of the Stereo 80 to ensure the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

TECHNICAL SPECIFICATIONS


Size - 260 · 50 · 20mm ($10\frac{1}{4}$ · 2 · $\frac{3}{8}$ ins)
 Finish - Black, with white markings
 Inputs - Mag P U 3mV RIAA corrected; Ceramic P U. 300 mV
 Radio 300 mV; Tape 30 mV
 S/N ratio - 60db
 Frequency range - 20Hz to 15KHz · 1dB · 10Hz to 25KHz \pm 3dB
 Power requirements - 20 to 35 volts
 Outputs - 100mV \pm AB monitoring for tape
 Controls - Press button for tape, radio and P U. selection Volume, Bass: 12dB to 14dB at 100Hz, Treble +11dB to -12dB at 10KHz

NEW

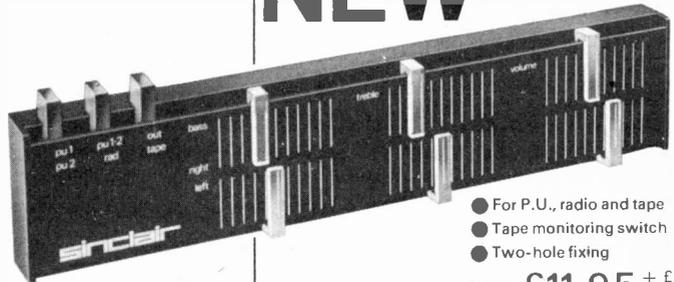

- For P.U., radio and tape
- Tape monitoring switch
- Two-hole fixing

R.R.P. **£11.95** + £1.19 V.A.T.

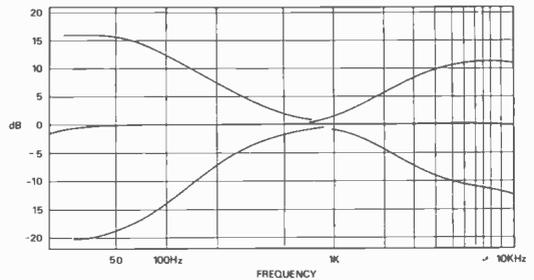


Project 80 FM tuner smaller, more efficient

A truly remarkable tuner in every way - its unbelievably compact size - its original circuitry - its dependable performance - all this in a boldly designed modern case measuring 85 · 50 · 20mm ($3\frac{1}{2}$ · 2 · $\frac{3}{8}$ ins). Greater adaptability (and possibly financial convenience) results from the tuner and stereo decoder section being made available separately.

TECHNICAL SPECIFICATIONS

Size - 85 · 50 · 20mm (approx $3\frac{1}{2}$ · 2 · $\frac{3}{8}$ ins)
 Tuning range - 87 to 108 MHz
 Detector - I.C. balanced coincidence, for good A.M. rejection
 AFC - Switchable, with thermistor control to prevent from drift
 One 26 transistor I.C.
 Twin dual varicap tuning
 Distortion - 0.3% at 1KHz for 75KHz deviation
 Ceramic filter in I.F. section
 Aerial impedance - 75 Ω or 240-300 Ω
 Sensitivity - 4 microvolts for 30dB quieting
 Power requirements - 12 to 45 volts

NEW

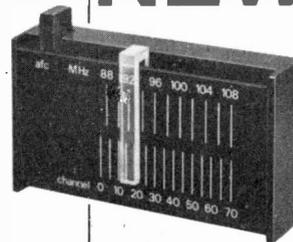

- AFC switch
- Twin dual varicap tuning
- 4-hole ceramic filter
- Slider tuning

R.R.P. **£11.95** + £1.19 V.A.T.

Project 80 stereo decoder

Making the Project 80 decoder separate from the F.M. tuner gives the constructor a wider choice of systems as well as saving money in cases where stereo reception may not be required. This unit gives a 40dB channel separation with an output of 150mV per channel. The gallium arsenide light emitting beacon automatically lights up to show when a stereo transmission is tuned in. Designed essentially as an integral part of Project 80 systems, this multiplex stereo demodulator may be used in many cases with existing single channel frequency modulated tuners to provide stereo reception.
 Size - 47 · 50 · 20mm ($1\frac{7}{8}$ · 2 · $\frac{3}{8}$ ins)
 One 19 transistor I.C.

NEW



- Solid-state stereo indicating beacon
- Readily adaptable for use with other tuners

R.R.P. **£7.45** + 0.74p V.A.T.

new constructional techniques

...and again Sinclair leads the world

- 1962 Micro-miniature power amp small enough to stand on a 10p. piece. Slimline pocket receiver smaller than a 20 cigarette pack
- 1963 Micro-6 receiver, smaller than a matchbox
- 1964 Pocket F.M. receiver, PWM amp.
- 1965 Z.12 power amplifier module, PZ.3 power supply
- 1966 Stereo 25 pre-amp/control unit
- 1967 Micromatic. Q.14 loudspeaker; the first Neoteric
- 1968 IC.10, the first ever integrated circuit for constructors' use

- 1969 Q.16 - improved version of Q.14 Systems 2000 and 3000: Project 60 launched
 - 1970 IC.12: Project 60S
 - 1971 Project 60 stereo FM tuner. Z.50: PZ.8
 - 1972 Improvements to Project 60 with Z.50 MK.2 and PZ.8 Mk.3 The Executive Calculator: Digital multi-meter Q.30 speaker
 - 1973 Cambridge Calculator
- PROJECT 80 LAUNCHED**


... and next ?

Project 80 active filter unit

This efficiently designed unit makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls are applied to each channel thereby making it easier to obtain ideal stereo balance in any kind of indoor environment

TECHNICAL SPECIFICATIONS

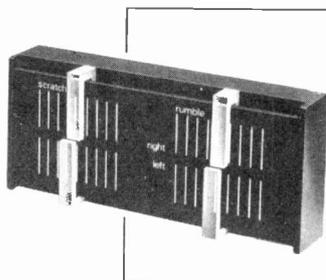Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/8 ins)
 Voltage gain - minus 0.2dB
 Frequency response - 36Hz to 22KHz, controls minimum
 Distortion - at 1KHz - 0.03% using 30V supply
 HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct. slope
 L.F. cut off (rumble) - 28dB at 20Hz, 9dB/oct. slope



NEW

- For scratch and rumble control
- Transistorised active circuitry


R.R.P. **£6.95** + 0.69p V.A.T.

Z.40 & Z.60 power amplifiers totally short-circuit proof

Either of these entirely new power amplifiers is intended for use in Project 80 installations although, of course, they are readily adaptable to an even wider range of applications. Both Z.40 and Z.60 incorporate built-in protection against shortcircuiting and risk of damage arising from mis-use is greatly reduced. Comprehensive instructions are supplied with each of the modules

Z.40 Technical Specifications
 Size - 55 x 80 x 20mm
 (2 1/8 x 3 1/8 x 3/8 ins) 9 transistors
 Input sensitivity - 100mV
 Output - 15 watts RMS continuous into 8 Ω (35V). 30 watts music power into 4 Ω (30V)
 Frequency response - 10Hz - 100KHz ± 1dB
 Signal to noise ratio - 64dB
 Distortion - at 10 watts into 8 Ω less than 0.1%
 Power requirements - 12-35 volts

Z.60 Technical Specifications
 Size - 55 x 98 x 20mm
 (2 1/8 x 3 7/8 x 3/8 ins) 12 transistors
 Input sensitivity - 100-250mV
 Output - 25 watts RMS into 8 Ω (45V). 50 watts music power into 4 Ω (50V)
 Distortion - typically 0.03%
 Frequency response - 10Hz to more than 200KHz ± 1dB
 Signal to noise ratio - better than 70dB
 Built-in protection against transient overload and short circuit
 Load impedance - 4Ω min, max safe on open circuit

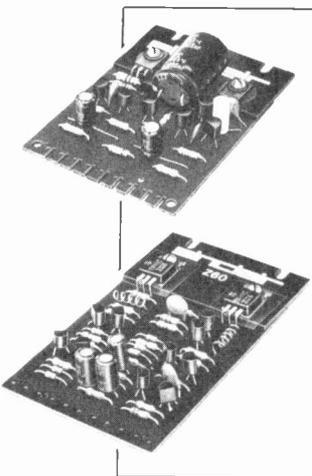

NEW


Z.40
 R.R.P. **£5.45** + 0.54p V.A.T.

Z.60
 R.R.P. **£6.95** + 0.69p V.A.T.

Sinclair power supply units PZ.8

the worlds most advanced unit in its class

Stabilised power supply unit. Re-entrant current limiting makes damage from overload or even direct shorting impossible, a principle never before incorporated in a commercially available constructor module. Normal working voltage (adjustable) 45V
 R.R.P. £7.98 + 0.79p V.A.T.
 Without mains transformer
 PZ.5 30V un stabilised
 R.R.P. £4.98 + 0.49p V.A.T.
 PZ.6 35V, stabilised
 R.R.P. £7.98 + 0.79p V.A.T.

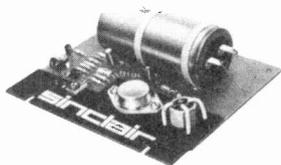

Recommended Project 80 applications

System	The Units to use	Units cost
Simple battery record player	Z.40	£5.45 + 54p V.A.T.
Mains powered record player	Z.40, PZ.5	£10.43 + £1.04 V.A.T.
30W. RMS continuous sine wave stereo amp.	2 - Z.40s, Stereo 80; PZ.6	£30.83 + £3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo	2 x Z.60s, Stereo 80; PZ.8	£33.83 + £3.38 V.A.T.
amplifier Indoor P.A.	Z.60, PZ.8	£14.93 + £1.49 V.A.T.
Car Radio	F.M. tuner, Z.40	£16.40 + £1.64 V.A.T.


sinclair

R.O. London Rd., St. Ives, Huntingdon PE17 4HS Reg. England 669483


Practical Electronics November 1973

From Sinclair the worlds most advanced hi-fi modules

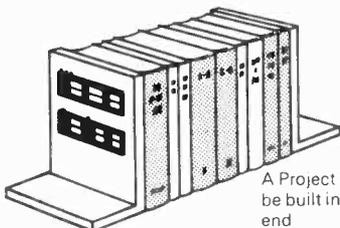
Sinclair Project 80 the ultra-modern non-obtrusive hi-fi



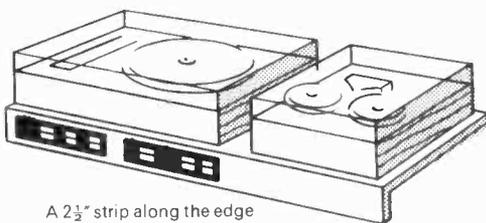
A Project 80 system could be built into a book-shelf end



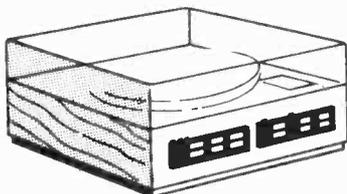
A 2½" strip along the edge a shelf could be sufficient to contain a complete system



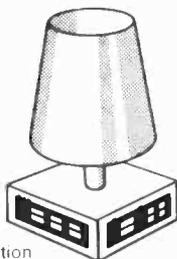
The modules mount very easily onto a playing plinth



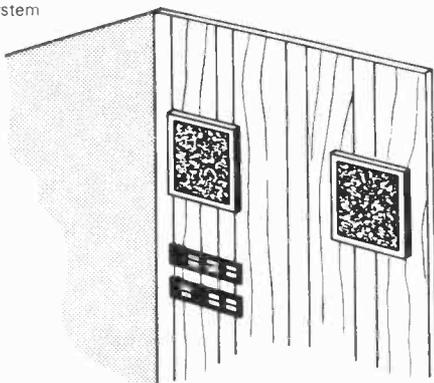
A novel application would be to build around the base of a lampshade



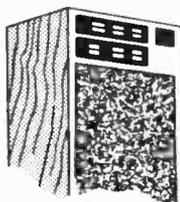Two Sinclair Q.16 loudspeakers suitably positioned together with Project 80 could be mounted on to a false wall.



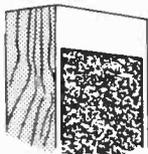Project 80 could be easily mounted onto a loudspeaker cabinet



When you have seen for yourself how fantastically slim and cleverly designed these modules are, further ways will suggest themselves in which they can become a pleasing part of your particular domestic environment.

To SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ

Please send post paid _____

for which I enclose Cash/Cheque for £ _____ including V.A.T.

Name _____

Address _____

PE11

Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed Stockists also offer this guarantee.

Should any defect arise in normal use, we will service it without charge. For damage arising from mis-use a small charge (typically £1.00) will be made.

sinclair

Sinclair Radionics Ltd.
London Road, St. Ives,
Huntingdon PE17 4HJ
Telephone St. Ives (0480) 64311

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

SITUATIONS VACANT

YOUR TALENT CAN EARN YOU MONEY

as a

T.V. Engineer

with

Radio Rentals

Britain's No. 1 T.V. Rental Company

Are you on the right lines in your present job? Switch to Radio Rentals and be assured a good future. Here are 5 star reasons for joining us.

- ★ Full Training given for Colour T.V.
- ★ 5-day week
- ★ Private use of a Company Vehicle or generous car allowance
- ★ 3 weeks' holiday per year, rising to 4 weeks
- ★ Good salary (up to £34.95 per week after 2 years)

Your present holiday arrangements will be honoured. Work towards a better future, better chances of promotion and more security. Telephone Mr. Mann, 01-540 1304 or write to:

RADIO RENTALS

86 The Broadway • Wimbledon • London • S.W.19

FOR SALE

TV LINE OUT-PUT TRANSFORMERS
Tidman Mail Order Ltd., 236 Sandycombe
Road, Richmond, Surrey TW9 2EQ
01-948 3702

CATALOGUE NO. 18, Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. **ARTHUR SALLIS RADIO CONTROL LTD.**, 28 Gardner Street, Brighton, Sussex.

AUDIO MIXER MODULES for hi-fi applications. Catalogue free. Large S.A.E. **HILLCREST ELECTRONICS**, 123 Harestone Hill, Caterham, Surrey.

FOR SALE Practical Electronics, Nov. '64 to Sept. '73. Unbound. Offers: **MR. ANGEL**, (01) 736 4057.

AUDIO MIXER MODULES. Catalogue free. Large S.A.E. **HILLCREST ELECTRONICS**, 123 Harestone Hill, Caterham, Surrey.

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. **K. R. WHISTON**, Dept. PE, New Mills, Stockport.

**ULSTER:
THE NEW UNIVERSITY**
INSTITUTE OF CONTINUING EDUCATION:
**MAGEE UNIVERSITY COLLEGE
LONDONDERRY**
C.C.T.V. TECHNICIAN

Applications are invited for the above post.

Duties will include the operation and maintenance of CCTV services and preparation of programme material.

Qualifications: HNC or equivalent, plus at least seven years' previous experience.

Salary scale: £1,881-£2,241 per annum.

Application forms and further particulars should be obtained from the Registrar, The New University of Ulster, Coleraine, Co. Londonderry, Northern Ireland (quoting Ref. No. 73/130/149/31/98) to whom completed applications, including the names and addresses of three referees, should be returned not later than 31st October, 1973.

FIBRE OPTICS

Flexible Light Pipe for conveying light to inaccessible positions. Fibroflex Type 1. Glass 1.4mm effective dia. PVC sheathed. 44p per metre. (VAT inc.), P. & P. 10p. Any quantity.

Polariser Sheet up to 1 sq. ft. max. size. 161p per sq. in. (VAT inc.), P. & P. up to 6 in. square 10p; over 6 in. square 30p

- ★ Cut down glare
- ★ See those nixie tubes
- ★ Cross them for light control
- ★ Make your own strain gauge for plastics and glass

Circuit Board Etching Kits. Full instructions. £1.37½ (VAT inc.), P. & P. 14p

Photographic CDS Light Cells—used (with part of original circuit free), 33p (VAT inc.), Post free.

All items are strictly C.W.O.

From: **ARVIN SERVICE COMPANY**
12 CAMBRIDGE ROAD
ST. ALBANS

EDUCATIONAL

A SUCCESSFUL CAREER IN RADIO

Get the success you deserve—take an ICS home study course. Pass C&G, M.P.T. exams **FIRST TIME!** Free books. Low cost. Personal tuition. Send **TODAY** for **FREE** Guide on Radio, TV, Electronics, Electrical Engineering.

Name

Address

ICS Dept. 730X
Stewarts Road,
London SW8 4UJ



TELEVISION TRAINING

(MONOCHROME AND COLOUR)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of 16 months' duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Next course commences January 2nd. Training courses in Marine Radiocommunication and Radar are also available. Write for prospectus to: London Electronics College, Dept. B/11, 20 Penywern Road, Earls Court, London SW5 9SU. Tel. 01-373 8721.

SERVICE SHEETS

SERVICE SHEETS • MANUALS • BOOKS

SERVICE SHEETS 40p plus S.A.E. ★ SERVICE SHEET CATALOGUE 25p
OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS
RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

NEW BOOKS & PUBLICATIONS

	PRICE
DICTIONARY OF RADIO AND TELEVISION by W.E. Pannett. 380 pp.	£1.80
TELEVISION ENGINEERS POCKET BOOK 6th Edition. by P.J. McGoldrick. 400 pp.	£2.50
WORLD RADIO TV HANDBOOK 1972. 26th Edition. 384 pp. Special reduced offer.	£1.10
GUIDE TO BROADCASTING STATIONS. 17th Edition. 176 pp.	£0.75
OUTLINE OF RADIO & TELEVISION. 405/625/Colour Edition. by J.R. Davies. 512 pp.	£2.50
UNDERSTANDING TELEVISION. 2nd Edition. by R.E.F. Street. 376 pp. 236 illus.	£1.80
PRACTICAL TELEVISION CIRCUITS. 2nd Edition. by G.White. 236 pp.	£3.25
VIDEO RECORDING: RECORD & REPLAY SYSTEMS. by G.White. 236 pp.	£0.85
TELEVISION SERVICING by G.N. Patchett. Vol. 1. Principles, Video, Sound Tuners.	£0.85
TELEVISION SERVICING by G.N. Patchett. Vol. 2. CRT, Sync-Sepe, Timebases, etc.	£0.60
TELEVISION SERVICING by G.N. Patchett. Vol. 3. Limiters, Apc, Flywheel-Sync etc.	£0.85
TELEVISION SERVICING by G.N. Patchett. Vol. 4. Practical Servicing, Fault-finding	£0.60
RADIO SERVICING by G.N. Patchett. Vol. 1. Basic Electro-Technology.	£1.00
RADIO SERVICING by G.N. Patchett. Vol. 2. Intermediate Radio Theory.	£0.85
RADIO SERVICING by G.N. Patchett. Vol. 3. Fault-Finding.	£2.20
PRACTICAL WIRELESS CIRCUITS. 18th Edition. by Staff of "Practical Wireless".	£1.50
RADIO CIRCUITS. 5th Edition. by W.E. Miller. 238 pp. Illustrated.	£1.50
PRACTICAL WIRELESS SERVICE MANUAL. 12th Edition. by H.W. Hellyer. 288 pp.	£1.50
WIRELESS SERVICING MANUAL. 10th Edition. by W.T. Cocking. 302 pp.	£3.00
FOUNDATIONS OF WIRELESS & ELECTRONICS by M.G. Scroggie. 552 pp.	£2.10
PHOTO-ELECTRONIC DEVICES by J.B. Dance. 182 pp. Illustrated.	£4.50
SEMICONDUCTOR PHOTOELECTRONIC DEVICES by Dr. Inz. A. Ambroziak. 344 pp.	£1.00
UNDERSTANDING THE SEMICONDUCTOR by C.N. Matthews. 128 pp.	£1.00
PRACTICAL INTEGRATED CIRCUITS by A.J. McEvoy & L. McNamara. 144 pp.	£3.00
SOLID-STATE DEVICES & APPLICATIONS by R. Lewis. 266 pp. 182 Illustrations.	£3.00
NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) Good prices paid.	

Send large S.A.E. for FREE booklists. Postage on above books is 5p in the £1.00 (UK only)...

BELL'S TELEVISION SERVICES

ALBERT PLACE, HARROGATE, YORKSHIRE. Telephone 0423-86844

DIGITAL CLOCK COMPONENTS

4/6 Digit Clock Chip £9.00; 6 Minitron Displays £6.00; Kit of Discrete Driver Transistors and Diodes £3.50; Minitron Sockets 25p each. 2N7447 drivers £1.20 each.

LOW COST LED LAMPS

Red 3mm dia. 20p each; Red 4.45mm dia. 23p each; Green 3mm dia. 55p each; Green 4.45mm dia. 55p each.

CALCULATOR DISPLAY

0-12 inches Character Height Flatpack £2.00 each.

SLIDER SWITCHES

1 pole 2 position—Miniature 14p each; 2 pole 2 position 14p each; 2 pole 3 position 21p each; 1 pole 4 position 23p each. U.K. Postage and packing 10p. Overseas 25p. VAT 10%

PERDIX COMPONENTS LTD.

Dept. PE73, 31 Green Lane, Chislehurst, Kent.

DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 69p per dozen; £4.12 per 100; £30.25 per 1,000; £275 per 10,000. VAT and post paid.

G.W.M. RADIO LTD.

40/42 Portland Road, Worthing, Sussex BN903 34897

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 15p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

5—N-Channel FETs 3819E—£1

Full specification devices complete with circuit details for building voltmeter, timer, ohmmeter, etc. Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LTD.

45 Station Road, Gerrards Cross, Bucks. MAIL ORDER ONLY

50 RESISTORS AT 0.56p EACH ALL COMPONENTS BRAND NEW—FULLY GUARANTEED

1/4W C/Film, Low Cost (22 ohms to 2.2M), your choice 28p/50; 1/4W Iskra C/Film (4.7 ohms to 4.7M) your choice 33p/50. All Resistor Values in Stock. Electrolytics: 10V (mf/price)—4.7/4p; 10/4p; 22/4.5p; 50/4.5p; 100/5p; 200/6p; 500/8p; 1,000/9p; 2,000/16p. 25V (mf/price)—2.2/4p; 4.7/4p; 10/4p; 22/4.5p; 50/4.5p; 100/5p; 200/7p; 500/11p; 1,000/16p. 50V (mf/price)—10/4p; 50/5p; 100/7p; 200/9p; 500/14p. 63V (mf/price)—2.2/5p; 4.7/5p; 10/6p; 22/6p. Transistors—2N3055 35p; FET 2N3819 25p; BFY51 13p; OC45/71 10p; Heatsinks—1 x TO3 9p, 1/2 x TO3 15p. All 16swg Black Anodised. Cases and Semiconductor PAKs see August and October Issues. Add 10% VAT to total order. Catalogue with full component range free.

ADFONIC (PE)

18 Yew Lane, Ashley, New Milton, Hants BH25 5BA. C.W.O. P. & P. at cost 9p min. Mail order Only.

PRECISION

POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.
0.47µF: ±5% 30p; ±2% 40p; ±1% 80p
1.0µF: ±5% 40p; ±2% 50p; ±1% 60p
2.2µF: ±5% 50p; ±2% 60p; ±1% 75p
4.7µF: ±5% 70p; ±2% 90p; ±1% 115p
6.8µF: ±5% 95p; ±2% 115p; ±1% 150p
10µF: ±5% 110p; ±2% 140p; ±1% 180p
15µF: ±5% 110p; ±2% 120p; ±1% 2270

TANTALUM BEAD CAPACITORS. Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 100µF 25V, 150µF 20V, 220µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 8p each; 6 for 45p; 14 for 95p. Special pack 6 off each value (78 capacitors) £4.50.

NEW!—TRANSISTORS. BC107, BC108, BC109. All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178 at 35p each or 3 for 95p.

POPULAR DIODES. IN914, 6p each; 8 for 45p; 18 for 90p. IN916, 8p each; 6 for 45p; 14 for 90p. IS44, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

NEW LOW PRICE—400 mW Zeners. Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5mA. All new and marked. Price 7p each; 6 for 39p; 14 for 84p. Special offer 6 off each voltage (66 zeners) £3.65.

RESISTORS. Carbon film 5%, 1/4W at 40°C, 1/4W at 70°C. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

440V A.C. CAPACITORS. 0.1µF, size 1 1/2in x 1/2in, 25p; 0.25µF, size 1 1/2in x 1/2in, 30p; 0.47 and 0.5µF, size 1 1/2in x 3/4in, 35p; 1.0µF, size 2in x 1/2in, 45p; 2.0µF, size 2in x 1in 75p.

SILICON PLASTIC RECTIFIERS 1.5A—Brand new wire-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

5p post and packing on all orders below £5.

Please add 10% VAT to all orders

MARCO TRADING

Dept. E11, The Maltings, Station Road Wem, Shropshire

BRAND NEW COMPONENTS by return.

Electrolytics 16V, 25V. 50V—0.47, 1, 2.2, 4.7, 10 mF, 4p; 22, 47, 43p (50V, 5p); 100, 51p (50V, 7p); 220, 6p (50V, 9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02, 2p; 0.04, 0.05, 3p; 0.068, 0.1, 31p. Polystyrene 63V E12 series 10-1,000pF, 2p; 1,200-10,000pF, 3p. Miniature highstab resistors, 5%, E12 series—Carbon Film 1/4W, 1Ω-10MΩ (10% over 1 MΩ). Metal Film 1/4W, 10Ω-2.2MΩ and 1W, 2.7Ω-10MΩ all 3p each. Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

TUNBRIDGE WELLS. Components from

Teleservice. S.A.E. or call in for list. Special offers, limited quantity; Matched AD161/2, 68p; 10 transistors similar 2N3702/3 unmarked, 35p; 12 1N914/6, 20p unmarked; air spaced twin gang receiver tuning capacitors, unused, 50p; thin grey connecting flex, 1p yd. Minimum order 40p, post free, but add 10% VAT. 108 Camden Road, Tunbridge Wells, Kent. Tel. 31803.

RADIO & TELEVISION AERIAL BOOSTERS

£2.95, five television valves 45p, 80p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7.50. Carr. £1.50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.

MINIATURE HIGHSTAB RESISTORS

5% 1/4W 22Ω to 2.2M E12 series 10 each value. Total 610, £3.

CERAMIC CAPACITORS 50V (pF) 1,500, 2,200, 3,300, 4,700, 6,800, 0.01, 0.1p each. BC108 9p. P. & P. 10p.

NEK ELECTRONICS (P3)

28 Carnegie Road, St. Albans, Herts. Mail order only.

Trampus electronic

Add 10% VAT (†) to all prices. All brand new, no rejects. Money Back Warranty.
TV DIGITAL INDICATOR: 0-9DP socket and filter £1.45.
LED TYPE †: 0-9DP DIL £2.25 each; 6x £2.10 each. 4 digit type £1.
LIGHT EMITTING DIODES. All with data and panel clip. TTL 209 4" dia. 20p. Red 4" dia. type 30p. Green 75p. INFRARED beam LED £1.10.
GAS detector £1.69. Ultrasonic transducer £2.
DALO PCB resist marking pen 60p. Copper board 12" x 6" SRBP 40p. FeC etch PAK 10p.
INTEGRATED CIRCUITS: with data if required.
IC LITE SWITCH: Photo amp/trigger 40mA/11-20V relay or TTL 87p. DIL relay £1.10.

IC digital clock

MOS/LSI type. 28 pin, 4 or 6 digit, 12/24hr. Chip with socket £12. PCB £1.69. KIT £21.49.
DVM Voltmeter £12. Data 30p. 3W AF amp £1.24.

741 DIL 8 pin 25p; 709 10p. DIL 25p; 748 25p; mono 710 8p. 555 TIMER/mono/astable osc. clock 80p.
REGULATORS: 1A 5 to 20V £1.49; 723 57p.
RECEIVER ZN414 £1.18. Mini Rx KIT £1.09.
1310 stereo decoder for tuner £2.69. KIT £3.

NEW LOW PRICES

GATES 7400/1/2/3/4/5/10/20/30/40/50, etc., 14p each. 7413 87p; 7441 75p; 7447 £1.09; 7470, 7472 25p; 7473, 7474 36p; 7475 80p; 7476 32p; 7490 50p; 7492 87p; 7480 69p; 7483 £1.10; 7486 37p; 7493 73p; 7494 83p; 7495 83p; 7496 80p; 74121 45p; 74141 99p; 74190/91/92/93/96 £2.39. DIL Plug/IC case 10mm high 16 pin 35p.

DIL SOCKETS: low or high profile 8/14/16 pin 18p.

SEMICONDUCTORS:

2N3055 40p; BC107 8p; BC108 8p; BC109 8p; BC147/8/9 10p; BC167/8/9 13p; BC177/8/9 15p; BC182/3/4 10p; BC212/3/4 11p; BCY70/72 15p; BD131/7 55p; BFY50/51/52 15p; B1843 UJT 24p; 2N706 11p; 2N2839 12p; 2N2906/7 3p; 2N2646 49p; 2N3053 17p; 2N3055 40p; 2N3614 55p; 2N3702/3/4/5/6/7/8/9/10/11 All 8p each.

FETS: 2N3819 27p; 2N3823 25p; SCR 400V: 1A 25p; 4A 55p. TRANSFORMER: 4A 6 and 12V £1.

CAPACITORS: Disc 22pF to 0.1µF 4p. 25V electrolytic 10, 50, 100µF 5p; 1,000µF 15p. PRE-SETS 5p each. RESISTORS ¼W 5% 11p each.

CARBON POTS 12p each. Dual 40p. Switch 12p. All Din Plugs 13p; sockets 9p; Vero RRP.

FLUORESCENT LIGHTS 12VOLT 27W

13" 8 watt fully built with diffuser.

TRIO and CODAR communications and Hi-Fi retailer. ELECTRONIC ORGANS from £67.

PW ELECTRONIC CAR IGNITION KIT £6.67.

VAT: YOU MUST ADD 10% (†) to all prices.

FREE CAT. S.A.E. Data sheets 8p each. P. & P. 8p. C.W.O. P.O. BOX 29, BRACKNELL, BERKS.

COMPUTER PANELS 6 assorted. No rubbish. £1 (25p). M.C. METERS 3 assorted 2in-3in. £1.15 (25p). 5 Fig. RESETTABLE COUNTER 18/22V. Works on 12V, £2.20 (15p). SILICON DIODES 650V 1A, 10 tagboard 35p (5p). New 800V 4A, 6-25p (5p). UNIT WITH 4 x BFT5L 4 Silicon Diodes, 4 Zeners, caps and resistors 45p (8p).

COPPER CLAD PAX PANELS 5 1/2in x 5 1/2in 6 for 45p c.p. 7 1/2in x 9in 25p c.p. 6 for £1.20 c.p. 8 1/2in x 9in 35p c.p. 6 for 30p c.p. 6 for £1.30 c.p. 10in x 10in 55p c.p. 6 for £1.40 c.p. WIRE KNIFE £1.00 (8p). Bank of 6 with 6-C407 driver trans. 50p (8p). POLYSTYRENE CAPACITORS 125V. 100, 150, 180, 220, 330, 390, 560, 680, 820, 1,200, 1,600, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 0-01, 0-012. 22p dozen (8p). Mixed with s/mica 100-50p c.p.

7LB ASSORTED COMPONENTS £1.60 c.p.

8LB ASSORTED COMPUTER PANELS £1.60 c.p.

Lists computer panels, etc. 10p stamps refunded on purchase.

J.W.B. RADIO

75 HAYFIELD RD., SALFORD 6, LANCS.

Postage in Brackets Mail Order Only

100 MIXED RESISTORS (our choice), many wire wound. 55p (10p). 100 mixed capacitors (our choice), silver MICA, polystyrene, ceramic, etc. 55p (10p). SPECIAL PACK includes 6 mixed pots, 10 mixed valve bases, 100 mixed resistors, 100 mixed capacitors. Good value at £2.50 (20p). Prices include V.A.T. postage in brackets. No used components. S.A.E. for list. G.R.C. 82 High Street, Windsor, Cheshire.

NORTHERN IRELAND READERS. BC107—10p; BC182L—10p; BC184L—10p; BC212L—10p; 2N3702—12p; 2N3055—65p; TIS43—40p; TIP20—58p. Sprague 5µF/150, 10µF/150, 25µF/100. All 10p each. Full range of radio spares, Eagle, etc. Send large S.A.E. for catalogue. P. & P. 5p per order. R.L.S. ELECTRONICS, 114 High Street, Holywood, Co. Down BT18 9HW.

R.T. SERVICES (MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Veroboard 6x5 0-1 Matrix, 2 for £1.

4x4 0-1 Matrix, 4 for £1. 12x3 0-15 Matrix, 75p each.

Mullard A.M. Module. I.F. Strip, LP1166, £1.10 inc. P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2 1/2 x 2 1/2 in with circuit, £1.37 inc. P.P.

Crouzet Gearing Motors, 30-60 r.p.m. New, £1.54 inc. P.P.

UHF TV Tuners. Transistorised, £1.65 inc. P.P.

VCRI38 CRT. New, boxed, £3.30 inc. P.P.

Brand New Panel VU Meters, 4 1/2 x 3 1/2 in calibrated, £3.30 inc. P.P.

Transformers: 7.5V + 7.5V 1/4, 66p inc. P.P. 18-0-18V, 200mA + 24V, 77p inc. P.P. 9-0-9V, 100mA, 69p inc. P.P. 12-0-12V, 100mA 69p P.P. 20V, 1A 88p inc. P.P.

Transformers: 52-0-52V, 1A + 22-0-22V, 200mA, £2.20 inc. P.P.

P.C. Board. S/S, 5 1/2 x 5 1/2 in, 10 for 70p inc. P.P.

Panel with 5-200 PIV 1A SCRs + 14 OA200 diodes plus components 70p inc. P.P.

2,500 mfd 100V capacitor 4 1/2 x 1 1/2". New, 85p inc. P.P.

Panel Meter 50µA. Brand new, 4 1/2 x 3 1/2". £3.30.

Panel with 2 SN7490, 2 SN7441 counting circuit with end connector, £2.20 inc. P.P.

Panel with 2 min. nixie tubes to slot in, £2 inc. P.P.

FACIAS AND CONTROL PANEL FRONTS • Made to Order

MANUFACTURED FROM HARDWEARING PLASTIC LAMINATE MATERIAL. AVAILABLE IN WIDE COLOUR CHOICE, INCLUDING WOODGRAIN. LEGEND PERMANENTLY MACHINE ENGRAVED. THE IDEAL AND ECONOMIC ANSWER FOR SINGLE, SHORT BATCH OR EXPERIMENTAL PANELS. SEND DIMENSIONED SKETCH FOR QUOTATION. WE ALSO MANUFACTURE ENGRAVED LABELS AND NAMEPLATES.

RAPOWE SIGN & PRODUCT CO.

32 Sheridan Road, Hereford Tel. 2415

TELERADIO ELECTRONICS ARE STOCKING THE MODULES FOR THE P.E. RONDO QUADRAPHONIC SYSTEM

Matrix Decoder £8.80

Pre-Amplifier £3.30

Stereo Amplifier £8.25

Controls & balance panel £9.35

Prices include VAT and Post !

Further information gladly supplied on request

TELERADIO

325-7 Fore Street, London N9 0PE

01-807 3719

COMPONENTS GALORE. Pack of 500 mixed components. Manufacturers' surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers, etc. Send £1 + 10p P. & P. C.W.O. to: CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

FOR BARGAIN LISTS worth seeing, plus FREE SAMPLES send S.A.E., 2 Richmond Terrace, Ulverston, Lancs.

COMPONENTS, HARDWARE, CARTRIDGES. GP91/350 90p. STYLI from 20p—V.A.T. included. 18-page lists, 3p stamp. R.F. SUPPLIES, Down Barton, Woodham Road, Woking, Surrey.

MISCELLANEOUS

BUILD THE

TREASURE TRACER MK III Metal Locator



- Varcap tuning
- Excellent sensitivity and stability
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- Completely new design. Send S.A.E. for leaflet!

Complete Kit Post 35p **£9.80**

Built, tested and guaranteed Post 35p **£13.75**

MINIKITS ELECTRONICS, 35g LANGLEY DRIVE, WANSTEAD LONDON E11 2LN (Mail order only)

CONSTRUCTION AIDS. Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

Build the Mullard C.C.T.V. Camera
 Kits are now available with comprehensive construction manual (also available separately at 76½p)
SEND 5" 7" S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
 15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

METER REPAIRS. Ammeters. Voltmeters, Multi-Range meters, etc., also Linear scale Transistorised Ohmmeters for sale. METER REPAIRS, 39 Chesholm Rd., London N16 0DS.

ALUMINIUM SHEET to individual sizes in standard packs, 3p stamp for details. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

CLEARING LABORATORY, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M.C. relays, components, etc. Lower Beeding 236.

GLASS FIBRE P.C. BOARD—large supplies available. 1/4 in single sided one ounce copper, 2p per sq ft (under 1ft); 75p per sq ft (over 1ft). 1/2 in double sided one ounce copper, 1p per sq ft (under 1ft); £1 per sq ft (over 1ft). Please add 10p per sq ft postage and packing. We can cut to your size at 1p per cut. SOLID STATE LIGHTING, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

A.L.S. PRESENTS OUR E.C. 100 Watt Hi-Fi Amplifier ready drilled P.C.B. with full instructions only £2 plus 10p post.
 We also supply: Service Sheets, Manuals, Books, etc.
 See our main advert in 'TELEVISION' or send S.A.E. for details.

10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA (B).

fibre optic suppliers

LOW COST LED—MLED 500, MV 54
MLED 500 is in TO92 case, for PC board mounting. MV 54 is T2 size, 2mm, miniature. Both emit visible red light. Current requirement 20mA, 150Ω resistors available for 5V d.c. (TTL) operation.

2NS777—SILICON PHOTO DARLINGTON AMPLIFIER
Economical, high sensitivity, TO92, LIGHT DETECTOR

	1	2	5	10	25
MLED500	22p	44p	£1.10	£2.20	£3.74
MV54	22p	44p	£1.10	£2.09	£3.52
150Ω					11p
2NS777	55p	£1.10	£2.53	£4.62	£9.90

ULTRASONIC TRANSDUCERS—TRANSMITTER RECEIVER PAIR
40kHz for burglar alarm, remote control, novelties. Great value at £3.85 per transmitter pair.

HNCP 37—NEUTRAL CIRCULAR POLARISER
Reduce glare on CRTs, meters, displays, panels. 50mm × 50mm (2in), 66p; 75mm × 75mm, £1.21; 150mm × 150mm, £4.40.

CROFON 1610—64 FILAMENT LIGHT CONDUIT
1.8mm active dia., 3.3mm o.d. Simply cut to length and conduct light where required. For displays, internal illumination, multiple point lighting. 1 metre, £1.32; 2m, £2.64; 5m, £5.50; 10m, £10.45.

FP40—PLASTIC OPTICAL MONO-FIBRE 1mm DIAMETER
Single strand unjacketed light guide, simple to use. 5 metres, £1.10; 10m, £1.98; 25m, £3.85; FP20 (0.5mm) and FP60 (1.5mm) also available.

MARE'S TAILS FOR DECORATIVE DISPLAYS
7,000 fibres, professionally finished, beautiful. Add lamp, stand, cover to make a Fibre Optic Lamp. Eye catching in boardroom, hall or foyer, £11.00 each.
All prices shown include P. & P., VAT, C.W.O. please. For full information on our complete range, send 9in × 6in S.A.E. to
FIBRE OPTIC SUPPLIERS (PE)
P.O. Box 702 London W10 6SL

DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ **POCKET-SIZED MAXI-VOLT** Big ½ inch Spark Generator (instant 15,000 volts!) Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz (85g). Send £1.35 for your Maxi-volt now!

★ **UNIQUE TRANSMITTER/RECEIVER KIT.** No licence, examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5.90 for yours now!

★ **PSYCHEDELIC MINI-STROBE KIT.** Take a pocket-sized lightning storm to Disco's and Parties. "BRAIN-FREEZE" EM with vari-speed stop-motion flashes. Includes super case, too. Send £2.20 now!

(All prices include VAT, packing & postage)

Send remittance to:

BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh
Ewell, Surrey (Mail order only)

Or for more details, send 15p for lists, plus free design project sheet

SWITCHES UNUSUAL

PRESSURE MAT—flexible, hard-wearing plastic mat containing 180 contacts. Contacts close when pressed, open when released. Rating 50V, 1A. Size 30in × 24in. £3.50.

MINI MAT—size 24in × 7in. £2. (Construction as above but more sensitive). Both items suitable for burglar alarm, counter, foot switch, games, seat belt indicator, car alarm, door opener. Uses limited by imagination.

POSTAGE 15p PER ITEM. C.W.O.

ELECTRONIC SWITCHING DEVICES
P.O. Box 10, Aspley, P.D.O. Nottingham
For further details send S.A.E.

NEW FROM ELBON

L.E.D.'s (Red Emitting) Ideally suited for panel indicators
Price only: 33p each or £2.50 for 10

Light SENSITIVE SWITCHES

Two types available giving wide operating voltages:

LITE-IC2 11V-20V working—£1 each—£8.50 for 10

LITE-IC3 20V-30V working—£1 each—£8.50 for 10

Applications include: Relay, Triac or Logic Drive, automatic light switching and door control, beam/break detection—burglar alarm, batch counting and code reading.

BARGAIN PACK!

2 LITE-IC2, 2 LITE-IC3 and 5 LED's all for £5.00

ALL PRICES INCLUDE VAT, PACKING AND CARRIAGE

Please send C.W.O. to:

LITE-IC, ELBON, SUMMERFIELD,
THE CRESCENT, WEST WITTERING, SUSSEX

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	½lb Reel
10-14	£1.27	72p
15-19	£1.27	72p
20-24	£1.30	75p
25-29	£1.38	83p
30-34	£1.43	89p
35-40	£1.54	91p

Please add 10% to all above prices to cover VAT
The above prices cover P. & P. in U.K. Supplied by
INDUSTRIAL SUPPLIES
102 Parrswood Rd., Withington, Manchester 20
Telephone No. 061-224 3553

LOW COST I.C. MOUNTING. I.C. socket pins in lengths of 100 pins for 60p. (P. & P. 5p). S.A.E. Details and sample. GASKELL, Oak Lodge, Tansley, Derbyshire.

HARDWARE—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

Do you suffer from tired eyes due to bright lights, or need a softer light for watching television in comfort? Well, we have the answer, a

GREENBANK DIMMER SWITCH

Just look at these features:

- ★ Velvet dim to full brightness at the touch of a finger
- ★ Positive off position
- ★ Built-in radio interference suppression
- ★ Controls up to 300 watts
- ★ Easy replacement for a standard light switch

All this for only

£3.75

complete

(500 watt model also available)

This price includes V.A.T., also P. & P. Why not write or phone now? Please send C.W.O. to:

GREENBANK ELECTRONICS

94 New Chester Road
New Ferry, Bebington
Cheshire L62 5AG
Tel. 051-645 3391

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

LADDERS

LADDERS 24½ft £12.39, carr. £1.10. Leaflet. HOME SALES LADDER CENTRE (PEE2), Haldane (North), Halesfield (1) Telford, Shropshire. Tel. 0952 586644.

ANNUAL WAREHOUSE CLEARANCE SALE

SAT. OCT. 6—NOV. 3
TUES.—SAT. 10 a.m.—5 p.m.

- * THOUSANDS OF BARGAINS *
- * TEST EQUIPMENT *
- * OSCILLOSCOPES *
- * SIGNAL GENERATORS *
- * COUNTERS *
- * CABINETS *
- * BRIDGES *
- * METERS *
- * TRANSMITTERS *
- * RECEIVERS *
- * POWER SUPPLIES *
- * LABORATORY EQUIPMENT *
- * GALVANOMETERS *
- * AUDIO EQUIPMENT *
- * VIDEO EQUIPMENT *
- * BATTERY CHARGERS *
- * MOTORS *
- * ETC. * ETC. *

20 TONS OF ELECTRONIC COMPONENTS

- * RESISTORS
- * CAPACITORS
- * TRANSFORMERS
- * POTENTIOMETERS
- * RELAYS
- * SWITCHES
- * METERS
- * COMPONENT PARTS

- * SEMICONDUCTORS
- * CABLE
- * ETC. * ETC. * ETC.
- * VALVES

REGRET NO LISTS AVAILABLE
PERSONAL CALLERS ONLY. CASH AND CARRY ONLY

ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

- Pack No.
- 1 500 Carbon resistors, ½, 1, 1.2W.
 - 2 100 Electrolytic Condensers.
 - 3 250 Ceramic, Polystyrene, Silver Mica, etc. Condensers.
 - 4 250 Polyester, Polycarbonate, Paper, etc. Condensers.
 - 5 25 Potentiometers, assorted.
 - 6 250 High-stab. 1%, 2%, 5% resistors.
 - 7 50 Assorted Tagstrips.
 - 8 1lb wt. Assorted Nuts, bolts, washers, spacers, etc.
 - 9 25 Assorted switches, rotary, lever, micro, toggle, etc.
 - 10 50 Preset Potentiometers.

ALL COMPONENTS NEW AND UNUSED
£1 + 25p p.p. per pack, £5 for 5 packs p/free

C.T. ELECTRONICS

Mail Order, Retail Shop, Components—
267 Acton Lane, LONDON W4 5DG 01-994 6275
Warehouse, Test Equipment, Surplus Goods—
20-24 Beaumont Road, LONDON, W.4
Audio Accessory Shop, Components—
17 Turnham Green Terrace, LONDON, W.4

Mullard Components

CARBON FILM RESISTORS

High stability, very low noise. E12 series 4R7-1M. Prices are per ohmic value. Ignore fractions.

0.33W 5%	1+	100+	1,000+
	0.7p	0.7p	0.6p

ELECTROLYTIC CAPACITORS

Miniature series. Tolerance -10% +50%.

All 4p each						
4V 6.3V	10V 16V	25V 40V	63V 63V	63V 63V		
47 33	22 15	10 6.8	1.0 4.7	2.2		
100 68	47 33	22 15	1.5 6.8	47		
220 150	100 68	47 33	2.2 10			
330 470	220 150	100 47	3.3 15			

POLYESTER CAPACITORS

C280 series. 250V PC mounting: 0.01, 0.015, 0.022, 2p; 0.033, 0.047, 0.068, 0.1, 3p; 0.15, 0.22, 4p; 0.33, 5p; 0.47, 6p; 0.68, 8p; 1.0, 10p; 1.5, 14p; 2.2, 16p.

All prices include VAT. Please add 8p postage and packing on orders below £2. Fast service. Cash with order only. Send 5p stamp for our comprehensive catalogue.

C. N. STEVENSON
304 Avery Hill Road
London SE9 2JN

SOLID STATE LAMPS

Try out the latest light emitting diodes

Experimenters' pack of four Motorola light emitting diodes (LEDs) complete with circuits, data and full instructions.

£1.10 per pack plus 5p postage c.w.o.


Trium Company Ltd., 12 Mount Ephraim, Tunbridge Wells, Kent

Please mention
PRACTICAL ELECTRONICS

when replying to

ADVERTISEMENTS

verobox

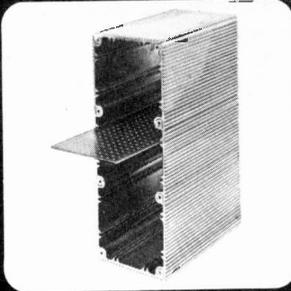

ALUMINIUM ENCLOSURES

- 80 standard sizes available from stock.
- Made from precision extrusions with integral board guide slots.
- Finned sides improve appearance and radiate heat.
- Parallel sides for ease of component mounting.



VERO ELECTRONICS LTD.

Eastleigh, Hants. SO5 3ZR
Tel: Chandler's Ford 2952 Telex: 47551
Subsidiaries and Agents
throughout the World.

OSMABET LTD.

We make transformers amongst other things.

AUTO-TRANSFORMERS, 110/200/220/240V.
500W. £9-80; 750W. £12-75; 1000W. £15-75; 2000W. £28-50; 3000W. £39-00; 4000W. £60-00, etc.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6.3V 6A CT. £2-10; 12V 1.5A. £1-85; 3A £2-15; 6A CT. £2-80; 18V 1.5A CT. £2-15; 24V 1.5A CT. £2-15; 3A CT. £2-85; 5A. £4-80; 8A. £6-75; 12A £9-40; 40V 3A CT. £2-75; 50V 6A CT. £11-25; 25V 2A + 25V 2A. £4-15.

LT TRANSFORMERS TAPPED SEC. Prim. 200/240V
0-10-12-14-16-18V 2A. £2-25; 4A. £2-40;
0-12-15-20-24-30V 2A. £3-00; 4A. £4-05;
0-5-20-30-40-60V 1A. £3-00; 2A. £4-20;
0-40-50-60-80-90-100-110V 1A. £4-20.

MIDGET RECTIFIER TRANSFORMERS
For FW rect. 1:200/240V a.c. 9-0-9V 0-3A. 12-0-12V 0-25A or 20-0-20V 0-15A. £1-45 each; 9-0-9V 1A, £1-20; 12-0-12V 1A or 20-0-20V 0.75A. £1-85 each.

MAINS TRANSFORMERS FOR POWER AMPLIFIERS
Prim. 200/240V a.c. TX6 sec. 425-0-425 500 Ma. 6.3V CT 6A. 6.3V CT 6A. 0.5-6.3V 3A. £15-00; TX1 425-0-425V 250 Ma. 6.3V CT 4A. 6.3V CT 4A. 0.5-6.3V 3A. £9-40; MT2A 250V 100Ma. 6.3V 2A. £1-50.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec. tapped 3-8-15ohms. A-A 6.6kΩ 30W. £4-80; A-A 3kΩ 50W. £8-00; 100W (EL34 KT88, etc.). £13-50; tapped Multi O/P 10W. £2-25.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30 to 3000W 30p.

LOUDSPEAKERS FOR POWER AMPLIFIERS
BAKER 25W. £6-40; 35W. £7-80; HI-FI, Major Module 20W w/tweeter Xover. £9-20; Baker speaker lists: FANE 30W. £10-50; 60W. £13-50; EM1 13 x 8in 3 or 15Ω. £1-60; speakers for HI-FI 5in 8Ω. £1-15; 8 x 5in 3, 8 or 15Ω £1-75.

LOUDSPEAKERS
2 1/2in, 8, 15 or 7.5Ω. 2 1/2in 25Ω. 3in, 3, 8 or 25Ω. 3 1/2in 8, 15 or 80Ω. 80p; 5in 3, 8, 15 or 25Ω. 5 x 3in 3, 8 or 25Ω. £1-05; 6 1/2in 3Ω. 6 x 4in 25Ω. 7 x 4in 3, 15 or 25Ω. 8 x 2 1/2in 3Ω. £1-25; 8 x 3in 15 or 25Ω. £1-50; 10 x 6in 3Ω. £1-50.

SPEAKER MATCHING TRANSFORMERS
12W 3 to 8 or 15Ω up or down. £1-15.

BULK TAPE ERASERS
Instant erasure, tape spools, cassettes, demagnetises tape heads a.c. 200/240V a.c. £2-50 plus P. & P.

CONDENSERS
Paper, tubular W/E 2-2mf 250V Xovers, etc. 15p. 25 p/100; Black 4mf 500V. 75p; 8mf 750V. 75p; Electrolytic. 9000mf 350V. 50p; 0-01/2KV. 12p.

V.A.T. extra on all orders
Carriage extra on all orders.

S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YQ
Tel. 01-958 9314

PARTIDGE MAINS ISOLATION TRANSFORMER. Pri: 105-250V, 5V steps, Sec: 240V, 13 amps. £15, carr. pack. £1-50.

PARNKO MAINS TRANSFORMER isolated windings. Pri: 200-250V. Sec: 90-120V at 4.5 amp. £4, carr. pack. 75p.

GARDNER'S POTTED TRANSFORMER, 0-250V. Pri: 200-250V. Sec. Input: 18V 500mA, 50V 150mA, 6V 250mA output. Size: 3in x 2 1/2in x 2 1/2in, £1, p.p. 28p. Ex equip. tested.

RIPLEY MAINS TRANSFORMER. Pri: 110V-240V, Sec: 12.5V: 0.12-5V 750mA/V: 0.7V: 1VIA, £1, p.p. 25p.

MAINS TRANSFORMER. Pri: 100-250V. Sec: 22:0-22 200mA. 22:0-22 100mA 0.24V 20mA/A, 50p, p.p. 25p.

MAINS TRANSFORMER. Pri: 230V. Sec: 14V, 120 amps. £15, p.p. £1-50.

MAINS TRANSFORMER. Pri: 100-240V a.c. 36.5-0-36.5V, 27mA, 0-21-5, 260 mA/A, 80p, p.p. 25p.

TRANSISTOR OUTPUT TRANSFORMER, Ratio 6:1, 120mH. Centre tap 2 watts. output, 20p, p.p. 8p.

SMOOTHING CHOKE, 11MH, 1 1/2in x 1 1/2in x 1 1/2in, 20p, p.p. 8p.

FINNED ALUMINIUM HEATSINK, 4 1/2in x 6in x 1in, 2 x 2N3055, £1, p.p. 13p.

GOODMANS 8in SPEAKERS 3Ω £1-50, p.p. 28p.

FINNED ALUMINIUM HEATSINK, 9in x 8in x 1 1/2in. in C. 4 x 2N3055, £2, p.p. 29p.

GARRARD MAG. TAPE DECKS: 1 1/2 p.p.s., 50V, solenoid operated brakes, etc. Mains voltage motors £7-50 each, p.p. 60p.

NOTEK 3 speed tape deck (1 1/2in x 3 1/2in x 7 1/2in) to reel 7in mains operated, £7-80, p.p. 63p.

10 REED SWITCHES operated by push buttons and magnets, 50p, p.p. 25p.

COMPONENT PANEL, 6 scr's (300V, 1.6A) 6 cond., 12 resistors, 6 diodes, 45p, p.p. 8p.

COMPONENT PANEL, 6 scr's (200V 4 amps), 6 condensers, 12 resistors, 30p, p.p. 8p.

COMPONENT PANEL (9 ICs FJH131) (1-CA300), 1 crystal 7-68kHz + various other components, £1, p.p. 8p.

COMPONENT PANEL, 2 x 500mF 50V, 3 x 100mF 25V, cap. 1 x 2N2612, 2 x 2N404, 3 diodes plus various other components, 10p, p.p. 9p.

COMPONENT PANEL, 24 OAB1 diodes, 10p, p.p. 6p.

FEEDER ROOT ELECTRICAL IMPULSE COUNTER NON-RESETABLE, A.C. 200-250V, £1-10, p.p. 13p.

GEC MAINS CIRCUIT BREAKERS, 2 amp or 5 amp, £1 each, p.p. 14p.

LEVER ACTION P.O. 1000 TYPE SWITCHES Lock 4-pole changeover, 15p, p.p. 4p. Ex equip. Lock 2-pole changeover, 10p, p.p. 4p. Ex equip.

MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,500µF 64V, 7,100µF 40V, 50p each, 20,000 30V, 25,000 25V, 35,000 15V, 30p each, p.p. 21p.

MULLARD FULLWAVE RECTIFIERS 6-48V, 15 amp, 75p, p.p. 10p.

BELLING LEE 1.5 amp in-line rubber covered interference suppressor, 25p, p.p. 8p.

RUBBER 3 PIN 6 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.

SOLENOIDS 12 VOLT PULL ACTION 2in x 1in x 3in, 40p, p.p. 8p.

SOLENOIDS 12-24V d.c. pull action 1 1/2in x 1 1/2in x 4in, 40p, p.p. 5p.

SOLENOIDS 240V a.c. pull action 2 1/2in x 1 1/2in x 4in, 50p, p.p. 9p.

SANGAMO WESTON TIME LAPPED METER Mains operated. 1 1/2in x 1 1/2in x 2in, £1-50 p.p. 7p.

ARROW RELAY, 240V a.c. coil, double pole change over, 1 make contact 10A, 240V a.c., 25p, p.p. 9p.

OMRON MKS MIDGET POWER RELAY, 12V d.c. Double pole changeover. New, 70p, p.p. 5p.

STC VARLEY, miniature relays 700Ω, 17.5-37V, persep cover, 4 pole changeover, 40p, p.p. 5p.

POTTER BRUMFIELD 12V d.c., 3 pole changeover with base, contacts rated 7A d.c., £1, p.p. 10p.

L.T. LOW PROFILE RELAYS, 4 pole c/overs. 500Ω 12-18V, 75p, p.p. 8p.

MAINS RELAYS, 200-250V a.c. 2 makes. Heavy duty contacts, 50p, p.p. 7p.

TELESCOPIC ARRAYS Chromed 7in closed, 28in extended, 6 section ball jointed base, 25p, p.p. 5p new.

PRINTED CIRCUIT BOARD/19 ACY 19's 10 OA200 Diodes: 1 reed relay: 1 AZ 229 zenner ass. capacitor/ resistors. Power supply 25V, 250 mA d.c. Output 240V a.c., £1, p.p. 25p. Ex equip.

WIRING CABLE Size-1-020. Various colours. 350yds, 60p, p.p. 28p.

TAPE POSITION INDICATOR Re-settable 3 digits, 30p, p.p. 5p.

All orders add 10% V.A.T.

FIELD ELECTRIC LIMITED
3 Shenley Road
Borehamwood, Herts.
Tel. 01-953 6009

BRAND NEW

SEMICONDUCTORS AND COMPONENTS

GUARANTEED

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

TRANSISTORS

40316 0-80
40318 0-80
40360 0-48
40361 0-48
40362 0-45
40363 0-61
40369 0-46
40394 0-58
40395 0-65
40406 0-44
40407 0-58
40408 0-50
40409 0-52
40410 0-53
40411 2-25
40414 3-55
40467A 0-69
40468A 0-44
40600 0-89
40601 0-67
40602 0-46
40603 0-58
40604 0-56
40636 1-10
40673 0-70
40674 0-58
40675 0-18
40676 0-18
40677 0-18
40800 0-18

KELLNER CONSTRUCTION KITS

WE ARE THE SOLE DISTRIBUTORS IN U.K.

- ES3 3 watt Mono Transistor Amplifier Kit £4.00
- EB15 15 watt Hi-Fi Transistor Amplifier Kit (two for stereo) with Tone Control and Pre-Amp £11.94
- ES30 30 watt Mono Hi-Fi Power Amplifier £8.32
- EN50 50 watt Mono Hi-Fi Power Amplifier £9.53
- EV3 Distortion Compensated Pre-Amplifier £3.00
- AV7 Aerial Amplifier. LW, SW, MW, VHF, T/V Channels 2-12 £1.83
- UHS70 FM Transmitter Kit. 65MHz-145MHz. A GPO Licence is required £2.52
- MUE7 Short Wave and VHF Receiver Kit. Companion to UHS70 25mHz-150mHz £2.93
- EW18 Electronic Dice Kit £5.91
- EW20 Electronic Dice with Sensor Button £6.64
- ST800 Strobe Light Kit, 120W/8 £7.11
- LO1000 Psychedelic Light Control, single channel £7.00
- LO350 Psychedelic Light Control, three channel £13.50
- NT15 Power Supply—4 to 30V, 1.5W £6.75
- NT85 Professional Stabilized Power Supply, 5 to 70V, 2A £11.34
- D800 800W Light Dimmer Speed Control £2.70
- WT7 Aircraft Communications Tuner 110-130MHz. Built and aligned £14.00
- WT9 Transmitter VFO for 2 meters [144mHz-146mHz]. Built and aligned £14.00

TTL LOGIC I.C.'s

SN7400	28p	SN7430	28p	SN7472	40p
SN7401	38p	SN7432	48p	SN7473	47p
SN7402	28p	SN7437	52p	SN7474	48p
SN7407	56p	SN7440	20p	SN7475	96p
SN7410	28p	SN7441	70p	SN7476	64p
SN7411	22p	SN7442	71p	SN7481	£1.25
SN7413	20p	SN7443	79p	SN7483	£1.00
SN7420	20p	SN7444	£1.04	SN7484	95p
SN7421	22p	SN7445	£1.85	SN7485	£1.90
SN7422	48p	SN7446	£1.25	SN7486	£1.00
SN7423	52p	SN7447	£1.30	SN7491	£1.60
SN7425	48p	SN7450	20p	SN7493	£1.00
SN7426	48p	SN7451	20p	SN7494	85p
SN7427	48p	SN7452	20p	SN7495	80p
SN7428	50p	SN7454	25p	SN7496	£1.00

We also stock the unusual numbers as follows:

SN74100	2-50	SN74153	1-63	SN74178	1-50
SN74107	0-48	SN74154	2-00	SN74180	1-55
SN74118	1-00	SN74155	1-65	SN74181	7-00
SN74119	1-92	SN74157	1-80	SN74190	1-96
SN74121	0-60	SN74160	1-60	SN74191	1-96
SN74122	1-35	SN74161	2-80	SN74192	1-90
SN74123	1-35	SN74164	2-80	SN74193	1-90
SN74141	0-90	SN74165	4-00	SN74194	1-60
SN74145	1-50	SN74167	6-25	SN74196	4-60
SN74150	3-35	SN74174	2-00	SN74198	4-60
SN74151	1-10	SN74175	1-85	SN74199	4-00

BRIDGE RECTIFIERS

PIV	50	100	200	400	600
1A	24p	28p	35p	35p	40p
2A	32p	37p	41p	46p	52p
4A	60p	70p	75p	85p	95p
6A	82p	76p	80p	£1.10	£1.25

GLASGOW BRANCH
65 BATH STREET, GLASGOW, SCOTLAND
Tel. 041-332 4133

NE555 TIMER I.C. 90p.
NE560 PHASE LOCKED LOOP, £4.48.
SCORPIO IGNITION KIT for improved performance £10 + 50p P. & P.

DIODES AND RECTIFIERS

IN5171 (1-5A 50pV)	8d	IN5402 (3A 200pV)	20p
IN5172 (1-5A 100pV)	9p	IN5404 (3A 400pV)	22p
IN5417 (1-5A 200pV)	10p	CL7005 (3A 600pV)	25p
IN5173 (1-5A 400pV)	11p	CL7006 (3A 800pV)	27p
IN5176 (1-5A 600pV)	12p	CL7007 (3A 1000pV)	27p
IN5177 (1-5A 800pV)	13p	CL1002 (10A 100pV)	85p
PL4007 (1-5A 1000pV)	20p	CL1003 (10A 200pV)	40p
IN5400 (3A 50pV)	15p	CL1004 (10A 400pV)	47p
IN5401 (3A 100pV)	17p	CL1005 (10A 600pV)	56p

ANODE AND CATHODE STUD

IN1183 (35A 50pV)	92p	IN1188 (35A 400pV)	£2.66
IN1184 (35A 100pV)	£1.12	IN1190 (35A 600pV)	£3.15
IN1186 (35A 200pV)	£1.57		

CATHODE STUD ONLY

IN3766 (35A 800pV)	£3.65	IN3768 (35A 1000pV)	£4.20
IN344	10p	BA141	17p
IN914	7p	BA142	17p
IN916	7p	BA144	12p
AA119	7p	BA145	17p
AA129	15p	BA154	12p
BA100	15p	BY100	15p
BA102	25p	BY126	15p
BA110	25p	BY127	17p
BA115	7p	BY140	21
		BY141	21
		BY237	12p
		BY210	8p
		BY211	3p
		BY212	8p
		OA9	10p
		OA10	10p
		OA17	20p
		OA20	7p
		OA202	10p
		OA73	10p
		OA210	27p

OPTOELECTRONICS

MNITRON 3015F 7-SEGMENT INDICATOR (16 PIN DIL) £2.30
DRIVER SN7447 £2.00
SOCKETS £2.00

TIL 209 LIGHT EMITTING DIODE. Made by TEXAS INST. (Red). 35p

MOTOROLA MC SERIES, RCA CA 3000 SERIES AND COSMOS, PLESSEY SL SERIES. TRY US FIRST FOR LINEAR AND DIGITAL INTEGRATED CIRCUITS.

ENCAPSULATED FULL-WAVE RECTIFIER. 1-8A 100piv 25p ea.

POTENTIOMETERS

Carbon:
Log. or Lin., less switch, 17p.
Log. or Lin., with switch, 28p.
Wire-wound Pots (3W), 38p.
Twin (anged Stereo Pots, Log. or Lin., 47p.

PRESETS (CARBON)
0-1 Watt 6p VERTICAL
0-2 Watt 6p OR
0-3 Watt 7p HORIZONTAL

SLIDE POTENTIOMETERS
5mm TRACK
SINGLE GANGED. LOG or LIN
1k to 1M. 30p each.
TWIN GANGED. LOG or LIN
1k to 500k. 60p each.
KNOBS. 5p each.

Small value
SUB-MIN. ELECTROLYTICS
wide range of values only 6p each

ALL PRICES EXCLUSIVE OF 10% VAT

Post and Packing 18p per order. Europe 25p. Commonwealth (Air) 65p (MIN.). Matching charge (audio transistors only) 16p extra per pair. Prices subject to stock availability.

Tel. 01-452 0161/2/3
Telex 21492
A. MARSHALL & SON
42 CRICKLEWOOD BROADWAY, LONDON, N.W.2
VISITORS WELCOME
HRS. 9-5.30 MON.-FRI.
9-5 SAT.

BUILD A CHORDING PROFESSIONAL SYNTHESISER



The Synthesiser shown above is the Dewtron "Apollo" A.1, which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts.

VCO-2 STABLE, PRECISION V/C OSCILLATOR gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. £24 each or £27 each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. £17. OFT-1 chording module £9. Modules (except VCO-1) guaranteed two years.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading groups. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I. Approved by a Musical Association. Send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES CASH SAVINGS

by buying modules and parts in bulk!
All modules are available separately:
Ring Modulator RM2, £8. Voltage-controlled Oscillator VCO1, £10.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £13. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £10, etc., etc. ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £5.50. REVERB Module and spring unit £15. V.A.T. 10% extra. V.A.T. paid orders over £75.

TRANSISTORS

AC126	14p	AF180	45p	BC158	14p	BF180	32p	BFY51	21p
AC127	16p	AF181	43p	BC159	14p	BF181	32p	2N3053	23p
AC128	14p	AF239	44p	BC177	20p	BF184	35p	2N3054	57p
AC141K	24p	BC107	12p	BC183L	14p	BF185	35p	2N3055	60p
AC142K	24p	BC108	10p	BC184L	12p	BF186	43p	TIP29	66p
AC176	20p	BC109	12p	BC187	18p	BF194	15p	TIP30	75p
AC187	18p	BC112	12p	BC294	16p	BF195	15p	TI591	48p
AC187K	24p	BC114	30p	BC440	50p	BF196	15p		
AC188K	24p	BC115	20p	BC460	68p	BF197	15p		
AD142	45p	BC116	20p	BD124	80p	BF200	32p		
AD149	45p	BC117	15p	BD131	60p	BF258	40p		
AD161	34p	BC125	14p	BD132	60p	BF259	40p		
AD162	34p	BC142	25p	BD139	63p	BF337	23p		
AF115	21p	BC113	25p	BDX32	£2.00	BFT42	44p		
AF116	21p	BC147	13p	BF115	25p	BFT43	44p	OA91	7p
AF117	21p	BC148	13p	BF121	35p	BFX84	40p	OA202	9p
AF118	49p	BC149	13p	BF15B	19p	BFX88	30p	IN4148	4p
AF139	40p	BC154	20p	BF167	20p	BFX89	67p	BY127	11p
AF178	45p	BC157	14p	BF179	39p	BFY50	21p	IN4006	8p

DIODES AND AND REC- TIFIERS

RESISTORS METAL FILM

5% TOL.
1W, 1/2W, 1/4W, E12 values to 2.7M all 1p each.
1W to 10M E12 values 3p each;
2W to 10M E12 values 4p each;
5W wire wound, 10W wire wound 8p and 9p each. See Cat. for values.

POTENTIOMETERS-CARBON TRACK

5K, 10K, 25K, 50K, 100K, 250K, 500K, 1M.
Log or lin less switch 11p
Log or lin with switch 23p
Dual log less switch 250K, 500K, 1M, 2M, only 39p
Dual lin less switch 5K, 10K, 25K, 50K, 100K, only 39p
Dual log with switch 10K, 100K, 250K, 500K, 1M only 55p

JACK PLUGS AND SOCKETS.

Standard insulated 11p; Stereo screened 18p; Stereo insulated 22p; Stereo screened 30p; 3.5mm insulated 8p; 3.5mm screened 12p; Standard socket switched 17p; Stereo socket switched 21p; 3.5mm socket switched 6p; Standard line socket 15p; Stereo line socket 22p; 3.5mm line socket 10p.

PHONO-D.I.N. PLUGS AND SOCKETS

Phono plug insulated 7p; Phono plug screened 11p; Phono line socket screened 12p; Metal coax plug 8p; 2, 3, 5 pin 180°, 240°, D.I.N. plugs 12p; 4, 6, 7 pin plugs 15p; 2, 3, 5 pin 180° line sockets 13p; 2, 3, 5 pin 180° chassis sockets 7p.

CABLES AND SCREENED WIRES

Min. mike cable single 7p/metre; Min. twin mike cable 11p/metre; Pick up wire single 7p/metre; Pick up wire twin 11p/metre; Stereo screened twin 10p/metre; 4 core individually screened 14p/metre; Speaker wire twin coded 6p/metre.

E. A. HALL (ELECTRONICS)

The Manse, Little Brington, Northampton NN7 4HX

Mail Order Only. C.W.O. Postage and packing 10p per order. Detailed Catalogue 6p. Please add V.A.T. on total order incl. postage and packing. Many other items in our catalogue.

If you have difficulty in obtaining

PRACTICAL ELECTRONICS

Please place a regular order with your newsagent or send 1 year's subscription (£2.65) to Subscription Department, Practical Electronics, Tower House, Southampton Street, London WC2E 8QX

BAKER 12" MAJOR £9-90

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

MAJOR MODULE KIT £12.50

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 13in.

NOTE—When ordering state 3 or 8 or 15 ohms.

BAKER LOUSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W	£8.80	Superb 12 in. 20W	£16.50	ALL PRICES INCLUDE V.A.T.
Major 12 in. 20W	£9.90	Group 25 12 in. 25W	£8.80	
Deluxe 12 in. 15W	£11.00	Group 35 12 in. 35W	£9.90	

BAKER LOUSPEAKER CO., BENSHAM MANOR PASSAGE

THORNTON HEATH, SURREY Tel. 01-684 1665

LOUSPEAKERS CATALOGUE AND ENCLOSURE PLAN 5p

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course". - Student D.L.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects". - Student J.A.O., Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". - Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to **B.I.E.T. Dept. BPE10, Aldermaston Court, Reading RG7 4PF.**

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

CUT OUT THIS COUPON

Tick or state subject of interest. Post to address below.

- | | | |
|--|--|---|
| MECHANICAL
A.M.S.E. (Mech.)
Boiler Inspect.
& Operation
C & G Eng. Crafts
C & G Fabricat.
Works
Diesel Eng.
Eng. Inspection
Eng. Metallurgy
Inst. Eng. & Tech
Inst. Motor Ind.
Mainten. Eng.
Mechanical Eng.
Sheet Metal Work
Welding | <input type="checkbox"/> Man. Prod.—cont.
<input type="checkbox"/> Quality Control
<input type="checkbox"/> Salesmanship
<input type="checkbox"/> Storekeeping
<input type="checkbox"/> Work Study
<input type="checkbox"/> Works
<input type="checkbox"/> Management
DRAUGHTSMANSHIP
A.M.I.E.D.
Design of Elec.
Machines
Die & Press Tool
Design
Electrical
<input type="checkbox"/> Draughtsman-
ship
<input type="checkbox"/> Gen. Draughts-
manship
<input type="checkbox"/> Jig & Tool Des.
<input type="checkbox"/> Tech. Drawing | <input type="checkbox"/> Constructional-cont.
<input type="checkbox"/> Building
<input type="checkbox"/> Building Drawing
<input type="checkbox"/> Build. Foreman
<input type="checkbox"/> Carpentry & Join.
<input type="checkbox"/> Civil & Municipal
<input type="checkbox"/> Engineering
<input type="checkbox"/> Constructional
<input type="checkbox"/> Engineering
<input type="checkbox"/> Construction
<input type="checkbox"/> Surveyors
<input type="checkbox"/> Institute
<input type="checkbox"/> Clerk of Works
<input type="checkbox"/> Council Eng.
<input type="checkbox"/> Geology
<input type="checkbox"/> Health Eng.
<input type="checkbox"/> Hydraulics
<input type="checkbox"/> Inst. of Builders
<input type="checkbox"/> Inst. Works &
<input type="checkbox"/> Highway Sup.
<input type="checkbox"/> Painting & Dec.
<input type="checkbox"/> Public Hygiene
<input type="checkbox"/> Road Engineer.
<input type="checkbox"/> Structural Eng.
<input type="checkbox"/> Surveying |
| ELECTRICAL & ELECTRONIC
A.M.S.E. (Elec)
C & G Elec. Eng.
C & G Elec. Inst.
C & G Elec. Tech.
Computer Elect.
Elec. Maths
Elec. Science
Electronic Eng.
Electrical Eng.
Install. & Wiring
Meters
& Measuring
Instruments | <input type="checkbox"/> RADIO & TELE-COMMUNICATIONS
Colour TV
C & G Radio (TV/
Electronics
C & G Telecomm
Tech
<input type="checkbox"/> Prac. Rad Elec.
(with kit)
<input type="checkbox"/> Radio Amateurs
Exam.
<input type="checkbox"/> Radio Servicing
& Repairs
<input type="checkbox"/> Radio & TV Eng.
<input type="checkbox"/> Trans. Course
<input type="checkbox"/> TV Main. & Serv. | <input type="checkbox"/> GENERAL
<input type="checkbox"/> Agricultural Eng.
<input type="checkbox"/> Council of Eng.
<input type="checkbox"/> Inst.
<input type="checkbox"/> Farm Science
<input type="checkbox"/> General Educat.
<input type="checkbox"/> Gen. Plastics
<input type="checkbox"/> Pract. Maths
<input type="checkbox"/> Pract. Slide Rule
<input type="checkbox"/> Pure & Applied
<input type="checkbox"/> Maths
<input type="checkbox"/> Refrigeration
<input type="checkbox"/> Rubber Tech.
<input type="checkbox"/> Sales Engineers
<input type="checkbox"/> Tech. Report
<input type="checkbox"/> Writing
<input type="checkbox"/> Timber Trade
<input type="checkbox"/> University Ent. |
| MANAGEMENT & PRODUCTION
Auto. Control
Computer Prog.
Electronic Data
Processing
<input type="checkbox"/> Estimating
<input type="checkbox"/> Foremanship
<input type="checkbox"/> In-t. Cost & Man
<input type="checkbox"/> Accountants
<input type="checkbox"/> Inst. Marketing
<input type="checkbox"/> Management
<input type="checkbox"/> Metallization
<input type="checkbox"/> Motor Trade Man.
<input type="checkbox"/> Network Plan.
<input type="checkbox"/> Numerical Cont.
<input type="checkbox"/> Operational
<input type="checkbox"/> Research
<input type="checkbox"/> Personnel Man.
<input type="checkbox"/> Planning Eng.
<input type="checkbox"/> Production Eng. | <input type="checkbox"/> AUTO & AERO
<input type="checkbox"/> Aero Eng.
<input type="checkbox"/> A.M.I.M.E.
<input type="checkbox"/> A.E.C. Cert.
<input type="checkbox"/> Auto Engineer.
<input type="checkbox"/> Auto Repair
<input type="checkbox"/> C & G Auto. Eng.
<input type="checkbox"/> Garage
<input type="checkbox"/> Management
<input type="checkbox"/> M.A.I.M.I. Dipl.
<input type="checkbox"/> Motor Vehicle
<input type="checkbox"/> Mechanics
<input type="checkbox"/> CONSTRUCTIONAL
<input type="checkbox"/> A.M.S.E. (Civil)
<input type="checkbox"/> Architecture | <input type="checkbox"/> G.C.E.
<input type="checkbox"/> 58 'O' & 'A'
<input type="checkbox"/> LEVELS SUBJECTS
<input type="checkbox"/> Over 10,000
<input type="checkbox"/> group passes |

Coaching for many major exams, including C & G and assistance in G.C.E./H.C.

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE10 Aldermaston Court, Reading RG7 4PF BPE10

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____

AGE _____

Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/asia) Ltd.; South Africa—Central News Agency Ltd. Publishers' Subscription Rate (including postage): For one year to any part of the world £2:65.

Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

Henry's

**DONT RELY ON YOUR MEMORY
BUY NOW AT BARGAIN PRICES**
Order your latest Henry's Catalogue Price 55p post paid
complete with Discount Vouchers




You pay less
VAT with Henry's
Low Prices

Now built and used by thousands of satisfied customers

BUILD THE TEXAN

20 + 20 WATT IC STEREO AMPLIFIER

As featured by Practical Wireless 1972

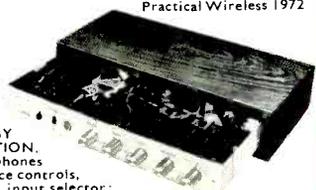


6-IC's, 10 transistors, stabilisers, Gardners low field transformer, Fibre Glass PC Panel, complete chassis work. Now available built and tested as well as in kit form.

HIGH QUALITY & STABILITY ARE PREDOMINANT FEATURES—DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, BY RELIABILITY AND EASE OF CONSTRUCTION. FACILITIES. On/off switch, indicator, headphones socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector; Mag. P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape-head, etc. Constructional details Ref. No. 21, 30p. Distributed by Henry's throughout UK.


FREE Teak cabinet with complete kit.

KIT PRICE £28.50 (+ VAT + 50p carr/packing) or
built and tested £35.00 (+ VAT + 50p carr/packing) as illustrated

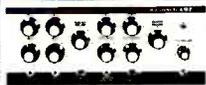EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT



- DISCO MINI:** A complete portable disco, fitted mixer/preamp, 2 decks all facilities. 100 watt amplifier for above. **£98.50**
- SL100:** 100 watt mixer/amplifier with slider controls. **£69.00**
- R50:** 50 watt mixer/amplifier. **£49.50**
- DISCO AMP:** 100 watt mixer/amplifier chassis unit. **£65.85**
- DISCO MIXER/PREAMPLIFIERS (O/P for up to 6-100 watt amplifiers):**
- SDLI (rotary controls):** **£49.50**
- SDLII (slider controls):** **£58.50**
- DISCO VOX (slider controls):** The complete disco unit. **£69.50**
- DJ100:** 100 watt power amplifier for above. **£38.75**
- DJ30L:** 3 channel 3kW sound to light. **£29.50**
- DJ40L:** as 30L plus built-in microphone. **£38.75**
- DIMANATIC:** 1kW adjustable speed auto dimmer. **£25.00**
- SCENESTROBE:** **£19.00**
- ROAD STROBE:** **£25.00**
- Disco anti-feedback microphone:** **£11.95**
- Coit 150 watt liquid wheel projector:** **£22.50**
- 150 watt Q1 liquid wheel projector:** **£50.00**
- 150 watt Q1 cassette wheel projector:** **£50.00**
- Spare Effects cassettes, large range of patterns:** **£8.00**
- Mini spot bank fitted 3 lamps:** **£11.00**
- Auto Trilite (mini with flashers):** **£17.00**
- MIXERS/MICS/SPEAKERS/LIGHTING, UK'S LARGEST RANGE**

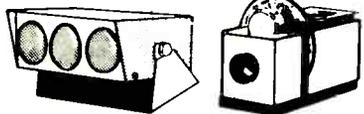

All prices carr. paid (UK) (VAT EXTRA). Barclaycard/Access call, write or phone your order 01-723 6963—easy terms for callers.

10% VAT TO BE ADDED TO ALL ORDERS.

BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable capacity diode tuning, stabiliser power supply, IC Decoder, high gain low noise, IF stages, LED indicators, Tuning meter, AFC. Easy to construct and use. Mains operated. Slim modern design with fibre glass PC, teak cabinet, etc. Available as a kit to build or ready built. Overall size: 8in x 2 1/2in x 6 1/2in. Produced to give high performance with a realistic price. (Parts list and constructional details Ref. No. 5, 30p.) Henry's are sole distributors UK and Europe.



Kit Price £21.00 (+ VAT)
or built and tested **£24.95 (+ VAT)**

LIVING SOUND LOW NOISE TOP QUALITY CASSETTES MADE BY EMI TO INTERNATIONAL STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID LESS THAN REC. PRICES.

	3 for	6 for	10 for	25 for
C60	£1.00	£1.80	£2.80	£6.75
C90	£1.33	£2.57	£4.20	£10.25
CI20	£1.62	£3.15	£5.00	£12.25



Quantity and trade enquiries invited.

LEARN A LANGUAGE—complete with phrase book. German, French, Spanish, Italian. £1.36 per course. £5 for any 4.

LOW COST HI-FI SPEAKERS SPECIAL OFFERS

EMI 13in 8in—full range speakers (post 20p each or 30p pair); *150TC—8 ohms Twin Cone 10 watt, £2.20 each or £4 pair; *450 10 watt c/o Twin Tweeters 3, 8 or 15 ohms, £3.50 each or £6.90 pair; EW 15 watt 8 ohms c/o Tweeter, £4.30 each or £7.90 pair; 350 20 watt c/o Tweeters 8 or 15 ohms, £7.50 each or £14.20 pair.



Polished wood cabinet £4.60, post 35p.

8 ohms full range (post 20p)
FR4 4in 5 watt, £4; FR65 6in 10 watt, £5.50;
FR8 8in 15 watt, £7.60; FR23 9 x 6in 15 watt, £6.00.

BASS AND MID RANGE—8 ohms (post 20p)
AA12 5in 15 watt, £3.20; B110 5 1/2in 15 watt, £5.60; B200 8in 15 watt, £6.45; B139/2 13in x 8in 30 watt LF, £12.25.

TWEETERS AND CROSSOVERS (post 20p)
K2006 10 watt 8 or 15 ohms, £1.90; FHT6 15 watt 8 ohms, £3.20; K2011 30 watt 8 ohms, £3.75; T27 KEF, £4.25; Axcnt 100 30 watt 8 ohms, £4.90; K4009 1kHz/5kHz c/o, £2; SN75 3kHz var. c/o, £1.75.

SPEAKER KITS (carr. etc. 35p)
20-2 8in 30 watt, £10 each; 20-3 8in 40 watt, £15 each; LINTON 2 20 watt, £15.95 pair; GLENDALE 3 30 watt, £28.95 pair; DOVEDALE 3 50 watt, £42 pair; KEF KK2, £20.40 each; KEF KK3, £32 each.

TEXAN STEREO SYSTEM

PLUS Price Savings



The Texan Stereo Systems include the high quality Texan Stereo amplifier assembled and ready to use. A pair of Type 200 20 watt Speaker-Tweeter systems, size 12 x 12 x 10in and a choice of Garrard players built into a plinth with cover with Goldring G800 magnetic cartridge. System 25 uses Garrard SP25 Mk.III and system 76 the Garrard AP76 de luxe turntable. All necessary leads are supplied.

SYSTEM 25 (list approx. £109) **£79.50**

SYSTEM 76 (list approx. £117) **£89.50**

(plus 10% VAT and plus £1.45 carr/packing).

BARCLAYCARD/ACCESS

Call, write or phone your order 01-402 4736. EASY TERMS FOR CALLERS

KITS - TEST GEAR - AMPLIFIERS - SPEAKERS - DECKS POWER SUPPLIES - TRANSISTORS - IC's

See pages 934, 935 and 936 of this magazine

BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene container and taking about 3 hours to assemble—that's the Sinclair Cambridge pocket calculator from Henry's. Some of the many features include interface chip, thick-film resistor pack, printed circuit board, electronic components pack. Size: 4 1/2in long x 2in wide x 1 1/2in deep. Free of charge with the kit for the more advanced technologist is a 32-page booklet explaining how to calculate Logs, Tangents, Sines, etc.



Price £24.95 (+ VAT)

Also assembled ready to use **£27.22 (+ VAT)**

Prices and descriptions correct at time of press E & OE.

Henry's RADIO LIMITED

EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381
354-356 High Fidelity and Tape Equipment 01-402 5854/4736
309 PA, Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW

Open:-
9 am-6 pm
6 days a week
All stores open all day Saturday