## STRICTLY CONFIDENTIAL


FOR PHILIPS SERVICE DEALERS ONLY.

COPYRIGHT 1936

# SERVICE DOCUMENTATION

# OCTODE-SUPER

337 A

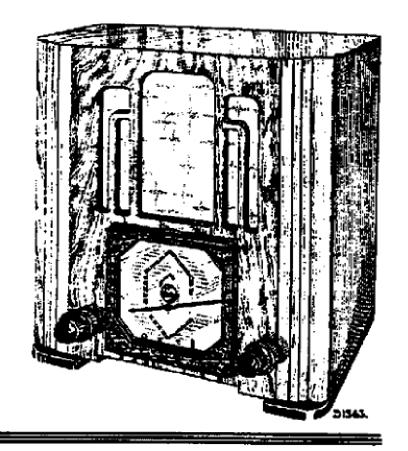

#### GENERAL REMARKS.

Receiver 337A is a super-heterodyne set with built-in moving-coil loudspeaker, for reception of the following frequency bands: 18.18 Mc—5.88 Mc (16.5—51 m) and 1508 Kc—517.2 Kc (199—580 m).

The set has four control knobs. The small knob on the left serves volume control, whilst the large knob fitted concentrically to it operates the continuously variable tone-filter. The small knob on the right serves for tuning and the large one operates the wavechange- and mains-switch. The receiver is provided with A.V.C., connections for a gramophone pick-up and for an extra loudspeaker with a high impedance. A safety contact on the buck ensures that the receiver is entirely "dead" when opened.

## Description of the circuit.

We will first describe the circuit diagram for the medium-wave band, and afterwards for the short-wave band. The voltage on the aerial comes across S11 and is induced in S12, which coil forms a part of the tuned circuit of grid 4 of L1 comprising C23. S12, the tuning condenser C7 and the trimmer C11. The voltage over C7 is conducted via R30, which is of significance for short waves only, to the 4th grid of L1. The circuit C8, S17 with the parallel

padding condenser Cl4 and the series padding condensers Cl6 and C29 is connected to the first grid of Ll. The padding condensers ensure that the frequency of the generator is always 475 Kc higher than the frequency to which the H.F. circuits are tuned in. The parallel condensers do this for the higher frequencies and the series padding condensers for the lower frequencies of the waveband.

C26 is the grid condenser and R10 the leak resistance, whilst R9 has been fitted to prevent parasitic oscillation. S18 is coupled with S17, which causes oscillation. The cathode, the first and second grid of L1 are to be considered as a triode oscillating in a frequency 475 Kc higher than that of the H.F. tuning. Conversion takes place in L1 and in the anode circuit next to the frequencies of the H.F. and the generator signal, are the sum and difference frequencies of these two signals. The circuit S19 with C17 is now tuned to the difference frequency of 475 Kc. S19 induces in S20 the voltage with a frequency of 475 Kc. S20 and S21 form together with C18 the secondary of the first bandpass filter.

The strength of the coupling between S19 and S20 determines the band-width of the band-pass filter. The voltage over C18 is further amplified in L2 and then reaches the band-pass filters before and after

337 A A 2

L3, so that the I.F. voltage, considerably amplified and filtered through 6 circuits, finally reaches the diode, where detection takes place. Regarding the I.F. band-pass filters the following must still be noted. The coupling between the primary and the secondary is strictly inductive. through which an uniform trend of the resonance curve is obtained whilst in this way it is also rendered impossible for whistling and heterodyning noises to penetrate as a result of capacitive coupling. C47 and C48 form at the second band-pass filter a tapping on 1/s of the secondary, in which way a lower voltage occurs on the grid of L3. The transformation ratio between primary and the secondary of the 3rd band-pass filter is about 4: 1, causing as well the signal to be decreased as a better adaptation of the circuits to the valves. The voltage over the secondary of the 3rd band-pass filter reaches the first diode-anode of L4, and a D.C. with a superimposed L.F. current occurs in the anode-cathode circuit, R17, R16, S26, S27, anode. R18 contrary to the diagram, is mounted parellel to R16 and R17, R16 is changed from 32000 Ohm to 0.1 M. Ohm. codenr. 28.770.450.

The L.F. voltage across R17, is applied via C37 to the control grid of L4 and is further amplified via a resistance-coupling element by L5. S31, C49, C41 and C40 form a filter to cut off frequencies above 5000 cycles. For short waves C40 is also connected in series, to suppress low frequencies in which way better reproduction of speech is obtained for short-wave reception.

The A.V.C. operates as follows: When via C38 a more powerful signal reaches the second diodeanode, a larger current occurs in the circuit anode, cathode, R1, R14, R22, R19, causing a larger negative voltage across R22, R14. This negative voltage is applied via R7 to L1, via R20 and R11 to L2 and via R12 to L3. L1, L2, L3 and L4 also receive a fixed negative bias across R1, which is applied via R14, R13 and R15 to the control grid of L4. C23, C24, C30, C34, C35 and C39 are the various decoupling condensers. L1 and L5 respectively receive negative grid bias from the drop of tension across R8 and R5, which resistances are decoupled by C25, C3. The continuously variable tone filter consists of C44, R26 and R27.

S6, C6 is an earial filter which is tuned to 475 Kc. Signals of this frequency are conducted directly to earth and can therefore not penetrate into the I.F. section. For short waves the wiring of the circuits of Ll is quite different. S7 is the aerial coil; S8 with the trimmer C9 and the tuning condenser C7 via C27 form the grid circuit. The oscillator consists of S13, C12, C8 (grid circuit)

and 514 (reaction coil).

For short-wave reception the oscillator fre uency is 475 Kc lower than the frequency on which the H.F. circuit is tuned. This method was selected to prevent damping and to ensure constant working of the Octode, especially for high fre uencies. The padding condensers have been included in the H.F. section. C9 is the parallel padding and C27 the series padding condenser. R6 serves for connecting the 4th grid to the chassis. The I.F. section is the same for short- and medium waves. C40 is taken up in the L.F. section, the result of which is that the reproduction of the low notes is somewhat weakened. L6 is the fullwave rectifying valve; the smoothing filter consists of Cl, S5 and C2.

### TRACING DEFECTS.



Fig. 5

Tracing defects is considerably simplified by using the Universal measuring apparatus as shown in fig. 5. The most usual defects are short-circuits in the wiring and interruptions in soldered joints. These are in indicated by C..., R... shortcircuited or interrupted. Before dismantling or unsoldering any part, first try to determine the cause of the defect by taking measurements. (See "Point to point" system, pages F1 and F2.) The manual is not complete, of course, because combinations may occur.

If the set has been received for repair, the best way to proceed is as follows:

- Insert in the receiver a set of valves from a properly functioning receiver and, if necessary, also try out the set with another loudspeaker.
- II. Examine whether gramophone reception is possible, if so see VII, if not see III.

## III. Check the voltage on C2.

- a. If is too high, there may be an interruption in the positive or negative lead from the H.F. supply to the apparatus (soldering tag etc.).
- b. If it is too low: C2, C33 or one of the bypass condensors e.g. C4, C43 etc. short-circuited; S28, S5 shorted to earth or S5, R1 interrupted.

### Check the voltage on C1.

- c. If it is too high: see a. further S5, R1 interrupted.
- d. If it is too low: see b. but S5, R1 are not interrupted.

Interruption in the primary-circuit of the transformer, mains-switch or safety contact. Measure the primary voltage. A defect in the transformer, measure the secondary voltage. A defect in the valveholder of L6.

## IV. L5 has abnormal current and voltage.

- No anode current: S28, R5 interrupted.
- 2. Anode current too high: R25 interrupted. C3 short-circuited.
- 3. R24 interrupted.

## V. L4 has abnormal current and voltage.

- 1. No anode current: R23, R29 interrupted, C43 short circuited.
- Anode current too high: C37, C34, C35 short-circuited.
- 3. R15, R13, R14 interrupted.

# VI. L4 and L5 have normal voltage and current but no gramophone reproduction.

- 1. R24, S28, C41 short-circuited.
- 2. C40, R17, C37, C42 interrupted.
- 3. Short-circuit in the screened connection from S31 to switch no. 1, or in the screened connection from R18 to switch no. 2.

## VII. Gramophone reproduction, but no reception.

- A. L3 has abnormal voltage and current.
- 1. No anode current: S25 interrupted.
- 2. Anode current too high: C24, C35, short-circuited, short-circuit in grid connection.
- 3. Anode current too low; R31, R4 interrupted; C5, C31, C46 short-circuited.
- 4. RI2, R22, R3 interrupted.

## B. L2 has abnormal voltage and current.

- No anode current: S22 interrupted.
- Anode current too high: C30, C39 shorted;
   R3, S20, S21 interrupted, short-circuit in grid connection.
- Anode current too low: C46, C31 shortcircuited, R4 interrupted.
- 4. R11, R20, R22, R14 interrupted.
- Ll has abnormal voltage and current.
- 1. No anode current: S19, R28, R8 interrupted, C32 short-circuited.
- 2. Anode current too high: C25, C23, C24, C35, C27 short-circuited, R3, R30 interrupted.
- 3. Anode current too low: C31, C46, C4 short-circuited, R4 interrupted.
- R6, R7, R22, R14 interrupted.

337 A E2

# D. L1, L2 and L3 have normal current and voltage.

If, when a signal of 475 Kc is applied to the control-grid (top) of L3 via a condenser of 0,1  $\mu$ F whilst the grid connection remains connected, there is no output:

C38, C21, C22, C36 short-circuited.

2. C21, C22 out of adjustment.

S26, S27 interrupted.

If, when a signal of 475 Kc is applied to the control-grid (top) of L2 via a condenser of 0,1  $\mu$ F whilst the grid connection remains connected, there is no output;

C19, C20 shortcircuited, or out of adjustment.

1. S23, S24 shortcircuited, or interrupted.

If, when a signal of 475 Kc is applied to the control- (4th.) grid (top) of Ll via a condenser of 0.1 µF whilst this grid is connected to earth via a resistance of 0,1 M.ohm (see figure 2), there is no output:

S19, C17 shortcircuited or C1? out of ad-

justment.

S20, S21, C18 shortcircuited or C18 out of adjustment.

If an H.F. signal is applied to this grid and there is no reception, whereas reception is obtained with an I.F. signal, the fault will be in the oscillator section.

If the oscillator does not work, this can be determined by connecting the first grid via a condenser of about 1000 µµF to earth. If a jump is noticeable in the current of grid 2, then the oscillator is functioning. However, if the oscillator does not function, the fault is to be found in C8 being short-circuited, a short-circuited trimmer C14, C12, or an interrupted coil S17, S13. To check the frequency of the oscillator proceed as follows: The aerial socket of an auxiliary receiver is connected via a condenser of 25 µµF to the anodecircuit of L2.

The auxiliary receiver is set at 666.7 Ke (450 m) and the apparatus to be examined at position II. The triple condenser of the receiver under test is now turned till the carrier wave of the oscillator is heard at its maximum strength in the loudspeaker of the auxiliary receiver. If the receiver under test is tuned to a wavelength of 1141.7 Kc (262.9 m) the oscillator-frequency is good because 666.7 Kc + 475 Kc = 1141.7 Kc. If there is a considerable difference, for instance 270 or 250 metres (1111 Kc respectively 1200 Kc) there must be a defect somewhere. C8, C14, C16, C29, C26 interrupted or short-circuited. The oscillator can be examined in the same manner for the wave-band I, but it must be considered that for this band the frequency of the oscillator-circuit is 475 Kc lower as the one of the H.F. circuit.

If there is no reproduction when a H.F. signal is applied to the aerial-contact of the receiver, but there is reproduction when a signal is applied to the 4th. grid of Ll. C7. C9. Cll can be short-circuited, one of the aerial- or grid circuit coils short-circuited if interrupted. or a bad contact in the wave-change switch.

## VIII. Gramophone reproduction and reception, but the quality of one of them is not satisfactory.

- A. Weak reproduction.
- 1. Voltages and currents are not normal.

2. C47, interrupted.

- 3. C44, C41. C45 short-circuited.
- The receiver is out of adjustment.
- 5. Defect in loudspeaker or in loudspeaker transformer.
- B. The sound is distorted.
- 1. One of the valves is operating in grid current.
- One of the grid-leak resistances is interrupted, for instance R24, R25.
- 3. A defect in the loudspeaker or the transformer.
- C. Automatic volume control not operating satisfactorily.

C38 interrupted.

- 2. Short-circuit in C30, C39, C34, C35, C24 or interruption in one of the resistances R14, R13, R15, R7, R22, R19, R20.
- D. The set hums.
- Single-phase rectification, one half of S2 interrupted or breakdown in the valve socket of L6.

2. Cl, C2 interrupted.

- One of the L.F. decoupling condensers is open circuited.
- 4. Loose earth connection to the chassis.
- E. The receiver crackles.
- Bad contact in aerial or earth lead.
- An intermittent short-circuit somewhere in the wiring.

Bad contact in the soldered joints.

- Bad contact in one of the switches, valves or volume control.
- F. The set oscillates.
- 1. C4, C23, C25, C30, C46, C5, C32, C33, C43 interrupted.
- G. Cabinet resonances.

Such resonances may occur through loose parts, such as valve screen caps, springs, strips, etc. When the vibrating part has been traced, it must be fixed, if necessary with a piece of felt.

VOORSCHRIFT. N.V. PHILIPS' RADIO 337A 337 A - 06 Apparaat: TE EINDHOVEN - HOLLAND 337 A plac 4 0 APD. FABRICAGE-VOORSCHRIFTEN # 36 - 37 4. **.** - '36 SPECI FICATIE Dat. traperi vituaerina Apparaat: 337A 0pm: = 02 ALUidspr. type 4233 Schema type Superhet Jultschakelaar 22.00 Golfbereiken 133.580 16.5.51 AMergeleverneant. 4 ت تنسنت Stroomsoort en frea Schaaltupe Aant-HF-kringen فأتر بعج فأبع عنة N. max L knop <u>rake links</u> \* MF-2+2+2 MF. In kHz. golfi. ) senati wyzer 75 mH: 늗 Overbrenging school 2 22 20 3CASE Yking Kleur 10 kHz soverzicht d Frim-vermogen mentes in Directo Opdruk Vi Buzonderheden Geroeligheid <117 x1 Sec. channel matio التفعفيل بتواري والمراجزات 250 19V iInai ca ties Witzer ach Tit Schaal 175 Type ant . kopp. Aistemindicator stroom koopeling Sperkringen) O Netfilter ME d) zie sinets Kast wyziging kruisjes. nesn Kwal . correctie 5hille 026 Venster Mex." Autom. vol.reg. Kaartensleuf 7625 Luidapr.dock 1.0111.05 Slent tuning resa. Opdruk achterw. 2/2 150235 Type, kleur, vol. knop A Netsp.groepen

Batt.spanningen <u>6gr</u> Anodestr verbr. = Extra luids praansl. 47702 Foou-Gram.opn. aansi. terugk. " Veiligh.contact nzzn Uity. vol. reg. radio 30/ pot meter toonreg. oorschriften HF. lamp(en) Poet. Mengiamp golf schak. AK2/P35) EK2 [P32] Osc. lamp MF-lamp(en) net schak. normael accomb gram schak. 2xAF3 /730) 21EF5 2°Det.lamp 77231 EBCI ABC1 1730) Spanningsatt. <u>جاسب الا 10 تواف</u>ت 2 E Eind lamp (en) Pai ins AL4 (P35) EL3 / 235/ Merk plaatje E Typeplaatje Lampen plaatje o Gelykricht amp ( P35) EZ3 1730 2x 8044-99 2×8055-49 Veri. lamp(en) 337A 337A-06 Afd. als 337 6 doon: (28A 337-06 als 337A-06 docod Lampen: zie tabel schaal: Mullard .. alleas kg namen ستخديم ال See . Racios gamatoone Hi ISPE doctor 337 A-06 Chassis Siera knoppedi of philite muliard alx377 A doch schoolondruk merk: Mullard Luidsprace: Rad. knoppen Siera philite !!! 337A A 65 X 304 •<u>\$</u>

Vervangen door: Vervangen door: Wijz, voorstal:

#### TRIMMING THE RECEIVER.

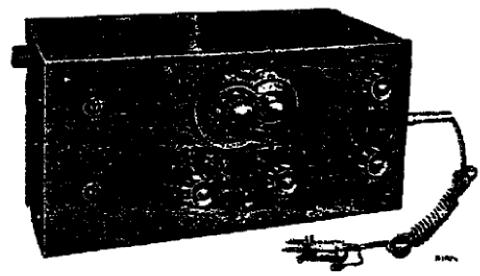



Fig. 1

A receiving set has been equipped with trimming condensers in order to eliminate possible differences in the capacity of the tuning circuits. If this would not be the case, these circuits would not be in step and an inferior amplification and selectivity would be obtained.

First the I.F. circuits are trimmed, as the I.F. amplifier has to be used for further adjusting. The tuned circuits of the I.F. part consist of inductively coupled bandpass filters. The width of the resonance curve of these filters is determined by the strength of the coupling between primary and secundary winding.

Trimming of I.F. circuits is done best by applying the I.F. signal to the grid of the valve in which anode circuit the I.F. transformer is located that has to be trimmed. In this manner the best resonance curve is obtained. So if C21, C22 have to be trimmed the signal is applied to the control grid of L3, for C19, C20 to L2 and for C17, C18 to L1. It is not necessary to use damping resistances in this apparatus when trimming the I.F. circuits as the coupling between primary and secundary of the I.F. transformers is fairly loose and thus no double peaks will occur.

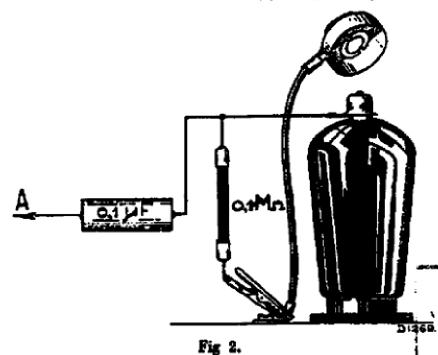When in this description "applying a signal" is



used, always a modulated signal is meant as a non-modulated signal would not give any reading on the outputmeter. Applying a signal to the

control grid is done as follows: The grid cap is taken away and the grid is connected via a resistance of 0.1 M.ohm to the chassis whilst the signal is applied to the grid via a condenser of 0.1 µF (see fig. 2 ). The volume control always should be turned on maximum; if the signal is too strong the attenuator of the service oscillator is turned back.

As far as trimming of the H.F.- and oscillator circuits is concerned the following should be noted: The generator part is tuned to a frequency which is 475 Kc higher than the one on which the H.F. circuit is tuned.

The H.F. circuit is tuned with an auxiliary apparatus for which can serve any properly functioning receiver which can be tuned to the trimming frequencies, or with an aperiodic amplifier, for instance G.M. 2404. Tuning the H.F. circuit is done as follows: The generator of the apparatus that is being trimmed is short-circuited by connecting the first grid of L1 to the chassis. A condenser of 25 μμF is connected between the anode contact of L1 and the acrial socket of the auxiliary receiver. The output indicator is connected to the auxiliary receiver. The signal is applied to the aerial socket of the receiver being trimmed and the auxiliary receiver is tuned to this signal. Next the tuning condenser of the receiver being trimmed is turned till maximum output is obtained. The H.F. circuit is now tuned exactly to the applied signal.

The short-circuit of the generator and the auxiliary receiver both are taken away and the output indicator is connected to the receiver being trimmed. Care should be taken not to turn the tuning condenser in the meanwhile. Next the trimmer of the generator is adjusted to maximum output.

The H.F. circuit of the shortwave band also is adjusted with the aid of an auxiliary receiver. However, care should be taken that the generator, when trimming this range, thould be tuned at a frequency which is 475 Kc lower than the one on which the H.E. circuit/ is taned. That means that if with the trimmer of the generator two maximum positions are found, the position with the highest capacity of the trimmer is the correct one.

For trimming both ranges a fixed condenser scale is used for which an auxiliary scale has to be taken.

A drawing M 1380 has been inserted and with the particulars given therein it will not be difficult to make a dial of celluloid.

The following apparatus and tools are needed for trimming:

- A service oscillator, e.g. G.M. 2880 with a waverange from 14—3000 m (21.5 Mc—100 Kc) see fig. 1.
- An artificial aerial for 14—200 m, and one for 200—3000 m; both are delivered with the above mentioned oscillator.
- An output indicator; e.g. with high resistance which can be connected parallel to the loudspeaker transformer. By switching a condenser between output indicator and receiving set



Fig. 3

care is taken that no D.C. will flow through the indicator. If the output indicator has low resistance of the same value as the loudspeaker the latter is replaced by the indicator. In that case an adaption box (G.M. 2295) can be used which comprises an adapted impedance with selenium rectifier through which direct reading can be obtained on a mayometer. Also the Universal Measuring Apparatus type 4256 (fig. 5) contains an output indicator.

- 4. An insulated screwdriver with as little metal as possible (fig. 3).
- An auxiliary dial.

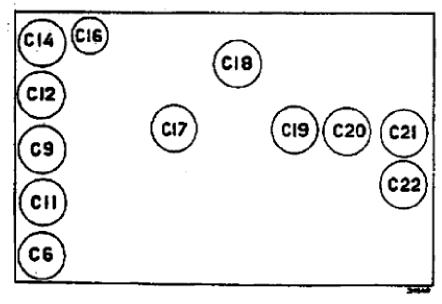


Fig. 4

An auxiliary receiver or an aperiodic amplifier.

## Trimming L.F. part.

Before aligning, the sealing wax of the trimming

condensers has to be softened, which can be done with a soldering iron that should not be too hot, to prevent melting of the solder.

For the positions of the trimming condensers see fig. 4

- 1. Signal of 475 Kc to the grid of L3, trim C21, C22.
- 2. Signal of 475 Kc to the grid of L2, trim C19, C20.
- 3. Signal of 475 Ke to the grid of L1. trim C17, C18.

### Adjusting acrial filter.

Signal of 475 Kc to aerial socket. Switch receiver on medium waveband. Variable condenser in maximum position. Trim C6 for minimum output.


Trimming of H.F. and generator circuits for medium waverange.

- 1. Adjust condenser with the auxiliary scale on 25 degrees from minimum position.
- 2. Apply signal of 1500 Kc via normal artificial aerial to aerial socket.
- 3. Trim C14 and C11 at maximum output.
- Short-circuit generator, connect auxiliary receiver.
- 5. Apply signal of 550 Kc, tune condenser of receiver at maximum output of auxiliary receiver.
- 6. Take away short-circuit of generator and auxiliary receiver.
- 7. Trim C16 at maximum output.
- 8. Short-circuit generator and connect auxiliary receiver.
- Apply signal of 1500 Kc and tune condenser of receiver at maximum output of auxiliary receiver.
- Take away short-circuit of generator and auxiliary receiver.
- 11. Trim C14 to maximum output.
- 12. Eventually repeat 4, 5, 6 and 7.

The trimmer Cl6 is located right underneath the condenser drive. For this reason special care should be taken when adjusting this trimmer not to move the variable condenser.

#### Trimming short-wave range.

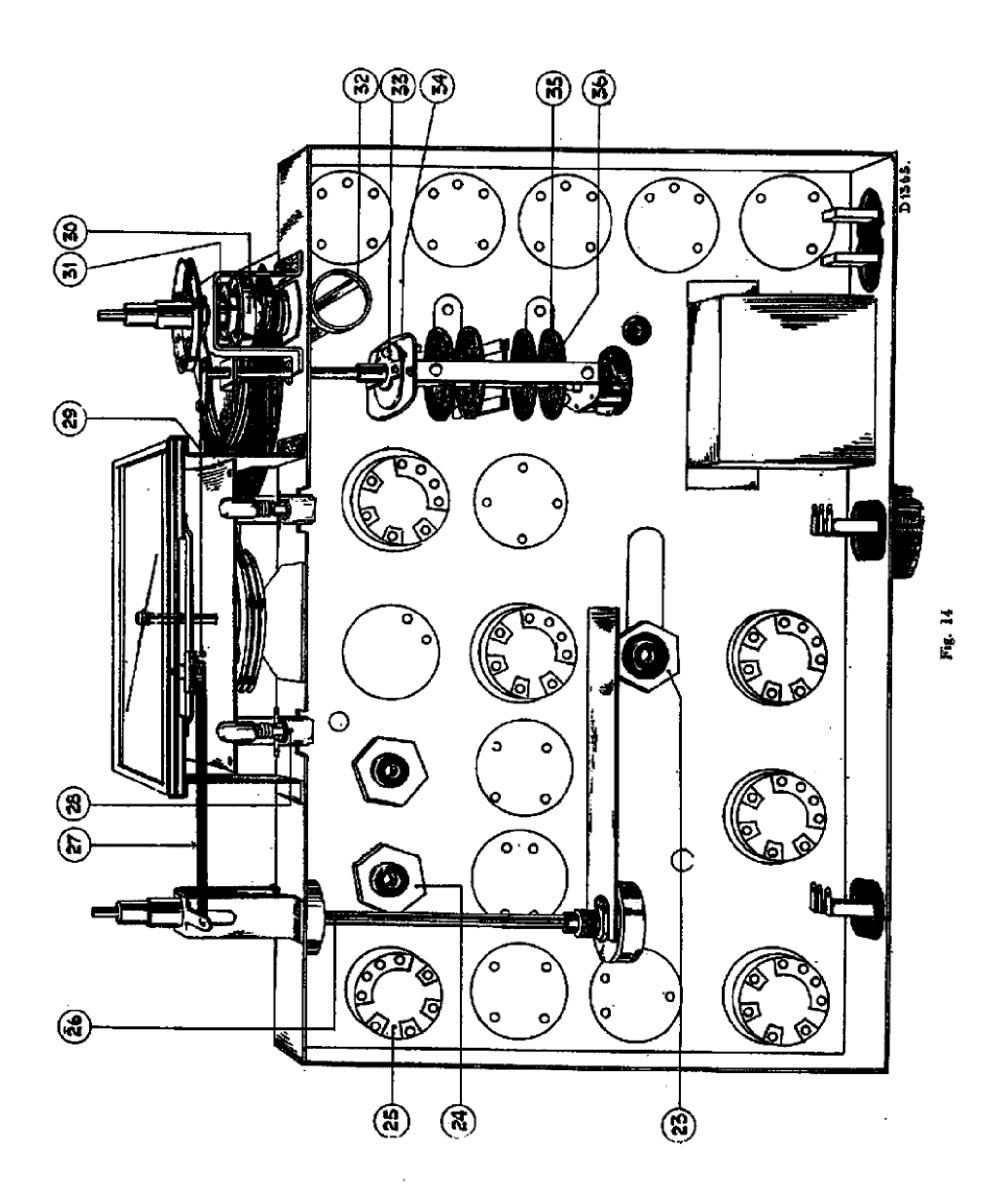- 1. Adjust condenser with the auxiliary scale on 17 degrees from minimum position.
- 2. Apply signal of 18 Mc (16.6 m) via artificial aerial of 400 ohms to aerial socket.
- Short-circuit generator and connect auxiliary receiver.
- 4. Trim C9 to maximum output of the auxiliary receiver.
- 5. Take away short-circuit of the generator and the auxiliary receiver.
- 6. Trim C12 to maximum output.



## LIST OF SPARE PARTS AND TOOLS

When ordering parts and tools always mention:

- Codenumber.
   Typenumber of the receiver.
   Description.

Fig.	Pos.	Description	Codenumber	Price
12	1	Cabinet	25.870.190	
12	3	Ornamental window	25.870.200	
12	4	Station dial	28.701.320	
12	5	Needle	28.896.080	
12	6	Small knobb	23.610.260	
12	7	Large knob	23.610.250	
13 13	B	Spring for fixing rear panel	28.750.040	
13	9 10	Spring for fixing rear panel	28.751.280	
13	11	Rear panel	28.397.763	
13	12	Mains two-pin plate	25.742,000	
13	13	Socket plate (pick-up)	28.870.750 28.888.360	
13	14	Protecting cover loudspeaker contact	23.992.541	
13	15	Socket plate (aerial-earth)	28.888,370	
13	16	Cardboard screening plate (small)	28.338.510	
13	17	Cardboard screening plate (large)	28.336.510	
13	18	Tension change-over disc	25.868.940	
13	19	Tension change-over plate	28.867.481	
13	20	Contact plate	28.838.040	
13	21	Valve cap (small)	28.906.022	
13	22	Valve cap (large)	28.855.310	
14	23	Nut for electrolytic condenser (small)	07.093.022	
14	24	Nut for electrolytic condenser (large)	07.093.010	
14	25	Valve socket 8 contacts	25.161.921	
14	26	Spindle for R17	28.145.200	
14	27	Spiral spring	28.740.250	
14	28	Holder for dial lamp	28.837.960	
14	29	Driving string	33.635.550	
14 14	30 31	Vernier unit (complete with spindle and friction)	28.881.980	
14	31 32	Spring for vernier unit	25.870.170	
14	33	Bracket for trimmer	28.920.500	
14	34	Arresting ball for wavechange switch	89.205.040 28.942.260	
14	35	Spring for wavechange switch	28.934.580	
14	36	Rotor without contacts	28.477.210	
		Stator contact	28.750.970	
· i		Clip for stater contact	28.077.390	
		Conducting cramp	28.077.380	
		Rotor contact 1.1	28.904.160	
		Rotor contact 2.1.2.	28.904.140	
		Rotor contact 3.1.3	28.904.150	
	:	Mains switch	08.524.260	
		Rivet for fixing mains switch		
		Clamping ring with incisions	28.445.821	
-		Paper ring	28.445.390	
		Protecting cap	28.250.431	
1		Service oscillator complete with 2 artificial aerials		
3		type G.M. 2880	09.991.260	
0		Insulated screwdriver	09.991.500	
- 1		Right angle screwdriver	09.990.360	
5		Adaptation box for outputmeter type G.M. 2295	09.991.310	
5		Universal measuring apparatus type 4256	09.991.030	
7		Universal mounting table	09.991.380 09.990.760	
i		Boxspanner for electrolytic condensers (small size)	09.991.540	
		Jack for coils	09.991.560	
10	1	Centring gauge	09.991.022	
- 1	-	Pertinax calipers	09.990.840	

337 A

## COILS


Desig- nation	Description	Code- No.	Price
S5	choke	28.546.050	
\$6 C6	stop circuit	28.570.260	
S7 S8 C9	acrial coil I	28.570.270	
S11 S12 C11	acrial coil II	28.570.280	
S13 C12 S14	osc. coil I	28.570.290	
S17 C14 S18	osc. coil II	28.570.300	
S19 C17 S20	I.F. coil	28.570.200	
S21 C18	I.F. coil	28.570.210	
S22 C19 S23	I.F. coil	28.570.200	
S24 C20 C47 C48	I.F. coil	28.570.250	
S25 C21 S26	I.F. coil	28.570,230	
S27 C22 C36	L.F. coil	28.570.240	
S28 S29	loudspeaker transformer	28.528.110	
S30	speech coil	25.152.420	
\$31 \$1	filter coil	28.587.000	
S2 S3 S4 S32	mains transformer	28.527.910	


## VALVES

L1 L2 L3 L4 L5 AK2 AF3 AF3 ABC1 AL4		
-------------------------------------	--	--

CONDENSERS						
Desig- nation	Value	Code No.	Price			
C1	32 µ.F	28.180.130				
C2	32 μ <b>F</b>	28.180.130				
C3	50 μ <b>F</b>	28.182.160				
C4	0,1   <b>1   1   1   1</b>   1	28.198.200				
<b>C5</b>	50000 բրե	28.198.170				
C6	10-170 μμΕ					
C7	10-470 μμΕ	28.211.390				
C8	10-470 μμΕ					
C9	2,5-30 μμΕ					
Cli	2,5-30 μμΕ					
C12	2,5-30 μμΕ					
C14 C16	2,5-30 μμΕ	28.211.150				
C17	10-170 μμ <b>F</b> 10-170 μμ <b>F</b>	20.211.130				
C18	10-110 μμΓ					
C19	10-170 μμΕ					
C20	10-170 μμΓ					
C21	10-170 μμΕ					
C22	10-170 μμΕ					
C23	50000 μμ <b>F</b>	28.198.430				
C24	20000 µµF	28.198.130				
C25	50000 μμ <b>F</b>	28.198.170				
C26	100 μμΓ	28.190.130				
C27	4500/3 μμΕ	28.190.310	İ			
C29	350 µµF	28.191.390	ļ			
C30	50000 μμΕ	28.198.170	1			
C31	50000 μμ <b>F</b>	28.198.170	† !			
C32	50000 μμΕ	28.198.170	1			
C33	50000 μμ <b>F</b>	28.198.170	ļ			
C34	0,1 μF	28.198.200				
C35 C36	0,1 µF	28.198.200	į			
C37	2100 μμ <b>F</b> 20000 μμ <b>F</b>	90 100 120				
C38		28.198.130 28.190.130				
C39	100 μμ <b>F</b> 10000 μμ <b>F</b>	28.198.100	ļ			
C40	10000 μμΕ	28.190.230				
C41	1600 μμΕ	28.190.250	]			
Č42	20000 μμΕ	28.198.130				
C43	0,1 μΕ	28.198.200				
C44	0,1 μΕ	28.199.370	İ			
C45	100 μμ <b>F</b>	28.190.130				
C46	50000 μμ <b>F</b>	28.198.170				
C47	25 μμ <b>F</b>		ļ			
C48	125 μμF					
C49	640 μμ <b>F</b>	28.190.210				

			100		. 000,1,00		cra
	28 770 950		100		00.000		214
	28,770,180		200	4	99 770 450		214
	28.770.450		R29		28.770.450		R13
	28.771.070		R28		28.770.550		R12
	28.811.020		R27		28.770.430		RII
	28.770.220		R26		28.770.420		RIO
	28.770.420		R25		28.770.130		R9
	28.770.530		R24 - :=	1 1	28.770.170		R8
	28.770.480		- R23		28.770.430		R7
	28.770.560		R22		28.770.540		R6
	28.770.500		R20		28.770.820		RS
	28.770.560		R19		28.771.080		R4
	28.770.460		R18		28.771.050		æ
	28.810.760		B17		28.771.100	0,1/2 M. Ohm	R2
	28.770.400	32000 Ohm	R16	-	28.770.100		2
Price	Code No.	Value	Designation	Price	Code No.	Value	Designation
	ANCES	RESIST.			ANCES	RESISTANCES	

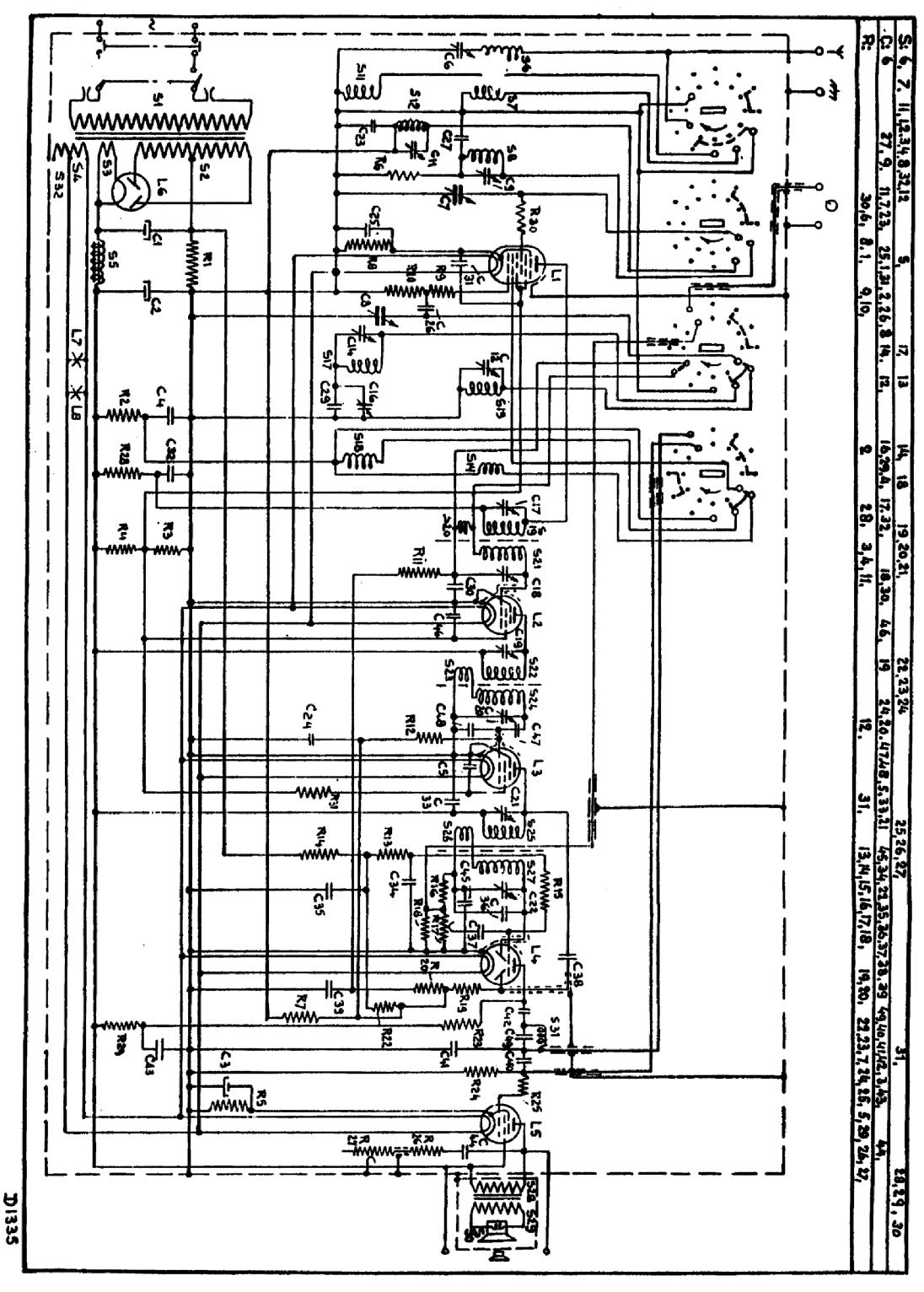

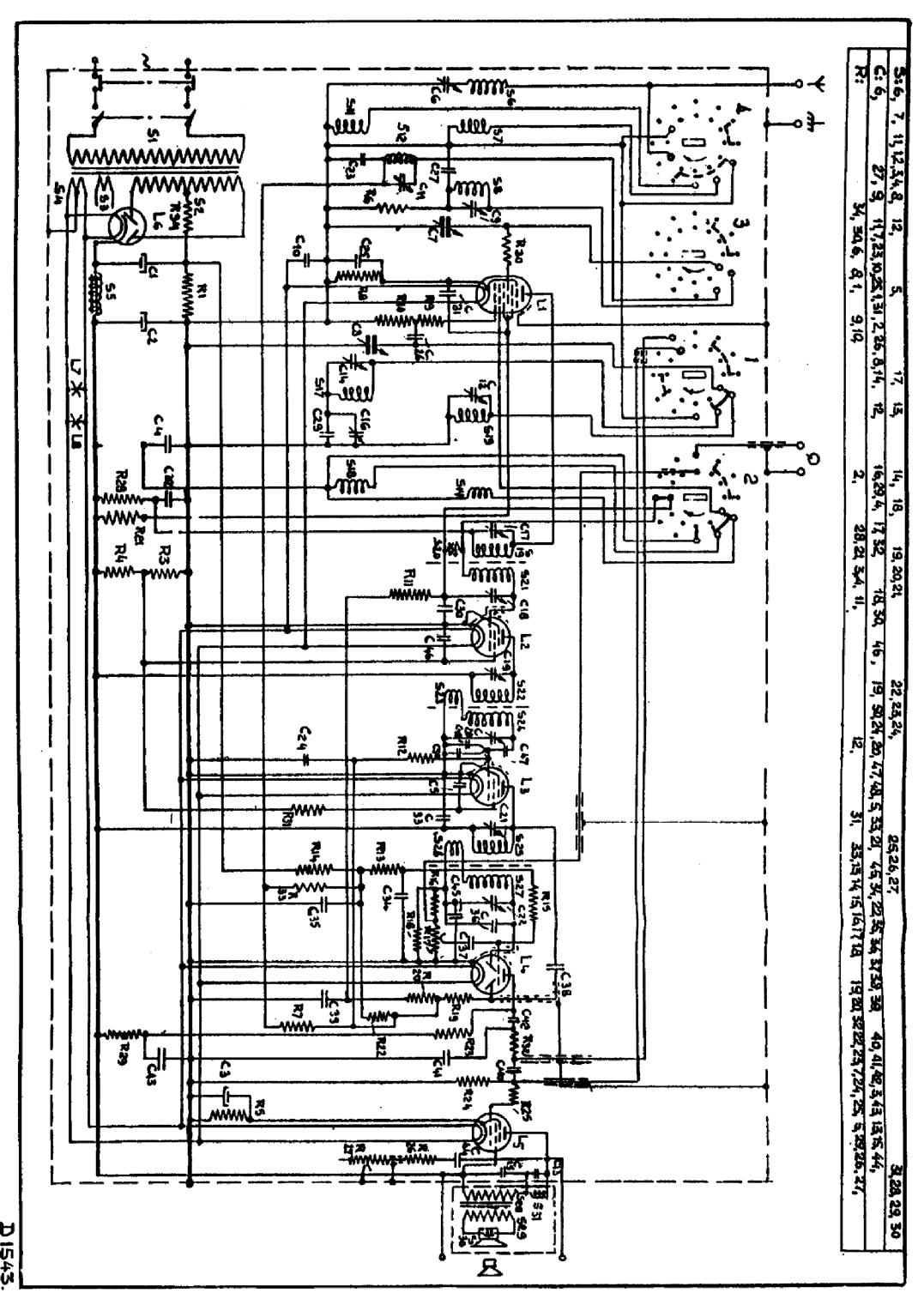

## 337 A-06

Supplement documentation for type 337 A-06. To be used together with documentation for type 337 A.

The circuit diagram of the receiver type 337A-06 is nearly the same as that of the receiver type 337A. The differences are mentioned below.

Considering the fact that other valves are used, the "Economical" series, some precautions are taken which are not fitted in type 337A.

So, C10 gives a decoupling of the filament of L1. R21 serves to give the screen grid of L1 the right tension, whilst R32 prevents the I.F. voltages to enter the L.F. part. R33 serves to reduce the influence of the A.V.C. on L1. Further a filter circuit is provided which consists of C13, S31 and C15, and cuts off the higher frequencies in the reproduction.

To prevent a defect of L6, R34 is placed in the plate-circuit, so the charge-current of Cl is limited.

The chapters "Description of the circuit diagram"; "Trimming the receiver"; "Tracing defects", "Dismantling and Repairs" and the list of spare parts and tools of the documentation for 337 A can be used, whilst a new Point to Point measuring table is given.

Please note that the code number of the rear panel is for type 337A-06; 28.398.520g and the code number for rotorcontact 4.1.4; 28.904.180.


Table of voltages and currents measured with the Universal Measuring Apparatus type 4256

	L1	L 2	L3	L 4	L 5	
Va	230	270	270	71	232	Volt
Vg′	g3-5 = 48 $g2 = 190$	88	87		270	Volt
-Vg	g4 = 1.4				6.35	Volt
Ia	0.6	8.2	8	0.62	<b>3</b> 6	m.A.
Ig′	g3-5 = 1.1 $g2 = 3$	2.2	2,2		4.2	m.A.

Vf = 6.3 V


Total consumption 70 V.A. (63 W)

# DRAWING AUXILIARU SCALE

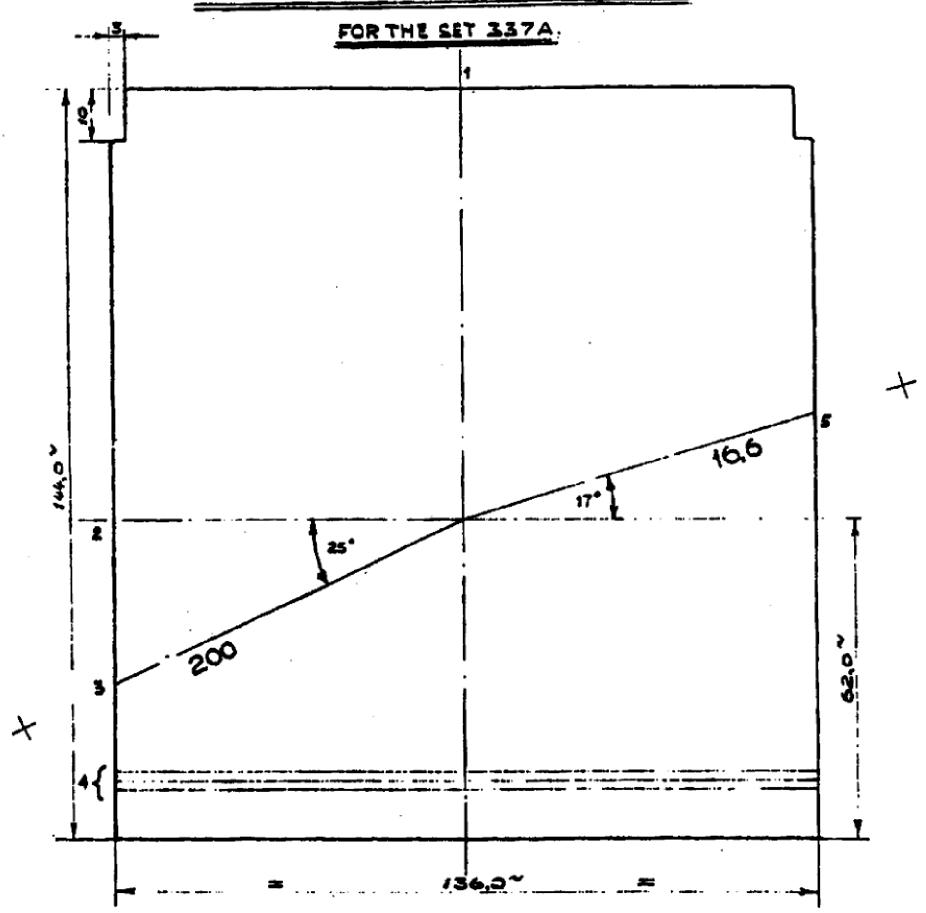

LINES 1.2.3,4 and 5 TO DRAW WITH SHARP SCRATCHING NEEDLE. NUMBERS 200 and 16.6 TO DRIVE IN WITH PUNCHFIGURE.

( TO FILL WITH BLACK INK.)

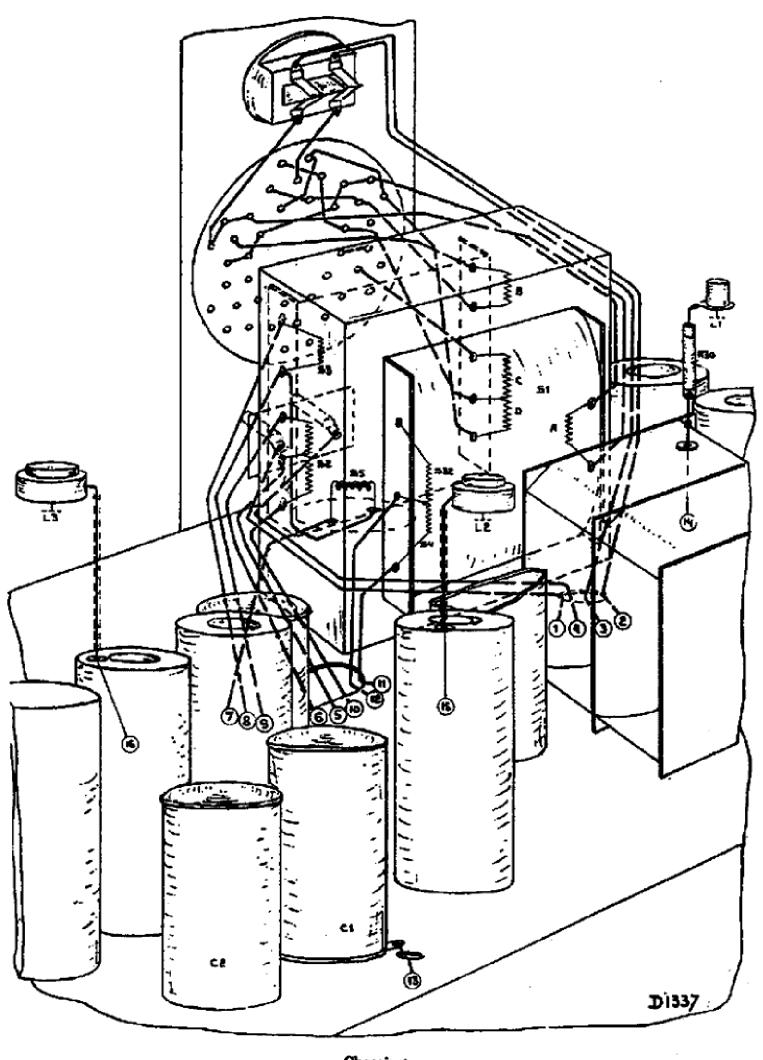

Chassis top.

