

3212 **Blueprint Section Every Month**

# **RADIO AGE**

*The Magazine of the Hour*



(See Story page 39)


**December  
1926**

**Death Ray Tube Rival of  
Radium ◀ Six Tube Shield-  
ed Receiver ◀ Parts Busi-  
ness is Not Dead**

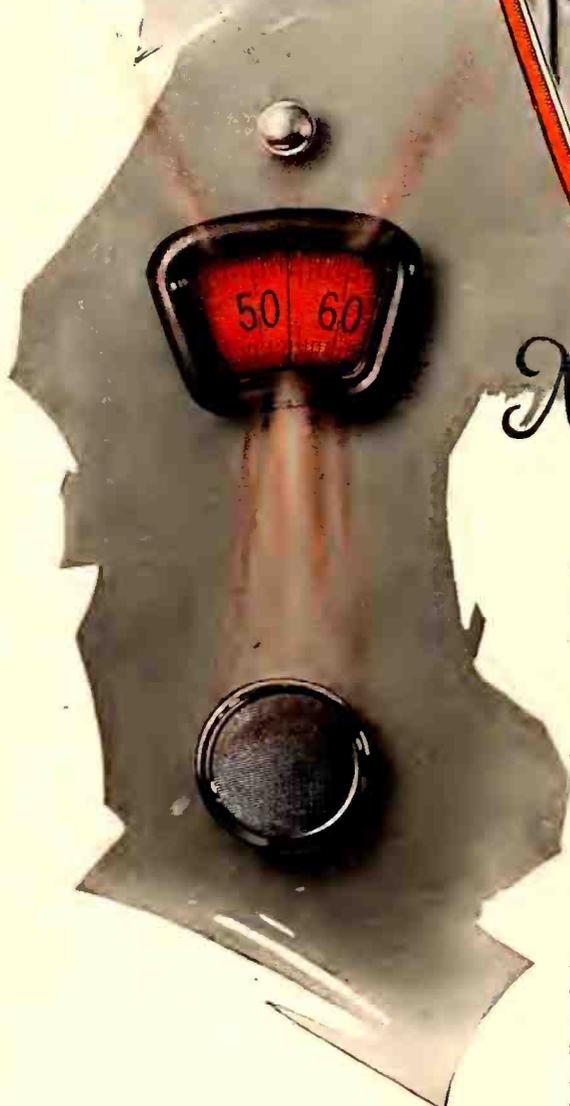**25¢**

**Complete Broadcast List**  
*In Each Issue*

Contrast the clumsy dials of only two years back . . . with the handsome illuminated controls MAR-CO makes today. Here is another good reason for building your set yourself!



## Now dials give place to glowing spots of light

PICTURE a soft, subdued light in the room . . .

- • • your set in the corner with glowing spots of light illuminating its swiftly readable *back panel* scales.
- • • this is radio at its handsomest . . .
- • • this is the panel arrangement, the type of skillful tuning, that distinguishes the 1927 trend in set construction.

Already, these new MAR-CO controls are specified on special equipment in a score of this season's most advanced circuits. At once, they have become the standard in tuning control design. Use them, in whatever set you build, to give the final touch of style, and the utmost in precision control.

MAR-CO controls are easy to install. The steel template pro-

vided reduces panel-drilling to the simple, fool-proof operation illustrated below. The original MAR-CO "friction-drive"—the action that makes backlash impossible—has been strengthened, to accommodate gang condensers. The MAZDA lamp supplied runs on your "A" battery, using only .1 ampere. The switch that controls this lamp may also be used as your filament switch; the lighted scales then serve as pilots. Scales read 0 to 100, or 100 to 0, as preferred. Price, including template, bulb, and bezel, \$3.50. Replacement bulbs, \$.20. Write today for the booklet that illustrates 15 standard makes of condensers mounted on MAR-CO back-panel controls. Martin-Copeland Company, Providence, R. I. Branch offices and representatives in principal cities.

Prominent among the advanced circuit designs which call for MAR-CO controls, is the

Radio Age "All-Range" Receiver

## MAR-CO Illuminated Controls

Here's how you drill the panel..



Screw Template to panel



Drill holes through Template



Remove window opening



Bezel covers rough edge

that's ALL you CAN'T go wrong!




# I Will Train You At Home To Fill a Big Pay Radio Job



"I give you all this apparatus so you can learn quickly at home the *Practical Way*"

J.E.S.

EXTRA COST

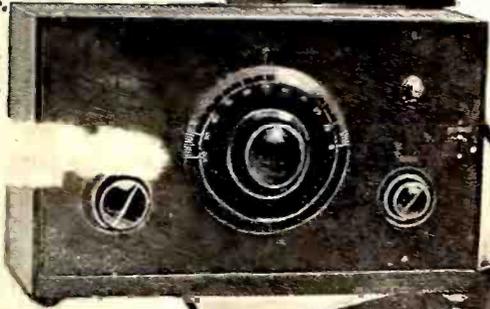

## You Get All of This

All instruments shown here and others sent to all my students free of extra cost under short time special offer. Clip coupon now—find out all about this big unequalled offer while you still have time to take advantage of it. This training is intensely practical—these instruments help you do the practical work. You learn workmanship and get added confidence in your ability.



\$70 in One Day For T. M. Wilcox

"I am in business for myself and RECENTLY MADE \$70 IN ONE DAY. I was an electrician of rich experience, occupying a splendid position as telephone superintendent when I enrolled with you believing it would open up greater opportunities—haven't been disappointed. Estimate Radio will be worth tens of thousands of dollars to me in next few years." T. M. Wilcox, Belle Island, Newfoundland.

### World Famous Training That "Pays for Itself"

My Radio course World-Famous as the training that "pays for itself." Make more money QUICK when you take up this practical course. Work on millions of antennae, receiving sets, offers you big chance to make spare time cash while you're learning. I'll show you how—teach you the latest "dope," furnish you with business cards, show you how to get the business and make it pay. My students don't wait a year to increase their income—they report QUICK INCREASES as a result of this course—often two or three weeks after starting. Howard Luce, Friedens, Pa., made \$320 in 7 weeks during spare time. D. H. Suitt, Newport, Ark., writes, "While taking the course I earned in spare time work about \$900." Earl Wright, Omaha, reports making \$400 in a short time while taking course—working at Radio in spare time! Sylvester Senso, Kaukauna, Wis., made \$500. These records not unusual—these men a few of hundreds.

### Your Satisfaction Guaranteed

We who know the results this practical tested training gets—the increased earnings it has brought to men everywhere—stand behind it all the way with a signed guarantee bond that we give you when you enroll. On completion if you're not entirely satisfied in every way, you get back every cent you've paid us. No strings to this offer—you yourself are the only judge. Get started today! It's your big chance for one of the bigger Radio jobs—mail coupon NOW for my Big FREE BOOK and proof! No obligation.

If you're earning a penny less than \$50 a week, clip coupon now. Send for AMAZING FREE BOOK, "Rich Rewards in Radio." Why go along at \$25 or \$35 or \$45 a week, when you could earn \$50 to \$250 in the same six days, as a Radio Expert? Hundreds of N. R. I. trained men are doing it—why can't you?

## Earn \$50 to \$250 a Week—

### RADIO EXPERTS IN BIG DEMAND

Radio needs trained men. Get into this new live-wire profession of quick success. It's the trained man, the Radio Expert, who gets the big jobs of this profession—paying \$75, \$100, \$200 a week and up. Every day N. R. I. trained men are taking good places in the Radio field—men just like you—their only advantage is TRAINING. You can prepare just as they did, by new practical methods. Our tested clear training makes it easy for you. Big Free Book contains all the proof.

## You Learn Quickly In Spare Time

So sure am I that I can train you successfully for a better future in this new Big-Pay profession, that I guarantee your training with a money-back bond. Lack of experience or education won't hold you back—common schooling all you need to start. You can stay home, hold your job, and learn quickly and pleasantly in your spare time. My practical, helpful methods enable you to start RIGHT AWAY toward one of the bigger Radio jobs paying \$50 to \$250 a week. No delay, no losing time from work—no scrimping or scraping to get your training.



Operates WMAQ  
"Accepted a position with the Chicago Daily News Station WMAQ. MY INCOME PRACTICALLY DOUBLED, thanks to you. I handle all consultation, also do operating. Your course taught me not only the theoretical but also the practical knowledge that makes my work easy for me." Keith Kimball, Station WMAQ, Chicago, Ill.

## Get This FREE BOOK

Most amazing book on Radio ever written—full of facts and pictures—tells all about the great new Radio field, how we prepare you and help you start. You can do what others have done—GET THIS BOOK. Send coupon today—no obligation.

J. E. SMITH, President  
NATIONAL RADIO INSTITUTE  
Dept. PU-3, Washington, D. C.



MAIL THIS COUPON TODAY  
J. E. SMITH, President  
NATIONAL RADIO INSTITUTE  
Dept. PU-3, Washington, D. C.  
Dear Mr. Smith—Without obligating me in any way, send me your free book, "Rich Rewards in Radio" and all information about your practical, home-study Radio Course.

Name ..... Age .....  
Street Address .....  
Town ..... State .....

## EMPLOYMENT SERVICE TO ALL GRADUATES

## Originators of Radio Home-Study Training

Please Mention Radio Age When Writing To Advertisers.

# RADIO AGE

The Magazine of the Hour

Established March, 1922

Volume 5

December, 1926

Number 12

## CONTENTS

FOR DECEMBER ISSUE

Cover Insert by Gordon K. Martin	
Start Radio with Crystal Set.....	5
By Armstrong Perry	
Baseboard vs. Chassis Construction.....	8
By H. Melchior Bishop	
Double Wave Remote Control Transmitter.....	9
By A. P. Peck	
Death Ray Tube Turns Gases to Solids.....	11
Highlights on Wavelengths and Frequencies.....	13
By Kirk B. Morcross	
Turning Soprano to Contralto.....	16
By I. J. Karr	
What Do We Get From Boston?.....	17
By Dorothy Brister Stafford	
Design and Manufacture of Resistance Units.....	20
By Joseph Morgan	
Versatility and Simplicity in This Set.....	21
Six Tube Receiver Completely Shielded.....	25
By McMurdo Silver	
Who Said the Parts Business is Dead?.....	33
By F. A. Hill	
Use Radio to Observe Continental Drift.....	35
By S. R. Winters	
Radio Storm Detector.....	36
Pickups and Hookups by Our Readers.....	37
New York-London High Speed Cable Link.....	39
With the Manufacturers.....	40
Art of Television not Far Off.....	42
By Albert W. Franklin	
Types of Rectifier Tubes Discussed.....	48
By Frank L. Eichner	
Correct List of Broadcast Stations.....	62-64-66-68-70
Classified Advertisements.....	71

Radio Age is published monthly by RADIO AGE, Inc.  
Member: Audit Bureau of Circulations.

Publication Office, Mount Morris, Ill.  
404 North Wesley Ave.,

Address all communications to RADIO AGE, Inc.  
Executive, Editorial and Advertising Offices  
500 N. Dearborn Street, Chicago, Ill.

FREDERICK A. SMITH, *Editor*  
F. A. HILL, *Associate Editor*  
M. B. SMITH, *Business Manager*

*Advertising Manager*  
HARRY A. ACKERBURG  
500 N. Dearborn St., Chicago, Ill.

*Eastern Representative*  
HEVEY & DURKEE, 15 West 44th St., New York, N. Y.

*Pacific Coast Representative*  
V. M. DEPUTY & ASSOCIATES, 515 F. W. Braun Bldg.,  
Los Angeles, Cal.

Final Advertising forms close on the 20th of the 2nd month  
preceding date of issue

Vol. 5, No. 12, Issued monthly. Subscription price \$2.50 a year. December 1926. Entered as second-class matter at post office at Mount Morris, Illinois, under the Act of March 8, 1879.

Copyright, 1926, by RADIO AGE, Inc.

## Chats With the Editor

SCIENTISTS at large will welcome Dr. Coolidge's recent perfection of a cathode ray tube whose use in research will open many avenues heretofore closed. A diagram of the tube, together with a brief description of its functions, is presented for the benefit of our readers.

Armstrong Perry tells how to get started in radio at a very slight expense by use of the crystal receiver. This is one of a series of articles which Mr. Perry has prepared for the beginner and should be fine reading for the man who is just on the threshold of radio.

A combined short-long wave receiver, and a wavemeter of the resonance indicating type, has been prepared for the enthusiast who does not care to be limited to a single wave band for reception. The wavemeter is for the more advanced experimenter.

Another receiver of interest, available in kit form, is the six tuber which is completely shielded. It is described and illustrated in the blueprint section of this issue.

Kirk B. Morcross gives our readers an idea of why the wavelength allocations made by the government are figured in kilocycles instead of meters. Many a fan who has been puzzled by the kilocycle terminology will find the explanation a rational and simple one and much better suited to our needs than any other method.

Side band transmission is detailed by I. J. Karr who tells of some of the work being done by the General Electric with that type of transmission. Three advantages are listed for the side band transmission, the greatest one from the listeners' standpoint being the reduction of interference. The broadcasters might welcome it since greater efficiency is secured.

*Frederick Smith*

Editor of RADIO AGE.



Eveready's exclusive Layerbilt  
 construction *makes this*  
*the most economical of "B" batteries*

IMPROVEMENT on top of improvement has been the history of Eveready Radio Batteries. Here, in the radically different Eveready Layerbilt, is the "B" battery which tops them all. The ability of this battery to give you unrivaled service and economy is due to its unique internal design. Instead of the usual assembly of round cells, it is built of flat layers of current-producing materials pressed firmly together. This construction makes use of the spaces now wasted between the round-type cells and avoids the usual soldered wire connections. Eveready Layerbilt is every inch a

battery. This exclusive Eveready Battery development packs more active chemicals in a given space and enables them to produce more current and give longer life.

Tuesday night means Eveready Hour—9 P. M., Eastern Standard Time, through the following stations:

WEAF—New York	WTAM—Cleveland
WJAR—Providence	WWJ—Detroit
WEEI—Boston	WGN—Chicago
WTAG—Worcester	WOO—Davenport
WFI—Philadelphia	WCOO { Minneapolis
WGR—Buffalo	{ St. Paul
WCAR—Pittsburgh	KSD—St. Louis
WSAI—Cincinnati	WRC—Washington

**EVEREADY**  
**Radio Batteries**  
*—they last longer*

This HEAVY-DUTY EVEREADY LAYERBILT BATTERY gives twice the service of the smaller Light-Duty batteries and greatly reduces your "B" battery operating cost.

Use Eveready Layerbilts on any set, and get not only this extra service, but also—the greatest "B" power operating economy—the utmost in "B" power dependability—D. C. (direct current) in its purest form, so necessary for pure tone quality. There is an Eveready dealer nearby.

Manufactured and guaranteed by  
 NATIONAL CARBON CO., Inc.  
 New York San Francisco  
 Canadian National Carbon Co., Limited  
 Toronto, Ontario

# RADIO EDITORIALS

PROBABLY no other single comment on the radio situation has ever attracted the attention of so many citizens or produced as general a flurry of protest as did the recent assertion of Thomas A. Edison that radio is losing its popularity.

Mr. Edison, it will be remembered, also said that no radio dealers were making money, and that radio music was "terrible," or words to that general bitter effect, and that the people were going back to the phonograph.

One of the faults found with Mr. Edison's statement is that it lacked figures to confirm the sweeping survey he made of the industry. The United States Department of Commerce has just issued a report which does not at all agree with Mr. Edison.

More than ten times the number of tube-type radio receiving sets were manufactured in 1925 than in 1923 (the last preceding census), according to the government figures which give the production for 1925 as 2,180,622 sets—an increase of 1045 per cent over the 1923 output.

The production of radio speakers, 2,606,866 was more than four times that of 1923, when 623,146 radio speakers were produced, the census figures show. Five times the number of radio tubes were made in 1925, the report giving the value of the 23,934,658 tubes produced at \$20,437,283.

This stupendous increase in production of radio apparatus brought the 1925 figure up to \$170,390,572, more than three times that of 1923 when the total output was valued at \$54,000,470.

The Government's figures are more than confirmed by reports from the industry. For example, one man, the largest producer of radio receiving sets and radio speakers planned months ago, under the most expert estimates, that his production for this year should be double that of last year. Yet even this increase has not been sufficient to meet the rapidly increasing demand and it has been found neces-

sary to step up production still further to 5,200 sets a day, so that all orders may be filled.

The official figures made public by the Department of Commerce show an increase of 215 per cent in the value of radio equipment produced in the country in the past two years.

\* \* \*

PLANS are under consideration for a radio show for dealers and jobbers to be held in Chicago next June, or possibly later. The purpose of this exposition will be to afford the trade an early opportunity to see the season's new products and get an earlier start on distributions than has been possible heretofore.

One difficulty about such a plan is the apparent danger that manufacturers would be able to see the models displayed by their competitors at such a show and have time, as well as opportunity to readjust their own output to reproduce some of the excellent features which have been devised by their rivals.

To avert this possibility, the promoters of the early summer show are asking manufacturers to pledge themselves not to change their models before a certain date after the trade show. Several manufacturers with whom we have discussed the matter believe that the expense of preparing exhibits at such an early date would be so great that many manufacturers would be barred. It is probable, however, that the next few years will see the development of two classes of radio shows; one for the public and an earlier one for the jobbers and dealers who wish to get started on their way to distribution and sales before the Fall months.

It is argued by others that the early show would assist in destroying that annoying interval in which radio business is practically at a standstill, so far as sales are concerned. Anything that will administer a knockout to the well known summer slump would be welcome to the trade generally.

# RADIO AGE

## The Magazine of the Hour

M. B. Smith  
Business Manager

A Monthly Publication  
Devoted to Practical  
Radio

Frederick A. Smith  
Editor

## Start Your Radio Work With a Crystal Receiver

By ARMSTRONG PERRY

**R**ECEIVING radio entertainment is almost incredibly easy, yet four families out of five still are without the necessary apparatus.


Perhaps some are scared by the fact that the best receiving outfits on the market cost more money than the average family earns in a year. Even an ordinary five-tube broadcast receiver costs as much as the monthly incomes of many a man, and the money spent for upkeep would pay the milk bill.

But why should a family that is satisfied with a four-room apartment or a five-room bungalow wait for a radio set built for a millionaire's palace? Why not start with a crystal detector set? Let the neighbors talk if they want to—maybe their big set is not paid for!

The programs of any broadcasting station within five miles can be picked up easily with a crystal detector receiver, day or night. With an antenna well insulated at the points of support, and from thirty to sixty feet high, satisfactory results can be obtained up to twenty-five miles. So the bulk of our population is within easy reach of radio entertainment. Why not enjoy it? It's free!

Some folks pooh-poo the crystal detector because it is cheap and less powerful than a tube set. The user of the crystal detector

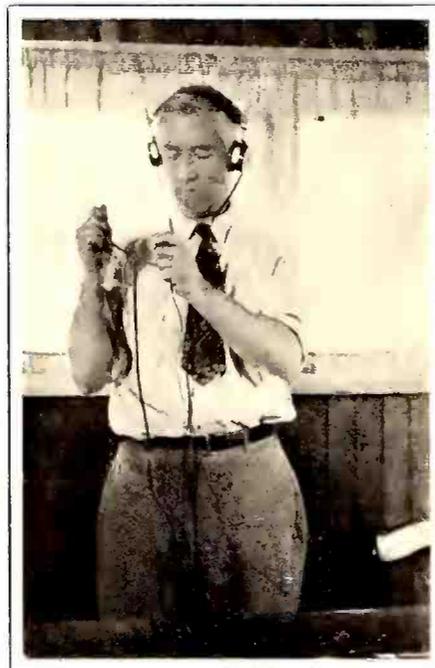can double-pooh-poo the average tube set because the quality of its music often is worse than that of



Hold the end of the aerial, and one phone cord tip, in one hand. In the other hand take the end of the ground wire and the other phone cord tip. You may be able to hear near-by stations without a detector as Armstrong Perry is doing in this picture

a fifteen-dollar phonograph, while the crystal detector never lowers the quality of the broadcast.


The crystal set is noiseless, except to those who are listening in with the phones. Loud speakers, on the other hand, are driving many involuntary listeners to dis-

traction. The owners of a New York building secured a permanent injunction against a neighboring restaurant whose loud speaker—a superlatively good one—made so much noise that it interfered with the work of employees of other concerns. The crystal set requires almost nothing for upkeep, while the tube set always is running up bills for batteries, tubes or electricity.

These arguments are not directed against the tube sets. Properly installed and operated, they are worth all they cost and more. It pays to buy the best one you can afford. But the man who sneers at a neighbor for installing a crystal detector set usually is the kind of a gink who does not know enough to operate any kind of a set. Don't let him keep you from enjoying radio.
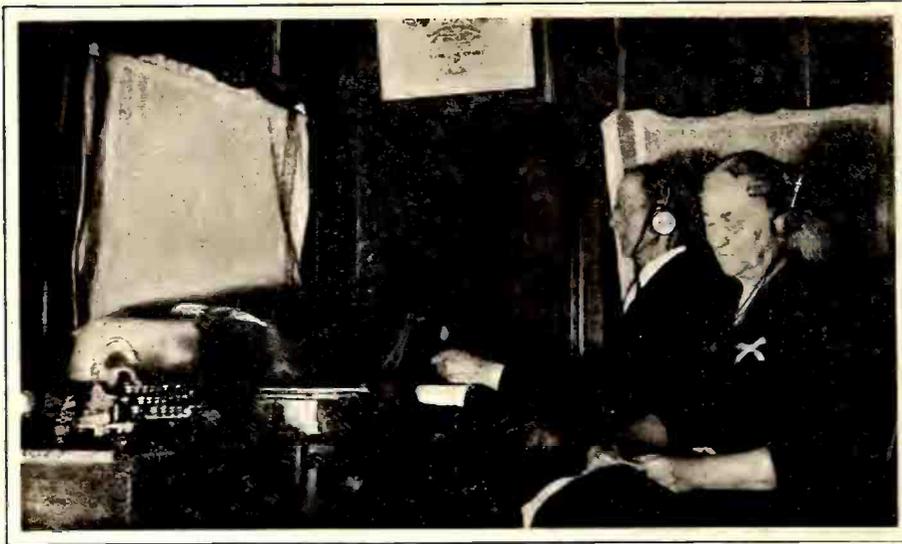
### Easy and Inexpensive

**F**EW persons realize how very easy and inexpensive it is to receive radio entertainment. Fasten one end of a wire to a branch high in a tree and bring the other end into your room. If it is bare, protect it so that the metal will touch nothing but insulators, which can be purchased for a few cents each. Fasten another piece of wire to a water pipe, first scraping the pipe and the wire to make them bright where they touch. Put a pair of phones on



Why deprive yourself of the joys of radio just because you cannot afford a set built for a millionaire's palace?

your head. Hold one tip of the phone cord in one hand, together with the end of the wire from the tree. Hold the other tip in the other hand, with the end of the wire that leads to the water pipe. The wires in the hand do not have to touch each other. If there is a broadcasting station near, you probably will hear what it is transmitting.

Now take a galena crystal such as is sold in radio shops and five-and-ten-cent stores for use in crystal detectors. Hold this in the left hand, between the thumb and fore finger. Do not touch the polished surface, or the oil from the skin may cover it so that it will not work. You have the wire from the water pipe, and the metal tip of the phone cord, in the palm of your hand held tightly by the last three fingers, and the crystal is between the thumb and first finger. The other tip of the phone cord is in the palm of the right hand, held by the last three fingers. Take the end of the wire that leads from the tree. Holding it between the thumb and first finger, touch it lightly to the polished surface of the crystal. You will hear the entertainment from the nearby station as loudly and distinctly as you can hear the voice of a friend on the telephone.

It may be too much trouble to climb a tree and put up an aerial wire. Never mind! For a dollar or less you can buy an an-

tenna plug that will fit into any electric light socket. There is a thumb screw on it to which you can attach a short length of wire to use instead of the wire in the tree. There is no danger of being shocked by the current. The plug lets only the radio waves through; the lighting current cannot pass, provided your wiring is not in conduit or BX. Holding the wire from the plug just as you would one from the tree, touch the crystal. The concert comes in perfectly, except as the hand may tremble and break the contact between wire and crystal.

The antenna plug is in two parts. One part screws into the socket, and there is only one way to put it in. The other has two prongs that go into holes in the screw plug. There are two ways to put that in, and either one may be correct. Usually there are two thumb screws to which the wire may be attached, one on each side. If you do not hear well with the wire on one, try the other. There are seven ways to use the plug, with one or two wires. Try them all.

#### The Arrester

**F**OR less than four dollars you can buy everything you need for hearing the radio entertainments. Having the essentials, including antenna or antenna plug, phones, crystal and a little wire, you can install them to suit your convenience. If you use an out-

side aerial, any permanent connection between the wire and the house must be made according to the regulations of fire insurance companies and city departments. There is little danger from lightning but there must be protection against it. In case the few dollars required for a lightning switch or arrester are not available, the wire can be brought in when the set is to be used and the end kept at a safe distance from the side of the house at all other times.

The first improvement is to rid yourself of the necessity for holding wires in your hands. This requires some device for keeping the crystal, wires and phones in contact. The crystal probably is embedded in metal; usually they are sold that way. Whether it is or not, it can be placed in a metal cup. Cups can be purchased, but it is easy to make one with a small piece of tin and a pair of shears. A thimble can be used, held open end up by nails or screws in a block of wood. If the crystal does not fit tightly, and if there are no set screws for holding it, pack it in with tinfoil, leaving the polished surface of the galena exposed. Most radio crystals are of galena, that mineral being the easiest to handle and most satisfactory in gen-



Wind the inductance coil on any round or square box having a diameter of about three inches



Attach a wire to a limb high up in a tree and bring the other end into the house

from the radio waves, is that all connections should be electrically tight. That means that wherever metal touches metal, the surfaces should be bright, free from oil or dirt, and soldered if possible. A little wood alcohol on a rag or brush quickly removes dirt. A piece of emery paper or a file will remove a corroded surface and cut down to bright metal. Connections should be made bright at the start and kept bright by frequent inspections and cleaning.

Another important principle is that all metal, from the aerial to the point where the ground wire connects with the set, should touch nothing outside the set that is a conductor of electricity. Where wood is used it should be perfectly dry.

Endless ingenuity has been exercised in designing devices for holding the crystal and the wires that connect it with other apparatus. Some assembled crystal detectors, supposedly dust proof, cost several dollars. Good little ones can be bought for fifty cents. A Boy Scout brought me one that he made himself for twenty-one cents. The galena rested on a paper clip and a safety pin served as a "cat whisker" to touch the crystal. It brought in stations that I could not hear with a twenty-five dollar outfit manufactured by the largest radio concern in the country.

One little trick that ship operators use is worth copying. Vibrations are likely to move the point of the "cat whisker" that rests on the crystal. Galena is not equally sensitive at all points, and it is necessary to have the contact as steady as possible. So a ship operator sometimes hangs his crystal detector up by a string where it can swing without bumping anything as the ship rolls and the engines shake her. Once adjusted, the "cat whisker" will stay in place indefinitely.


The limited range of the crystal detector frees the listener from most of the interference that troubles his neighbor with the high-power set. Women who can hear and repeat everything that is said around half a dozen

whist tables while they themselves are holding up their own end of a conversation will be actually lonesome with only three or four stations at most coming in at one time. But some folks cultivate a different attitude toward radio, and insist on tuning out all but one station if possible. It is easier to eliminate interference from a crystal detector set than from a tube set, because there is so much less of it to eliminate. Two things are necessary: an inductance coil and a condenser.

An inductance coil, or tuning coil, may be wound on an oatmeal box or any other round or square form having a diameter of about three inches. Bell wire, or smaller sizes of insulated wire are used, and the turns are wound as closely as they will lie. The number of turns depends upon the tuning range desired. The more turns, the longer the wavelengths that can be received.

To avoid studying technical details, a beginner may as well experiment. Start with a large number, say fifty to seventy-five. If the desired stations can be brought in loudly enough, the number of turns is practically correct. If not, cut off the turns one at a time until the desired result is obtained. Directions that are correct in theory for

(Please turn to page 63)

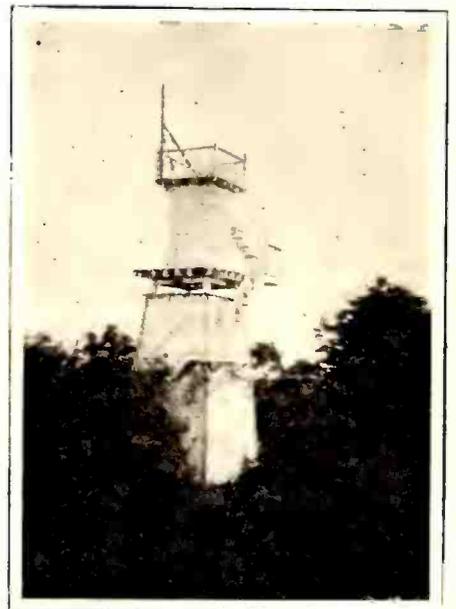

A water tank makes a convenient anchorage for the far end of the aerial, and a short mast will give additional height

### Make Tight Connections

ONE of the first principles, which many ignore with the result that they lose half the energy that they might pull in

# Difference Shown Between Baseboard and Chassis Construction

By H. MELCHIOR BISHOP

**P**RACTICALLY all amateur built radio sets, that is, about ninety per cent of them, are of baseboard construction. There are many reasons for this.

One reason is that the average designer in presenting his circuit to his readers, builds a set in this form and photographs it for the illustration of his article. This has many advantages. In the first place, every instrument is in the same horizontal plane, and by means of a plan or top view the general layout of the instruments can be clearly and unmistakably shown. Secondly, the same thing is true of the wiring. Thirdly, when the average human being has an instrument which must be fastened in a particular place, his "fancy lightly turns," so to speak, to a board. The board is the standard, everyday, utility fastening down place.

Although the baseboard method of construction is the one most commonly used by the novice when constructing his set, almost all manufacturers and a large proportion of the more advanced amateur experimenters use the panel mounting or chassis type of construction exclusively. This method consists, in general, of supporting all instruments by the panel itself, or by brackets and shelves fastened to the panel, and thus doing away entirely with the baseboard.

Let us see why this method, which offhand seems to be more complicated and difficult without in any way adding to the efficiency of the set, should be so universally adopted.

In the first place, we shall see, if we look further into the matter, that this chassis method of construction allows us to place our instruments in the most favorable positions for shortening the wiring without reducing the distance between these instruments to a point where unfavorable reactions in the form of feed-

back and conflation of magnetic fields takes place.

## Shortening Leads

**T**HIS is so, due to the fact that associated instruments may be placed in exactly the most suitable positions with respect to each other by merely supporting them by suitable brackets. For instance, a tube socket may be placed directly over its associated radio or audio frequency transformer, shortening the grid and plate leads to a fraction of an inch in length.

The second advantage of this type of construction is the greater ease of wiring it affords, due principally to the fact that the set can be reached from the bottom and sides as readily from the back.

This also means that in case of any trouble, the various component parts of the set will be much more accessible for examination and repair or replacement, as the case may be.

Thirdly, the chassis form of construction is much more rigid than is the baseboard type. Due to this greater rigidity, there is less chance for rough handling (especially the rigors of shipping) to cause breaks and defects in the wiring of the set.

The fourth advantage of the chassis built set is its greater compactness, which makes for a smaller and more portable set. This compactness is due chiefly to the fact that the instruments can be placed more advantageously in this form of set than in the baseboard type.

Fifth and last among the advantages of the chassis type of set is its appearance, which is far more neat and workmanlike than that of the baseboard mounted set.

In spite of the above mentioned numerous advantages of the chassis mounted set, there are certain cases where the baseboard set still is, and probably always will be, supreme.

## Fine For Testing

**F**IRST of these is the experimental set. In this type, to allow extreme flexibility, a large baseboard (often referred to as a bread board) is used and the various instruments are mounted thereon with wood screws. This breadboard set is very flexible in its general adaptability due to the fact that instruments may be moved or entirely replaced by others by the mere twist of a screwdriver.

Another use of the baseboard set which is closely akin to the above use is the temporary set. By this I mean a set which has passed the breadboard development stage, and is ready for a try-out of a month or so to test its efficiency. It is useless in a case of this kind to go to the trouble of designing a suitable chassis, and the old reliable baseboard will serve here with most admirable adequacy. It has, for this use, the added advantage of a certain ease in changing connections due to the instruments being all in one place, which is not afforded by the less flexible chassis built set.

Still another use of the baseboard set is the one which is mentioned near the beginning of this article—that of the illustrative set. Its use here is due chiefly to the clearness and openness of this type of construction, which lends itself admirably to clear photographing, and is in addition easily built.

To summarize, it has been shown by the preceding exposition that the baseboard type of set construction is best and handiest for the more temporary and experimental type of sets. On the other hand, for a permanent and workmanlike receiver, the chassis type of construction is king, and rightly so, due to its greater rigidity, strength, neatness, and general efficiency due to short wiring and advantageous instrument placing.



power supply. Just how the double wave feature and the remote control of the transmitter were accomplished will be outlined below. The photographs show the rough layout of the original set which gave excellent results, and the circuit diagram shows all of the connections in detail.

A five-pole, double-throw switch was secured for use in changing from one wave band to another. This was hooked up as shown, as can readily be seen, changing the position of the switch, throws one or the other of the two tuning units into the circuit. As shown, this installation calls for three variable condensers and two sets of tuning inductance. If it is impossible to tune the antenna circuit to resonance on one of the required working wave lengths, a fourth variable condenser will be necessary. This is to be connected in series with the antenna coil of the circuit where no condenser is shown. This is only one possibility. The other is that the wire wave antenna circuit may not be large enough, and therefore, a parallel antenna tuning condenser will be necessary. This, however, will be determined by the characteristics of your antenna and counterpoise system.

### Two Highest Bands

**T**UNING units used in transmitters are too well known to merit discussion here. The writer used some old inductances that happened to be on hand and had no trouble at all. His set, as shown, has been made to work on the 40, 80 or 150 to 200 meter bands. Obviously only two of these can be used interchangeably, and when the third is required one of the circuits must be re-tuned. The set is now in operation on the 80 and 150 to 200 meter bands.

Practically all of the apparatus used in this circuit is standard. "S" tubes are used for rectification, while a "brute force" filter insures a perfect DC note, and also gives an oscillatory current that is suitable for phone modulation. There are a good many amateurs who

have to resort to remote controlling of transmitters in order to get the best of results, and the writer is one of them. The problem of installing phone modulation in remote controlling is a serious one unless the amateur happens to be wealthy enough to install the Heising method which, of course, lends itself admirably to remote control.

There are three other systems of modulation that are available for the average poorly financed ham. One of them is merely a modification or refinement of one of the others. The first that we will consider is the old stand-by, the loop system. The writer used this very satisfactorily with 30 foot leads between the loop and the microphone when operating on 180 meters. For 85 meter work, however, this system is not practical, probably because of the long leads. The other main system is the placement of the microphone in the center tap lead from the inductance to the filament circuit. Here again, the long leads are quite satisfactory for 180 meter phone transmission, but on 85 meter work the long leads give trouble. Therefore, the system shown in the diagram was worked out with the aid of 2 QS, and it proved quite satisfactory. True, it requires a little more apparatus, but still is not as expensive as the Heising system, and has practically no upkeep other than the battery. This method consists of placing the microphone in the center tap lead just as described above, but having the microphone located at the transmitter instead of at the control end. Placed up against this microphone, and strapped to it with ordinary friction tape, is a low resistance telephone receiver. This, in turn, is connected through an ordinary telephone repeating coil, to a microphone and battery. Speaking into the microphone causes the diaphragm of the receiver to vibrate, and this action vibrates the diaphragm of the microphone in the center tap circuit.

A further refinement can be added in the form of a relay

which short circuits the actual transmitting microphone when the circuit of the other microphone is opened. This allows the use of CW transmission at all times without any further operation than the opening of the microphone switch.

### Controls Near Operator

**A**S will be noted in the diagram, the power supply rectifier, filter and key are located at the control end. A milli-ammeter is also placed near the operator so that a constant check may be kept on the operation of the set. A second ammeter placed with the transmitting apparatus is of inestimable assistance when tuning the transmitter.

The antenna system the writer used for working on two waves will undoubtedly be of interest. When one of the oscillatory circuits was tuned to operation on 40 meters, the antenna circuit was tuned to its third harmonic and excellent results were obtained. For 80 meter work, the antenna circuit was tuned in the usual manner with a series condenser. For operation on the 150 to 200 meter band, the pick-up coil in the antenna circuit was connected in series with the loading coil in order to boost the wave length of the antenna circuit. If a comparatively large pick-up coil is employed, it can be shunted by a variable condenser, and the antenna circuit can be tuned to the required high wave. However, about the best results obtained were observed when only a small loading coil was used, and this was shunted by a tuning condenser. This is to be preferred to the placement of the tuning condenser in parallel with the pick-up coil itself.

The above description and the photographs and diagram should give some hams a few good ideas for the remodelling of their transmitters. The apparatus shown in the photographs should not be taken as a criterion, however, as it was merely assembled in order to test the efficiency of the remote control modulation methods, and the practicability of the two wave transmitter.

# Death Ray Tube Turns Gases Into Solids

**A** VACUUM tube which produces as many electrons per second as a ton of radium—and there is only a pound of that rare substance in the world—was announced by Dr. W. D. Coolidge of the research laboratory of the General Electric Company at a meeting of the Franklin Institute of Philadelphia, on the occasion of the award to him of the Howard N. Potts gold medal of the Institute for his outstanding work in the development of x-ray tubes.

Radium is constantly disintegrating, and in so doing is bombarding electrons—infinitely small particles of matter or electricity—into space at very high velocities. The rate at which radium disintegrates is beyond human control; nothing that man can do seems to affect the rate at which the element breaks down. The cathode ray tube likewise bombards high speed electrons into space, but at a rate that can be controlled by man, and in quantities far greater than by all the radium in the world. The electrons given off by radium are of higher average velocity than those so far produced with the cathode ray tube, but otherwise the two are alike.

So much more concentrated are the rays from the tube that many startling experiments have been conducted with the new device. Crystals of the mineral calcite apparently become red hot coals when exposed for a moment to the rays, but they are glowing with cold light; ordinary salt is turned brown, and considerable time elapses before it again becomes the colorless substance it usually is; bacteria and small flies are almost instantly killed by exposure to the rays; ordinarily colorless acetylene gas is transformed into a yellow solid which cannot be dissolved; and a rabbit's gray hair has been destroyed, to be replaced later by a

## *Vacuum Tube Produces More Electrons Than Radium*

profuse growth of longer, snow-white hair.

Cathode rays have been known to some extent for many years. At first, however, they were known only within vacuum tubes, but about 30 years ago a European scientist, Lenard, succeeded in making the electrons pass through a tiny piece of extremely thin aluminum foil cemented to the glass wall of the tube. Im-

provements have been numerous since then, but with previous tubes the metal "windows" were much smaller and the operating voltages much lower than with the new tube.

### **Unusual Features**

**S**EVERAL unusual features have been incorporated in the new tube. There is a "window" three inches in diameter, of nickel foil the thickness of which is measured in thousandths of an inch and which is capable of withstanding a total atmospheric pressure of more than 100 pounds. A heated tungsten fila-




Dr. W. D. Coolidge, famous X-ray tube scientist, is given the Potts medal of the Franklin Institute for work on new wonder electron producer

ment, originally used by Dr. Coolidge in the x-ray tube and now known to all as an essential part of radio tubes, furnishes the supply of electrons. The glass tube has been shielded with a copper tube so that the stream of electrons cannot strike the glass and cause punctures, thereby permitting operation of the tube at voltages far higher than any previously attained, and the tube is also the first which it has been possible to seal off from an evacuating system; the tube thereby has been made as portable and as easy to use as an x-ray tube.

Electrons are released by the heated tungsten filament, or cathode, at relatively low velocity—a matter of a mile or two per second. Between the cathode and the anode—the “window” and the copper tube which serves as a shield—there is impressed upwards to 350,000 volts of direct current. This causes the electrons given off by the filament to speed up to an average velocity

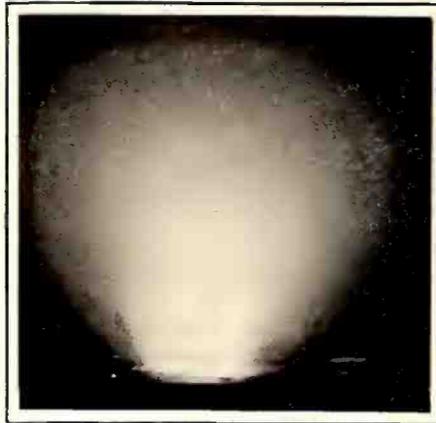of 150,000 miles per second or more, depending upon the voltage, within the short space of about one inch between the cathode and the copper tube shield. Having attained this high velocity, the electrons coast the rest




This photograph shows ball of purplish glow surrounding window of tube

of the way through the highly evacuated tube and pass through the anode, or window and into the atmosphere with but slight diminution in velocity.

The nickel window is soldered to a disk of invar, an alloy which expands the same amount as does glass when heated. The invar disk, in turn, is fused to the glass tube, thereby making the seal air tight. The thin piece of nickel itself could not withstand the atmospheric pressure of 100 pounds—the difference between the outside air and the almost perfect vacuum within the tube—so it is reinforced with a honeycomb structure of molybdenum metal, a design that affords a maximum of strength with a minimum of cross-section area.

If the tube is operated in a darkened room, a hum is heard and the window of the tube is seen to be surrounded by a ball of purplish haze, about two feet in diameter with 350,000 volts and more or less depending upon the voltage. This glow, which shows the penetration of the cathode rays in air, results from the air being ionized or broken up by the

(Please turn to page 46)

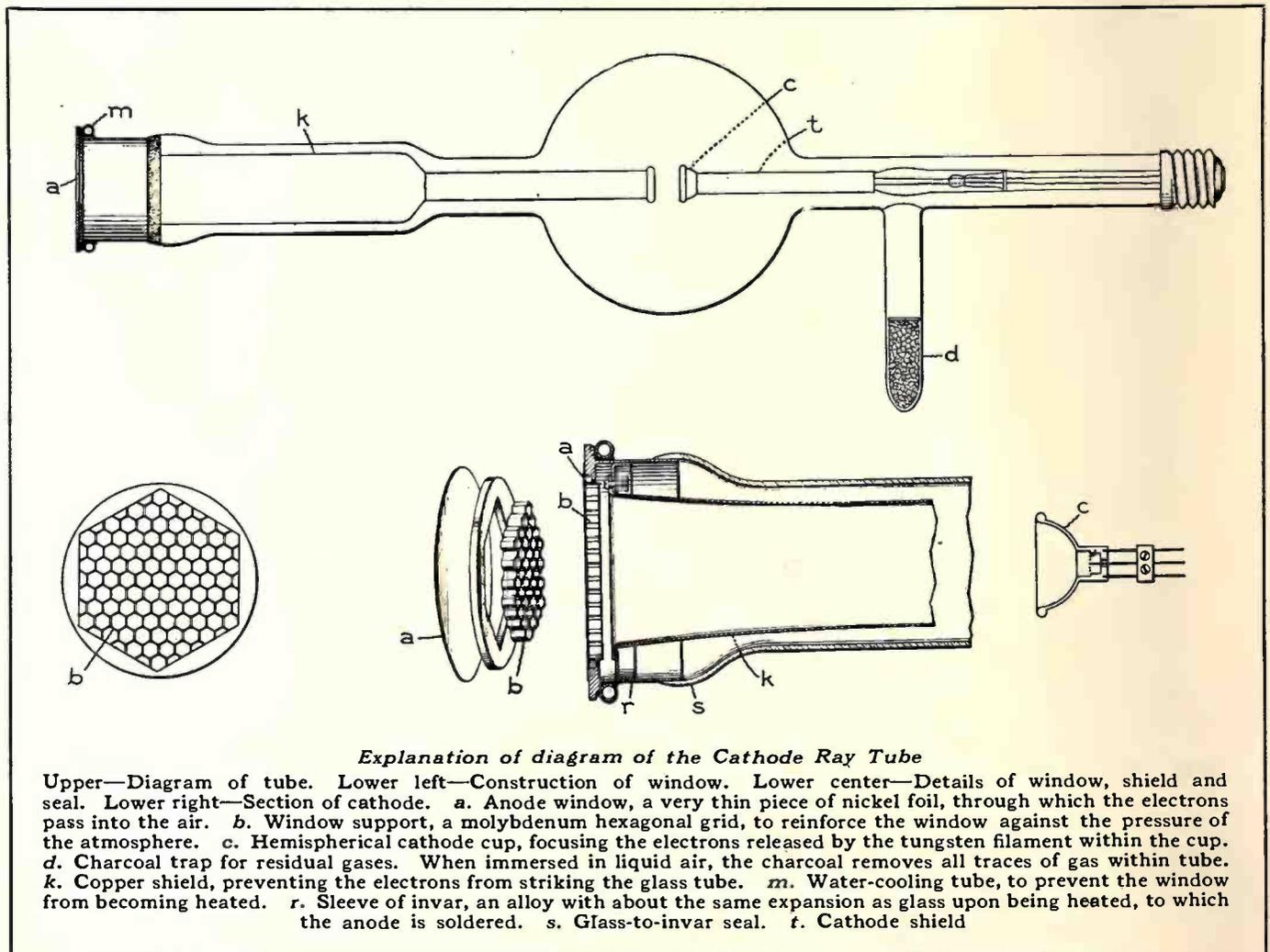

Explanation of diagram of the Cathode Ray Tube

Upper—Diagram of tube. Lower left—Construction of window. Lower center—Details of window, shield and seal. Lower right—Section of cathode. *a.* Anode window, a very thin piece of nickel foil, through which the electrons pass into the air. *b.* Window support, a molybdenum hexagonal grid, to reinforce the window against the pressure of the atmosphere. *c.* Hemispherical cathode cup, focusing the electrons released by the tungsten filament within the cup. *d.* Charcoal trap for residual gases. When immersed in liquid air, the charcoal removes all traces of gas within tube. *k.* Copper shield, preventing the electrons from striking the glass tube. *m.* Water-cooling tube, to prevent the window from becoming heated. *r.* Sleeve of invar, an alloy with about the same expansion as glass upon being heated, to which the anode is soldered. *s.* Glass-to-invar seal. *t.* Cathode shield

# High Lights on Wavelengths and Frequencies Used

By KIRK B. MORCROSS

**L**IKE the story of the empty bucket, there being nothing in it, the subject of wavelengths and frequencies may not strike a responsive cord of interest in many of us. Why should we care about these apparently non-essential things in the background of the varied and colorful field of radio? We admit of course that meters, representing wavelengths, and kilocycles, representing frequencies, or rather, meters, or kilocycles are a necessary evil incident to the performance of the radio drama but after this fact has become ensconced in our minds why worry any more about the matter? The wavelength is there or the frequency if you prefer, and that settles it. Radio will go forward just as well without our delving further into the idiosyncrasies of these phenomena.

But after all, are wavelengths and frequencies in the background; can we be content without giving them a little "worry" and will the art of radio go forward just as well without some study on our part of these terms? The answer to these questions is decidedly in the negative. You probably don't agree with this now, but wait, and I will try to convince you. If I fail then you will have the satisfaction of knowing I am mistaken; if I succeed, why then, we are all going to receive some benefit.

First of all we will admit that waves are in the background, very much so. But what is a background? The dictionary defines it as a "subordinate position" or "that part of a picture behind the principal objects." Radio is a panoramic picture and in the background of that picture, giving it depth, setting and naturalness come wavelengths and frequencies. But here is something that must be proved. Let us do so.

The very earliest investigators


of electromagnetic waves measured the lengths of those waves. It was an important and natural thing to do in order to further the progress of the art. Investigations in those pristine days of radio were marked by attempts to make better wavemeters. The old spark transmitting sets employed highly damped waves which required a measurement of decrement to determine the "spread" of the waves. The instrument used was a "decrementer" which was also a wavemeter. As the number of radio stations increased the measurement of their wavelengths became a matter of prime importance. The more stations the more interference and the more interference, the more necessary it was to measure wavelengths accurately.

So down through the corridors of radio progress have come wavelengths and at the dawn of broadcasting we recall that broadcasting stations were assigned waves in two bands, 360 and 400 meters. Then as the need of space in ether became acute a great many bands were made available for broadcasting. The 360-and 400-meter bands

corresponded to 833 and 750 kilocycles.
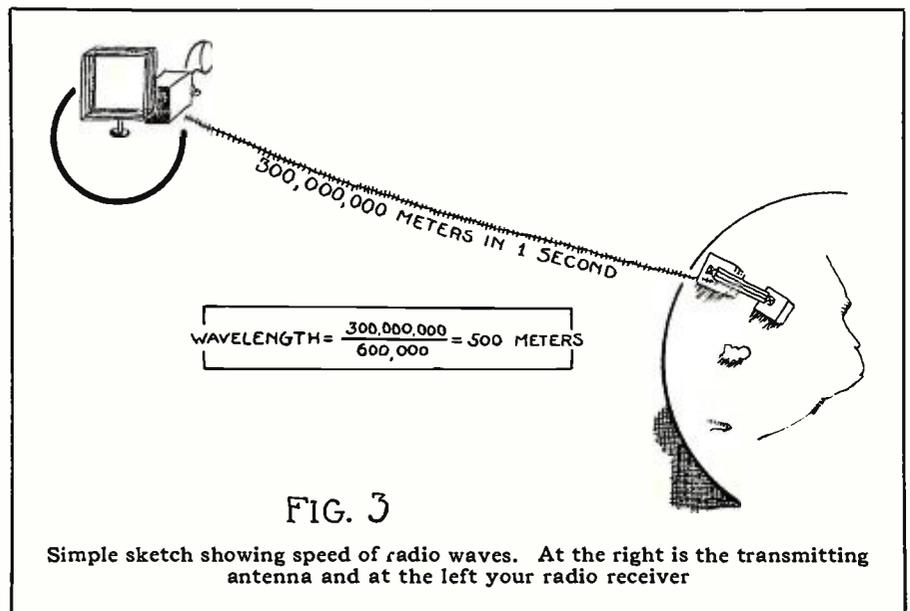
## Multiples of Ten

**G**RADUALLY the 833-kilocycle stations were allocated to other bands and at the present time the majority of broadcasting stations are assigned frequencies in kilocycles which are all even multiples of ten. Right here we begin to get suspicious that something is the matter with wavelengths else why this changing of the designations to kilocycles? Thereby hangs a tale which, incidentally, will occupy a deal of space in this article—later. Unfortunately Congress has failed to pass legislation giving the necessary authority to the Secretary of Commerce to specify frequencies to be used by broadcasting stations and a recent ruling of Attorney General Sargent disclosed that a station may legally select its own frequency. As a result, some stations have reverted to the 833-kilocycle wave while other stations have chosen some other frequencies which are not multiples of ten. That this may result in serious inter-



ference will be understood by a later explanation in this article. It is hoped that the next session of Congress will see the enactment of an authoritative radio law which among other things will ensure the use of proper kilocycle values by broadcasting stations.

We see that wavelengths and frequencies are in the background of radio sure enough but what an important background it is! A little "worrying" about them is certainly going to be worth while especially when it is mentioned that by so doing a little bit of the subject is going to be carved out of that background and placed right in the broadcasting stations and the receiving set. This discussion includes the experimenter, the amateur and the broadcast listener alike and without these members of the radio fraternity where would radio be today? Certainly if it can be shown that this subject is worth while to those people we are safe in saying that radio is going forward.

### Tuning Fork Simile

CONSIDER a tuning fork—the kind we used in physics laboratory—which has, say, a period of vibration of 500 times per second. That may be a little too fast for easy comprehension and yet some sort of idea of it may be obtained by imagining a frequency of 10 vibrations per second and gradually increasing the number. One of these complete vibrations of the tuning fork is represented by the "still movie" in Figure 1. At A the fork is struck and bends to the

left; at B it passes through its normal position and then springs to the right as at C; at D it again passes through the normal position and then comes to E, the position from which it started. The fork has made one complete vibration in one five-hundredth of a second. Of course other vibrations follow and as each one is completed an air wave is sent out. These striking the ear drum 500 times each second, produce a musical note of rather high pitch. (No, I am not going to take up the old, old controversy of whether or not that sound is there when you don't hear it!)

Now sound travels, in ordinary air at the rate of 1090 feet per second, for simplicity let us say 1100 feet. Place yourself at that distance from the fork and have some one hit it with a hammer (see Fig. 2). One second later the first air wave will strike your ear. In the meantime 500 waves have been sent out and they are evenly distributed over the intervening space. The distance between these waves (in other words, their wavelength) is  $\frac{1100}{500} = 2.2$  feet.

The simple explanation just given may be a little removed from radio; nevertheless it leads naturally to a consideration of what transpires in the antenna of a broadcast station. Consider such an antenna as shown in Figure 3. Let us assume that this antenna is so tuned that the alternating currents set up in it have a frequency of 600,000 cycles per second. Try to count them! At any rate that frequency is in the broadcast band and be-


fore proceeding further let us thoroughly understand the meaning of one cycle making up this frequency.

Beginning with a zero valve the current flows through the antenna circuit in one direction, then reverses and flows through the circuit in the opposite direction. This completes one cycle. Note the analogy to the tuning fork explanation. This all takes place in one six-hundred-thousandth of a second; 600,000 complete reversals of the current occur each second. This phenomena occurs right in the antenna of the broadcasting station because the antenna has capacity to earth and this forms a complete path for radio currents just as a loop of copper wire forms a complete circuit for a direct current. (This explanation concerns the carrier frequency of the broadcasting station; the effect of modulation can be neglected).

As each cycle is completed in the antenna a wave is shot out into space. Again, as in the case of the tuning fork place yourself at a distance. This time you will have to make it 300,000,000 meters or about 186,000 miles in order that we may follow out the analogy. Hence equip yourself with a receiving set out in space and see what happens. In just one second after the first cycle of current is completed in the antenna the first wave reaches your set. But during that time 600,000 waves will have been sent out and filling the intervening space, they will each be separated by a distance of  $\frac{300,000,000}{600,000} = 500$  meters. Hence the wavelength of the broadcasting station is 500 meters.
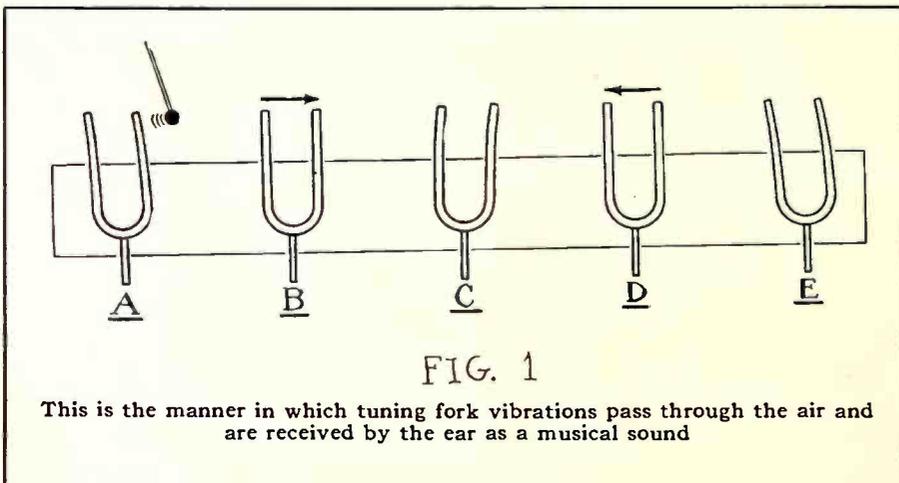
### Speed of Radio Waves

WE CANNOT carry this comparison with the tuning fork too far. The waves from the fork travel very slowly—by comparison; they travel through air, not ether. The speed of the radio waves and likewise their frequency are entirely beyond comprehension. Parenthetically it may be mentioned that recent theories indicate that "ether" and "ether waves" are nonenti-



ties but that does not concern us here.

We have seen that dividing the velocity of radio waves in meters per second by the cycles per second gives the frequency. To save space and ink, frequency is expressed in kilocycles per second where each kilocycle represents one thousand cycles. Thus to obtain meters we divide 300,000 by the known number of kilocycles, or to obtain kilocycles we divide 300,000 by meters. The letter "f" is understood to mean frequency in kilocycles per second while the Greek letter  $\lambda$  (lambda) means wavelength in meters. For greater accuracy in computation the number 299,820 replaces 300,000.

You may become thoroughly up to date on this wavelength-frequency conversion business by investing the small sum of five cents. Send this amount to the Superintendent of Documents, Government Printing Office, Washington, D. C. and ask for "Miscellaneous Publications of the Bureau of Standards No. 67" and you will receive a large chart giving accurate conversions at a glance.

Have you noticed how of late the lists of broadcasting stations in newspapers and magazines are designating those stations in kilocycles as well as meters? The reason for this is, simply told, due to convenience. The distrib-

ution of broadcasting stations in the ether is determined fundamentally by kilocycles and as long as the kilocycle designations are all even multiples of ten it is an easy matter to learn the various frequency assignments.

Broadcasting stations were originally designated in meters and so it is not easy for us to become accustomed to kilocycles. We naturally agree that kilocycle designations represent a greatly simplified plan as compared to specifying stations in meters employing numbers which are generally expressed in decimals and which appear to have no special relationship whatever. Quite naturally the question arises: Why not assign wavelengths which are even multiples of ten? Such a procedure would be practical but the results would be ridiculous because while the ten-meter separation of the long wave broadcasting stations would be about right to prevent undue interference, that separation would be far more than necessary to prevent interference between the shorter wave stations. Result: a lot of waste space in the ether.

Very good so far, but what are the underlying reasons for the greater adaptability of kilocycles? They are two in number and they both relate to the carrier waves or frequencies radiated by broadcasting stations.

It has been found that these carrier frequencies may have a certain minimum separation without undue interference and that this separation is the same regardless of the corresponding wavelengths. This required separation is determined by the width of side bands and by the beats produced between carrier frequencies.

Side bands are frequencies due to the modulation of the carrier which are somewhat higher or lower than the carrier frequency. Side bands normally occupy a space about five kilocycles each side of the carrier frequency. Thus we see that a broadcasting station requires more than a narrow streak through the ether. (Remember this fact when considering the adoption of a sharply tuned circuit: some of the side bands may be cut off and away goes the quality of received music). Since side bands extend out approximately five kilocycles each side of the carrier frequency a group of broadcasting stations spaced ten kilocycles apart must be very accurately fitted into the ether. It must not be assumed however, that these side bands always occupy this amount of space; they swell and shrink according to the modulation at the broadcasting station. Interference may occur between broadcasting stations even though a

(Please turn to page 60)

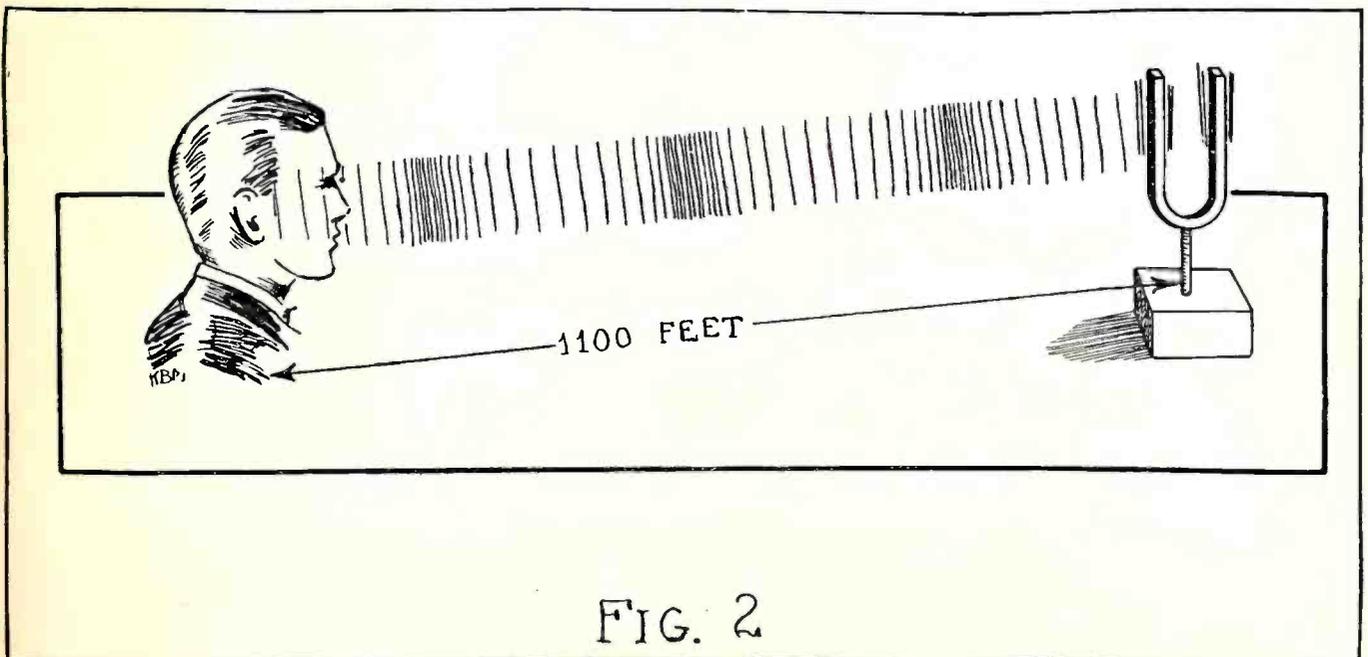


FIG. 2

# Turning Soprano to Contralto is Feat of Single Side Band Set

By I. J. KARR\*

**R**ADIO broadcast signals whittled down to a single side band are now being put on the air by the newly developed transmitter at the South Schenectady laboratory of the General Electric Company. The usual signal consists of two side bands and a carrier. In the newly developed radio transmission system the carrier is eliminated and one side band is suppressed.

The single side-band system is used on license 2XAH and operates on 1400 meters. Programs of WGY have been broadcast on the higher wavelength and the stripped signal has been received by station WCAD of St. Lawrence University, Canton, N. Y., and rebroadcast on that station's wavelength.

There are three advantages fairly definitely established in the new system. First, it increases efficiency. The ordinary radio signal considered in three parts, consists of the energy at the carrier frequency, energy distributed in the frequency band extending from the carrier upward and energy in a band extending from the carrier downward. The power of the carrier frequency alone, makes up somewhat more than half of the total power even when the modulation is as complete as possible. With the same amount of power in the transmitter twice the signal strength may be obtained.

The second advantage of single-side-band transmission is a decrease in interference. A narrower frequency band from the transmitter permits the use of more selective circuits at the receiving end. This reduces the exposure to noise thus improving the signal-to-noise ratio.

Another and third advantage is the smaller frequency band, thereby conserving the available range for other radio transmission.

Audible sounds by which broadcast material is classified consist of frequencies, or complex wave forms whose frequencies lie between about 30 and 15,000 cycles per second. Such frequencies when converted into electrical impulses, could not be radiated efficiently from an antenna so modulation is necessary. In other words, the low audio frequencies are combined with a higher frequency so the resultant may be radiated.

## Frequency Combination

**W**HEN two frequencies are combined by a vacuum tube a very interesting phenomenon takes place. If a radio frequency carrier of frequency R cycles per second is modulated with a second frequency of A cycles per second, there will be four frequencies present in the resultant. These will be R, A, R plus A, and R minus A. The R plus A frequency is known as the "upper side-band" and R minus A, as the "lower side-band." It should be noted that any of these frequencies may be discriminated against or entirely eliminated by suitable means. The audio frequency seldom appears to any appreciable extent in the output, its frequency being so far removed from the tuned frequency of the output circuit. Thus, there are three frequencies present in the output of the conventional transmitter. These are: R, the "carrier" frequency, R plus A, the "upper side-band" frequency and R minus A, the "lower side-band" frequency.

In a conventional receiver these same frequencies appear and from them the original audio frequency A is reproduced by the phenomenon of modulation. The lower side-band" may be caused to combine again or "uncombine" thus giving back the original A frequency. Similarly the "upper side-band" gives back the audio frequency.

These two components add to give the reproduced signal.

It is practically impossible to build a single transmitter or receiver to accommodate the band of audible frequencies between 30 and 15,000 cycles and the engineer is pleased if his transmitter handles the band from 30 to 7000 cycles. Incidentally, this band would give excellent quality.

To illustrate the preceding explanation, suppose a carrier of 1000 kilocycles is produced and modulated by the audio band reaching from 30 to 7000 cycles. For every audio frequency there will be two resulting frequencies and these will divide into two bands, the "carrier plus" band and the "carrier minus" band. Specifically, the "lower side-band" will reach from 993 kilocycles to 999.97 kilocycles. The "upper side-band" will lie between 1000.03 kilocycles, and 1007 kilocycles. These questions may now be asked: Since the carrier beating with the frequencies held in either side-band will give the original audio back again at the receiver, why is it necessary to radiate both side bands? Also, why not supply the carrier itself at the receiver and avoid the waste of energy from the transmitter which lies in the carrier? The "single side-band" system is based on these principles.

Since no carrier is transmitted, it is essential that one be supplied at the receiver. In the case of the example above, if the "lower side-band" is radiated, 993 to 999.97 kilocycles, and a receiver heterodyne frequency of 1000 kilocycles is supplied then the original 30 to 7000 cycle band is reproduced.

## Change Singer's Voice

**A** VERY interesting phenomenon is observed in receiving single side-band signals. If the receiver heterodyne frequency is

(Please turn to page 58)

\*Radio Engineer, General Electric Co.

# What Do We Get From Boston?

By DOROTHY BRISTER STAFFORD

**I**F we are to believe the reiterated statement dinned into our ears nightly by a multitude of radio entertainers last winter, it is "Beans, Beans, Beans," but those of us who think of Boston as "WBZ, Springfield," or "WBZ, New England," know that we are indebted to the home of the Cabots and the cod for vastly more than the succulent Saturday night supper dish.

When we first went adventuring in radio, and found that one of the oldest of the Westinghouse stations reared its antennæ in the environs of the historic seat of culture and tradition, we expected to be completely overwhelmed by Harvard accents and heavy programs of intensive education. We were agreeably surprised to find that while naturally the New England station was strong on its educational features, —as it should be, with almost unlimited material to draw upon,—there was a versatility in its broadcasts that ranged all the way from University extension lectures to snappy dance programs and hockey games. A couple of years ago—when radio was radio—and not a bedlam of heterodyning howls as this winter, we were in the habit of tuning to WBZ nightly, and usually were rewarded by some excellent feature just a little different from what was coming out of the general run of stations, such as the Nature League talks by Thornton W. Burgess (the Peter Rabbit man), or the singing McEnelleys, in those days a decided novelty. But last winter, much to our chagrin, it seemed that every time we set forth intent upon hearing some distinguished speaker from the New England station we wound up with a real estate ballyhoo down in Jacksonville. It is with much satisfaction we note this winter that right seems to be going to triumph over might, and WBZ get back in its proper place upon our dials.

Those of us who are wont to regard radio as an entertainment

proposition pure and simple, are a little inclined to discount the value of the many educational features that pour forth upon the air nightly, and when we do run across them, listen vaguely for a moment or two and then go on to something requiring less concentration, possibly wondering if anyone does take the trouble to seriously follow the elaborate courses prepared for their enlightenment. On its face it seems a marvelous opportunity for the thousands who have been denied the benefits of higher education. Ordinarily one might wax exceedingly eloquent over the blessings of radio as a disseminator of knowledge, were it not for the fact that from the testimony of many a broadcaster, we had almost arrived at the conclusion that the radio audience is not only not thirsting for enlightenment, but is decidedly unappreciative of the efforts of earnest program directors to give it anything above the most ordinary run of entertainment. After all the tumult and the shouting about the betterment of radio, and the wonderful programs that have been coming to us this winter, it is rather discouraging to have to accept the

assertion of many a sponsor of high-class entertainment that the general public is not interested in the better class of programs. These purveyors of good music and the like, of course have to gauge the results they are obtaining from the written responses they receive, and one wonders if possibly there aren't many thousands of listeners who do enjoy and appreciate the programs, but are not the kind of people who would think of writing a letter about it. And in the early days of broadcasting it is true that there were many who had unpleasant experiences from attempting to express their appreciation of something fostered by concerns with the wrong idea of radio publicity. We personally know of one case, where the name obtained from the listener's cordial little note, apparently was placed upon what is known in advertising parlance as a "sucker-list," and after his mail had been cluttered up for several weeks with all sorts of advertising matter, this listener naturally lost his original enthusiasm for radio entertainment. But we scarcely believe that such a condition could exist today even in regard



Leo Reisman and his Hotel Brunswick Orchestra broadcast by WBZ



Prof. Robert Emmons Rogers of M. I. T. who broadcasts courses in literature from WBZ

to publicity programs. We had just worked out this little argument to refute the theory of a program director friend of ours that we of the radio audience are dead from the neck up, when we happened upon an instance in our own immediate circle that almost led us to believe he was right, and that the yearning for culture was just what he called it—"a lot of bunk."

We drifted into a home where one always hears a lot about the finer things in music and art—in fact the hostess prides herself upon her patronage of the symphony, her frequent trips to the metropolis in the opera season and a general disdain for anything proletarian. To our astonishment the house was filled with the raucous yowlings of a station, which we, broadminded though we are, have long considered impossible.

"Good gracious, Ann," we said, "why are you listening to that trash? The Philharmonic is coming in splendidly tonight." Our friend was quick on the retort.

"It's the children's night to stay up," she said. "And they don't understand the better music."

At this moment a leather-lunged quartette broke the tension with a stirring rendition of "Keep Your Skirts Down, Mary Ann."

"Do you mean to say they understand that?" we asked her.

The fact was that the two

small boys, absorbed in some important children's business, weren't paying the slightest attention to the radio, while their pedantic mother was, for once in her life, indulging her inhibitions and listening to the sort of thing she really liked. Since then we have had a good deal of respect for the broadcasters who, probably without a great deal of encouragement, continue to give us the best there is to be had in the way of entertainment and instruction.

Which dissertation on the seeming ingratitude of that portion of the radio audience which should know better brings us to



Prof. William C. Monohan, Massachusetts Agricultural College, conducts farm courses over WBZ

the pleasing counter testimony of WBZ, as to the returns from the educational features, which form a prominent part of this station's programs. For, as you probably know, WBZ was the pioneer in broadcasting educational courses, the first experiments being conducted as far back as 1923. Prior to that time Columbia had put out a course in Browning, the theory being, as one of WBZ's instructors phrased it, "if radio listeners could stand Browning they could stand anything." The Springfield station seriously took up the business of dispensing knowledge in the Fall of '24 with courses in Contemporary American Literature, Conversational French and Appreciation of Music. The lectures were presented by instructors of recognized prestige, and

that these representative teachers might know if their efforts were being wasted upon desert air, the unique experiment of asking those taking the courses to pay an enrollment fee of one dollar was launched, with the surprising result that more than 2,500 enrolled the first season. This proved that there were quite a number of people, who not only were willing to listen to educational radio, but were willing to pay for it. An interesting angle is that these listeners were not confined to stern New England, where one might expect to find a serious-minded audience, but represented all parts of this country and Canada.

Professor Robert E. Rogers of the Massachusetts Institute of Technology, who gave the experimental course in Literature, has collected many interesting statistics from the letters which came to him that first winter from listeners in far distant sections—many with a wistful touch—but all teeming with appreciation of the opportunity afforded those who are privileged in no other way to hear the things, that, to quote the instructor, "they have at some time been accustomed to and lost, or have always thirsted for and never attained." Extracts such as the following from letters that came in countless numbers convinced those sponsoring the programs that they were engaged in something quite worth while.

This was from a small town in North Carolina:



James E. Murley, sports announcer and press representative of station WBZ

"This is my first opportunity to attend college lectures anywhere, much less in historic Boston. I feel like saying Thank God for radio."

Another wrote:

"This town is forty miles from a public library, but I am going to try so hard to get the books you suggest."

All the way from Georgia came this sincere tribute:

"This course is of estimable value to students living in villages far removed from those things which make life worth while to them, and for me, literally starving for such, it is a God-sent message."

The letter that contributed most to Professor Rogers' happiness was written from an R. F. D. route in Ohio, and he calls it "a real Iliad of the fight of an American family not merely to exist, but to keep alive mentally." An extract runs:

"Until Cousin Frank bought us our radio we had not heard a lecture for twelve years, nor a good play since the first few months of our marriage when we went to Chicago and saw *The Garden of Allah*, and *Maude Adams* and *Sothorn* and *Marlowe*. Now we have orchestras and organ recitals every evening. I want to enroll in your course and I hope I can complete it. It is such a fine, generous offer for folks like me who can't get away from home."

Thousands more enrolled last winter and the season of 1926 finds WBZ with its educational broadcasts as an established feature, with standard courses ranging all the way from French and Agricultural subjects to Applied Psychology. Since its inauguration in Boston, educational radio has spread in the past two years to every part of the country, the excellent intensive courses provided by several western universities being too well known to require further comment.

The most important addition to WBZ's varied activities this winter is the complete series of the Boston Symphony Orchestra concerts, which are being put on the air in their entirety for the first time. The real music lovers of the country are overjoyed at the

opportunity of hearing this great organization, and together with the Victor and Brunswick programs which comes from WJZ, the Boston station is well supplied with music of the highest class.

To the dancing element of the radio audience WBZ means McEnelly's and Reisman's, for these two sterling dance orchestras are known the length and breadth of the land. The former, led by Edwin J. McEnelly, records for Victor, and the latter, with Leo Reisman at its head plays at the Hotel Brunswick, and the newcomer who tunes into the New England



George H. Jaspert, Director of Westinghouse station WBZ

station in one of its more serious moments will get the surprise of his life if he happens along when one of these lively aggregations is on the air. There are further dance programs by Bill Boyle's Copley Plaza Orchestra, and the Hotel Westminster group, which add to the gaiety of the station. One of the unique features of this broadcaster's popular programs is the Aleppo Temple Band, something which never fails to appeal to the masculine part of the radio audience. This huge organization of 218 pieces, has a standard far above that of the average amateur band, and anyone who has listened in on the regular weekly concerts given by these be-fezzed gentlemen, is likely to have his dials set in the same position the following week.

WBZ has a number of alert young announcers, and we don't

believe there is a genuine Harvard accent in the crowd. Those who have daylight reception are familiar with the expert handling of football games from Princeton, Brown, Harvard and Holy Cross, by "Jim" Murley, sports announcer, who also takes care of WBZ's publicity, when he isn't at the microphone; and the uproarious hockey games which come from the Boston Arena one night each week during the winter are breathlessly described by Frank Ryan.

In fact it seems that WBZ has overlooked no type of radio listener in preparing its programs, and one might wish that its example could be followed by several middle-west and western stations that seem to operate on the theory that their audiences will listen to anything that happens to come to the studio doors, and that it is a waste of time to prepare programs with a special class of listener in mind.

And since we have been talking about the question of the appreciation of the radio public, and to just what extent we are to regard broadcasting as an established form of entertainment, we might quote from a letter we received the other day, which we believe illustrates the attitude of the average intelligent listener.

"Your article on radio programs came along on a busy day, and I laid it aside with a vague wonder as to what on earth you could find in this subject to interest you much less to write about. That night I had expensive tickets for a concert. It poured rain—the taxi slid around in the traffic until I arrived at the concert hall a nervous wreck. The auditorium was stifling hot, the man in front of us was suffering from an acute sinus, the flapper and the boy friend back of us were afflicted with giggles, the artiste of the evening apparently had an attack of temperament and behaved like a bear, and Sam growled all the way home over the injustice of dragging a tired business man forth to such an exhibition under the guise of pleasurable entertainment.

"The next evening the new novel I had been looking forward

(Please turn to page 69)

# Design and Manufacture of Resistance Units

By JOSEPH MORGAN\*

**I**N the design of radio apparatus, whether for transmitting or receiving, we must always consider three quantities; inductance, capacity and resistance. Inductance and capacity are utilized chiefly in apparatus used for obtaining resonance at certain frequencies (tuning). Much valuable experimentation has been made on inductance coils and condensers so that for the last few years we have had coils and condensers having extraordinary good electrical and mechanical properties. Unfortunately the development of resistance units has not kept pace with coils and condensers. This is not because the resistance unit is any less important, but chiefly because the problem is a much more difficult one.

Before tracing briefly the history of the design of high resistance units, it may be advantageous to list some of the more important applications of such units to present day radio. In radio, chief uses for high resistance units are for grid leaks, amplifier, coupler units, potentiometers, and for A and B eliminators. A good high resistance unit must be constant in value, noiseless, free of appreciable inductance or capacity, compact, durable, and have sufficient carrying capacity.

Naturally the first type of resistance unit was a coil of resistance wire. The limitations of this type of unit are many. In the first place, such a unit is very bulky if the resistance exceeds 100,000 ohms. Second, they are incapable of carrying much current without undue heating. Third, it is impossible to construct high resistance wire-wound units which have inductance and capacity sufficiently low for grid leaks and coupling units.

In order to overcome certain of these disadvantages, some years

ago a unit was devised which consisted of two metal electrodes dipped in ink. The resistance was controlled by the distance between the two electrodes and the concentration of the ink. This unit was in many ways very imperfect. It was not compact; it was not portable; it was not permanent; and the resistance could not be adjusted within ten per cent of the desired value.

Shortly after this, the very familiar unit consisting of a piece of paper dipped in India ink and clamped between two copper contacts was developed. There was scarcely any virtue outside of cheapness and compactness which was possessed by this type of resistor. It could not be made within 20 per cent of the desired value; it changed from day to day; was entirely unable to carry currents even of the order of a few milliamperes, without breaking down. Its chief merit was that of a humidity indicator, but unfortunately it does not seem to have been employed for this purpose.

An improvement upon the aforementioned type was made by enclosing the carbon paper and contacts in a small glass tube. Even with this protection, these units were erratic in behavior.

It was at this point in the development of high resistance units that the International Resistance Company engineers began experimenting with a view to the development of a strictly scientific product. After many months of patient research, a method was found for coating the inside of glass tubes with a thin layer of metal. The glass tube was provided with brass caps and the caps were in metallic contact with the metal coating through the medium of low melting point alloy. While this type of resistor was an improvement over previous units, the film of metal was necessarily so thin in order to obtain the desired high resistance

that it was impossible to make a perfect contact with the alloy in the brass caps. Further the heat due to carrying the largest currents required for coupling units, made permanent changes in the resistance of these microscopically thin metallic films. This type of resistor frequently showed excellent characteristics immediately after manufacture. However, after several months of use these units deteriorated rapidly due to crystallization of the conducting film. Almost every conceivable type of substance was deposited on the inside of these glass tubes. Every known kind of glass and countless alloys for sealing in were tried. Each new specimen was subjected to the most rigorous scientific tests. Literally thousands of specimens were constructed.

## Metallized Resistor

**O**UT of all this experimentation, there was finally evolved the present type of metallized resistor with the glass core which fulfills the most exacting requirements which could be placed upon a high resistance unit. The glass tube, internally coated with a thin film, was abandoned. In its place a fine glass filament is used. This filament is spun on a very ingenious and efficient machine in lengths of five hundred feet and is entirely uniform in diameter. The glass fibre is then passed through a conducting solution, and then into a high temperature furnace through which a steady flow of gas is maintained. This process results in the production of a perfectly homogeneous conducting surface, thoroughly hardened upon one of the finest insulators known. The coated filament has many advantages over the internally coated tube. First, due to the much smaller area of the filament it is possible to have quite a thick coating of conducting material and at the same time produce a very high resistance.

(Please turn to page 44)

\*Engineering Dept., International Resistance Co., Philadelphia.

# Versatility and Simplicity Are Features of This Set

**M**ANY broadcast listeners, as well as experimenters, have often expressed a desire for a receiver in which versatility and simplicity of arrangement have been combined. In answer to these requests the set described herein has been constructed and thoroughly tested in the laboratory, as well as under actual operating conditions from the highest to the lowest wavelength which it covers. All of this has been accomplished with extreme satisfaction.

Plug-in coils, five in all, allow easy transition from one band to the next in the broadcast spectrum. The Aero coils used, when in conjunction with a variable condenser of 140 micro-microfarads (.00014 mfd) cover the following ranges: Coil 1, 15 to 33.5 meters; Coil 2, 31.5 to 68 meters; Coil 3, 57 to 133 meters; Coil 4, 125 to 250 meters and Coil 5 from 235 to

## *Wavemeter Added For Benefit of Experimenters*


550 meters. These coils, designed by F. J. Marco, a well-known amateur of Chicago, who is engaged in consultation work at present, have an overlap on all coils so there is no possibility of a lapse in covering the entire range of broadcast frequencies. Thus the broadcast listener may select programs from WGY, KDKA and others whose wavelengths are shown in our Short Wave Broadcasting section in every issue. He may also take in the ordinary broadcast programs from 200 to 550 meters. For the amateur the set is ideal because he may skip at will in the 20, 40, 80 and 150 meter bands.

For the advanced experiment-


er a wavemeter of the resonance indicator type (for transmission) has been included, the coils being the standard Aero coils with the tickler windings stripped off, leaving only the secondary. The range covered by the meter is the same range as that of the receiver. The meter may be used either as the resonance type, or as a straight wavemeter in connection with the grid meter driver described by Hoffman on page 7 of the September RADIO AGE.

Martin Copeland's new illuminated controls have been used on both the receiver and the wavemeter, as will be seen from an inspection of the pictures on these pages.

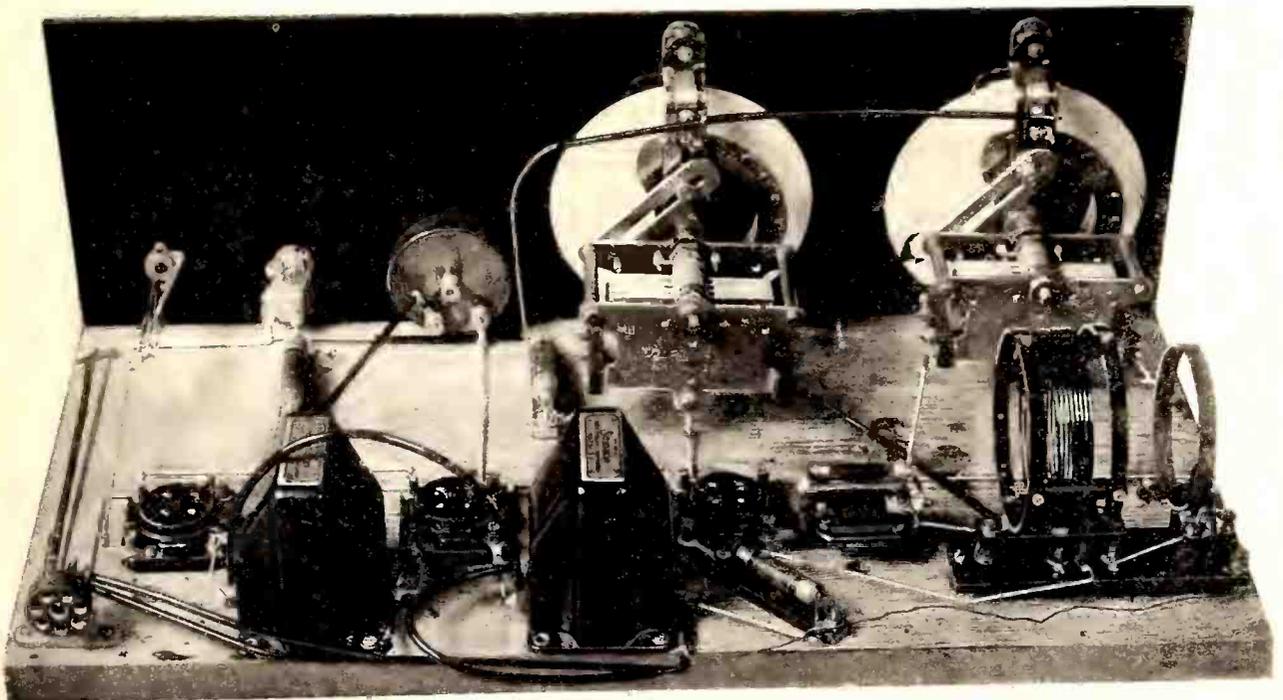Reference to the schematic circuit on page 24 will give the builder an idea of the electrical connections. The coil marked A and G in the diagram is a fixed tune primary which serves as an energizer for all of the



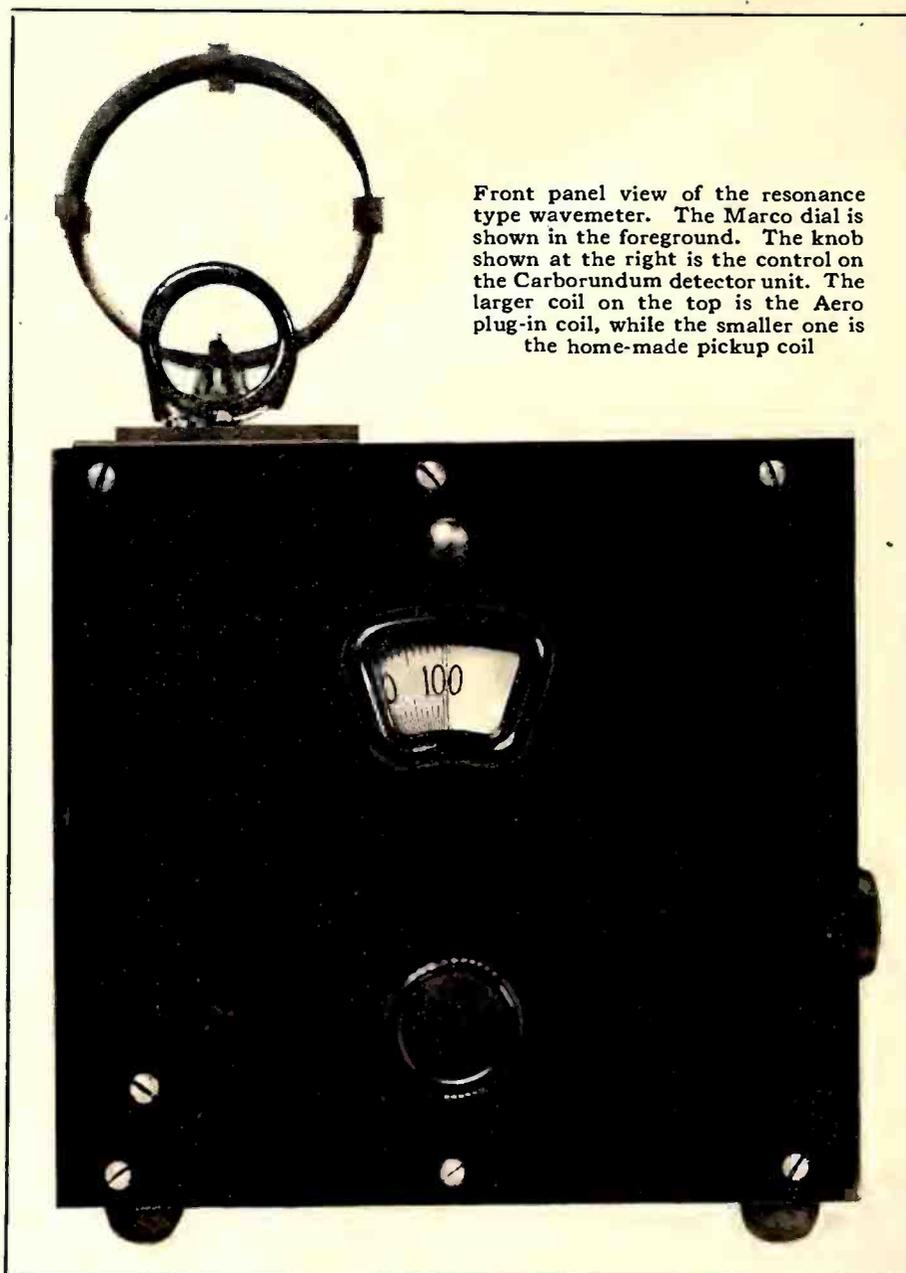Rear view of the completed short-long wave receiver showing Marco illuminated controls, Aero plug-in coils as well as other units mentioned in the text of the accompanying article




Front panel view of the resonance type wavemeter. The Marco dial is shown in the foreground. The knob shown at the right is the control on the Carborundum detector unit. The larger coil on the top is the Aero plug-in coil, while the smaller one is the home-made pickup coil

plug-in coils. While its tuning is fixed, nevertheless its inductive relationship to the various secondaries may be altered at will.

Condenser C1 is a Cardwell taper plate type 167-E having a maximum capacity of .00015 mfd (150 mmf) for spanning the secondary. The regenerative condenser C2 is another Cardwell taper plate, type 168-E of .00025 mfd (250 mmf). The grid condenser is a Sangamo .00001 mfd with a Durham grid-leak whose value may be from 3 to 7 megohms.

**FILAMENT** control is fixed. The detector, as used in our tests, consisted of a 199 tube. The resistance for that particular tube was an Amperite 199 which allows proper operation of a 199 from a six volt source. This is shown as R1 in the diagram. R2 is a 10,000 ohm Allen-Bradley fixed resistance (cartridge type) used as a choke in the plate circuit of the detector tube. Since it is non-inductive it can have neither a fundamental nor harmonics and this on occasions has helped in preventing blind spots in short wave receiver tuning. (Blind spots are those which occur when in tuning across a given band the tube stops oscillating, and excessive regenerative coupling is necessary to again induce oscillation.) R3 is an

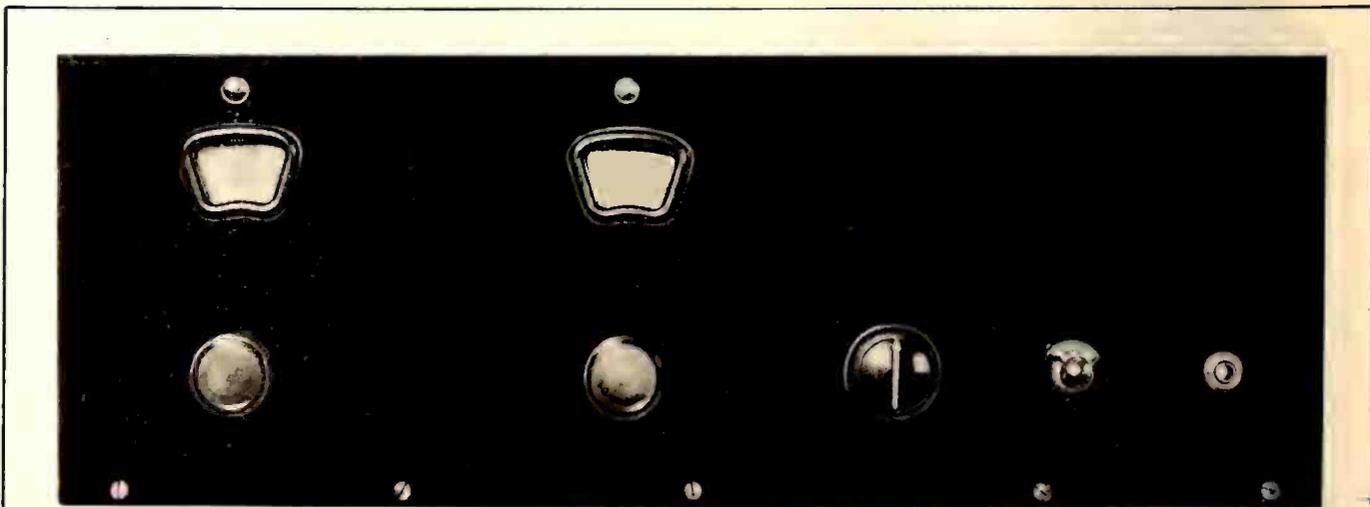

This front view of the receiver shows the Marco controls, Centralab variable resistor across the first audio grid circuit for volume control, then the Yaxley switch and the phone or loudspeaker jack. The little knobs above the Marco controls are for turning on and off the lights back of the celluloid dials, current being taken from the same source as for the filaments


Amperite type 201-A while R4 may be an Amperite 112 for use with a 112 power tube. If quarter ampere tubes are used throughout, the last two may be put on a single 112 resistor instead of 2 single 201A resistors.

Audio transformers are the Samson 3 to 1 ratio, this kind having been used for good results on broadcast frequencies where quality is desirable. On the amateur bands, with code, quality is not especially desired, but rather volume.

Sockets used were those made by Bremer-Tully which are cushioned. For short waves cushioning is not a bad idea to cut down tube jarring. Filament and plate connections terminate in a Jones base mounting. A Centralab O-200,000 ohm variable resistor placed across the grid circuit of the first audio, serves to control volume. The set is turned on and off by means of the Yaxley filament switch. A phone jack of the same make is provided for headphones or loud speaker.

Properly built this receiver is perhaps the most selective one we have yet used. It is especially desirable when tuning on the broadcast band to split the band into two sections by the use of Coils 4 and 5, the former covering from 125 to 250 meters, and the latter from 235 to 550 meters. Biasing of the two audio grids is accomplished by means of a C battery which may either be placed in the rear of the baseboard, or kept separate on the table.

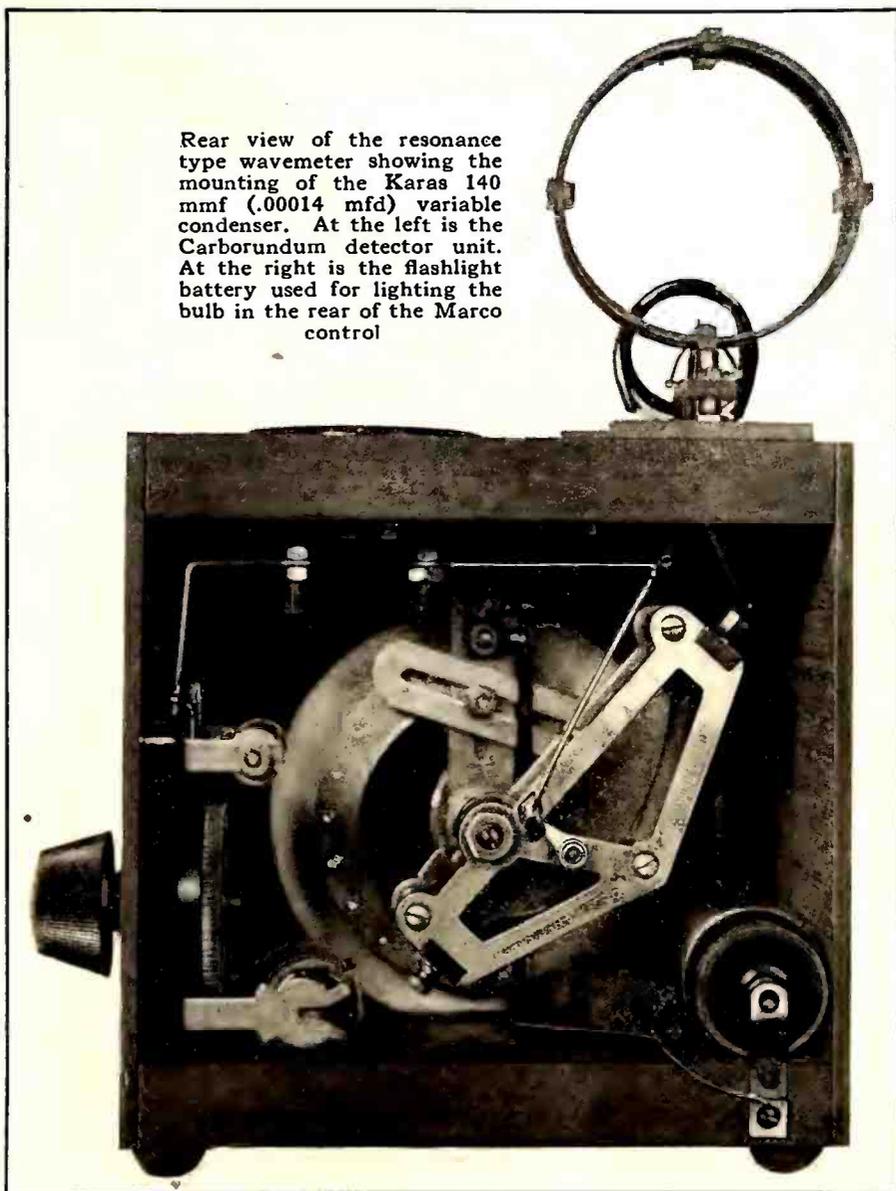**P**LACEMENT of the parts is illustrated in the photograph of the rear view of the receiver



Rear view of the resonance type wavemeter showing the mounting of the Karas 140 mmf (.00014 mfd) variable condenser. At the left is the Carborundum detector unit. At the right is the flashlight battery used for lighting the bulb in the rear of the Marco control


at the bottom of page 21. The front panel picture is shown at the bottom of page 22, while the schematic is shown at the bottom of page 24. By following these views the construction of the receiver is a simple matter. The panel length is 7 by 26 inches. It can be made shorter if desired.


By means of metal template furnished with the Marco illuminated controls, the drilling of the panel for the bezel is quite simple. Drill the top and bottom holes of the template first; then affix the template tightly against the panel and follow the drilling course for the bezel. Since the template is held tight against the panel, the holes for the bezel will be accurately placed. When all holes are drilled, remove the template

and chip or knock out the window.

Construction of the wavemeter is also a simple proposition. The panel used is a 7 by 7 piece of Insuline. It is prepared for the insertion of the Marco illuminated control as previously described.

Two coils are used, as shown in the schematic diagram on page 23. The smaller coil (L2) is a pickup winding consisting of about five turns of busbar wire (round) wound on a form 1½ inches in diameter. Spaghetti is first placed on a length of busbar wire, then it is coiled tightly around a form 1½ inches in diameter and then removed. The pickup coil will be self-supporting and have good insulation between. This coil is

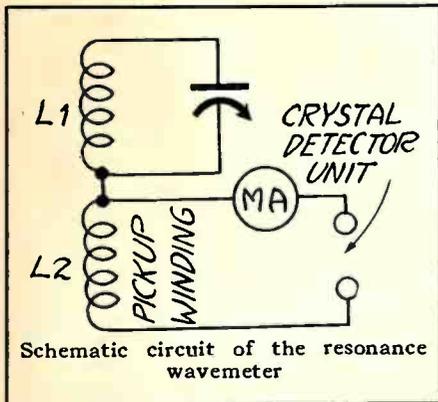

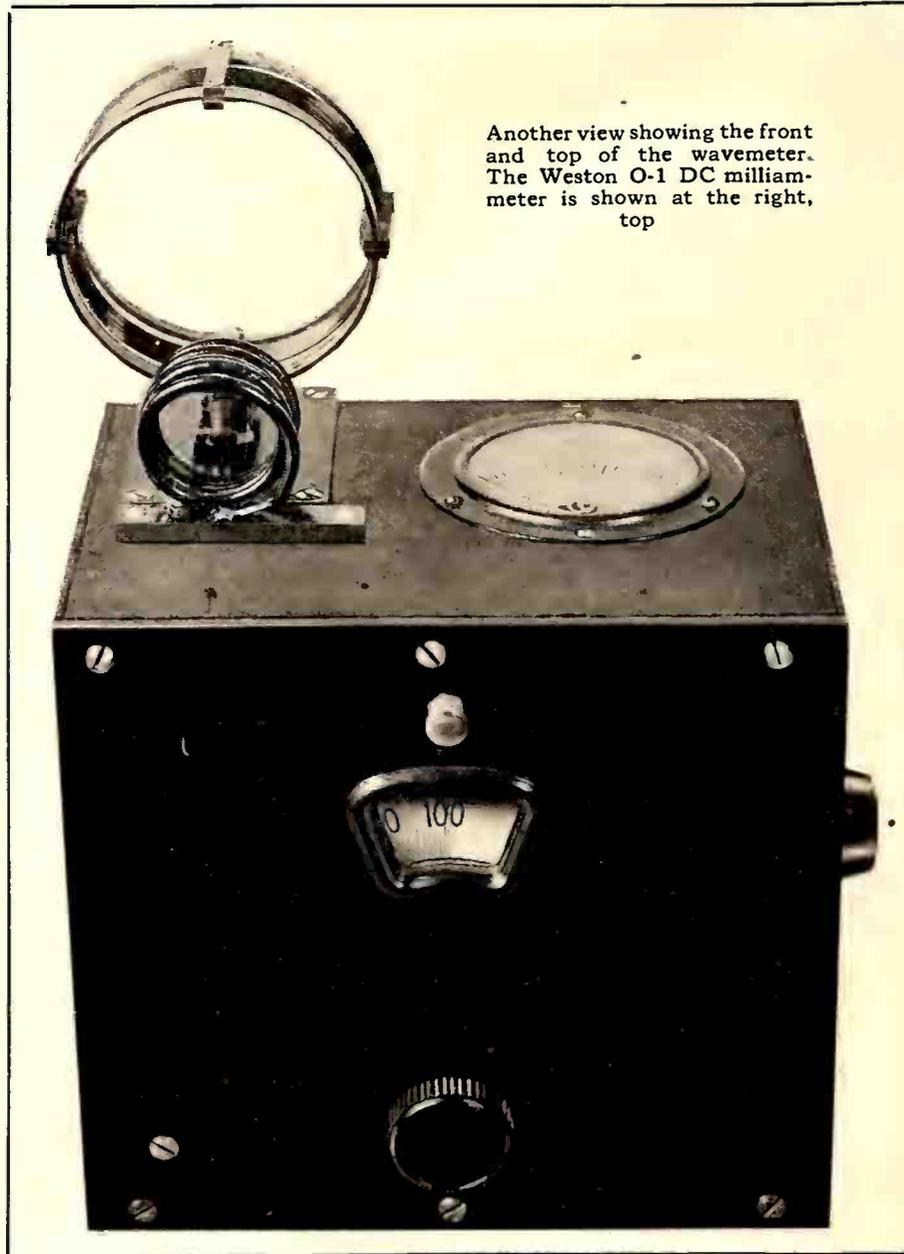

Another view showing the front and top of the wavemeter. The Weston O-1 DC milliammeter is shown at the right, top

the variable condenser rotated, at the point of resonance the milliammeter will begin registering. When the needle reaches its highest point on the scale, the resonant frequency of the transmitter will have been found. By properly calibrating each of the coils against a standard, the wavelength of any transmitter within the band may be ascertained. For use in determining the fundamental of coils, etc., the grid meter driver described by Hoffman in the September RADIO AGE should be carefully studied.

A small 3 cell flashlight battery is shown in the housing for lighting the bulb in the rear of the Marco control. The Carborundum stabilizing unit also makes use of a small single cell flashlight battery for applying a potential to the fixed crystal.


This receiver has been in use in the laboratory for the past sixty days on both code and voice work covering the entire broadcast and amateur range. Its selectivity on the broadcast band is excellent and good quality of reproduction secured.


It has also been used with A and B elimination with fine results. The recent A eliminator made by Briggs and Stratton, Inc., known as the Radi-A, was utilized in securing filament supply, while the Majestic B eliminator was connected up for the plate potential. Both of these devices operated without any hum when head phones were used on the receiver. The same held true for loud speaker operation.

equipped with General Radio plugs while the G. R. jacks are placed on top of the meter housing. The coil L1 is any one of the five Aero coils, which are already equipped with General Radio plugs. The tickler winding is stripped out of the coils so these windings will not affect the wavemeter inductance. A Karas .00014 mfd (140 mmf) condenser is connected across L1 from one end to the other. Coil L2 is coupled to L1 at the rotor of the condenser. As shown in the schematic the Weston O-1 DC milliammeter is in series with coil L2 and the crystal detector which is one of the Carborundum stabilizing crystal detector units which have been found admirable for this

purpose. The schematic shows the manner in which the connections are made.

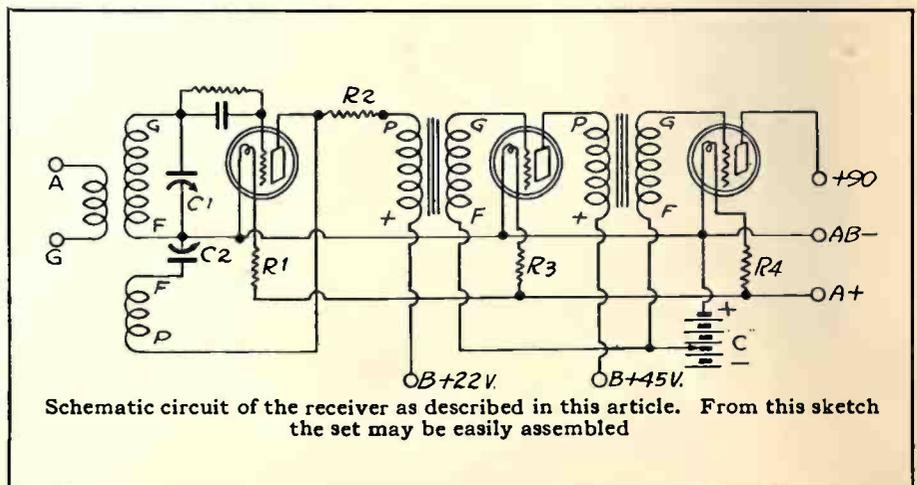When the wavemeter is placed near a transmitter and



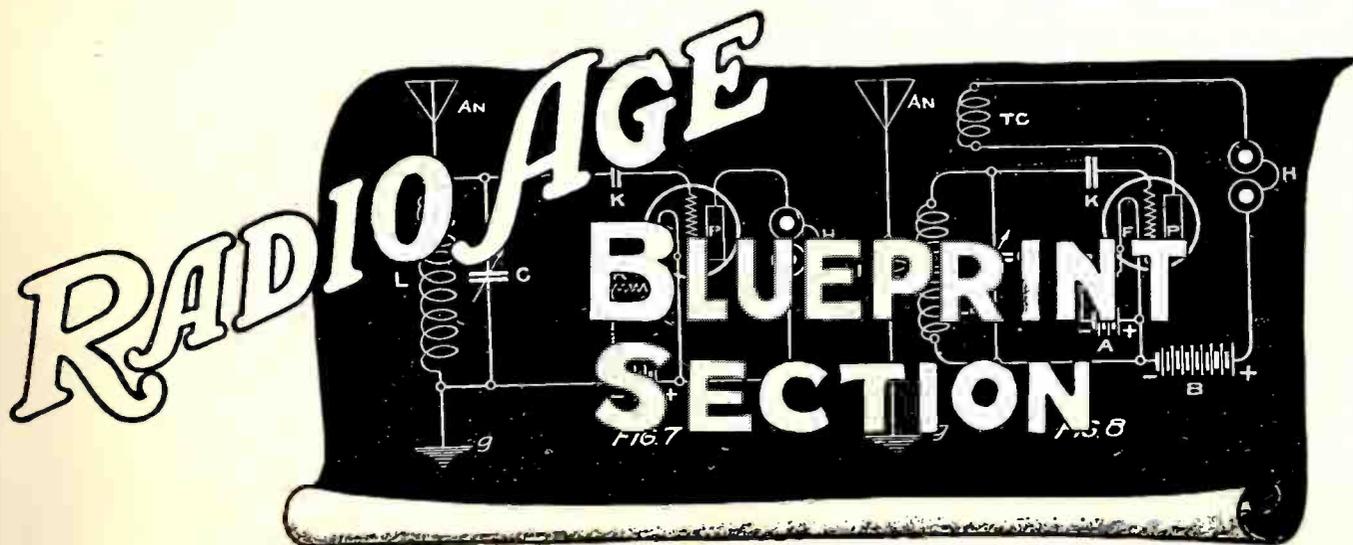

# New Six Tube Receiver Kit Is Completely Shielded

By McMURDO SILVER


**I**NSPECTION of this season's receivers indicates that practically all are of the tuned RF variety and that though in this respect they certainly are not new or radical, yet certain new features are evident which make them more than interesting. Among these features may be mentioned simplicity of tuning control, quality of reproduction, the use of complete shielding, and, possibly more important, there is evident a very persistent endeavor to equalize amplification throughout the entire wavelength range to be covered—a feature woefully absent in previous designs.

The receiver to be described in this article may well be selected as an example by means of which the outstanding engineering advances of the season may be explained inasmuch as they are practically all contained in this single design. Not only those of an electrical nature are evident but the more important mechanical advances tending to mechanical strength and longer life of receivers are excellently exemplified in the Shielded Six, the name by which the outfit illustrated,

which is available in kit form, is known.

Radio frequency amplification employed in the receiver is ex-

tremely interesting and is remarkably efficient, for RF transformers employing an extremely high value of coupling between primary and secondary are used. This high value of magnetic coupling is obtained without detrimental capacitive coupling between windings by spacing the primary turns over the full length of the secondary winding and further by locating them on a tube which is one-quarter of an inch away at all points from the secondary winding. This feature of maximum inductive coupling with the lowest possible value of primary inductance is one which does not appear to have been properly appreciated in previous years though it is extremely important, as can be shown very simply. It is known that the larger the inductance in the plate circuit of a vacuum tube, be it either detector or RF amplifier, the greater will be the tendency of the circuit to oscillate up to a limiting critical point which is approximately the point at which the plate circuit becomes resonant with the grid circuit. In an RF amplifier oscillation is absolutely

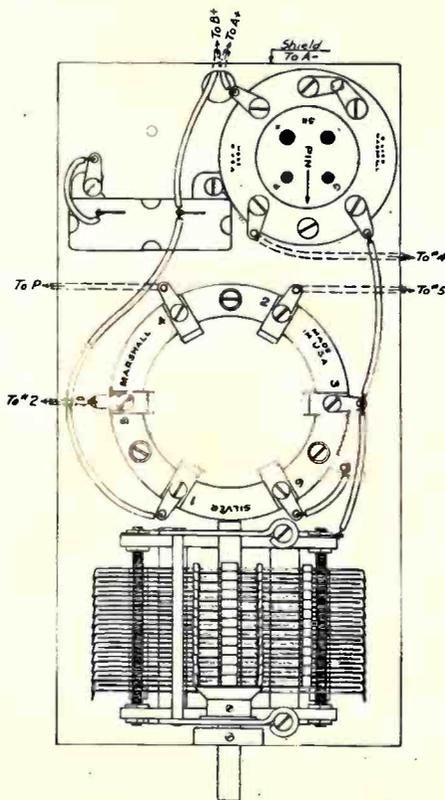

Pictorial sketch of the tuned RF unit inside the shield

(Please turn to page 28)

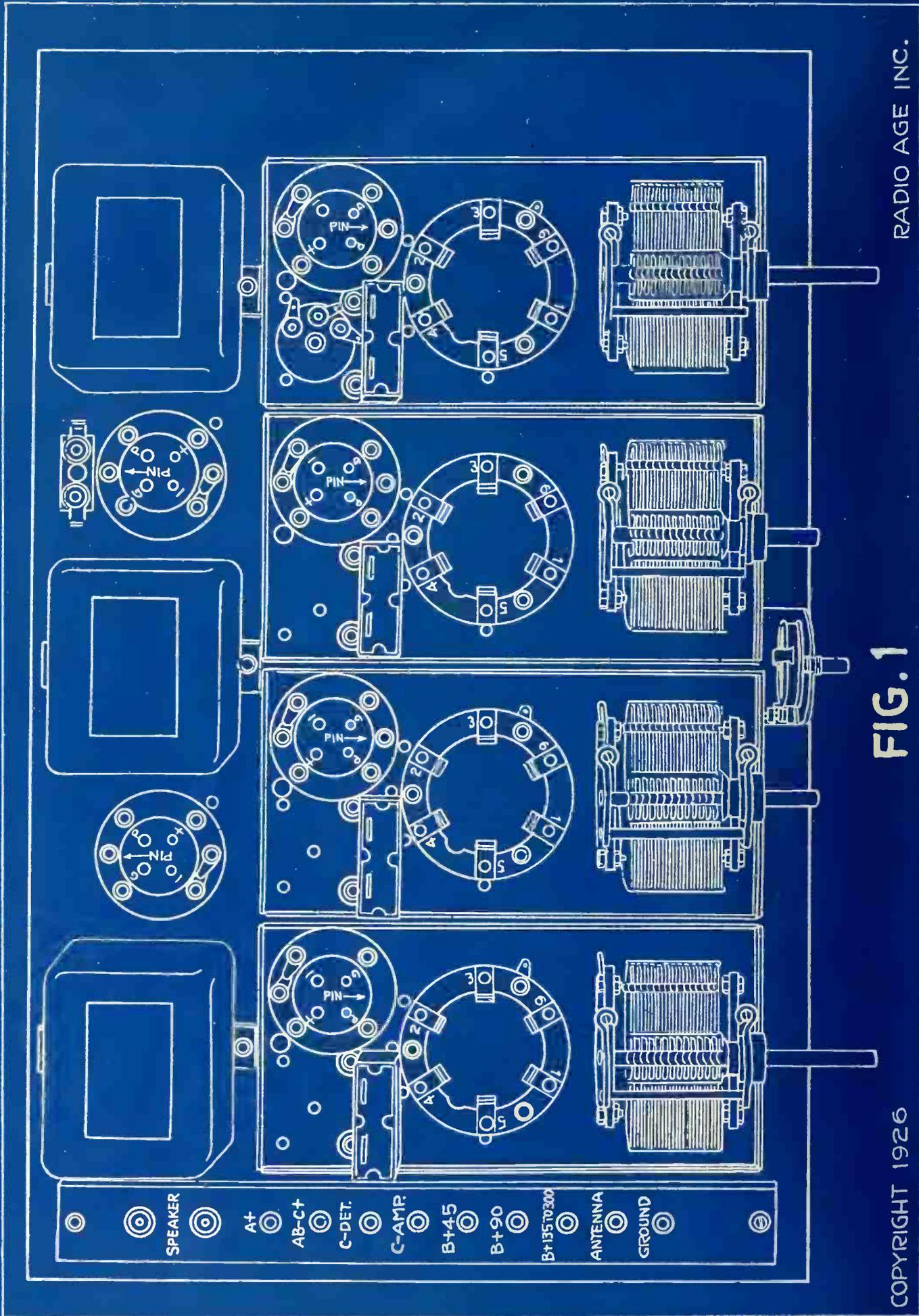


FIG. 1

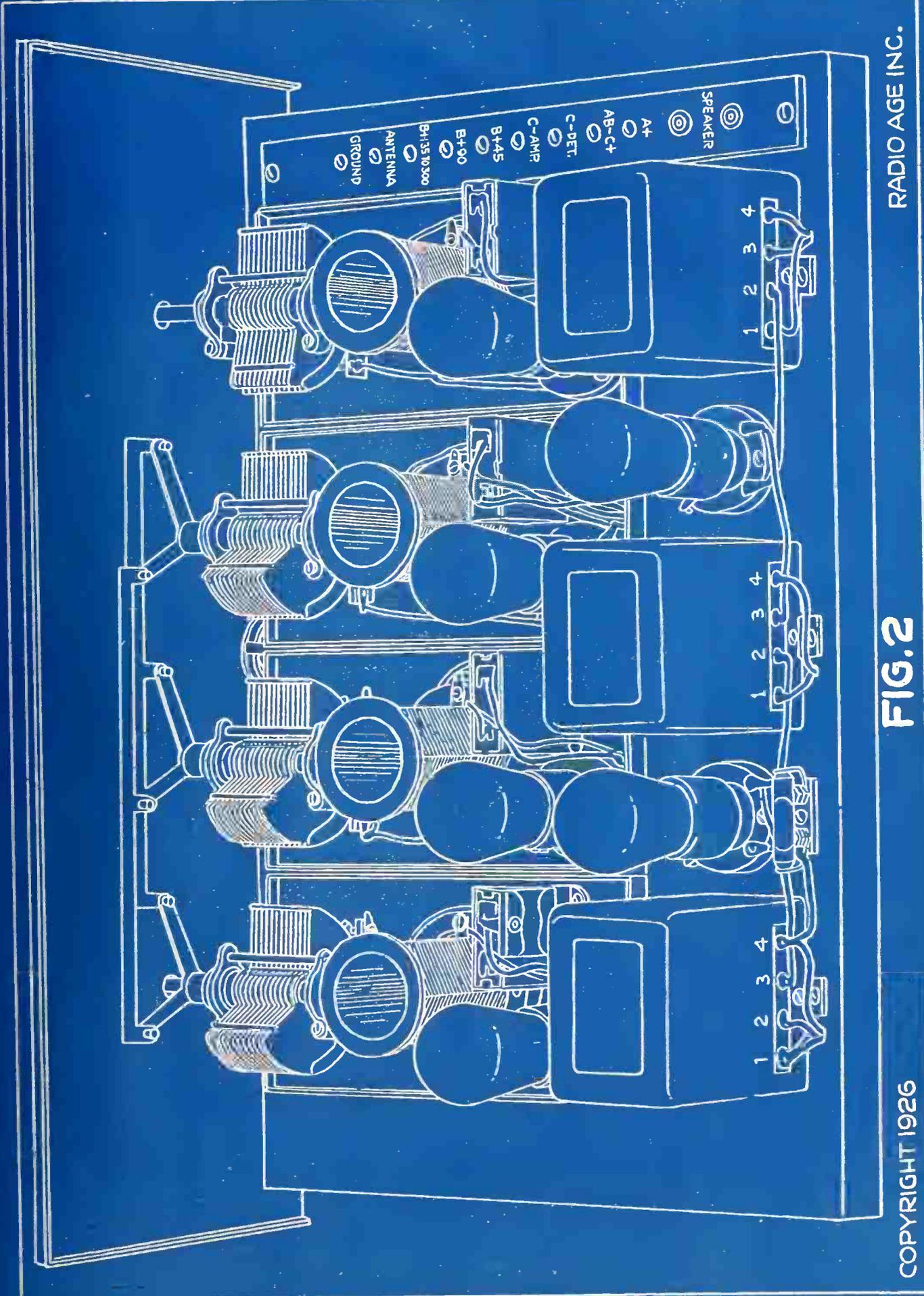


FIG. 2


RADIO AGE INC.

COPYRIGHT 1926

undesirable and is the limiting factor in the efficiency of practically all designs. For this reason it is evident that the primary inductance of an RF transformer should be kept as low as possible, yet the primary should be so placed with relation to the secondary that maximum inductive coupling results with a minimum of primary inductance. This theory, capable of mathematical substantiation, and evident in the product of the best engineers, is in direct contradiction to the older belief that the primary with turns bunched closely together and located at the filament end of the RF transformer secondary represented the peak of efficiency.

Coupling co-efficient between primary and secondary of the RF transformers is such that the tuning of each stage is slightly broader than would be allowable in a two stage tuned RF amplifier. This is a vital necessity for with three stages of RF amplification employed the side-bands of received signals would be cut were the RF stages too selective. Further, the possibility of effective gang control would become increasingly remote as the selectivity of the RF stages was increased. This matter of gang control is an important one for it would be practically an impossibility to handle a four control receiver, particularly when it is borne in mind that the average man often has difficulty in handling the conventional three-dial outfit.

In the Shielded Six the antenna stage is separately tuned by means of a variable condenser shunting the RF transformer secondary. Thus variations in antenna characteristics which affect the tuning of the first RF stage are not allowed to react unfavorably upon the operation of the receiver inasmuch as this stage is independently manually controlled. In order to minimize the effect, however, and to allow accommodation of the receiver to varying lengths of antennas, a switch is provided on the primary of the antenna transformer which permits the inclusion of a part or the whole of the primary winding in the antenna circuit.

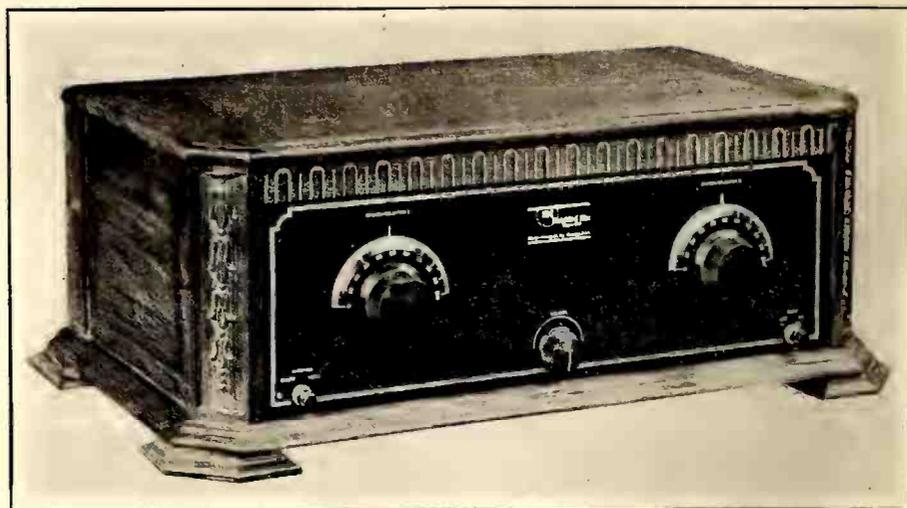

The completed receiver described by the author is shown above

Inasmuch as the input and output characteristics of the second, third, and detector stages are practically identical, and as the coils and condensers are manufactured with more than the required degree of uniformity, these three circuits are tuned by a single control dial which, through the agency of a mechanical link motion, actuates the three variable condensers required for the tuning of the different RF transformers.

It will be noticed that all of the RF circuits are completely shielded by aluminum housings which enclose completely all parts of each stage. Aside from an extremely important function of this shielding which will be considered later, one of its most important purposes is to prevent the pick-up of signal energy directly by the coils, wiring, or other parts of the different RF circuits. The importance of this will be appreciated if it is realized that the various tuned circuits in this receiver, or in any tuned RF receiver, are intended to operate in the fashion of a filter. Thus the incoming signal flows to the first tuned stage from the antenna and is amplified by this section which serves at the same time to eliminate unwanted signals picked up indiscriminately by the antenna. The second and all successive stages serve to enhance this filtering effect with the result that in a properly designed receiver under ordinary conditions only one station at a time can be heard, all

others being filtered out by the action of the tuning circuits. In the case of very strong powerful stations enough energy is frequently picked on the various coils of a receiver to operate the set with the result that the desired filtering action is entirely absent since the signal is not forced to progress through the various circuits from the antenna but is picked up in part by the detector circuit coil, as well as other coils and instruments. The obvious condition is that selectivity may not be obtained in congested areas with a tuned RF receiver, the circuits of which are not thoroughly shielded.

The other purpose which complete shielding serves is to equalize the amplification of the RF amplifier over the entire wavelength range. Inasmuch as shielding represents only one method employed to obtain this end and as this is a feature in which practically all of the older receivers are sadly deficient, it might be well to explain why it is necessary to employ special methods to obtain it.

In an ordinary RF amplifier, or tuned RF receiver, it is a well known fact that the tendency to oscillate is greatest at the shorter wavelengths and that the amplification is least at the long wavelengths. This trouble may be, for purposes of explanation, attributed to the increasing efficiency of RF transformers with increasing frequency or decreasing wavelength. This is an inherent characteristic of all RF

transformers and inasmuch as they are necessary in tuned RF receivers some means must be found to compensate for this deficiency if satisfactory uniform amplification is to be obtained at both long and short wavelengths in a receiver.

Another angle of considering the matter is that as the transformer efficiency increases or as the frequency increases the tendency of the circuit to oscillate becomes greater and greater, and not in direct proportion to the increase in frequency. It is therefore necessary if uniform amplification is to be obtained to provide some means which will counteract oscillation as the frequency increases at a rate almost exactly proportional to the increase in oscillation tendency. No one single method is adequate to accomplish this, though a number of individual methods will be found in different receivers, one of the most popular ones being the use of an adjustable primary inductance in the RF transformer in which the primary winding takes the form of a variometer or a coupling coil, the position of which is adjusted as the receiver is tuned.

In the Shielded Six five individual methods are used, the cumulative effect of all of which is to oppose oscillation in a very slightly greater effect than the tendency is manifest at all wavelengths. These methods are: (a) Interstage shielding; (b) placement of coils upon shielding; (c) reversed tickler; (d) series grid resistances; (e) manual control on first stage with loading on successive stages.

The first feature, that of interstage shielding, needs little explanation for it is generally accepted that coupling between circuits is extremely detrimental in an RF amplifier, or, for that matter, in any other type of amplifier, and may only satisfactorily be eliminated by complete shielding or isolation of each individual stage circuit.

Method "B" takes advantage of the increase in resistance of the RF transformer coils which may be effected by their relation to the shielding. Normally, the resistance at long wavelengths

remains practically uniform with the shielding positioned as it is in the Six. As the frequency increases, however, due to the effect of the metal upon the coils, the resistance goes up quite rapidly which is the exact effect desired to compensate for the increasing tendency toward oscillation. However, the resistance increase cannot be made sufficiently rapid by the use of shielding to effectively compensate for the tendency toward oscillation and, as a result, allow of uniform amplification. Therefore a reversed tickler is employed in each stage, coupling energy from the plate circuit of each vacuum tube back to its grid circuit in a direction intended to oppose oscillation. For reasons well known to the art, the efficiency of this coupling increases as the frequency increases which is exactly what is desired to compensate for the oscillation tendency. Like the increase in coil resistance due to shield placement, however, this method alone does not increase rapidly enough in its effect with increases in frequency to provide uniform amplification. Therefore still another method is employed.

This method takes the form of series resistances located between the grid of each radio frequency amplifier and its tuned secondary circuit. These resistances tend to slightly oppose oscillation at long wavelengths, but, due to inductive effects, their alternating current resistance goes up as the frequency increases and they therefore operate to increasingly oppose oscillation with frequency increase.


All of these methods are used to render uniform the amplification of the second and third RF stages throughout the entire wavelength range of the receiver and to keep them in an extremely sensitive condition throughout this range. Inasmuch as the characteristics of antennas with which the Six would be used are bound to vary and cannot be predetermined, it will be realized that the amplification of the first RF stage will vary with variations in antenna resistance and that, as a result, no methods of automatic sensitivity control may

be adequately employed. Therefore a manual control in the form of a resistance is used to regulate the sensitivity and amplification of the first RF stage. This resistance is unique in its application as it is arranged in such a fashion that a load is always kept on the primary in the second stage RF transformer. Were this not done, and were the control of the first tube effected through the agency of a filament rheostat or a series plate resistance, the load on the second RF stage would vary and, as a result, the amplification of the balance of the RF amplifier would not remain uniform.

In the methods employed a series plate resistance is used in the first RF stage which is so arranged that as more resistance is included in the plate circuit and the load automatically lessens on the second RF transformer. At the same time a portion of the resistance is shunt with the RF transformer primary decreases serving to increase the load in a directly opposite fashion. Thus the first RF stage can be pushed up to the point of oscillation and the sensitivity of the receiver in the hands of an experienced operator rendered practically unlimited. This resistance, one portion of which is in shunt with the primary winding of the second RF transformer and the tickler winding with the first RF transformer, is, by virtue of this fact, an excellent volume control, for, by means of it, the volume of a receiver may be cut to practically nothing or may be increased to a roar at will.

The audio frequency amplifier employs two stages of very heavy transformers which have a frequency characteristic in which the amplification increases as the frequency decreases. (It is a well-known fact that practically all commercial loud speakers will respond very poorly to frequencies below 100 cycles, if at all in many cases. This effect is further enhanced by the output transformer which prevents saturation of the loud speaker before its signal handling capacity is reached by the direct plate current of this last power tube.

(Please turn to page 32)

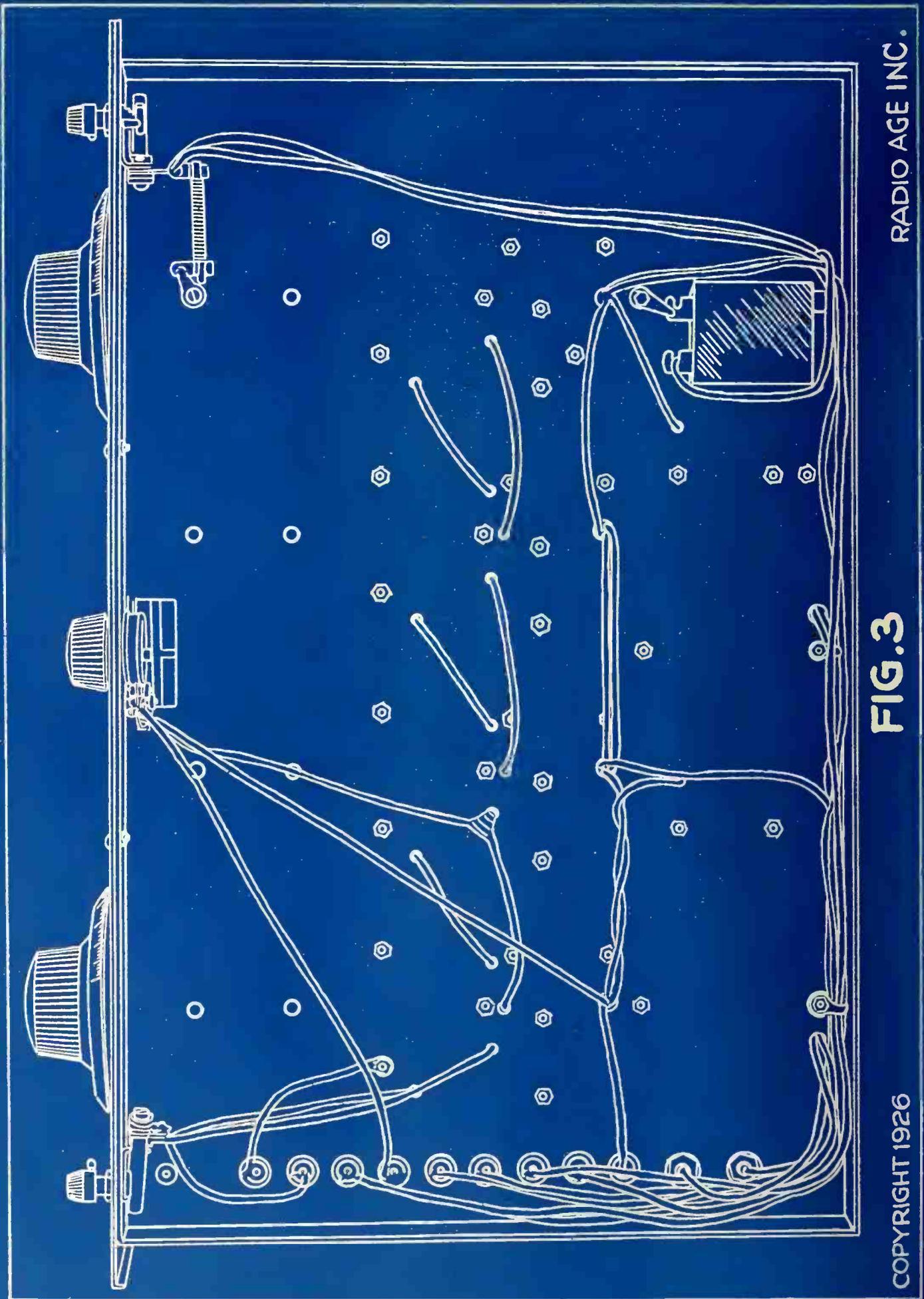

RADIO AGE INC.

COPYRIGHT 1926

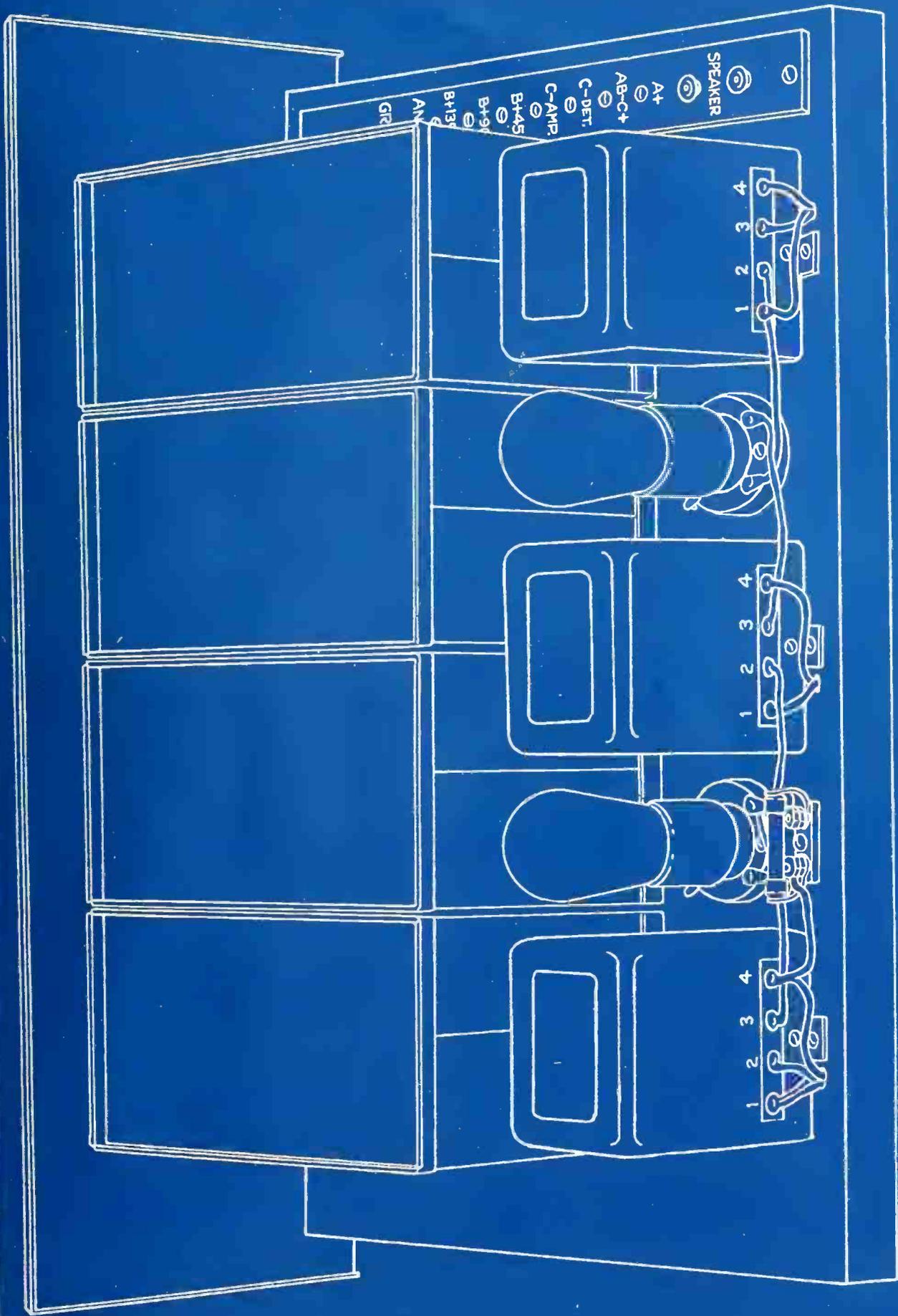


FIG. 4

The C bias on the first AF amplifier is rather interesting in that it is only one volt. This low value is selected as it has been determined that the grid voltage of this tube will never reach this value and consequently the grid of the tube may never run positive, which would cause distortion. An important effect realized by the use of the low C voltage is a decrease in the effective plate impedance of the first amplifier tube which allows of better low frequency reproduction.

Mechanically the receiver is particularly interesting inasmuch as it is available in kit form and, as a kit, represents the first all-metal construction ever available to the home-builder. The photograph of the front panel illustrates the simplicity of the assembly. On this panel will be found the antenna tuning dial together with a second dial controlling the second, third, and detector stage tuning. In the lower center of the panel is the volume control resistance while in the lower right-hand corner is the on-off switch. No filament rheostat is used, a fixed resistance providing automatic control of the non-critical amplifier tubes. At the left hand end of the panel will be seen the antenna switch allowing the use of either long or short antenna.

In one of the rear view photographs the entire assembly is clearly revealed to the eye. A terminal strip will be seen carrying all battery, antenna, ground, and speaker binding posts. This terminal strip is fas-

tened upon a steel chassis which in turn carries the walnut finish brass front panel. Located directly behind this panel are the four individual aluminum stage shields which contain all the RF apparatus of each amplifier circuit. Directly behind this shield assembly is seen the audio amplifier consisting of three trans-

formers between which are located the two audio amplifying tubes.

In one photograph the link motion serving to connect the three condensers which are tuned together is clearly visible. This is a mechanical motion practically entirely without play and serves the purpose of ganging the individually measured and surprisingly uniform condensers in a most satisfactory fashion.


Five UX201A or CX301A tubes are used, with a UX171 or CX371 power tube in the last audio stage.

The construction of this receiver is extremely simple for every step is clearly illustrated in the photographs and in the wiring diagram. It is practically impossible to make a mistake for all of the parts are standard and available upon the market. Thus with the proper parts procured, they can hardly be mounted in any other than the correct fashion upon the pierced steel chassis which is also a standard item. The testing of the receiver once finished is simplicity itself for there is practically no error to be made in the assembly and nothing can go wrong. Thus with the receiver once connected up there remains no problem unsolved and the builder can enjoy the pleasure of tuning in station after station by means of the two control dials—a pleasure which it is difficult to fully appreciate unless one has tuned an extremely sensitive, selective receiver producing more than ample volume with a tone quality which is startling in its fidelity.

In our next issue we hope to have complete constructional data on the building of a superheterodyne with no repeat positions on the oscillator dial—the set is now in the final stages and awaiting operation tests. We believe the receiver will be ready for readers in the January issue.

Robert J. Casey, nationally known radio humorist, unravels a corkingly funny yarn on the subject of broadcast conditions as we find them at this time. Be sure to get your January issue and laugh with Mr. Casey.

—Editor.

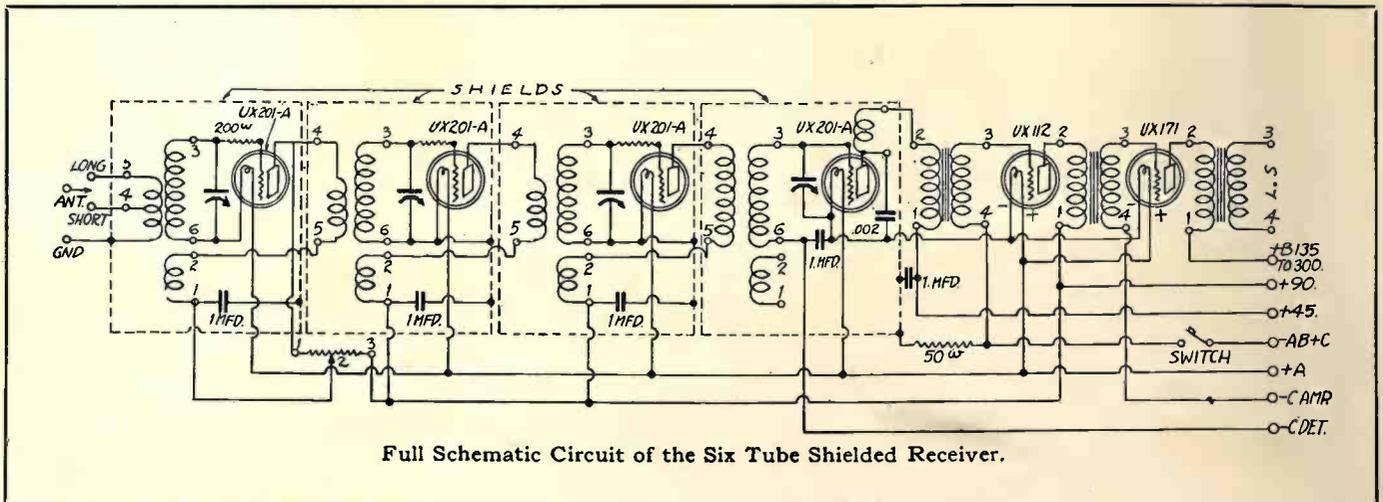

# Who Said the Parts Business Is Dead?

By F. A. HILL

(Associate Editor)

**M**ORTICIANS who may be lurking in the offing, awaiting the early demise of the parts business, are due for an indefinite vigil ending with keen disappointment at the failure of the said parts business to give up the ghost.

This much has been gleaned from interviews and letters secured from those members of the radio industry who are specializing in the manufacture of parts and accessories required in the building of radio sets. Every now and then a glib tongued individual will break forth with the pronouncement that the parts business is dead; that radio is like the phonograph or the automobile, and that no one would ever conceive of the idea of making their own phonograph or automobile. This announcement, generally sponsored by an individual who is engaged in manufacturing a complete receiver (factory built) has so far gone unchallenged.

In an effort to get at the facts in the case recently this magazine interviewed a number of parts manufacturers who have been in the game for some time and who have established a reputation for honest, high quality products. Their reactions will be given as an indication of the virility of the parts business.

W. A. Ready, president of the National Company, Inc., engineers and manufacturers of many parts now used by home builders, sounds the keynote of the matter in this fashion: "Our business, which consists mainly of parts, shows an increase of 41 per cent during the month of September of this year over the same month of last year. It is the writer's humble opinion that the day the parts business dies will be the day the science of radio shall cease to progress. We are very far from that day, at present. The thrill of personal accomplishment is still very strong in the minds of

every active, intelligent American."

Taking the example of another manufacturer whose viewpoint represents a different sphere of activity, we hear from Francis R. Ehle, president of the International Resistance Company, manufacturers of the Durham metallized resistors, who states: "While the majority of sales of our resistors are to manufacturers, a large percentage of them are to jobbers. From the number of jobber orders that have been received during the past month, we would certainly not say the parts business is 'dead.' There seems to be more interest in circuits this year than in previous years—that is, worth while circuits, and we look forward to a very successful season from the sale of Durham resistors to individual set builders through our jobbers and dealers."

## Double the Business

**M**ANUFACTURING a wide variety of parts used by home builders, Arthur Moss, treasurer of Electrad, Inc., throws further light on the subject in the following statement: "Decidedly, the parts business is not dead. Our organization is doing practically double the fan business it did a year ago, and three times as much fan business as it did three years ago. Quality parts will sell and a quality line will grow. The parts buyer is with us to stay as long as a radio is here because of the very nature of radio. A soldering iron to a fan is the same as a saw to a carpenter. Each would be lost unless he could actually do the job with his own hands. The parts business has become more concentrated—that is—the fan business is drifting into the hands of such parts manufacturers as put out reliable products. There may not be the same number of fans there were two years ago, but the successful parts manufacturer is today getting a

greater share of this concentrated buying public."

E. Cornell Martin, vice-president of the Martin-Copeland Company, furnishes us with a pithy analysis of the parts business which is well worth remembering: "During this season there has been a very definite trend towards a greatly increased business in parts of the better type. Many owners of factory built sets have become interested in building their own receivers. This desire to do something constructive one's self is a very pronounced trait of the people of this country. Our business has shown a very substantial increase each of the five years we have been manufacturing radio parts. Parts have just as definite a place in the merchandising of radio as factory built receivers. Careful analysis of the business of stores handling both lines will show that no small part of their profit has been made on the parts. They are free from the necessity of giving service and bring customers to the store on many repeat occasions."

One organization had figured on confining their production to the needs of manufacturers of complete sets, but the jobber demand became so insistent it became necessary to alter the previous policy. We quote H. E. Osmun, sales manager of the Central Radio Laboratories: "We have been very optimistic about radio parts sales and find our optimism justified in every way by the early business. About this time last fall we felt it was scarcely worthwhile to push the sale of our products to jobbers, believing at the time we could interest others connected with the industry that the manufactured set was the thing and that we should concentrate our attention on sales to manufacturers. The jobbing business, however, came in with no effort on our part and with such steadily increasing vol-

ume it was forced on our attention. Since the first of the year we have devoted a great deal of time and thought in developing sales to the home set builder and the man who wishes to improve his present receiver. There can be no question about its success because our sales to jobbers have steadily increased every month since the first of the year with the exception of the two summer months of July and August, and even in these months our parts sales to jobbers were greater than they were a year ago in October."

#### Where Crowds Go

**T**ACKLING the question from another viewpoint, E. Tyrman, president of the High Frequency Laboratories, states: "The question of the condition of the parts business can best be answered by looking into a responsible wholesaler's place of business. There is always a crowd, and this crowd represents the public that is really interested in radio. Despite the statement of many set manufacturers these home builders and experimenters are having much more satisfaction in listening to their own receiver. The confused broadcast conditions require extremely selective sets and the price of factory built receivers to meet this requirement, is prohibitive for many fans. I am convinced there is at present more interest in high class apparatus than during any previous season."

In many cases parts manufacturers have left that part of the business and gone into the complete set market. Here we have an organization that quit the set business to engage in parts. The opinion of Amsco Products, Inc., is voiced by Zeh Bouck in a recent letter: "We are at present exclusive manufacturers of parts, having made our exit from the set building field a year back. Making predictions justified by the extent of the present business, I should say we are anticipating through our advertising work a most successful season in the parts business. The parts business is a long way from suffering from senile dementia. As long

as the patent situation makes it impossible for individual manufacturers to make the best possible equipment, the home made set must stand supreme. The average radio fan today has at his disposal a thousand and one patents and by tactfully infringing upon them he can make a set definitely superior to ninety-nine out of a hundred commercial receivers."

Tobe Deutschmann Company, speaking through F. D. Rankin, gives us the following insight into their business: "The condenser business is more or less riding on the crest of a wave at the present time. We find the activity in amateur building is on the increase. Circuits of B eliminators and power supply sets have been publicized continually and as a result there is an ever increasing demand for condensers and high current carrying capacity resistors. The sale of grid leaks, forming a vital part of set construction, has been increasing steadily and for this reason we are justified in saying at this time, the parts business is not on the wane by any means."

#### Concentrated Buying

**T**HERE have been too many radio dealers in the field according to an analysis submitted for the Benjamin Electric Mfg. Co., through P. A. Powers, advertising manager, who has the following to say: "The radio parts business dead? Not as long as our sales are running twice as large as they were at this time last season. So far there has been more activity in the parts business than at any time since the advent of radio. I believe this experience is typical of most of the leading parts manufacturers. The reports that salesmen are sending in indicate many dealers are going out of the parts business, but we regard this as a desirable condition in many ways. There have always been too many dealers in the field. It now looks as if the sale of parts will be concentrated among the more capable dealers using sound merchandising policies and handling well known quality products. This should be an advantage both

to manufacturers and consumers of radio products. We expect no great boom in parts sales at this time, but see no reason to believe otherwise than that there will be a satisfactory and growing demand for those products which meet market requirements."

Stating they have no reason whatever to complain of the condition of the parts business, the Allen-Bradley Co., through F. F. Loock, sales manager, gives the following brief statement covering their organization: "Speaking from our experience with our jobbers this Fall, we have no reason to assume the parts business is dead or, for that matter, is even dying. It is a fact some jobbers have given up the handling of parts but, on the other hand, this makes the parts business just as much more attractive for the remaining jobbers and dealers. In consequence we are enjoying a very healthy parts business. Frankly, we have no reason whatever to complain."

#### No Service on Parts

**R**EAL activity in the set builders realm is discerned by M. Openshaw, sales promotion manager of the Radial Company, who make the well known Amperite automatic current controls: "If the parts business is dead, or even dying, it is surely one of the liveliest corpses we have ever encountered. As a matter of fact we are in a particularly favorable position to deny such an altogether exaggerated rumor because as manufacturers of a self-adjusting rheostat specified as standard equipment in popular construction sets, we have an actual gauge of the real activity in the set builders realm. It is quite true that a year or so ago many of the jobbers were inclined to go out of the parts business and devote themselves to sets. What were the results? The jobber had to give service; he had to take back a large number of sets for repair and what not; in short there was nothing but grief. Since that time a remarkable business has developed in kits and jobbers were quick to realize the advantages which this

(Please turn to page 54)


# Using Radio to See If Continents Drifting Apart

By S. R. WINTERS

**I**N order to test the theory that continents and islands of the earth are wandering or drifting apart, a network of longitude determinations are being made at strategic points around the world during October and November. Radio signals, sent from seven or eight powerful broadcasting stations, in the United States and other countries, will be used in checking the differences in longitude in various parts of the world and in testing the validity of the theory that the earth is unstable.

It is anticipated that these longitude determinations will be made with extreme accuracy—less than 0.02 of a second for the different longitude stations. This great accuracy would have been impossible under the old methods of using land telegraph lines and cables for sending time signals to longitude or astronomical parties. By means of radio, however, time signals transmitted from either Annapolis, Maryland, or Bellevue, District of Columbia, can be received in the astronomical observatories from Europe to Alaska and the Hawaiian Islands. Thus, it is anticipated by astronomers, that in one step the difference in longitude or time between London or Paris and San Francisco or Honolulu can be determined.

**P**RINCIPAL observing stations, selected because of their strategic locations inasmuch as they are at nearly the same latitude and spaced 8 hours apart in longitude, will be at San Diego, California; at the Algiers Observatory, Algeria; and at the Shanghai Observatory, China. The United States will make observations at four stations: Washington, D. C.; San Diego, Calif.; Honolulu, Territory of Hawaii; and Manila, Philippine Islands. The United States Naval Observatory will occupy the two first named observing stations and the U. S. Coast and Geodetic

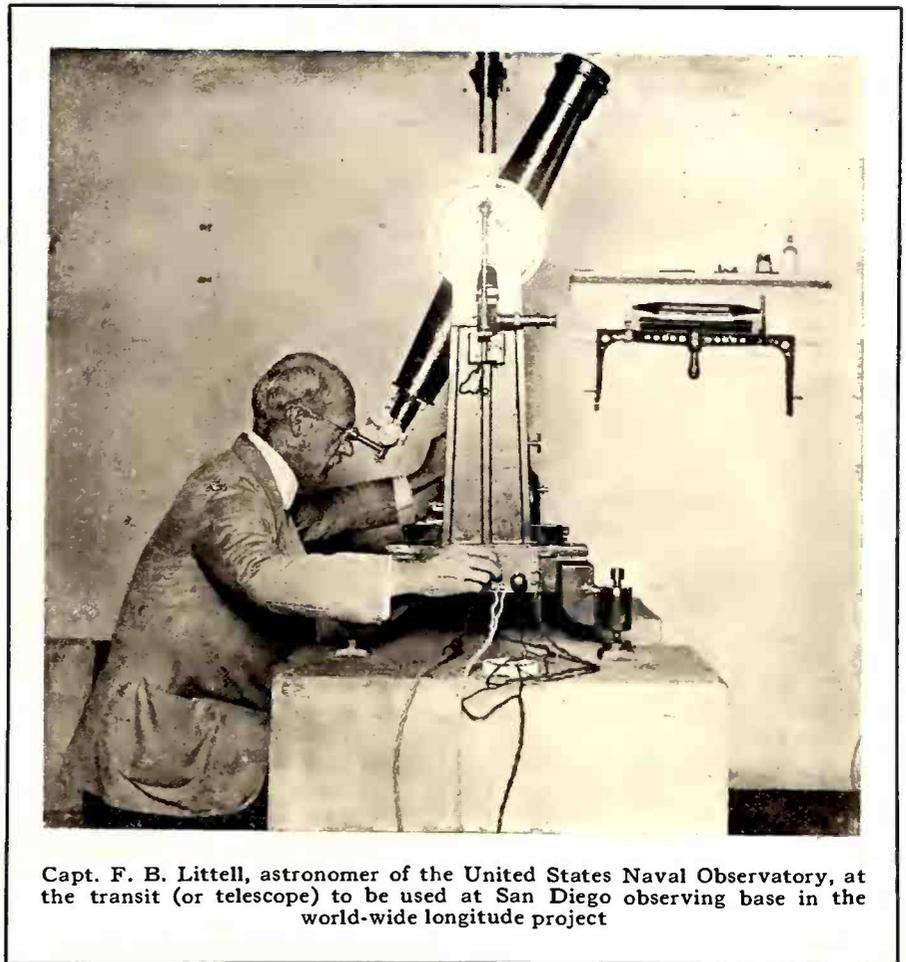

Capt. F. B. Littell, astronomer of the United States Naval Observatory, at the transit (or telescope) to be used at San Diego observing base in the world-wide longitude project

Survey will make observations at the other two stations.

Radio time signals will be sent three times daily during October and November from at least seven powerful transmitting stations, some of which will use both short and long waves. The participating stations and their assigned wavelengths are as follows: Arlington, Virginia, or Bellevue, District of Columbia, 74.7 and 24.9 meters; Annapolis, Maryland, 17,145 meters; Honolulu, Territory of Hawaii, 11,500 and 36.8 meters; Saigon, French-Indo China, 17,000 and 25 meters; Bordeaux, France, 18,900 meters; and d'Issy, near Paris, France, 32 meters.

The observing parties will be equipped with telescopes for reck-

oning time as the stars cross the meridian of the heavens and with radio receiving outfits for picking up the time signals from the transmitting stations. The Naval Observatory has designed a special radio recorder for the purpose, this equipment making an automatic graphic record of the time signals. The Coast and Geodetic Survey will also use an automatic radio receiving device, which records the time signals on a sheet of paper wound around the drum of a chronograph. In another instance, a photographic method will be employed in recording the radio signals. These radio signals will be compared with the local clocks or chronometers.

# The Radio Storm Detector

**N**EWSPAPERS throughout the country recently published the story of the French Government's official cloud painter, an artist who spends his days on the roof of the highest building in Paris gazing into the sky and recording what he sees, with paint and brush. Comparatively few people know that New York City for many years also had a professional sky-gazer, or that the unusual work to which he was assigned is now being done far more effectively by a simple little radio device—the first of its kind in the world. The purpose of our talk tonight is to describe the important part that this little device—known as the "storm detector"—plays in the work of insuring uninterrupted electric service for the largest city in the world.

Let us, for a moment, get back to New York's human sky-gazer and the reason for his job. This man's sole duty was to sit on the roof of the famous Waterside station with a telescope to his eye, looking for heavy clouds foreshadowing a storm or sudden darkness, and to get word concerning the oncoming storm to the man in charge of the generating equipment as quickly and as accurately as possible.

You may wonder why it is necessary to watch the skies so sharply for the first sign of an approaching storm. The answer is that electricity, in such great quantities as are required in New York City, cannot be stored, but must be generated as it is required; yet we must not use any more generating equipment than is really necessary if we are to operate with the high degree of efficiency and economy made imperative under present-day conditions. During a sudden storm in working hours in a city like New York, literally a million people may at the same moment press the button for electric light; our job—which is not always easy—is to see that they all get this light when it is needed.

*Recent Radio Talk Given over WJZ by Arthur Williams, (Vice President, Commercial Relations, New York Edison Co.)*

The generating stations of The New York Edison system have a capacity of approximately a million horsepower, but it would not be efficient operation to generate so much power except when actually needed. That generating station is most efficient which can most accurately anticipate the minute-to-minute changes in the public's demand for current and thus at all times generate enough current to fill the needs of the community and yet avoid any waste of energy.

## Demand May Be Doubled

**D**URING a heavy storm or sudden period of darkness in business hours the demand for current may be doubled within a few minutes. It has frequently been necessary during a storm to increase our service by 260,000 horsepower, and even more, within a few moments. During the total eclipse of the sun several months ago the increase in service demands caused by the turning on of additional lights throughout the city approximated one hundred thousand horsepower. It is not, however, possible to double the output of power in a few minutes. In fact, it takes nearly an hour to get one of our many huge turbo-generators—the machines in which steam energy is converted into electrical energy—warmed up and operating properly. That is why we must know that storm clouds are headed for New York City long before they get here.

The wireless storm detector on the roof of the Waterside station now gives us warning of an approaching storm when it is still fifty miles away, sometimes hours before the storm breaks over New York. Incidentally this little radio device,

unlike other receiving sets, is helped, not hurt, by static, for the atmospheric conditions which cause static are the conditions which operate the storm detector. This detector consists of an ordinary radio aerial, a short-circuiting switch, a spark gap, a coherer, a relay and battery, a bell, and a condenser with a ground connection.

The nerve center of the entire New York Edison system is the System Operator's room at Waterside. Upon the System Operator rests the responsibility for the maintenance of electrical service throughout the city. He must anticipate every demand for service and give the orders which will enable the system to meet it. On the big board before his desk hundreds of little colored lights indicate the condition of every generator and every transmission line; meters show the capacity of the entire system and the current transmitted on the various feeders; a gauge shows the boiler pressure. Behind him is the radio storm detector which apprises him of approaching storms and their accompanying darkness long before a cloud is in sight from any point in New York City. At his desk the System Operator has direct telephone connection with 80 men. At his left a telegraphic system, similar to that used by our fire department, enables him to give any message simultaneously to any or to all of the forty sub and generating stations in the system.

## Storm Rings Bell

**W**HEN a heavy storm headed for New York gets within fifty miles of the city, the wireless detector at Waterside begins to ring intermittently and rather quietly; the System Operator immediately passes word along to the boiler and generating rooms, so that they may get ready to put more generating equipment into use; as the storm gets closer and closer to the city, the radio detector rings louder

(Please turn to page 61)



# Pick-ups and Hook-ups by our Readers



THE material appearing under the title "Pickups and Hookups by Our Readers" in RADIO AGE, is contributed by our readers. It is a department wherein our readers exchange views on various circuits and the construction and operation thereof. Many times our readers disagree on technical points, and it should be understood that RADIO AGE is not responsible for the views presented herein by contributors, but publishes the letters and drawings merely as a means of permitting the fans to know what the other fellow is doing and thinking.

A LARGE number of Washington radio fans are reporting the reception of HHK at Port au Prince, Haiti. The Department of Commerce states this is a government station opened recently, which operates on 361.2 meters and power 1080 watts.

AN UNKNOWN radio broadcasting station in Mexico is reported to be denouncing President Calles almost daily over the air, much to the disgust of his friends and followers. So far it has escaped identification and carries on its propaganda.


REPORTS from England state that British broadcast listeners are urging the transmission of still pictures by radio, so that they may "look in" as well as "listen in" on important events.

A station in London, known as 2VT, has been licensed to project radio movies on 200 meters under the system invented by John L. Baird, but so far no radio prints or pictures have been offered the public. Two systems for broadcasting pictures are said to be in operation abroad, one in Vienna and another in Germany. Over here, C. F. Jenkins is working with the Navy in the broadcasting of weather maps, but no pictures are yet available.

THE Army radio net, which includes the Alaskan cable, has become a very speedy service, as the delivery of two recent messages will attest: A radiogram from Fort Sam Houston, Texas, to the Washington message center was delivered in forty-five minutes, while another transmitted from Anchorage, Alaska, to Seattle via cable, was relayed by radio through San Francisco, and Fort Leavenworth to Washington in one hour and thirty-five minutes.

JAPANESE broadcasting interests have been combined and the Tokyo, Nogoya and Osaka stations will be operated by the Japanese Broadcasting Association. Each station, however, will continue to present individual programs.

FANS who tune in transoceanic stations, or try to do so, will be glad to know the power of those transmitters seems to be increasing rapidly so reception over here should be more practicable. Eighty-one foreign stations are now rated at 1000 watts or over, and twenty-two of them are of 1650 or more watts. The highest powered station listed is Daventry 5XX, rated at 16 KW. It is still on its long wave of 1600 meters but will change to a lower wave about December 1. The next powerful stations are Vienna, Austria, with 7000 watts on 517.2 meters, and the Moscow station of Russia supposed to be using about the same power but on a long wave.

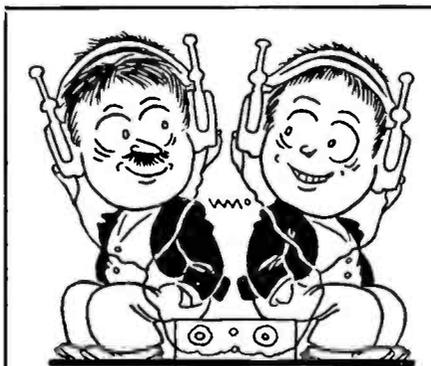

"I didn't know Jones was a college man, did you?"  
"Sure, I was listening in with him when he graduated."

A NEW public wireless circuit between Germany and Brazil has been opened, according to advices to the Department of Commerce. The German transmitter is in Nauen near Berlin, and the Brazilian receiving station is at Rio de Janeiro, but messages are accepted for any and every part of either country. Messages cost 2.75 reichsmarks per word. The opening of this line is expected to aid materially in developing German commercial prestige in South America.

THOMAS KILWIN, 2505 W. Dodier St., St. Louis, Mo., using a home made three tube set, furnishes a list of distant reception that belies the recent chaos which has been observed in the ether lanes.

AT LEAST two broadcasting stations, which have changed their wave lengths from their assigned channels, are now interfering with the weather reports broadcast by NAA, Arlington, Va., on 434.5

meters every morning, afternoon and night. The Navy Department points out the trouble is not so much that listeners ashore are deprived of this official information, but the interference is far more serious at sea where many small craft are not equipped except with ordinary broadcast receivers. Not having regular radio operators who read code, many coast-wise vessels such as tugs, towing barges and pleasure craft, utilize the radio-phone broadcasts from NAA for securing weather and time reports, as well as for picking up news and entertainment. Cooperating with the Department of Commerce, the Naval Communication Service is making an effort to persuade the broadcasters operating in the neighborhood of 435 meters to arrange their program so that they do not interfere with the weather reports transmitted by Arlington at 10:30 a. m., 3:15 p. m. and 10:05 p. m.

### Biggest Flashlight



The biggest flashlight in the world was one of the exhibits at the Sesquicentennial Exposition, at Philadelphia, of the National Carbon Company, Incorporated, makers of "Eveready" flashlights and radio batteries.

This huge flashlight, measur-

ing six and a half feet in length and two and a half feet in diameter, is an exact working reproduction, on a gigantic scale, of one of the popular models manufactured by the company. It is powered, however, from the electric lighting system of the exposition and has a 2,000-watt lamp.

### Automatic Control



SINCE the advent of B eliminators, trickle chargers and other recent accessories to radio sets there has been a need for a simple automatic control. This demand has been met by the issue of the Yaxley automatic power control illustrated above. It is designed for sets using B eliminator and trickle charger. The power control automatically cuts out the trickle charger, cutting in the A battery and B eliminator when the filament control switch on the receiver is turned on. When the switch is cut off the automatic control switches back to the trickle charger after having taken off the A battery and B eliminator.


### Resistance-Controlled Regeneration for Short Wave Receivers

By EDWARD T. HOWELL  
(Radio 9 C V I)

EMBRYONIC hams whose purses are limited, as well as to others whose space is limited, may welcome the fact that oscillation of the detector can be controlled by a simple resistance device instead of by the more expensive variable condenser used in the Weagant and other types of circuits.

A movable tickler of course will control oscillation, but who wants to go back to the old rotating tickler, with which you could tune a station in and out nearly as well as with the tuning condenser, and which caused trouble with the shaft and pigtail connections? Modern plug-in coils also practically necessitate a different fixed tickler with each coil.

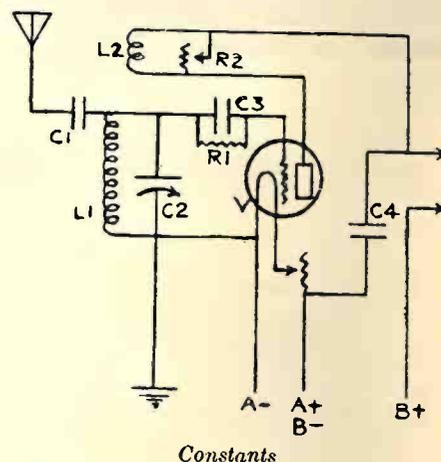The diagram shows the lay-out of the new method. The writer claims no priority for the idea, but merely wishes to present it in a workable form.



- Constants
- V 201A tube.
  - L1 10 turns No. 18 wire spaced. 3 in. diam. (for 40 meter band.)
  - L2 3 turns 3 in. diam. 1 in. from L1. If L2 is wound in same direction as L1, the plate lead comes from top end of L2. (Just the opposite from that shown in figure.)
  - C1 25 mmf. or smaller. (2 pennies about 1/4 in. apart.)
  - C2 100 mmf. variable.
  - C3 100 mmf.
  - C4 2000 mmf.
  - R1 5 megohms.
  - R2 50000 ohm Radiohm.

Advantages of this type of control are that the fixed by-pass condenser of rather large capacity enables a small tickler to be used; no r. f. choke is needed; on turning the Radiohm toward maximum resistance, the tube goes into oscillation with a gentle "plop," fully as smoothly as with the variable by-pass condenser control; there is a welcome freedom from capacity effects which are so noticeable with rotating ticklers; and finally, this particular device seems to make smooth contact at all positions of the lever.

The construction and mounting of the coils is left to the reader. In the receiver under discussion the wire was simply wound on a 3 inch cardboard tube, no particular effort being made toward "low loss" construction. 4's and 5's came in R5 and R6 on a hot afternoon in August with only a ten foot indoor antenna and no ground connection.

\*Past President and former Chairman, Technical Committee. Milwaukee Amateurs' Radio Club.

# New York and London Now Linked by the Speediest Cable in the World

**T**HE New York end of the fastest cable in the world was laid recently at Hammels, Long Island. It links this country with England, by way of Bay Roberts, Newfoundland. The Newfoundland end was landed August 22 and the entire task occupied just three months, for the cable ship *Colonia* set out from Penzance, England, early in June.

This is the nineteenth trans-Atlantic cable and the eighth to be operated across the Atlantic by the Western Union. The cost of laying it was estimated at \$1,000 a nautical mile. Its speed is 2,500 letters a minute, eight times faster than the ordinary cable. This speed is made possible by the fact that the copper conductor is sheathed in a wrapping of permalloy, an alloy of nickel and iron developed in the Bell Telephone Laboratories for the Western Electric Company and having a magnetic permeability many



Uncoiling the sea-earth section of the new permalloy cable off Hammels Beach, near Rockaway. The cable weighs from 20 to 36 tons per mile and the men who handle it on the barge must show considerable dexterity to keep it from getting out of hand

times that of any other known substance.

In contrast to the landing at Newfoundland, when 150 fisher-


men hauled in the shore end through a heavy surf and during a driving rain storm, the landing of the New York end was accomplished under perfect weather conditions — brilliant sunlight and a quiet sea.

A barge took the shore end from the *Colonia* off Staten Island and brought it within about half a mile of Hammels Beach. A large crowd was on hand to watch the picturesque sight of the heavy cable, about three inches in diameter, being floated to the shore on barrels.

A rowboat first came ashore with stout rope to which the cable was attached by steel strands. The rope was wound on a winch set up on a truck about 300 yards up the beach. Then, one by one, the barrels to which the cable was lashed were lowered over the side of the barge. The winch wound away and the glistening black cable started on the last lap of its long journey.

Two deckhands, in trying to keep the bobbing barrels in line, fell out of their dory into the surf, but the water was shallow

(Please turn to page 57)

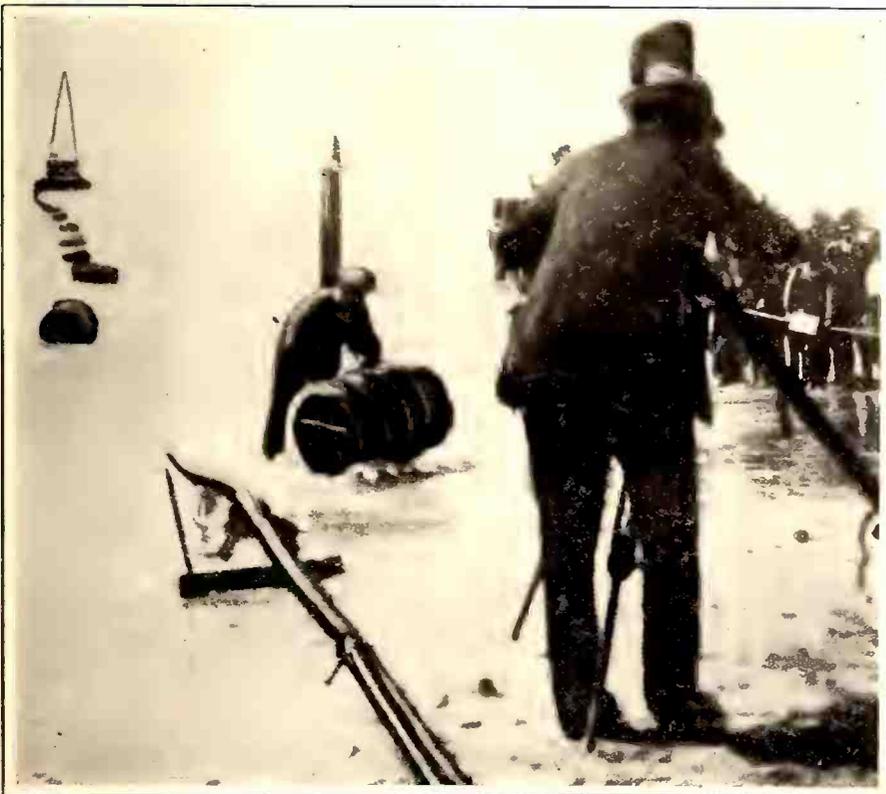

Bringing the shore end of the cable in from the barge by floating it on barrels

# WITH THE MANUFACTURERS




## Power Compact



ABOVE is shown Thordarson power foundation unit for B-elimination and power amplification. It contains a power supply transformer, two filter choke coils, a center tapped filament supply, and two buffer condensers all in one compound filled case. In two types; R-171 for Raytheon tube BH and power amplifying tube UX 171, and type R-210 for UX 216-B rectifying tube and UX 210 power amplifying tube.

Manufactured by the Thordarson Electric Manufacturing Co., Chicago, Illinois.

## Eby's Vernier Dial

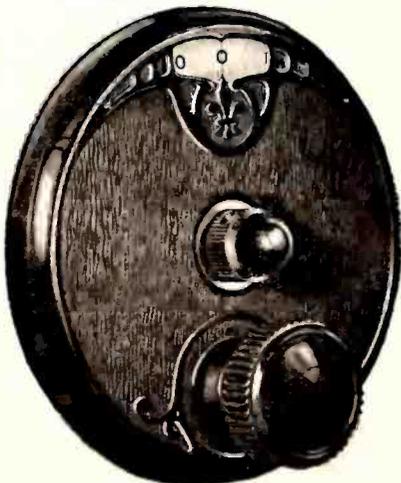


Above is the new shielded vernier dial made by Eby. It has dual range for rotation, and a hair line indicator. It is furnished in only one style as shown

## Walker Promotes New Idea

George W. Walker, of Victoreen fame, has embarked in the manufacture and marketing of an entirely new line of radio products.

The new line will consist of individual units completely assembled and shielded, for use in all popular circuits.

## Klosner Socket

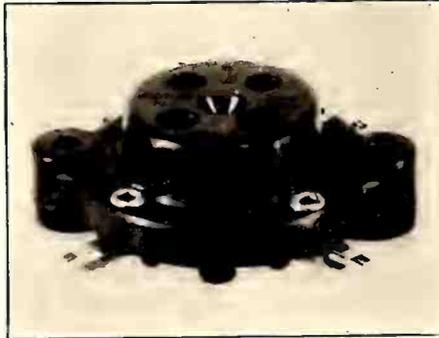

Uniformly tight contact on both the old UV and the new UX type of prongs is claimed for the latest socket issued by the Klosner Radio Corporation, which may be used either on sub-base or base-board construction. Single hole mounting, eyelet assembly and spring grip terminal lugs are noted as features.

## New Radio Company

The Electrophone Corporation, Chicago, manufacturers of Electrophone for the instruction of the deaf, have branched into the radio manufacturing business.


Their first product is a very compact, six tube, single dial control portable receiver, equipped with speaker, unit, loop aerial, tubes and batteries, with a total weight of 28½ lbs. This product is known as the *Hyatt* portable and is the result of years of experience by Ralph E. Hyatt.

E. A. Davenport, formerly Assistant Sales Manager of Jewett Radio Corp., of Pontiac, Mich., has been engaged as Sales Manager of the Radio Division.
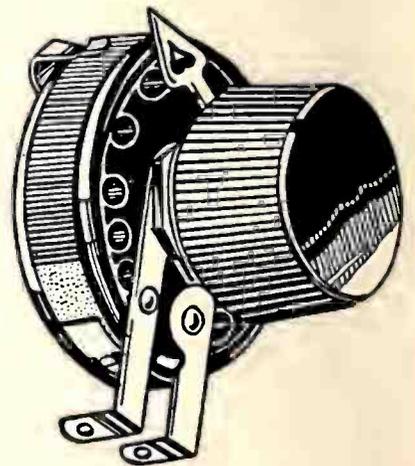
## Want Trade Show

**J**OBBERs of Chicago have united to put on a radio exposition for the trade during the summer of 1927.

A survey made among thousands of dealers to determine the logical time for this trade show disclosed the fact the dealer did not want the show held so far in advance of the season that the manufacturers would have time to copy the popular models of competitors, thus after the dealer had made his commitments he would be forced in the late summer to take on these additional models thereby creating a subsequently larger percentage of dead stock of the less popular cabinets. The majority of dealers prefer a show early enough to permit of selection and delivery in time for the opening of the season and yet late enough to prevent any radical changes being made in models by manufacturers after dealers have made their season's commitments.



Amsco's "Tom Thumb" rheostat is shown above. Efficient design has concentrated a full power rheostat into an inch and a quarter diameter extending less than three quarters of an inch in back of the panel. Single hole mounting.

### Use Aurora Borealis For Line Batteries

THE RECENT mystery at Westinghouse Station WBZ of Springfield and WBZA of Boston which enabled the engineers to talk by telegraph to each other without battery current being supplied to the line has been disclosed.

The two stations operated in synchronism maintain a direct line connection between Boston and Springfield where studios and transmitters are located respectively. This line carries three different circuits as three distinct uses are made of this connection; one for broadcasting, a second for controlling the stations' assigned frequency and the third for telegraph intercommunication.

The telegraph system between WBZ and WBZA is operated by means of simplexing the line, and the battery current must be put on the line at either or both stations to use the telegraph. In the course of an evening's broadcast, the engineers at both stations are constantly in communication by means of the telegraph.

The evening of the mystery was no exception, but during the early part of the broadcast the telegraph instruments kept making signals which the operators could not read. The telegraph line had been receiving the necessary current for maintaining communication from the Springfield station and in order to trace the cause of the strange signals, Engineer Wolfe took the Springfield battery off the line. The meters showed, however, that the line was still receiving current and he signaled Engineer Robinson at Boston and asked if Boston was supplying current.

Engineer Robinson replied in the negative but it was still found that the telegraph system could be operated without current being supplied at either end of the line. At that time, approximately nine o'clock, the Northern Lights were at their greatest intensity and for more than one hour and a half the operators discovered the Aurora

Borealis was supplying sufficient current to operate the WBZ telegraph system. With the disappearance of the Aurora Borealis about 10:30 p. m. the operators were forced to put back the batteries on the line to operate the telegraph.

Another interesting feature caused by the Aurora Borealis during the time this phenomenon of nature operated the WBZ telegraph was the change in the direction of the current which occurred every few minutes.

### Radi-A Unit



RADIO AGE is showing above a new instrument that replaces both "A" battery and charger. It permits operation of any radio receiving set directly from 110-volt alternating current circuit of 50 or 60 cycles. Radi-"A" draws a maximum of about 75 watts from the power line and furnishes a constant, smooth 6-volt current directly to the set at all times, regardless of how long or how often it is used. This instrument operates without hum or distortion and maintains the radio receiver at peak reception at all times.

Radi-"A" is unique in that it is *not* a battery and charger combined in a single unit but is, to the contrary, a complete "A" power unit in itself. The entire operating mechanism consists of five simple units—transformer, Tungar rectifying bulb, electrolytic condenser, choke coil, and automatic switch. These parts are contained in a compact, neat,

pressed steel cabinet which is finished in sepia diamond crystal.

The instrument requires very little attention and contains but one moving part—the automatic switch. The purpose of this switch is to provide automatic control of power within the Radi-"A" as the radio set switch is turned on and off. This automatic relay has a movement of only about  $\frac{1}{8}$  inch and every time it operated, it breaks only a maximum current of  $\frac{7}{10}$  of an ampere and it has double contact points of silver contact metal to prevent sticking and corrosion.

Unlike most other devices designed to serve the same purpose, Radi-"A" does not require a separate switch. Its automatic switch is controlled by the switch of the radio receiver itself. When the set switch is turned on, Radi-"A" is automatically placed in active operation and conversely, when the set switch is turned off, Radi-"A" is likewise shut off.

A further convenience in connection with Radi-"A" is the "B" eliminator plug receptacle, permitting connection of the "B" eliminator directly to Radi-"A" so that both the "B" eliminator and Radi-"A" are controlled at the same time by means of the radio receiver switch.

Radi-"A" is a product of Briggs and Stratton Corporation, Milwaukee, well known manufacturers of automotive electrical equipment. Radi-"A" received its initial introduction to the radio public at the Third Annual Radio World's Fair in New York in September.

It was also shown at the Chicago Radio Show where it met with considerable interest.

### Vernier Dial

W. F. LOUGHMAN, INC., have designed a vernier dial without the use of a cheap material or poor workmanship to cut the price.

The "White Cross" Dialier is a 360 degree dial with a 6-1 ratio. It can be used for both clockwise and counter-clockwise rotating shafts since it is calibrated for 360 degrees.

# Art of Television Not Far Off

## *Soon Will Attach Device to Set, to See Desired Events*

By ALBERT W. FRANKLIN\*

**T**HE radio age is upon us. The electrical age, acknowledged by authorities to be still in its infancy, has been surpassed by the meteoric progress of the art of radio. This progress has in its scope the perfection of one most important invention to humanity—the art of television.

Like the development of the moving pictures, television will follow the perfect transmission of photographs. Just when can be only a matter of time.

At present there are several means of transmitting photographs from one point to another by wire, cable or radio. The various systems of themselves offer no solution to the problem of transmitting moving pictures. Nor has any one as yet proposed what appears to be a commercially feasible and practical solution. From a logical viewpoint just what is the seemingly impossible barrier? Let us consider the systems.

### Caselli's 1856 Method

**O**UTSTANDING advantages of the Belin system, the Bartlane, Hanson, A. T. & T., Leishman, Korn, R. C. A. or Jenkins system as compared to one another, are evident from a brief resumé of their characteristics.

As early as 1856 Caselli sent various designs by telegraphy, using for the transmitter a tin-foil-covered cylinder on which the designs were drawn in insulating compound. A needle acting very much like the stylus of a phonograph served the purpose of a contact pin traveling spirally over the surface of the revolving cylinder. Thus the circuit was made and broken as the lines passed under the contact pin, while at the receiving end, by an electro-chemical action, a similar cylinder synchronized with the transmitter reproduced the designs directly.

Discovery of the effect of light on the electrical resistance of selenium became known in 1873 and shortly afterwards various schemes to substitute selenium for Caselli's process were attempted. The most noteworthy were those of Semlocq and Pero-sino in 1878. After quite a lengthy interval Korn (in 1904) employing Semlocq's plan with several modifications, succeeded in transmitting photographs a few hundred miles. The method now in use by the R. A. C. is to place a negative of the photo on a glass cylinder. On this is focused a very narrow beam of light used as a stylus. By reflecting the varying intensity of the light passing through the cylinder the registry is effected and then follows an amplifier system which then allows the photo to be reproduced in several ways: either by a tape recorder which records the photo as a continuous line of dots and dashes; by means of a relay which operates a special pen and reproduces a pen and ink sketch, or by means of photographic reproduction, a light shutter being controlled by the current variations and controlling the light from a lamp focused on a sensitized rotating cylinder.

### Belin Full of Originality

**W**ITH such a system successful photo transmission has been accomplished by radio transmission from London to New York.

The first photo which was transmitted over the Atlantic was sent by a system based upon the half-tone method of screening. The photo was automatically divided into a predetermined number of dots per square inch. A photo-electric cell then determined into which of eighteen groups a dot belonged, each group being given a distinguishing letter. By means of special relays, the letter was automatically transmitted and at the receiving

station, the letter was converted into a dot and placed into its proper position in the photograph. Even though the photo was converted into 12,000 squares, much of its detail was lost. A more nearly perfect system is the Leishman process which employs a similar but modified principle and operates on trans-Atlantic cables.

Perhaps the most original scheme is that developed by Belin. His process resolves itself upon the fact that bichromated gelatin becomes insoluble under strong light—his own discovery. Thus he places a film of wet gelatin under a negative whereupon the portions of the film swell up more or less in proportion to the intensity of exposure. This forms a sort of relief map of the negative and is wound on a cylinder over which a stylus traces its path. A microphone attached to the stylus varies the resistance of a local circuit which is coupled to a transmitter. At the receiving station an oscillograph has its mirror deflected, altering the projection of a beam of light focused on a synchronized rotating cylinder having a sensitive photographic film on it.

### How Jenkins Does It

**J**ENKINS' method of analyzing is based on aberration by means of prismatic rings. These rings are of glass, the edges ground in such a manner that a beam of light passing through is given an oscillating motion. By means of two such rings geared at a predetermined ratio, a negative is explored in minute strips, and a photo-electric cell employed to convert light into electrical values.

The Bartlane system is a coding process which operates by a printing telegraph. Holes are punched into a tape and reproduced at the receiving end by passing the type in front of a beam of light. Synchronism is

\*Chief Engineer, Chas. Freshman Co., Inc.

maintained by holes punched into the tape alongside the coding group.

By this time you may have noticed that there are two distinct classes into which we can place photo-transmission—the purely physical transmission, such as the Bartlane, Leishman and Korn systems, and the purely modulated electrical or radio transmission, such as the R. C. A., Jenkins, Belin and A. T. & T.

Of these the modulated systems stand the better change of development into practical television. It is, however, very doubtful that any one system will not be radically changed so this may be realized. Near perfection has been achieved in single photographic transmission. The average time it requires to transmit a good picture is about ten minutes. Since all the systems require that the photo be analyzed into minute strips—about 1/100" wide, this precludes the possibility of resolving the same procedure into a practical solution.

For motion pictures we need sixteen pictures per second. Our nearest approach to television is one picture every ten minutes, unless recent claims from London of ten every second are correct. There is such a wide gap that all methods proposed up until the present time have failed.



However, with such marvelous inventions as the photo-electric cell, the Thalofide cell (one converting the light energy into electrical energy, the other acting as a varying resistance controlling the current in the circuit), the Moore lamp capable of responding to very high frequencies and which may play an important part in future development work, and the prismatic rings of Jenkins, we may expect a swifter solution.

The present day receiver is so far advanced in engineering design, that it will not be obsolete for many years to come. Thus, it may be entirely possible to equip the set with a "televisor," as we can aptly call the device, and have at our leisure and pleasure, not only all the latest news and best entertainment, but also the very portrayal of the events as they transpire!

THE NEW SHIELDED HAMMARLUND ROBERTS Hi-Q\*

\$63<sup>05</sup>

CABINET EXTRA

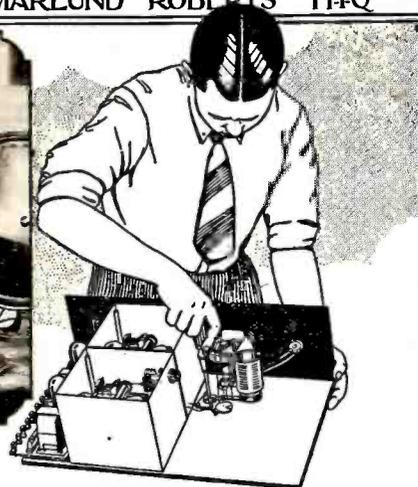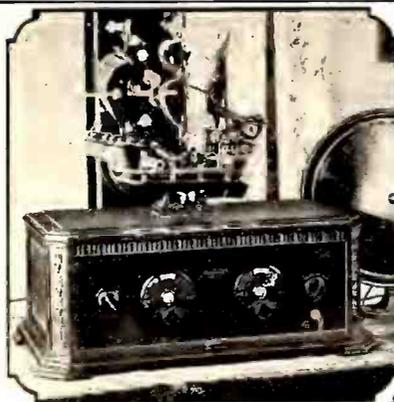

Build this New Shielded Hammarlund-Roberts Hi-Q\* Receiver

Designed by Leading Engineers Includes Every Modern Feature

THE New Shielded Hi-Q Receiver incorporates every modern feature, including Automatic Variable Coupling, through which the same control operates tuning condenser and primary coil simultaneously. This gives maximum and equal amplification over the entire tuning range.

You know, of course, that the point just below oscillation is the point of greatest selectivity and efficiency. Now, through Automatic Variable Coupling, the Hammarlund-Roberts Board of Engineers have secured this maximum effectiveness—not on just a small section of the wave band, but over the entire range! This advanced idea gives a degree of selectivity and undistorted tone-quality which is totally new in radio.

Parts for the Hi-Q have been selected not only for their individual quality, but because of their perfect synchronization. In high detection frequency, in high power output, in clarity of tone—in every department of reception, its 5 tubes equal the 8 of most factory-made receivers costing upwards of \$150.00.



The Foundation Unit Consists of drilled and engraved Micarta panel and sub-panel and all necessary elements to start building. Everything marked.

\$10<sup>50</sup>

- Associate Manufacturers
- Benjamin Electric Mfg. Co.
  - Carter Radio Co.
  - Durham Resistors
  - Eby Mfg. Co.
  - Hammarlund Mfg. Company
  - Martin-Copeland Co.
  - Radiall Company
  - Samson Electric Co.
  - Sangamo Electric Co.
  - Westinghouse Micarta



Get This Book

This wonderful book written under the supervision of the same ten famous engineers who built the Hi-Q Receiver contains the simplest instructions ever put into print. Get a copy to-day and learn how to have a marvelous radio at very low cost.

25c



\* High ratio of reactance to resistance. High ratio — Great selectivity — Loud signals.

Hammarlund—Roberts, 1182-D Broadway, New York City

RADIO AGE SUBSCRIPTION BLANK

Radio Age, Inc.  
500 North Dearborn Street  
Chicago

\$2.50 A YEAR

Gentlemen: Please enter my subscription for RADIO AGE, the Magazine of the Hour, for one year, beginning with the ..... issue, for which I enclose \$2.50.

Name .....

Street Address .....

City .....

State .....

Send cash, money order or draft.

(12-26)

**See that screw**

**A SCREW DRIVER  
ADJUSTS AN XL  
IN CROWDED  
PLACES**



**RESULTS** in easier tuning, more distance, volume and clarity—greater stability. Indorsed by leading radio authorities.

Model "N"  
A slight turn obtains correct tube oscillation on all tuned radio frequency circuits. Neutrodyne, Roberts two tube, Browning-Drake, McMurdo Silver's Knockout, etc., capacity range 1.8 to 20 micro-micro farads. Price \$1.00

Model "G"  
With grid clips obtains the proper grid capacity on Cockaday circuits, filter and intermediate frequency tuning in heterodyne and positive grid bias in all sets.



Capacity range: Model G-1 .00002 to .0001 MFD. Model G-5 .0001 to 0.005 MFD. Model G-10 .0003 to .001 MFD. Price \$1.50

**X-L Push Post**  
Push it down with your thumb, insert wire, remove pressure and wire is firmly held. Releases instantly. Price 15c. Also furnished seven to a strip. Nicely marked in white with seven standard markings. Price \$1.50.

Information on Request

**X-L RADIO LABORATORIES**  
2424 N. Lincoln Ave. Chicago, Ill.

Centralab Radiolms, Modulators, Potentiometers or Rheostats are standard on 69 leading radio sets. Ask your dealer, or write for descriptive literature.

**CENTRAL RADIO LABORATORIES,**  
24 Keefe Ave., Milwaukee, Wis.

**Centralab**



**Blue Prints**

**FREE** Write for a complete description of the Peer of all receivers—the World's Record Super 8, 9 and 10 the wonder receivers that hold 4 fully verified World's Records for distance. The World's Record Super is one of the few receivers to bring London into Chicago during the last two International Contests. Thousands of testimonials hail the World's Record Super 8, 9 and 10 as the marvels of Radio. Write for free list of records and testimonials today!

**Easy to Build**

You can build an exact duplicate of the original World's Record Super models by following our Blue Prints. Building instructions complete in every detail with each set of Blue Prints make it easy for anyone to build this remarkable receiver with perfect success. Complete Building instructions and Blue Prints \$5.00. Remit with order or we will send C. O. D.

**Mail the Coupon Today!**

**M-S SYNDICATE**

Box 2131, Cleveland, Ohio

M-S SYNDICATE,  
Box 2131, Cleveland, Ohio  
 Please send me free literature and verifications of the records made by the World's Record Supers.  
 Am enclosing \$5 for Blue Prints, etc.  
 Send me Blue Prints, etc., C. O. D.

NAME.....  
ADDRESS.....

**Design and Manufacture of Resistor Units**

(Continued from page 20)

Second, it is comparatively easier to put a protecting layer over the conducting filament. Third, it is easier to make measurements of the conductivity of the coated fibre as the fibre is fed out of the coating machine. The ease of measurement obtained in the case of the fibre insures a uniform product.

After the conducting coating has left the furnace it is next coated with durable protective film of insulating varnish which is then thoroughly dried by the application of heat. This impenetrable coating completely protects the conducting filament against atmospheric changes.

As the coated glass filament passed through the various stages of manufacture, its resistance per unit length is continuously tested. Literally, there is no inch of this fibre which has not been measured for resistance.

After the wire has passed through the measuring devices it is cut automatically in two foot lengths. It is then kept in sealed tubes until it is required for assembling the complete unit. Finally the wire is cut into lengths approximately 1 3/4" long and mounted in a glass tube with brass caps at two ends.


A new form of power resistor has recently been developed by the engineers of the company. In this type of unit the filament is wound into the form of a helix, the diameter of this helix being exactly the outside diameter of the enclosing tube. The two ends of the helix are embedded in an alloy within the caps. The helix permits the use of a very long heavily coated fibre in a very small space. With this device it is possible to dissipate from two to five watts depending upon the size of the unit with less than ten per cent variation in the resistance of the unit.

The alloy in which the filament is embedded in the caps, is the result of innumerable experiments. Its properties are such that it makes perfect electrical contact with the filament. The cap grips the contacting filament

so tightly that it is impossible to pull the filament out without shattering it. It is almost as if the cap, filament and alloy were made of one piece.

After the resistors are assembled they are again tested. The resistance units are normally made within a five per cent variation. On special orders it is quite possible to make them within two and one half per cent.

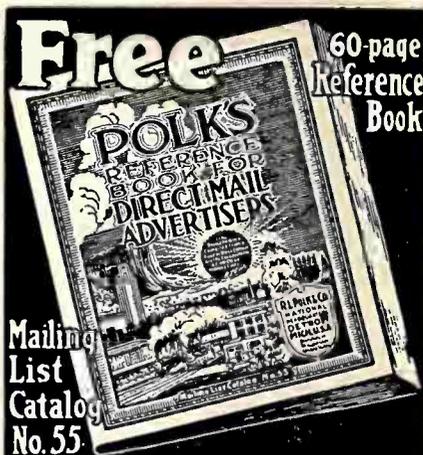All the meters used in the manufacture and assembly tests are constantly checked against laboratory standards. Production lots of samples are also tested periodically in a three stage amplifier to make certain they are noiseless.



Mailing List Catalog No. 55

**POLK'S REFERENCE BOOK FOR DIRECT MAIL ADVERTISERS**

Shows how to increase your business by the use of Direct Mail Advertising, 60 pages full of vital business facts and figures. Who, where and how many prospects you have. Over 8,000 lines of business covered.

Write for your FREE copy.

**R. L. POLK & CO., Detroit, Mich.**  
599 POLK DIRECTORY BUILDING  
Branches in principal cities of U. S.

**PATENTS**

**To the Man with an Idea**


I offer a comprehensive, experienced efficient service for his prompt, legal protection and the development of his proposition.

Send sketch of model and description, for advice as to cost, search through prior United States patents, etc. Preliminary advice gladly furnished without charge.

My experience and familiarity with various arts frequently enable me to accurately advise clients as to probable patentability before they go to any expense.

Booklet of valuable information and form for properly disclosing your idea free on request. Write today.

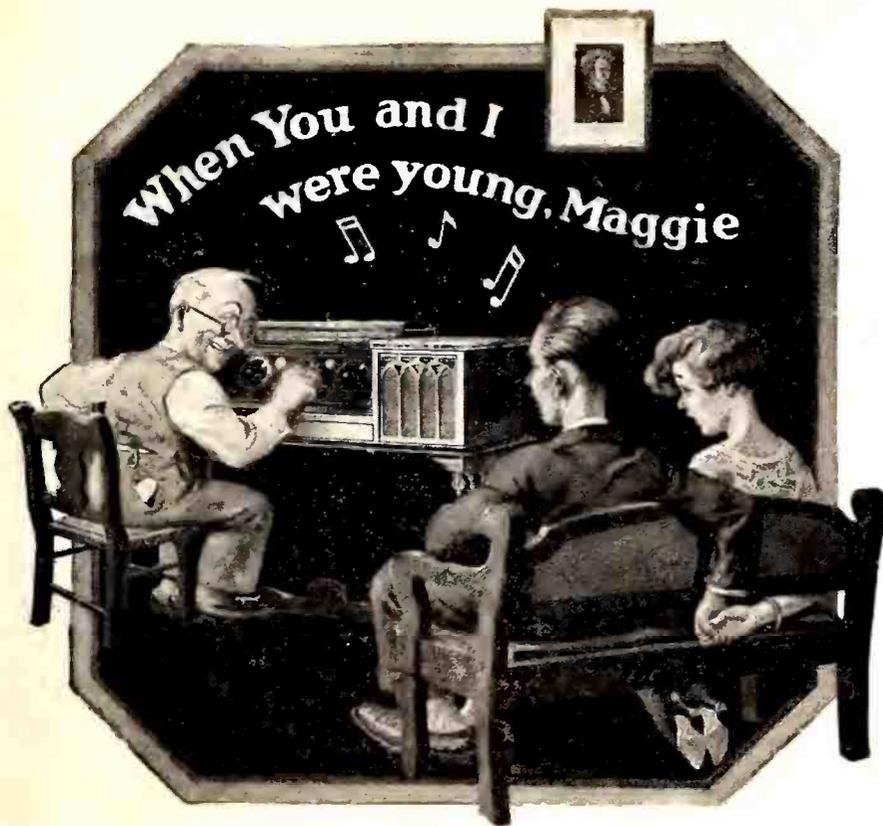**RICHARD B. OWEN, Patent Lawyer**  
81 Owen Bldg., Washington, D. C.  
41-M Park Row, N. Y. City



## Many Are Being Fooled in Radio By Believing Service Unnecessary

ANY radio, no matter what its price may be, nor who makes it, will only be as satisfactory as the trained service behind it.

In buying a radio there are a number of important things to consider—

APPEARANCE—  
TONE—  
VOLUME—  
DISTANCE—  
EASE OF TUNING—  
and last but far the most important—  
SERVICE.

Tone and Volume can very easily be determined by listening. The only real way to prove distance and ease of tuning is by operating the instrument yourself, but the quality of service must be determined only by careful investigation.

Far too often it seems customary to claim that radio service is unnecessary. For four years this company has been building a factory trained service organization until today it consists of 4364 men who know Ozarka instruments in every detail. These men have been trained directly under Ozarka Engineers, the men who originated and developed Ozarka Instruments.

You'll find it well worth your time to investigate this organization before you decide on your radio. A trained Ozarka service man is near you—why not discuss this matter with him?

When anyone tells you that radio service is not necessary, think it over, your own good sense will tell you differently. You have a right to receive from your radio consistent operation, night after night and year after year—the right service by a service man who knows how, will guarantee you that lasting satisfaction you are entitled to.

The claim that service will not be necessary is the poorest type of salesmanship—it only leads to dissatisfaction later—far too often it is used to cover up the fact that the seller is not in a position to deliver service.

In the past, the selling of radio instruments has depended largely on having stock on hand to deliver—in the rush to buy very few paid any attention to what service could be delivered in case any little trouble came up.

Today, service in radio is not only being recognized and demanded but people who know, go even farther and demand—service by factory trained men.

You would never consider letting any all round mechanic repair your car—then treat your radio in exactly the same manner. Demand not only service but the service of men who know—the day of the radio wizard who knows all radio instruments is gone—the factory trained service man has taken his place.

# OZARKA

INCORPORATED

120 W. Austin Avenue B

CHICAGO, ILL.



\$132.50 F. O. B. Chicago. Ozarka Senior 5 Tube Model complete with Loud Speaker and all accessories. Also built in a 7 Tube Model



\$100 F. O. B. Chicago. Ozarka Junior 5 Tube Model complete with built-in speaker and all accessories.



\$215 F. O. B. Chicago. Ozarka Console 5 Tube Model, solid walnut cabinet, complete with all accessories. Also built in a 7 Tube Model

## We have a few Openings for the Right Men

WHILE there are today 4364 Ozarka representatives, some territory is still open. We want men who believe in the future of radio—men who are tired of working for some one else—men who would like to add to their present income by devoting their evenings to Ozarka.

At the start you can keep your present position. Later on, after you have proven what you can do, then you will give us all your time because it will pay far more than your present position.

The man we want may not have much money but he is not broke. He has lived in his community for some time—he has a reputation that his word is good. He may not have made any startling success but he has never "put over something" just to make money. He may know nothing about radio or salesmanship but he will be successful if he is willing to study what we are willing to teach him, without cost.

The field in radio is wide open for the trained man. The success of the 4364 Ozarka representatives proves what men can do. If you are interested, ask for a copy of the Ozarka Plan, a 100 page book which tells a true story of how big money and a permanent business can be built in radio. It is a story of life; of why some men fail while others succeed. This book has shown many men how to start making extra money immediately and within a very short time establish a business of their own.

## Cardwell Condensers



"The  
Standard  
of  
Comparison"

**T**HE Sixth Christmas of the Cardwell Condenser, the basic design of which has never been radically changed, finds its popularity undimmed.

The Type "C" has the Ideal Tuning Curve, starting at straight frequency and increasing to straight wave length. The Taper Plate Type "E" is midway between straight frequency and wave length.

Write for our 36 page booklet

Allen D. Cardwell Mfg. Corp.  
81 Prospect St., Brooklyn, New York

## ERLA

## Fixed Crystals



## Finest and Most Dependable Made

Erla crystals still reign supreme for use in any circuit employing a crystal detector. Super-sensitive, permanently adjusted, assuring full volume at all times. Ideal for reflex sets.


Buy this better crystal at your dealer. If he cannot supply you, we will send it prepaid to any city in the United States for only \$1.00.

**ELECTRICAL RESEARCH  
LABORATORIES**

2500 Cottage Grove Ave., Chicago, Ill.

Get your copy of the  
1926 Annual

## Operates Phonographs Elec- trically

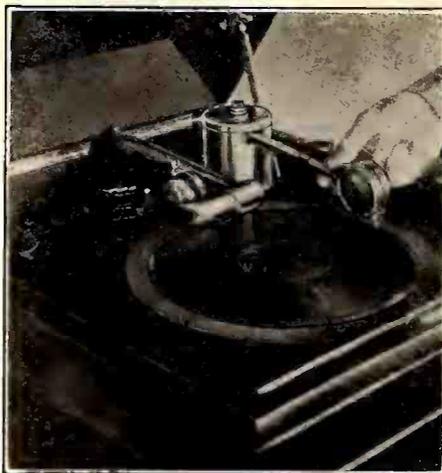

Richer and smoother tone is claimed for the device illustrated above which replaces the regular tone arm and horn on a phonograph and which operates the old style phonograph electrically. Amplification is secured either through the horn itself or for greater volume with the aid of a good power amplifier stage.

### On Air Again

**S**TATIONS WIOD and WMBF of Miami are again on the air with their regular programs. In fact WMBF began broadcasting the Saturday following the recent storm, with an improvised aerial and was soon reported as heard in Portland, Me. WIOD was also early in its return to the air.

### Chief Operator



Walter R. Lindsay, recently appointed Chief Operator of Station WMAQ at Chicago, who is an old time sea-going "op".

## Death Ray Tube Turns Gases Into Solids

(Continued from page 12)

rays or electrons. The penetration of the rays depends not only upon the voltage but upon the density of the substance they strike, so that with most solid substances the penetration is slight, and with dense metals almost negligible.


### Startling Experiments

**O**NE of the most startling experiments performed with the new tube has been the production of a yellow compound when the rays are passed through acetylene gas. This compound, similar to that produced in very small amounts by radium treatment of the colorless gas, can be produced in relatively large quantities with the cathode ray tube either as a light, fluffy powder or as a varnish-like film on substances within the gas chamber, depending upon the electrical conditions. The compound has been found to be insoluble in all the many chemicals so far tried. It seems, therefore, that a protective coating for metals, to which it adheres tightly. Other substances, such as castor oil, can also be solidified by exposure to the rays.

In ascertaining the effect of the rays on living tissues, small circular areas of the ear of a gray rabbit were subjected to short exposures to the rays. Exposure of a tenth of a second caused a temporary loss of hair over that area. When the exposure on another area was increased to one second a scab was formed. When this fell away it took the hair with it, and weeks later the area became covered with a profuse growth of longer, snow-white hair. Exposure for a minute resulted in the formation of a scab on each side of the ear. A hole was left in the ear when the scabs fell away, and the edge later became fringed with white hair. In other experiments, bacteria and flies were killed almost instantly by the rays.


A crystal of calcite, a colorless and transparent mineral, glows with a bright orange light if sub-

(Please turn to page 52)

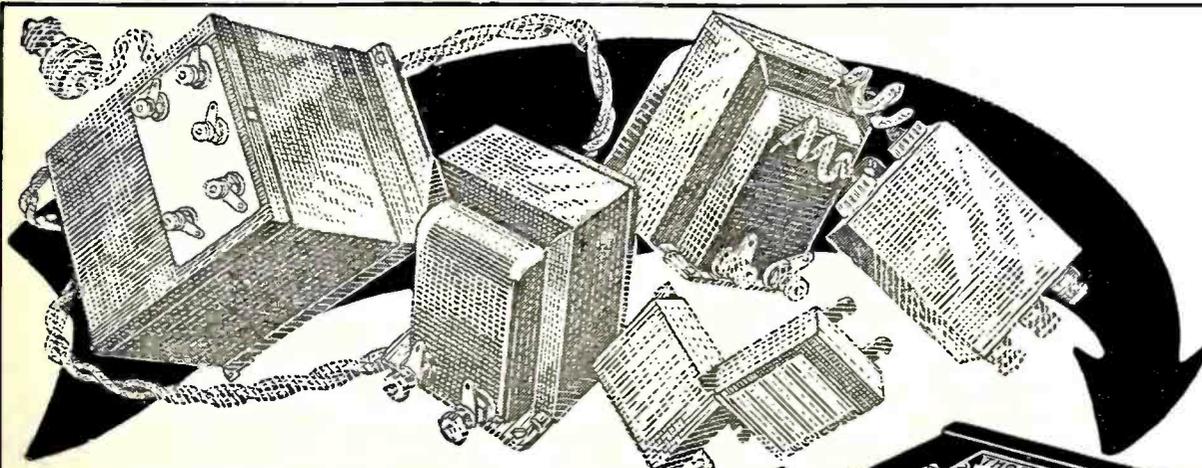

# All in One!

## THORDARSON POWER COMPACT

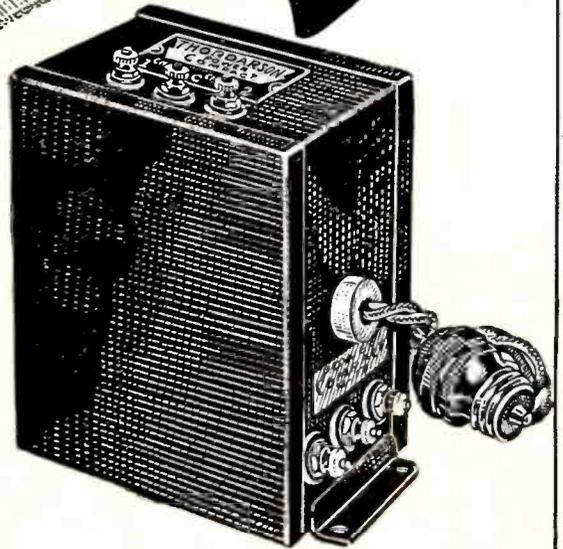

### TYPE R-171

Contains a power supply transformer for Raytheon BH rectifier, 2 filter chokes, 2 buffer condensers, and a filament supply for UX 171 power amplifying tube.

\$15.00

### TYPE R-210

Contains a power supply transformer for UX 216-B rectifier, 2 filter chokes, and a filament supply of 7½ volts for UX 210 power amplifying tube.

\$20.00

## The Complete Foundation Unit for power amplification and B supply

**Simplified Assembly.** The Power Compact contains within itself the greater part of the complete B supply unit. With the Type R-171, only 14 leads complete the Raytheon assembly. All terminals are carefully located for the greatest ease of assembly.

**Compactness.** The only additional apparatus required to build the B supply are the condenser block (Raytheon type), a Raytheon tube BH, and the resistance units. The complete eliminator occupies a space of but 6 in. x 9 in. without crowding.

**High Efficiency.** The power supply of either Power Compact furnishes the proper current for maximum efficiency of the rectifiers used; the chokes are of sufficient capacity to carry the maximum output. Conservatively rated, will not heat up in continuous service.

**High Voltage Output.** The R-171 Power Compact assembly will deliver a maximum plate voltage output of 300 volts at 30 milliamperes, or 275 volts at 40 milliamperes.

The R-210 type assembly will deliver 400 volts to the plate of the power tube, and in addition, will supply a constant 90 volts to the receiver at any current drain up to 40 milliamperes.

**Silent in Operation.** There is no traceable hum, either mechanical in the compact itself, or electrical through the loudspeaker.

**Complete Supply for Power Amplification.** The Power Compact not only supplies B voltage, but also provides for the filament current and grid bias of the stage of power amplification. *Makes it possible to use power amplification even on sets designed for dry battery operation.*

**Electrically Centered Filament Supply.** The power tube filament supply is tapped at the exact electrical center for grid return. The center tap is taken from the common lead of two perfectly balanced windings—completely obliterating the A. C. hum. (An exclusive Thordarson feature.)

Write for instruction booklets SD-49 and SD-50.

If your dealer cannot supply, order direct from the factory.

**THORDARSON ELECTRIC MANUFACTURING CO.**  
*Transformer Specialists Since 1895*  
**WORLD'S OLDEST AND LARGEST EXCLUSIVE TRANSFORMER MAKERS**  
*Huron and Kingsbury Streets — Chicago, Ill. U.S.A.*

# Types of Rectifier Tubes Discussed

By FRANK L. EICHNER

**I**N THE past year, the B Battery eliminator has become a fact rather than a passing fancy. More and more radio set owners are acknowledging the fact that a good eliminator is better than the longest lived B batteries. The power is always there and beyond the cost of running it from the house current, there is no appreciable upkeep.

A word at this time on the subject of rectifier tubes may be of interest to the man who has an eliminator or to the fan who intends to build one.

There are two distinct types of rectifier tubes—the filament and the non-filament gaseous tube. I shall discuss the filament type first.

The filament type tube may be divided into two classes—half-wave and full-wave. There is only one full-wave, filament type tube at present on the market. This is the Rectron UX213. The characteristics of this tube are listed below. The tube contains two separate plates and two filaments which are connected in parallel.

Here are the operating characteristics:

Filament voltage—5 volts




Radio Corporation's 216-B Rectifier

Filament current—2 amperes.

Maximum plate voltage (A. C.)—220 volts per anode.

The capacity of this tube is 65 milliamperes the voltage dropping with the load at the output.

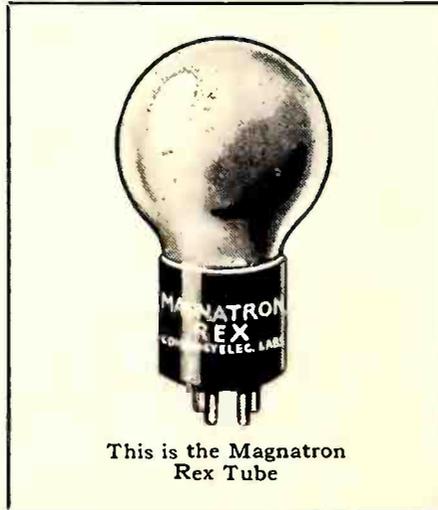The half-wave rectifier tubes are more numerous. There is the Rectron UX 216-B, the Magnatron "Rex," the Perryman



This is the Magnatron Rex Tube

Rectifier and many others. I have only tried the tubes named, however, and I shall confine myself to a brief description of them.

The Rectron UX216-B is lighted from a 7.5 volt source and draws 1.25 amperes. The maximum A C voltage which can be applied to the plate is 550 volts. It will pass 65 milliamperes and when more than this is required, two of these can be connected for full-wave rectification. An A. B. C. power unit for 199 type tubes can be made with two of these tubes if the filaments of the 199 tubes are connected in series.

The Magnatron "Rex" has some of the characteristics of the 216-B with the exception of the plate voltage. The maximum voltage used by the author was 300 volts.

The Perryman tube draws 1.125 amperes at 5 volts and will pass about 40 milliamperes.


300 volts was also used on this tube. The "Rex" tube will pass about 50 milliamperes. These tubes can also be used for an A. B. C. power unit as explained above.

Now for the gaseous tubes. The oldest gas filled tube on the market is the "S" tube. This tube has no filament, and is a half-wave rectifier. It will pass 50 milliamperes and can be used at high voltages.

Newer and with more simplicity of construction are the Raytheon tubes, types B and BH.

The type B tubes have a maximum plate voltage of 250 volts per anode. Both tubes, by the way, are full-wave rectifiers. The type B has a maximum current of 60 milliamperes. The type BH will take 350 volts per anode and will pass 85 milliamperes. Ere this time, most radio magazines will have published full specifications for an A. B. C. power unit, using this tube.

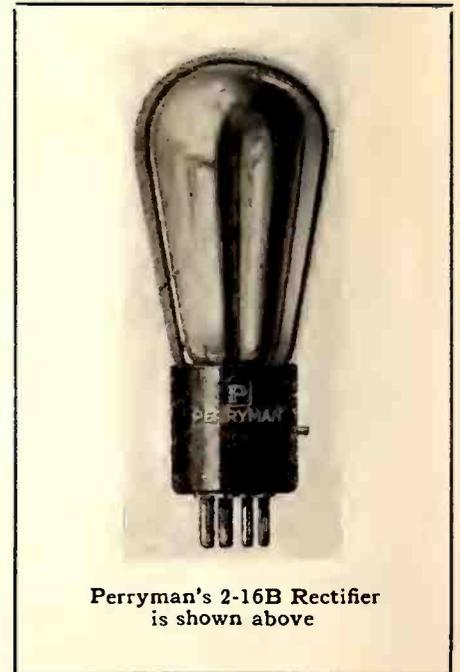A word on the operating principle of these tubes. They operate on the "short path principle" whereby a rarified gas acts as an insulator between surfaces which are close together. If the space between the anode and cathode is short



Perryman's 2-16B Rectifier is shown above

enough and a suitable gas is used at a very low pressure, an electron will pass between these points without danger of encountering molecules of gas and of ionization by collision. Therefore, the helium gas which is used is made to act as a perfect insulator at low pressures.

The filament type tubes are eminently satisfactory as rectifiers, but the fact that large filaments and plates are necessary create what is known as "back current" and this increases the load on the filter circuit, making the filtering out of the A. C. hum almost an impossibility.

The relatively small surfaces in the Raytheon tubes reduce the "back current" to a negligible quantity, thus giving increasing ease in eliminating the A. C. hum.

I hope that the foregoing data may answer the needs of those fans who are about to build or to buy an eliminator. Most units using Raytheon tubes are sold with the tubes as a part, but in the filament type rectifiers the builder or buyer is generally left to his own devices.

**New Type Reproducer**



A physician and an army officer have discovered what is stated to be a new method of sound amplification represented in the reproducer shown above. Its inventors have taken a leaf from Nature's notebook and followed closely her mechanism for sound amplification.

# PROVED!

**FORTY** Thousand Tests on different sets have proved the satisfactory performance of the good Ferbend "B" Eliminator. 40,000 Ferbend "B" Eliminators are now in use. This wonderful instrument is in its second successful year of usefulness. Until you have used a Ferbend "B" Eliminator you have not known the ultimate in radio enjoyment.

The satisfaction of Ferbend owners is proved again and again—every day of every month—by the steady flow of hundreds of unsolicited testimonial letters from users of this very fine instrument. The few reproduced here are merely examples of what every mail brings from all sections of America. This flow of testimonials proves beyond a doubt the splendid performance, reliability, convenience and long-lasting qualities of the Ferbend "B" Eliminator. "No Hum"—"More Volume"—"Less Static"—"More Clarity"—"Complete Satisfaction." These reports from users are repeated again and again all through the testimonials. They prove the Ferbend "B" Eliminator is "over the top" to say.

**USERS ARE ENTHUSIASTIC**

Fort Riley, Kans.  
Am getting wonderful results with my Eliminator and good reports from those I have sold.  
Floyd M. Farwell,  
WIRE CHIEF, Sig. Det.

Ambridge, Pennsylvania  
We are more than delighted with your Eliminator. Have had it since February and have had splendid results.  
F. L. McGRAW.

Petaluma, Calif.  
I am highly pleased with your Eliminator. It will out-perform any "B" Eliminator on the market today. I have demonstrated it to friends owning Eliminators costing \$50 to \$75 and they all agree with me.  
Ralph J. Me.

Dryden, Ont.  
I am more than pleased with your "B" Eliminator and there is no doubt about it being better than any wet battery on the market.  
D. M. Kentner.

Montreal, Quebec, Canada  
I have sold all six of your "B" Eliminators and every one is pleased with it. It is one of the best on the market regardless of price.  
Alfred A. Michand.

Yankton, So. Dak.  
Our Eliminator has served its purpose wonderfully and we enjoy our radio very much since we received it.  
Gust. Rindquist

New Orleans, La.  
The "B" Eliminator I purchased from you some time ago is very satisfactory and I am much pleased with it.  
W. M. Kline.

Mt. Morris, N. Y.  
The "B" Eliminator purchased months ago has given more than best results. Would not part with it for anything.  
Frank J. Huver.

Amsterdam, N. Y.  
The Eliminator is great. Have advised all my friends to get it for I know none could work any better or give more satisfaction.  
Reg. Firth.

Brooklyn, N. Y.  
I highly recommend your Eliminator to anyone regardless of the kind they expect to buy. Have had mine for over a year.  
W. G. Stein.



**\$12.50**

**COMPLETE**

Nothing else to buy. Replaces "B" Batteries. Operates direct from Electric Light Socket on 110-120 volt A.C. lighting circuit. Delivers up to 100 volts.

## FERBEND "B" ELIMINATOR

### Within Reach of ALL

Second successful year—40,000 in use. Amazingly low in price—amazingly high in performance. An unequalled value in radio. Equal or superior to any "B" Eliminator regardless of price. We made this claim over a year ago. Today this statement still stands true—proved by overwhelming evidence.

### NEW IMPROVEMENTS

developed and perfected by the Ferbend Electric Co., now give even greater lasting satisfaction to Ferbend users. New solution and new special alloy electrodes make possible a perfect electrolytic rectifier having longer life than any other type of rectifier.

**FERBEND Wave Trap**

This Company also manufactures the famous Ferbend WAVE TRAP—the instrument which has been widely imitated but never equalled. It is the only original and genuine. Priced at

**\$8.50**

**Ask Your Dealer—or Send Direct**

If you prefer, we will make shipment direct to you upon receipt of price, or C. O. D. if desired. Use for 10 days to convince yourself—if unsatisfactory, write us within that time and purchase price will be refunded. Use coupon now.

THE FERBEND "B" ELIMINATOR is approved and passed by the rigid Laboratory Tests of Radio News, Popular Radio and Radio Broadcast.

FERBEND ELECTRIC CO., 431 W. Superior St., Chicago, Ill.

**MAIL THIS COUPON TO-DAY!**

FERBEND ELECTRIC CO., 431 W. Superior St., Chicago

Send at once. Payment enclosed.  Send C. O. D.  Send Literature

Name.....

Address.....

City..... State.....

Please Mention Radio Age When Writing To Advertisers.

# \$50<sup>00</sup>

## Cash Prizes

Every Month in

## RADIO AGE

To encourage our readers in developing their ideas along radio, electrical, mechanical or scientific lines, Radio Age will offer each month two prizes of twenty-five dollars each for the best new and original stories or pictures, or both, submitted to its Editors covering the fields of radio, telegraphic and telephonic communication, maritime, automotive or railroad transportation, aviation or any of the present day scientific, electrical or mechanical arts.

One prize will be awarded for the best article along radio lines, while the second one will cover ideas other than radio. Sketches should accompany the contestant's manuscript, which should be limited to 1,000 words. Decision will rest entirely with the Editors of this magazine and awards made each month.

Articles which do not win a prize will be published in Radio Age if found desirable and will be paid for at our usual rates. Address all manuscripts for this contest to

Contest Editor

**RADIO AGE, INC.**

500 N. Dearborn St.  
Chicago, Ill.

## Imagine Talking Over This Power Line!



Above is shown the result of opening a disconnect switch on the modern 110,000 volt transmission line of the Georgia Railway & Power Company at Atlanta, Ga. This unusual view presents in graphic detail the tremendous power carried in present-day transmission lines.

Over these same power lines there is operating a Western

Electric power line carrier telephone system furnished by the Graybar Electric Company, which uses the conductors carrying this tremendous voltage as the medium for telephone communication. This adaptation of power lines for telephonic purposes is one of the recent advances of science in the art of communication.

### Wired Radio Programs

**A**N experiment intended to provide telephone subscribers of Saint Paul with radio broadcast programs picked up by a central receiving station is being carried out by the Tri-State Telephone and Telegraph Company. It is proposed to install loud speakers in the residences of the phone subscribers, and offer them entertainment picked up by a centrally located radio receiver. Officials of the company say that they do not plan to superimpose the programs on the regular telephone lines, but to utilize spare wires for this purpose. So far it has proven feasible, and it is reported that less distortion and interference is experienced by the subscribers, who, of course, do not have to provide themselves with radio receivers. On the other hand, it has its disadvantages over radio since the recipients must be satisfied with what selections are sent them.

## DESIGNED to OUTLAST World Storage "A" Battery



**Two-Year  
Guarantee  
Bond  
in Writing**

Famous the world over for reliable, enduring performance. Solid Rubber Case lasting protection against acid or leakage.

**Approved and Listed as  
Standard by Leading  
Authorities**

Including Radio News Laboratories, Popular Sci. Inst. Standards, Pop. Radio Laboratories, Radio Broadcast Laboratories, Radio in the Home and Lefax, Inc.

**Send No Money**

Just state number wanted and we will ship same day order is received, by express C.O.D. Pay expressman after examining batteries. 6% discount for cash with order. Remember, you save 50% on World Batteries—so send your order today.

**WORLD BATTERY COMPANY**  
Dept. 38  
1219 S. Wabash Ave., Chicago, Ill.

**NEW  
LOW  
PRICES**

**Solid Rubber Case  
Radio Batteries**  
6-Volt, 100-Ampere \$10.00  
6-Volt, 120-Ampere \$12.00  
6-Volt, 140-Ampere \$13.00

**Solid Rubber Case  
Auto Batteries**  
6-Volt, 11-Plate \$10.00  
6-Volt, 13-Plate \$12.00  
12-Volt, 7-Plate \$14.50

Set your radio dial at 238.9 meters for the World Storage Battery Station WSPC. Variety—new talent—always interesting. Jerry Sullivan, Dir. and Announcer. "Chi-O-A-W-go"

KDKA WSBC

WEAF

# FREE This 84 Page WONDER BOOK

Send For It TO-DAY

You must have this latest guide to Radio prices and Radio quality. All of our vast resources and radio experience have been utilized to assemble for you in one gigantic institution, the best and newest things in radio. The Randolph catalog is indeed the radio market place of the world—a masterpiece of merchandising that befits our house—THE LARGEST EXCLUSIVE RADIO MAIL ORDER HOUSE IN THE WORLD.



## Radio Bargains

### OVER 2000 ITEMS

From the most beautiful, fully equipped console radio set, down to the smallest part or tool for the set builder—kits, parts and supplies of every conceivable type and style. 5, 6, 7 and 8 tube sets, with three dial, two dial, and the newest and most popular single simplified control. All sets are assembled in beautiful, genuine mahogany and walnut cabinets in a choice of latest types and designs.

A complete line of "B" batteries, eliminators, including the famous Raytheon Eliminators; latest types loud speakers, cone speakers, "A" power units. Everything in radio at money saving prices.

### RADIO KITS


Includes the following well known circuits, designed and approved by the world's foremost radio engineers: Madison Moore Super; Victoreen Super; Silver Marshal Six; Sargent's Infradyne; Remler Super; Short Wave Kits; 9-in-Line Super; New Acme Reflex; Cockaday; Neutrodyne; Browning-Drake; all classes of radio frequency. Super Heterodyne and every other approved popular circuit.



We Save You Money because we handle radio exclusively and sell a tremendous volume of everything in Radio.

Volume purchases regulate prices. We command rock bottom prices from manufacturers, and in many cases we contract for entire factory output of exclusive products. You will benefit by our great volume of purchases and sales, by securing anything you may want in radio at a substantial saving.
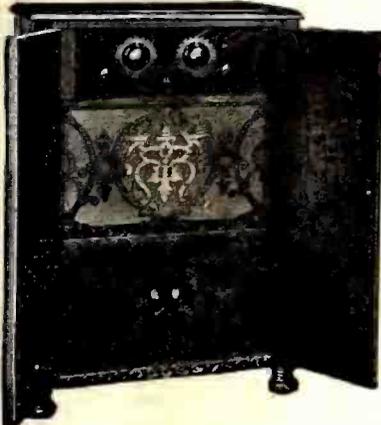
### The New Ampliphonic Six The Latest Two-Dial Receiver WITH THE Genuine Amplion Unit



Genuine dark tone and shaded walnut cabinet. Stands 39 in. high. Top measures 27x16 in. Beautifully etched burl walnut panels. Built-in loud speaker with Amplion unit. Large doors open to smaller doors enclosing a large compartment for batteries, chargers, eliminators, etc., everything concealed in this exquisitely designed radio cabinet.

**6 Tube Tuned Radio Frequency**  
6-tube tuned radio frequency two dial control receiver. 3 stages of direct and transformer amplification. Has provision for power tube and an additional tap for increased "B" battery voltage. Very latest construction including solenoid coils, bakelite sockets taking all the latest X-type tubes, modified straight line condensers. Wonderful volume, nothing like it on the market at more than twice the price. Without Accessories



Closed view

**\$79.50**

### Symphonic Five

Brown Spanish leatheroid finish cabinet with gold engraved walnut panel to match. Contrasted beautifully with the black fine tuning knobs. Two small knobs control volume and clarity. The volume control is of the finest smooth slow variation type. Roller bearing. Condensers are of the modified straight line frequency type, substantially constructed and of latest design. All is sub-panel mounted, using the new X-type socket. Latest development in solenoid coils. Two stages of low ratio audio amplification with high grade transformer offers the true amplification required for both low and high notes.

**\$24.90**

Without Accessories

The set complete with five type X201A tubes, two 45 volt "B" batteries, one 100 Amp. Hr. storage battery, complete aerial equipment, one battery cable attached, including cone speaker of the same type as pictured..... **\$54.75**



### Columbia Senior Six

Beautiful table set. New localized control. One hand to tune with, three rotating drums easily controlled and easily logged. Dark finish etched panel mahogany finished hand-rubbed cabinet. Size 7x22.

6-tube set, giving tremendous volume, wonderful tone quality, latest straight line condensers, solenoid coils; sub-base mounting and new amplification. Designed to sell for over \$100.00. Price, **\$36.50** without accessories

Set complete with two 45 volt "B" batteries, 100 amp. hr. Storage "A" battery, one 4 1/2 volt "C" battery, six type X201A tubes, complete aerial kit, attached battery cable, quality cone speaker or Victor horn type loud speaker..... **\$65**



### Columbia Grand 6-Tube Console Set

Here's a sensational bargain in a console radio with built-in loud speaker and adjustable unit. Spacious compartment for all batteries, etc. Very latest type 6 tube tuned radio frequency receiver. Low loss modified straight line frequency condensers. Has three stages of low ratio audio amplification. Designed to accommodate new power tube. Equipped with X-type sockets. Beautiful gold etched panel with handsomely engraved designs. Price of set with accessories..... **\$42.65**  
This set with all accessories which include 2 45 volt "B" batteries, 100 Amp. Hr. storage "A" battery, 6 201A tubes, aerial and ground equipment—everything complete, nothing else to buy..... **\$65.95**

### You Must Have This Book

Space limitations here prevent our telling you more about the Randolph Catalog. Simply fill out and mail the coupon—or you may send a postal or letter—and this truly remarkable Radio book will come to you ABSOLUTELY FREE. MAIL THE COUPON NOW.



Beautiful hand rubbed, two-toned mahogany finished cabinet, size 18 x 19 x 36. Built-in loud speaker.

### This Coupon Brings the Great RADIO Book FREE

RANDOLPH RADIO CORPORATION  
180 N. Union Ave., Dept. 186 Chicago, Illinois  
Send me—free—your 84-page, 1927 Radio Book.

Name \_\_\_\_\_  
Street and No. \_\_\_\_\_  
R.F.D. \_\_\_\_\_ Box \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

## Randolph Radio Corporation

180 North Union Avenue - Dept. 186 - Chicago, Ill.

Please Mention Radio Age When Writing To Advertisers.



**EVERYWHERE**



Registered

U. S. Pat. Off.

**TRANSFORMERS  
Have Made Finer Radio  
Reception Possible**

These improved transformers assure selection of radio programs at choice, regardless of broadcast conditions. They combine tremendous power with an unexcelled purity of tone and amplify the weakest signals to full loud speaker volume. They operate with all types of standard tubes. Unsurpassed for quality, clarity and volume.

**Praised  
Endorsed-Approved**

"H. F. L. Audio Transformers have insured real tone in my receiver. Get DX through Chicago locals without trouble...KFI and 50 others with static and external noises reduced in practically all cases."

H. F. L. Units have been heartily endorsed by such leading Radio Authorities as Radio News—Citizen's Radio Call Book—and Radio Age.

H. F. L. Users Write: "Picked up Rome, Italy, from Evanston. Also Aberdeen and Edinburgh." "Lima, Peru, came in on my H. F. L. Receiver with full loudspeaker volume." "Get coast to coast from Chicago regularly using H. F. L. Units."

**PRICES**

H. 210 Iron core transformers with an exceptionally high amplification factor. Each unit carries laboratory calibration. Range 32,000 to 42,000 cycles. Price \$8.00.

H. 215 Air core transformer, tuned stage, designed to amplify signals at a maximum efficiency of 37,000 cycles. Each unit carries the laboratory calibration. Price \$8.00.

F. 320 Audio frequency transformer which will amplify signals to greatest volume with incomparable faithfulness of tone. These units are the result of an entirely new principle in transformer construction. Price \$8.00

L. 425 Radio Frequency Choke Unit. Price \$5.50

L. 430 Low Loss Radio Frequency Transformer. Price \$5.50

**Jobbers Write Dealers  
Today**

Try H. F. L. Units for Better Results  
If your Dealer cannot supply you order direct.

**HIGH FREQUENCY  
LABORATORIES**

133 N. Wells Street  
Chicago Illinois

**Death Ray Tube Turns  
Gases Into Solids**

(Continued from page 46)

jected to the rays, and the glow of cold light continues for hours. The glow comes from an area very near the surface of the crystal since the rays penetrate but little into the substance. Immediately after the crystal has been rayed, numerous bluish-white sparks or scintillations can be noticed beneath the surface of the crystal; these are electrical explosions, the result of the bombardment of the atoms in the crystal by the high-speed electrons.

Granite, a mixture of several minerals, glows with several brilliant colors, some of the colors fading away immediately and others remaining for some time. Numerous other substances can be made to change in color, some permanently and others for a short time.

The commercial possibilities of the tube, still a laboratory development, are unknown but it is expected that the tube will be invaluable in scientific investigations regarding electronic phenomena.

**Dual Range Meter**



Shown above is a new Westinghouse high resistance DC voltmeter with a dual range, 0-7½ volts and 0-150 volts which will serve for measurement of either A, B or C voltages. Three foot leads are supplied with pin jack terminals for plugging in on any of the standard sets provided with voltmeter jacks

**CHELSEA**

Send for the latest folders on our new 3, 5, 6 and 7 Tubes Sets, \$26 and up.

Chelsea Radio Co., Chelsea, Mass.

One of the Oldest Established  
Radio Manufacturers



**World Radio  
Storage "B" Battery**

**275**

12 Cell—24 Volt  
Proved value. Thousands of users find reception almost magical. Clear, true power—instantly and unendingly. Wise economy. Sturdy construction—Solid Rubber Case protection. Recharged for almost nothing. Endorsed and listed as standard by famous Radio institutions including Pop. Radio Laboratories, Pop. Sci. Inst. Standards, Radio News Lab., Lefax, Inc., and other Radio authorities. What more need be said? **Extra Offer: 4 Batteries in series (96 volts) \$10.50.**

**Send No Money** Just state number wanted and we will ship same day order is received, by express C. O. D. Pay expressman after examining batteries. 5% discount for cash with order. Remember—you save 50% on World Batteries.

**WORLD BATTERY COMPANY**

1219 So. Wabash Ave., Dept. 81 Chicago, Ill.  
Makers of the Famous World Radio "A" Storage Battery  
Prices: 6-volt, 100 Amp. \$10.00; 120 Amp. \$12.00; 140 Amp. \$13.00.  
All equipped with Solid Rubber Case.

Set your radio dials at 288.3 meters for the World Storage Battery Station W5BC. Variety—New Talent—Always Interesting.  
JERRY SULLIVAN—Director and Announcer—Chi-CA-W-20

**Bradley-Amplifier**  
Resistance-Coupled  
PERFECT AUDIO AMPLIFIER



Provides audio amplification with minimum distortion. Bradley unit molded resistors used in the Bradley Amplifier do not vary with age and are not affected by atmospheric conditions. Can be used to replace transformer amplifiers in standard radio sets with decided increase in tone quality.

**Allen-Bradley Co.**

Electric Controlling Apparatus

289 Greenfield Avenue Milwaukee, Wis.

**WORLD'S FINEST  
LOUD SPEAKER**

A three-foot cone speaker—unit developed by the inventor of the Tropadyne. Easily assembled, saving 80% of the cost. Complete Kit with blue prints sold on rigid money-back guarantee—shipped prepaid or C. O. D.—\$10.00

ENGINEERS' SERVICE COMPANY

25 Church St. New York, N. Y.

**RADIO** We want to hear from hard-hitting radio dealers operating live-wire stores who want to make the best jobber connection in America.

**DEALERS**

Our eight big warehouses furnish you with the finest products in radio. And we ship fast.

**WANTED**

Write today on your letterhead for big catalog of nationally advertised lines.

Ask for L 1008

**WAKEM & McLAUGHLIN, Inc.**  
225 E. ILLINOIS STREET, CHICAGO, ILL.

# World's Smallest Radio



Smaller than a typewriter and weighing only 5 1-2 pounds, with a sending radius of 300 miles, a tiny transmitter has been built by United States Marine Corps aviators and installed in marine airplanes for "talking" to other pilots and to ground stations. In 50 separate tests, the little sender worked "perfectly" 47 times, and aviators said the three failures were due to factors outside the transmitter.

Capt. Francis E. Pierce, communications officer for the marine flying corps at San Diego, California, (shown in photograph) designed the transmitter. He built the first one from junk salvaged from the navy dump on North Island. The government contributed nothing while officers and men gave about \$22 toward the building of the transmitter. The entire set, including transmitter, receiver, batteries and dash controls, weighs 17 1-4 pounds.

The transmitter, around which most interest centers, is built on an aluminum sheet. The front aluminum panel measures 9 by 10 inches and the base 9 by 9 1-2. The milliammeter for measuring the total current in the tuned plate tank circuit and the variable tank circuit is mounted on the front. On the base are the clips for the one-inch-square quartz crystal, ground to a frequency of 3000-4000 kilocycles; the grid biasing resistance; the plate blocking condenser; socket for 50-watt tube; the grid and plate chokes; the inductance for the plate circuit, and the keying relay. For installation, the transmitter is slung on a shock absorber cord behind the pilot. Only the dash control is visible when the set is ready for use, and both transmitter and receiver are said to be fool proof.

Power is derived from a wind-driven generator, 10 volts being delivered through a wire wound resistor from an original 30-volt supply.



## TROUBADOUR




NEW  
DRUM  
TYPE

\$30.

Just as the amorous nobles of old Spain, France and Italy charmed a continent with their hauntingly beautiful music and poetry—so has the marvelous reproduction of the TROUBADOUR impressed itself upon the Radio World of today. It is Music and Song and Poetry unaltered, undistorted—true. Distinctively artistic in design, body finished in rich walnut brown, base and faces in dull black Morocco leather finish. Troubadour's weight of 11 pounds is absolute assurance against vibration, while Quali-Tone's advanced construction results in a new quality of reproduction—that amazes listeners by its depth, resonance and purity. Height, 15 1-4 inches, Diameter 13 1-2 inches, Depth 5 1-2 inches.

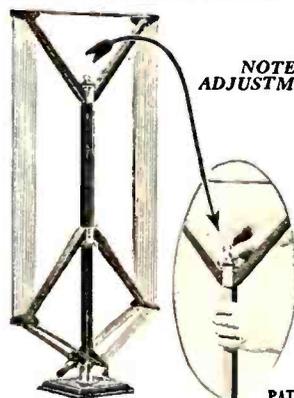SEND for literature describing Quali-Tone's complete line, which includes the Junior Speaker—\$7.50, Quali-Tone No. 2 Speaker—\$10, Quali-Tone No. 3—\$15, Quali-Tone No. 4—\$25 and Quali-Tone Radio Units at \$6 and \$7.50.



NOTE  
ADJUSTMENT!

PATENTED

### 8,000 MILE RECORD

The Quali-Tone Loop pictured above holds two World's Records for distant reception, having brought in stations 8,000 miles away. Write for verification of these records. Exclusive Thumb-screw Adjustment keeps wires taut always. Guaranteed to improve the reception of any receiver. . . .


Price \$10

DEALERS Write for discounts. JOBBERS Send for circulars.

DURO METAL PRODUCTS CO.

2653 North Kildare Avenue,

Chicago

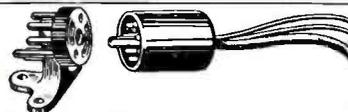

Remember . . .

on your present set, or the one you're building, you can't sacrifice the added convenience, neatness and mechanical superiority of the

**Jones**  
**MULTI-PLUG**  
THE STANDARD CONNECTOR

Type BM, with 4 ft. cable, price \$3.50

Ask Your Dealer

HOWARD B. JONES

618 S. Canal St.

Chicago, Ill.

A Dollar Bill will bring you our 1926 Annual—Only a few left



### ALKEMITE

Chemically treated crystal brings Distance and Volume. 50 cents each.

Supersensitive tested Galena 75c per pound. Wood's

Metal. 1/4 pound \$1.00. Postage prepaid.

THE MINERAL NOVELTY CO.

Box A 1005. Joplin, Mo.

### CONE UNIT

For use on cones of any size up to 4 feet. Most powerful and efficient made. Sold on rigid money back guarantee.

C. O. D. or Prepaid \$7.50

TUNBAR RADIO CO.

26 Cortland St.

New York



# SELECTONE TRANSFORMERS

TESTED - MATCHED - GUARANTEED

Designed by E. H. Scott, whose famous receiver, the WORLD'S RECORD SUPER 9 established FOUR world records for long distance reception.

**HIGHEST AMPLIFICATION  
FINEST TONE QUALITY**

SELECTONE Untuned Transformer—R400—has specially designed closed iron core, which limits inter-stage coupling and is impregnated in a vacuum so that all characteristics of coil remain constant. The coil design gives an extremely high amplification. Can be used in any circuit requiring a long wave transformer. **PRICE \$6.00**

**PERFECTLY MATCHED  
GREATEST SELECTIVITY**

SELECTONE Tuned Stage Transformer—R410—is air core. Each transformer is matched to within one turn before sealing in case. The matching of these filters is so perfect that where extreme selectivity is desired, two can be used and are guaranteed to match perfectly. **PRICE \$6.00**

Either 199 or 201A Tubes Can Be Used

**FREE** Send for illustrated literature describing Selectone Transformers and tests they undergo.

**JOBBERS and DEALERS**—See your Distributors or write direct.

**SCOTT TRANSFORMER CO.**

7-9 So. Clinton Street, Chicago, Ill.

## A & B Battery \$2 Charger ONLY

**Satisfaction Guaranteed**



Charges any type of storage A or B battery, using a few cents worth of ordinary house current, either alternating or direct. Cannot injure battery. Complete directions enclosed. Anyone

can operate. No expensive "extras" to buy. Why pay \$10.00 to \$15.00 for a charger when you can get this splendid **GUARANTEED R. B. Charger** by mailing us two dollars (bills, money order, check or stamps) plus ten cents in stamps or coin to pay mailing costs. Charger will be sent postpaid. If you are not satisfied, return within five days and we will refund your money. Order at once—TODAY.

**R. B. SPECIALTY COMPANY**

Dept. E-6

308 East Third St., Cincinnati, Ohio

Be Sure To  
Subscribe to Radio Age  
\$2.50 a Year

## New Idea In Cabinets



Good taste and usefulness are combined in the art cabinet shown above which has been designed by a mid-Western concern for radio users or set builders.

The sides of the cabinet are made in the form of art panels, while the doors are arranged likewise. Batteries, both A and B, or power supply devices may be placed in the bottom. The radio set itself is put in the upper portion of the cabinet which looks like the typical phonograph housing. The panels and the set are removable.

Watch the January issue for more data on superheterodynes.

**American Radio** Now—  
**50% DISCOUNT RADIO!**  
ON  
**BIG NEW 1927 CATALOG-FREE**

Dealers, Agents, Set Builders—get our big 1927 Catalog—225 nationally advertised lines. Lowest prices in America! Largest, most complete stock. Radio's latest developments. It's FREE—send for your copy now. **AMERICAN AUTO & RADIO MFG. CO., Inc.** 1470 McGee Street, Kansas City, Mo.

(Continued from page 34)

fact afforded. All they had to do was to ship the parts from their stock, there was no grief, and there was a steady sale. The result is that all those jobbers who felt inclined to get out of the parts business are getting back into it with both feet. What makes the actual state of affairs rather deceiving is the fact the proportion of manufacturers sales to the set manufacturers and to the trade has changed. For example whereas a few years ago the sales of a certain manufacturer may have been 70 per cent to jobbers and 30 per cent to manufacturers, they may now be 50 per cent to the manufacturer and 50 per cent to the jobber. However the radio business has increased to such an extent that in actual dollars and cents the manufacturer is selling much more than ever before to the trade. A recent private survey which we made personally among a number of representative manufacturers of standard, advertised, quality parts, shows clearly the above condition to be true. Unanimously these manufacturers agree their parts business to the trade is greater than ever before and all seem confident that with the number of excellent kits which are appearing on the market, and with proper consideration of the human element in the radio industry (which makes it difficult for a fan to be easily satisfied) the parts business is not only very far from dying, but is in an exceedingly healthy condition with every prospect of a long and useful life before it."

Opinions of other well known manufacturers arrived too late to be quoted in full, but bear out to a remarkable degree the fallacy of the statement that the parts business is dead.

### Limited Licenses


AS SOON as Congress convenes, it is now understood that the old joint resolution limiting the term of radio licenses and requiring a waiver to all wavelength priority, unsigned in the rush of the closing days, will be signed forthwith.




\$15<sup>00</sup>

(West of Rockies, \$18.00)

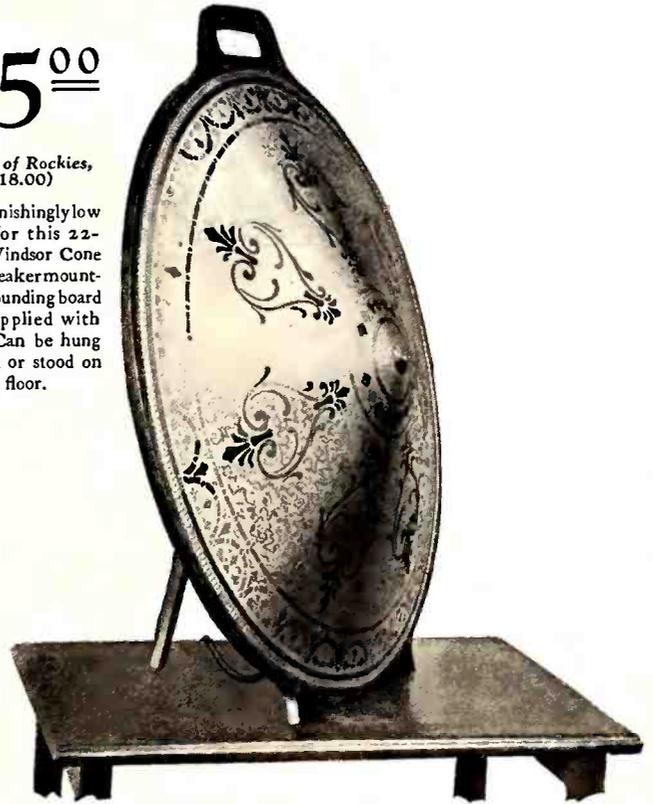An astonishingly low price for this 22-inch Windsor Cone Loudspeaker mounted on sounding board and supplied with easel. Can be hung on wall or stood on table or floor.



# This Amazing New Cone Speaker Hangs on Wall or Stands on Table!

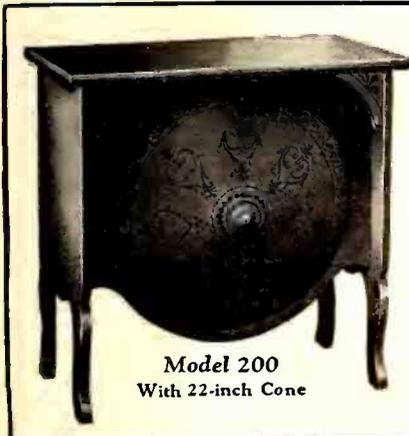

Model 200  
With 22-inch Cone

This Windsor Cone Loudspeaker Console is equipped with a 22-inch Windsor Cone Loudspeaker. Its top is 30" x 17" and is 29" high. The battery shelf provides ample space for batteries, charger, battery eliminator and other equipment. Beautifully finished in either Mahogany or Walnut. Price only . \$29<sup>00</sup>

(West of Rockies, \$35)

NOW the radio world enjoys a new sensation—a 22-inch cone loudspeaker mounted on a sounding board and equipped with an easel back so that it can be hung on the wall, stood on a table, or placed on the floor.

And this is the famous Windsor Cone Loudspeaker that reproduces *all* the tones as they are broadcast. From the deepest throated pipes of the largest organ to the softest note of a crooning lullaby—from full volumed brass of a band playing "The Stars and Stripes Forever" to the last faint note of "Home Sweet Home" played by a master violinist—*every* tone, *every* sound is reproduced with perfect fidelity in all its beauty, just as it entered the microphone.


This wall and table model Windsor Cone Loudspeaker has no equal in value in the world of radio. When compared with the average cost of cone-type loudspeakers of even smaller size and without the sounding board and easel back, the cost of this Windsor model is amazingly low.

Dealers everywhere are showing this new radio wonder. Go to your dealer today—see and hear this marvelous loudspeaker—note its extreme utility—compare its low price with others—compare its tone—its volume—then you will have no other. If your dealer should not have one, send your name and address for complete information and prices on the entire Windsor line of Cone and Horn Loudspeakers and Loudspeaker Consoles.

*Note to Dealers* Write or wire today for details of the highly profitable Windsor selling franchise.

**WINDSOR FURNITURE COMPANY**  
World's Largest Manufacturers and Originators of Loudspeaker Consoles  
1416 CARROLL AVE. . . . CHICAGO, ILLINOIS  
Los Angeles Branch, 917 Maple Ave.

In this Windsor Console is combined both the Windsor Moulded Composition Horn Loudspeaker and the 18-inch Windsor Cone Loudspeaker. The top is 30" x 17" and stands 29" high. Ample battery and equipment space is provided by large shelf in rear. Price finished in Walnut or Mahogany. \$48<sup>00</sup>  
(West of Rockies \$55)

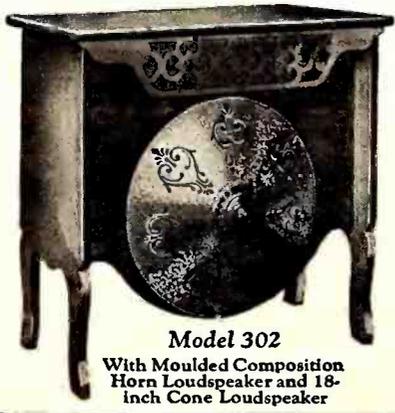

Model 302  
With Moulded Composition Horn Loudspeaker and 18-inch Cone Loudspeaker

# EXPERTS DON'T GUESS



Expert radio men use expensive instruments to measure the B-voltage delivered by a B-Power Unit. They realize the importance of correct B-Power.

The B-T B-Power Unit is designed with the idea of eliminating all guess-work. No variable resistances—no knobs to turn. The Unit is adjusted once and thereafter the correct voltage is delivered at the touch of the switch. The B-T method of adapting the B-Power Unit to different size sets is as simple as it is fool-proof.

Capacity 150 volts at 60 milliamperes. Adjustable to sets requiring less by the exclusive B-T method.


Price complete with Raytheon Tube \$49.50

Lose no time in investigating this new B-T product, which is now available at high-grade dealers.
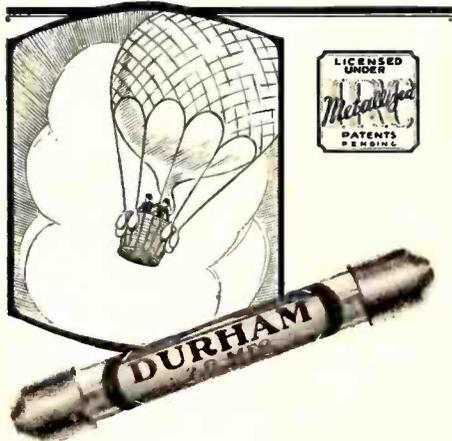
## BETTER TUNING

The Tenth Edition *Better Tuning* gives full information on the B-T Unit, our views on "eliminators" in general, Power Six Kit set described; how to change your Counterphase Kit set to a Power-Six Model, new Counterphase-Eight and many other subjects—56 pages—10 cents.

**BREMER-TULLY MFG. CO.** 520 S. CANAL St. CHICAGO, ILL.



# Noiseless!

The Durham Metalized Resistor is scientifically built to function as smoothly and noiselessly as the balloon gliding swiftly and silently towards the sky. Fixed in resistance value, and moisture- and temperature-proof.

10 meg. to 500 ohms, from 50 cts. to \$1.00

**DURHAM**  
METALLIZED  
**RESISTORS**

INTERNATIONAL RESISTANCE CO.  
Dept. C, Perry Bldg. Philadelphia, Pa.

## Simplex Issues Fine Micrometer Coupler

EXPERIMENTERS and dyed-in-the-wool fans will welcome a micrometer coupler in which the inductive relationship of the plate coil (tickler) is governed by a micrometer movement through a knob on the panel.

This method of making minute inductive changes in the tickler circuit removes one of the objections previously held against the straight tickler tuned set since it was difficult to get a small enough movement of the tickler to allow ease in tuning.

The new coupler is made by the Simplex Radio Devices, Inc., and has a single hole mounting, is equipped with ball bearings and all in all is a nice workman-like job.



## MURRAY UNIT REALLY ENDS TROUBLE

For constant Radio "A" power; can be operated while set is in use. Simply connect to light socket. No adjustment; no wires to change; no low batteries. Equipped with hydrometer in cap for gravity test and 2-amp. G. E., Tungar bulb. Delivered ready to use.

Agents Wanted! Murray Distributor 4837 N. Robey St., CHICAGO **\$2950 LIST**

Turn! Dial-get programs everywhere: **30 Days FREE!**

**MIRACO** Literature 5

Users report Miraco Radios get Coast to Coast, Canada to Mexico, loud and clear on speaker; outperform \$100 to \$200 sets. Some bear Europe. Marvellous bargain! Don't buy unless 30 Days Trial proves it Most Selective, Clearest and Most Powerful Distance Getter among big fine 5-tube radios. Solid walnut cabinet. Write for **Factory Prices—SAVE Up to 1/2** Every set completely assembled, rigidly tested, fully guaranteed. Ultra-G, \$49.75 list. Speaker, batteries, tubes, etc. at big savings.

**MIRACO RADIO GETS EM COAST to COAST**

Free literature, users' testimony and BIG SPECIAL OFFER! **USER-AGENTS WANTED** Write for Discoums

Send for Proof 523-E Miraco Bldg., Cincinnati, O.

Matchless in Performance **DE LUXE Double CONE SPEAKERS**

Two free edge, full floating diaphragms. Beautiful design; finish: mahogany wood stand.

18" De Luxe.....\$25.00  
12" De Luxe Jr.....\$16.50  
Standard.....\$13.75  
Special.....\$ 9.50

Write for Descriptive Folder "L"

Dealers Inquiries Invited

Empire Elec. Products Co. 132-134 Greene St. New York

**Yale GROUND HOG**

The Perfect Ground **DOUBLES POWER AND DISTANCE**

Marvelous newly-invented ground gives incredibly improved reception. Doubles power and distance users say. Reduces leakage. Stops jangling even in midsummer. Results never before equalled. Satisfaction guaranteed or money back at once. Proven absolutely essential to clear, powerful distance reception. Draws and holds moisture indefinitely. Highly sensitive to radio energy. **SEND NO MONEY**—To introduce, we offer to those who act at once, regular \$5.00 size for only \$2.00. Send name today and pay \$2.00 plus 17c postage on delivery. Or send only \$2.00 with order and save postage. **FREE**—Full description of Ground Hog and details of amazing low priced battery offer on request—write today

Yale Specialty Supply Co. 137 W. 5th St., Kan. City.

**AUDIO FREE AMPLIFICATION**

The four types thoroughly explained in a fully illustrated booklet 9" x 12". This booklet will be sent to you absolutely **FREE** if you will send me six cents in stamps to cover cost of handling and postage.

W. McMANN  
64 Church St., Dept. R. A., New York City

**6 Volt STORAGE RADIO "A" BATTERY**

Most amazing battery value ever offered! A genuine World 6-volt Radio "A" Battery with 25 ampere capacity for only \$5! It is just the thing for Trickle charger. Famous World Quality assured. Equipped with **Solid Rubber Case**

An assurance against acid and leakage. Order shipped same day—subject to your examination on arrival. Extra offer: 5% discount for cash in full with order. **ACT TODAY!**

**World BATTERY COMPANY**  
1219 S. Wabash Ave. Dept. 136 Chicago, Ill.

**New York and London Now  
Linked by Speediest Cable**

*(Continued from page 39)*

at that point and they continued their work by wading up to their waists. About ten yards from the shore a third man, fully dressed, stood knee-deep in the water and cut the barrels from the cable as they drifted in. A fourth man rolled the barrels up on the beach.

When the last of the barrels came in the cable was buried in a shallow trench. All that remained then was to make the station connections and to splice the 170-mile shore end, which weighs 117 tons, to the oceanic end, which was kept afloat with the aid of a buoy. The entire cable is 3,400 nautical miles long. Its main section is about an inch in diameter.

The innermost section of this slender line of communication which links two continents is the copper conductor, less than one-fifth of an inch thick, which carries the electric current. Around this wire are wrapped six flexible copper tapes to carry the current around the gap in case the cable breaks. Also wrapped around the conductor is the continuous strip of permalloy, and next to the permalloy is the insulation, consisting of three layers of gutta percha.

Over the gutta percha insulation is a layer of jute yarn to act as a cushion for the armor which protects the cable from breaks that might be caused by the wreckage of sunken ships. This armor consists of 18 galvanized steel wires, each having a diameter of .09 inches. These are wrapped with a fabric to prevent oxidation under water. Finally, the cable is wrapped with two servings of jute yarn saturated in coal tar, wound on spirally and forming the outer covering.



**BAD  
TUBES—**

—are known to be the cause of a large percentage of the trouble occasioned set owners. Taking the tubes to the dealer from whom they were bought for testing is very troublesome—besides you are put to the necessity of asking for service which is often—given reluctantly.

With a Jewell Junior Tube Tester, the set owner is enabled to check his radio tubes at home—thus weeding out the bad ones and either rejuvenating or replacing them by good ones. In this way reception is always maintained at its maximum.



**Pattern No. 107  
Jr. Tube Checker for testing tubes at home**

*Send for Circular No. 735*

**Jewell Electrical Instrument Co.**

1650 Walnut St.

Chicago

*"Twenty-six Years Making Good Instruments"*

**We Carry a Complete Line of Parts  
for the Following Circuits:**

**AERO-DYNE**

St. James

Qualitone

Short Wave

Browning-Drake

Hammerlund Roberts HI-Q

Madison Moore

Samson T. C.

Victoreen

Radio Age Super 9

World's Record Super 8

In writing us SPECIFY just what hook-up you are especially interested in and we will promptly place our prices before you.

WHOLESALE


RETAIL

**NEWARK ELECTRIC Co.**

*"Nothing But Radio"*

226 WEST MADISON STREET

TELEPHONE  
MAIN 4627

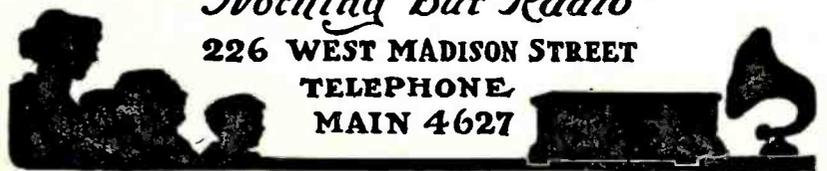

CHICAGO

ILLINOIS

**PATENT YOUR IDEAS**

Inventions developed. Patents secured in the U. S. and Foreign countries. Satisfactory Terms. Write, call or phone HANOVER 3662 for confidential advice and Invention Recording Blank.



**Z H POLACHEK** REG. PATENT ATTORNEY CONSULTING ENGINEER  
70 WALL ST. NEW YORK

# Greater Distance Finer Selectivity Greater Power

with

## AERO COIL

SUPER-SENSITIVE


### INDUCTANCE UNITS



TUNED RADIO FREQUENCY KIT
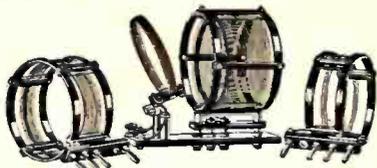
## \$12.00

The Aero Coil Tuned Radio Frequency Kit illustrated above will positively improve the performance of any receiver. Patented Aero Coil construction eliminates radio frequency losses and brings tremendous improvement in volume, tone and selectivity. Kit consists of three matched units. The antenna coupler has variable primary. Uses .00035 condenser. 3 page color circuit, layout and instruction sheet for building the supersensitive 5 tube Aero-Dyne receiver packed FREE with each kit. Extra copies, 75c each.



LOW WAVE TUNER KIT

## \$12.50

Completely interchangeable. Adapted by experts and amateurs. Range 15 to 130 meters. Includes three coils and base mounting, covering U. S. bands, 20, 40 and 80 meters. You can increase the range of this short wave tuner by securing coils No. 4 and 5. Combined range of 15 to 550 meters. Both interchangeable coils fit same base supplied with short wave kit and use the same condensers. Coil No. 4 price \$4.00; Coil No. 5, price \$4.00. These Aero Coils are available at your dealers. Get yours today!

**Aero Products, Inc.**  
Dept. 106, 1772 Wilson Avenue  
Chicago, Ill.

## Bradleyometer

THE PERFECT POTENTIOMETER

Uses graphite disc resistors which are noiseless and not affected by atmospheric conditions. Metal parts are nickel plated. One hole mounting. Finish and knob matched Bradleystat. Made in 200 and 400 ohm ratings.



**Allen-Bradley Co.**

Electric Controlling Apparatus

289 Greenfield Avenue Milwaukee, Wis.

## Turning Soprano to Contralto is Feat of Single Side Band Set

(Continued from page 16)

exactly right, then true reproduction results and this is the only condition under which true reproduction may result. If the heterodyne frequency is low or high, then the reproduced signal will be low or high. *It is thus possible to make a contralto out of a soprano or vice-versa at the pleasure of the operator.*

The apparatus comprising the transmitter may be considered in two sections, the single-side band equipment and the power amplifier chain. The single side-band apparatus is installed in a metal screened room. This precaution is taken to prevent the powerful fields of the amplifiers from disturbing the delicate balance of the modulators where the power level is in the neighborhood of one watt. In metal cabinets are two balanced modulators and the first stage of the power amplifier chain. This stage and the following stages raise the power level from about one watt to about fifty thousand watts. Quartz crystals are used for obtaining the desired carrier frequencies.

The filters are located overhead in the shielded room. Outside of the wire screened room is the power amplifier chain, three stages being provided to increase the power level to that desired.

## "B" BATTERY ELIMINATOR

Only \$7.95

**MONEY-BACK GUARANTEE**  
No more worry with "B" Batteries! Hook up a Roll-O "B" Battery Eliminator and forget battery troubles forever. This wonderful new invention means better reception, sharper tuning. Gives you more real pleasure from your set.  
Completely Equipped—No "Extras" to Buy  
Operates perfectly on direct or alternating current, giving up to 90 volts current, and using the full wave of the power supply. Simple directions enclosed—anyone can plug it in to any kind of set up to six tubes. Constant voltage gives set more power. Costs no more than set of good "B" Batteries. Solidly built in beautifully finished metal case, with genuine Bakelite top.

Send \$1.00

**SEND YOUR ORDER NOW**

Don't blame your set because run down "B" Batteries won't let it work right. Order your Eliminator NOW. Write name and address on a piece of paper, pin a dollar bill to it, and mail it TODAY. Pay postman balance (\$8.95 plus a few cents postage) when he delivers your Eliminator. Use it ten days. If not more than satisfied, return it and get your money back.  
Roll-O Trickle Charger, for either "A" or "B" Batteries, only \$3.95 (plus few cents postage). Send \$1.00 with order—balance C. O. D. Satisfaction guaranteed or money refunded.  
**THE ROLL-O RADIO CO.**  
Dept. R-2 Third and Sycamore, Cincinnati O.

Why  
your set  
needs  
**AMPERITE**



Because clear reception and long tube life necessitate that delicate and self-adjustable control which only AMPERITE can give.

Eliminates hand rheostats.  
Simplifies set-wiring.

Accepted as the only perfect filament control in every popular construction set.

Price \$1.10 Complete  
FREE—Write for "The Radiall Book," containing the latest popular hook-ups and construction data, to Dept. R. A.-17

*Radiall Company*

50 FRANKLIN ST., NEW YORK

## AMPERITE

REG. U.S. PAT. OFF.

The "SELF-ADJUSTING" Rheostat

## All Specified Parts

FOR THE

## World's Record Super 8, 9 and 10

WRITE TODAY

For free catalog of all the parts needed for these marvelous receivers that have made four WORLD'S RECORDS. We stock complete parts just as specified and recommended by the designer: panels drilled and engraved as per specifications.

Every Record Authentic and Fully Verified

FREE Verifications of startling World's Records sent upon request.

THOR RADIO CO.,  
319 Crilly Bldg. Chicago

Free Mailing Lists  
Will help you increase sales  
Send for FREE catalog giving counts and prices on thousands of classified names of your best prospective customers—National, State and Local—Individuals, Professionals, Business Concerns.  
99% Guaranteed by refund of 5¢ each  
**ROSS-Gould Co.** 315 N. 10th St. St. Louis



\$158-\$225 MONTH Railway Mail Clerks  
Travel for "Uncle Sam." Men, Boys.  
\$18 up. Steady work. Travel—See your country. Common education sufficient. Write immediately for free 32 page book, with sample coaching lessons and full particulars. Do it today sure.  
FRANKLIN INSTITUTE Dept. 0324 ROCHESTER, N. Y.

**New Radio Service  
For All Amateurs**

THE Barawik Company of Chicago, pioneer radio merchants, announce the installation of a new department devoted entirely to the interests of short wave enthusiasts. The interest in short wave transmission and reception is continually growing because of the ease with which tremendous distances can be covered. For both the established transmitting amateur and the experienced broadcast listener, the Barawik Company has inaugurated this new department.



F. J. Marco, well-known amateur and radio consultant, who will direct the new radio service for the Barawik Company


F. J. Marco, consulting engineer, and owner of the experimental short wave station 9ZA, has been retained to direct this special department of the Barawik Company.

In the direction of this new department for the Barawik Company, Mr. Marco will endeavor to establish a center of short wave information and engineering service for the U. S. as well as internationally. The Barawik Company will be in a position to give technical information and supply all equipment pertaining to this field. In the design of the new equipment and the correction of difficulties with existing apparatus, the Barawik Company will constantly issue catalogs and bulletins.

The Barawik Company is making it possible for all those who are not already in the game to enter it.

*Be sure to order your  
January Number  
Now—  
a treat is in store for  
you.*

**DEPENDABILITY**

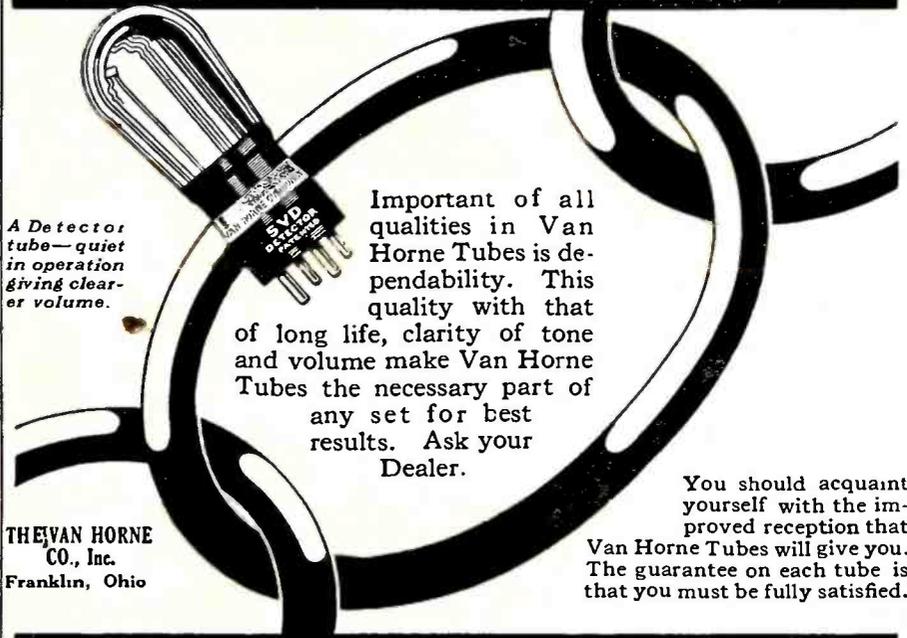

A Detector tube—quiet in operation giving clearer volume.

Important of all qualities in Van Horne Tubes is dependability. This quality with that of long life, clarity of tone and volume make Van Horne Tubes the necessary part of any set for best results. Ask your Dealer.

You should acquaint yourself with the improved reception that Van Horne Tubes will give you. The guarantee on each tube is that you must be fully satisfied.

THE VAN HORNE  
CO., Inc.  
Franklin, Ohio

**VAN HORNE  
Radio Tubes**

Subscribe to Radio Age  
\$2.50 a Year

**Build a Better Set  
Than You Can Buy!**

This receiver has been tested and compared in many laboratories with practically every quality set now on the market and were a manufacturer to build this outstanding circuit of the year it would easily come within the \$300 class.

THE NEW  
**HENRY-LYFORD  
RECEIVER**

Has been endorsed and approved by Radio News, Radio, Popular Radio, Citizens Call Book and this magazine, read about it in the November issue of the Radio Age.


IT'S A PLUG-IN COIL RECEIVER WITH A DELIBERATELY UNBALANCED CIRCUIT

**Complete Parts \$69<sup>50</sup>**  
All parts fully guaranteed and neatly packed including blue prints

If your dealer cannot supply you, order direct  
It's As Near Perfect As They Come and  
**EASY TO BUILD**

UNIVERSITY RADIO CORP.  
50 Park Place, N. Y. C.  
Please send me booklet describing in detail full particulars of the Henry-Lyford.

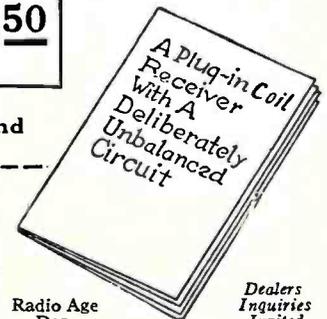Name \_\_\_\_\_  
Street \_\_\_\_\_  
City and State \_\_\_\_\_



Radio Age  
Dec.

Dealers  
Inquiries  
Invited



Dubilier Ducon  
Price \$1.50

## Aerials have gone out of style - - -

**I**N THE old days, when radio was new, the "fan" was known by crazy festoons of wire that decorated his housetop or yard. These were the old fashioned aerials, and no one has forgotten all the grief they caused.

Modern radio may use the hidden loop, or the short indoor aerial. But there is a better way. The Dubilier Ducon enables you to use the complete wiring system of your house without risk, and with better results than most out door aerials give.

You simply screw a Dubilier Ducon into any lamp socket, and connect it with the antenna binding post of your set. You will find that it increases selectivity—especially in crowded neighborhoods, and will reduce "static" in the summertime.

Try a Dubilier Ducon on your set tonight. They are sold by all good dealers on five days' trial for \$1.50.

**Dubilier**  
CONDENSER AND RADIO CORPORATION

## High Lights on Wavelengths and Frequencies Used

(Continued from page 15)

ten-kilocycle separation is maintained. Such interference may be due to the use of a receiving set of poor selectivity or it may be caused by the receiving set being too near the broadcasting station.

### Where Squeals Originate

**W**HEN two broadcasting stations are operating on frequencies differing by ten kilocycles they will produce a beat note of 10,000 cycles in the phones of a receiving set tuned to one of the stations. Suppose that these stations shift their assigned frequencies in such a manner that they are separated by only seven kilocycles. You will now have a beat of 7,000 cycles in the receiving set. The 10,000-cycle beat is a pretty high, faint squeak and scarcely noticeable to the normal ear. The 7,000-cycles beat, however is likely to be annoying.

We see from these remarks the importance of keeping broadcasting stations on their assigned frequencies with the dual object of eliminating the beats and the side band interference. It seems that the ten-kilocycle separation between broadcasting stations is almost ideal: it makes available the maximum number of ether channels without undue interference. Then too, the use of this spacing expresses frequency assignments in good round numbers, an advantage in itself. It seems probable that this is the best scheme for allocating broadcasting stations which can be devised except in case a fundamentally different plan of modulation comes in vogue. The problem becomes one of keeping stations strictly on their assigned frequencies and we can readily see how chaos may result from indiscriminate use of frequencies.

It is a pretty safe guess that if all broadcasting stations had from the very beginning been designated by kilocycles the use of meters would seem strange and difficult. Who would want to remember that station WXQ had a wavelength of 344.6 meters, and that station BPR had a

wavelength of 215.7 meters, that another station had some other odd wavelength and so on, when those stations can be designated by kilocycles in whole numbers which are multiples of ten?

Let us take out a portion of the wavelength background of radio and view it in the light of broadcasting. Imagine that you can see the successive waves shooting out from the antenna of a broadcasting station operating on a frequency of 600 kilocycles. This means that 600 waves will cut through your receiving antenna in one second and each wave produces a cycle of current in your receiving circuit. To paint the picture somewhat differently: the alternating currents in the transmitting circuit are converted into waves and shot out into space; the waves are reconverted into alternating currents in your receiving set. Thus we see that waves exist only in space and when you tune your receiving circuit you are making it responsive to a certain frequency. A wave of 468.5 meters would have to be a great contortionist to get in your receiving set since such a wave is about a third of a mile in length! However, the frequency of 640 kilocycles corresponding to that wavelength can live quite comfortably in the small cabinet housing your receiving circuit.

DEPENDABLE RADIO EQUIPMENT

## TRANSMITTING APPARATUS

A Complete Stock at  
"CHIRAD"

**I**N addition to our regular broadcast apparatus we carry a very good stock of transformers, chokes, grid leaks, high test condensers, etc., for transmitting purposes.


*New Catalog Now Ready*

Dealers and set builders, write for our new catalog and special discounts. Please address us on your business letterhead.


**CHICAGO RADIO APPARATUS COMPANY**  
415 South Dearborn St.,  
Chicago

CHIRAD—RADIO—CHIRAD
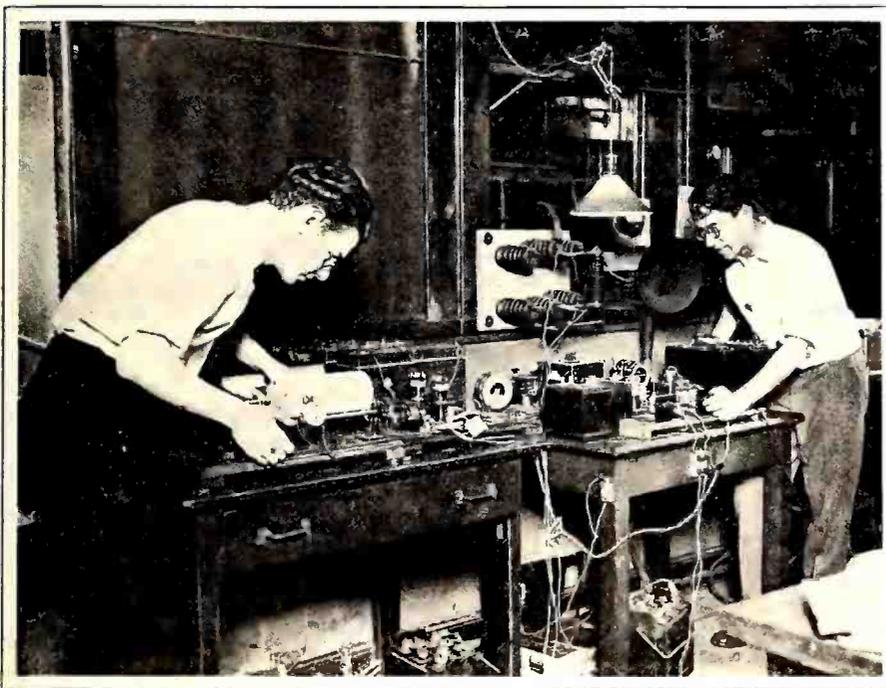
## U. of Chicago Gets Weather Maps by Radio



Experiments to determine the possibility of transmitting weather maps from Arlington to Chicago by means of radio are under way at the University of Chicago following the installation of new receiving apparatus in the university's laboratory. Tests over much shorter distances have already proven successful, Dr. F. L. Moulton, in charge of the experiments, stated. C. Francis Jenkins, inventor of the apparatus, is keeping in touch with progress made by the studio from Washington, every day

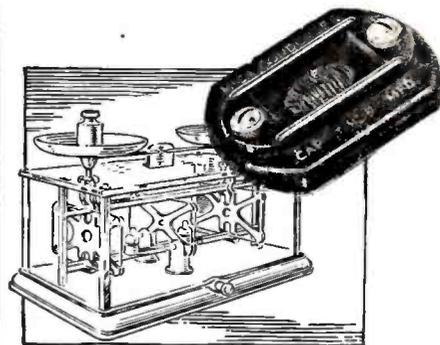

"Weighs out right capacity as accurately as the apothecary weighs out a precious drug." A.C.L.

TECHNICAL men are quick to appreciate Sangamo condensers in intermediate capacities. One engineer, well known to readers of radio publications,—Austin C. Lescarbourea—sends us the following characteristic comment, which is published with his consent:

"In my laboratory we develop new circuits and variations of old circuits, publishing the results in radio magazines. Needless to say, we are using and specifying Sangamo condensers throughout. In my opinion there is no other fixed condenser that can compare with the Sangamo in accuracy, permanent capacity, value, neatness, and handiness.

"The Sangamo condenser weighs out just the right capacity as the apothecary weighs out a precious drug."

## SANGAMO Mica Condensers

are made in 34 sizes, ranging from 0.00004 mfd. to 0.012 mfd. Sangamo Wound Condensers are ready in capacities from 1-10 mfd. to 4 mfd.; Series A guaranteed for continuous operation at 250 volts AC, 400 volts DC; Series B guaranteed at 500 volts AC, 1000 volts DC; also 12 and 14 mfd. blocks.



Sangamo Electric Company  
6332-10 Springfield, Illinois

RADIO DIVISION, 50 Church Street, New York

SALES OFFICES—PRINCIPAL CITIES  
For Canada—Sangamo Electric Co. of Canada, Ltd., Toronto  
For Europe—British Sangamo Co., Ponders End Middlesex, Eng.  
For Far East—Ashida Engineering Co., Osaka, Japan

### The Radio Storm Detector

(Continued from page 12)

and more frequently; the System Operator orders more boilers and generators put into use.

It is a race between man and nature. The faster the storm travels and the more intense the darkness accompanying it, the harder the men in the generating stations must work to beat it. No baseball game or horse race was ever more interesting. Usually when the storm is within half an hour of the city, our generating stations are all ready to cope with the situation. Finally the black clouds appear over Manhattan; hundreds of thousands of persons, perhaps a million—in the big office buildings, in the homes, the factories, the hospitals, the schools—all step to the wall and push a button; all want light at once, and they get it—thanks to the genius of Thomas Alva Edison, the development of the science of radio, the splendid organization of the Edison Company's operating men, and the determination of the Company to be always "At Your Service."



Horns  
\$22.50-\$25.00

Units  
\$10.00-\$12.00

### DOUBLE ENJOYMENT

From your set with

## Burns

### LOUD SPEAKER

Volume with Perfect Tone

Why sacrifice the excellent work of the set by using an inferior speaker? A BURNS will reproduce with pleasing exactness every tone and sound that the set can pick up.

At your dealers or direct.

American Electric Company

STATE AND 64TH STREETS  
CHICAGO, U. S. A.  
Ask about Burns "B" Eliminator

## Correct List of Broadcast Stations

KDKA	Westinghouse Electric & Mfg. Co.	EastPittsburgh, Pa.	309	KFQU	W. E. Riker	Holy City, Calif.	231
KDLR	Radio Electric Co.	Devils Lake, N. D.	231	KFQW	C. F. Knierim	Seattle, Wash.	216
KDYL	Newhouse Hotel	Salt Lake City, Utah	246	KFQZ	Taft Products Co.	Hollywood, Calif.	226
KFAB	Nebraska Buick Auto Co.	Lincoln, Neb.	341	KFRB	Hall Bros.	Beeville, Texas	248
KFAD	Electrical Equipment Co.	Phoenix, Ariz.	273	KFRD	City of Paris	San Francisco, Calif.	268
KFAF	A. E. Fowler	San Jose, Calif.	217	KFRU	Stephens College	Columbia, Mo.	500
KFAU	Independent School Dist.	Boise, Idaho	280	KFRW	Western Broadcasting Co.	Olympia, Wash.	219
KFBB	F. A. Buttrey & Co.	Havre, Mont.	275	KFSD	Airfan Radio Corp.	San Diego, Calif.	246
KFBC	W. Z. Azbill	San Diego, Cal.	380	KFSG	Echo Park Evan. Assn.	Los Angeles, Calif.	275
KFBK	Kimball-Upson Co.	Sacramento, Calif.	535	KFUL	Thomas Groggan & Bros.	Galveston, Texas	258
KFBL	Leese Bros.	Everett, Wash.	224	KFUM	W. D. Corley	Colorado Springs, Colo.	240
KFBS	School District No. One	Trinidad, Colo.	238	KFUO	Concordia Seminary	St. Louis, Mo.	545
KFBU	St. Matthews Cathedral	Laramie, Wyo.	375	KFUP	Fitzsimmons General Hospital	Denver, Colo.	234
KFCB	Nielson Radio Supply Co.	Phoenix, Ariz.	238	KFUR	Peery Bldg. Co., Inc.	Ogden, Utah	224
KFDD	St. Michael Cathedral	Boise, Idaho	275	KFUS	Louis L. Sherman	Oakland, Calif.	256
KFDM	Magnolia Petroleum Co.	Beaumont, Texas	316	KFUT	University of Utah	Salt Lake City, Utah	261
KFDX	First Baptist Church	Shreveport, La.	236	KFUU	H. C. Colburn and E. L. Mathewson	Oakland, Calif.	220
KFDY	South Dakota State College	Brookings, S. D.	306	KFVD	Chas. & W. J. McWhinnie	Venice, Calif.	205
KFDZ	Harry O. Iverson	Minneapolis, Minn.	231	KFVE	Benson Broadcasting Corp.	St. Louis, Mo.	240
KFEC	Meier & Frank	Portland, Ore.	248	KFVG	First M. E. Church	Independence, Kans.	236
KFEL	Eugene P. O'Fallon, Inc.	Denver, Colo.	254	KFVI	Headquarters Troop, 56th Cavalry	Houston, Texas	240
KFEQ	Scroggin & Co.	Oak, Neb.	268	KFVN	Carl E. Bagley	Fairmont, Minn.	227
KFEY	Bunker Hill & Sullivan	Kellogg, Idaho	233	KFVR	Moonlight Ranch	Denver, Colo.	244
KFFP	First Baptist Church	Moberly, Mo.	242	KFVS	Cape Girardeau Battery Sta., Cape Girardeau	Mo.	224
KFGQ	Crary Hardware Co.	Boone, Iowa	226	KFVY	Radio Supply Co.	Albuquerque, N. M.	250
KFH	Hotel Lassen	Wichita, Kans.	268	KFWB	Warner Bros. Pictures	Hollywood, Calif.	252
KFHA	Western State College of Colo.	Cunnison, Colo.	252	KFWC	L. E. Wall	San Bernardino, Calif.	291
KFHL	Penn. College	Oskaloosa, Iowa	240	KFWF	St. Louis Truth Center	St. Louis, Mo.	214
KFI	E. C. Anthony, Inc.	Los Angeles, Calif.	467	KFWH	F. Wellington Morse, Jr.	Eureka, Calif.	254
KFIF	Benson Polytechnic Institute	Portland, Ore.	248	KFWI	Radio Entertainments, Inc.	San Francisco, Calif.	250
KFIO	North Central High School	Spokane, Wash.	272	KFWM	Oakland Educational Society	Oakland, Calif.	316
KFIQ	First Methodist Church	Yakima, Wash.	256	KFWO	Lawrence Mott	Avalon, Calif.	211
KFIU	Alaska Electric Light & Power Co.	Juneau, Alaska	226	KFWU	Louisiana College	Pineville, La.	238
KFIZ	Commonwealth Reporter	Fond du Lac, Wis.	273	KFWV	Wilbur Jerman	Portland, Ore.	213
KFJB	Marshall Electric Co.	Marshalltown, Iowa	248	KFXB	Bertram C. Heller	Big Bear Lake, Calif.	203
KFJC	R. B. Fegan	Junction City, Kans.	219	KFXD	Service Radio Co.	Logan, Utah	205
KJFF	National Radio Mfg. Co.	Oklahoma City, Okla.	261	KFXF	Pike's Peak Broadcasting Co.	Denver, Colo.	430
KFJI	E. E. Marsh	Astoria, Ore.	246	KFXH	Bledsoe Radio Company	El Paso, Texas	242
KFJM	University of North Dakota	Grand Forks, N. D.	278	KFXJ	R. G. Howell	near Edgewater, Colo.	216
KFJR	Ashley C. Dixon & Son	Portland, Ore.	263	KFXR	Classen Film Finishing Co.	Oklahoma City, Okla.	214
KFJY	Tunwall Radio Co.	Fort Dodge, Iowa	246	KFXZ	Harry M. Costigan	Flagstaff, Ariz.	205
KFJZ	W. E. Branch	Ft. Worth, Tex.	254	KFYF	Carl's Radio Den.	Oxnard, Calif.	214
KFKA	Colo. State Teachers College	Greeley, Colo.	273	KFYJ	Houston Chronicle Pub. Co. (Portable)	Houston, Tex.	238
KFKB	J. R. Brinkley	Milford, Kan.	431	KFYO	Buchanan-Vaughan Co.	Texarkana, Tex.	210
KFKU	The University of Kansas	Lawrence, Kans.	275	KFYR	Hoskins-Meyer, Inc.	Bismarck, N. Dak.	248
KFKX	Westinghouse Elec. & Mfg. Co.	Hastings, Neb.	288	KGAR	Tucson Citizen	Tucson, Ariz.	244
KFKZ	Chamber of Commerce	Kirkville, Mo.	225	KGBS	A. C. Dailey	Seattle, Wash.	227
KFLR	University of New Mexico	Albuquerque, N. M.	254	KGBU	Alaska Radio Co.	Ketchikan, Alaska	229
KFLU	San Benito Radio Club	San Benito, Texas	236	KGBW	Martin Brotherson	Joplin, Mo.	283
KFLV	Swedish Evangelist Church	Rockford, Ill.	229	KGBX	J. B. Abercrombie	St. Joseph, Mo.	348
KFLX	George Roy Clough	Galveston, Texas	240	KGBY	Albert C. Dunning	Shelby, Nebr.	203
KFMR	Morningside College	Sioux City, Iowa	261	KGBZ	Federal Livestock Remedy Co.	York, Nebr.	333
KFMX	Carlton College	Northfield, Minn.	337	KGCA	C. W. Greenley	Decorah, Iowa	280
KFNF	Henry Field Seed Co.	Shenandoah, Iowa	461	KGCB	Wallace Radio Institute	Oklahoma, Okla.	331
KFOA	Rhodes Department Store	Seattle, Wash.	454	KGCG	Moore Motor Co.	Newark, Ark.	234
KFOB	KFOB, Inc.	Burlingame, Calif.	225	KGCH	Wayne Hospital	Wayne, Nebr.	450
KFON	Echophone Radio Shop	Long Beach, Calif.	233	KGCI	S. M. Rhodes	San Antonio, Texas	240
KFOO	Latter Day Saints' Union	Salt Lake City, Utah	236	KGCL	Louis Wasmer	Seattle, Washington	230
KFOR	Tire & Electric Co.	David City, Neb.	226	KGCM	Robert B. Bridge	San Antonio, Texas	263
KFOT	College Hill Radio Club	Wichita, Kans.	231	KGCN	Alva E. Smith	Concordia, Kansas	210
KFOX	Tech. High School	Omaha, Nebr.	248	KGCR	Cutler's Broadcasting Service	Brookings, S. D.	252
KFOY	Beacon Radio Service	St. Paul, Minn.	252	KGCX	First State Bank	Vida, Mont.	240
KFPL	C. C. Baxter	Dublin, Texas	252	KGDE	Jaren Drug Co.	Barrett, Minn.	232
KFPM	The New Furniture Co.	Greenville, Texas	242	KGO	General Electric Co.	Oakland, Calif.	361
KFPR	Los Angeles County Forestry Dept.	Los Angeles, Calif.	231	KGTT	Glad Tidings Tabernacle, Inc.	San Francisco, Calif.	207
KFPW	St. Johns M. E. Church	Cartersville, Mo.	258	KGU	Marion A. Mulrony	Honolulu, Hawaii	270
KFPY	Symons Investment Co.	Spokane, Wash.	273	KGW	Morning Oregonian	Portland, Ore.	492
KFQA	The Principia	St. Louis, Mo.	261	KGY	St. Martins College	Lacey, Wash.	278
KFQB	Lone Star Bdcast Co.	Fort Worth, Texas	508	KHJ	Times-Mirror Co.	Los Angeles, Calif.	405
KFQD	Anchorage Radio Club	Anchorage, Alaska	300	KHQ	Louis Wasmer	Spokane, Wash.	395
KFOP	G. S. Carson, Jr.	Iowa City, Ia.	224	KICK	Atlantic Automobile Co.	Anita, Ia.	273

## Start Radio with a Crystal Receiver

(Continued from page 7)

given conditions may not fit your conditions. That is why it is well to work out your own problems instead of following the other fellow's design.

A condenser is used with the inductance coil. One rated at .001 microfarads capacity comes about as near meeting the needs of the crystal detector set builder as any, but it is well to start with an elastic unit. Buy a frame, thirteen or more plates and a dial from the five-and-ten, or better ones that will last longer from a radio shop. Assemble all the plates, test out the condenser, then reduce the number of plates until the correct capacity for your needs is obtained.

**T**HERE is a certain balance that must be maintained between the coil and condenser. In the appendices of the radio textbooks found in public libraries are tables showing how much inductance and capacity are needed to tune to a given wavelength and keep out other wavelengths. More or less of each may be used, as long as the inductance and capacity, multiplied together, give the product required for the given wavelength. Don't remove the appendix just because the contents

are hard to digest—some other fellow may want to use it! Figuring out a coil and condenser for a desired range of wavelengths is not a very hard job for anyone who has covered grammar school arithmetic.


When you have your coil, hitch one end of it to the aerial and the other end to the ground wire. Connect the ends of the coil with the terminals of the condenser. If this does not work well, try connecting the condenser between the aerial and the coil. Then try it between the coil and the ground wire. The crystal should be connected between the two ends of the coil, with one phone cord tip on each side of the crystal. Or, the phones may be tried between the coil and the crystal, on either side of the latter.

While the experimental work is in progress, the parts may as well be strung out on a table where they can be hooked up and unhooked with the least trouble. After you have found a hook-up that brings in what you want, there will be time to design panels, cabinets, or lay-outs. Some like to anchor the apparatus to the table.

Circuit diagrams and constructional details for all types of crystal sets can be found in books at the libraries. Many have been published in this magazine. The Superintendent of Documents, Government Printing Office, Washington, D. C., sells good pamphlets at five to ten cents each. State colleges and universities have designed sets and issued instructions that can be obtained free of charge or for small sums.

Whether you are interested primarily in pleasure or profit, you cannot afford to overlook radio, for you can build a crystal set for less than five dollars that will keep you in touch with broadcasting stations within a radius of five to twenty-five miles and possibly reach out further. Most of the parts can be used later in a tube set, if you decide to build one, which you probably will!

## Every Radio Fan should have this book

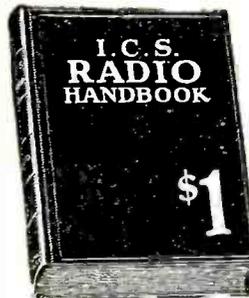

100,000 SOLD  
514 PAGES

Compiled by  
HARRY F. DART, E.E.

Formerly with the Western Electric Co., and U. S. Army Instructor of Radio. Technically edited by F. H. DOANE.

**B**E A RADIO expert—it's easy for the 100,000 who own this compact, complete Radio Handbook. Written in good, plain, understandable language. Crammed full of facts, every one useful and important. Explains how receivers and transmitters work, how to build and operate them. Whatever you or your friends want to know, it's here. Will save you many times its small cost.

**TELLS ALL ABOUT:** Electrical terms and circuits, antennas, batteries, generators and motors, electron (vacuum) tubes, most receiving hook-ups, radio and audio frequency amplification, broadcast and commercial transmitters and receiving, super-regeneration, codes, license rules. Many other features.

Nothing else like it. Make this extraordinary book your radio library—just this one little giant is all you need. Everything in one index, under one cover, in one book, for one dollar.

Just mail the coupon with a dollar bill and your name and address, and this 514-page I. C. S. Radio Handbook will be sent to you by return mail. Note the other good books listed below at low prices.

### INTERNATIONAL CORRESPONDENCE SCHOOLS

Box 8781-F, Scranton, Penna.


I enclose \$..... for which send me, post-paid, the Handbooks marked X, at \$1 each. It is understood that if I am not entirely satisfied I may return them within five days and you will refund my money.

- RADIO HANDBOOK, 514 PAGES, \$1**
- Automobile Handbook, 354 pages - \$1
- Electrical Handbook, 414 pages - \$1
- Chemistry Handbook, 348 pages - \$1
- Pharmacy Handbook, 324 pages - \$1
- Traffic Handbook, 358 pages - \$1
- Building Trades Handbook, 409 pages - \$1
- Machine Shop Handbook, 335 pages - \$1
- Salesman's Handbook, 352 pages - \$1
- Advertising Handbook, 415 pages - \$1
- Bookkeeper's Handbook, 302 pages - \$1
- Civil Engineer's Handbook, 411 pages - \$1
- Steam Engineer's Handbook, 298 pages - \$1

Name.....

Address.....

Enclose \$1.50 instead of \$1 for each book if you want the Leatheroid binding. All of the above books can be had in this binding except the Traffic Handbook and the Building Trades Handbook.

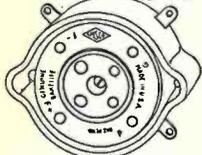**FLOATING SOCKETS**

Stop microphonic noises, mechanical feed-back and audio vibration!

Amsco Floating Sockets make it possible to operate your tubes at highest efficiency.

They take all the new type tubes—with the click that guarantees positive contact.

Ask your dealer or write for leaflet  
**AMSCO PRODUCTS, INC.**  
Broome and Lafayette Streets  
New York City



Learn **Electricity** in 12 Weeks by Actual Work in the Great Shops of Corne. Earn while you learn. Radio and Auto course Free. Special limited offer of **FRED** Railroad Fare to Chicago. **SEND AT ONCE FOR BIG NEW FREE BOOK!**


**COYNE ELECTRICAL SCHOOL** Dept. 96-76  
1300-1310 West Harrison Street Chicago, Illinois

### The Write Gift for Children

Individual Name **\$1.00**  
**PENCIL SETS**  
De Luxe Set: **1** post paid

Finest genuine sheepskin leather case with coin pocket, richly embossed. Any name engraved in 18 kt. gold. Contains pencils and penholder in assorted colors, point protector, ruler, sharpener. Absolutely supreme in its class.

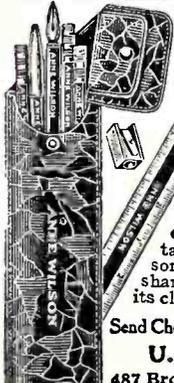Send Check, Money Order or U. S. Postage.  
**U. S. PENCIL CO., Inc.**  
487 Broadway Dept. Z, New York



KJBS	J. Brunton & Sons Co.	San Francisco, Calif.	234	WABY	John Magaldi, Jr.	Philadelphia, Pa.	242
KJR	Northwest Radio Service Co.	Seattle, Wash.	384	WABZ	Colis Place Baptist Church	New Orleans, La.	275
KLDS	Reorganized Church of Jesus Christ, Independence, Mo.		441	WADC	Allen T. Simmons	Akron, Ohio	258
KLS	Warner Brothers	Oakland, Calif.	250	WAFD	Albert P. Parfet	Port Huron, Mich.	275
KLX	Tribune Publishing Co.	Oakland, Calif.	508	WAGM	R. L. Miller	Royal Oak, Mich.	275
KLZ	Reynolds Radio Co.	Denver, Colo.	265	WAGS	Willow Garage, Inc.	Sommerville, Mass.	250
KMA	May Seed & Nursery	Shenandoah, Iowa	461	WAHG	A. H. Grebe	Richmond Hill, N. Y.	316
KMJ	Fresno Bee	Fresno, Calif.	234	WAIT	A. H. Waite & Co.	Taunton, Mass.	229
KMMJ	M. M. Johnson Co.	Clay Center, Nebr.	229	WAIU	American Insurance Union	Columbus, Ohio	294
KMO	Love Electric Co.	Tacoma, Wash.	250	WAMDR	Raddison Radio Corp.	Minneapolis, Minn.	244
KMOX	Voice of St. Louis	St. Louis, Mo.	280	WAPI	Alabama Polytechnic Institute	Auburn, Ala.	461
KMTR	Echophone Mfg. Co.	Los Angeles, Calif.	372	WARC	American Radio & Research	Medford, Mass.	261
KNRC	C. B. Juneau	Hollywood, Calif.	208	WASH	Baxter Laundry Co.	Grand Rapids, Mich.	256
KNX	Los Angeles Express	Los Angeles, Calif.	337	WATT	Edison Elec. Illum. (Portable)	Boston, Mass.	244
KOA	General Electric Co.	Denver, Colo.	322	WBAA	Purdue University	W. Lafayette, Ind.	273
KOAC	Oregon Agriculture College	Corvallis, Ore.	280	WBAC	James Milliken University	Decatur, Ill.	270
KOB	N. Mex. College of Agric.	State College, N. Mex.	349	WBAK	Pennsylvania State Police	Harrisburg, Pa.	275
KOCH	Omaha Central High School	Omaha, Neb.	258	WBAL	Consolidated Gas & Power Co.	Baltimore, Md.	246
KOCW	Oklahoma College for Women	Chickasha, Okla.	252	WBAP	Carter Publications, Inc.	Ft. Worth, Tex.	476
KOIL	Mona Motor Oil Co.	Council Bluffs, Iowa	306	WBAW	Braid Elec. Co. & Waldrum Drug Co.	Nashville, Tenn.	236
KOIN	KOIN, Inc.	Portland, Ore.	319	WBAX	John H. Stenger, Jr.	Wilkes-Barre, Pa.	256
KOMO	Birt F. Fisher	Seattle, Wash.	306	WBBC	P. J. Testan	Brooklyn, N. Y.	250
KOWW	Frank A. Moore	Walla Walla, Wash.	285	WBBL	Grace Covenant Presbyterian Church	Richmond, Va.	229
KPJM	Wilburn Radio Service	Prescott, Ariz.	215	WBBM	Atlas Investment	Chicago, Ill.	226
KPO	Hale Bros., Inc.	San Francisco, Calif.	428	WBBP	Petoskey High School	Petoskey, Mich.	238
KPPC	Pasadena Presbyterian Church	Pasadena, Calif.	229	WBBR	People's Pulpit Assoc.	Rossville, N. Y.	416
KPRC	Houston Printing Co.	Houston, Texas	297	WBBS	First Baptist Church	New Orleans, La.	252
KPSN	Star-News	Pasadena, Calif.	316	WBBW	Ruffner Junior High School	Norfolk, Va.	222
KQW	First Baptist Church	San Jose, Calif.	333	WBBY	Washington Light Inf.	Charleston, S.C.	268
KQV	Doubleday-Hill Electric Co.	Pittsburgh, Pa.	275	WBBZ	C. L. Carrell	(Portable,) Chicago Ill.	216
KRE	Berkeley Daily Gazette	Berkeley, Calif.	256	WBCN	Foster & McDonnell	Chicago, Ill.	266
KSAC	Kansas State Agricultural College	Manhattan, Kans.	341	WBES	Bliss Electrical School	Takoma Park, Md.	222
KSD	Pulitzer Publishing Co.	St. Louis, Mo.	545	WBMS	G. J. Schowerer	North Bergen, N. J.	224
KSEI	Broadcasting Association	Pocatello, Idaho	261	WBNY	Baruschrome Corp.	New York, N. Y.	322
KSL	Radio Service Corp.	Salt Lake City, Utah	300	WBOQ	A. H. Grebe & Co., Inc.	Richmond Hill, N. Y.	236
KSMR	Santa Maria Valley Railroad	Santa Maria, Calif.	283	WBRC	Birmingham Broadcasting Co.	Birmingham, Ala.	248
KSO	A. A. Berry Seed Co.	Clarinda, Iowa	242	WBRE	Baltimore Radio Exchange	Wilkes-Barre, Pa.	231
KTAB	Associated Broadcasters	Oakland, Calif.	303	WBRL	Booth Radio Laboratories	Tilton, N. H.	365
KTBI	Bible Institute	Los Angeles, Calif.	294	WBRS	Universal Radio Mfg. Co.	Brooklyn, N. Y.	394
KTBR	M. E. Brown	Portland, Ore.	263	WBT	Charlotte Chamber of Commerce	Charlotte, N. C.	275
KTHS	New Arlington Hotel	Hot Springs, Ark.	375	WBZ	Westinghouse Elect. & Mfg. Co.	Springfield, Mass.	333
KTNT	N. Baker	Muscatine, Iowa	333	WBZA	Westinghouse Elect. & Mfg. Co.	Boston, Mass.	333
KTUE	Uhalt Electric	Houston, Texas	263	WCAC	Connecticut Agricultural College	Mansfield, Conn.	275
KTW	First Presbyterian Church	Seattle, Wash.	454	WCAD	St. Lawrence University	Canton, N. Y.	263
KUOA	University of Arkansas	Fayetteville, Ark.	300	WCAE	Kaufman & Baer Co.	Pittsburgh, Pa.	461
KUOM	University of Montana	Missoula, Mont.	244	WCAJ	Nebraska Wesleyan University	University Place, Nebr.	254
KUSD	University of South Dakota	Vermillion, S. D.	278	WCAL	St. Olaf College	Northfield, Minn.	337
KUT	University of Texas	Austin, Texas	231	WCAM	City of Camden	Camden, N. J.	236
KVOO	Southwestern Sales Corp.	Bristow, Okla.	375	WCAO	Brager, of Baltimore	Baltimore, Md.	275
KWCR	H. F. Parr	Cedar Rapids, Iowa	278	WCAP	Chesapeake & Potomac Tel. Co.	Washington, D. C.	469
KWG	Portable Wireless Telegraph Co.	Stockton, Calif.	248	WCAR	Southern Radio Corp.	San Antonio, Texas	263
KWKC	Wilson Duncan Studios	Kansas City, Mo.	236	WCAT	School of Mines	Rapid City, S. Dak.	240
KWKH	W. G. Patterson	Kennonwood, La.	312	WCAU	Universal Broadcasting Co.	Philadelphia, Pa.	278
KWSC	State College of Washington	Pullman, Wash.	349	WCAX	University of Vermont	Burlington, Vt.	250
KWTC	J. W. Hancock	Santa Ana, Calif.	261	WCAZ	Carthage College	Carthage, Ill.	246
KWUC	Western Union College	Le Mars, Iowa	252	WCBA	Charles W. Heimbach	Allentown, Pa.	254
KWWG	City of Brownsville	Brownsville, Texas	278	WCBD	Wilbur Glenn Voliva	Zion, Ill.	345
KXRO	Brott Laboratories	Seattle, Wash.	240	WCBE	Uhalt Radio Co.	New Orleans, La.	263
KYW	Westinghouse Electric & Mfg. Co.	Chicago, Ill.	535	WCBH	University of Mississippi	Oxford, Miss.	242
KZM	Preston D. Allen	Oakland, Calif.	240	WCBM	Hotel Chateau	Baltimore, Md.	229
WAAD	Ohio Mechanical Institute	Cincinnati, Ohio	258	WCBR	C. H. Messter	Portable	210
WAAF	Chicago Daily Drivers Journal	Chicago, Ill.	278	WCBS	H. L. Dewing	Portable, Boston Mass.	242
WAAM	Isaiah R. Nelson	Newark, N. J.	263	WCCO	Washburn-Crosby Co.	Anoka, Minn.	416
WAAT	F. V. Bremer	Jersey City, N. J.	235	WCFL	Chicago Fed. of Labor	Chicago, Ill.	492
WAAW	Omaha Grain Exchange	Omaha, Nebr.	384	WCFT	Knights of Pythias Home	Tullahoma, Tenn.	252
WABB	Harrisburg Radio Co.	Harrisburg, Pa.	204	WCLO	C. E. Whitmore	Camp Lake Wis.	231
WABC	Asheville Battery Co.	Asheville, N. C.	254	WCLS	H. M. Couch	Joliet, Ill.	214
WABI	1st Universalist Church	Bangor, Me.	240	WCMA	Culver Military Academy	Culver, Ind.	258
WABO	Hickson Elec. Co., Inc.	Rochester, N. Y.	278	WCOA	City of Pensacola	Pensacola, Fla.	222
WABQ	Haverford College Radio Club	Haverford, Pa.	261	WCRW	Clinton R. White	Chicago, Ill.	416
WABR	Scott High School	Toledo, Ohio	263	WCSH	Henry R. Rines	Portland, Maine	500
WABW	College of Wooster	Wooster, Ohio	207	WCSSO	Wittenberg College	Springfield, Ohio	248
WABX	Henry B. Joy	Mt. Clemens, Mich.	246	WCWK	Chester W. Keen	Fort Wayne, Ind.	234


**Dry Cell Batteries  
or Eliminators?**

WITH so many and varied battery substitutes on the market this fall, the question of whether to use "B" batteries or socket-power devices is going to assume important proportions in the minds of many radio enthusiasts. Set owners and prospective set owners already are asking whether batteries or house-current attachments are more dependable, more economical, more generally satisfactory for "B" current supply.

Unfortunately, these questions cannot be answered as promptly and as emphatically now as they may be answered a few years hence. Socket-power devices, for "B" power supply may be vastly improved within the next few years and may be produced at considerably smaller costs than those which prevail today. On the other hand, the useful life of dry batteries may be decidedly lengthened by laboratory and manufacturing achievements in the near future. In this connection it may be well to remember that comparatively recently the process of building dry "B" batteries in layer cells rather than in cylindrical units, has lengthened battery life, for average use, approximately fifty per cent.

However, careful comparison of dry-cell "B" batteries and house-current "B" power devices as they are today, has brought to light certain general rules which may guide the set owner toward selection of the "B" power supply which is best suited to the needs of his individual set.

Radio receiving sets must be divided into two general classes, insofar as power requirements are concerned—namely, those which consume so much power that dry cell "B" batteries are inadequate to meet the demand for power, and those which consume so little power that dry cell "B" batteries can be relied upon to run them economically and dependably. So, after all, the real key to the set owner's solution of the problem of batteries versus "eliminators," lies in ascertaining whether his set is within the class which can depend only upon "eliminators" or within the class

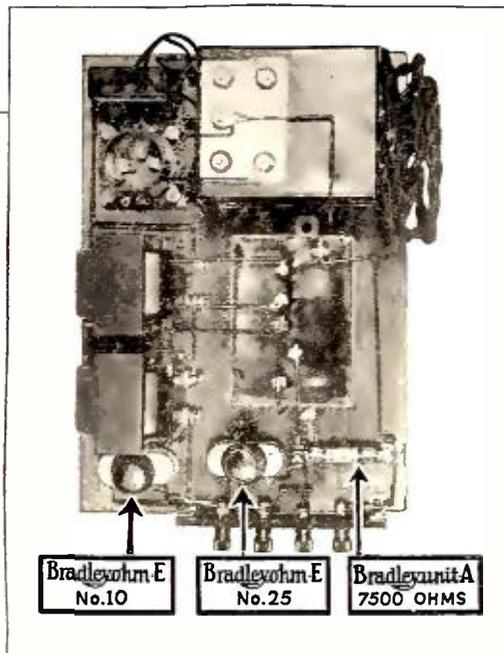

**What a whale of a difference  
a few Bradleyohms make  
—in a B-Eliminator!**



**Bradleyohm-E**

For B-eliminator service requiring wide voltage control, Bradleyohm-E is essential. It is an oversize Bradleyohm with sufficient capacity to handle all normal B-eliminator requirements. Be sure to ask for Bradleyohm-E in the checkered carton. Your dealer can get them for you.



**Bradleyunit-A**

This solid, molded, fixed resistor has no glass or hermetic sealing in its construction. It is a solid unit with silver-plated end caps that are not affected by temperature, moisture and age. By all means, use Bradleyunit-A when you need a fixed resistor.

MAGAZINES and newspapers have been publishing circuits and instructions for assembling B-eliminators. Many types of kits have been used, but the outstanding feature has been the almost unanimous recommendation to use Bradleyohm-E for plate voltage control and Bradleyunit-A for the fixed resistor.

The leading manufacturers of B-eliminators have long since adopted Allen-Bradley variable and fixed resistors as standard equipment for their B-eliminators. In fact, the Bradleyohm-E has become almost as universally used in Raytheon tube B-eliminators as the Raytheon tube itself. The scientifically-treated graphite discs in these remarkable units have never been equaled for silent, stepless plate voltage control so essential for the satisfactory operation of a radio set with a B-eliminator.

When you build your B-eliminator, always insist that Bradleyohm-E and Bradleyunit-A are included with kit. You then will be assured of perfect voltage control. Send for folder "How to Build a B-eliminator" describing seven popular hookups.

**ALLEN-BRADLEY CO.**

289 Greenfield Ave. :: Milwaukee, Wis.

*Use*  
**Allen-Bradley**  
**Perfect Radio Devices**

WCWS Chas. W. Selene (Portable).....	Mass.	210	WGR Federal T. and T. Co.....	Buffalo, N. Y.	319
WCX Detroit Free Press.....	Pontiac, Mich.	517	WGST Georgia School of Technology.....	Atlanta, Ga.	270
WDAD Dad's Auto Accessories, Inc.....	Nashville, Tenn.	226	WGWB Radiocast Corporation.....	Milwaukee, Wis.	384
WDAE Tampa Daily Times.....	Tampa, Fla.	273	WGY General Elec. Co.....	Schenectady, N. Y.	379
WDAF Kansas City Star.....	Kansas City, Mo.	366	WHA University of Wisconsin.....	Madison, Wis.	535
WDAG J. Laurence Martin.....	Amarillo, Texas	263	WHAD Marquette University.....	Milwaukee, Wis.	275
WDAH Trinity Methodist Church.....	El Paso, Texas	268	WHAM Eastman School of Music.....	Rochester, N. Y.	278
WDAY Radio Equipment Corp.....	Fargo, N. Dak.	261	WHAP W. H. Taylor Finance Corp.....	New York, N. Y.	431
WDBE Gilham-Schoen Elec. Co.....	Atlanta, Ga.	270	WHAR F. D. Cooks Sons.....	Atlantic City, N. J.	275
WDBJ Richardson Wayland Elec. Corp.....	Roanoke, Va.	229	WHAS Courier-Journal & Louisville Times.....	Louisville, Ky.	400
WDBK M. F. Broz.....	Cleveland, Ohio	227	WHAZ Rensselaer Polytechnic Institute.....	Troy, N. Y.	379
WDBO Rollins College.....	Winter Park, Fla.	240	WHB Sweeney School Co.....	Kansas City, Mo.	366
WDBZ Kingston Radio Club.....	Kingston, N. Y.	233	WHBA C. C. Shaffer.....	Oil City, Pa.	250
WDEL Wilmington Elec. Specialty Co.....	Wilmington, Del.	266	WHBC Rev. E. P. Graham.....	Canton, Ohio	254
WDGY Dr. George W. Young.....	Minneapolis, Minn.	263	WHBD Chamber of Commerce.....	Bellefontaine, Ohio	222
WDOD Chattanooga Radio Co., Inc.....	Chattanooga, Tenn.	256	WHBF Beardsley Specialty Company.....	Rock Island, Ill.	222
WDRG Doolittle Radio Corp.....	New Haven, Conn.	268	WHBG John S. Skane.....	Harrisburg, Pa.	231
WDWF Dutee Wilcox Flint, Inc.....	Cranston, R. I.	441	WHBL C. L. Carrell (Portable).....	Chicago, Ill.	216
WDXL DXL Radio Corp.....	Detroit, Mich.	297	WHBM C. L. Carrell, (Portable).....	Chicago, Ill.	216
WDZ J. L. Bush.....	Tuscola, Ill.	278	WHBN First Ave. Methodist Church.....	St. Petersburg, Fla.	238
WEAF Broadcasting Co. of America.....	New York, N. Y.	491	WHBP Johnstown Automobile Co.....	Johnstown, Pa.	256
WEAI Cornell University.....	Ithaca, N. Y.	254	WHBQ St. John's M. E. Church South.....	Memphis, Tenn.	233
WEAM Bor. of N. Plainfield.....	North Plainfield, N. J.	261	WHBU Riviera Theatre & Bing's Clothing.....	Anderson, Ind.	219
WEAN The Shepard Co.....	Providence, R. I.	367	WHBWD R. Kienzle.....	Philadelphia, Pa.	216
WEAO Ohio State University.....	Columbus, Ohio	294	WHBY St. Norbert's College.....	West de Pere, Wis.	250
WEAR Willard Storage Battery Co.....	Cleveland, Ohio	389	WHDI W. H. Dunwoody Institute.....	Minneapolis, Minn.	278
WEAU Davidson Bros. Co.....	Sioux City, Iowa	275	WHEC Hickel Electric Co., Inc.....	Rochester, N. Y.	258
WEBC Walter Cecil Bridges.....	Superior, Wis.	242	WHFC Hotel Flanders.....	Chicago, Ill.	258
WEBH Edgewater Beach Hotel.....	Chicago, Ill.	370	WHK The Radio Air Service Corp.....	Cleveland, Ohio	273
WEBJ Third Avenue Railway Co.....	New York, N. Y.	273	WHN George Schubel.....	New York, N. Y.	361
WEBL R. C. A. Show (Portable).....	New York, N. Y.	226	WHO Banker's Life Co.....	Des Moines, Ia.	526
WEBQ Tate Radio Corp.....	Harrisburg, Ill.	226	WHT Radiophone Broadcasting Corp.....	Deerfield, Ill.	238
WEBR H. H. Howell.....	Buffalo, N. Y.	244	WIAD Howard R. Miller.....	Philadelphia, Pa.	250
WEBW Beloit College.....	Beloit, Wis.	268	WIAS Home Electric Co.....	Burlington, Iowa	254
WEBZ Savannah Radio Corp.....	Savannah, Ga.	263	WIBA Capital Times-Strand Theatre.....	Madison, Wis.	236
WEDC E. Denmark Station.....	Chicago, Ill.	422	WIBG St. Paul' Protestant E. Church.....	Elkins Park, Pa.	222
WEEI The Edison Elec. Illuminating Co.....	Boston, Mass.	349	WIBH Elite-Radio Stores.....	New Bedford, Mass.	210
WEHS Oliver G. Fordham.....	Evanston, Ill.	203	WIBI Frederick B. Zittel, Jr.....	Flushing, L. I., N. Y.	219
WEMC Emanuel Missionary College.....	Berrien Springs, Mich.	316	WIBJ C. L. Carrell (Portable).....	Chicago, Ill.	216
WENR All-American Radio Corp.....	Chicago, Ill.	266	WIBM Billy Maine (Portable).....	Chicago, Ill.	216
WEW St. Louis University.....	St. Louis, Mo.	360	WIBO Nelson Brothers.....	Chicago, Ill.	226
WFAA Dallas News & Dallas Journal.....	Dallas, Tex.	476	WIBR Thurman A. Owings.....	Weirton, W. Va.	246
WFAM Times Publishing Co.....	St. Cloud, Minn.	273	WIBS T. F. Hunter.....	Elizabeth, N. J.	203
WFAV University of Nebraska.....	Lincoln, Neb.	275	WIBU The Electric Farm.....	Poynette, Wis.	222
WFBK First Baptist Church.....	Knoxville, Tenn.	250	WIBW Dr. L. L. Dill.....	Logansport, Ind.	220
WFBE J. V. De Walle.....	Seymour, Ind.	226	WIBX WIBX, Inc.....	Utica, N. Y.	234
WFBG The Wm. F. Gable Co.....	Altoona, Pa.	278	WIBZ A. D. Trum.....	Montgomery, Ala.	231
WFBJ St. John's University.....	Collegeville, Minn.	236	WIL Benson Radio Co.....	St. Louis, Mo.	258
WFBM Onondaga Hotel Co.....	Syracuse, N. Y.	252	WIOD Earl G. Fisher Co.....	Miami, Fla.	248
WFBM Merchants Heat & Light Co.....	Indianapolis, Ind.	268	WIP Gimbel Bros.....	Philadelphia, Pa.	508
WFBR Fifth Infantry National Guard.....	Baltimore, Md.	254	WJAD Jackson's Radio Eng. Laboratories.....	Waco, Texas	353
WFBZ Knox College.....	Galesburg, Ill.	254	WJAF J. S. Fenberg.....	Ferndale, Mich.	407
WFCI Frank Crook, Inc.....	Pawtucket, R. I.	229	WJAG Norfolk Daily News.....	Norfolk, Neb.	270
WFDG F. D. Fallain.....	Flint, Mich.	234	WJAK Kokomo Tribune.....	Kokomo, Ind.	254
WFI Strawbridge and Clothier.....	Philadelphia, Pa.	394	WJAM D. M. Perham.....	Cedar Rapids, Iowa	268
WFKB Vesta Battery Corp.....	Chicago, Ill.	217	WJAR The Outlet Co.....	Providence, R. I.	306
WFRL Robert Morrison Lacey.....	Brooklyn, N. Y.	205	WJAS Pittsburgh Radio Supply House.....	Pittsburgh, Pa.	275
WGAL Lancaster Elec. Supply & Const. Co.....	Lancaster, Pa.	248	WJAX City of Jacksonville.....	Jacksonville, Fla.	337
WGBB H. H. Carman.....	Freeport, N. Y.	244	WJAZ American Bdcast Corp.....	Mt. Prospect, Ill.	329
WGBC First Baptist Church.....	Memphis, Tenn.	278	WJBA D. H. Lentz, Jr.....	Joliet, Ill.	207
WGBF Fink Furniture Co.....	Evansville, Ind.	236	WJBB Financial Journal.....	St. Petersburg, Fla.	254
WGBL Scranton Broadcasters, Inc.....	Scranton, Pa.	240	WJBC Hummer Furniture Co.....	LaSalle, Ill.	234
WGBS Gimbel Brothers.....	Astoria, L. I., N. Y.	316	WJBI Robert S. Johnson.....	Red Bank, N. J.	219
WGBU Florida Cities Finance Co.....	Fulford By-The-Sea, Fla.	278	WJBK E. F. Goodwin.....	Ypsilanti, Mich.	233
WGBX University of Maine.....	Orono, Me.	234	WJBL Wm. Gushard Dry Goods Co.....	Decatur, Ill.	270
WGCP May Radio Broadcast Corp.....	Newark, N. J.	252	WJBO Valdemar Jensen.....	New Orleans, La.	268
WGES Oak Leaves Broadcasting Corp.....	Chicago, Ill.	316	WJBR Omro Drug Stores.....	Omro, Wis.	227
WGHF Fort Harrison Hotel.....	Clearwater, Fla.	266	WJBT John S. Boyd.....	Chicago, Ill.	468
WGHP G. H. Phelps.....	Detroit, Mich.	270	WJBU Bucknell University.....	Lewisburg, Pa.	211
WGM Verne and Elton Spencer.....	Jeanette, Pa.	372	WJBV Union Course Laboratories.....	Woodhaven, N. Y.	288
WGMUA, H. Grebe & Co. (Portable) New York.....		236	WJBW C. Carlson, Jr.....	New Orleans, La.	270
WGN The Tribune.....	Chicago, Ill.	303	WJBX Henderson & Ross.....	Osterville, Mass.	280

for which batteries are not only more economical, but also more satisfactory generally.

Of course, at present, the high power sets which must use "eliminators," are comparatively few in number. There are some, however, which operate at abnormally high voltages—180 volts or more—and such sets will exhaust the very best of the heavy duty "B" batteries so rapidly that the upkeep expense becomes burdensome. On such receivers, the comparatively high first-cost of the really dependable socket-power device is fully justified.

For the customary types of receivers operating at normal "B" voltage of 90 or 135 volts, well made, heavy duty "B" batteries usually are cheaper than any other form of "B" power supply, are not subject to any of the power interruptions to which any house-current device is subject, and, of course, supply the only pure direct current. The money spent for a good "eliminator" will keep the average set of this class supplied with heavy duty "B" batteries for three years or more and unless the "eliminator" can be used for three years without repairs or replacements, the eliminator will be much more costly than batteries in the long run.

Most of the instances of so-called battery trouble can be traced to the use of the wrong size "B" battery. Practically all of the receiving sets in use today should be powered with the heavy duty size, rather than the smaller light duty "B" battery.

### Spokane To Get New Broadcasting Station

**C**ONSTRUCTION on a broadcasting station to cost between \$50,000 and \$75,000, will be started at Spokane, Wash., immediately.

The new station will be linked with four other new Pacific coast plants, making one of the most powerful broadcasting chains in the country.

Announcement of the coming of this new station to Spokane was made recently by W. A. Watson of Seattle, superintendent and engineer of the chain. J. H. Sahlin of Spokane, is local manager and director.

# THE RADIO AGE BUYERS' SERVICE

What do you want to purchase in the radio line? Let RADIO AGE save you time and money by sending in the coupon below. Enter the number of the article you would like to know more about in the spaces provided in the coupon:

- |                            |                            |
|----------------------------|----------------------------|
| 1 "A" Batteries, all kinds | 45 Jacks                   |
| 2 Aerials                  | 46 Jars, battery           |
| (a) Loop                   | 47 Keys, transmitting      |
| (b) Outdoor                | 48 Knobs                   |
| 3 Ammeters                 | 49 Laboratories, testing   |
| 4 Amplifiers               | 50 Lightning arresters     |
| 5 "B" batteries, all kinds | 51 Loud speakers           |
| 6 Batteries (A and B)      | 52 Lugs, battery           |
| (a) Dry                    | 53 Meters, all types       |
| (b) Wet                    | 54 Mica                    |
| 7 Battery chargers         | 55 Mountings               |
| 8 Battery substitutes      | 56 Nuts                    |
| (a) "A" battery            | 57 Panels                  |
| (b) "B" battery            | 58 Paste, soldering        |
| 9 Battery supplies         | 59 Patent attorneys        |
| 10 Bezels                  | 60 Phone connectors        |
| 11 Binding posts           | 61 Phonograph adapters     |
| 12 Books on radio          | 62 Plugs                   |
| 13 Broadcasting equipment  | 63 Pointers                |
| 14 Buzzers                 | 64 Potentiometers          |
| 15 "C" batteries           | 65 Rectifiers              |
| 16 Cabinets                | 66 Resistances, fixed      |
| 17 Code practice sets      | 67 Rheostats               |
| 18 Coils, all forms        | 68 Scrapers, wire          |
| 19 Condensers, fixed       | 69 Screw drivers           |
| 20 Condensers, variable    | 70 Screws                  |
| 21 Contact points          | 71 Schools, radio          |
| 22 Cords, headset, etc.    | 72 Sets, transmitting      |
| 23 Couplers, vario, etc.   | 73 Sets, receiving         |
| 24 Crystals                | (a) Factory Built (b) kits |
| 25 Desks                   | 1 Crystal                  |
| 26 Detector (crystals)     | 2 Radio Frequency          |
| 27 Detector tubes          | 3 Reflex                   |
| 28 Detector units          | 4 Regenerative             |
| 29 Dials                   | 5 Super-heterodyne         |
| 30 Dies                    | 74 Shellac                 |
| 31 Drills                  | 75 Sockets                 |
| 32 Electrolyte             | 76 Solder                  |
| 33 Fibre                   | 77 Supports, aerial        |
| 34 Filters                 | 78 Switches                |
| 35 Fuses, tube             | 79 Transformers, a. f.     |
| 36 Grid leaks              | 80 Transformers, r. f.     |
| 37 Ground clamps           | 81 Transformers, sending   |
| 38 Head phones             | 82 Tubes, all types        |
| 39 Horns, all types        | 83 Variometers             |
| 40 Hydrometers             | 84 Wave meters             |
| 41 Inductances             | 85 Wave traps              |
| 42 Insulation              | 86 Wire, all kinds         |
| 43 Insulators, all types   |                            |
| 44 Irons, soldering        |                            |

#### RADIO AGE BUYERS' SERVICE

500 N. Dearborn St., Chicago, Ill.

Please see that I am supplied with buying specifications and prices on the articles numbered herewith:

--	--	--	--	--	--	--	--	--	--

I am a— Dealer     Jobber     Mfgs.' Rep.     Manufacturer

Firm (If identified with Radio industry).....

My Occupation .....

My Name .....

Address .....

City ..... State .....

WJBY Electric Construction Co.....Gadsden, Ala. 270  
 WJJD Supreme Lodge, L. O. of Moose.....Mooseheart, Ill. 370  
 WJR Jewett Radio & Phonograph Co.....Pontiac, Mich. 517  
 WJUG U. B. Ross.....New York, N. Y. 517  
 WJY Radio Corp. of America.....New York, N. Y. 405  
 WJZ Radio Corp. of America.....Bound Brook, N. J. 454  
 WKAF WKAF Broadcasting Co.....Milwaukee, Wis. 261  
 WKAQ Radio Corp. of Porto Rico.....San Juan, P. R. 341  
 WKAR Michigan State College.....East Lansing, Mich. 286  
 WKAU Laconia Radio Club.....Laconia, N. H. 422  
 WKBA Arrow Battery Co.....Chicago, Ill. 210  
 WKBB Sanders Bros.....Joliet, Ill. 283  
 WKBC H. L. Ansley.....Birmingham, Ala. 225  
 WKBE K. & D. Electric Co.....Webster, Mass. 270  
 WKBF N. D. Watson.....Indianapolis, Ind 244  
 WKBG C. L. Carrell (Portable).....Chicago, Ill. 216  
 WKBH Callaway Music Co.....LaCrosse, Wis. 250  
 WKBI F. L. Schoenwolf.....Chicago, Ill. 220  
 WKBJ Gospel Tabernacle Inc.....St. Petersburg, Fla. 280  
 WKBL Monrona Radio Mfg. Co.....Monroe, Mich. 252  
 WKBM J. W. Jones.....Newburgh, N. Y. 215  
 WKBO Camith Corporation.....Jersey City, N. J. 309  
 WKBP Enquirer and News.....Battle Creek, Mich. 265  
 WKBQ Starlight Amusement Park.....New York, N. Y. 285  
 WKBR C. J. Heiser.....Auburn, N. Y. 225  
 WKBS P. M. Nelson.....Galesburg, Ill. 361  
 WKBV Knox Battery and Electric Co.....Brookville, Ind. 236  
 WKDR Edward A. Dato.....Kenosha, Wis. 428  
 WKJC Kirk Johnson & Co.....Lancaster, Pa. 258  
 WKRC Kodol Radio Corp.....Cincinnati, Ohio 422  
 WKY Hull and Richards.....Oklahoma City, Okla. 275  
 WLAL First Christian Church.....Tulsa, Okla. 250  
 WLAP Wm. V. Jordan.....Louisville, Ky. 275  
 WLB University of Minnesota.....Minneapolis, Minn. 278  
 WLBL Wisconsin Dept. of Markets.....Stevens Point, Wis. 278  
 WLJB Liberty Weekly, Inc.....Elgin, Ill. 303  
 WLIT Lit Bros.....Philadelphia, Pa. 394  
 WLS Sears Roebuck & Co.....Crete, Ill. 345  
 WLSL Lincoln Studios.....Cranston, R. I. 441  
 WLTS Lane Technical High School.....Chicago, Ill. 258  
 WLW Crosley Radio Corp.....Harrison, Ohio 422  
 WLWL Paulist Fathers.....New York, N.Y. 384  
 WMAC C. B. Meredith.....Casenovia, N. Y. 275  
 WMAF Round Hills Radio Corp.....Dartmouth, Mass. 441  
 WMAK Norton Laboratories.....Lockport, N. Y. 266  
 WMAL M. A. Leese Optical Co.....Washington, D. C. 290  
 WMAN Haskett Radio Station.....Columbus, Ohio 278  
 WMAQ Chicago Daily News.....Chicago, Ill. 447  
 WMAY Kingshighway Presbyterian Church.....St. Louis, Mo. 248  
 WMAZ Mercer University.....Macon, Ga. 261  
 WMBB American Bond & Mortgage Co.....Chicago, Ill. 250  
 WMBC Michigan Broadcasting Co., Inc.....Detroit, Mich. 256  
 WMBF Fleetwood Hotel Corp.....Miami Beach, Fla. 384  
 WMBI Moody Bible Institute.....Chicago, Ill. 288  
 WMC Commercial Pub. Co.....Memphis, Tenn. 500  
 WMCAGreely Sq. Hotel Co.....Hoboken, N. J. 341  
 WMRJ Peter J. Prinz.....Jamaica, N. Y. 227

WMSG Madison Sq. Gard. Bdcast. Corp. New York, N. Y. 302  
 WNAB Shepard Stores.....Boston, Mass. 280  
 WNAC Shepard Stores.....Boston, Mass. 430  
 WNAD University of Oklahoma.....Norman, Okla. 254  
 WNAL Omaha Central High School.....Omaha, Nebr. 258  
 WNAT Lenning Brothers Co.....Philadelphia, Pa. 250  
 WNAX Dakota Radio Apparatus Co.....Yankton, S. Dak. 244  
 WNBH New Bedford Hotel.....New Bedford, Mass. 248  
 WNJ Radio Shop.....Newark, N. J. 252  
 WNOX Peoples Tel. & Tel. Co.....Knoxville, Tenn. 268  
 WNRC W. B. Nelson.....Greensboro, N. C. 224  
 WNYC Dept. of Plants & Structures.....New York, N. Y. 526  
 WOAI Southern Equipment Co.....San Antonio, Texas 394  
 WOBB Longacre Eng. & Const. Co.....Chicago, Ill. 555  
 WOAN J. D. Vaughn.....Lawrenceburg, Tenn. 283  
 WOAW Woodman of the World.....Omaha, Nebr. 526  
 WOAX Franklyn J. Wolff.....Trenton, N. J. 240  
 WOCB Orlando Broadcasting Co.....Orlando, Fla. 294  
 WOC Palmer School of Chiropractic.....Davenport, Iowa 484  
 WOCL A. D. Newton.....Jamestown, N. Y. 275  
 WODA O'Dea Temple of Music.....Paterson, N. J. 391  
 WOI Iowa State College.....Ames, Iowa 270  
 WOK Neutrowound Radio Mfg. Co.....Homewood, Ill. 217  
 WOKO Harold E. Smith.....Peekskill, N. Y. 232  
 WOO John Wanamaker.....Philadelphia, Pa. 508  
 WOOD Grand Rapids Radio Co.....Grand Rapids, Mich. 242  
 WOQ Unity School.....Kansas City, Mo. 278  
 WOR L. Bamberger and Co.....Newark, N. J. 405  
 WORD People's Pulpit Assn.....Batavia, Ill. 275  
 WOS State Market Bureau.....Jefferson City, Mo. 441  
 WOWO Main Auto Supply Co.....Fort Wayne, Ind. 227  
 WPAK N. D. Ag. College.....Agricultural College, N. D. 275  
 WPAP (See WQAO).....Cliffside, N. J. 361  
 WPCC North Shore Cong. Church.....Chicago, Ill. 258  
 WPCB Concourse Radio Corp.....New York, N. Y. 273  
 WPDQ H. L. Turner.....Buffalo, N. Y. 205  
 WPG The Municipality of Atlantic City.....Atlantic City, N. J. 300  
 WPRC Wilson Printing & Radio Co.....Harrisburg, Pa. 216  
 WPSC Pennsylvania State College.....State College, Pa. 261  
 WQAA Horace A. Beale, Jr.....Parkersburg, Pa. 220  
 WQAC Gish Radio Service.....Amarillo, Tex. 234  
 WQAE Moore Radio News Station.....Springfield, Vt. 246  
 WQAM Electrical Equipment Co.....Miami, Fla. 285  
 WQAN Scranton Times.....Scranton, Pa. 250  
 WQAO Calvary Baptist Church.....Cliffside, N. J. 361  
 WQJ Calumet Rainbo Broadcasting Co.....Chicago, Ill. 447  
 WRAF The Radio Club (Inc.).....LaPorte, Ind. 224  
 WRAH S. N. Read.....Providence, R. I. 235  
 WRAC Economy Light Co.....Escanaba, Mich. 256  
 WRAM Lombard College.....Galesburg, Ill. 244  
 WRAW Antioch College.....Yellow Springs, Ohio 263  
 WRAW Avenue Radio & Electric Shop.....Reading, Pa. 238  
 WRAX Beracah Church, Inc.....Philadelphia, Pa. 268  
 WRBC Immanuel Lutheran Church.....Valparaiso, Ind. 278  
 WRC Radio Corp. of America.....Washington, D. C. 468  
 WRCO Wayne Radio Co.....Raleigh, N. C. 252  
 WREC Wooten's Radio Shop.....Coldwater, Miss. 254

## RADIO AGE SUBSCRIPTION BLANK

Radio Age, Inc.  
 500 North Dearborn Street  
 Chicago

**\$2.50 A YEAR**

Gentlemen: Please enter my subscription for RADIO AGE, the Magazine of the Hour, for one year, beginning with the ..... issue, for which I enclose \$2.50.

Name.....  
 Street Address.....  
 City.....  
 State.....

Send cash, money order or draft

(12-26)

**Only a Few 1926  
 Annuals Left  
 Get Yours for a  
 Dollar Bill**

### What Do We Get From Boston?

(Continued from page 19)

to turned out to be the veriest rot, and it was with only a mild curiosity as to what you were up to now that I started the article. I had never come in contact with radio, and thought of it as something that appealed to small boys and people in isolated places. As real entertainment for people living in a city, I had never considered it, and I was literally amazed to learn what it had developed into.

"We had a set installed that week, and Sam said a few nights afterward, 'If you want to know where I am spending my evenings this winter it's right on that davenport. I can get all the entertainment I need right here at home.'

"He even cancelled his football tickets, for he said he had put in fifteen years freezing up at Ferry Field each fall, and he could get just as much of a thrill out of the games from the loud speaker. I accused him of senility, but agree with his statement that it requires too much effort to get anywhere nowadays. We'll probably tire of the radio in time, but it seems to be such an overwhelming proposition, and as Sam says we've gotten started so late it will take us a long time to get around the country. We've just discovered the bridge lessons . . . I wonder if there aren't a lot of people like ourselves who are overlooking radio simply because they don't know what it means. We have done some proselyting ourselves, and it has solved the Christmas problem in several cases. If you discover any more new continents let us know."

### FIVE TUBE RADIO



**\$25.00**  
**AGENTS WANTED**  
**BIG COMMISSION**

Demonstrating agent wanted; every county. Exclusive to right man. Sell what public wants—five tube, long distance, loud speaker radio with single dial control. Price within reach of all, \$25.00 retail; liberal discount to agents. Sell in spare time—evenings. No selling or radio experience necessary. Territory going fast. 100 page Radio Book FREE. Write today—don't delay. C. S. FISCHER, 122 W. Austin Ave., Chicago

# Send for Latest RADIO CATALOG and GUIDE

## Valuable Information FREE

The new 164-page 1927 edition of the *Barawik Builder's Guide* is now ready. This is the book that hundreds of thousands of radio enthusiasts turn to when they want the latest and best in radio at big discounts. It's a handy and most reliable radio reference guide. Keep up to date by utilizing Barawik service. It will help you to solve many a radio problem as well as saving you tremendous sums on the very things you need and use most. You want the latest—We have it—at bargain prices, too.

The new *Guide* is brimful of the best approved standard radio sets, parts and kits, at savings that will appeal to the thrifty. Profusely illustrated with reliable guaranteed goods at tremendous savings. Be sure to get your copy before you spend another cent for sets, parts and radio supplies.

## Complete Parts for all the Newest Circuits

In every issue of RADIO AGE and other radio magazines you will find the newest circuits of the world's greatest radio engineers. You will want to build these sets from the parts specified. BARAWIK service keeps up to date on all the new wrinkles. The new BARAWIK Guide is brimful of valuable information. We have the specified parts for all the new circuits, complete, ready to ship you the instant your order arrives. Take advantage of this unequalled service. Get what you want—quick—at a big saving. No order too large or too small for us. 300,000 fans thrive by using BARAWIK service. We can please you, too. Get your free copy of the complete 164-page Guide for 1927 NOW. Delay means loss to you.

## Special Amateur Section—Short Wave Equipment

Another new Barawik idea is the *Amateur Section* under the direction of F. J. Marco, 92A, wherein is presented for the first time a complete line of short wave receivers, transmitters and all the necessary amateur equipment so dear to the amateur experimenter—all at bargain prices. Don't miss the opportunity to look into this inviting field.

### Get Your Free Copy Today—NOW

To everyone mailing the coupon or writing us a letter or postcard we will mail free the new 1927 Barawik Radio Guide, with its 164 pages of everything interesting for the Radio fan. Never in the history of radio has such a tremendous collection of radio supplies been presented to the public. Build the set of your dreams now. Get the things you have always longed for. You can do it, for our low prices will make the most expensive articles reasonable in price.

*Mail Coupon Now.* Get this Guide into your hands before you buy another part. It will mean money in your pocket. Write today; also please send names of other radio fans.



# BARAWIK CO.

540-544-A MONROE ST., CHICAGO, U. S. A.

NAME.....  
 ADDRESS.....  
 FRIEND.....

## RADIO AGE SUBSCRIPTION BLANK

Radio Age, Inc.,  
 500 North Dearborn Street,  
 Chicago

**\$2.50 A YEAR**

Gentlemen: Please enter my subscription for RADIO AGE, the Magazine of the Hour, for one year, beginning with your next issue, for which I enclose \$2.50.

Name.....

Street Address.....

City.....

State.....

Send cash, money order or draft.

(12-26)

WREO Reo Motor Car Co. Lansing, Mich. 285  
 WRES H. L. Sawyer. Woloaston, Mass. 300  
 WRHF Wash. Radio Hospital Fund. Washington, D.C. 256  
 WRHM Rosedale Hospital, Inc. Minneapolis, Minn. 252  
 WRK Doron Bros. Hamilton, Ohio 270  
 WRM University of Illinois. Urbana, Ill. 273  
 WRMU A. H. Grebe & Co., Inc. Motor Yacht "MU-1" 236  
 WRNY Experimenter Publishing Co. New York, N. Y. 374  
 WRR City of Dallas. Dallas, Tex. 246  
 WRST Radiotel Mfg. Co., Inc. Bay Shore, N. Y. 216  
 WRVA Larus & Brother Co., Inc. Richmond, Va. 256  
 WSAI United States Playing Card Co. Cincinnati, Ohio 326  
 WSAJ Grove City College. Grove City, Pa. 229  
 WSAN Allentown Call Publishing Co. Inc. Allentown, Pa. 229  
 WSAR Daughty & Welch Electrical Co. Fall River, Mass. 254  
 WSAV Clifford W. Vick. Houston, Tex. 248  
 WSAX Zenith Radio Corp. (Portable). Chicago, Ill. 268  
 WSAZ Chase Electric Shop. Pomeroy, Ohio 244  
 WSB Atlanta Journal. Atlanta, Ga. 428  
 WSBC World Battery Co. Chicago, Ill. 288  
 WSBF Stix Baer & Fuller. St. Louis, Mo. 273  
 WSBT South Bend Tribune. South Bend, Ind. 315  
 WSDA Seventh Day Adventist Church. New York, N. Y. 263  
 WSKC World's Star Knitting Co. Bay City, Mich. 261  
 WSM Nashville Life & Accident Ins. Co. Nashville, Tenn. 283

WSMB Saenger Amuse. Co. & Maison B. Co. New Orleans, La. 319  
 WSMH Shattuck Music House. Owosso, Mich. 240  
 WSMK S. M. K. Radio Corp. Dayton, Ohio 275  
 WSOE School of Engineering. Milwaukee, Wis. 246  
 WSRO Harry W. Fahrlander. Hamilton, Ohio 252  
 WSSH Tremont Temple Bap. Church. Boston, Mass. 261  
 WSUI State University of Iowa. Iowa City, Iowa 484  
 WSVS Seneca Vocational School. Buffalo, N. Y. 219  
 WSWS Richmond Harris & Co. Batavia, Ill. 275  
 WTAB Fall River Daily Herald Publishing Co. Fall River, Mass. 266  
 WTAD Robt. E. Compton. Carthage, Ill. 236  
 WTAG Worcester Telegram. Worcester, Mass. 545  
 WTAL Toledo Radio & Electric Co. Toledo, Ohio 252  
 WTAM Willard Storage Battery Co. Cleveland, Ohio 389  
 WTAQ C. S. Van Gordon. Eau Claire, Wis. 254  
 WTAR Reliance Electric Co. Norfolk, Va. 261  
 WTAW Agricultural & Mech. Col. of Texas. College Sta. Texas 270  
 WTAX Williams Hardware Co. Streator, Ill. 231  
 WTAZ Thomas J. McGuire. Lambertville, N. J. 261  
 WTIC Travelers Insurance Co. Hartford, Conn. 476  
 WTRC 20th Dist. Republican Club. New York, N. Y. 240  
 WWAE Electric Park. Plainfield, Ill. 384  
 WWJ Evening News Assn. (Detroit News) Detroit, Mich. 353  
 WWL Loyola University. New Orleans La. 275  
 WWRL Woodside Radio Labs. Woodside, N. Y. 258

**Dominion of Canada**

CFAC Calgary Herald. Calgary, Alta. 434  
 CFCA Toronto Star Pub. & Prtg. Co. Toronto, Ont. 356  
 CFCF Marconi Wireless Teleg. Co., (Ltd.) Can. Montreal, Que. 411  
 CFCH Abitibi Power & Paper Co. (Ltd.) Iroquois Falls, Ont. 500  
 CFCK Radio Supply Co. Edmonton, Alta. 517  
 CFCN W. W. Grant (Ltd.) Calgary, Alta. 434  
 CFCR Laurentide Air Service. Sudbury, Ont. 410  
 CFCT Victoria City Temple. Victoria, B. C. 329  
 CFCU The Jack Elliott (Ltd.) Hamilton, Ont. 341  
 CFHC Henry Birks & Sons. Calgary, Alta. 434  
 CFKC Thorold Radio Supply. Thorold, Ont. 248  
 CFQC The Electric Shop (Ltd.) Saskatoon, Sask. 329  
 CFRQ Queens University. Kingston, Ont. 450  
 CFXC Westminster Trust Co. Westminister, B. C. 291  
 CFYC Commercial Radio (Ltd.) Vancouver, B. C. 411  
 CHBC The Calgary Albertan. Calgary, Alta. 434  
 CHCM Riley & McCormack (Ltd.) Calgary, Alta. 434  
 CHCS The Hamilton Spectator. Hamilton, Ont. 341  
 CHIC Northern Electric Co. Toronto, Ont. 357  
 CHNC Toronto Radio Research Society. Toronto, Ont. 357  
 CHUC International Bible Ass'n. Saskatoon, Sask. 329  
 CHXC R. Booth, Jr. Ottawa, Ont. 434  
 CHYC Northern Electric Co. Montreal, Que. 411  
 CJCA Edmonton Journal. Edmonton, Alta. 511

CJGL A. Couture. Montreal, Que. 279  
 CJGC London Free Press. London, Ont. 329  
 CKAC La Presse. Montreal, Que. 411  
 CKCD Vancouver Daily Province. Vancouver, B. C. 397  
 CKCK Leader Pub. Co. Regina, Sask. 476  
 CKLC Dominion Battery Co. Toronto 357  
 CKCO Ottawa Radio Association. Ottawa, Ont. 434  
 KCKX P. Burns & Co. (Ltd.) Calgary, Alta. 434  
 CKFC First Congregational Church. Vancouver, B. C. 411  
 CKLC Wilkinson Electric Co. (Ltd.) Calgary, Alta. 434  
 CKNC Canadian National Carbon Co. Toronto, Ont. 357  
 CKOC Wentworth Radio Supply Co. Hamilton, Ont. 341  
 CKY Manitoba Tel. System. Winnipeg, Man. 384  
 CNRA Canadian National Railways. Moncton, N. B. 312  
 CNRC Canadian National Railways. Calgary, Alta. 436  
 CNRE Canadian National Railways. Edmonton, Alta. 517  
 CNRM Canadian National Railways. Montreal, Que. 411  
 CNRO Canadian National Railways. Ottawa, Ont. 435  
 CNRR Canadian National Railways. Regina, Sask. 476  
 CNRS Canadian National Railways. Saskatoon, Sask. 329  
 CNRT Canadian National Railways. Toronto, Ont. 357  
 CNRV Canadian National Railways. Vancouver, B. C. 291  
 CNRW Canadian National Railways. Winnipeg, Man. 384

**Republic of Mexico**

CYB Mexico City. 380 | CYL Mexico City. 400 | CZE Mexico City. 350

**Republic of Cuba**

PWX Cuban Telephone Co. Havana 400 | 5DW R. S. Calderon. Matanzas 200 | 6KW F. H. Jones. Tuinucu 272  
 2BY F. W. Borton. Havana 260 | 6VY Jose Ganduxe. Cienfuegos 260 | 7SR S. Rionda. Central Elia 350  
 20K M. G. Velez. Havana 360 | 6JK F. H. Jones. Tuinucu 340 | 8BY A. Ravelo. Santiago de Cuba 250  
 20L Oscar Collado. Havana 257

**Great Britain**

2LO London. 365 | 5XX Daventry. 1600 | 2ZY Manchester. 378  
 5IT Birmingham. 479 | 2RN Dublin. 390 | 5NO Newcastle. 404  
 5WA Cardiff. 353 | 6BM Bournemouth. 386 | 5SC Glasgow. 422  
 2BE Belfast. 440

**France**

YN Lyons. 550 | FL Paris (Eiffel Tower). 2,650 | 8AJ Paris. 1,780 | ESP Paris. 458

**Short Wave Phone Broadcasting**

2XK Schenectady, N. Y.*	KC 4600	Meters 65.16	KDKA Pittsburgh, Pa.*	KC 5100	Meters 58.79
KDKA Pittsburgh, Pa.*	4760	63.00	2XAF Schenectady, N. Y.*	9143	32.79

\*Crystal Control

# CLASSIFIED ADVERTISEMENTS

If you have anything to buy or sell, don't overlook RADIO AGE'S classified advertisements.

The classified advertising rates are but five cents per word for a single insertion. Liberal discounts are allowed on three, six and twelve-time insertions, making rate of 4 1-2, 4 and 3 cents a word per insertion respectively. Unless placed through an accredited advertising agency, cash should accompany all orders. Name and address must be included at foregoing rates. Minimum contract charge \$1.00.

All classified ads for the January issue must be sent in by November 25.

## AGENTS WANTED

WANTED, AN ACTIVE MAN TO TAKE ORDERS for Hardy fruit trees, berry bushes, evergreens, flowering shrubs and roses. Liberal commission. Free replacement. Sales instruction and outfit free. Sherman Nursery Company, attention Mr. Smith, Charles City, Iowa.

Gold Wave Aerial. Greatest Side Line out. Guaranteed to bring in more stations—gives greater distance and selectivity. Reduces static to a minimum. Sells all dealers handling radio. Unlimited field. Big commissions and re-orders. Luxem and Davis Mfg. Co., 6231 Broadway, Dept. 61, Chicago.

MAN in each town to plate auto parts, reflectors, bath fixtures, silver mirrors, refinish beds, chandeliers by new method; \$10 daily; no capital or experience required; outfits furnished; write today. Gunmetal Company, Avenue J, Decatur, Illinois.

SELLS for \$9.75. Prints ad on wrapping paper, envelopes, etc. \$1.00 commission. Send 10c for sample work. Automatic Ad-Stamp, Joplin, Mo.

## BOOKS AND MAGAZINES

What could be better than magazine subscriptions for holiday gifts. Send stamp for our special list of subscription bargains. Midland Products, Dept. R. A., 524 Courtland Ave., Park Ridge, Illinois.

Twentieth Century Book of Receipts, Formulas and processes, an 807 cloth bound book containing 10,000 proven formulas for the manufacturer, workshop, laboratory, office and home. Sent prepaid upon receipt of \$4.00. Send stamp for our 48 page catalog of latest and best practical, scientific mechanical and industrial books. Midland Products Co., Dept. RA, 524 Courtland Ave., Park Ridge, Ill.

## BUSINESS OPPORTUNITIES

LAND FREE if planted to bananas. Bananas bear a full crop the second year. \$5.00 monthly will plant five acres, which should pay \$1,500 profit annually. Reliable Companies will cultivate and market your bananas for 1/3. Bananas ripen every day and you get your check every 90 days. For particulars address National Development Company, Empire Building, Block 135, Pittsburg, Pennsylvania.

## CODE

DO YOU WANT TO MEMORIZE THE WIRELESS TELEGRAPH CODE? THE CORYDON SNYDER CODE METHOD IS EASIEST, QUICKEST. PATENTED. Send 10c coin for complete method to Corydon Snyder, 1243 Rosemont Avenue, Chicago, Illinois.

## COLLECTIONS

Three Collection Letters That Actually Collect: Product, 23 years' experience, \$1.75. Address J. A. Hillman, Lynchburg, Virginia.

## DOGS

BEAUTIFUL REGISTERED BULL PUPS \$15. Bulldogs, 501 Rockwood, Dallas, Texas.

For Sale—Arkansas Hounds, trained and untrained, 30 years dog business, long trial, guaranteed, terms, list free. W. B. Caraway, Alma, Arkansas.

## MISCELLANEOUS

FOR SALE: WATCHMAKER'S LATHE at a bargain. R. Jaegermann, 5815 Eaton Ave., St. Louis, Missouri.

## PERSONAL

LONELY HEARTS: Exchange letters; make interesting new friends in our jolly club. Particulars free. Eva Moore, Box 908, Jacksonville, Florida.

## RADIO

Build the Quadraformer Super V. A real five tube set. Set of Genuine Quadraformers \$12.75 including instructions. Booklet 25c. Literature on request. R. P. Tomamichel, 2244 Seminary Avenue, Chicago, Illinois.

TROUBLE-SHOOTING. Do you know the key to the knowledge of any electrical circuit? You can find correct answer in a booklet written by nationally known authorities on Radio and Electricity. Ask your radio dealer for, "Practical Guide for Every Radio Builder and Owner" or send 10c to-day to Universal Test Equipment Co., 2939 N. Oakley Ave., Chicago, Ill. Sold at all news stands in the city of Chicago.

Buyers Service for Readers of Radio Age. I will buy for you standard radio merchandise if you cannot obtain same in your locality. Remit list price of articles wanted, and if same are not obtainable by me I will make refund. R. P. Tomamichel, 2244 Seminary Ave., Chicago, Illinois.

EXPERIMENTERS. Complete Chemical Apparatus and Radio Catalog. 1000 Illustrations. Price 25c; refunded on \$5.00 order. Laboratory Materials Company, 646 East 71st Street, Chicago.

End all your troubles and join the Questionnaire Club, something every radio fan should belong to, send stamp for full particulars, Web Radio Co., Box 849, Chicago, Ill., Dept. QC.

Guaranteed tubes, 199 and 201A types \$1.00 each. \$7.50 units to make a loud speaker of your Phonograph only \$2.49. \$4.00 list head phones going at \$1.69. This is real value, a standard make 3 tube set with long range and lots of volume for \$8.95. (less accessories), while they last. \$12.00 loud speakers with genuine Bakelite Bell at \$6.95. Write for our price before you buy your radio parts. Outlet Sales, 112 Calvert Ave., Detroit, Michigan.

Do you want to build a real radio set at low cost? The circuit of the Web Wonder Four is just out, send stamp for full particulars, Web Radio Co., Box 849, Chicago, Ill. Dept. B. P.

Chokes for Speaker or Filter service, 20H—25MA \$1.00—30H 50MA—\$1.75, 50H 60MA \$2.00 prepaid. Write for list of Audio Transformers impedance amplifiers, Raytheon transformers, etc. Radio Parts Sales Co., Box 24, Orange, N. J.

RADIO TROUBLES OVER. Hoff's trouble finder locates, explains Remedy, 103 radio ailments. Particulars free. Smith, 516 Main, St. John, N. B.

IVORY RADIO PANEL beats them all. Write for FREE Sample. Ivorylite Radio Panel Co., 3222 Ave. F, Fort Worth, Texas.

A new circuit just out, something different. Send 2 cent stamp for information how to build your own set. Web Radio Company, Box 849, Chicago, Ill.

Want to dispose of my Kennedy Universal Receiver type 110 and two stage Amplifier type 525. Excellent condition guaranteed. No reasonable offer refused. K. F. Oerlein, 2943 Cambridge St., Philadelphia, Pa.

ATTENTION SET BUILDERS. Increase efficiency and selectivity by installing a set of binocular type radio frequency coils. Set Builders take extensively. Set of three \$6.45. Money-saving price list mailed upon request. All articles sold on money back guarantee. Midwest Radio Supply, Dept. C., Box 222, Racine, Wisconsin.

Radio books—Construction of a modern Super Heterodyne Type Receiver including Testing and Operation \$1.00; Henley's 222 Radio Circuit Designs. 267 pages, \$1.00; The ABC of Vacuum Tubes used in Radio Reception 132 pages, 75 cents; Henley's Workable Radio Receivers 196 pages \$1.00; Experimental Wireless Stations 392 pages \$2.00; Wireless Telegraphy and Telephony Simply Explained 154 pages \$1.00. Sent prepaid on receipt of price. Send stamp for our 48 page catalog of latest and best practical, scientific, mechanical and industrial books. Midland Products Co., Dept. RA, 524 Courtland Ave., Park Ridge, Illinois.

SILICON Transformer Steel cut to order .014". 10 lbs. 25 cents, 5 lbs. 30 cents, less than 5 lbs. 35 cents per lb., 4 cubic inches to the lb. .007" for radio frequency transformers, 50c cubic inch, postage extra. At least 1/2 cash with order—balance C. O. D. Geo. Schulz, Calumet, Michigan.

Bakelite subpanels with five built in X type sockets, connections marked size 7x23, five dollars by mail order. Subpanel brackets, seven inches long, two and half inches high, one dollar a set. Satisfaction guaranteed or money refunded. Arrow Radio Products, 350 Fifth Avenue, Venice, Calif.

99.7% Pure aluminum for Rectifiers, B Eliminators, Trickle chargers and transmitters 1-2" round, 1-4x1" rectangular 5c inch, 1-4"x3-4c inch 2, 3-8" round lead elements 3 1-2" long 15c, 7 for \$1.00 all with brass terminals, prepaid to 5 zone. No order less than \$1.00. Geo. Schulz, Calumet, Michigan.

## CRYSTALS—NOT GALENA

CELERUNDUM—the most sensitive crystal rectifier in the world. It is non-metallic sensitive all over; low resistance; greater volume. Will not burn out. Twelve crystals for \$1.00 post paid.

De-Tex-It—A truly great fixed detector—Positive contact—Thousands in use. The best rectifier for Crystal Sets, Reflex T R Frequency and Super Hets 3 for \$2.00 postpaid.

WE HAVE A BOOK THAT TALKS and sings, plays the piano and tells stories. Inside attractive covers is a compact, practical and complete radio outfit. No operating expense; no batteries or tubes to replace. Everything is included—(crystal set aerial and ground leads indoor antenna and pair of phones). The Talking Book, \$5.00 complete connect it in a second and it goes for a life time. No overhead. E. W. Pitt Company, 115 Federal St., Boston, Mass.

PURE ALUMINUM and lead rectifier elements, holes drilled, with brass screws and nuts per pair 1/16", 1"x4", 13c, 1x6, 15c, 1 1/4x6, 17c, 1 1/2x6, 19c, single elements half price. Sheet aluminum 1/16", \$1.00 1/8" \$1.50. Lead \$1.00 square foot all prepaid. Geo. Schulz, Calumet, Michigan.

CONDENSERS. 800 VOLT FILTER .1 mfd 45c, .25 51c, .5 60c, 1. 75c, 2. \$1.20, 3. \$1.80, 4. \$2.40. 1500 VOLT FILTER, .1 51c, .25 60c, .5 75c, 1. \$1.05, 2. \$1.55, 3. \$2.70, 4. \$3.60. ELIMINATOR BLOCKS, 2, 2, and 8 \$5.70, 2, 2, 8, and 1 \$6.15, 2, 2, 8, 1 and 1 \$6.60, 1 and 1 in series 90c. Many other capacities. Acme transformers and chokes. THE RADIO CLUB, INC., La Porte, Ind.

3 element Rectifier jars for B eliminators, B battery chargers and transmitters, 1 jar takes the place of 2 ordinary jars, 1/4" x3/4" 99.7% pure aluminum, rubber covers, binding posts 3/16" inside diameter \$1.00 each, 4 for \$3.00, prepaid to 5th zone, 1/2 cash with order, balance C. O. D. Satisfaction or money back, Georgia Schulz, Calumet, Mich.

Audio transformers 70c up. \$2.00 brings a 50 H 60 MA choke for use with your "B" eliminator or as a Bypass for your speaker. Write for list of transformers and parts. Radio Parts Sales Co., Box 24, Orange, N. J.

Save up to 50% on Nationally Advertised Radio parts. Send for our new price list of Radio Kits, "B" eliminators, Radio Receivers and Parts. NATIONAL RADIO-PRINT CO., Room 404, 200 Broadway, New York.

Radio Panel Lamp. Rests on top cabinet. Lights dial. Uses battery current. Complete with bulb \$1.25, postpaid. Satisfactory or money back. Robert Stevenson, Lancaster, Ohio.

SAVE MONEY on radio sets and parts. List free. All merchandise guaranteed. GEMRAD COMPANY, 631 E. Okmulgee, Muskogee, Okla.

## SALESMEN WANTED

Make \$100 WEEKLY in spare time. Sell what the public wants—long distance radio receiving sets. Two sales weekly pays \$100 profit. No big investment, no canvassing. Sharpe of Colorado made \$955 in one month. Representatives wanted at once. This plan is sweeping the country—write today before your county is gone. OZARKA, INC., 431 N. LaSalle Ave., T, Chicago.

Radio Age Classified Ads Bring Results

Please mention Radio Age when writing to advertisers

# An Index to the Best in Radio Hookups!

**H**OW long have you postponed making that favorite hookup of yours because you couldn't find reliable and clear diagrams? We have laid aside a limited number of back issues of RADIO AGE for your use. Below are listed hookups and diagrams to be found in them. Select the ones you want and enclose 30 cents in stamps for each one desired.

## September, 1924

- How Careful Mounting Will Improve Reception.
- One Tuning Control for Hair's Breadth Selectivity.
- Four Pages of Real Blueprints of a New Baby Heterodyne.

## November, 1924

- Blueprints of a Single Tube Loop Set and a Capacity Feed-back Receiver.
- A 3-Tube Low Loss Regenerator.
- Mastering the 3-Circuit Tuner.

## January, 1925

- A Six-Tube Super-Het.
- An Efficient Portable Set.
- A Tuned Plate Regenerator.
- Making a Station-Finder.

## February, 1925

- A Three Circuit Regenerator.
- A Real Low Loss Set.
- Blueprints of a 3-tube Reflex.

## March, 1925

- A 5-Tube R. F. Receiver.
- How to Wind Low Loss Coils.
- A Short Wave Receiver.
- Blueprints of a Two-Tube Ultra Audion and a Regenerative Reflex.

## April, 1925

- A 3-Tube Portable Set.
- "B" Voltage from the A. C. Socket.
- An Amplifier for the 3-Circuit Tuner.
- Blueprints of a Five-Tube Radio Frequency Receiver.

## May, 1925

- A "Quiet" Regenerator.
- How to Make a Tube-Tester.
- A Unique Super-Het and an Improved Reintartz.
- A Six-Tube Portable Receiver Illustrated with Blueprints.

## June, 1925

- Reducing Static Disturbances.
- A Seven-Tube Super-Heterodyne.
- Browning-Drake Receiver.
- Overcoming Oscillations in the Roberts Receiver.

## July, 1925

- Learning Tube Characteristics.
- How Much Coupling?
- Blueprints of Conventional Radio.
- Symbols and Crystal Detector Circuit.

## August, 1925—50c per copy

- How to Attain Smooth Tuning.
- Alternating Current Tubes.
- Deciding on a Portable Super.
- And a big 60-page blueprint section.

## September, 1925

- Thirty-one ways to prevent self-oscillation.
- Tuning efficiency with two controls.
- Ideal Audio Amplifier Circuits.
- Blueprint section.

## October, 1925

- Auto-Transformer Coupling.
- Some Facts about Quality.
- An Improved Slide-Wire Bridge.
- Blueprints of Circuits Using Single and Dual Controls.

## November, 1925

- A Good Audio Oscillator.
- An Efficient Short-Wave Transmitter.
- Blueprints—Adding R. F. Stages.

## December, 1925

- Tuned R. F. and Regeneration.
- Radio Age Model Receiver.
- Inductive Gang-Control Receiver.
- Tuning with Chart Curves.

## January, 1926

- Radio Age January Model Set.
- A Four-Tube Toroid Set.
- Power Supply Device—Blueprint Feature.
- Finishing Your Radio Cabinet.

## February, 1926

- February Radio Age Model Set.
- Plug-in Coil Receiver.
- Universal Testboard—Blueprint.
- Eliminating Audio Distortion.

## March, 1926

- Improving the Browning-Drake.
- Rheostatless Tubes in a Set.
- Which Type Intermediate?
- How to Make a Wavemeter—Blueprint.

## April, 1926

- Shielding Your Receiver.
- Home Testing Your Tubes.
- Balanced Capacity Receiver.
- Several Sets on One Antenna.

## May, 1926

- Short Wave Transmitter—Blueprint.
- Simplifying Battery Charging.
- List of European Broadcasters.
- Protecting your Inventions.

## June, 1926

- Antenna Design.
- Simple Crystal Set.
- Improving the Neutrodyne.
- Golden Rule Receiver—Blueprints.

## July, 1926

- Compact Portable Super.
- Short Wave Receiver.
- Shielded Golden Rule Set.

## August, 1926

- Receiver, Transmitter and Wavemeter.
- Beginners 200 mile Crystal Set.
- History of Amateurs.
- Changing to Single Control.

## September, 1926

- How to Make a Grid Meter Driver
- Short Wave Wavemeter
- Power Amplifier for Quality (Blueprint)

## October, 1926

- Crystal Control Low Power Transmitter (Blueprint)
- Raytheon Design for A B C Elimination
- What Type Loud Speaker to Use
- Nine Tube Super Brings Back Faith


## November, 1926

- Blueprints of the Henry-Lyford.
- World's Record Super With Large Tubes.
- How to Use a Power Tube in Your Set.
- Illuminated Controls on 4 Tube Receiver.

Radio Age, Inc., 500-510 N. Dearborn St., Chicago

# SM

## 'Ever heard a real receiver?

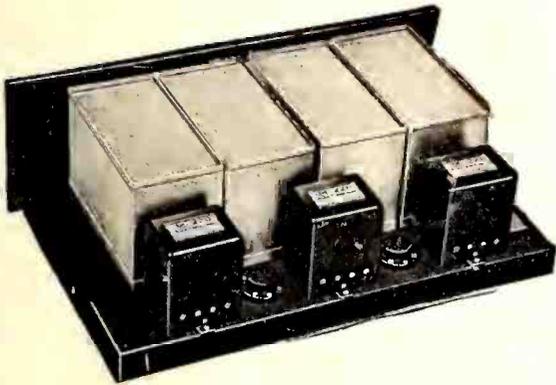

## 630 Silver Shielded Six

**H**AVE you ever heard a real receiver? That's a simple question, but not one person in one hundred can say "yes."

Have you ever heard a radio set that made you lie back, light up your favorite pipe, and say "This is the life"? When you've listened to a symphony over the radio, haven't you always felt that it would be just a bit clearer if you were in the concert hall?

Have you ever wanted just a little more volume on that distant station—just a bit more selectivity to cut out the interfering locals? And haven't you wished but two dials would tune the whole contraption instead of lots and lots of little knobs?

Have you ever heard a Silver-Marshall Shielded Six "doing its stuff"? It is guaranteed to give you better reproduction than you've ever heard. With the Six, you actually feel the vibration when you hear a cello or an organ—the timbre of a violin is true—a piano sounds as it should. And on a full orchestra—well, just ask the man who has built one about tone quality—he'll probably overwhelm you with enthusiasm.

For selectivity, for bringing in distance, the Shielded Six is right there beside the best. You can put it together on the living-room table with three tools in three hours, and the same evening bring in stations local and distant with uncanny ease—with only two dials.

You can buy every part needed for the Shielded Six solidly packed in a wooden kit-box—everything necessary except cabinet and accessories. Just ask for the 630 kit—it costs \$95.00—and it will build a set you can't duplicate for \$200 factory built. Or if you have some parts, you can get the Essential Kit, No. 633, for \$45.00.

And remember—when you build a Shielded Six you're getting a set with years of research work behind its design with every part laboratory tested. You're getting a guarantee that its tone quality is beyond compare. Radio Broadcast, Radio Age, Radio News, The Citizen's Radio Call Book, all and more, have verified these claims—have endorsed the Shielded Six unqualifiedly.

*Prices 10% higher west of the Rockies.*

*Do you know that the unofficial report of the largest telephone manufacturing company in the world set Silver-Marshall 220 Audio Transformers up as the very finest they have ever tested? Do you know that you can obtain these same transformers from your dealer at \$6.00 each—guaranteed?*

## SILVER-MARSHALL, INC.

850 W. JACKSON BLVD.

CHICAGO, U. S. A.

# The Masterpiece of Masterpieces!



Model 6-F-II

\$119.50

Slightly Higher  
Denver and West

**T**HIS "Masterpiece of Masterpieces" startles and surpasses all expectations.

It is the most perfect radio that has ever been designed. It is massive—it is beautiful. It is just what you want for your home. For no matter how exquisite your furnishings are, this artistic genuine mahogany upright console will lend additional beauty. And yet it is priced so moderately that almost every family can easily afford to own one.

#### Genuine R C A Radiotrons

are recommended for use with Freshman Masterpiece Receivers. A special package containing—1 UX-112 power tube, 1 UX-200A detector tube and 3 UX-201A amplifying tubes—matched and tested for the set in which they are shipped is sold by Authorized Freshman Dealers.

*Sold on Convenient Terms  
by Authorized Freshman Dealers*

**CHAS. FRESHMAN CO., Inc.** Freshman Building, New York  
2626 W. Washington Blvd., Chicago, Ill.

## New and Improved **FRESHMAN MASTERPIECE**

—the thing that makes it wonderful is its tone quality. The large cone speaker has been designed to exactly match Freshman's new QUALITY radio receiver. This special cone speaker easily handles the full power that this new set delivers.

Yet, in spite of its ability to handle great volume, when the power is reduced the softest and mellowest tones come forth in a manner never before achieved.

### *Simplicity*

Its ease of operation, with its three distinct controls, allows any novice to tune in the station wanted day after day at the same points on the dials. This efficient means of operation eliminates the overlapping of wave lengths, which assures distinct separation of one broadcasting station from the others.

Write for our new 48 page book illustrating and describing the entire line of Freshman Masterpiece Receivers and other apparatus.

# The Most Perfectly Toned Radio Ever Produced