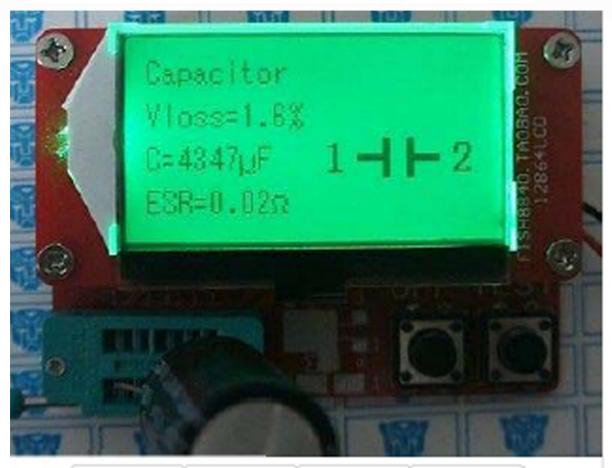
Small 12864 LCD Transistor Tester Capacitance ESR Meter Diode Triode MOS LCR NPN





2014 latest M328 version of the software ,more functions. Chip: Atmega328 128*64 big Backlight LCD display, only 2mA when stand by.

Using 9V battery (Not inlouded)

NEW Function:

- 1: Automatic detection of NPN and PNP transistors, n-channel and p-channel MOSFET, diode (including double diode), thyristor, transistor, resistor and capacitor components
- 2: Automatic test the pin of a component, and display on the LCD
- 3: Can detect the transistor, MOSFET protection diode amplification coefficient and the base to determine the emitter transistor forward biased voltage
- 4: Measure the gate and gate capacitance of the MOSFET threshold voltage
- 5:Use 12864 liquid crystal display with green backlight

Specifications:

1. One -button operation, automatic shutdown.

MINI-MANUAL

Only 20nA shutdown current.



After Power On the module first displays a splashscreen with sopyright notice though the design and technical development was performed in Germany and later copied by chinese guys

the original developer was: kh_kuebbeler@web.de

http://www.mikrocontroller.net/topic/248078?page=6



After splashscreen the module displays current batteryvoltage



After display of the battery-voltage the module will start performing test

- IF testobject is detected - otherwise errormessage will be displayed.

Transistor Testing

Line 1 at display shows what kind of transistor has been detected.


Automatically detect NPN, PNP bipolar transistors, N-channel and P-channel MOS FET, JFET, diodes, two diodes, thyristors small power unidirectional thyristor.





Automatic identification components pin arrangement .

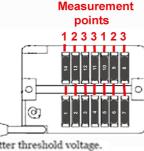Measuring bipolar transistor current amplification factor and base - emitter threshold voltage.



Attention!
There are various kinds of PCB's out there with different measure-points! In general the points are indicated by numbering on the PCB!






recognize that line 2 displays allocation of the transistorpins related to the testinpoints E=Emitter B=Base C=Collector G=Gate D=Drain S=Source

P-E-MOS 123=GDS C = 2.74nF 1 Vt = 2.0V





examples on testing SMDtransistors

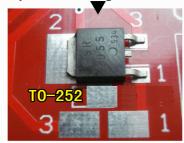


Via the base - emitter threshold voltage and high current amplification factor to identify Darlington transistors. Can detect bipolar transistors and MOS transistors protection diodes.

Measuring the gate MOS FET threshold voltage and the gate capacitance.

Thyristor and Triac Measurement



Triac & Thyristor

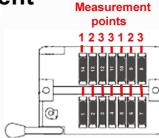



Measurement of Diodes and LED's

Can be in the correct order and the diode symbol display two diodes, and gives the diode forward voltage.

LED is detected as a diode forward voltage higher. Combo of the LED is identified as two diodes.

Eeverse breakdown voltage is less than 4.5V Zener diode can be identified.

Can measure a single diode reverse capacitance. If the bipolar transistor connected to the base and collector or emitter of a pin , it can measure the collect:

junction reverse capacitance .








Duo LED Measurement



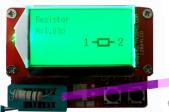10. Resistance measurement resolution is 0.1 ohms, 50M ohms can be measured



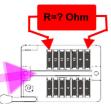

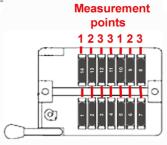





Measurement of a Trimmer or Potentiometer results to display of 2 resistors (depending to the location of the gripoff wiper) and the values of both resistors together display the total value of the trimmer or potentiometer.

Can simultaneously measure two resistors and resistor symbol is displayed. Displayed on the right with a decimal value of 4. Resistance symbol on both side number. So you can measure the potentiometer.

If the potentiometer wiper is not transferred to an extreme position, we can distinguish the middle and both




Measurement of SMD-Resistor at the SMD testing area (see at page 2!)

Measurement of Capacitors (also electrolytic)

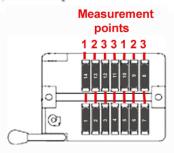Can measure capacitanceCan measure capacitance of 30pF-100mF, resolution 1pF.











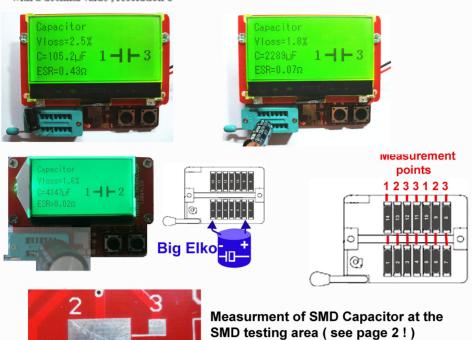2uF more capacitors can simultaneously measure the equivalent series resistance ESR values. The two can be displayed with a decimal value, resolution o




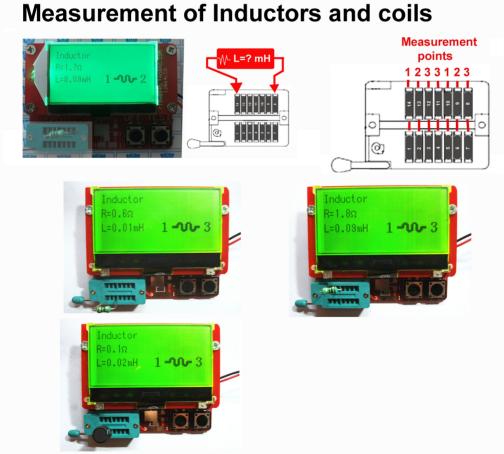


Notice: Before measuring capacitance, the capacitor must be discharged, otherwise very likely damage the meter.

Package Include:

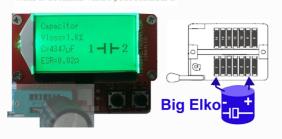 2uF more capacitors can simultaneously measure the equivalent series resistance ESR values. The two can be displayed with a decimal value, resolution o



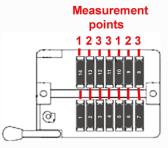

Can be in the correct order and the diode symbol display two diodes , and gives the diode forward voltage.


LED is detected as a diode forward voltage higher. Combo of the LED is identified as two diodes.


Eeverse breakdown voltage is less than 4.5V Zener diode can be identified.

Can measure a single diode reverse capacitance. If the bipolar transistor connected to the base and collector or emitter of a pin , it can measure the collector in punction reverse capacitance .

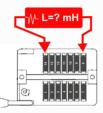can be obtained with a single measurement rectifier bridge connection





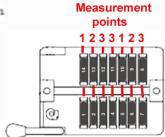


Notice: Before measuring capacitance, the capacitor must be discharged, otherwise very likely damage the meter.

Package Include:

1 x Small 12864 LCD Transistor Tester Capacitance ESR Meter Diode Triode MOS NPN LCR (not include the battery)

Spare drawings for measurement notes

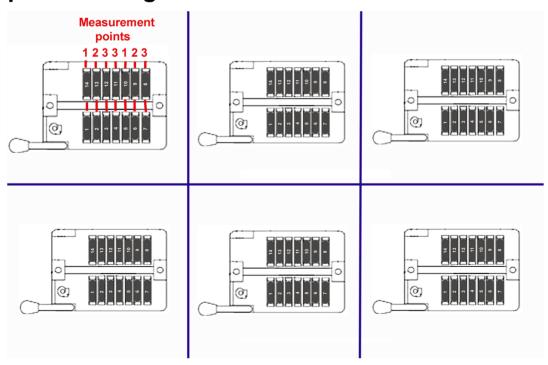

Modifikation des Fish8840



The problem is the high waste of current - even when the module is in "power off mode". The trace below the Diode D5 is the source of the waste.



After the cut and removal of the part of that trace there still is the need to lead the power to the input of the powerregulator.




The resistor divider of R15 and R8 is needed for sensing correct the battery voltage and therefor there must be inputvoltage must be present at this point.




For soldering wire to this point some solder must be pplied carefully.



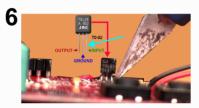Then the bridging a isolated wire can be soldered to the joint at R15.



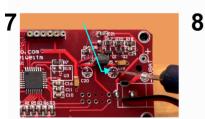The other end must be fixed to the input leg of the power-regulator (right leg).



the best point to fix the second alternate end of wire is the hole of the unpopulated C18 at the positive upper hole.




The violett colored path displays the final path of the bridging wire.



In this picture the red coated isolated wire is in it's fianl location and the Mod is completed.




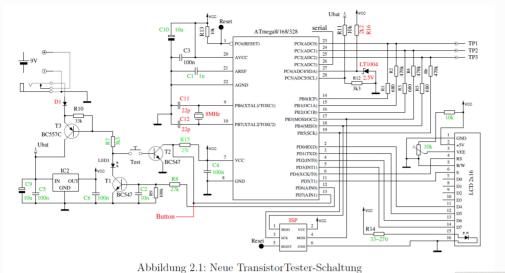10
For Testing purpose checkout after perfomence of the Mod the correct function by testing a resistor. After Bootscreen the battery detection should display correct voltage of the battery and perform correct testing. After this Mod the "turn off mode" of the module should have been dumped from nearly 100mA down to average current of less than 5 mA.









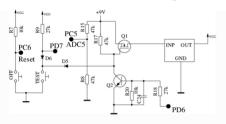


Main PCB

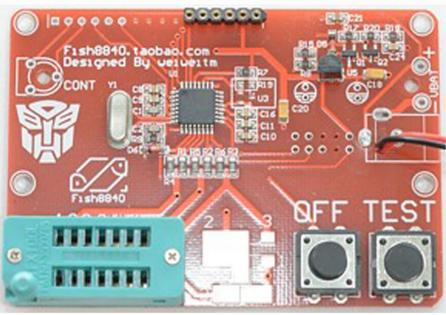



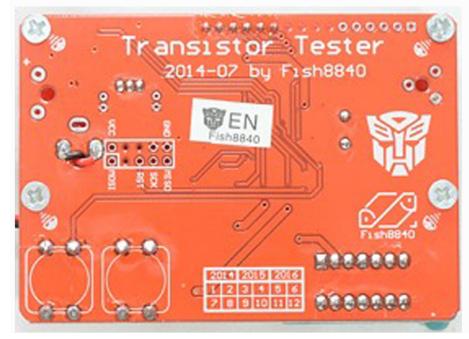

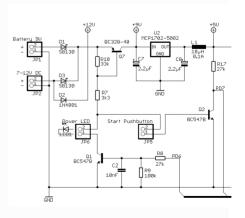

Main PCB solderside