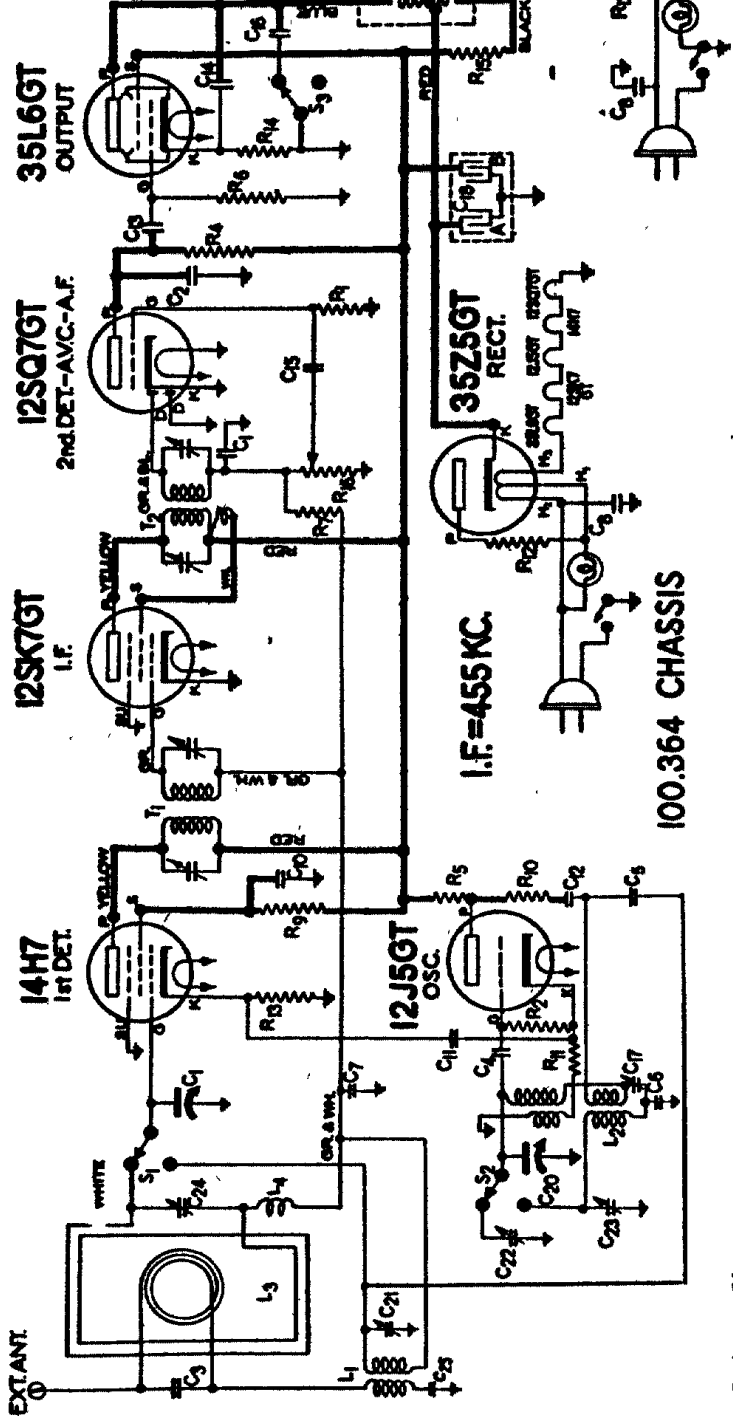


THE PARTIAL SCHEMATIC BELOW PERTAINS TO CHASSIS 100.364-1. OTHERWISE THE CIRCUIT IS SIMILAR TO CH.100.364



SEARS, ROEBUCK & CO.

MODELS 7016, 7031A
Chassis 100.364
Chassis 100.364-1

105-125 V { 50-60 cycle 30 W. (100.364,
105-125 V { 50-60 cycle 42 W. (100.364-1)
ALIGNMENT FREQUENCIES
1400 KC, 600 KC.
14 MC.
..... 455 KC.
LOUD SPEAKER
Type ... (P.M. Dynamic (100.364)
Size ... (Electro Dynamic (100.364-1)
Field Resistance-3600 ohms (100.364-1)

POWER SUPPLY
100.364 & 100.364-1 chassis are supplied for either 25 or 50-60 cycle power supplies.
FREQUENCY RANGES
American 535 to 1735 KC.
Foreign 5.6 to 16.1 MC.
INTERMEDIATE FREQUENCY
POWER OUTPUT
Type Pentode
Undistorted9 Watts
Maximum 1.7 Watts
ELECTRICAL CHANGES IN 100.364 CHASSIS

Part Number	Diagram Number	Description	LIST PRICE
W50039	C1-C2	Condenser-Mica 200 Mfd.	.20
W50783	C3-C4	Condenser-Mica 110 Mfd.	.20
W10510	C-5	Condenser-3 Mfd.	.12
W50597	C-6	Condenser-Mica .0048 Mfd.	.35
W10619	C7-C8	Condenser-.05 Mfd. 600 Volts	.20
W10193	C10-C13	Condenser-.01 Mfd. 600 Volts	.15
W10414	C-14	Condenser-.02 Mfd. 600 Volts	.15
W10817	C-15	Condenser-.004 Mfd. 600 Volts	.15
W10680	C-16	Condenser-.04 Mfd. 600 Volts	.20
W10817	C-16	Condenser-.004 Mfd. 600 Volts	.15
W10834	C-17	Condenser-Polymer (100.364-1 Only)	.35
W500256		Condenser-Electrolytic A-40 Mfd. 150 Volt	1.00
		B-20 Mfd. 150 Volt	
W500744	C-18	(50-60 Cycle Models Only) Condenser-Electrolytic A-80 Mfd. 150 Volt	1.80
		B-20 Mfd. 150 Volt	
W500442	C19-C20	(25 Cycle Models Only) Condenser-Variable tuning with drum	2.60
W500647	C21-C22	Condenser-Trimmer, 5 section	.45
W106345	C24	Condenser-.01 Mfd. 600 Volts	.15
W10193	C25	Condenser-.01 Mfd. 600 Volts	.15
W102976	R1	Resistor-Carbon, 10 Meg. 1/4 Watt	.12
W10582	R2	Resistor-Carbon, 47,000 Ohms 1/4 Watt	.12
W10553	R4	Resistor-Carbon, 220,000 Ohms 1/4 Watt	.12
W10557	R5	Resistor-Carbon, 470,000 Ohms 1/4 Watt	.12
W10559	R6	Resistor-Carbon, 470,000 Ohms 1/4 Watt	.12
W10570	R7	Resistor-Carbon, 2.2 Meg. 1/4 Watt	.12
W10578	R9	Resistor-Carbon, 58,000 Ohms 1/4 Watt	.12
W105690	R10-R11	Resistor-Carbon, 180 Ohms 1/4 Watt	.12
W10752		Resistor-55 Ohms 1 Watt, Wire Wound	.15
W10013	R12	(50-60 Cycle Models Only) Resistor-50 Ohms 1 Watt, Wire Wound	.15
W10079	R13	(25 Cycle Models Only) Resistor-Insulated, 1200 Ohms 1/4 Watt	.12

The 100.364 chassis as first produced used a P.M. dynamic speaker and a 6 volt pilot light. Later versions use an electro-dynamic speaker whose field is connected across the B supply in order to obtain the required excitation. These later models, which are identified by 100.364-1, also use a 110 volt pilot light. The later models have the tone control connected in the 12SQ7 plate instead of the 35L6GT plate as in the earlier models.
W50046 L1 Coil-Short Wave Antenna80
W50046 L2 Coil-Oscillator (S.C. & S.N.) 1.00
W50046 L3 Loop Antenna & Cabinet Back for Plastic Cabinets 1.70
W50051 L4 Loop Antenna & Cabinet Back for Wood Cabinets 2.00
W50051 L4 Leading Coil25